
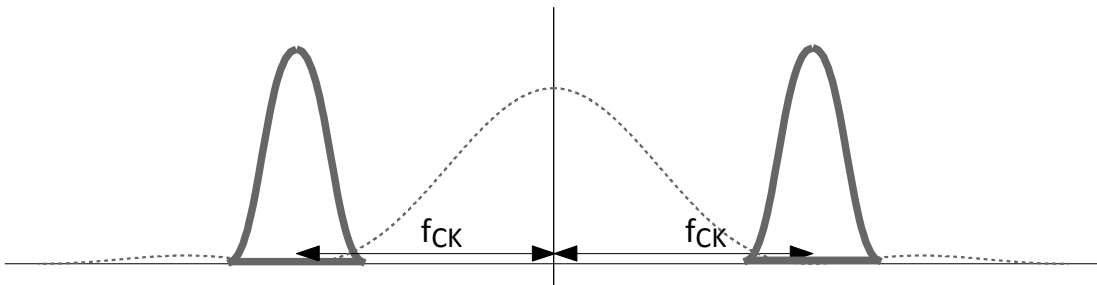


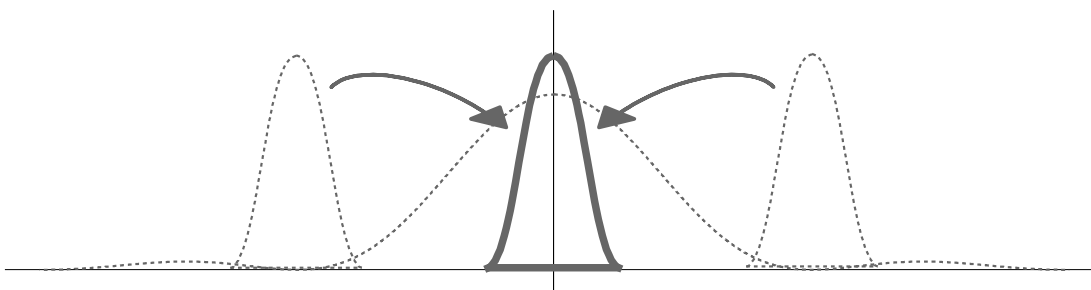
Signal spectrum (random bits)
 (there is no energy at the clock frequency, whatever the bit pattern)




Non-linear processing can retrieve the embedded clock
 (which is not a pure line, but a spread out (=jittered) signal)



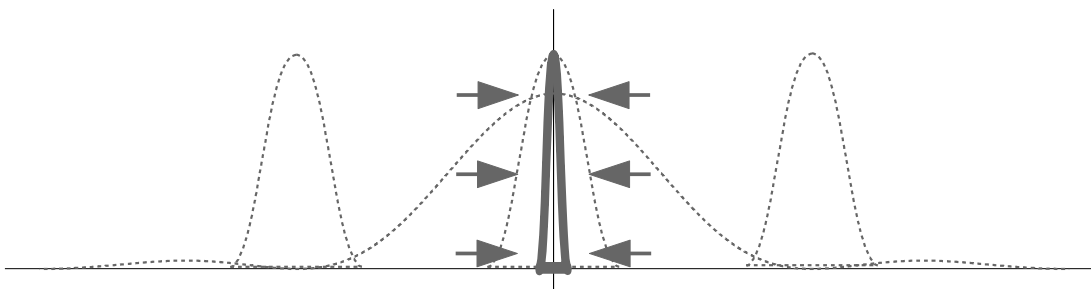The phase comparator extracts the clock jitter and shifts it to d.c.
 (Clock jitter = VCO clock - RX embedded clock)



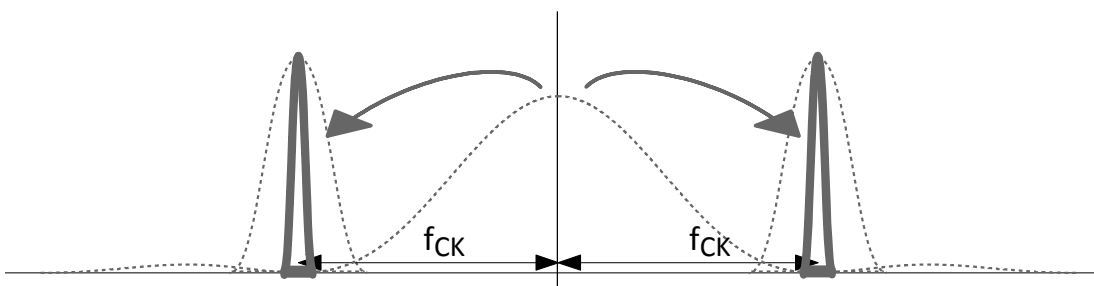The PLL filter block is a lag corrector and rejects most of the high frequency jitter
 (its output signal is then fed as a FM modulating signal to the VCO)



The VCO is frequency modulated by output of the loop filter
 (As the modulation is a relatively low index FM, its spectrum around f_{CK} is almost the same)