

CMOS Transistor Switching

Copyright (c) 2011-2013 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".

Please send corrections (or suggestions) to youngwlim@hotmail.com.

This document was produced by using OpenOffice and Octave.

Simple Transistor Model (1)

Cutoff, subthreshold, or weak-inversion mode

When $V_{GS} < V_t$:

$$I_d = 0$$

Triode mode or linear region (the ohmic mode)




When $V_{GS} > V_t$ and $V_{DS} < (V_{GS} - V_t)$

$$I_d = k' \frac{W}{L} \left[(v_{gs} - v_t) v_{ds} - \frac{1}{2} v_{ds}^2 \right]$$

Saturation or active mode



When $V_{GS} > V_t$ and $V_{DS} \geq (V_{GS} - V_t)$
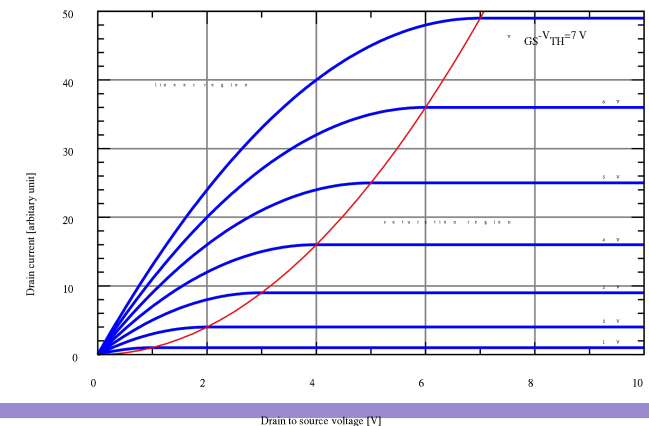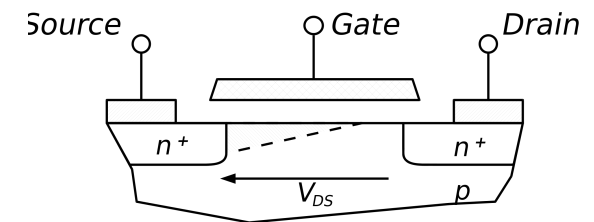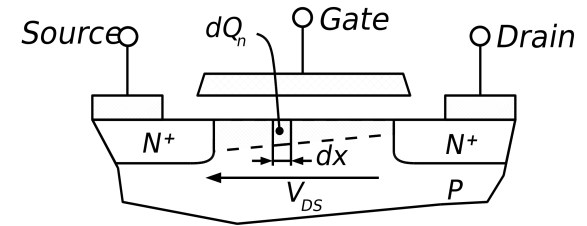
$$I_d = \frac{1}{2} k' \frac{W}{L} (v_{gs} - v_t)^2$$




Characteristic Curve

Notation

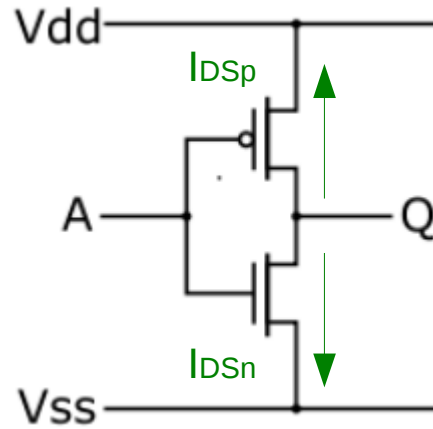
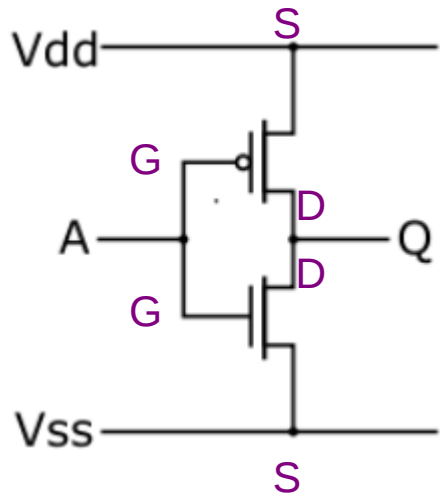


Current
Notation

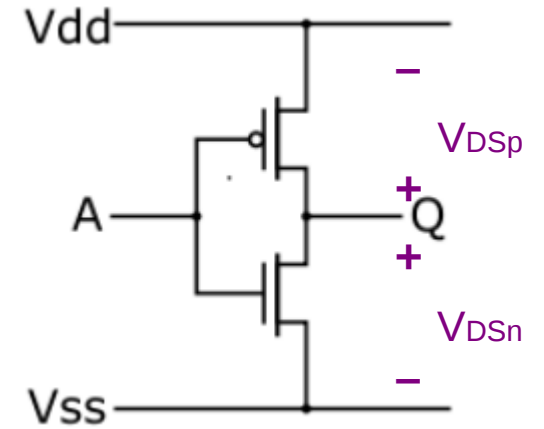


Voltage
Notation

Output Voltage

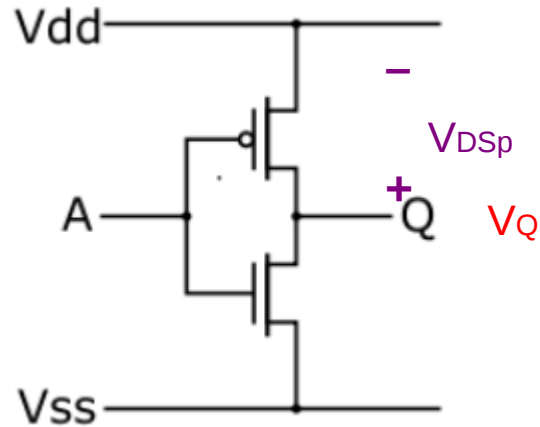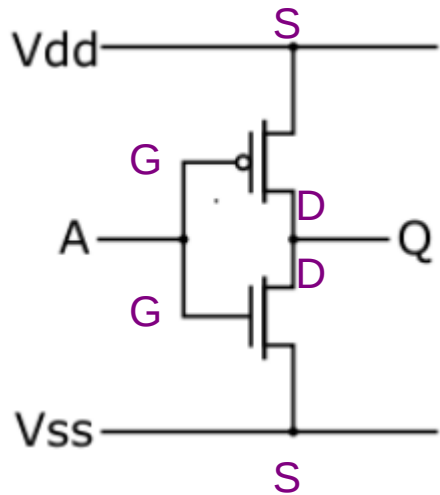

Voltage
Notation

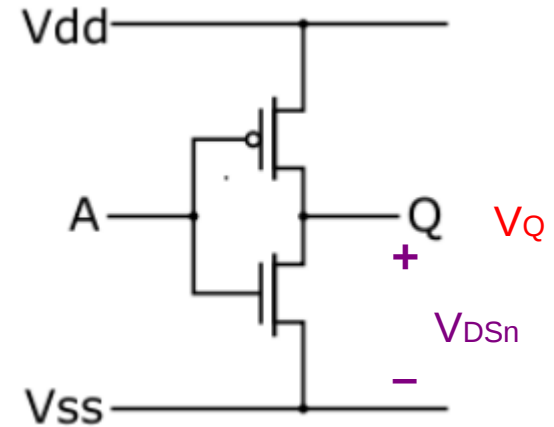
$$\begin{aligned} V_Q &= V_{DS_p} + V_S \\ &= V_{DS_p} + V_{dd} \end{aligned}$$




Voltage
Notation

$$\begin{aligned} V_Q &= V_{DS_n} + V_S \\ &= V_{DS_n} + V_{ss} \end{aligned}$$



Characteristic Curves (1)

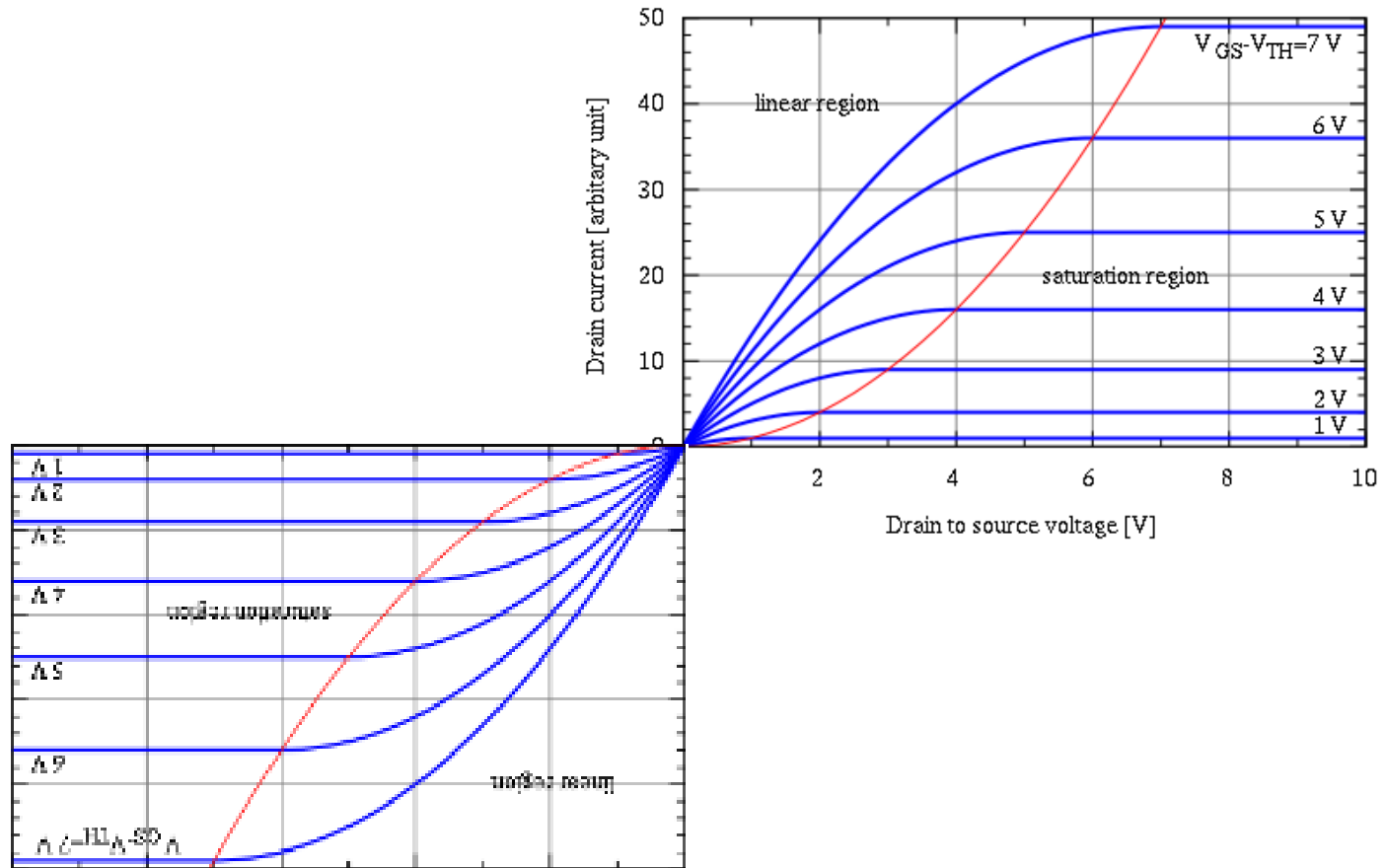





Characteristic Curves (2)

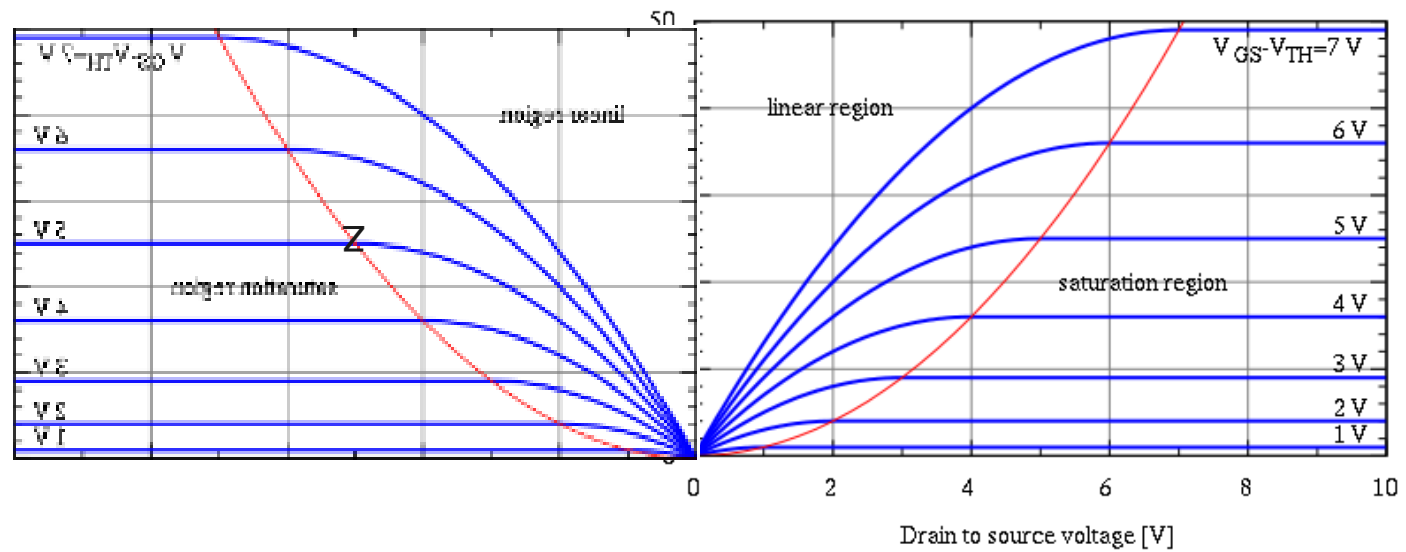





Voltage Transfer Curve (1)

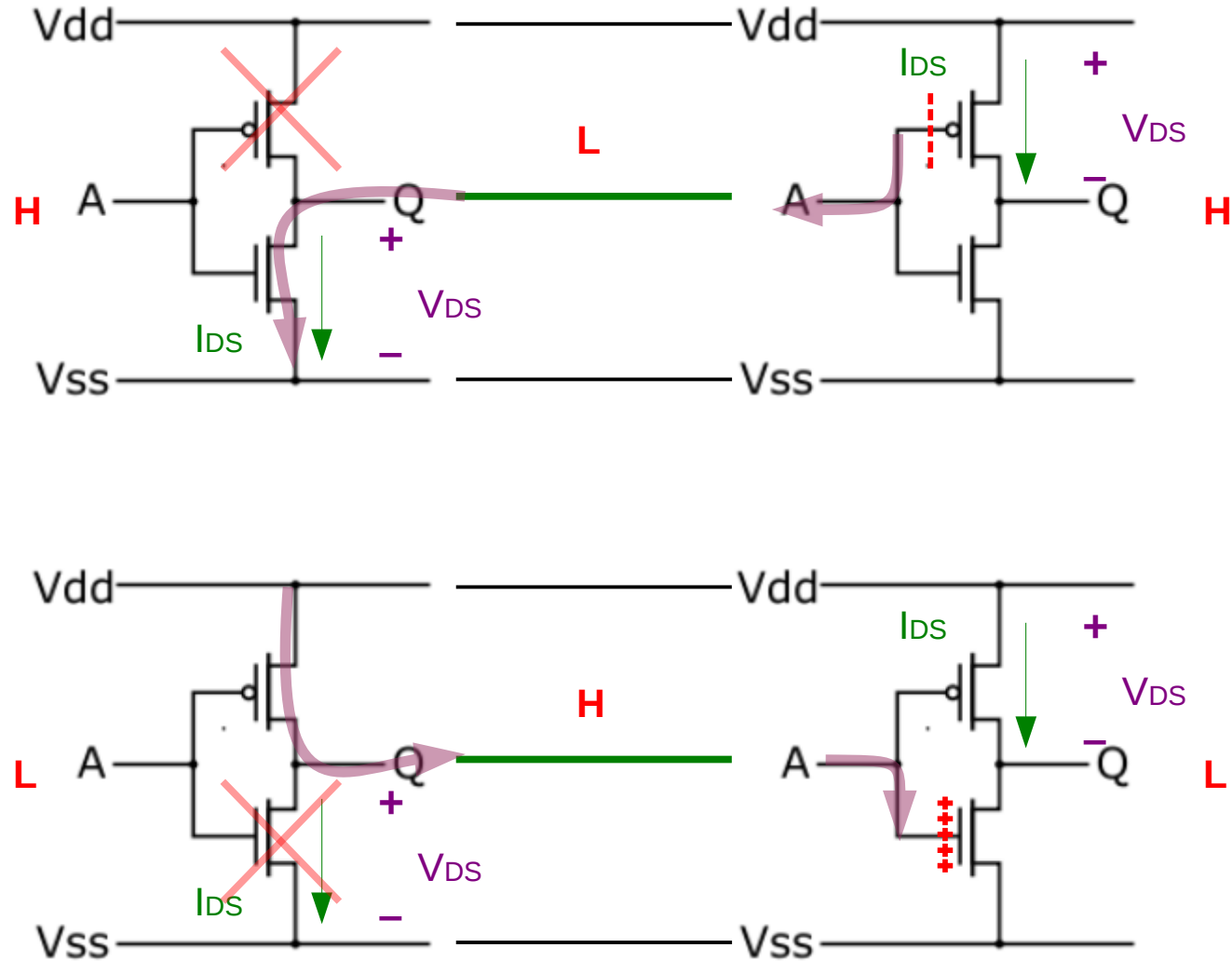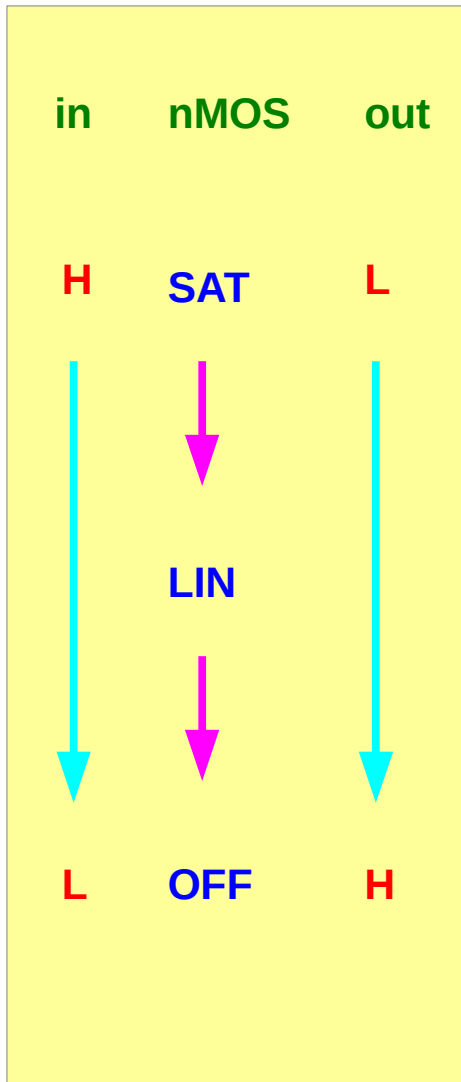

Voltage Transfer Curve (2)

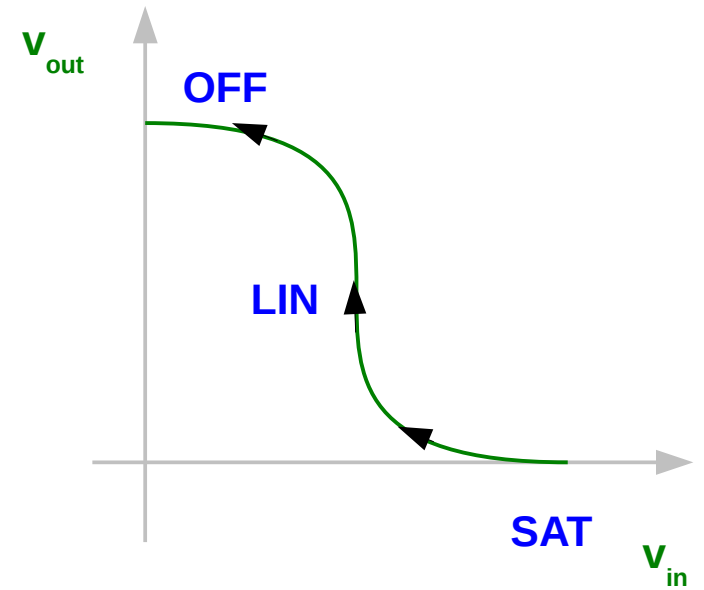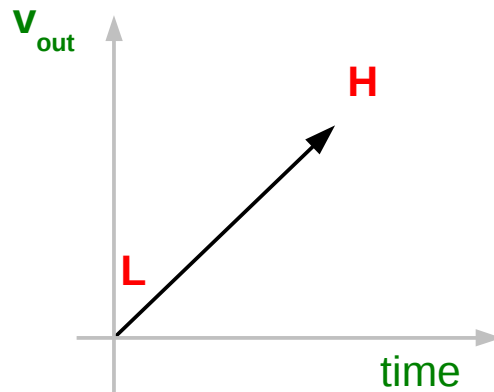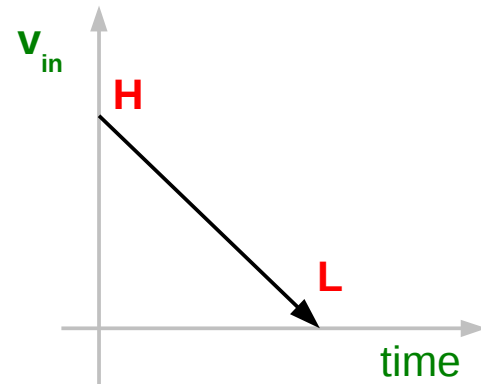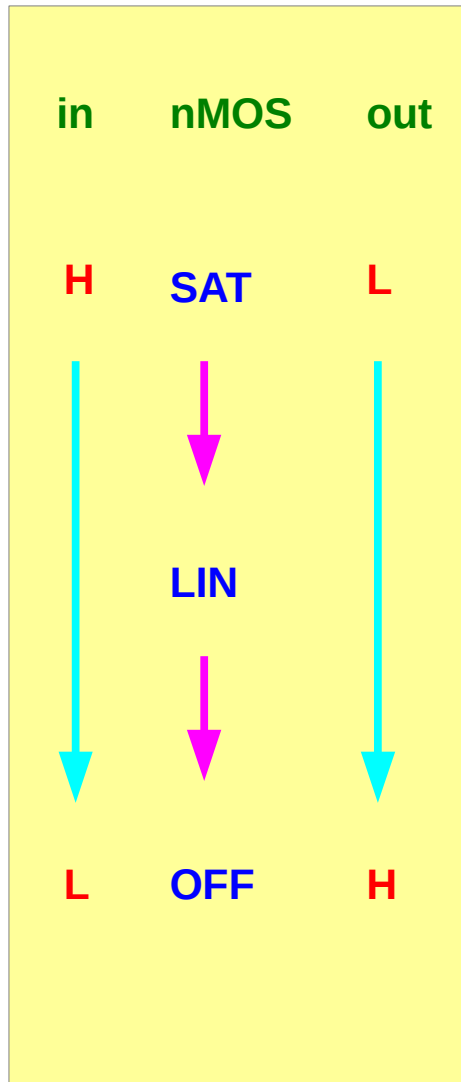

Voltage Transfer Curve (2)

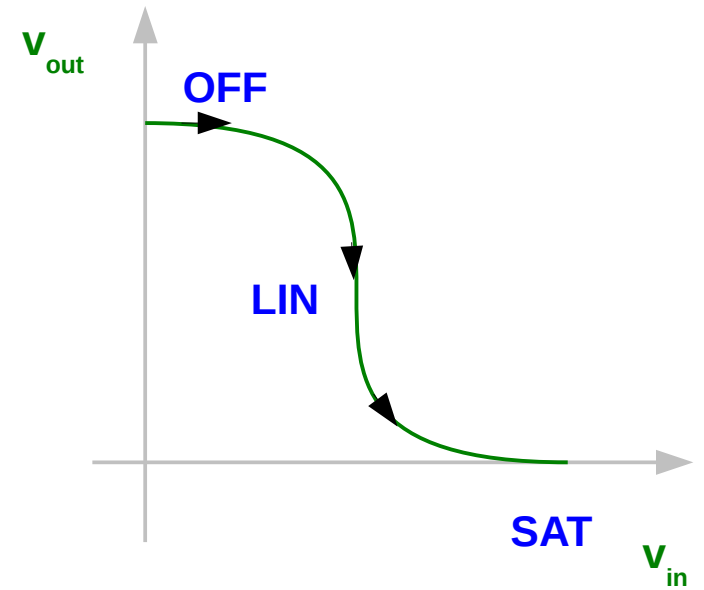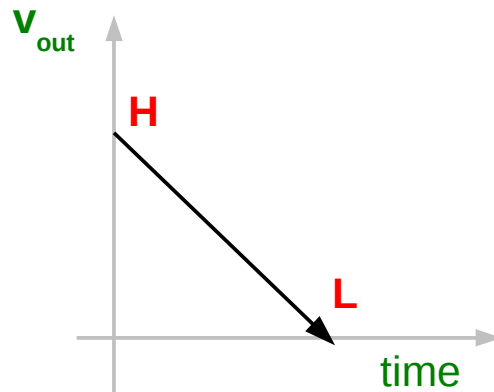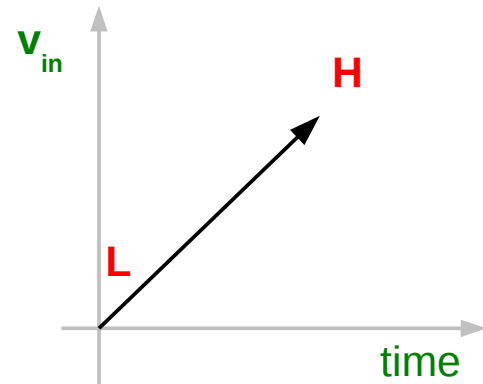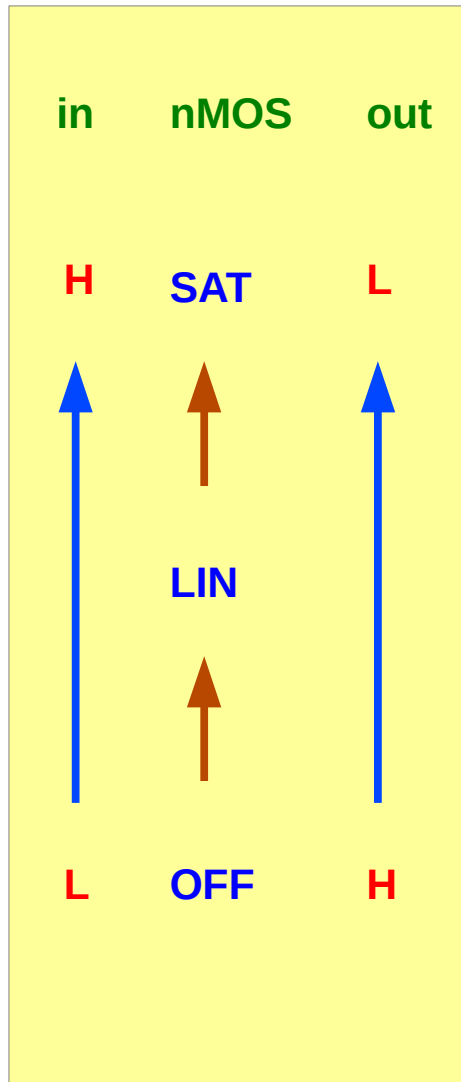

References

- [1] <http://en.wikipedia.org/>
- [2] <http://www.allaboutcircuits.com/>
- [3] W. Wolf, "Modern VLSI Design : Systems on Silicon"
- [4] N. Weste, D. Harris, "CMOS VLSI Design: A Circuits and Systems Perspective"