

CMOS Transistor Sizing (3G)

Noise Margin

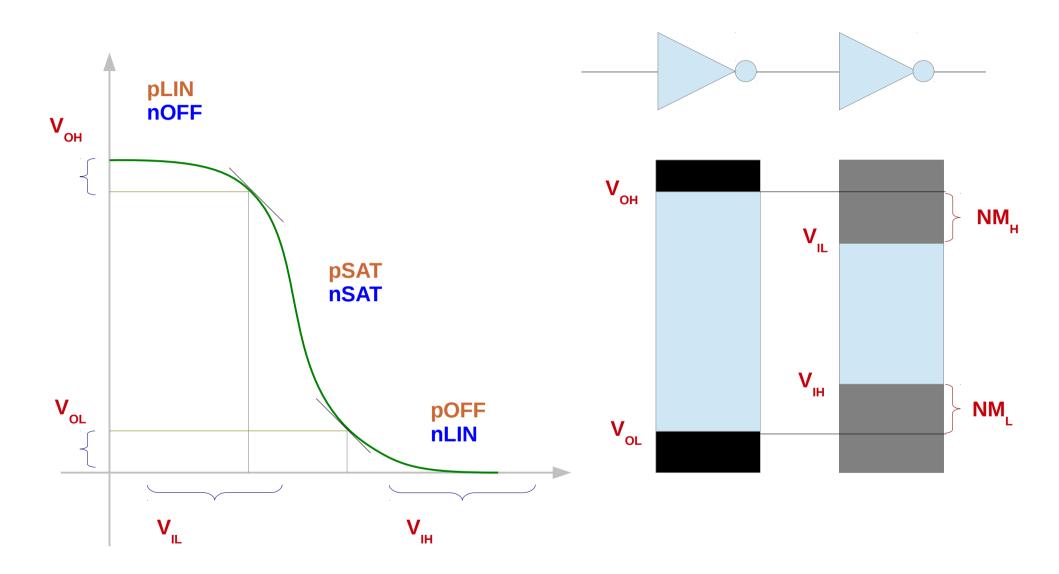

Transconductance Parameter (1)

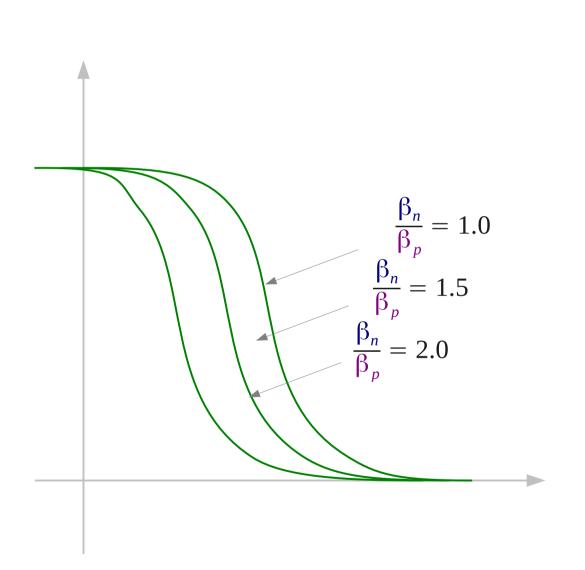

When
$$V_{GS} > V_{t}$$
 and $V_{DS} < (V_{GS} - V_{t})$

$$I_d = \frac{k' \frac{W}{L}}{L} \left[(v_{gs} - v_t) v_{ds} - \frac{1}{2} v_{ds}^2 \right]$$


When
$$V_{GS} > V_{t}$$
 and $V_{DS} \ge (V_{GS} - V_{t})$


$$I_d = \frac{1}{2} \frac{k' \frac{W}{L}}{L} (v_{gs} - v_t)^2$$

$$\beta_{p} = k'_{p} \left(\frac{W}{L}\right)_{p}$$

$$\beta_{n} = k'_{n} \left(\frac{W}{L}\right)_{n}$$

Transconductance Parameter (2)

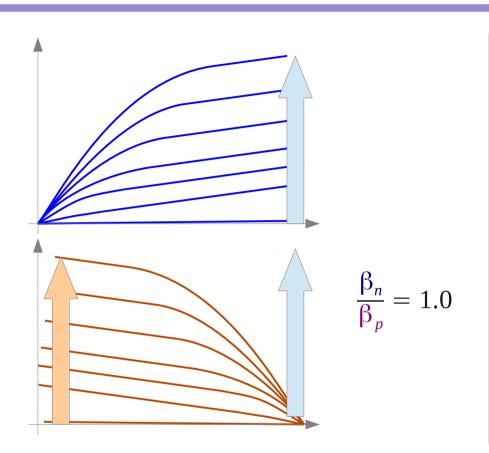

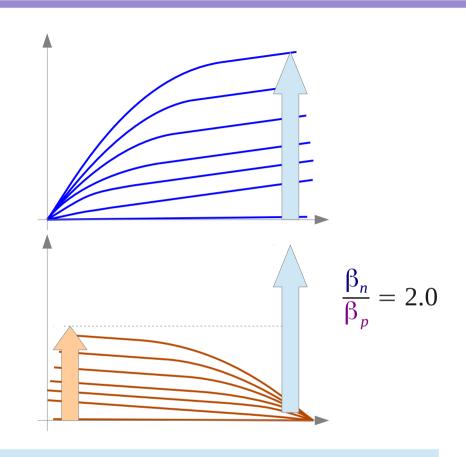


When $V_{GS} > V_{t}$ and $V_{DS} < (V_{GS} - V_{t})$

$$I_d = \left[\beta \left[(v_{gs} - v_t) v_{ds} - \frac{1}{2} v_{ds}^2 \right] \right]$$


When $V_{GS} > V_{t}$ and $V_{DS} \ge (V_{GS} - V_{t})$


$$I_d = \frac{1}{2} \beta \left(v_{gs} - v_t \right)^2$$


Transconductance Parameter (3)

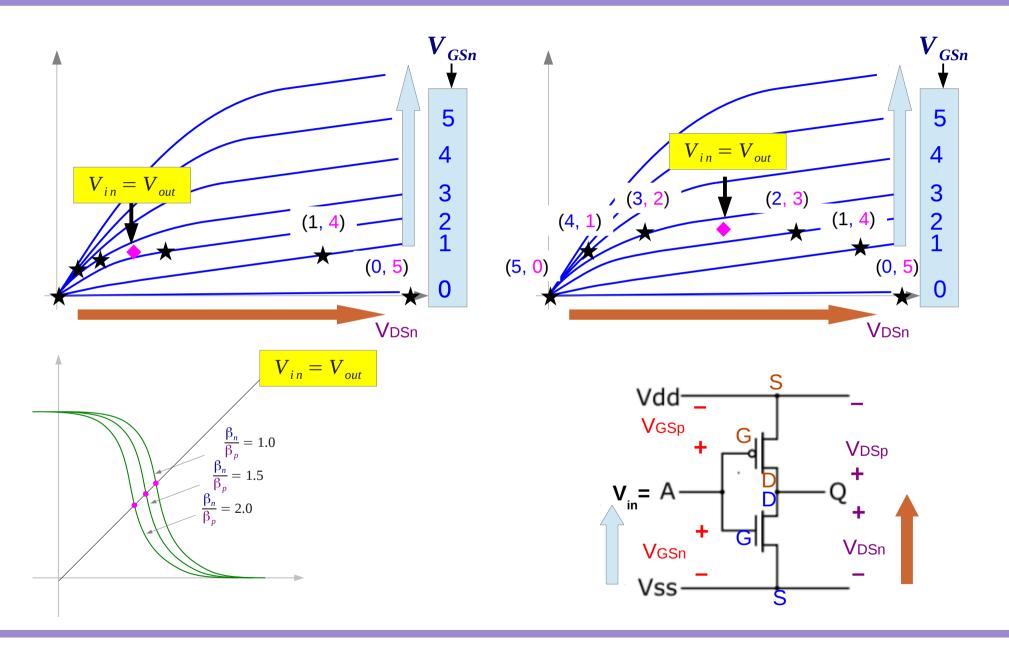


Rising and Falling Time (1)

 


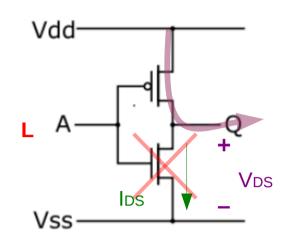


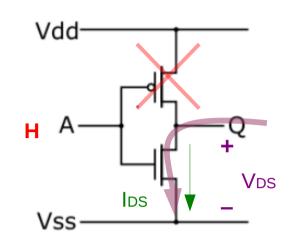

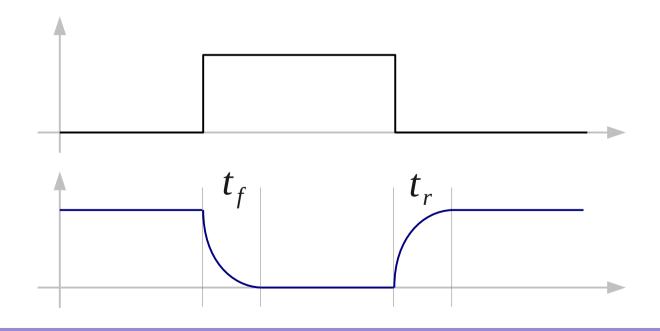

Rising and Falling Time (2)

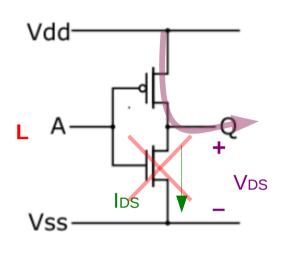

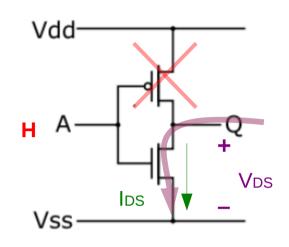

$$\frac{\beta_n}{\beta_p} = 1.0$$


$$R_n = R_p$$

$$\frac{\beta_n}{\beta_p} = 2.0$$

$$R_n < R_p$$


Rise Time

$$t_r = R_p C_L$$

 



Fall Time


$$t_f = R_n C_L$$

 


Propagation Delay

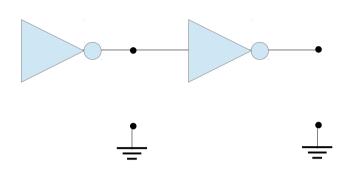


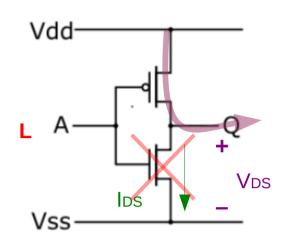

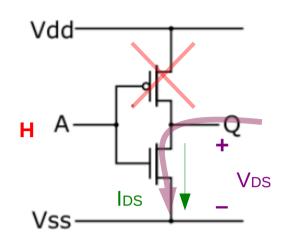

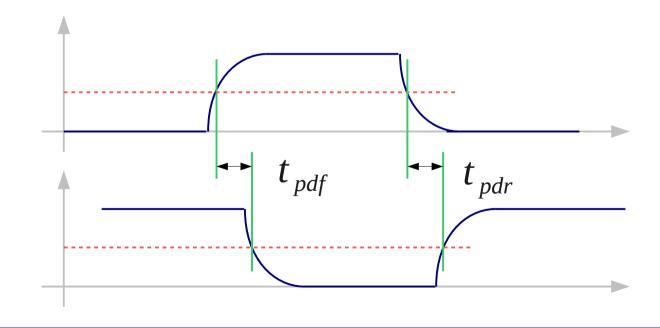

Load Capacitance

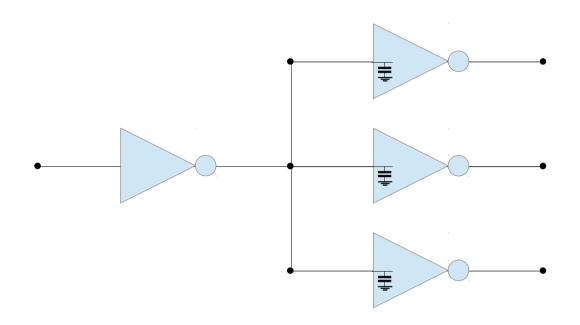

$$C_{in} = 3C_g$$

Big Capacitance

- A signal connected off-chip
- A signal with very long wire
- A clock signal driving many flip-flops

Characteristic Curve

References

- [1] http://en.wikipedia.org/
- [2] http://www.allaboutcircuits.com/
- [3] W. Wolf, "Modern VLSI Design: Systems on Silicon
- [4] N. Weste, D. Harris, "CMOS VLSI Design: A Circuits and Systems Perspective"
- [5] J. P. Uyemura, "Introduction to VLSI Circuits and Systems"