

Sequential Gates


Copyright (c) 2011-2013 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".



Please send corrections (or suggestions) to youngwlim@hotmail.com.

This document was produced by using OpenOffice and Octave.


D Latch with Mux (1)

 



D Latch with Mux (2)

  


D Latch with Pass Gate (1)

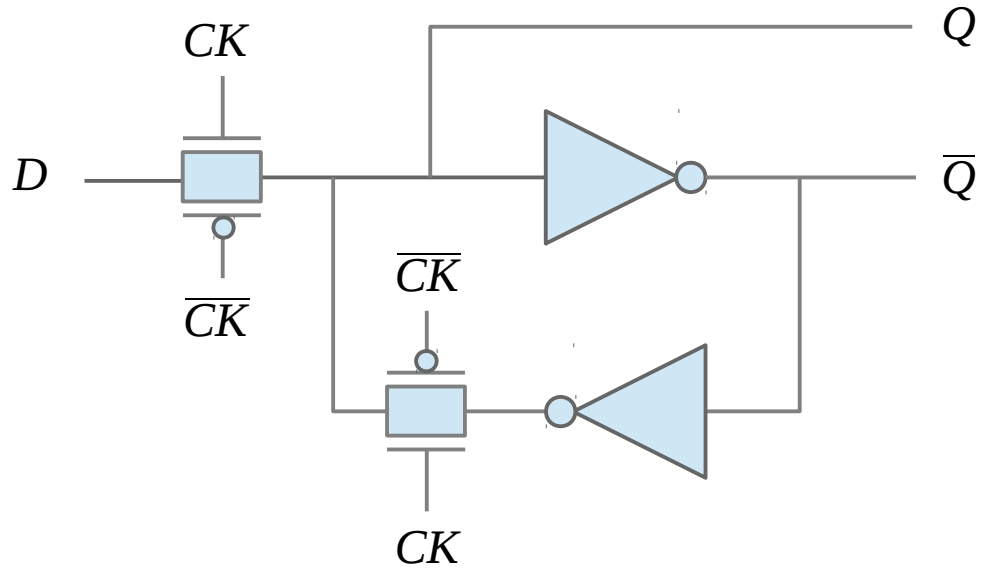


D Latch with Pass Gate (2)

  

D Flip Flop with Pass Gate (1)

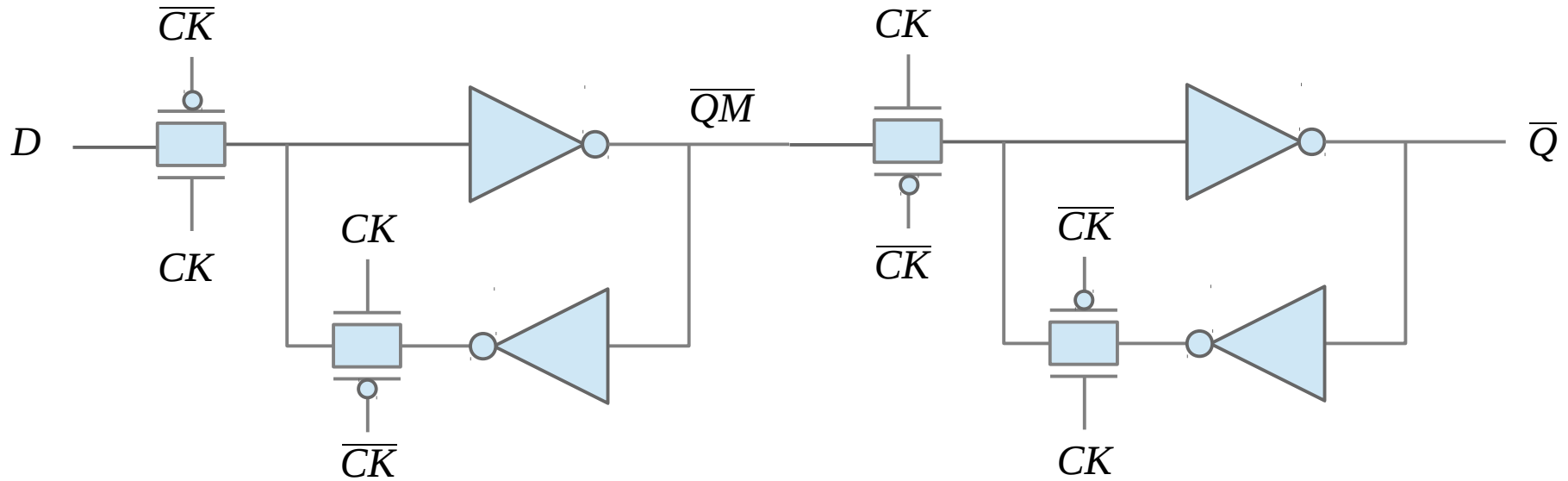

D Flip Flop with Pass Gate (2)

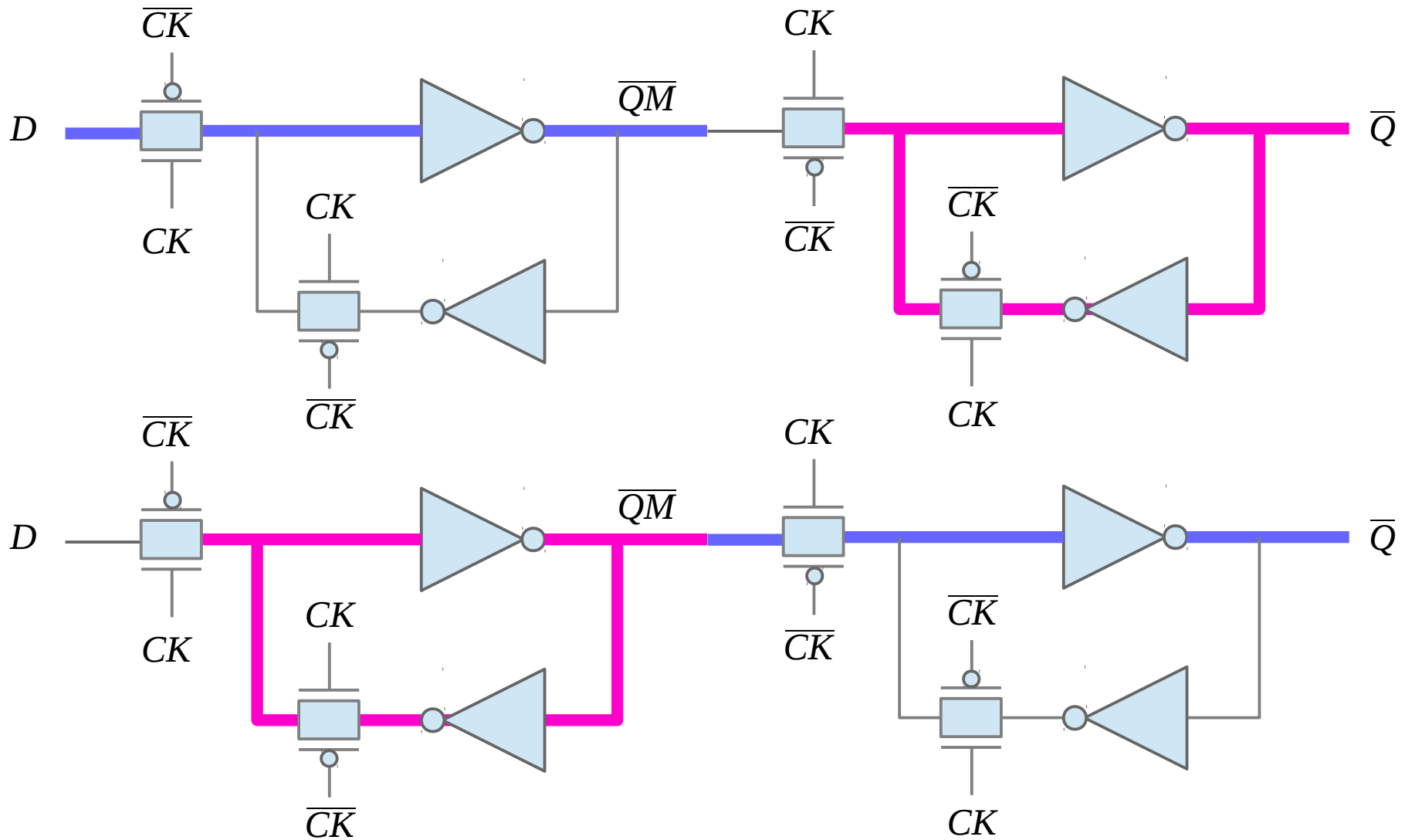

Sequential Element Types

- CMOS Latches
- CMOS FlipFlops
- Pulsed Latches
- Latches and FlipFlops with a Reset
- Latches and FlipFlops with an Enable

References

- [1] <http://en.wikipedia.org/>
- [2] <http://www.allaboutcircuits.com/>
- [3] W. Wolf, "Modern VLSI Design : Systems on Silicon"
- [4] N. Weste, D. Harris, "CMOS VLSI Design: A Circuits and Systems Perspective"
- [5] J. P. Uyemura, "Introduction to VLSI Circuits and Systems"