

Variable Block Adder (1A)

-
-

Copyright (c) 2022 - 2010 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".

Please send corrections (or suggestions) to youngwlim@hotmail.com.

This document was produced by using OpenOffice and Octave.

Carry Skip Adder

The maximal delay Δ of a Carry Skip Adder is encountered when **carry** is generated in the **least-significant bit** position,

- rippling through $k-1$ bit positions,
- skipping over $R-2 = N/k-2$ groups in the middle,
- rippling to the $k-1$ bits of most significant group and
- being assimilated in the N -th bit position to produce the sum S_N :

$$\begin{aligned}\Delta_{\text{CSA}} &= (k - 1) \Delta_{\text{rca}} + (R - 2) \Delta_{\text{SKIP}} + (k - 1) \Delta_{\text{rca}} \\ &= 2 (k - 1) \Delta_{\text{rca}} + (R - 2) \Delta_{\text{SKIP}} \\ &= 2 (k - 1) \Delta_{\text{rca}} + (N/k - 2) \Delta_{\text{SKIP}}\end{aligned}$$

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers


Carry Skip Adder

$$\begin{aligned}\Delta_{CSA} &= (k - 1) \Delta_{rca} + (R - 2) \Delta_{SKIP} + (k - 1) \Delta_{rca} \\ &= 2(k - 1) \Delta_{rca} + (R - 2) \Delta_{SKIP} \\ &= 2(k - 1) \Delta_{rca} + (N/k - 2) \Delta_{SKIP}\end{aligned}$$

Carry Skip Adder is faster than RCA at the expense of a few relatively simple modifications.

The delay is still linearly dependent on the size of the adder N , however this linear dependence is reduced by a factor of $1/k$

$$N = R \cdot k$$

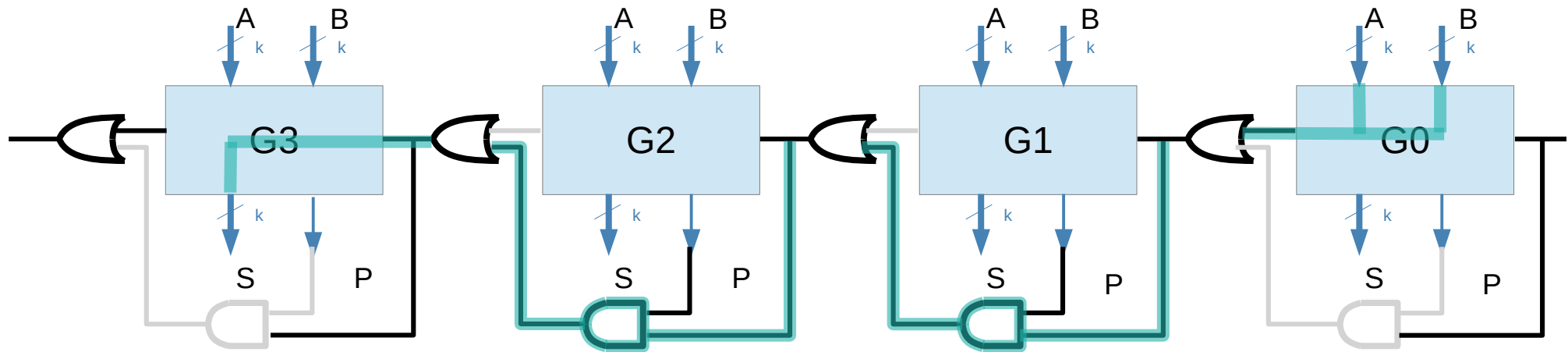

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

Variable Block



however, unlike the **carry select** structure, the **variable block** adder must also worry about the delay from the **Cin** input through the block's **ripple chain**

Thus, after the carry chain passes the midpoint of the logic, the blocks begin decreasing in length.


This balances the path delays in the system and improves performance

The division of the overall structure into blocks depends on the details of the logic structure and the length of the entire computation


 
 
https://en.wikipedia.org/wiki/Carry-lookahead_adder



Carry Skip Adder

 

   
$$P = p_i \cdot p_{i+1} \cdot p_{i+2} \cdot \dots \cdot p_{i+k-1}$$



Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers


Carry Skip Adder

 

Delay d_1 from A, B to P – parallel, the same delay in each group —


Delay d_2 from A, B to C – serial, the accumulated delay from $1sb$ —

 Delay d_3 from A, B, C_i to C_o – ripple carry delay —




Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

Carry Skip Adder

 


 Delay d_3 from A, B, C_i to C_o – ripple carry delay



Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers


Carry Skip Adder

 

$$N = R \cdot k$$

$$d1 \propto k$$
 
$$d2 \propto R \left(= \frac{N}{k} \right)$$





Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

Carry Skip Adder

$$N = R \cdot k$$

$$d1 \propto k$$
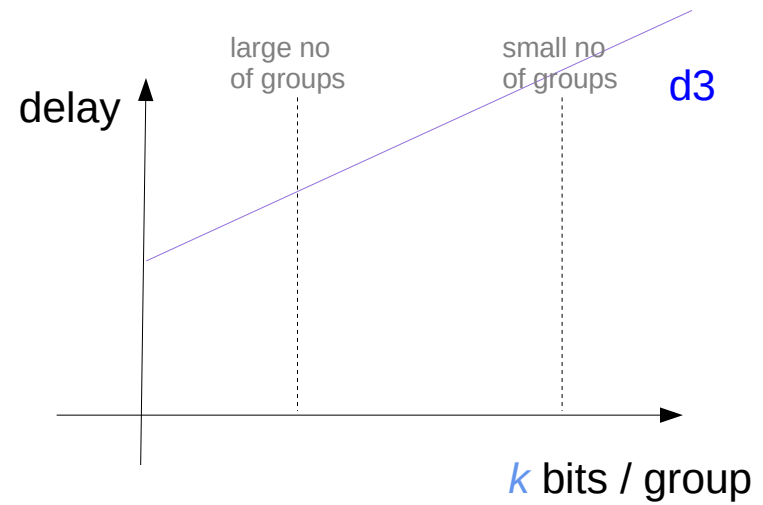 
$$d2 \propto R \left(= \frac{N}{k} \right)$$



Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

Variable Block




the organization of the blocks in the **variable block carry** structure bears some similarity to the **carry select** structure

the early stages of the structure grow in length,
with short blocks for the low order bits,
building in length further in the chain
in order to equalize the arrival time
of the carry from the block
with that of the previous block

https://en.wikipedia.org/wiki/Carry-lookahead_adder




Carry Skip Adder

   to equalize the arrival time of the carry from the block with that of the previous block




Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

Carry Skip Adder

   


Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

Carry Skip Adder

 




Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

Carry Skip Adder

 

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

Carry Skip Adder

   

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers


Carry Skip Adder

All carries propagated more quickly by varying the block sizes
Accordingly the initial blocks of the adder are made smaller, so as to quickly detect carry generates that must be propagated

The middle blocks are made larger because they are not the problem case,

And then the most significant blocks are made smaller so that the late arriving carry inputs can be processed quickly

 https://en.wikipedia.org/wiki/Carry-skip_adder



Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers



Carry Skip Adder

The longest path length through the **carry skip block** is potentially much shorter than the path from carry-in to carry-out through a **ripple carry block**.

However, the carry skip block has a slightly longer path from the least significant $\langle g, t \rangle$ input to carry output

Hence, this adder will only be faster when skipping groups makes up for the **extra gate overhead** accumulated by going from generate/transfer to carry-out

  The maximum path length through a one block wide carry skip adder is the same as though a ripple carry adder, since the bottom block in a skip adder is a ripple carry



Binary Adders, T W Lynch, Master Thesis, University of Texas at Austin 1996

Two separate ripple carry adders


Cin signal is used to determine which adder's outputs should be used

if the **Cin** signal is **true**, the output (carries) are selected from the **true-Cin-adder**


if the **Cin** signal is **false**, the output (carries) are selected from the **false-Cin-adder**

redundant hardware removes **Cin** data dependency

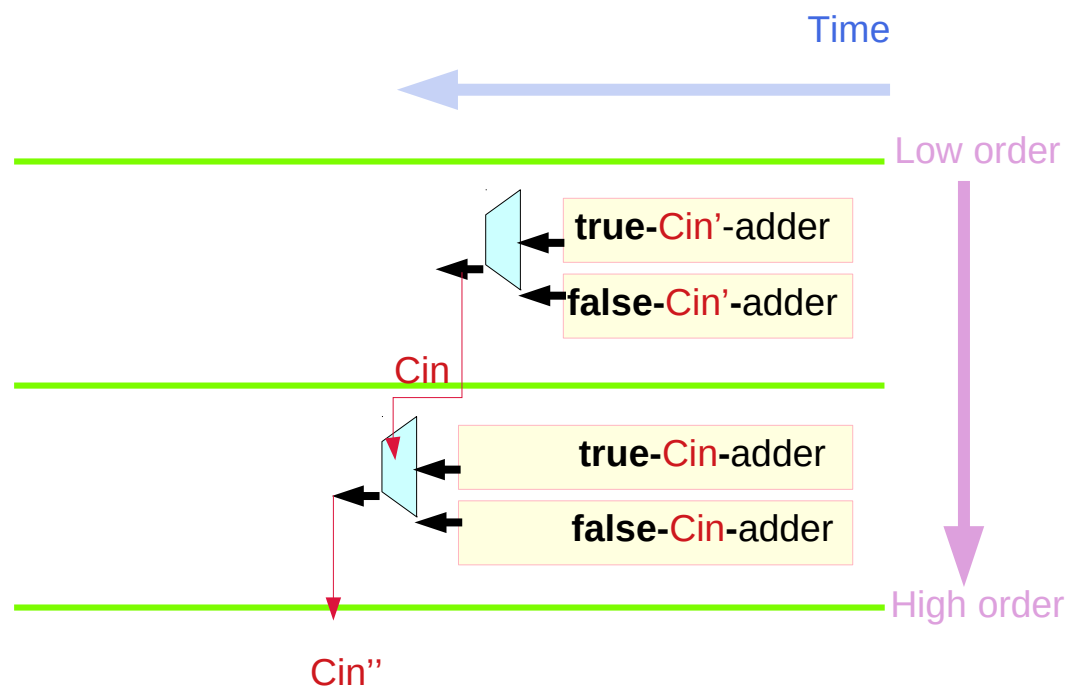first start redundant computation
later select the correct one



Timing in broken carry chains

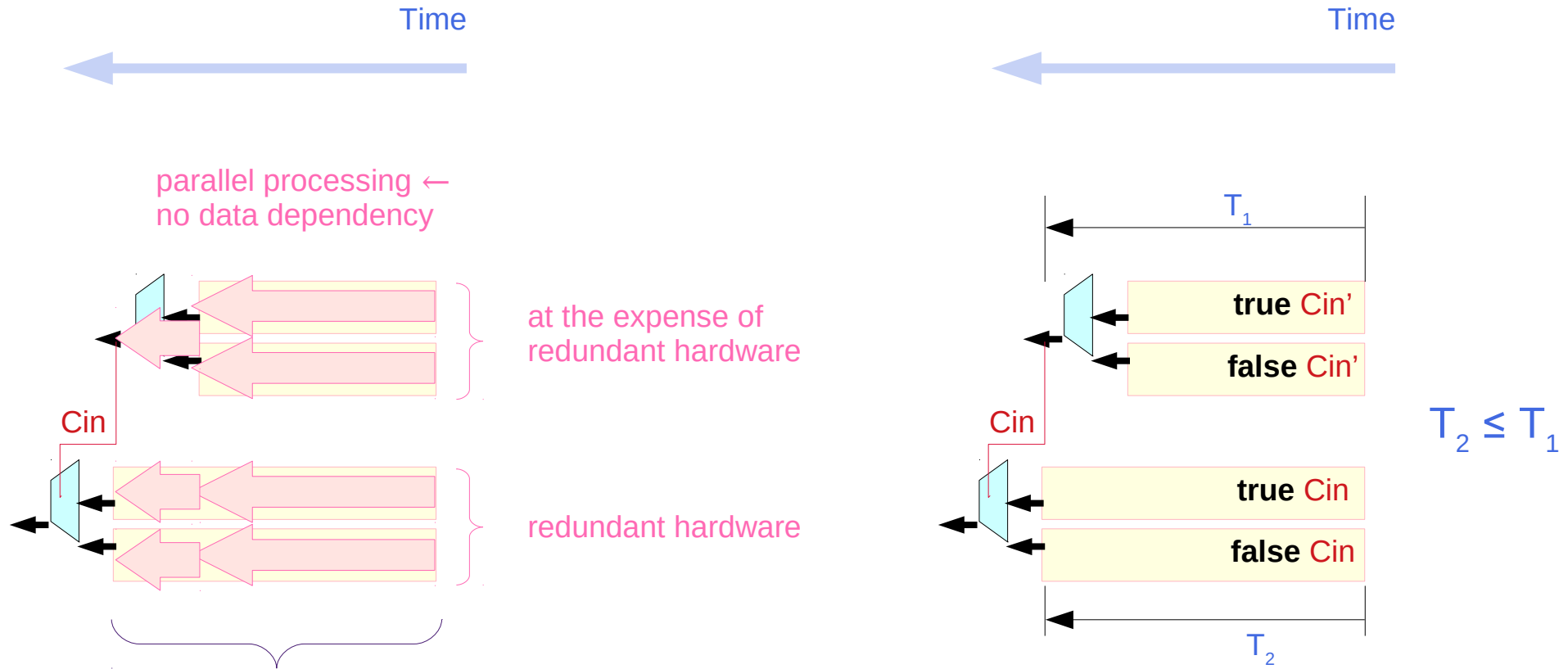


These computations can take place before the completion of the **previous columns**, since they do not depend on the actual value of the Cin signal

the length of the adders and the breakpoint are carefully chosen such that the **adders** finish computations just as their Cin become available


High Performance Carry Chains for FPGAs, S. Hauck, M. M. Hosler, T. W. Fry

Carry Select Fast Carry Logic

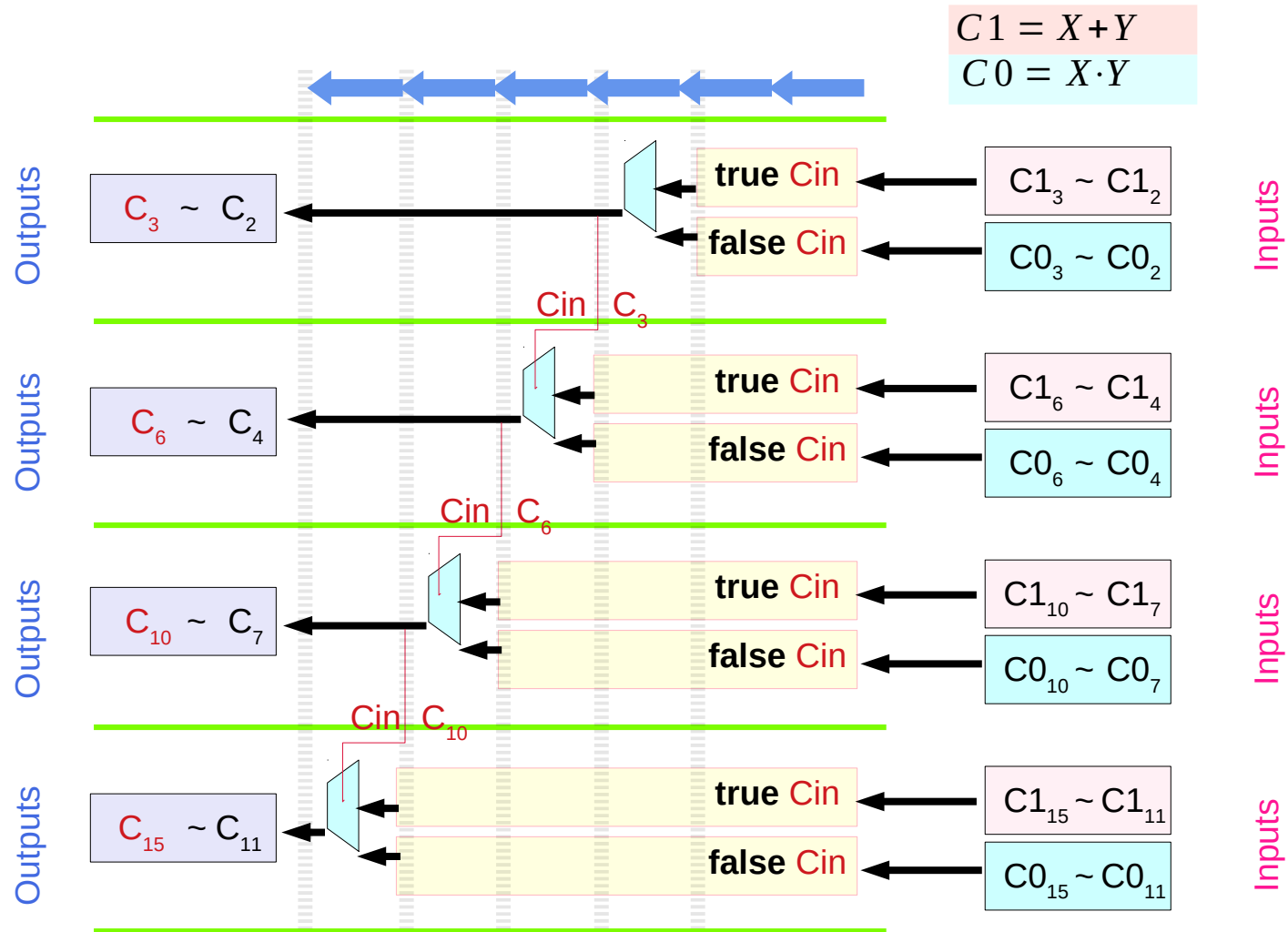

High Performance Carry Chains for FPGAs, S. Hauck, M. M. Hosler, T. W. Fry

Variable Block

 
$d1 > d2$  $d1 < d2$

$d1 < d2$


decreasing length

Increasing length

short blocks for the low order bits

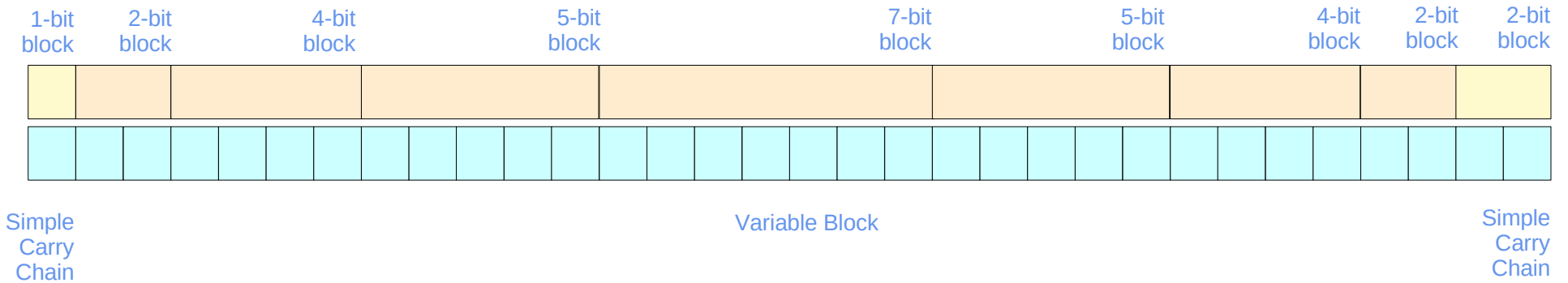

 the delay from the **Cin** input through the block's **ripple chain**




https://en.wikipedia.org/wiki/Carry-lookahead_adder

Variable Block

We use a block length from low order to high order cells of 2, 2, 4, 5, 7, 5, 4, 2, 1 for a normal 32 bit structure

8+17+7

 The first and last block in each adder is a simple ripple carry chain, while all other blocks use the variable block structure.



https://en.wikipedia.org/wiki/Carry-lookahead_adder

Variable Block

Delay values of the variable block carry chain relative to other carry chains

The idea behind **Variable Block Adder** (VBA) is to minimize the longest critical path in the carry chain of a **Carry Skip Adder**, while allowing the groups to take different sizes.

Such an optimization in general does not result in an increased complexity as compared to the Carry Skip Adder

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

Variable Block

The first and last blocks are smaller,
and the intermediate blocks are larger.

That compensates for the critical paths originating
from the ends by shortening the length of the path
used for the carry signal to ripple in the end groups,
allowing carry to skip over larger groups in the middle.

There are two important consequences of this optimization:

- (a) the total delay is reduced as compared to a **Carry Skip Adder**
- (b) the delay dependency is not a linear function
of the adder size N as in a **Carry Skip Adder**.

This dependency follows a square root function of N instead

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

Variable Block

For an optimized VBA, it is possible to obtain a closed form solution expressing this delay dependency

It is also possible to extend this approach to **multi-levels** of carry skip as done in a determination of the optimal sizes of the blocks on the first and higher levels of skip blocks is a **linear programming problem**, which does not yield a closed form solution.

Such types of problems are solved with the use of **dynamic programming** techniques.

The speed of such a **mult-level** VBA adder surpasses **single-level** VBA and that of fixed group Carry-Lookahead Adder (CLA).

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

Variable Block

For an optimized **VBA**, it is possible to obtain a closed form solution expressing this delay dependency which is given as:

where: c_1 , c_2 , c_3 are constants.

$$\Delta_{VBA} = c_1 + \sqrt{c_2 N + c_3}$$

It is also possible to extend this approach to **multiple levels** of carry skip as done.

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

Variable Block

- (1) the speed of the logic gates used for CMOS implementation depends on the output load: **fan-out**, as well as the number of inputs: **fan-in**.
- (2) CLA implementation is characterized with a large fan-in which limits the available size of the groups.

On the other hand **VBA** implementation is simple.

Thus, it seems that **CLA** has passed the point of diminishing returns as far as an efficient implementation is concerned.

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

Variable Block

This example also points to the importance of **modeling** and incorporating appropriate **technology parameters** into the algorithm.

Most of the computer arithmetic algorithms developed in the past use a simple **constant gate delay model**.

(2.) a fixed-group CLA is not the best way to build an adder.

It is a **sub-optimal** structure which after being optimized for speed, consists of groups that are different in size yielding a largely **irregular** structure

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

Variable Block

There are other advantages of VBA adder that are direct result of its **simplicity** and **efficient** optimization of the critical path.

Those advantages are exhibited in the **lower area** and **power consumption** while retaining its speed.

Thus, VBA has the **lowest energy-delay product** as compared to the other adders in its class.

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

Delay model

Oklobdzija addition VLSI

On implementing addition in VLSI technology

Delay dependency : Fan-out, Fan-in,

Delay estimates :

$$D_NAND = 1 + 0.3F_o + 0.5(F_i - 2)$$

$$D_NOR = 1 + 0.5F_o + 0.5(F_i - 2)$$

$$D_NAND = 0.7 + 0.3F_o$$

t denote the time required for a carry signal to ripple across a bit

T denote the time required for the signal to skip over a group of bits

m denotes the optimal number of groups for an n-bit carry chain

m is the smallest positive integer satisfying

$$n \leq m + \frac{1}{2}mT + \frac{1}{4}m^2T + (1 - (-1)^m)\frac{1}{8}T$$

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

Delay model

n : the number of **bits** in a carry skip adder

m : the number of **groups** into which the bits are divided

x_1, \dots, x_m : the **sizes** of the groups beginning with the most significant bit

T : the **time** required for a carry signal to **skip over** a **group of bits**

To be precise we should write $T = T(x)$ to indicate that

T depends on the size x of the group over which the carry is skipped

However, T changes very slowly with x over the range of group sizes


So we assume that T is **constant**

For a given n , the following three step procedure gives

An optimal way of dividing an n bit adder into groups of bits


Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

Variable Block

 

- total $n = 32$ bits
- $m = 9$ groups
- i -th group has x_i bits (size)
- constant skip delay $T = T(x_i)$

Carry Skip Adder

 

t denote the time required for a carry signal to **ripple** across a bit
 T denote the time required for the signal to **skip** over a group of bits
 m denotes the **optimal number of groups** for an n -bit carry chain

Procedure

(I) Let m be the smallest positive integer such that

$$n \leq m + \frac{1}{2}mT + \frac{1}{4}m^2T + (1 - (-1)^m)\frac{1}{8}T$$

(II) Let

$$y_i = \min\{1 + iT, 1 + (m + 1 - i)T\}, \quad i = 1, \dots, m$$

and construct a **histogram** whose i -th column has height y_i
for example, for $T=3$, and $n=48$, we have $m=7$

(III) It is easily verified that the area of the histogram in (II) is

$$m + \frac{1}{2}mT + \frac{1}{4}m^2T + (1 - (-1)^m)\frac{1}{8}T \geq n$$

so these are at least n unit squares in the histogram
starting with the first row, shade in n of the squares, row by row
Let x_i denote the number of shaded squares in column i of the histogram,
 $i = 1, \dots, m$

- total $n=48$ bits
- $m=7$ groups
- i -th group has x_i bits (size)
- constant skip delay $T = T(x_i) = 3$

Example 1 - (1)

For a 48 bit adder we have, from Figure

$$x_1 = x_7 = 4, x_2 = x_6 = 7, x_3 = 8, x_4 = x_5 = 9$$

The maximum delay is experienced
by a signal generated in the second bit position
and terminating in the 47th bit position

the delay is $mT = 21$

- total $n = 48$ bits
- $m = 7$ groups
- i -th group has x_i bits (size)
- constant skip delay $T = T(x_i) = 3$

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

Example 1 - (2)


$$n \leq m + \frac{1}{2}mT + \frac{1}{4}m^2T + (1 - (-1)^m)\frac{1}{8}T$$

$$48 \leq m + \frac{3}{2}m + \frac{3}{4}m^2 + (1 - (-1)^m)\frac{3}{8}$$

- total $n = 48$ bits
- $m = 7$ groups
- i -th group has x_i bits (size)
- constant skip delay $T = T(x_i) = 3$

1	4
2	8
3	15
4	22
5	32
6	42
7	55
8	68
9	84
10	100

48 < 55

 


Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

$m = 7$

Example 1 - (3)

$n = 48$
 $m = 7$
 $T = 3$

 

$$y_i = \min\{1+iT, 1+(m+1-i)T\}, \quad i = 1, \dots, m$$

$$y_1 = \min\{1+1 \cdot T, 1+7 \cdot T\} = 1+1 \cdot T = 4$$

$$0 \leq x_1 \leq 1+1 \cdot T = 4$$

$$y_2 = \min\{1+2 \cdot T, 1+6 \cdot T\} = 1+2 \cdot T = 7$$

$$0 \leq x_2 \leq 1+2 \cdot T = 7$$

$$y_3 = \min\{1+3 \cdot T, 1+5 \cdot T\} = 1+3 \cdot T = 10$$

$$0 \leq x_3 \leq 1+3 \cdot T = 10$$

$$y_4 = \min\{1+4 \cdot T, 1+4 \cdot T\} = 1+4 \cdot T = 13$$

$$0 \leq x_4 \leq 1+4 \cdot T = 13$$

$$y_5 = \min\{1+5 \cdot T, 1+3 \cdot T\} = 1+3 \cdot T = 10$$

$$0 \leq x_5 \leq 1+3 \cdot T = 10$$

$$y_6 = \min\{1+6 \cdot T, 1+2 \cdot T\} = 1+2 \cdot T = 7$$

$$0 \leq x_6 \leq 1+2 \cdot T = 7$$



$$y_7 = \min\{1+7 \cdot T, 1+1 \cdot T\} = 1+1 \cdot T = 4$$

$$0 \leq x_7 \leq 1+1 \cdot T = 4$$

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

$$0 \leq x_i \leq y_i, i = 1, \dots, m$$

Example 1 - (4)

  

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

Example 2 - (1)

consider a 54 bit adder

From 2(i), we see that again $m=7$.

If we shade 54 squares in Figure, we see that

$$x_1 = x_7 = 4, x_2 = x_6 = 7, x_3 = x_5 = 10, x_4 = 12$$

Yields an optimal division of the adder.

Again the maximum delay is $mT = 21$

- total $n = 54$ bits
- $m = 7$ groups
- i -th group has x_i bits (size)
- constant skip delay $T = T(x_i) = 3$

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

Example 2 - (2)


$$n \leq m + \frac{1}{2}mT + \frac{1}{4}m^2T + (1 - (-1)^m)\frac{1}{8}T$$

$$54 \leq m + \frac{3}{2}m + \frac{3}{4}m^2 + (1 - (-1)^m)\frac{3}{8}$$

- total $n = 54$ bits
- $m = 7$ groups
- i -th group has x_i bits (size)
- constant skip delay $T = T(x_i) = 3$

1	4
2	8
3	15
4	22
5	32
6	42
7	55
8	68
9	84
10	100

54 < 55

 


Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

$m = 7$

Example 2 - (3)

$n = 54$
 $m = 7$
 $T = 3$

 

$$y_i = \min\{1+iT, 1+(m+1-i)T\}, \quad i = 1, \dots, m$$

$$y_1 = \min\{1+1 \cdot T, 1+7 \cdot T\} = 1+1 \cdot T = 4$$

$$0 \leq x_1 \leq 1+1 \cdot T = 4$$

$$y_2 = \min\{1+2 \cdot T, 1+6 \cdot T\} = 1+2 \cdot T = 7$$

$$0 \leq x_2 \leq 1+2 \cdot T = 7$$

$$y_3 = \min\{1+3 \cdot T, 1+5 \cdot T\} = 1+3 \cdot T = 10$$

$$0 \leq x_3 \leq 1+3 \cdot T = 10$$

$$y_4 = \min\{1+4 \cdot T, 1+4 \cdot T\} = 1+4 \cdot T = 13$$

$$0 \leq x_4 \leq 1+4 \cdot T = 13$$

$$y_5 = \min\{1+5 \cdot T, 1+3 \cdot T\} = 1+3 \cdot T = 10$$

$$0 \leq x_5 \leq 1+3 \cdot T = 10$$

$$y_6 = \min\{1+6 \cdot T, 1+2 \cdot T\} = 1+2 \cdot T = 7$$

$$0 \leq x_6 \leq 1+2 \cdot T = 7$$



$$y_7 = \min\{1+7 \cdot T, 1+1 \cdot T\} = 1+1 \cdot T = 4$$

$$0 \leq x_7 \leq 1+1 \cdot T = 4$$

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

$$0 \leq x_i \leq y_i, i = 1, \dots, m$$

Example 2 - (4)

  

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

Example 3 - (1)

Consider a 64 bit adder
From 2(i) we compute $m=8$.

the corresponding histogram is shown in Figure

The optimal group sizes are:

$$x_1 = x_8 = 4, x_2 = x_7 = 7, x_3 = x_6 = 10, x_4 = x_5 = 11$$

The delay of the longest signal is $mT = 24$

- total $n = 64$ bits
- $m = 8$ groups
- i -th group has x_i bits (size)
- constant skip delay $T = T(x_i) = 3$

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

Example 3 - (2)


$$n \leq m + \frac{1}{2}mT + \frac{1}{4}m^2T + (1 - (-1)^m)\frac{1}{8}T$$

$$64 \leq m + \frac{3}{2}m + \frac{3}{4}m^2 + (1 - (-1)^m)\frac{3}{8}$$

- total $n = 64$ bits
- $m = 7$ groups
- i -th group has x_i bits (size)
- constant skip delay $T = T(x_i) = 3$

1	4
2	8
3	15
4	22
5	32
6	42
7	55
8	68
9	84
10	100

64 < 68

 


Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

$m = 8$

Example 3 - (3)

$n = 64$
 $m = 8$
 $T = 3$

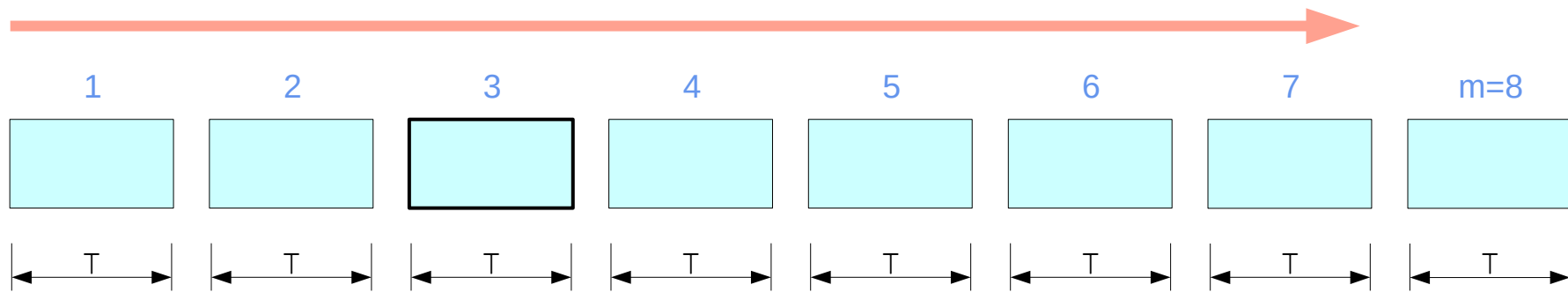

$$y_i = \min\{1+iT, 1+(m+1-i)T\}, \quad i = 1, \dots, m$$

$$y_1 = \min\{1+1 \cdot T, 1+8 \cdot T\} = 1+1 \cdot T = 4$$

$$0 \leq x_1 \leq 1+1 \cdot T = 4$$

$$y_2 = \min\{1+2 \cdot T, 1+7 \cdot T\} = 1+2 \cdot T = 7$$

$$0 \leq x_2 \leq 1+2 \cdot T = 7$$

$$y_3 = \min\{1+3 \cdot T, 1+6 \cdot T\} = 1+3 \cdot T = 10$$

$$0 \leq x_3 \leq 1+3 \cdot T = 10$$

$$y_4 = \min\{1+4 \cdot T, 1+5 \cdot T\} = 1+4 \cdot T = 13$$

$$0 \leq x_4 \leq 1+4 \cdot T = 13$$

$$y_5 = \min\{1+5 \cdot T, 1+4 \cdot T\} = 1+4 \cdot T = 13$$

$$0 \leq x_5 \leq 1+4 \cdot T = 13$$

$$y_6 = \min\{1+6 \cdot T, 1+3 \cdot T\} = 1+3 \cdot T = 10$$

$$0 \leq x_6 \leq 1+3 \cdot T = 10$$

$$y_7 = \min\{1+7 \cdot T, 1+2 \cdot T\} = 1+2 \cdot T = 7$$

$$0 \leq x_7 \leq 1+2 \cdot T = 7$$



$$y_8 = \min\{1+8 \cdot T, 1+1 \cdot T\} = 1+1 \cdot T = 4$$

$$0 \leq x_8 \leq 1+1 \cdot T = 4$$

$$0 \leq x_i \leq y_i, i = 1, \dots, m$$

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

Example 3 - (4)

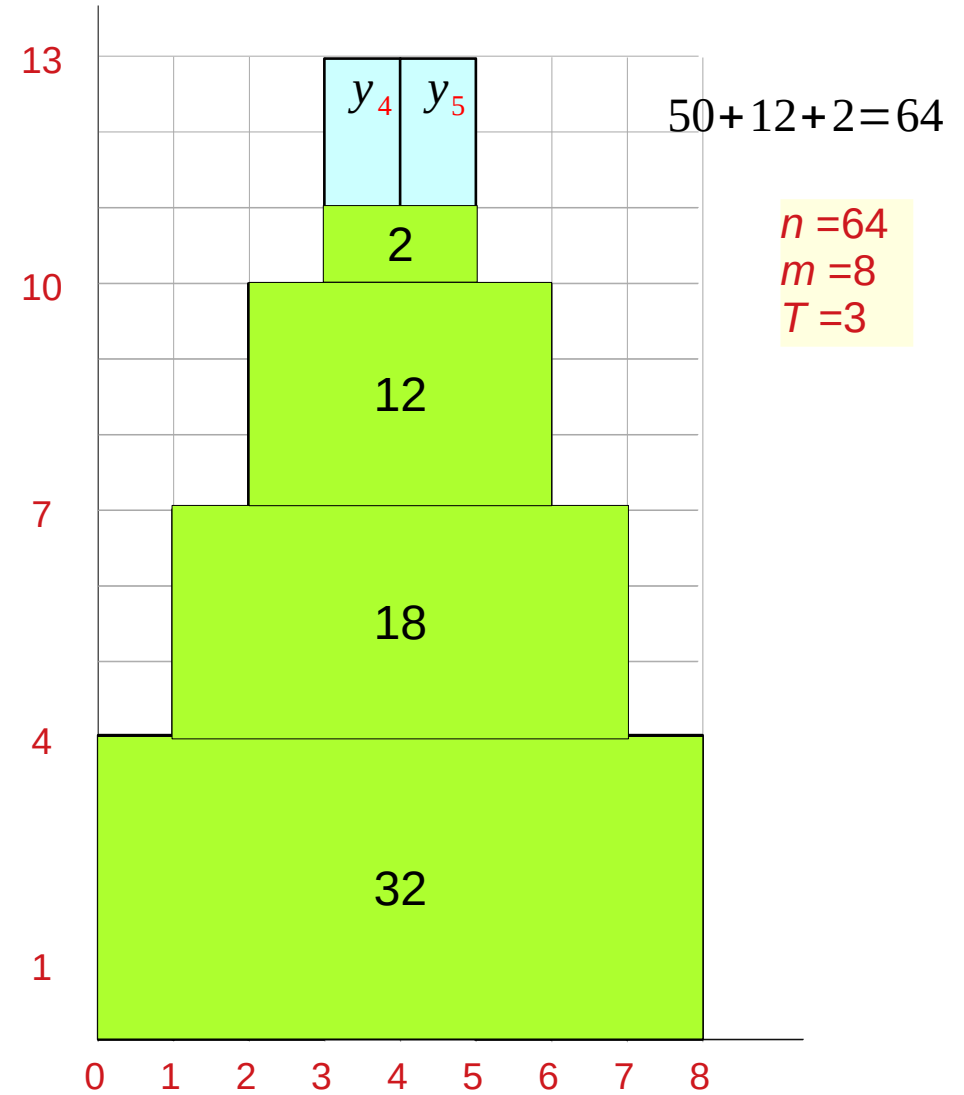 

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

Ripple delay and skip delay

For a 32-bit adder, and the VBA scheme, we divided the Carry chain into blocks of sizes 1, 3, 5, 7, 7, 5, 3, 1.

Why this division is optimal?

Let t denote the time required for a carry signal to ripple across a one bit in the carry chain, and let T denote the time required for the signal to skip over a group of bits.

$$\Delta_{rca} = 1 \quad \text{ripple delay over a bit}$$

$$\Delta_{SKIP} = T \quad \text{skip delay over a group}$$

By simulation of the blocks, we have found that $t = 0.8$ ns and $T = 165$ ns.

To simplify our analysis, we normalize them

So that $t = 1$ and $T = 2$.

Then we apply the theory developed for finding the optimal division of a carry chain

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

Maximum propagation time P

Lemma 1 When the bits of a carry skip adder are grouped according to the scheme (i)-(iii), the **maximum propagation time** of a carry signal is mT

- n bits
- m groups


The carry generated at the 2^{nd} bit position and terminating at the $(n-1)$ clearly has propagation time mT . We must show that any other signal has propagation time smaller than or equal to mT .

Consider a signal originating in the i -th group and terminating in the j -th, $i < j$.

Denote its **propagation time** by P . Clearly

$$P \leq (x_i - 1) + (j - i - 1)T + (x_j - 1) \leq mT$$

Propagation delay P

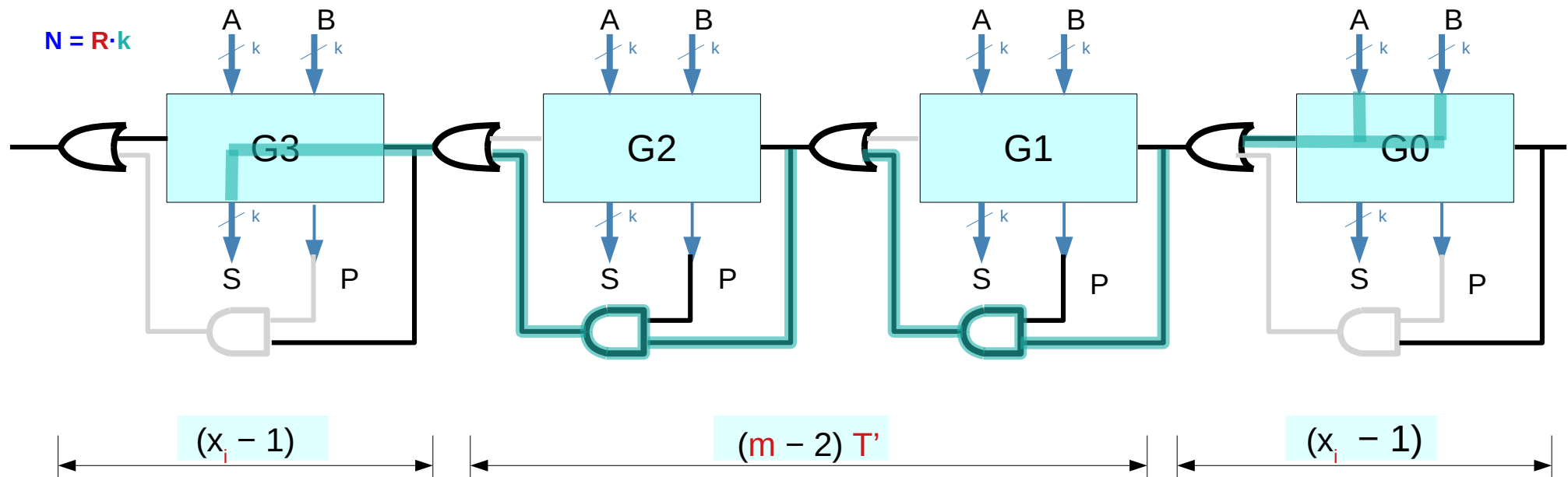


$\Delta_{rca} = 1$ ripple delay over a bit

$\Delta_{SKIP} = T$ skip delay over a group

$$P \leq (x_i - 1) + (j - i - 1)T + (x_j - 1) \leq mT$$

Propagation delay P

 

$$P \leq (x_i - 1) + (j - i - 1)T + (x_j - 1) \leq mT$$

$$x_i \leq \min\{1 + iT, 1 + (m + 1 - i)T\}$$


$$x_j \leq \min\{1 + jT, 1 + (m + 1 - j)T\}$$

Assume a carry signal is generated in the i -th group and terminated in the j -th, $i < j$.

P denotes propagation time

$$P \leq \min\{1 + iT, 1 + (m + 1 - i)T\} + \min\{1 + jT, 1 + (m + 1 - j)T\} + (j - i - 1)T - 2$$

Delay model

 


Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

Three cases

Case 1

$$\min\{1+iT, 1+(m+1-i)T\} = 1+iT$$

$$\min\{1+jT, 1+(m+1-j)T\} = 1+jT$$

 

Case 2

$$\min\{1+iT, 1+(m+1-i)T\} = 1+iT$$


$$\min\{1+jT, 1+(m+1-j)T\} = 1+(m+1-j)T$$



Case 3

$$\min\{1+iT, 1+(m+1-i)T\} = 1+(m+1-i)T$$
 
$$\min\{1+jT, 1+(m+1-j)T\} = 1+(m+1-j)T$$




Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

Case 1

1. First, assume

$$\min\{1+iT, 1+(m+1-i)T\} = 1+iT$$

$$\min\{1+jT, 1+(m+1-j)T\} = 1+jT$$

 

$$1+jT \leq 1+(m+1-j)T \quad \Rightarrow \quad 2jT \leq (m+1)T \quad \Rightarrow \quad 2jT - T \leq mT$$

$$P < 1+iT + 1+(m+1-i)T + (j-i-1)T - 2 = 2jT - T \leq mT$$

$$x_i \leq \min\{1+iT, 1+(m+1-i)T\} = 1+iT$$

$$x_j \leq \min\{1+jT, 1+(m+1-j)T\} = 1+jT$$

$$\begin{aligned} P &\leq \min\{1+iT, 1+(m+1-i)T\} + \min\{1+jT, 1+(m+1-j)T\} + (j-i-1)T - 2 \\ &= 1+iT + 1+jT + (j-i-1)T - 2 \\ &= 2jT - T \leq mT \end{aligned}$$

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

Case 2

2. Now, assume

$$\min\{1+iT, 1+(m+1-i)T\} = 1+iT$$

$$\min\{1+jT, 1+(m+1-j)T\} = 1+(m+1-j)T$$



$$P \leq 1+iT + 1 + (m+1-i)T + (j-i-1)T - 2 = mT$$

$$P \leq \min\{1+iT, 1+(m+1-i)T\} + \min\{1+jT, 1+(m+1-j)T\} + (j-i-1)T - 2$$


$$P \leq 1+iT + 1+(m+1-j)T + (j-i-1)T - 2 = mT$$

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

Case 3

 3. Finally, assume

$$\min\{1+iT, 1+(m+1-i)T\} = 1+(m+1-i)T$$



$$\min\{1+jT, 1+(m+1-j)T\} = 1+(m+1-j)T$$

$$P \leq 1+(m+1-i)T + 1+(m+1-j)T + (j-i-1)T - 2 = 2mT - (2iT - T) \leq 2mT - mT = mT$$

$$P \leq \min\{1+iT, 1+(m+1-i)T\} + \min\{1+jT, 1+(m+1-j)T\} + (j-i-1)T - 2$$

$$\begin{aligned} P &\leq 1+(m+1-i)T + 1+(m+1-j)T + (j-i-1)T - 2 = 2(m+1-i)T - T \\ &\leq 2(m+1-i)T - T = 2mT - (2iT - T) = mT \end{aligned}$$

$$\begin{aligned} 1+iT \geq 1+(m+1-i)T &\implies 2iT \geq (m+1)T \implies 2iT - T \geq mT \\ &\implies -(2iT - T) \leq -mT \end{aligned}$$

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

Maximum delay of a carry signal


Lemma 2 Let D denote the **maximum delay** of a carry signal in a n bit carry skip adder with **group sizes** chosen **optimally**. Then

$$(m-1)T \leq D \leq mT$$

Since we have exhibited a division of the carry chain into **groups** in such a way that the **maximum delay** of a carry signal is mT

We clearly have $D \leq mT$

- n bits
- m groups

 

Even number $r = 2k$ of groups (1)

Let x_1, x_2, \dots, x_r denote the **optimal group sizes** corresponding to D .
For the moment assume that $r = 2k$ is **even**.

By considering carries originating in **group i**
and terminating in **group** , $r - i + 1$, $i = 1, \dots, k$
we deduce the following system inequalities

the **maximum delay** of a carry signal is mT

$$D \leq mT$$

- n bits
- m groups

- n bits
- r groups – optimal

$$1, 2k = r - (1 - 1), \quad i = 1$$

$$2, 2k - 1 = r - (2 - 1), \quad i = 2$$

$$k, k + 1 = r - (k - 1), \quad i = k$$

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

Even number $r = 2k$ of groups (2)

$$r = 2k$$

$$P \leq (x_i - 1) + (j - i - 1)T + (x_j - 1) \leq mT$$

- n bits
- r groups



$$(x_1 - 1) + (r - 2)T + (x_r - 1) \leq D$$

$$(x_2 - 1) + (r - 4)T + (x_{r-1} - 1) \leq D$$

$$(x_3 - 1) + (r - 6)T + (x_{r-2} - 1) \leq D$$

$$(x_k - 1) + (r - 2k)T + (x_{k+1} - 1) \leq D$$

$$mT \leq D$$

  


Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

Even number $r = 2k$ of groups (3)

$$r = 2k$$

$$P \leq (x_i - 1) + (j - i - 1)T + (x_j - 1) \leq mT$$

- n bits
- r groups

 

$$(j - i - 1) = r - 2 = 2(k - 1)$$

$$(j - i - 1) = r - 4 = 2(k - 2)$$

$$(j - i - 1) = r - 6 = 2(k - 3)$$

$$(j - i - 1) = r - 2k = 2(k - k)$$

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

Even number $r = 2k$ of groups (4)

$$r = 2k$$

$$P \leq (x_i - 1) + (j - i - 1)T + (x_j - 1) \leq mT$$

$$\begin{aligned}
 (x_1 - 1) + 2(k-1)T + (x_{2k} - 1) &\leq D & i = 1 \\
 (x_2 - 1) + 2(k-2)T + (x_{2k-1} - 1) &\leq D & i = 2 \\
 (x_3 - 1) + 2(k-3)T + (x_{2k-2} - 1) &\leq D & i = 3 \\
 \vdots & & \\
 (x_k - 1) + 2(k-k)T + (x_{k+1} - 1) &\leq D & i = k \\
 & & \leq D
 \end{aligned}$$

$$n - 2k + (k+1)rT - k(k+1)T \leq (k+1)D$$

- n bits
- r groups

$$\sum_{i=1}^r x_i = n$$

$$\sum_{i=1}^k i = \frac{k(k+1)}{2}$$

$$2k = r$$

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

Even number $r = 2k$ of groups (5)

$$r=2k$$

$$n - 2k + (k + 1)rT - k(k + 1)T \leq (k + 1)D$$

$$\frac{n-2k}{k+1} + rT - kT \leq D$$

$$\frac{n-2k}{k+1} + 2kT - kT \leq D$$

$$\frac{n-2(k+1)+2}{k+1} + kT \leq D$$

$$\frac{n+2}{k+1} + (k+1)T - (T+2) \leq D$$

$$2\sqrt{(n+2)T} - (T+2) \leq D$$

$$\sqrt{4nT+8T} - (T+2) \leq D$$

arith mean \geq geo mean

$$\frac{n+2}{k+1} + (k+1)T \geq 2 \cdot \sqrt{\frac{n+2}{k+1} \cdot (k+1)T}$$

$$\frac{n+2}{k+1} + (k+1)T \geq 2\sqrt{(n+2)T}$$

min when $\frac{n+2}{k+1} = (k+1)T$

$$\frac{n+2}{T} = (k+1)^2$$

$$(k+1) = \sqrt{\frac{n+2}{T}}$$

Odd number $r = 2k+1$ of groups (1)

Let x_1, x_2, \dots, x_r denote the **optimal group sizes** corresponding to D .
For the moment assume that $r = 2k+1$ is **odd**.

By considering carries originating in **group i**
and terminating in **group $r-i+1$** , $i = 1, \dots, k$
we deduce the following system inequalities

the **maximum delay** of a carry signal is mT

$$D \leq mT$$

- n bits
- m groups

- n bits
- r groups – optimal

$$1, 2k+1 = r - (1-1), \quad i = 1$$

$$2, 2k = r - (2-1), \quad i = 2$$

$$k, k+2 = r - (k-1), \quad i = k$$

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

Odd number $r = 2k+1$ of groups (2)

$$r = 2k + 1$$

$$P \leq (x_i - 1) + (j - i - 1)T + (x_j - 1) \leq mT$$

- n bits
- r groups



$$(x_1 - 1) + (r - 2)T + (x_r - 1) \leq D$$

$$(x_2 - 1) + (r - 4)T + (x_{r-1} - 1) \leq D$$

$$(x_3 - 1) + (r - 6)T + (x_{r-2} - 1) \leq D$$

$$(x_k - 1) + (r - 2k)T + (x_{r-k+1} - 1) \leq D$$

$$kT + (x_{k+1} - 1) \leq D$$

  


Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

Odd number $r = 2k+1$ of groups (3)

$$r = 2k + 1$$

$$P \leq (x_i - 1) + (j - i - 1)T + (x_j - 1) \leq mT$$

- n bits
- r groups

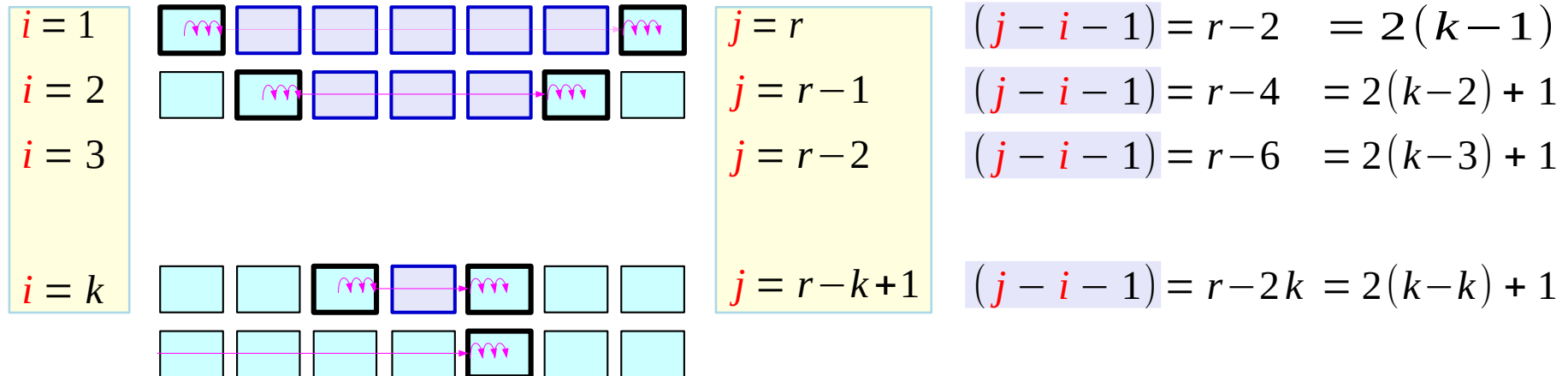

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

Odd number $r = 2k+1$ of groups (4)

$$r = 2k + 1$$

$$P \leq (x_i - 1) + (j - i - 1)T + (x_j - 1) \leq mT$$

$$(x_1 - 1) + 2(k - 1)T + T + (x_{2k+1} - 1) \leq D$$

$$(x_2 - 1) + 2(k - 2)T + T + (x_{2k} - 1) \leq D$$

$$(x_3 - 1) + 2(k - 3)T + T + (x_{2k-1} - 1) \leq D$$

$$(x_k - 1) + 2(k - k)T + T + (x_{k+2} - 1) \leq D$$

$$kT + (x_{k+1} - 1) \leq D$$

$$n - 2k - 1 + (r + 1)kT - k(k + 1)T \leq (k + 1)D$$

- n bits
- r groups

$$\sum_{i=1}^r x_i = n$$

$$\sum_{i=1}^k i = \frac{k(k+1)}{2}$$

$$2k + 1 = r$$

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

Odd number $r = 2k+1$ of groups (5)

$$r = 2k+1$$

$$n - 2k - 1 + (r+1)kT - k(k+1)T \leq (k+1)D$$

$$\frac{n-2k-1}{(k+1)} + \frac{(r+1)kT}{(k+1)} - kT \leq D$$

$$\frac{n-2k-1}{(k+1)} + \frac{(2(k+1))kT}{(k+1)} - kT \leq D$$

$$\frac{n-2k-1}{(k+1)} + kT \leq D$$

$$\frac{n-2(k+1)+1}{(k+1)} + (k+1)T - T \leq D$$

$$\frac{(n+1)}{(k+1)} + (k+1)T - (T+2) \leq D$$

$$2 \cdot \sqrt{(n+1)T} - (T+2) \leq D$$

$$\sqrt{4nT+4T} - (T+2) \leq D$$

arith mean \geq geo mean

$$\frac{(n+1)}{(k+1)} + (k+1)T \geq 2 \cdot \sqrt{(n+1)T}$$

min when $\frac{(n+1)}{(k+1)} = (k+1)T$

$$\frac{n+1}{T} = (k+1)^2$$

$$(k+1) = \sqrt{\frac{n+1}{T}}$$

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

Delay model

$$r=2k$$

$$\sqrt{4nT+8T} - (T+2) \leq D$$

$$r=2k+1$$

$$\sqrt{4nT+4T} - (T+2) \leq D$$

$$\sqrt{4nT+4T} - (T+2) \leq \sqrt{4nT+8T} - (T+2)$$

$$\sqrt{4nT+4T} - (T+2) \leq D$$

We will not produce an upper bound on mT .

Since m is the smallest positive integer satisfying

$$(m-1) + \frac{1}{2}(m-1)T + \frac{1}{4}(m-1)^2T + (1 - (-1)^{m-1})\frac{T}{8} < n$$

$$n \leq m + \frac{1}{2}mT + \frac{1}{4}m^2T + (1 - (-1)^m)\frac{1}{8}T$$

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

Delay model

$$(m-1) + \frac{1}{2}(m-1)T + \frac{1}{4}(m-1)^2T + (1 - (-1)^{m-1})\frac{T}{8} < n$$

$$(m-1) + \frac{1}{2}(m-1)T + \frac{1}{4}(m-1)^2T + (1 - (-1)^{m-1})\frac{T}{8} + 1 \leq n$$

$$(m) + \frac{1}{2}(mT - T) + \frac{1}{4}(m^2T - 2mT + T) + (1 - (-1)^{m-1})\frac{T}{8} \leq n$$

$$m - \frac{1}{4}T + \frac{1}{4}m^2T + (1 - (-1)^{m-1})\frac{T}{8} \leq n$$

$$m^2T^2 + 4mT \leq 4nT + T^2 - (1 - (-1)^{m-1})\frac{T^2}{2}$$

$$\frac{1}{4}m^2T \leq n - m + \frac{1}{4}T - (1 - (-1)^{m-1})\frac{T}{8}$$

$$m^2T^2 + 4mT + 4 \leq 4 + 4nT + T^2 - (1 - (-1)^{m-1})\frac{T^2}{2}$$

$$\left(\frac{1}{4}m^2T\right) \cdot 4T \leq \left(n - m + \frac{1}{4}T - (1 - (-1)^{m-1})\frac{T}{8}\right) \cdot 4T$$

$$(mT + 2)^2 \leq 4 + 4nT + T^2 - (1 - (-1)^{m-1})\frac{T^2}{2}$$

$$m^2T^2 \leq 4nT - 4mT + T^2 - (1 - (-1)^{m-1})\frac{T^2}{2}$$

$$(mT + 2) \leq \sqrt{4 + 4nT + T^2 - (1 - (-1)^{m-1})\frac{T^2}{2}}$$

$$mT \leq -2 + \sqrt{4 + 4nT + T^2 - (1 - (-1)^{m-1})\frac{T^2}{2}}$$

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

Delay model

$$r=2k \quad \sqrt{4nT+8T} - (T+2) \leq D$$

$$r=2k+1 \quad \sqrt{4nT+4T} - (T+2) \leq D$$

$$mT \leq -2 + \sqrt{4 + 4nT + T^2 - (1 - (-1)^{m-1})\frac{T^2}{2}}$$

$$mT - D \leq T + \frac{T^2 - 8T + 4 - (1 - (-1)^{m-1})\frac{T^2}{2}}{\sqrt{4nT+8T} + \sqrt{4nT+4+T^2 - (1 - (-1)^{m-1})\frac{T^2}{2}}} \quad \text{even } r$$

$$mT - D \leq T + \frac{T^2 - 4T + 4 - (1 - (-1)^{m-1})\frac{T^2}{2}}{\sqrt{4nT+4T} + \sqrt{4nT+4+T^2 - (1 - (-1)^{m-1})\frac{T^2}{2}}} \quad \text{odd } r$$

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

Delay model

$$mT \leq -2 + \sqrt{4nT + T^2 + 4 - (1 - (-1)^{m-1}) \frac{T^2}{2}}$$

$$r = 2k$$

$$\sqrt{4nT + 8T} - (T + 2) \leq D$$

$$mT - D \leq T + \frac{T^2 - 8T + 4 - (1 - (-1)^{m-1}) \frac{T^2}{2}}{\sqrt{4nT + 8T} + \sqrt{4nT + T^2 + 4 - (1 - (-1)^{m-1}) \frac{T^2}{2}}}$$

$$r = 2k + 1$$

$$\sqrt{4nT + 4T} - (T + 2) \leq D$$

$$mT - D \leq T + \frac{T^2 - 4T + 4 - (1 - (-1)^{m-1}) \frac{T^2}{2}}{\sqrt{4nT + 4T} + \sqrt{4nT + T^2 + 4 - (1 - (-1)^{m-1}) \frac{T^2}{2}}}$$

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

$r=2k$ even r

$$r=2k$$

$$mT \leq -2 + \sqrt{4nT + T^2 + 4 - (1 - (-1)^{m-1}) \frac{T^2}{2}}$$

$$-D \leq -\sqrt{4nT+8T} + (T+2)$$

$$mT - D \leq T - \sqrt{4nT+8T} + \sqrt{4nT + T^2 + 4 - (1 - (-1)^{m-1}) \frac{T^2}{2}}$$



$$mT - D \leq T + \frac{T^2 - 8T + 4 - (1 - (-1)^{m-1}) \frac{T^2}{2}}{\sqrt{4nT+8T} + \sqrt{4nT + T^2 + 4 - (1 - (-1)^{m-1}) \frac{T^2}{2}}}$$

$r=2k$ even r


$$r=2k$$

$$X \stackrel{\text{def}}{=} 4 - (1 - (-1)^{m-1}) \frac{T^2}{2}$$

$$mT \leq -2 + \sqrt{4nT + T^2 + X}$$

$$-D \leq -\sqrt{4nT+8T} + (T+2)$$

$$mT - D \leq T - \sqrt{4nT+8T} + \sqrt{4nT+T^2+X}$$

$$(-\sqrt{a} + \sqrt{b}) \cdot \frac{(+\sqrt{a} + \sqrt{b})}{(+\sqrt{a} + \sqrt{b})} = \frac{(-a + b)}{(+\sqrt{a} + \sqrt{b})}$$


$$\left(-\sqrt{4nT+8T} + \sqrt{4nT+T^2+X} \right) \cdot \frac{(\sqrt{4nT+8T} + \sqrt{4nT+T^2+X})}{(\sqrt{4nT+8T} + \sqrt{4nT+T^2+X})}$$

$$\{-\sqrt{4nT+8T} + \sqrt{4nT+T^2+X}\} \cdot \{+\sqrt{4nT+8T} + \sqrt{4nT+T^2+X}\}$$

$$= -(4nT+8T) + (4nT+T^2+X) = T^2 - 8T + X$$

$$mT - D \leq T + \frac{T^2 - 8T + X}{\sqrt{4nT+8T} + \sqrt{4nT+T^2+X}}$$

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

$r=2k+1$ odd r

$$r=2k+1$$

$$\sqrt{4nT+4T} - (T+2) \leq D$$

$$-\sqrt{4nT+4T} + (T+2) \geq -D$$

$$mT \leq -2 + \sqrt{4nT + T^2 + 4 - (1 - (-1)^{m-1}) \frac{T^2}{2}}$$

$$-D \leq -\sqrt{4nT+4T} + (T+2)$$

$$mT - D \leq T - \sqrt{4nT+8T} + \sqrt{4nT + T^2 + 4 - (1 - (-1)^{m-1}) \frac{T^2}{2}}$$



$$mT - D \leq T + \frac{T^2 - 4T + 4 - (1 - (-1)^{m-1}) \frac{T^2}{2}}{\sqrt{4nT+4T} + \sqrt{4nT + T^2 + 4 - (1 - (-1)^{m-1}) \frac{T^2}{2}}}$$

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

$r=2k+1$ odd r


$$r=2k+1$$

$$X \stackrel{\text{def}}{=} 4 - (1 - (-1)^{m-1}) \frac{T^2}{2}$$

$$mT \leq -2 + \sqrt{4nT + T^2 + X}$$

$$-D \leq -\sqrt{4nT+4T} + (T+2)$$

$$mT - D \leq T - \sqrt{4nT+4T} + \sqrt{4nT+T^2+X}$$

$$(-\sqrt{a} + \sqrt{b}) \cdot \frac{(+\sqrt{a} + \sqrt{b})}{(+\sqrt{a} + \sqrt{b})} = \frac{(-a + b)}{(+\sqrt{a} + \sqrt{b})}$$


$$\left(-\sqrt{4nT+4T} + \sqrt{4nT+T^2+X} \right) \cdot \frac{(\sqrt{4nT+4T} + \sqrt{4nT+T^2+X})}{(\sqrt{4nT+4T} + \sqrt{4nT+T^2+X})}$$

$$\{-\sqrt{4nT+4T} + \sqrt{4nT+T^2+X}\} \cdot \{+\sqrt{4nT+4T} + \sqrt{4nT+T^2+X}\}$$

$$= -(4nT+4T) + (4nT+T^2+X) = T^2 - 4T + X$$

$$mT - D \leq T + \frac{T^2 - 4T + X}{\sqrt{4nT+4T} + \sqrt{4nT+T^2+X}}$$

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

r=2k even r

$$X \stackrel{\text{def}}{=} 4 - (1 - (-1)^{m-1}) \frac{T^2}{2}$$

- odd m $X = 4$

- even m $X = 4 - T^2$

$$\sqrt{4nT + T^2 + 4 - (1 - (-1)^{m-1}) \frac{T^2}{2}} = \sqrt{4nT + T^2 + X}$$

- odd m

$$(-1)^{m-1} = 1$$

$$(1 - (-1)^{m-1}) = 0$$

$$\sqrt{4nT + 4 + T^2}$$

- even m

$$(-1)^{m-1} = -1$$

$$(1 - (-1)^{m-1}) = 2$$

$$\begin{aligned} &\sqrt{4nT + T^2 + 4 - T^2} \\ &= \sqrt{4nT + 4} \end{aligned}$$

$$mT - D \leq T + \frac{T^2 - 8T + X}{\sqrt{4nT + 8T} + \sqrt{4nT + T^2 + X}}$$

$$\leq T + \frac{T^2 - 8T + 4}{\sqrt{4nT + 8T} + \sqrt{4nT + T^2 + 4}}$$

$$\leq T + \frac{-8T + 4}{\sqrt{4nT + 8T} + \sqrt{4nT + 4}}$$

$$mT - D \leq T + \frac{T^2 - 4T + X}{\sqrt{4nT + 4T} + \sqrt{4nT + T^2 + X}}$$

$$\leq T + \frac{T^2 - 4T + 4}{\sqrt{4nT + 4T} + \sqrt{4nT + T^2 + 4}}$$

$$\leq T + \frac{-4T + 4}{\sqrt{4nT + 4T} + \sqrt{4nT + 4}}$$

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

$r=2k$ even r

$$mT - D \leq T + \frac{T^2 - 8T + X}{\sqrt{4nT + 8T} + \sqrt{4nT + T^2 + X}}$$

$$X \stackrel{\text{def}}{=} 4 - (1 - (-1)^{m-1}) \frac{T^2}{2}$$

$$mT - D \leq T + \frac{T^2 - 4T + X}{\sqrt{4nT + 4T} + \sqrt{4nT + T^2 + X}}$$

For n sufficiently large, we have $mT - \Delta < T + 1$

And since $mT - \Delta$ is an integer, $mT - \Delta \leq T$

This completes the proof of the lemma

Delay model

The scheme 2(i)- 2(iii) given above
for dividing the bits of a carry skip adder
Into groups is optimal for $2 \leq T \leq 7$

Assume the scheme is not optimal and
let D be the maximum delay

Corresponding to an optimal division of the bits into groups

Assume there are r groups in the optimal division.

Since a carry in signal to the least significant bit group can skip over

Each group we have $rT \leq D \leq mT$, so $r \leq m$

If $r = m$ then $D = mT$ and the theorem holds by Lemma 1

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

Delay model

If $r = m-1$ m and r have different parities

and it follows from (5) that

$mT - D < T$ for $2 \leq T \leq 7$
so that $D > (m-1)T = rT$

This means that a signal
which skips over each of the r groups
has delay less than the maximum %DELTA

Similarly, if $r < m-1$, $D > (m-1)T > rT$
So that a signal which skips over each group
has delay $< D$

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

Delay model

It follows that a signal with delay D must start in a group i ,

ripple to the end of this group, then skip over $s < r$ groups and either terminate, or ripple through the first few bits of a group $j > i$

Let x_i and x_j denote the lengths of the i -th and j -th groups respectively.

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

Delay model

Assume that i is chosen as small as possible
and j as large as possible.

A signal originating in group i ,
rippling to the end of this group
and then skipping over the next s group has delay

$$D \leq (x_i - 1) + sT \leq (x_i - 1) + (r - 1)T \leq (x_i - 1) + (m - 2)T.$$

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

Delay model

Since $\%DELTA \geq (m-1)T$ this implies that $x_i \geq T=1$

Divide group I into two groups such that the group containing the most significant Bits has size T .

Since the i -th group is the first group in which a signal having maximum delay can Originate, this subdivision does not increase the delay of any carry signal of maximum delay

However, it increases the number of groups by 1

Suppose now that a carry signal originates in a group I , ripples to its end,

Skips over $s \leq r-2$ groups and finally ripples through the first few bits of a group J and terminates. We then have

$$\%DELTA \leq (x_{i-1}) + sT + (x_{j-1}) \leq x_i + x_j - 2 + (m - 3)T$$

pp

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

Delay model

So that either $x_i \geq T+1$ or $x_j \geq T+1$.

This means that we can subdivide one of the groups I, j without increasing $\%DELTA$

Continuing in this way, we can always increase the number r of group
In an optimal division of a carry chain by 1 without increasing $\%DELTA$
If $r < m$


This means that we can arrive at an optimal division of the carry chain
Into m groups.

We must then have $\%DELTA \geq mT$ which, together with Lemma 2,
Implies $\%DELTA = mT$

This completes the proof of the theorem

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

Delay model

 

$$y_i = \min \{ 1 + iT, 1 + (m + 1 - i)T \}$$


$$y_1, \dots, y_m$$

$$0 \leq x_i \leq y_i, i = 1, \dots, m$$

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

$$\sum_{i=1}^m x_i = n$$

Delay model

 

$$y_i = \min\{1+iT, 1+(m+1-i)T\}$$

$$y_1, \dots, y_m$$

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

Delay model

Given m , an optimal division of the carry chain into groups

Can be obtained as follows

Let

$$y_i = \min \{ 1 + iT, 1 + (m + 1 - i)T \}$$

Given y_1, \dots, y_m solve the minimization problem

$$\min_x \max \{ x_1, \dots, x_n \}$$

Subject to

$$0 \leq x_i \leq y_i, i = 1, \dots, m$$

And

$$\sum_{i=1}^m x_i = n$$

Any solution x_1, \dots, x_m gives optimal group sizes for a division of the carry chain

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

Delay model

The x 's can be computed iteratively as follows:

Initially take $x_1 = x_m = 0$

At each iteration, increase as many of the x 's as possible by one unit, without violating the constraints

$$0 \leq x_i \leq y_i, i = 1, \dots, m \quad \sum_{i=1}^m x_i \leq n$$

An easy calculation shows that

$$\sum_{i=1}^m y_i = m + \frac{1}{2}mT + \frac{1}{4}m^2T + (1 - (-1)^m)\frac{1}{8}T \geq n$$

Thus, at some iteration, we have $\sum_{i=1}^m x_i = n$ and
The algorithm terminates

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

Delay model

For $n=32$, we have $m=7$, $(y_1, y_2, y_3, y_4, y_5, y_6, y_7) = (3, 5, 7, 9, 7, 5, 3)$
The above algorithm gives $(x_1, x_2, x_3, x_4, x_5, x_6, x_7) = (3, 5, 5, 6, 5, 5, 3)$

A carry chain divided in this way has maximum delay $D = mT = 14$
Since one unit of delay is 0.8ns , the maximum delay for 32-bit carry chain
is $D = 14 * 0.8\text{ns} = 11.2\text{ns}$
This time involves only the delay in the carry chain

It is easy to check that this is also the delay for a chain divided into groups of
sizes $1, 3, 5, 7, 7, 5, 3, 1$.
Thus this is also an optimal subdivision

The worst case delay includes the time needed to generate p_i and g_i signals
Delay of the carry chain, and the time for producing last sum bit s_n

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

Delay model

Implement it with a string of multiplexers

The multiplexer cell is designed as very fast

Multiplexers are designed as very fast structures using buffered pass gates and in this sense are similar to the Manchester carry chain which has been shown to be the most effective implementation of a carry chain

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

Delay model

The implementation of a single carry block is done by mixing a **4 to 1 multiplexer** (actually used as a 3 to 1)

In the last stage with a string of 2 to 1 multiplexers

a carry bypass is connected to inputs 3 and 4 of the 4:1 multiplexer (group carry multiplexer) and the selection of the carry bypass is activated by the NAND gate signaling when the condition for group propagate is reached and activating the group multiplexer in turn.

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

Delay model

The 32-bit implementation of the VBA adder is obtained
By connecting the groups of the sizes calculated
For the full length of $n=32$ bits

To increase the speed further we used a faster inverting version
Of the multiplexer, alternating between C_i and C_{b_i} signals

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers