FPGA Carry Chain Adder (1A)

•


•

Copyright (c) 2010 -- 2020 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".

Please send corrections (or suggestions) to youngwlim@hotmail.com.

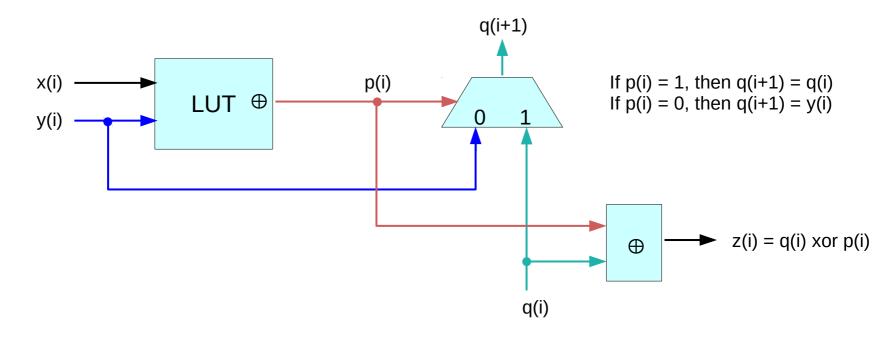This document was produced by using OpenOffice and Octave.




$$\begin{aligned} s_i &= (a_i \oplus b_i) \oplus c_i = p_i \oplus c_i \\ c_{i+1} &= (a_i \cdot b_i) + (a_i \oplus b_i) c_i = \overline{p_i} \cdot g_i + p_i \cdot c_i = \overline{p_i} \cdot a_i + p_i \cdot c_i = \overline{p_i} \cdot b_i + p_i \cdot c_i \end{aligned}$$

when
$$\overline{p}_i = 1$$
, then $a_i = b_i$
when $g_i = 1$, then $a_i = b_i = 1$

p(i)	0	1
0	0	1
1	1	0

g(i)	0	1
0	0	0
1	0	1

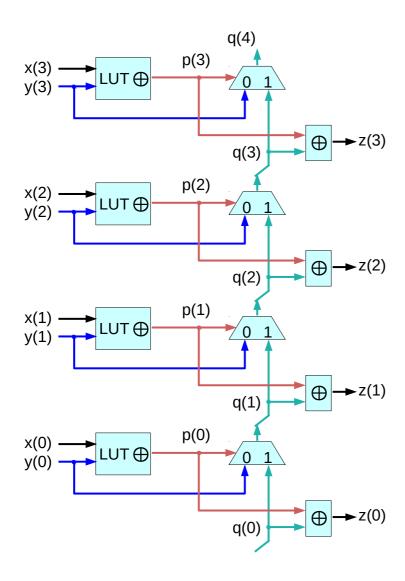Synthesis of Arithmetic Circuits: FPGA, ASIC and Ebedded Systems, J-P Deschamps et al



Synthesis of Arithmetic Circuits: FPGA, ASIC and Ebedded Systems, J-P Deschamps et al

FPGA Carry Chain

FPGAs generally contain dedicated computation resources for generating fast adders


The Virtex family programmable arrays include logic gates (XOR) and multiplexers that along with the general purpose lookup tables allow one to build effective carry-chain adders

The carry chain is made up of multiplexers belonging to adjacent configurable blocks

the lookup table is used for implementing the exclusive or function

$$p(i) = x(i) xor y(i)$$

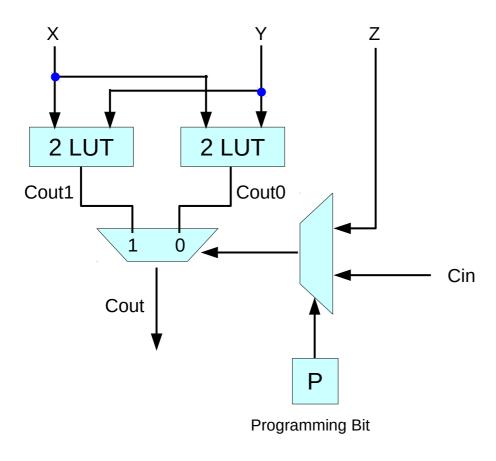https://en.wikipedia.org/wiki/Carry-lookahead_adder




Cout1, Cout2: functions of X, Y, Cin

Cout1 = X+Y when Cin=1 Cout0 = X Y when Cin=0

Cout = $(X + Y) Cin + X Y \overline{Cin}$

Cout = P' Cin + G $\overline{\text{Cin}}$... P' = relaxed P

Cout1	Cout0	Cout	Name
0	0	0	Kill
0	1	Cin	Inverse Propagate
1	0	Cin	Propagate
1	1	1	Generate

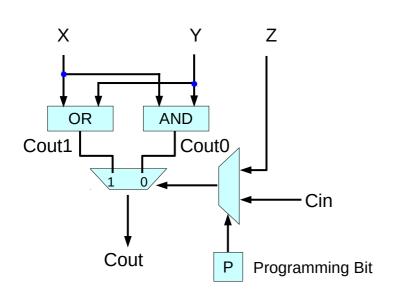

		Cin	Cin	
X	Υ	Cout1	Cout0	
0	0	0	0	$\overline{X} \overline{Y}$
0	1	1	0	$\overline{X} Y$
1	0	1	0	$X\overline{Y}$
1	1	1	1	ΧY

Cout: functions of X, Y, Cin

Cout(X, Y, 1) = Cout1 = X + YCout(X, Y, 0) = Cout0 = X Y

Cout1 = X + Y when Cin=1 Cout0 = XY when Cin=0


Cout1 = P' $\underline{\text{Cin}}$... P' = relaxed P Cout0 = $\underline{\text{Cin}}$


High Performance Carry Chains for FPGAs, S. Hauck, M. M. Hosler, T. W. Fry

If \underline{Cin} , then $\underline{Cout} = (\overline{X} \ Y + X \ \overline{Y} + X \ Y)$ If \underline{Cin} , then $\underline{Cout} = X \ Y$

Cin $(X + Y) + \overline{Cin} X Y$ Cin $(X Y + X Y + X Y) + \overline{Cin} X Y$ Cin $(X Y + X Y) + (Cin + \overline{Cin}) X Y$ P Cin + G

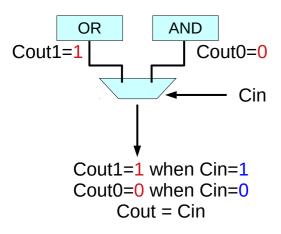Cin $(X + Y) + \overline{Cin} X Y$ Cin P' + $\overline{Cin} G$... P' : relaxed P




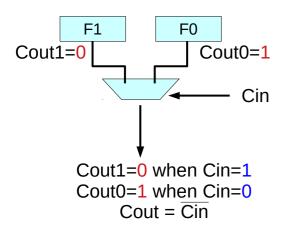

Cout0	Cout1	Cout	Name
0	0	0	Kill
0	1	Cin	Propagate
1	0	Cin	Inverse Propagate
1	1	1	Generate

Cout1	Cout0	Cout	Name
0	0	0	Kill
0	1	Cin	Inverse Propagate
1	0	Cin	Propagate
1	1	1	Generate

Carry Chain

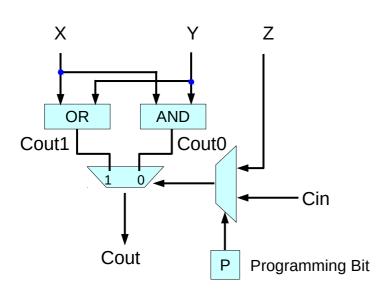

•	_		_	•	, , , ,
1	0	, -	1	0	$X\overline{Y}$
1	1		1	1	ΧY
Cout1	Cout0	Cout	Name)	
0	0	0	Kill		
0	1	Cin	Inve	rse F	Propagate
1	0	Cin	Prop	baga	te

1

0

1

Χ

0

0

Cin

0

0

 $\begin{array}{c} \overline{\overline{X}} \ \overline{\overline{Y}} \\ \overline{X} \ \underline{Y} \\ X \ \overline{Y} \end{array}$

Cout0

Generate

Cin Cout1

0


1

Car	ry Ou	t,	
Χ	Υ	Cin	
0	0		Cin
0	1	Cin	Cin
1	0	Cin	Cin
1	1	Cin	Cin

Cout1=1 when Cout0=0 when Cout = Cin	
Cout1=0 when Cout0=1 when	
Cout = \overline{Cin}	inverse propagate

1

Parity Checker

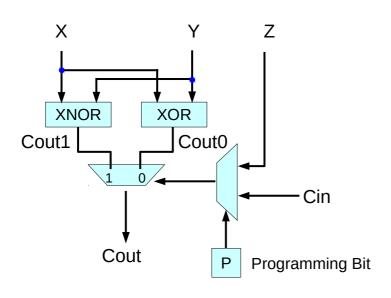

		Cin	Cin	
Χ	Υ	Cout1	Cout0	
0	0	1	0	$\overline{X} \overline{Y}$
0	1	0	1	$\overline{X}Y$
1	0	0	1	$X\overline{Y}$
1	1	1	0	ΧY


Cout1	Cout0	Cout	Name
0	0	0	Kill
0	1	Cin	Inverse Propagate
1	0	Cin	Propagate
1	1	1	Generate


Computing Par	ity	
X ⊕ Y ⊕ Cin		
0 ⊕ 0 ⊕ Cin	Cin	
0 ⊕ 1 ⊕ Cin	Cin	
1 ⊕ 0 ⊕ Cin	Cin	
1 ⊕ 1 ⊕ Cin	Cin	

Cout1=1 when Cin=1
Cout0=0 when Cin=0
Cout = Cin propagate

Cout1=0 when Cin=1
Cout0=1 when Cin=0
Cout = Cin inverse propagate

Ripple Carry Chain

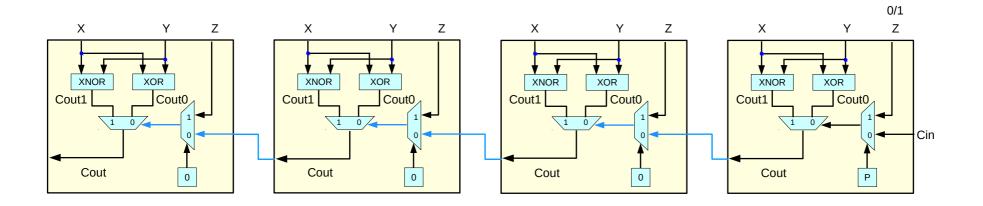

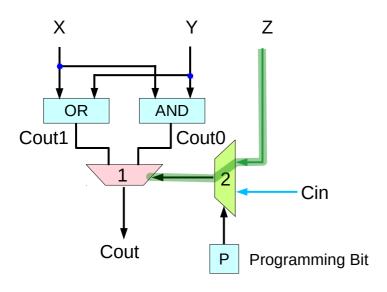


the logic cells - resources to compute a function the exact location of logic cells depends on the user. a user can start or end a carry computation at any place in an fpga.

to start a carry chain, the first cell in the chain must be programmed to ignore the Cin signal

program mux2 in the cell to route input Z to mux1 instead of Cin


When it is desired to have a carry input to the first cell of the chain (implementing combined adder/subtractors)

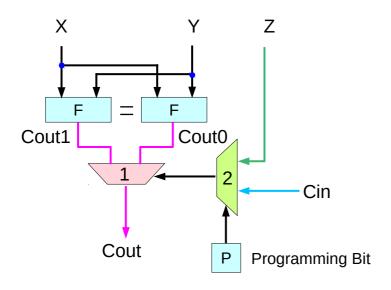But in many carry computations, the first cell has only 2 inputs, and forcing the carry chain to wait for the arrival of an additional, unnecessary input will only needlessly slow down the circuit's computation.



The first cell with only 2 inputs thus either 2-LUT in the cell could compute this value. if we program both 2-LUTs with the same function, he output will be forced to the proper value regardless of the input, and thus either the Cin or the Z can be routed to mux1 without changing the computation


Ripple Carry Chain

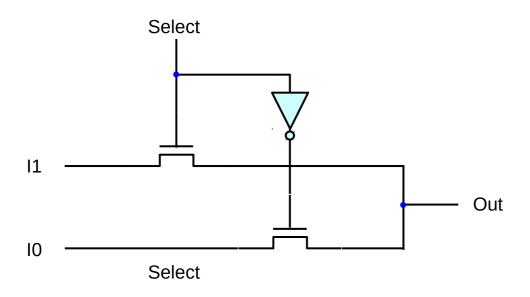

however, this is only true if mux1 is implemented such that if the two inputs to the mux are the same, the output of the mux is identical to the inputs regardless of the state of the select line

Fig1b shows an implementation of a mux that does not obey this requirement since the carry chain is part of an fpga, the input to this mux could be connected to some unused logic in another ow which is generating unknown values. if that unused logic had multiple transitions which caused the signal to change guicker than the gate could react, then it is possible that the select signal to this mux could be stuck midway between true and false (2.5V for 5V CMOS) in this case, it will not be able to pass a true value from the input to the output and thus will not function properly for this application.

Ripple Carry Chain

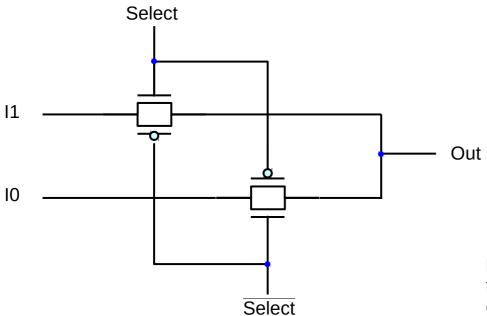

however a mux built like that in fig1c, with both n-transistor and p-transistor pass gates will operate properly for this case. thus, we will ssume throughout any other mux implementation with the same property could be used (including tristate driver based muxes which an restore signal drive and cut series RC chains)

however, this is only true if mux1 is implemented such that if the two inputs to the mux are the same, the output of the mux is identical to the inputs regardless of the state of the select line Fig1b shows an implementation of a mux that doesnot obey this requirement since the carry chain is part of an fpga, the input to this mux could be connected to some unsused logic in another ow which is generating unknown values. if that unused logic had multiple transitions which caused the signal to change quicker than the gate could react, then it is possible that the select signal to this mux could be stuck midway between true and false (2.5V for 5V CMOS) in this case, it will not be able to pass a true value from the input to the output and thus will not function properly for this application.

however a mux built like that in fig1c, with both n-transistor and p-transistor pass gates will operate properly for this case.

thus, we will ssume throughout any other mux implementation with the same property could be used (including tristate driver based muxes which an restore signal drive and cut series RC chains)

in an fgpa, the cells represent resources that can be used to compute arbitrary functions. however, the location of functions whithin this structure is completely up to the user. thus, a user may decide to start or end an carry computation at any place in the array. in order to start a carry chain we must program the first cell in the carry chain to ignore the Cin signal. one easy way to do this is to program mux2 in the cell to route input Z to mux1 instead of Cin for situations where one wishes to have carry input to the first stage of an adder (which is usual for implementing combined adder/subtractors as well oas other circuits) this is the right solution.


however, in other cases this may not be possible.

the first stage in many carry computations is only a 2-input function, and forcing the carry chain to wait for the arrival of an additional, unnecessary input will only needlessly slow down the circuit's computation. this is not necessary

in these circuits, the first stage is only a 2-input function.


thus, either 2-LUT in the cell could compute this value.

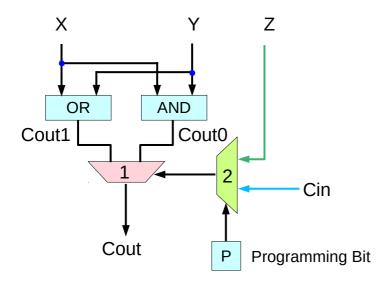
if we program both 2-LUTs with same function, the output will be forced to the proper value regardless of the input, and thus either the Cin or the Z signal can be routed to mux1 without changing the computation.




Significantly slower
Two muxes on the carry chain in each cell
Delay 1 for first cell
Delay 3 for each additional cell in the carry chain
1 delay for mux 2 and 2 delays for mux 1
Overall 2n-2 for an n-cell carry chain

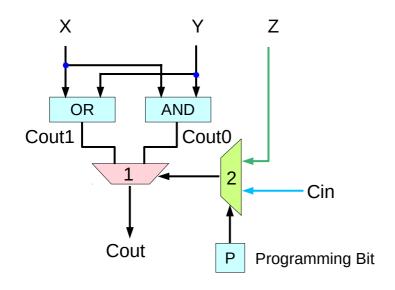The critical path comes from th 2-LUTs and not input Z Since the delay through the 2-LUTs will be larger than Through mux 2 in the first cell




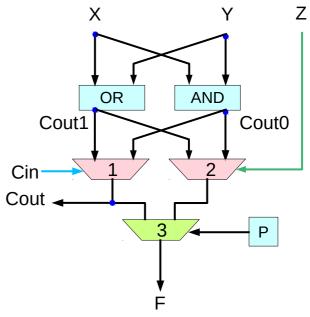

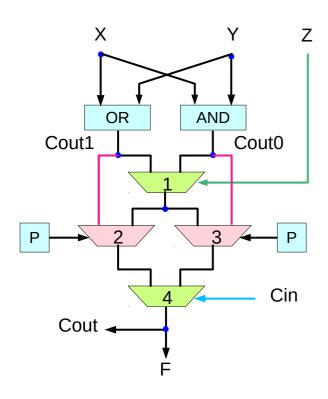- not logically equivalent
- no longer use the Z input in the <u>first</u> cell since Z is only attached to mux2 and mux 2 does not lead to the carry cells




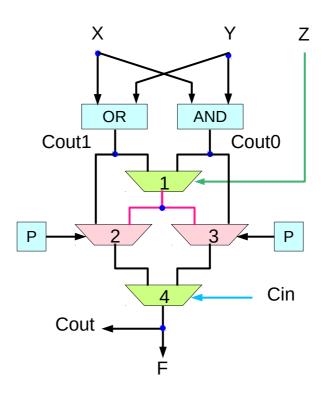for cells in the middle of a carry chain mux2 passes Cout1 mux3 passes Cout0 mux4 receives Cout1 and Cout0 provides a standard ripple carry path.



For the first cell in a carry chain with a carry input (provided by input Z), mux2 and mux3 both pass the value from mux1

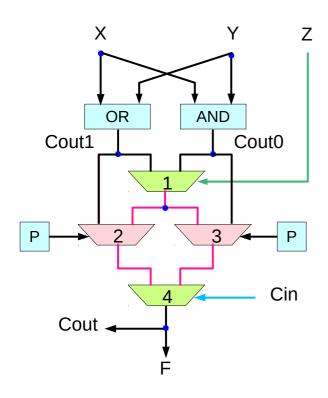
the two main inputs to mux4 are identical the output of mux4 (Cout) will be the same as the output of mux1 (ignoring Cin)




mux1's main inputs are driven by two 2-LUTs (OR, AND) controlled by X and Y mux1 forms a 3-LUT with the other 2-LUTs

When mux2 and mux3 pass the value from mux1 (Cout1 and Cout2 respectively) the circuit is configured to continue the carry chain


Functionally equivalent

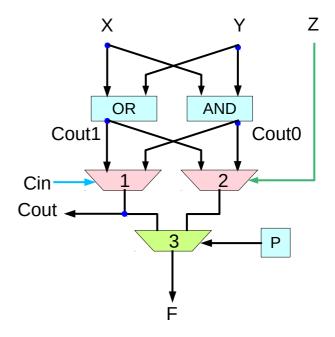


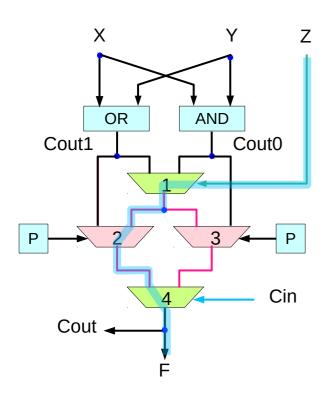

a delay of 3 in the first cell
(1 in mux1, 1 in mux2, 1 in mux4)
2 in all other cells in the carry chain
an total delay of 2n+1 for an n-bit carry chain

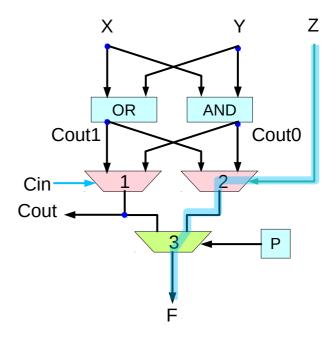1 gate delay slower than that of fig 2a, a carry input to the first cell is enabled



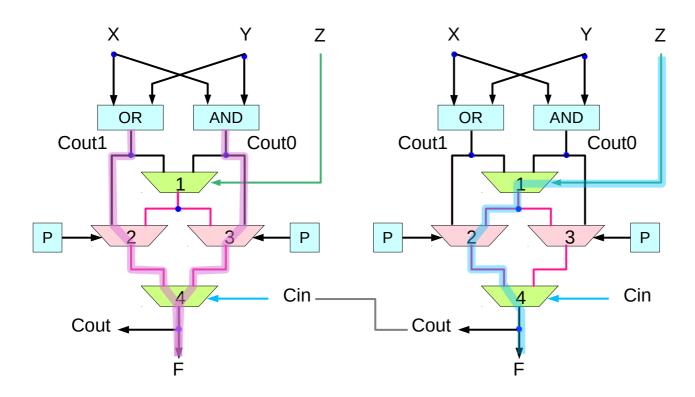



Also, for carry computations that do not need this feature, the first cell in a carry chain built from fig 2b can be configured to bypass mux1, reducing the overall delay to 2n, which is identical to that of fig2a.

High Performance Carry Chains for FPGAs, S. Hauck, M. M. Hosler, T. W. Fry

in order to implement a n-bit carry chain with a carry the design of fig 2a requires an additional cell at the beginning of the chain to bring in this input, resulting in a delay of 2(n+1)=2n+2, which is lower than that of the design in fig2b

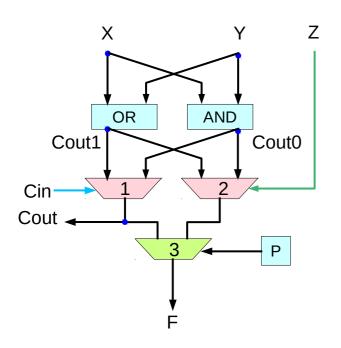
thus, the design of fig 2b is the preferrred ripple carry design among those presented so far



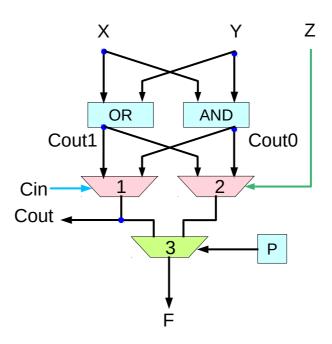

in order to implement a n-bit carry chain with a carry input the design of fig 2a requires an additional cell at the beginning of the chain to bring in this input, resulting in a delay of 2(n+1)=2n+2, which is lower than that of the design in fig2b

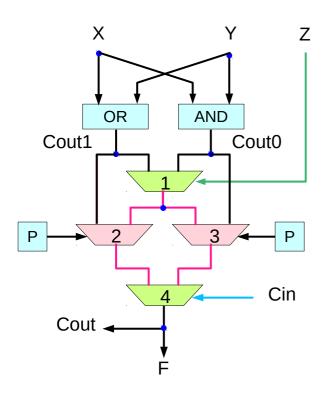thus, the design of fig 2b is the preferrred ripple carry design among those presented so far



a delay of 3 in the first cell (1 in mux1, 1 in mux2, 1 in mux4) 2 in all other cells in the carry chain an total delay of 2n+1 for an n-bit carry chain

t1 gate delay slower than that of fig 2a, a carry input to the first cell is enabled

Also, for carry computations that do not need this feature, the first cell in a carry chain built from fig 2b can be configured to bypass mux1, reducing the overall delay to 2n, which is identical to that of fig2a.


in order to implement a n-bit carry chain with a carry input, the design of fig 2a requires an additional cell at the beginning of the chain to bring in this input, resulting in a delay of 2(n+1)=2n+2, which is lower than that of the design in fig2b


thus, the design of fig 2b is the preferrred ripple carry design among those presented so far


However, carry chains built from this design have a delay of 3 in the first cell (1 in mux1, 1 in mux2, 1 in mux4) and 2 in all other cells in the carry chain, yielding an overall delay of 2n+1 for an n-bit carry chain. thus, although this design is 1 gate delay slower than that of fig 2a, it provides the ability to have a carry input to the first cell in a carry chain, something that is important in many computations.


Also, for carry computations that do not need this feature, the first cell in a carry chain built from fig 2b can be configured to bypass mux1, reducing the overall delay to 2n, which is identical to that of fig2a.

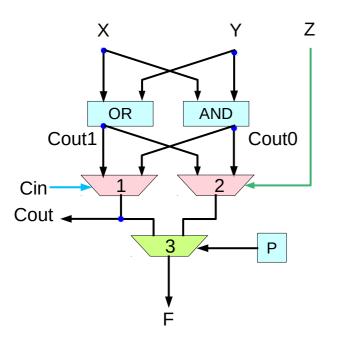on the other hand, in order to implment a n-bit carry chain with a carry input, the designof fig 2a requires an additional cell at the beginning of the chain to bring in this input, resulting in a delay of 2(n+1)=2n+2, which is lower than that of the design in fig2b thus, the design of fig 2b is the preferrred ripple carry design among those presented so far




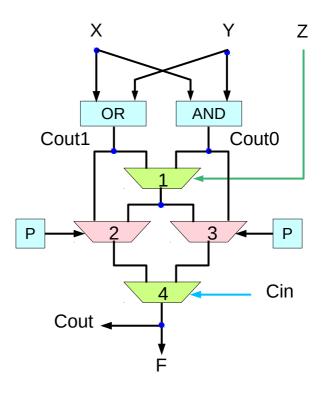

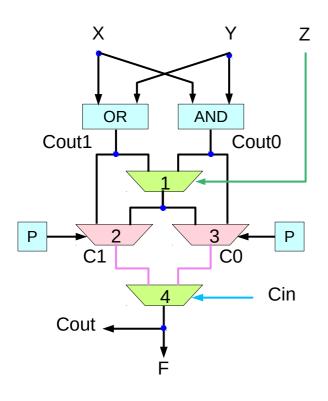

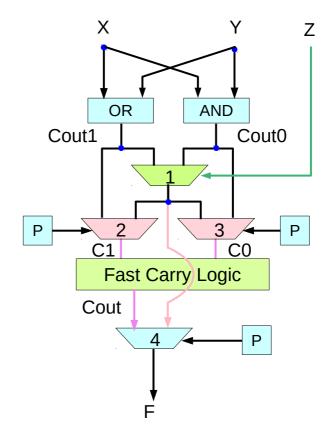
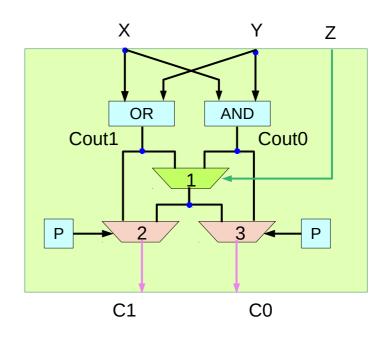
$$Cout_i = (Cout_{i-1} \cdot C1_i) + (\overline{Cout_{i-1}} \cdot C0_i)$$




$$Cout_i = (Cout_{i-1} \cdot C1_i) + (\overline{Cout_{i-1}} \cdot C0_i)$$


Fast Carry Logc

Carry Select Adder
Carry Lookahead Adder
Brent-Kung
Variable Block
Ripple Carry Adder

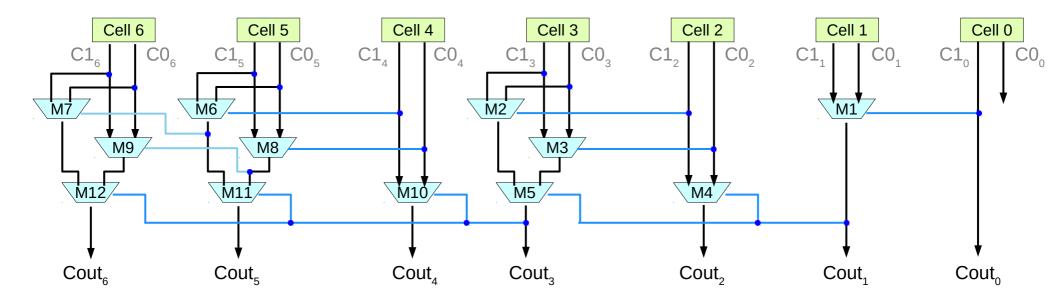https://en.wikipedia.org/wiki/Carry-lookahead_adder


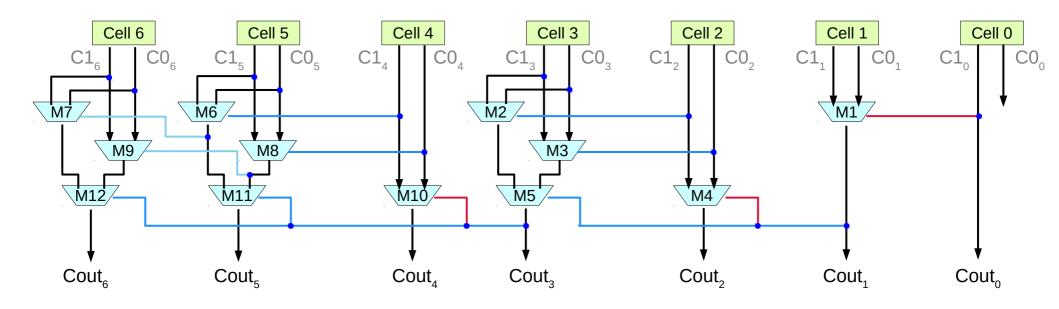
$$Cout_i = (Cout_{i-1} \cdot C1_i) + (\overline{Cout_{i-1}} \cdot C0_i)$$




$$Cout_i = (Cout_{i-1} \cdot C 1_i) + (\overline{Cout_{i-1}} \cdot C 0_i)$$

$$Cout_1 = (Cout_0 \cdot C1_1) + (\overline{Cout_0} \cdot C0_1)$$

$$Cout_1 = (C 1_0 \cdot C 1_1) + (\overline{C} 1_0 \cdot C 0_1)$$

$$Cout_{i+1} = (Cout_i \cdot C 1_{i+1}) + (\overline{Cout_i} \cdot C 0_{i+1})$$

$$Cout_{i+1} = \left(\left[\left(Cout_{i-1} \cdot C \, \mathbf{1}_i\right) + \left(\overline{Cout_{i-1}} \cdot C \, \mathbf{0}_i\right)\right] \cdot C \, \mathbf{1}_{i+1}\right) + \left(\overline{\left[\left(Cout_{i-1} \cdot C \, \mathbf{1}_i\right) + \left(\overline{Cout_{i-1}} \cdot C \, \mathbf{0}_i\right)\right]} \cdot C \, \mathbf{0}_{i+1}\right) + \left(\overline{Cout_{i-1}} \cdot C \, \mathbf{0}_i\right) + \left(\overline{$$

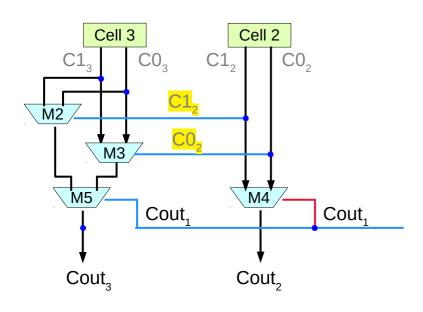


$$(C1_3 C1_2 + C0_3 \overline{C1}_2)Cout_1 + (C1_3 C0_2 + C0_3 \overline{C0}_2)\overline{Cout}_1$$

$$\begin{split} &Cout_{i} = \left(Cout_{i-1} \cdot C \cdot \mathbf{1}_{i}\right) + \left(\overline{Cout_{i-1}} \cdot C \cdot \mathbf{0}_{i}\right) \\ &Cout_{i+1} = \left(Cout_{i} \cdot C \cdot \mathbf{1}_{i+1}\right) + \left(\overline{Cout_{i}} \cdot C \cdot \mathbf{0}_{i+1}\right) \\ &Cout_{2} = \left(Cout_{1} \cdot C \cdot \mathbf{1}_{2}\right) + \left(\overline{Cout_{1}} \cdot C \cdot \mathbf{0}_{2}\right) \\ &Cout_{3} = \left(Cout_{2} \cdot C \cdot \mathbf{1}_{3}\right) + \left(\overline{Cout_{2}} \cdot C \cdot \mathbf{0}_{3}\right) \\ &= \left(\left(\left(Cout_{1} \cdot C \cdot \mathbf{1}_{2}\right) + \left(\overline{Cout_{1}} \cdot C \cdot \mathbf{0}_{2}\right)\right) \cdot C \cdot \mathbf{1}_{3}\right) \\ &+ \left(\left(\left(Cout_{1} \cdot C \cdot \mathbf{1}_{2}\right) + \left(\overline{Cout_{1}} \cdot C \cdot \mathbf{0}_{2}\right)\right) \cdot C \cdot \mathbf{0}_{3}\right) \\ &= \left(C \cdot \mathbf{1}_{3} C \cdot \mathbf{1}_{2} Cout_{1} + C \cdot \mathbf{1}_{3} C \cdot \mathbf{0}_{2} \overline{Cout_{1}}\right) \\ &\left(\left(\left(\overline{Cout_{1}} \cdot C \cdot \mathbf{1}_{2}\right) \cdot \left(\overline{Cout_{1}} \cdot C \cdot \mathbf{0}_{2}\right)\right) \cdot C \cdot \mathbf{0}_{3}\right) \\ &= \left(\left(\left(\overline{Cout_{1}} + \overline{C \cdot \mathbf{1}_{2}}\right) \cdot \left(\overline{Cout_{1}} + \overline{C \cdot \mathbf{0}_{2}}\right)\right) \cdot C \cdot \mathbf{0}_{3}\right) \\ &= \left(\overline{Cout_{1}} Cout_{1} + \overline{C \cdot \mathbf{1}_{2}} Cout_{1} + \overline{Cout_{1}} \overline{C \cdot \mathbf{0}_{2}} + \overline{C \cdot \mathbf{1}_{2}} \overline{C \cdot \mathbf{0}_{2}}\right) \cdot C \cdot \mathbf{0}_{3} \\ &= \left(\overline{C \cdot \mathbf{1}_{2}} Cout_{1} + \overline{C \cdot \mathbf{0}_{2}} \overline{Cout_{1}}\right) \cdot C \cdot \mathbf{0}_{3} \\ &= \left(\overline{C \cdot \mathbf{1}_{2}} Cout_{1} + \overline{C \cdot \mathbf{0}_{2}} \overline{Cout_{1}}\right) \cdot C \cdot \mathbf{0}_{3} \\ &= \left(\overline{C \cdot \mathbf{0}_{3}} \overline{C \cdot \mathbf{1}_{3}} Cout_{1} + C \cdot \mathbf{0}_{3} \overline{C \cdot \mathbf{0}_{3}} \overline{Cout_{1}}\right) \end{split}$$


High Performance Carry Chains for FPGAs, S. Hauck, M. M. Hosler, T. W. Fry

33

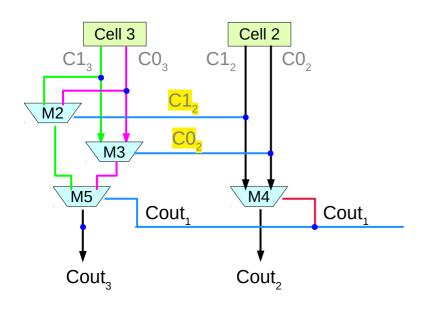

$$(C1_3C1_2 + C0_3\overline{C1}_2)Cout_1 + (C1_3C0_2 + C0_3\overline{C0}_2)\overline{Cout}_1$$

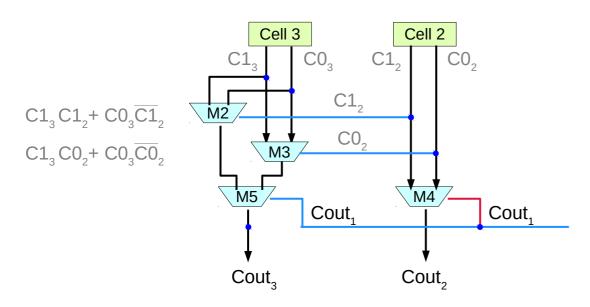
$$\begin{split} &= (\overline{Cout_1}\overline{Cout_1} + \overline{C1_2}Cout_1 + \overline{Cout_1}\overline{C0_2} + \overline{C1_2}\overline{C0_2}) \cdot C0_3 \\ &= (\overline{C1_2}Cout_1 + \overline{C0_2}\overline{Cout_1}) \cdot C0_3 \\ &= (C0_3\overline{C1_2}Cout_1 + C0_3\overline{C0_2}\overline{Cout_1}) \end{split}$$



$$(C1_3 C1_2 + C0_3 \overline{C1}_2)Cout_1 + (C1_3 C0_2 + C0_3 \overline{C0}_2)\overline{Cout}_1$$

$$= C1_3 \cdot (C1_2 Cout_1 + C0_2 \overline{Cout_1})$$

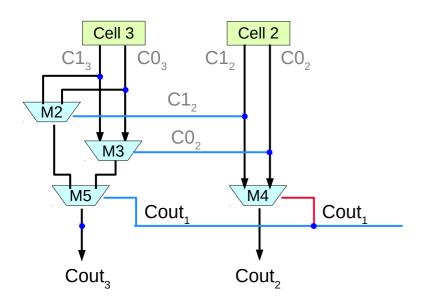+ $C0_3 \cdot (\overline{C1_2} Cout_1 + \overline{C0_2} \overline{Cout_1})$



$$\begin{split} Cout_{i} &= \left(Cout_{i-1} \cdot C \, \mathbf{1}_{i}\right) + \left(\overline{Cout_{i-1}} \cdot C \, \mathbf{0}_{i}\right) \\ Cout_{i+1} &= \left(Cout_{i} \cdot C \, \mathbf{1}_{i+1}\right) + \left(\overline{Cout_{i}} \cdot C \, \mathbf{0}_{i+1}\right) \\ \\ Cout_{i+1} &= \left(\left[\left(Cout_{i-1} \cdot C \, \mathbf{1}_{i}\right) + \left(\overline{Cout_{i-1}} \cdot C \, \mathbf{0}_{i}\right)\right] \cdot C \, \mathbf{1}_{i+1}\right) \\ \\ &+ \left(\overline{\left[\left(Cout_{i-1} \cdot C \, \mathbf{1}_{i}\right) + \left(\overline{Cout_{i-1}} \cdot C \, \mathbf{0}_{i}\right)\right]} \cdot C \, \mathbf{0}_{i+1}\right) \end{split}$$

References

- [1] http://en.wikipedia.org/
- [2] J-P Deschamps, et. al., "Sunthesis of Arithmetic Circuits", 2006