

Capacitor


Copyright (c) 2011 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".

Please send corrections (or suggestions) to youngwlim@hotmail.com.

This document was produced by using OpenOffice and Octave.

Charge

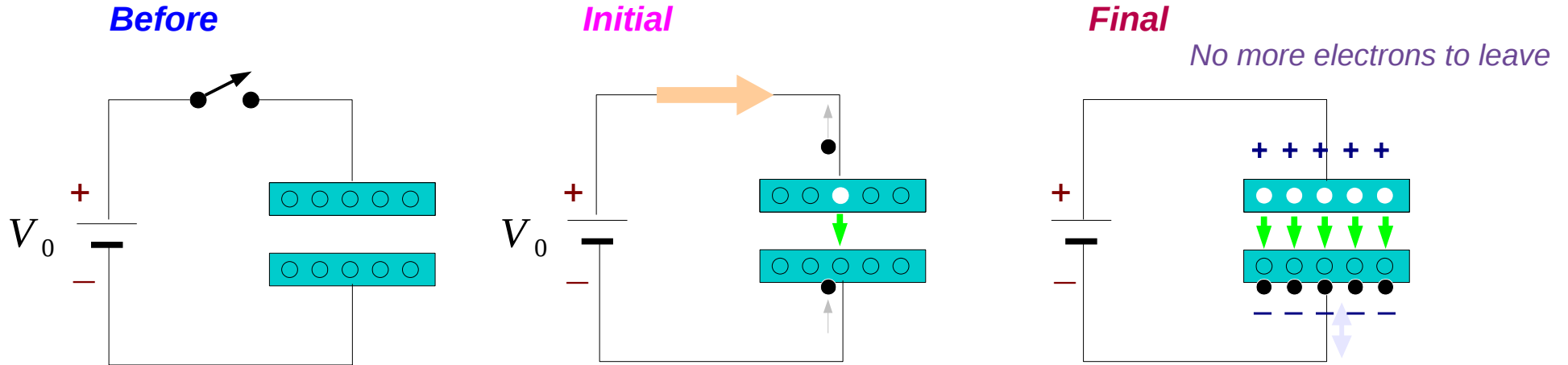

$$i_c = C \cdot \frac{d v_c}{d t}$$

$$v_c(0^-) = v_c(0^+) \quad \text{unyielding voltage}$$

$$i_c(0^-) \neq i_c(0^+) \quad \text{current jump}$$


crowded electrons prevent other electrons from arriving

Energy stored in Electric Field


$$v_c(\infty) = V_0$$

$$i_c(\infty) = 0$$


Discharge

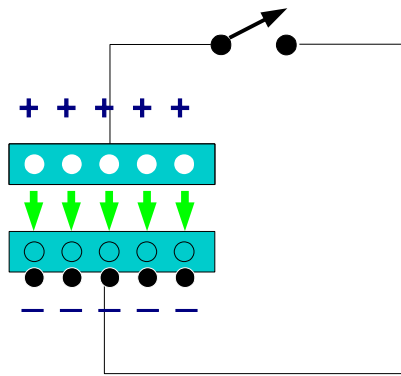

Initial

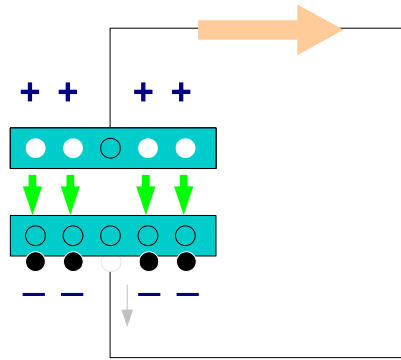

Final

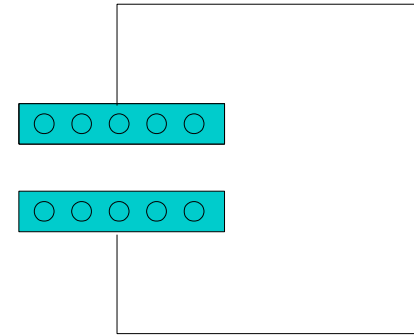

No more electrons moving

$$i_c = C \cdot \frac{dv_c}{dt}$$


$$v_c(0^-) = v_c(0^+) \quad \text{unyielding voltage}$$

$$i_c(0^-) \neq i_c(0^+) \quad \text{current jump}$$

$$v_c(\infty) = 0$$

$$i_c(\infty) = 0$$

Charge


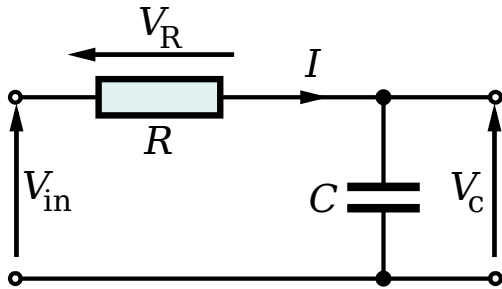


$$i_c = C \cdot \frac{d v_c}{d t}$$



unyielding voltage

current jump

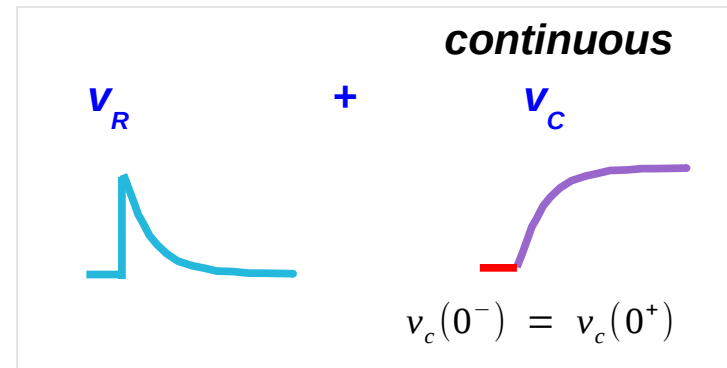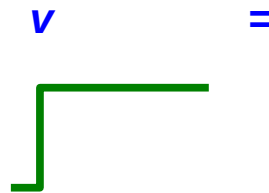
the capacitor voltage slowly follows the shape of the applied step input voltage



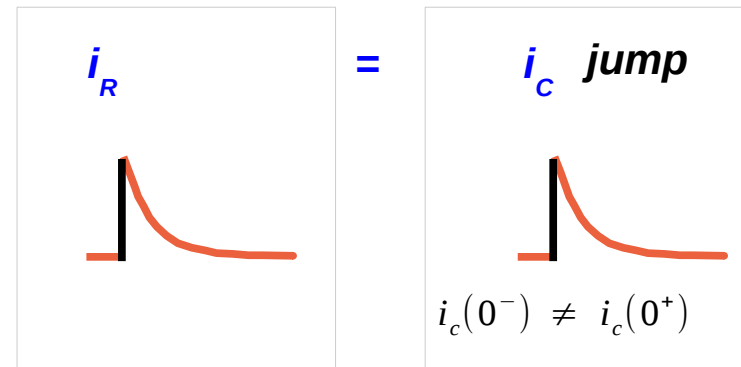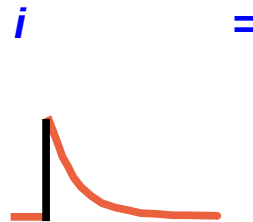the capacitor current changes abruptly by the applied step input voltage and then slowly becomes zero



Discharge


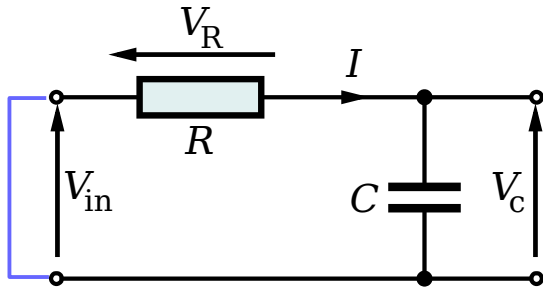


$$i_c = C \cdot \frac{d v_c}{d t}$$



unyielding voltage

current jump

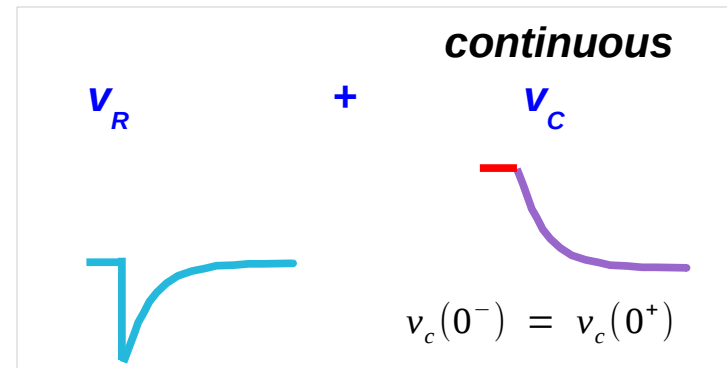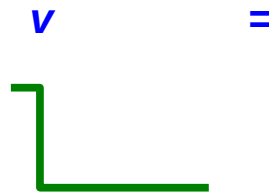
the capacitor voltage slowly follows the the shape of the applied step input voltage



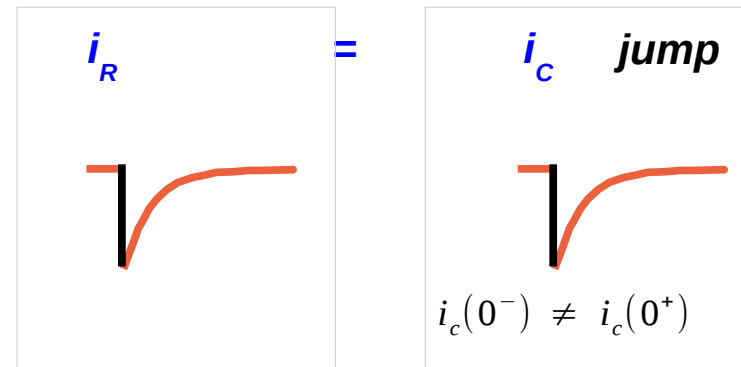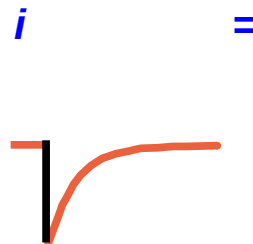
the capacitor current changes abruptly by the applied step input voltage and then slowly becomes zero



Pulse


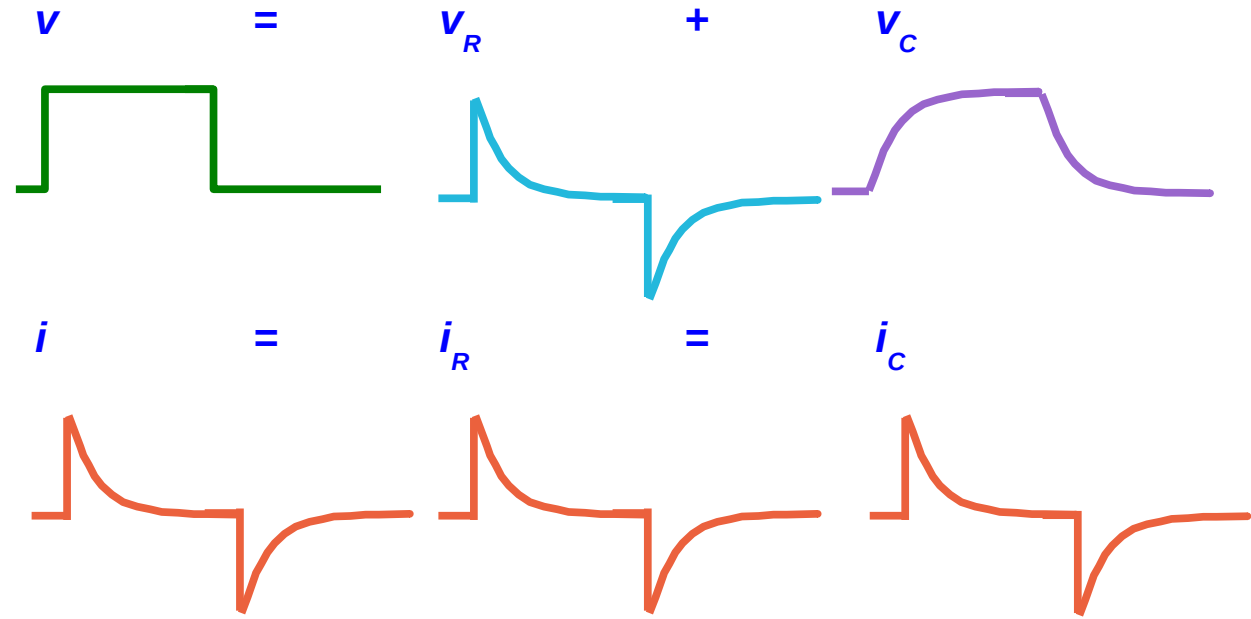


Pulse

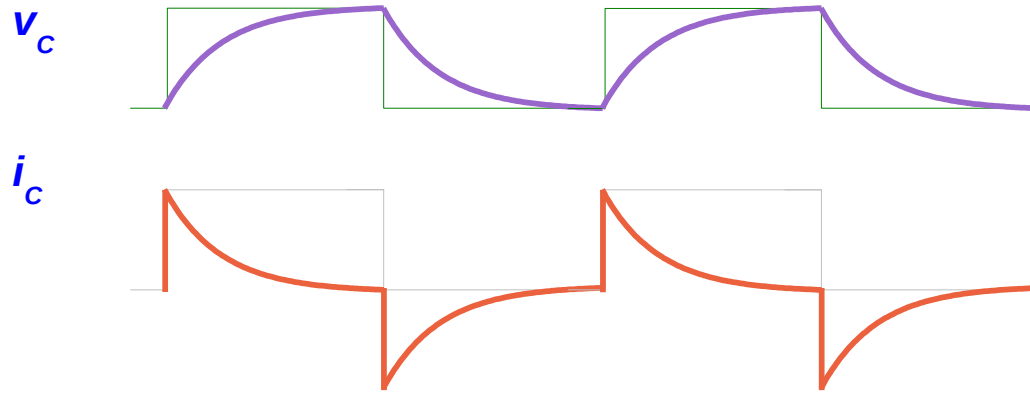


$$i_c = C \frac{dv_c}{dt}$$


ω ↑ i_c ↑ X_c ↓

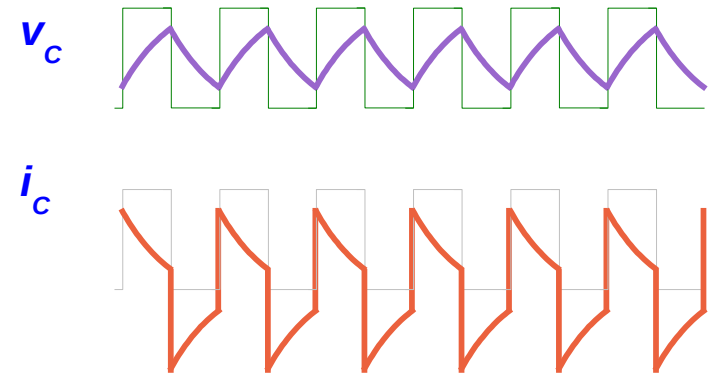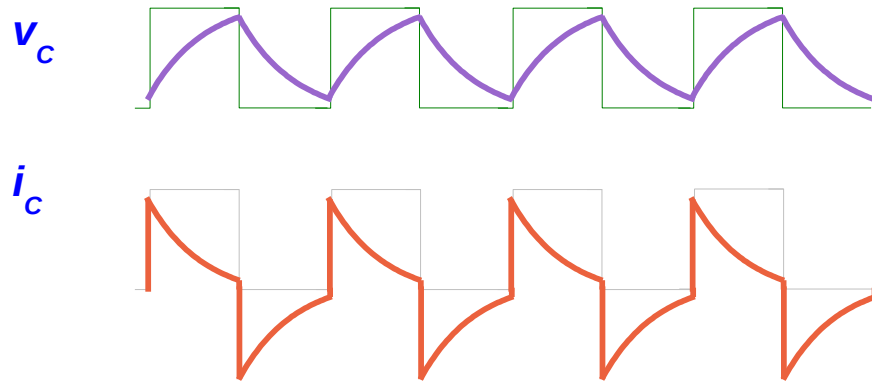


Everchanging signal pairs

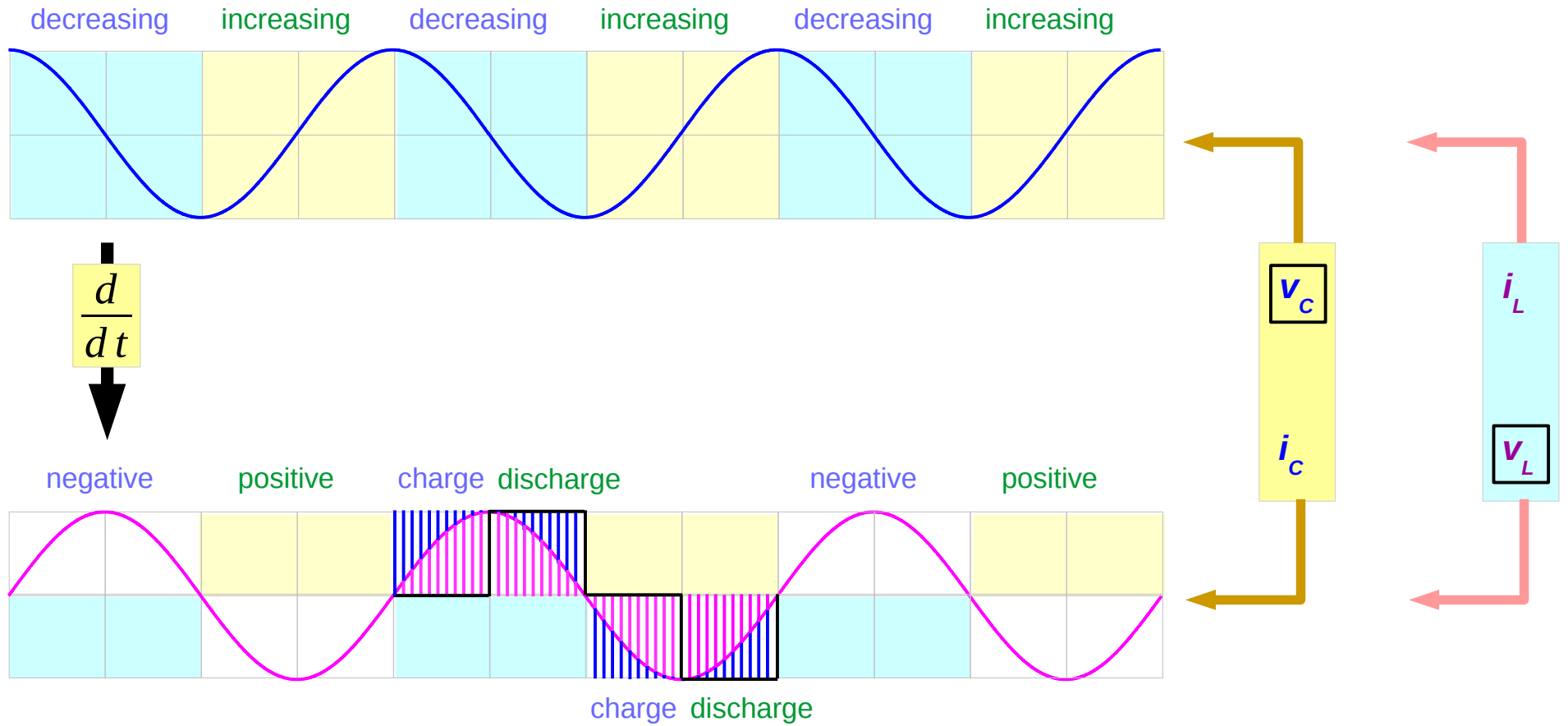

Capacitor Current

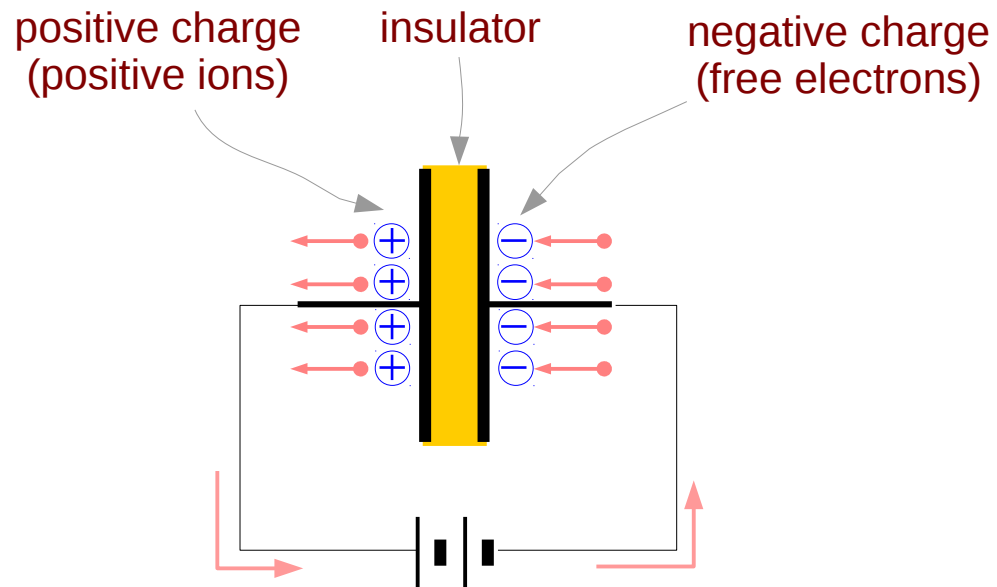

Think as electrons move to the left

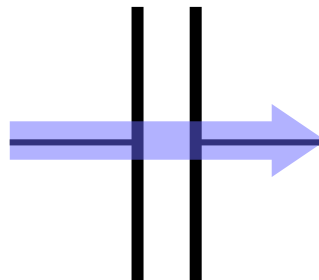


Displacement Current

Continuous Charging and Discharging Operations


Incremental Voltage Increment → Continuous Charging

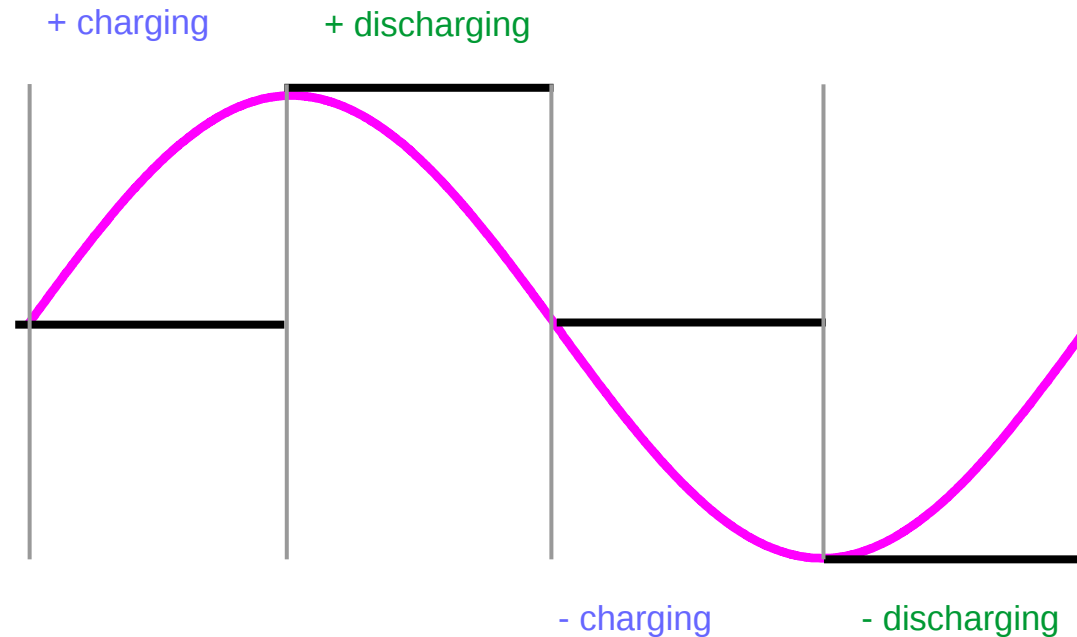Incremental Voltage Decrement → Continuous Discharging




Fully Charged and Fully Discharged

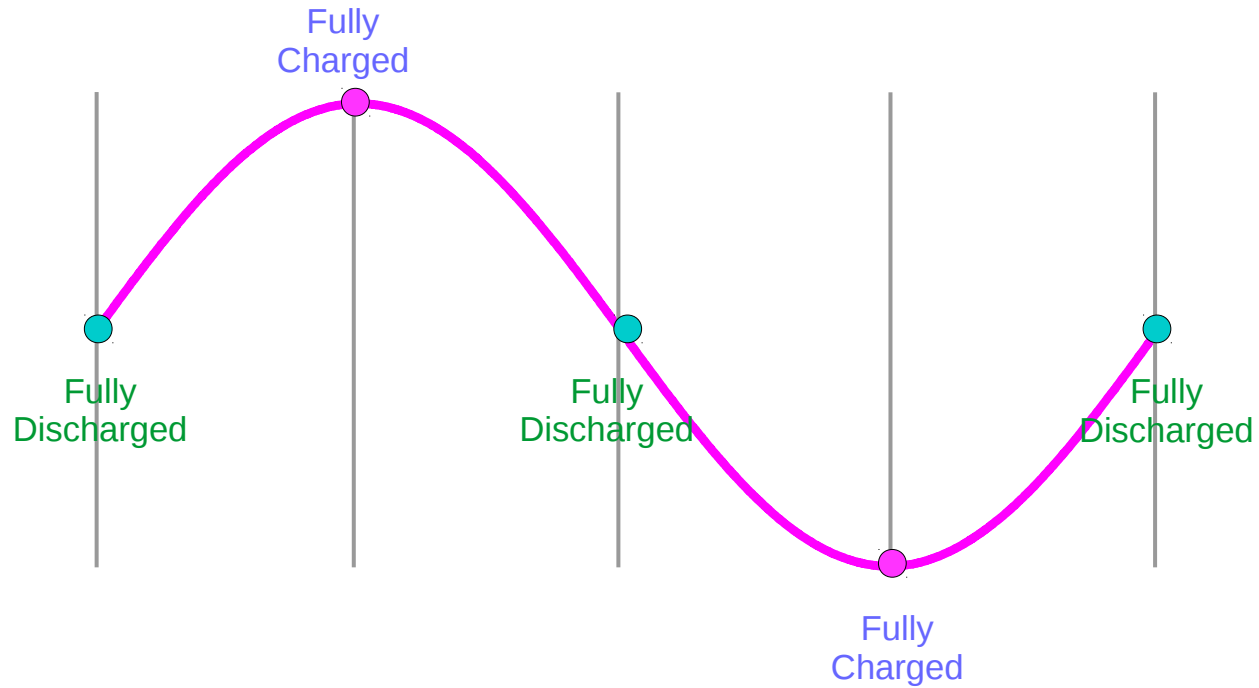Incremental Voltage Increment → Continuous Charging
Incremental Voltage Decrement → Continuous Discharging




Fully Charged and Fully Discharged

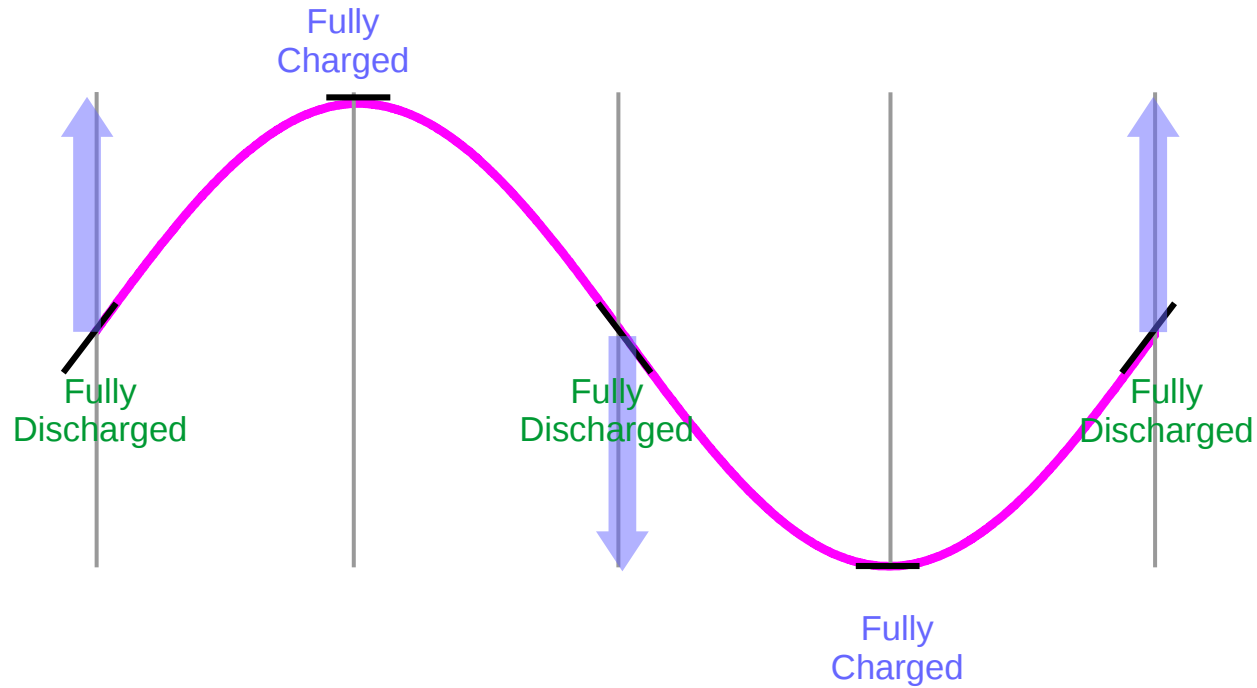
Incremental Voltage Increment → Continuous Charging
Incremental Voltage Decrement → Continuous Discharging



Everchanging signal pairs

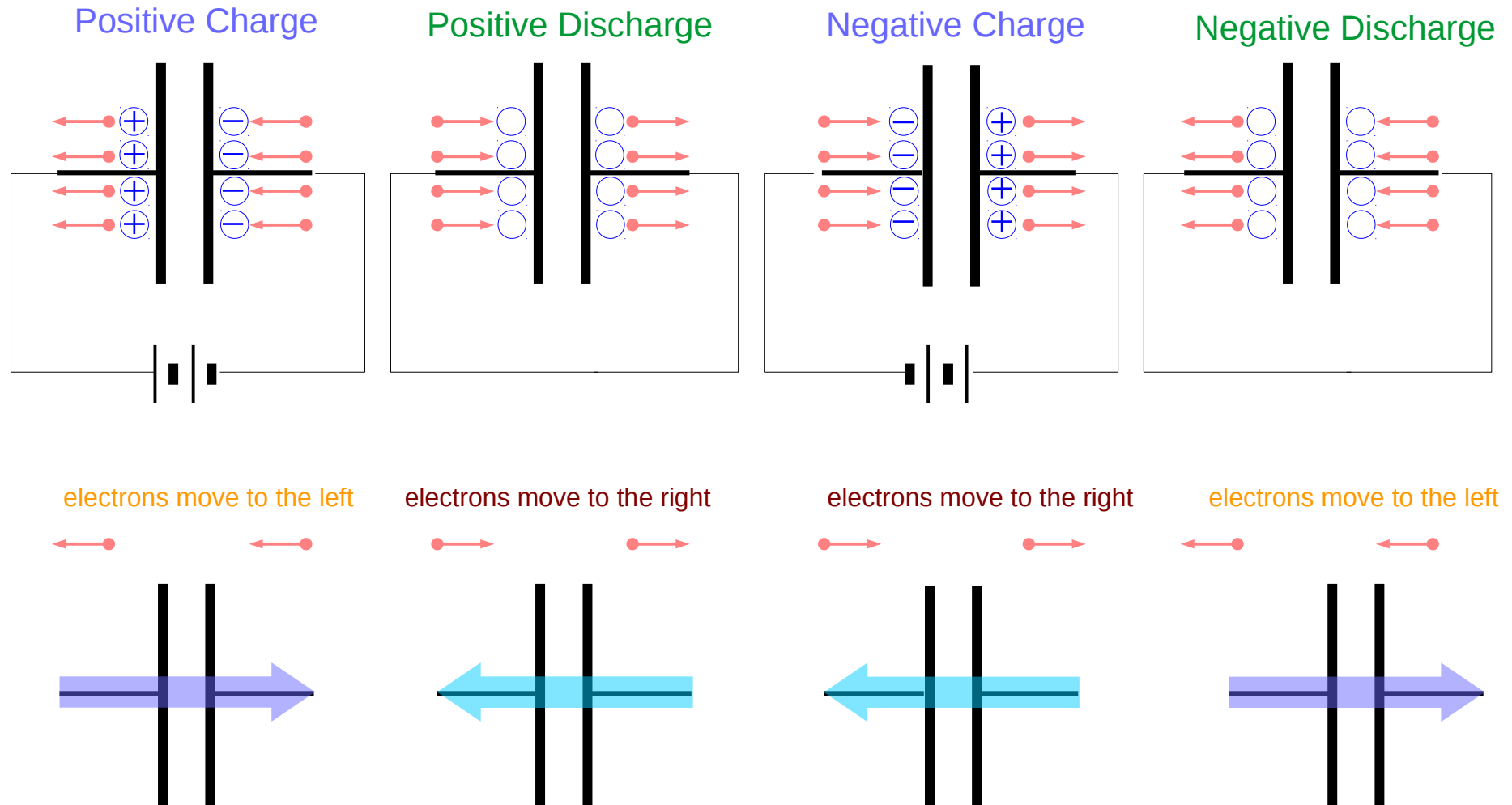


Everchanging signal pairs

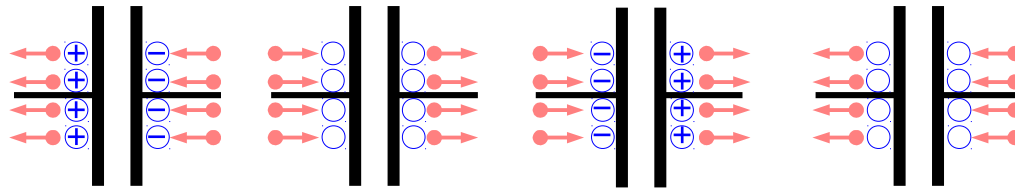


charge

discharge

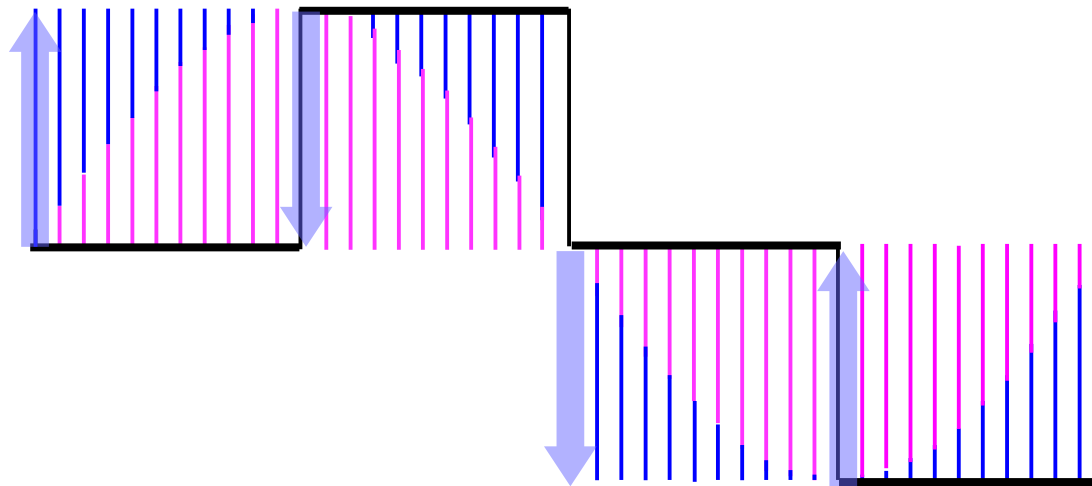


charge

discharge

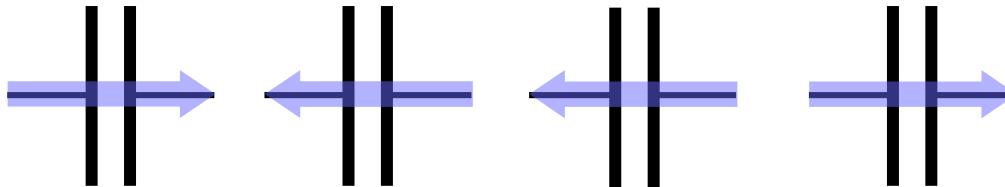


Everchanging signal pairs

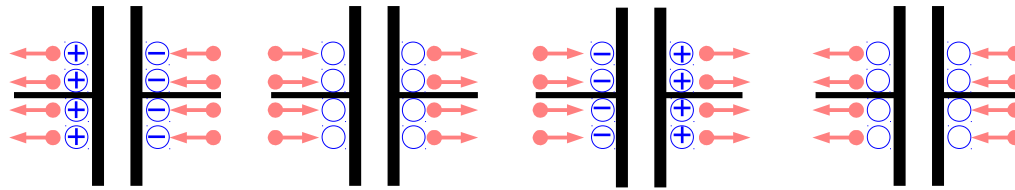


charge

discharge

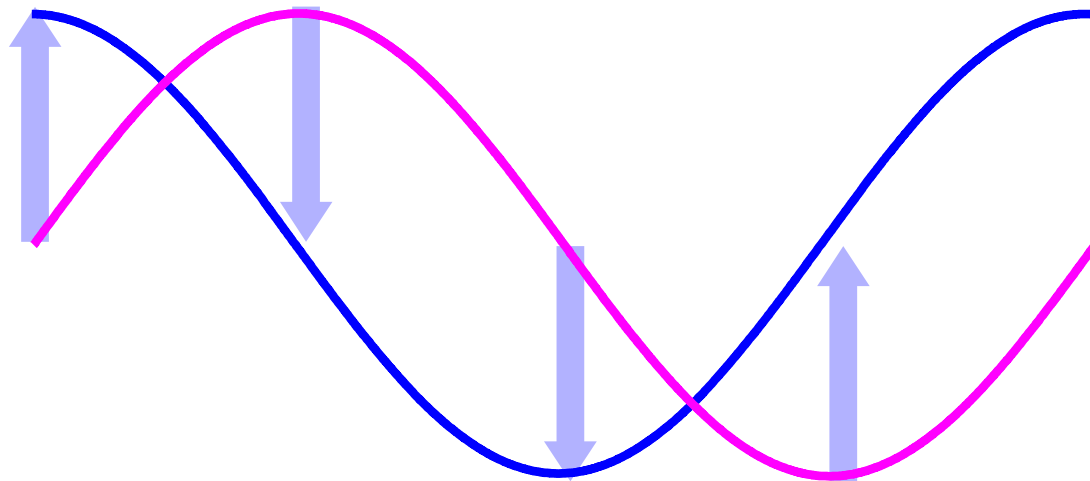


charge


discharge

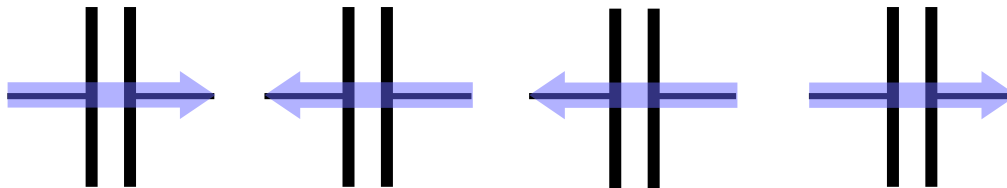

Everchanging signal pairs

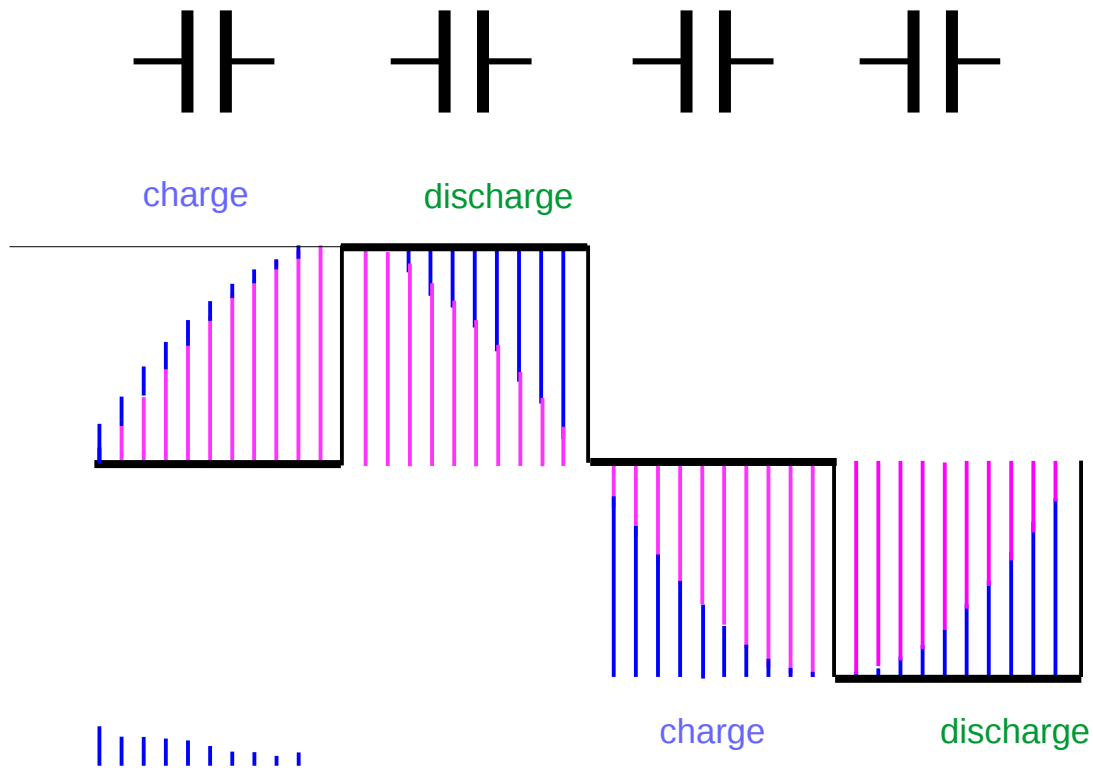


Everchanging signal pairs

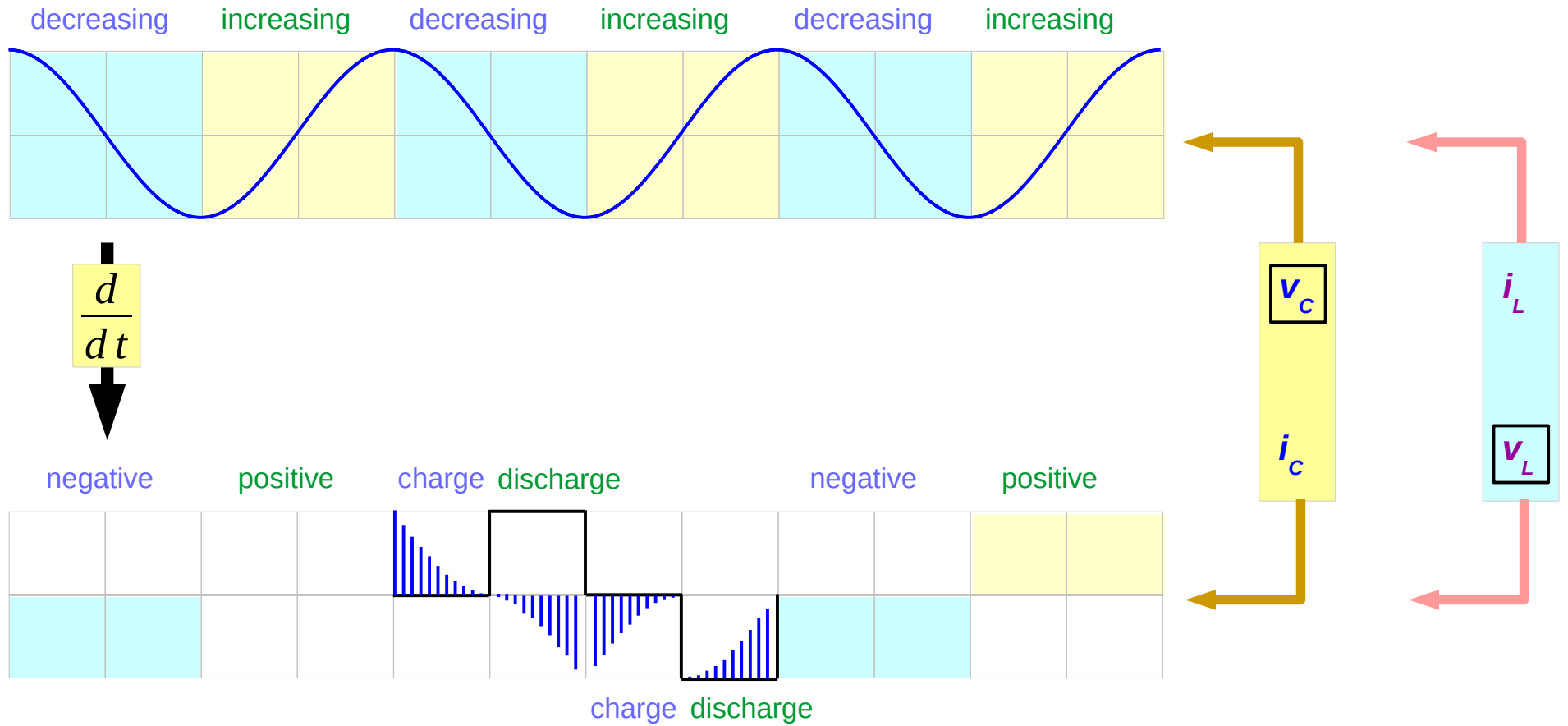

I leads V by 90°

*Initial
charge*

 


SHORT

V = 0

I : peak


*Full
charge*

 

OPEN

I = 0

V : peak

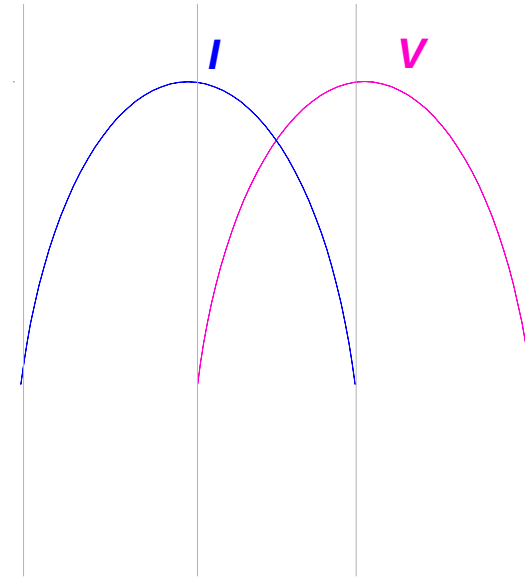

References

[1] <http://en.wikipedia.org/>

[2] J.H. McClellan, et al., Signal Processing First, Pearson Prentice Hall, 2003