

BJT Amplifier ac Model (H.10)

20170619

Copyright (c) 2016 - 2017 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".

References

Based

[1] Floyd, Electronic Devices 7th ed

[2] Cook,

[2] en.wikipedia.org

α_{ac} ac alpha (I_c / I_e)

β_{ac} ac beta (I_c / I_b)

r_e' ac emitter resistance

r_b' ac base resistance

r_c' ac collector resistance


$$I_c = \alpha_{ac} I_e$$

$$I_c = \beta_{ac} I_b$$

$$V_{BQ} + V_b$$




$$I_B + I_b$$

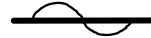

$$I_b$$



$$V_{CEQ} + V_{ce}$$

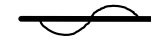

$$\beta_{ac}$$



$$I_{CQ} + I_c$$



$$I_c$$




r-parameter Equivalent Circuit




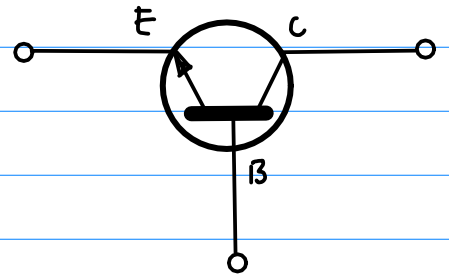
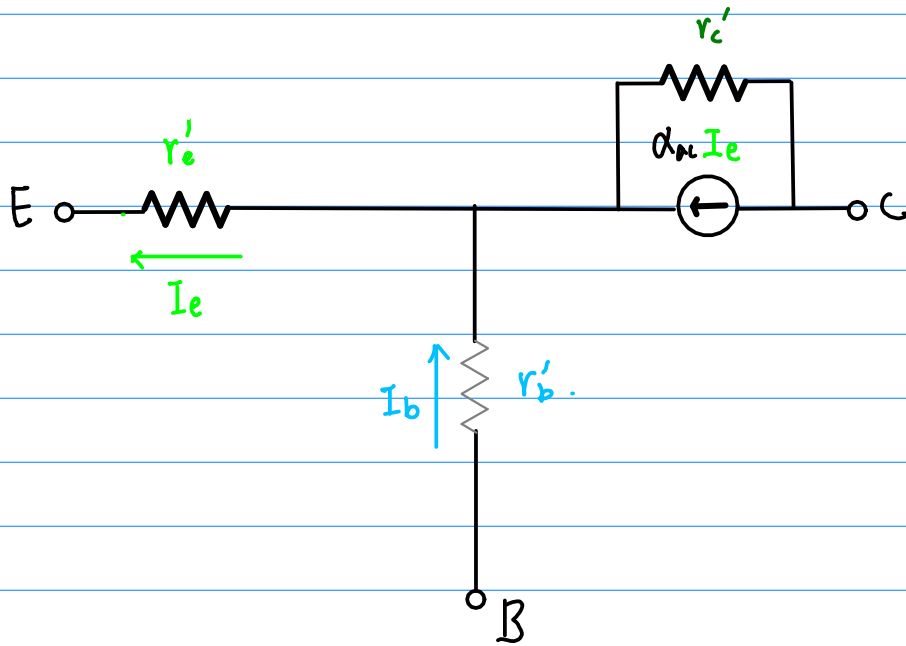




r_b' : small enough to neglect

r_c' : large " " " (a few 100k Ω)

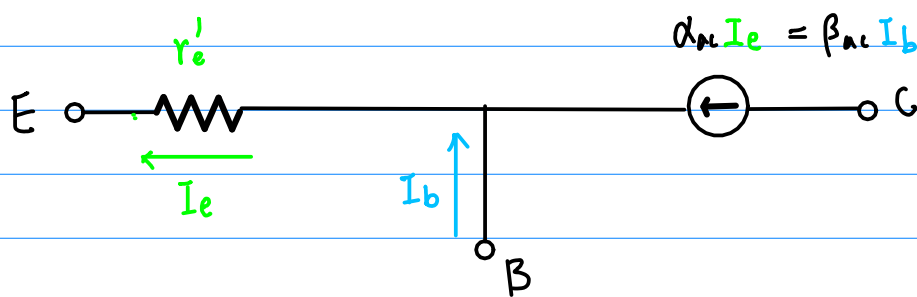

t model

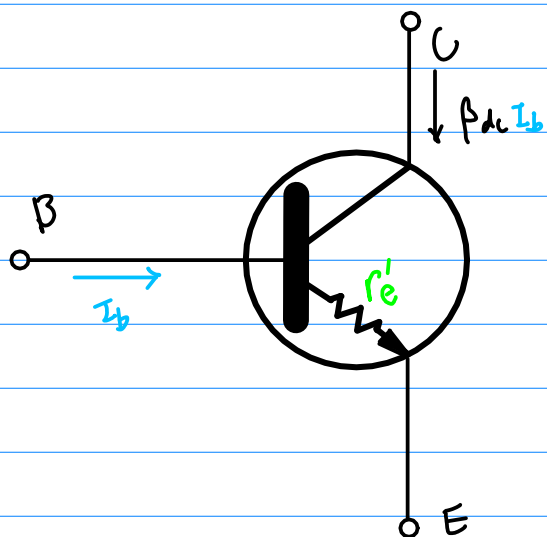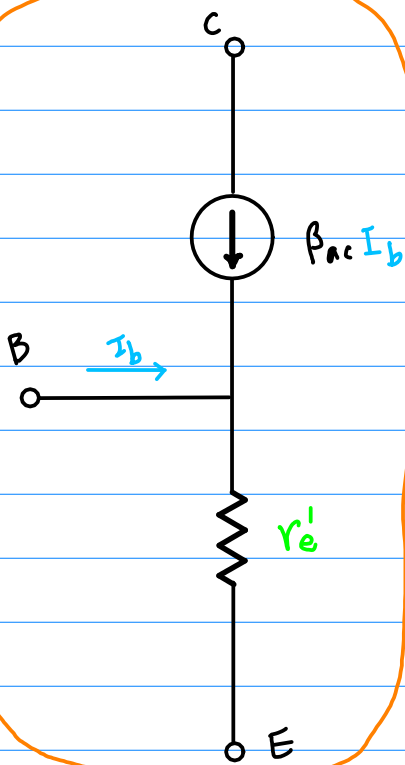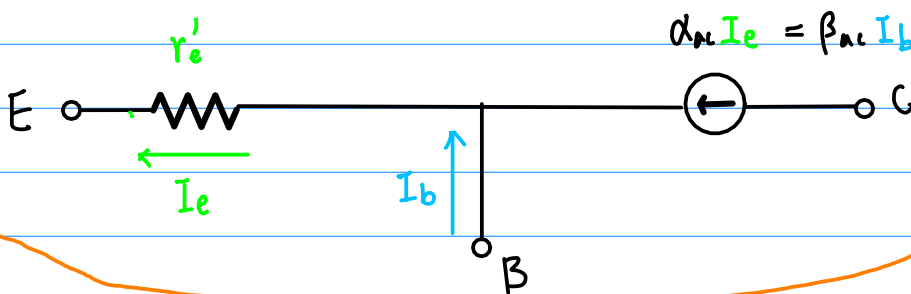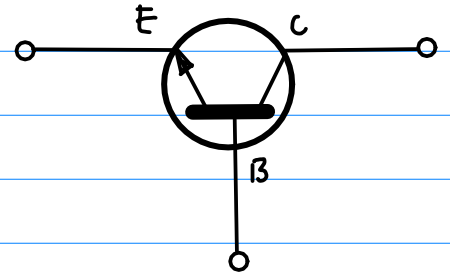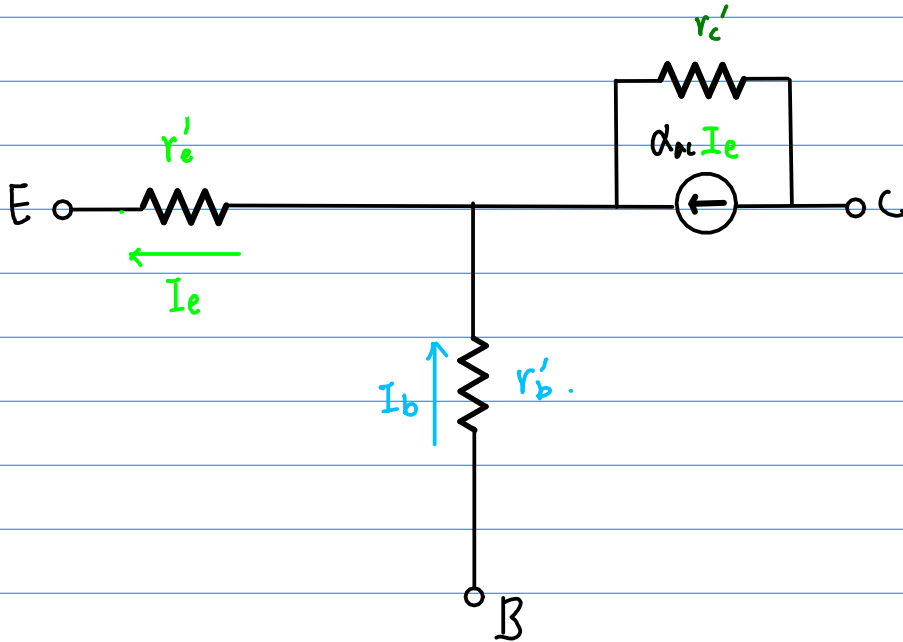

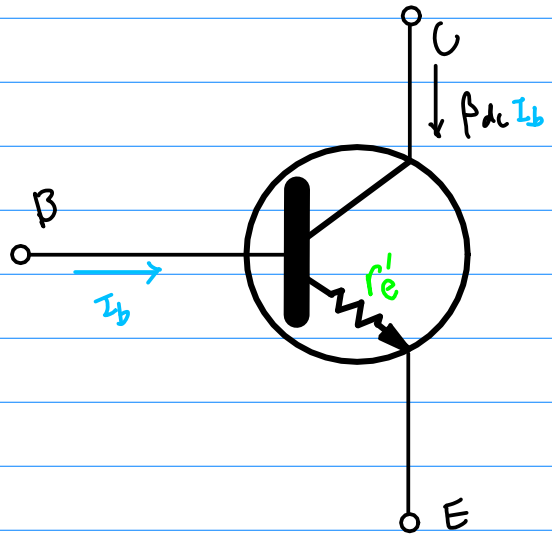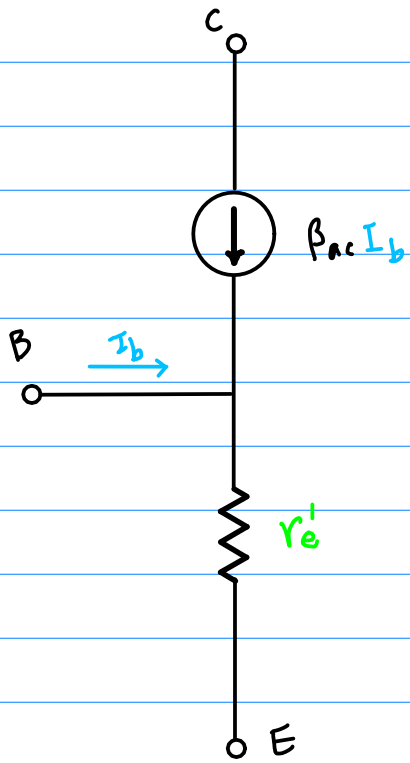

h parameters

h_i	Input Impedance (resistance)	Output shorted
h_r	Voltage Feedback Ratio	Input Open
h_f	Forward Current Gain	Output shorted
h_o	Output Admittance (conductance)	Input Open

Common Emitter

Common Base

Common Collector

h_{ie}

h_{ib}

h_{ic}

h_{re}

h_{rb}

h_{rc}

h_{fe}

h_{fb}

h_{fc}

h_{oe}

h_{ob}

h_{oc}

$$\alpha_{ac} = h_{fb}$$

$$\beta_{ac} = h_{fe}$$

$$r'_e = \frac{h_{re}}{h_{oe}}$$


$$r'_c = \frac{h_{re} + 1}{h_{oe}}$$


$$r'_b = h_{ic} - \frac{h_{re}}{h_{oe}} (1 + h_{fe})$$

Variations in h_{FE} (Current Gain)


$$\beta_{DC} = h_{FE} \quad 100 \sim 300$$

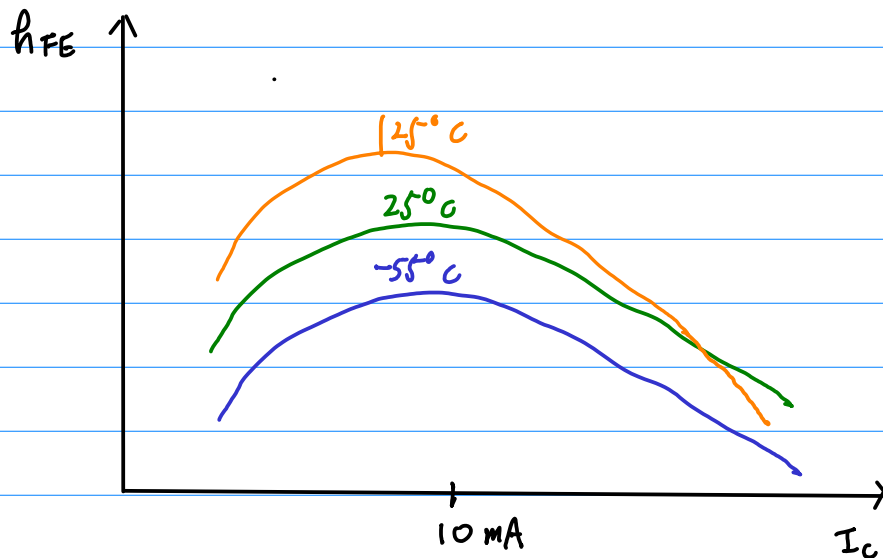- individual transistors
- temperature
- I_C





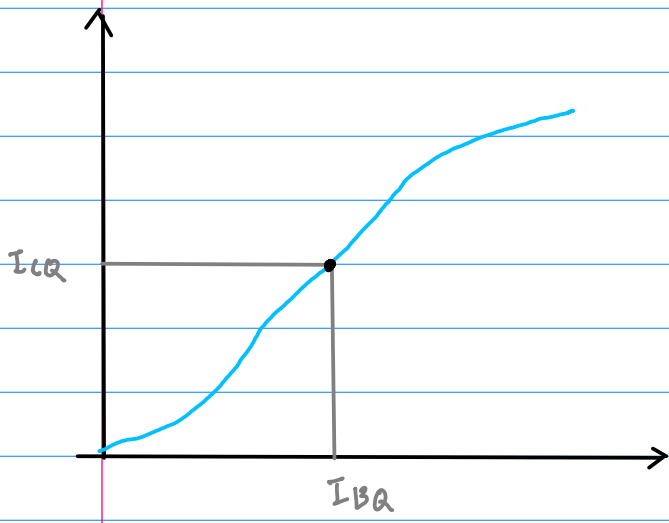



$$\beta_{DC} = \frac{I_C}{I_B}$$


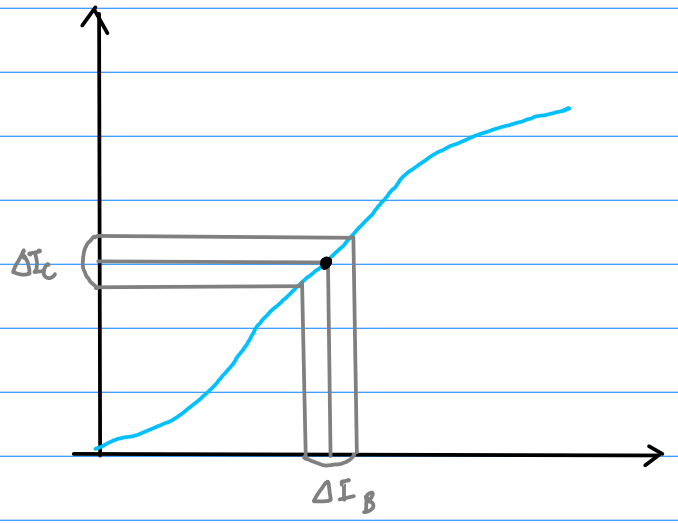

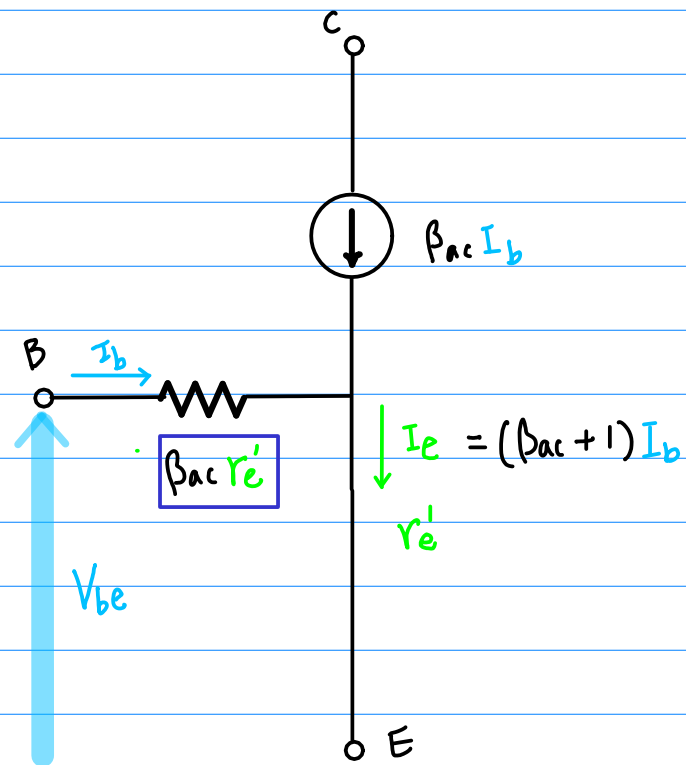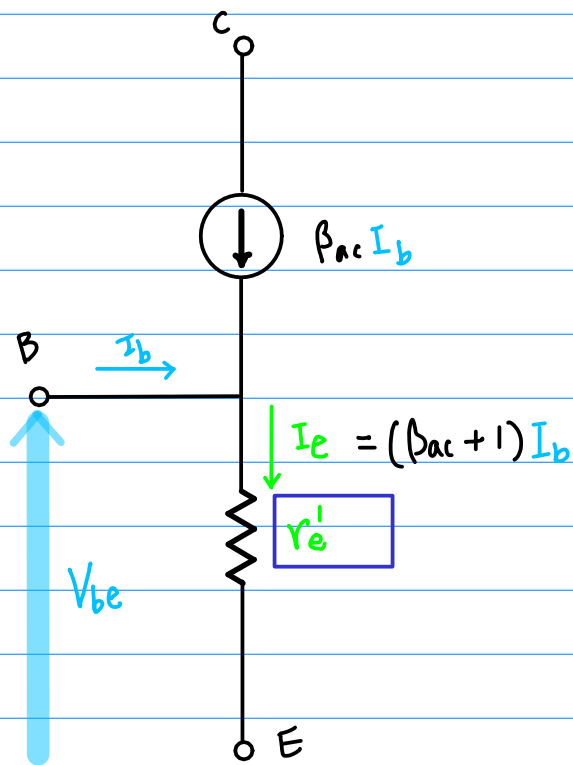
$$\beta_{ac} = \frac{\Delta I_C}{\Delta I_B}$$


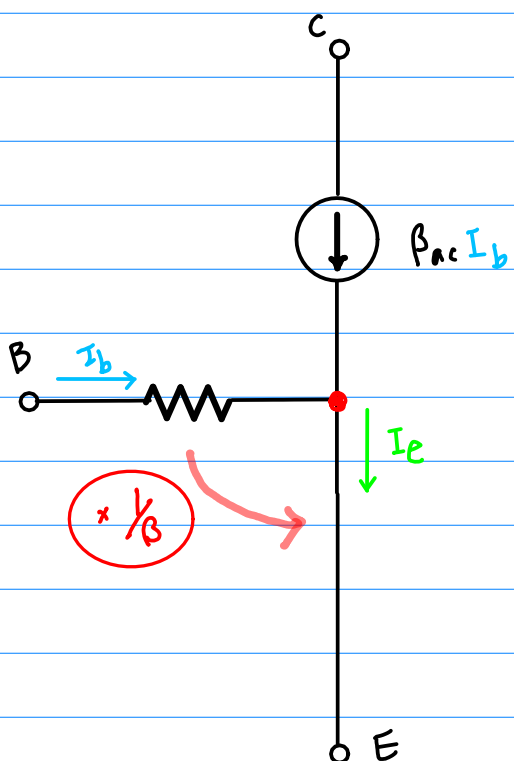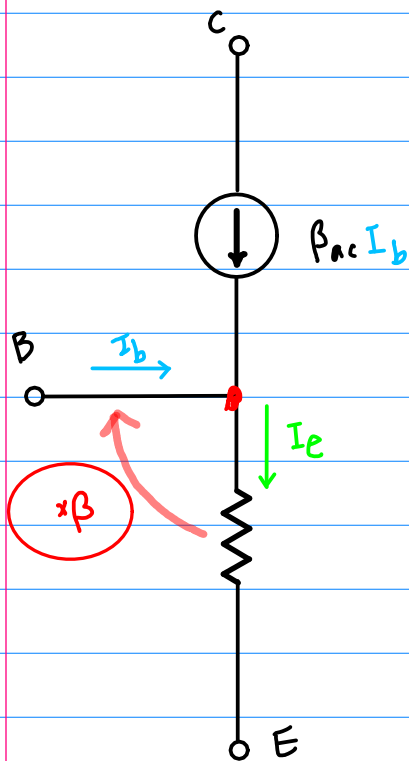
$$\begin{aligned}
 V_{be} &= I_e r_e' = (\beta_{ac} + 1) I_b r_e' \\
 &= \beta_{ac} I_b r_e' \\
 &= I_b (\beta_{ac} r_e')
 \end{aligned}$$



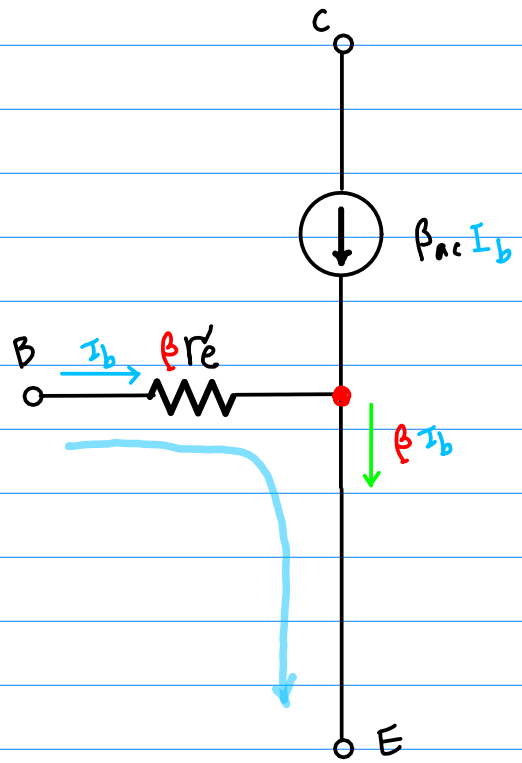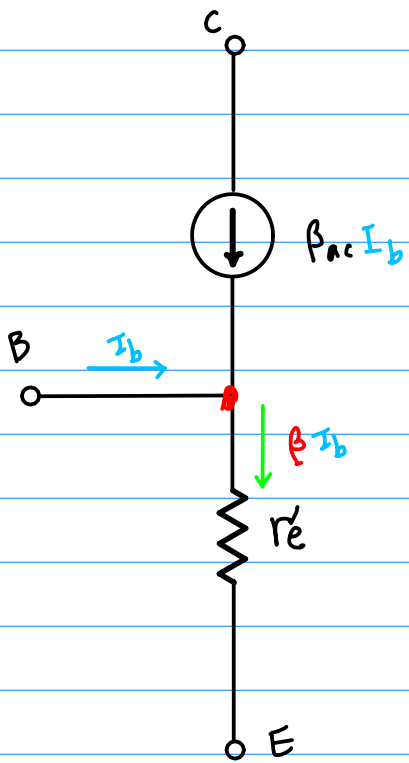

KVL $\beta I_b r_e$

constrained by


$I_e \cong \beta I_b$

\equiv



KVL $I_b \beta r_e$



constrained by

$I_e \cong \beta I_b$

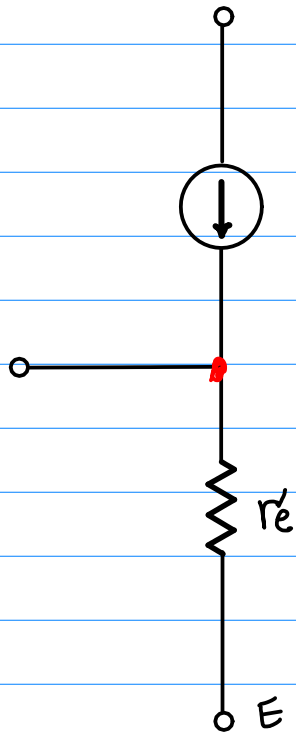

Without
 $I_e \cong \beta I_b$

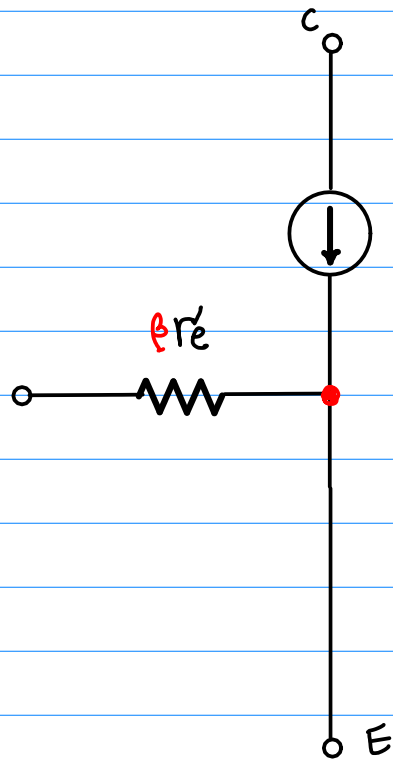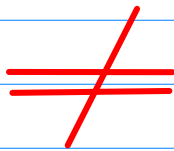

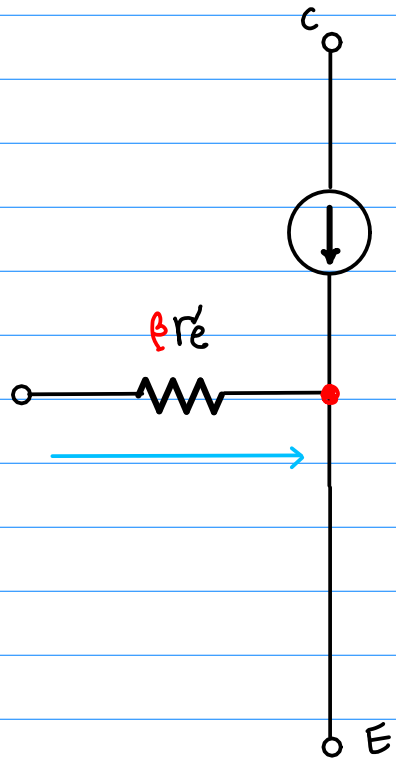
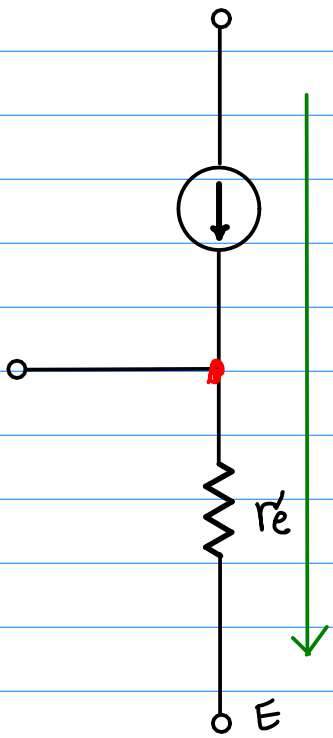


Z_o involves I_c, I_e

→ use the (t) model

Z_i involves I_b

→ use the (π) model

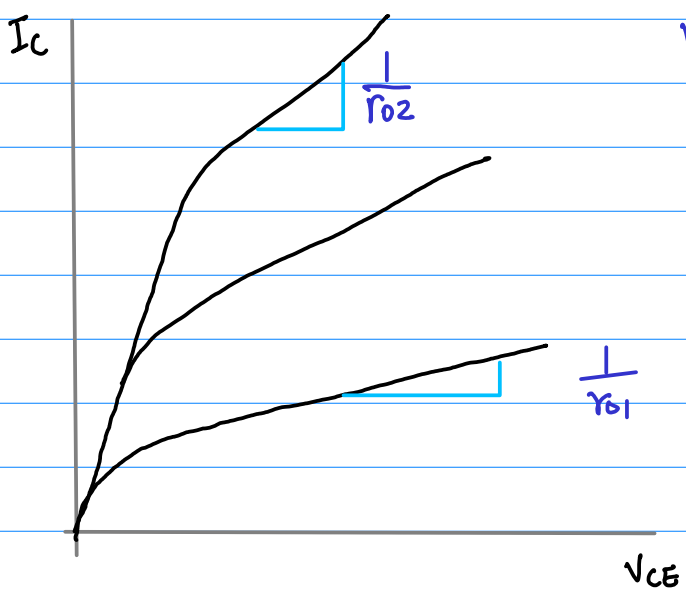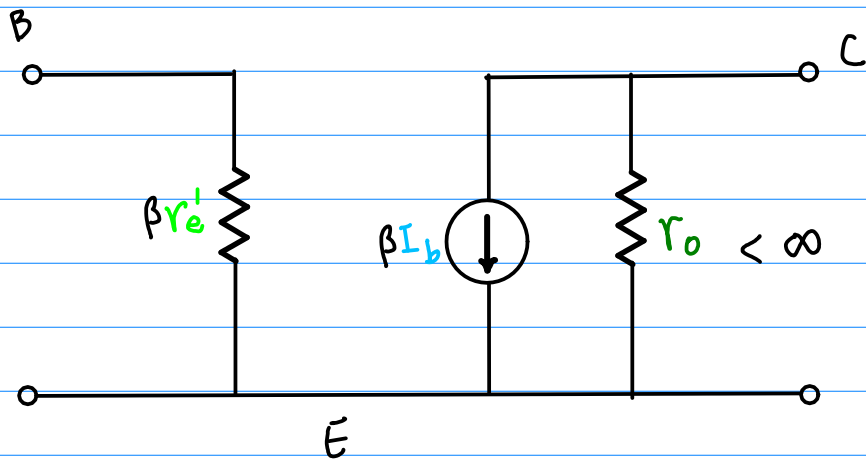

$r_{o1} > r_{o2}$

$\frac{r_{o1} + r_{o2}}{2}$ mean

r_o

$$I = I_S \left(e^{\frac{V_D}{nV_T}} - 1 \right)$$

I is the diode current,

I_S is the reverse bias **saturation current** (or scale current),

V_D is the voltage across the diode,

V_T is the **thermal voltage**, and

n is the *ideality factor*, also known as the *quality factor* or sometimes *emission coefficient*. The ideality factor n typically varies from 1 to 2 (though can in some cases be higher), depending on the fabrication process and semiconductor material and is set equal to 1 for the case of an "ideal" diode (thus the n is sometimes omitted). The ideality factor was added to account for imperfect junctions as observed in real transistors. The factor mainly accounts for **carrier recombination** as the charge carriers cross the **depletion region**.

The **thermal voltage** V_T is approximately 25.85 mV at 300 K, a temperature close to "room temperature" commonly used in device simulation software. At any temperature it is a known constant defined by:

$$V_T = \frac{kT}{q},$$

where k is the **Boltzmann constant**, T is the absolute temperature of the p-n junction, and q is the magnitude of charge of an **electron** (the **elementary charge**).

The reverse saturation current, I_S , is not constant for a given device, but varies with temperature; usually more significantly than V_T , so that V_D typically decreases as T increases.

```

[ (%i1) Is : 1.36 * 10^-15;
  (%o1) 1.36 10^-15


[ (%i2) Vt : 25.85 * 10^-3;
  (%o2) 0.02585

[ (%i5) I(v) := Is * (%e^(v/Vt) - 1);
  (%o5) I(v) := Is (%e^v/Vt - 1)

[ -->

[ (%i7) plot2d([I(v)], [v,0.6,0.8],
  [plot_format, gnuplot],
  [gnuplot_postamble, "set grid;"])$

```

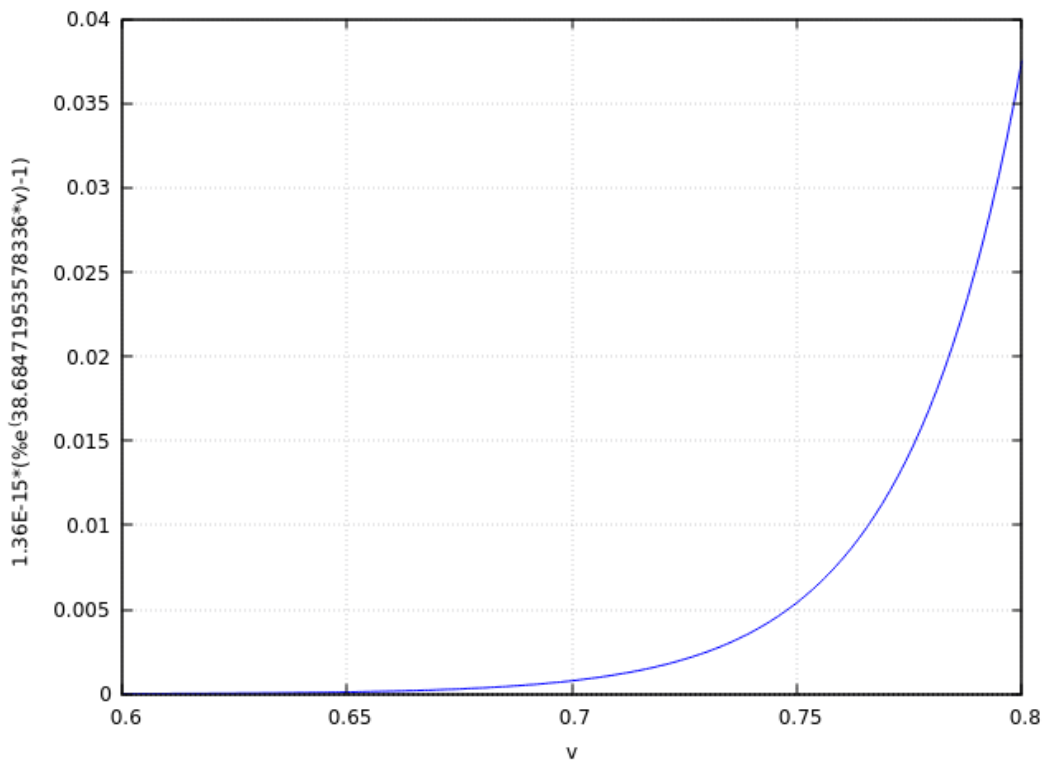

$$I = I_s \left(e^{\frac{v}{V_T}} - 1 \right) \cong I_s e^{\frac{v}{V_T}}$$


$$\frac{dI}{dv} = \frac{I_s}{V_T} e^{\frac{v}{V_T}} = \frac{1}{V_T} I$$

$$v : V_{be}$$

$$I : I_c$$

$$\frac{1}{r_e'} = \frac{I_c}{25.85 \text{ mV}}$$


$$r_e' = \frac{25.85 \text{ mV}}{I_c}$$

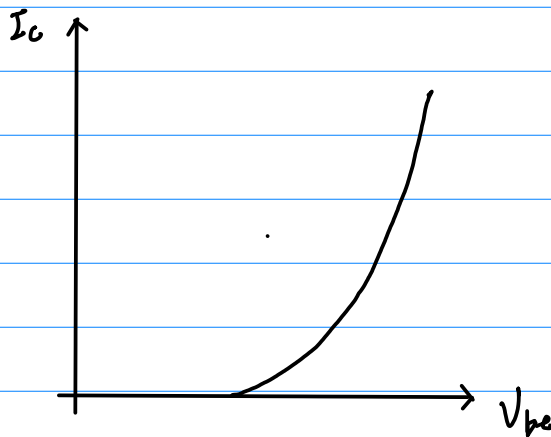

$$\frac{25 \text{ mV}}{I_c = 1 \text{ mA}} = 25 \Omega$$

$$\frac{25 \text{ mV}}{I_c = 2 \text{ mA}} = 12.5 \Omega$$
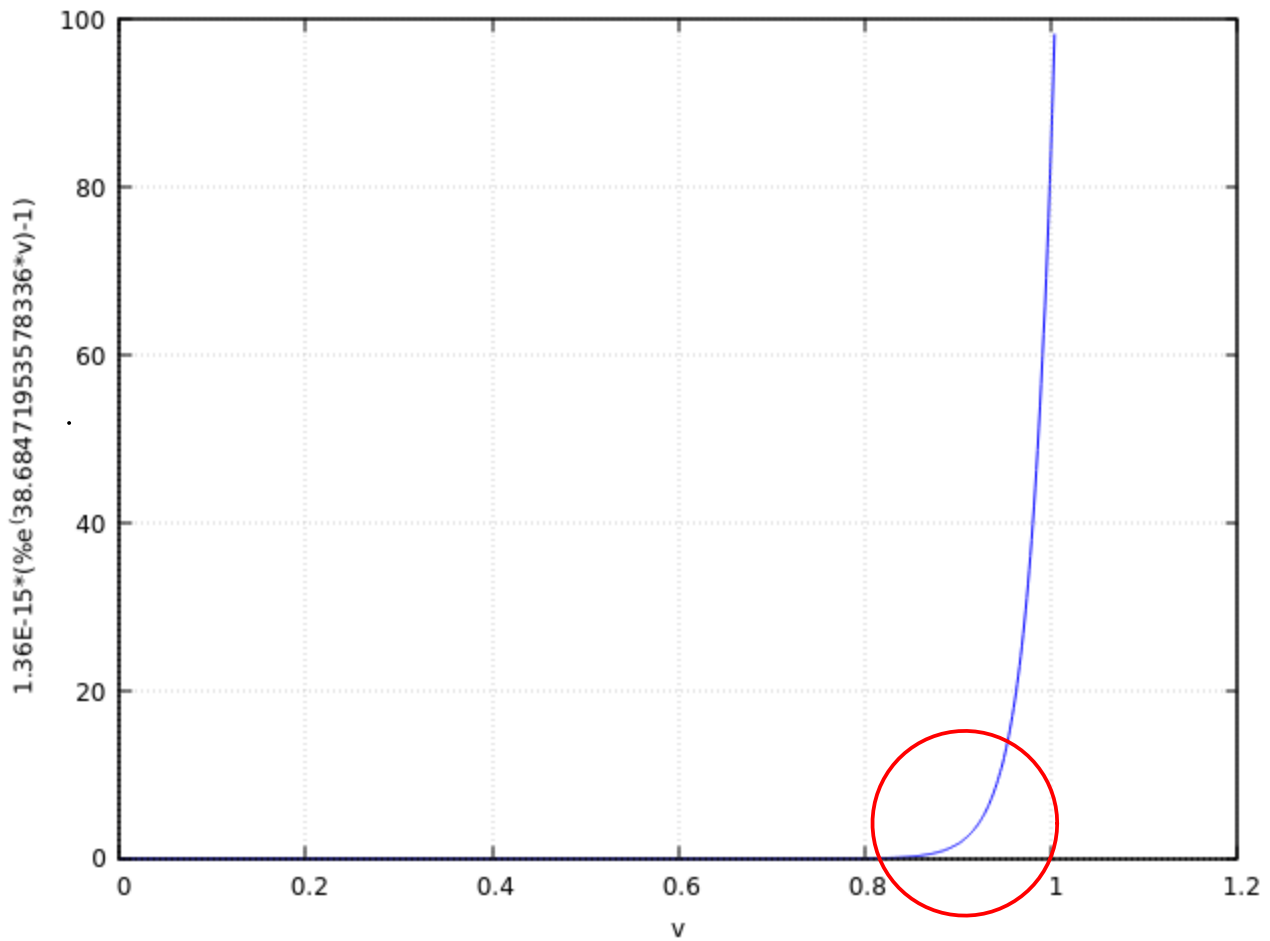
$$\frac{25 \text{ mV}}{I_c = \frac{1}{2} \text{ mA}} = 50 \Omega$$



in this small voltage range
the slope of a derivative
changes rapidly

slope = 0 ~ slope=infinity