

Filter (H.1)


20150610

20150613 10:00 ~ 12:00 115

Copyright (c) 2015 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".

1st Order Differential Equations

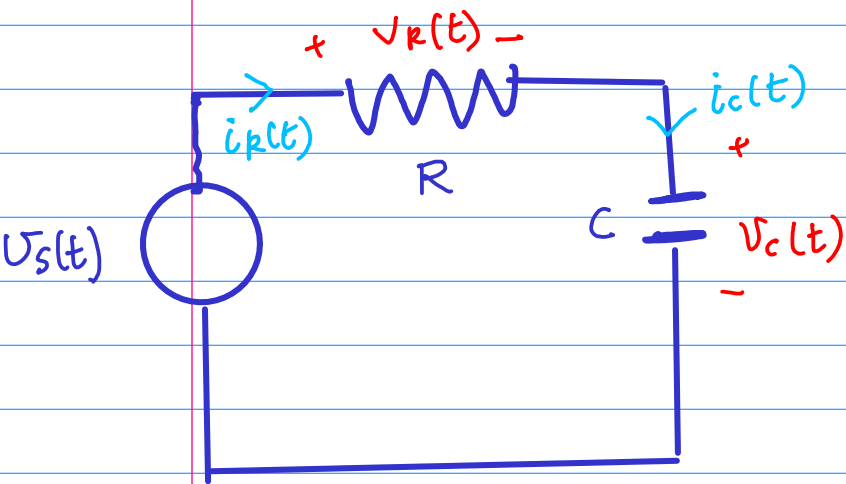


① KCL

② KVL


$$RC \frac{dV_C}{dt} + (-V_C(t)) = V_S(t) \quad V_C(t)$$

$$RC \frac{di_C}{dt} + (+i_C(t)) = C \frac{dV_S}{dt} \quad i_C(t)$$


DC input

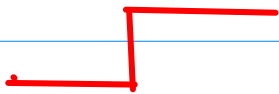

Steady State Transient Steady State

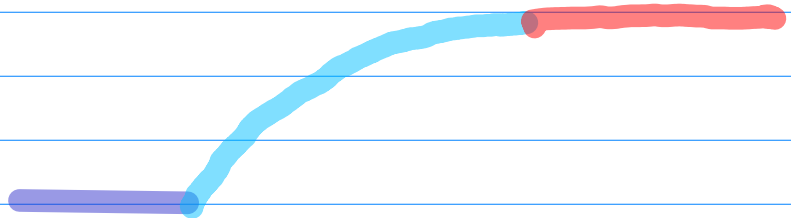


Sinusoid input

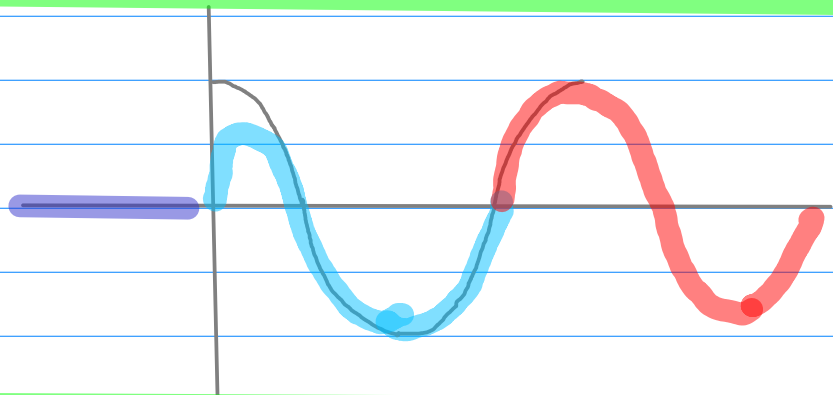

①

(RCL)

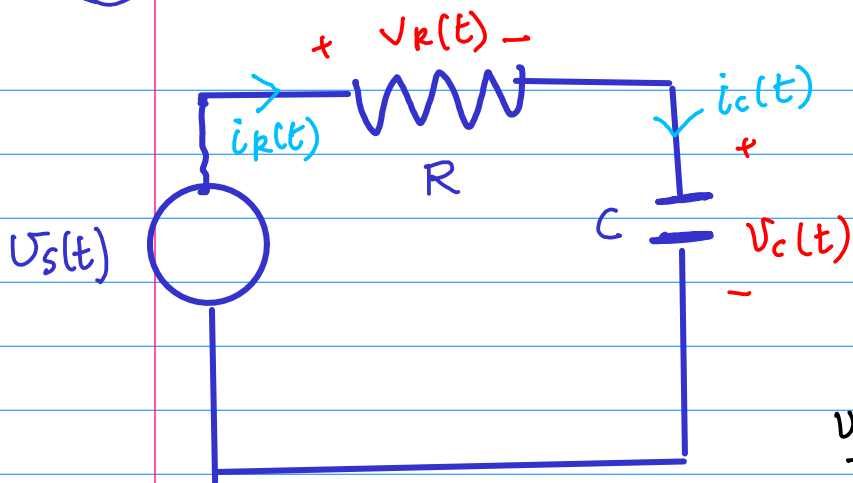

$$i_s(t) = \frac{U_s(t) - v_C(t)}{R}$$

$$i_C(t) = C \frac{dv_C}{dt}$$

$$\frac{U_s(t) - v_C(t)}{R} = C \frac{dv_C}{dt}$$


$$C \frac{dv_C}{dt} + \frac{1}{R} v_C(t) = \frac{1}{R} U_s(t)$$

$$\left\{ \begin{aligned} 1 \cdot \frac{dv_C}{dt} + \frac{1}{RC} v_C(t) &= \frac{1}{RC} U_s(t) \end{aligned} \right.$$

$$RC \frac{dv_C}{dt} + 1 \cdot v_C(t) = U_s(t)$$

2

KVL

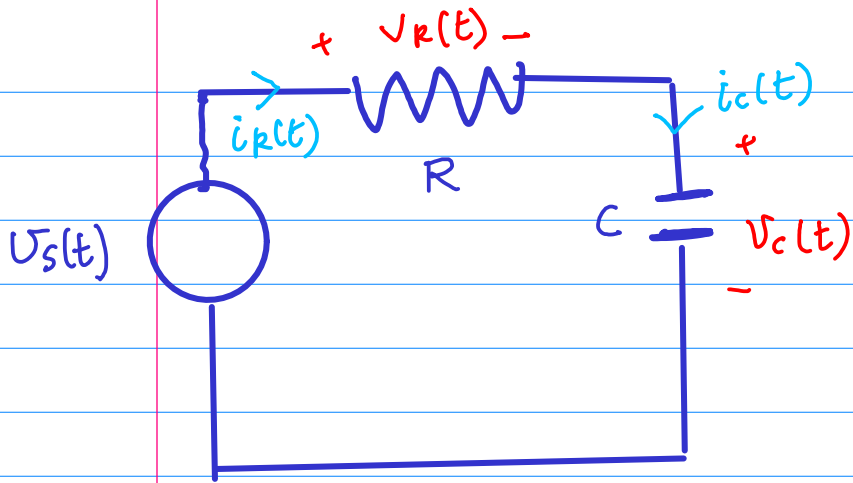

$$-U_s(t) + U_R(t) + U_C(t) = 0$$

$$i_C = C \frac{dU_C}{dt}$$

$$\int_{-\infty}^t i_C(t) dt = C U_C(t)$$

$$-U_s(t) + R i_C(t) + \frac{1}{C} \int_{-\infty}^t i_C(t) dt = 0$$

$$\frac{d}{dt} \left\{ -U_s(t) + R i_C(t) + \frac{1}{C} \int_{-\infty}^t i_C(t) dt = 0 \right\}$$

$$-\frac{dU_s(t)}{dt} + R \frac{d i_C(t)}{dt} + \frac{1}{C} i_C(t) = 0$$

$$\left. \begin{aligned} 1 \cdot \frac{d i_C}{dt} + \frac{1}{RC} i_C(t) &= \frac{1}{R} \frac{d U_s}{dt} \\ RC \frac{d i_C}{dt} + 1 \cdot i_C(t) &= C \frac{d U_s}{dt} \end{aligned} \right\}$$


③

$V_S(t) = V \cos \omega t$ sinusoid input

find forced response particular solution

..... Steady state

..... $t = \infty$

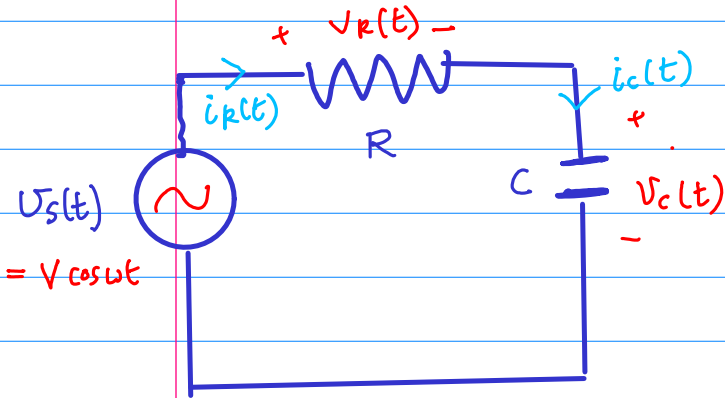

$$1. \frac{dV_C}{dt} + \frac{1}{RC} V_C(t) = \frac{1}{RC} V_S(t)$$

$$1. \frac{dV_C}{dt} + \frac{1}{RC} V_C(t) = \frac{1}{RC} V \cos \omega t$$

particular solution $V_C(t)$

$$\text{Assume } V_C(t) = A \sin \omega t + B \cos \omega t$$

$$= C \cos(\omega t + \phi)$$

$$A\omega \cos \omega t - B\omega \sin \omega t \leftarrow \frac{dV_C}{dt}$$

$$\frac{1}{RC} A \sin \omega t + \frac{1}{RC} B \cos \omega t \leftarrow \frac{1}{RC} V_C(t)$$

$$\left(\frac{A}{RC} - B\omega \right) \sin \omega t + \left(\frac{B}{RC} + A\omega \right) \cos \omega t = \frac{V}{RC} \cos \omega t$$

$$\begin{cases} \frac{A}{RC} - B\omega = 0 \\ \frac{B}{RC} + A\omega - \frac{V}{RC} = 0 \end{cases}$$

$$A = RC\omega B$$

$$\frac{B}{RC} + RC\omega^2 B - \frac{V}{RC} = 0$$

$$\frac{V}{RC} (1 + R^2\omega^2) B = \frac{V}{RC}$$

$$A = \frac{V\omega RC}{1 + \omega^2 (RC)^2}$$

$$B = \frac{V}{1 + \omega^2 (RC)^2}$$


$$V_C(t) = \frac{V\omega RC}{1 + \omega^2 (RC)^2} \sin \omega t + \frac{V}{1 + \omega^2 (RC)^2} \cos \omega t$$

Sinusoidal Steady State Response

Sinusoid (Input)

forced response = particular solution
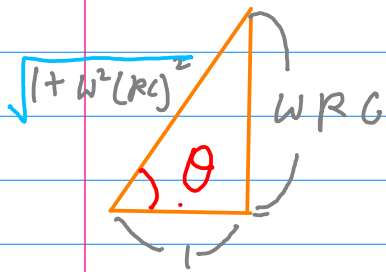
$$v_d(t) = \frac{V \omega RC}{1 + \omega^2 (RC)^2} \sin \omega t + \frac{V}{1 + \omega^2 (RC)^2} \cos \omega t$$



$$\sin \theta = \frac{\omega RC}{\sqrt{1 + \omega^2 (RC)^2}}$$

$$\cos \theta = \frac{1}{\sqrt{1 + \omega^2 (RC)^2}}$$

$$v_d(t) = V \left(\frac{\omega RC}{1 + \omega^2 (RC)^2} \sin \omega t + \frac{1}{1 + \omega^2 (RC)^2} \cos \omega t \right)$$

$$v_d(t) = \frac{V}{\sqrt{1 + \omega^2 (RC)^2}} \left(\frac{\omega RC}{\sqrt{1 + \omega^2 (RC)^2}} \sin \omega t + \frac{1}{\sqrt{1 + \omega^2 (RC)^2}} \cos \omega t \right)$$

$$= \frac{V}{\sqrt{1 + \omega^2 (RC)^2}} \left(\sin \theta \sin \omega t + \cos \theta \cos \omega t \right)$$


$$= \frac{V}{\sqrt{1 + \omega^2 (RC)^2}} \left(\cos \omega t \cos \theta + \sin \omega t \sin \theta \right)$$

$$v_d(t) = \frac{V}{\sqrt{1 + \omega^2 (RC)^2}} \cos(\omega t - \theta)$$

Sinusoidal Steady State Response

Sinusoid (Input)

forced response = particular solution

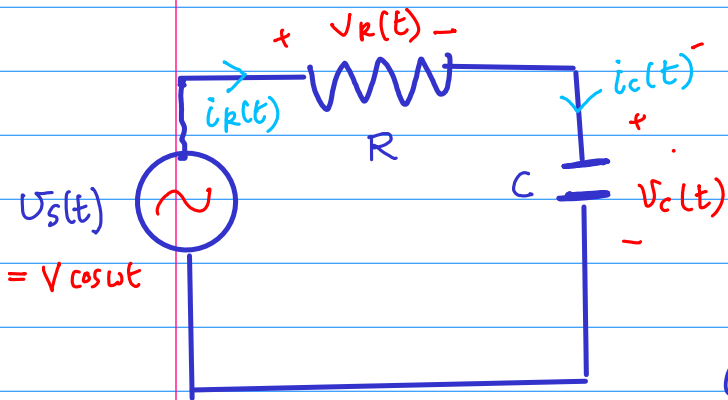

$$1. \frac{dv_C}{dt} + \frac{1}{RC} v_C(t) = \frac{1}{RC} V \cos \omega t$$

particular solution $v_{cp}(t)$


Assume $v_C(t) = A \sin \omega t + B \cos \omega t$
 $= C \cos(\omega t + \phi)$

★ particular sol로 풀았기 때문

→ $t = \infty$ 일 때



$$v_C(t) = \frac{V \omega RC}{1 + \omega^2 (RC)^2} \sin \omega t + \frac{V}{1 + \omega^2 (RC)^2} \cos \omega t$$
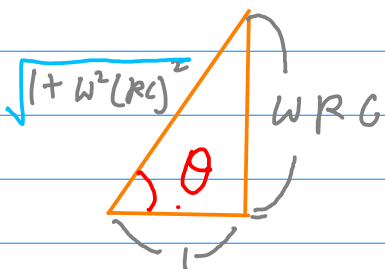
$$v_C(t) = \frac{V}{\sqrt{1 + \omega^2 (RC)^2}} \cos(\omega t - \theta)$$






$$\sin \theta = \frac{\omega RC}{\sqrt{1 + \omega^2 (RC)^2}}$$
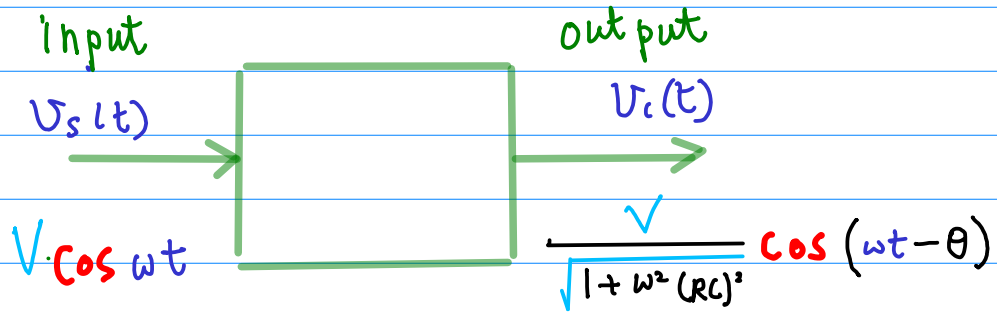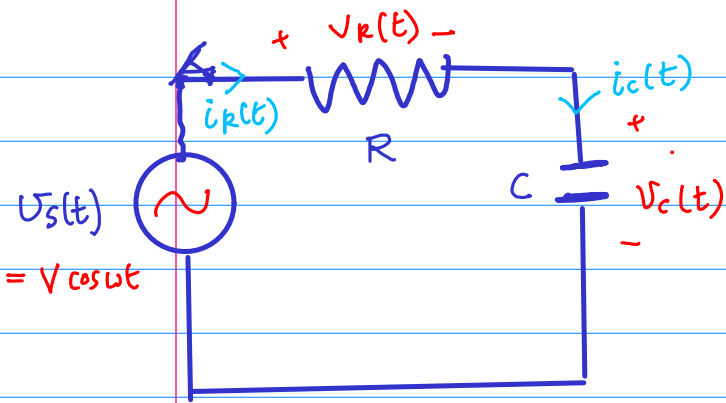
$$\cos \theta = \frac{1}{\sqrt{1 + \omega^2 (RC)^2}}$$




$V \longrightarrow \frac{V}{\sqrt{1 + \omega^2 (RC)^2}}$

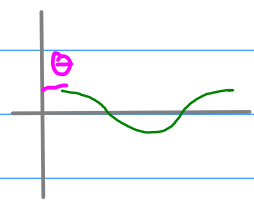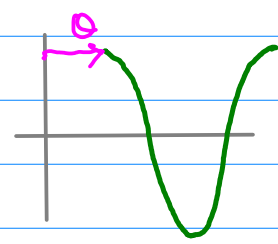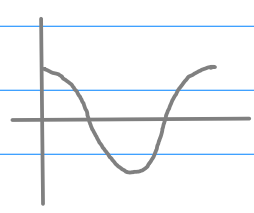$\omega t \longrightarrow \omega t - \theta$



Phasor Approach

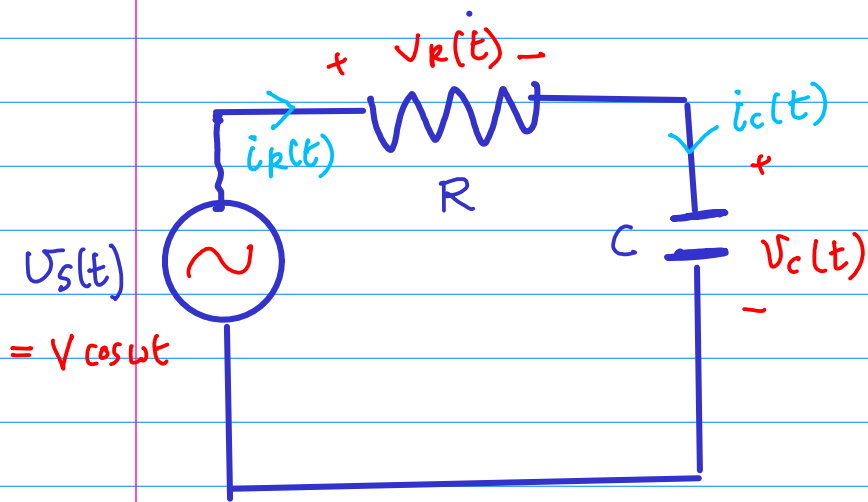

$$\begin{aligned} Z &= Z_R + Z_C \\ &= R + \frac{1}{j\omega C} \end{aligned}$$

$$V_s = V \angle 0$$


$$V_C = \frac{Z_C}{Z_R + Z_C} V_s$$

↑
phasor

↑
phasor

$$V_C = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} V_s = \boxed{\frac{1}{1 + j\omega RC}} V_s$$

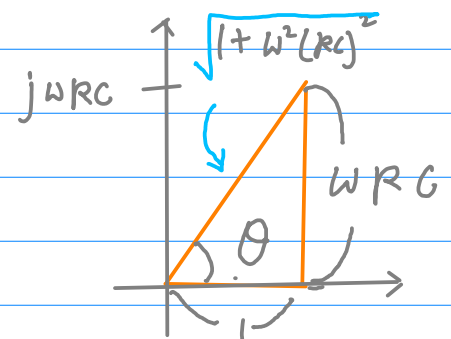
$$\boxed{\frac{1}{1 + j\omega RC} = \frac{1}{\sqrt{1 + (\omega RC)^2}} \angle -\tan^{-1} \omega RC}$$



$$V_C = \left(\frac{1}{\sqrt{1 + (\omega RC)^2}} \angle -\tan^{-1} \omega RC \right) (V \angle 0)$$

$$= \frac{V}{\sqrt{1 + (\omega RC)^2}} \angle -\tan^{-1} \omega RC \Rightarrow \frac{V}{\sqrt{1 + \omega^2(RC)^2}} \cos(\omega t - \theta)$$
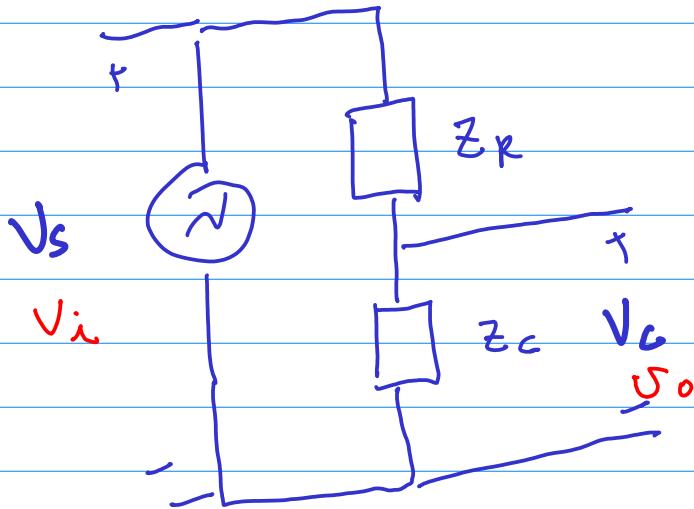
$$r_1 e^{j\theta_1} r_2 e^{j\theta_2} = r_1 \cdot r_2 e^{j(\theta_1 + \theta_2)}$$




$$V_c = \frac{Z_c}{Z_p + Z_c} V_s$$

$$\frac{1}{1 + j\omega RC}$$

$$1 + j\omega RC$$

A complex number
→ Vector

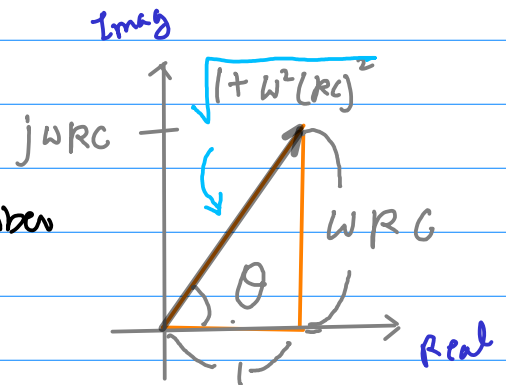

$$\tan \theta = \frac{\omega RC}{1}$$

$$r \rightarrow |1 + j\omega RC| = \sqrt{1 + (\omega RC)^2}$$

$$\theta \rightarrow \text{ang}(1 + j\omega RC) = \tan^{-1} \omega RC$$

$$1 + j\omega RC = \sqrt{1 + (\omega RC)^2} e^{j \tan^{-1} \omega RC}$$

$$= r e^{j\theta}$$

$$\frac{1}{r e^{j\theta}} = \frac{1}{r} e^{-j\theta}$$

$$\frac{1}{1 + j\omega RC} = \frac{1}{\sqrt{1 + (\omega RC)^2}} \angle -\tan^{-1} \omega RC$$

$$x = r \cos \theta$$

$$y = r \sin \theta$$

$$r = \sqrt{x^2 + y^2}$$


$$\tan \theta = \frac{y}{x}$$

$$x + iy = r \cos \theta + ir \sin \theta$$


$$= r(\cos \theta + i \sin \theta)$$

$$= r e^{i\theta}$$
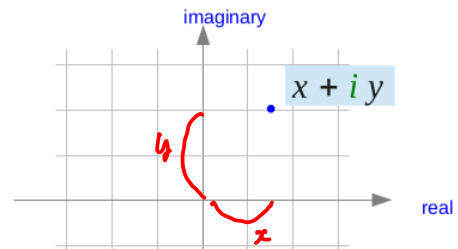
$$e^{i\theta} = \cos \theta + i \sin \theta$$



(c) Complex Number (I)

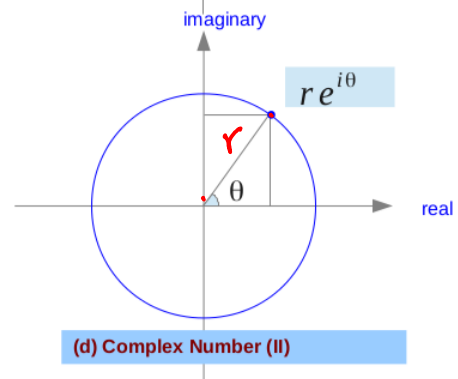


(d) Complex Number (II)





Filter



steady state

$t = \infty$


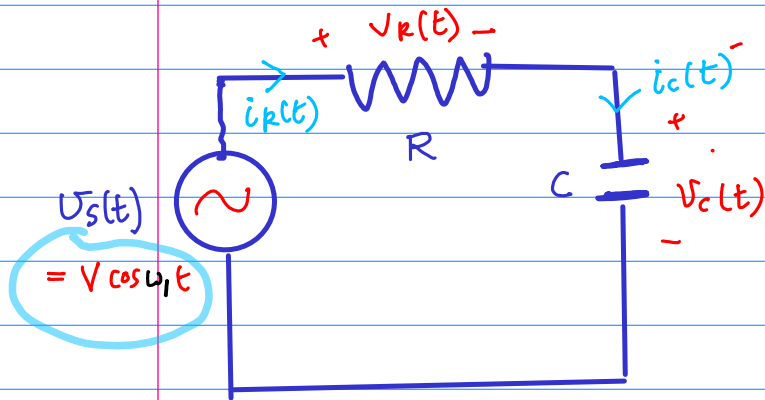


$$\omega_1 < \omega_2 < \omega_3$$

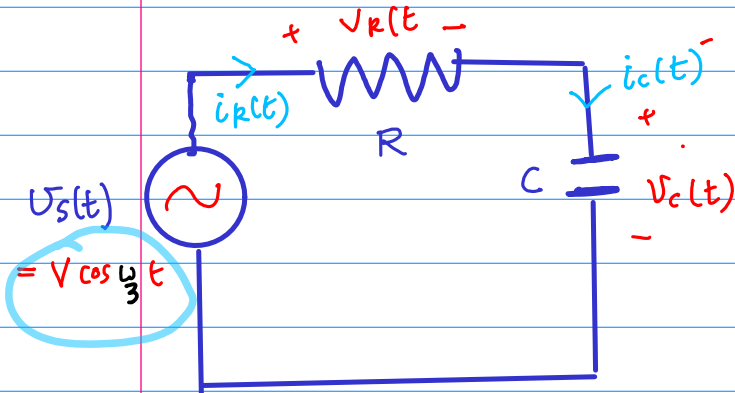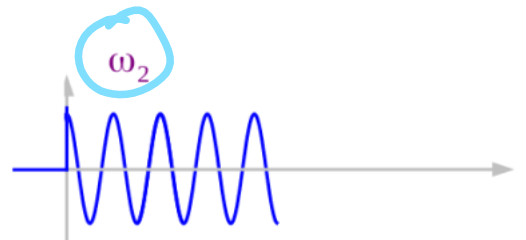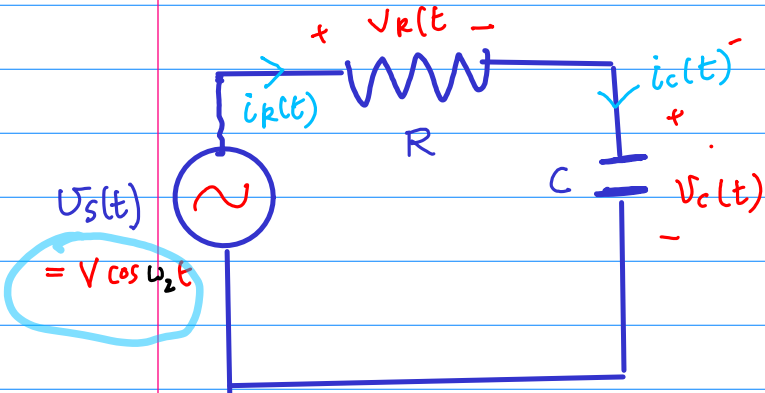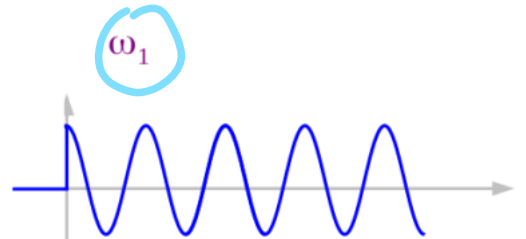

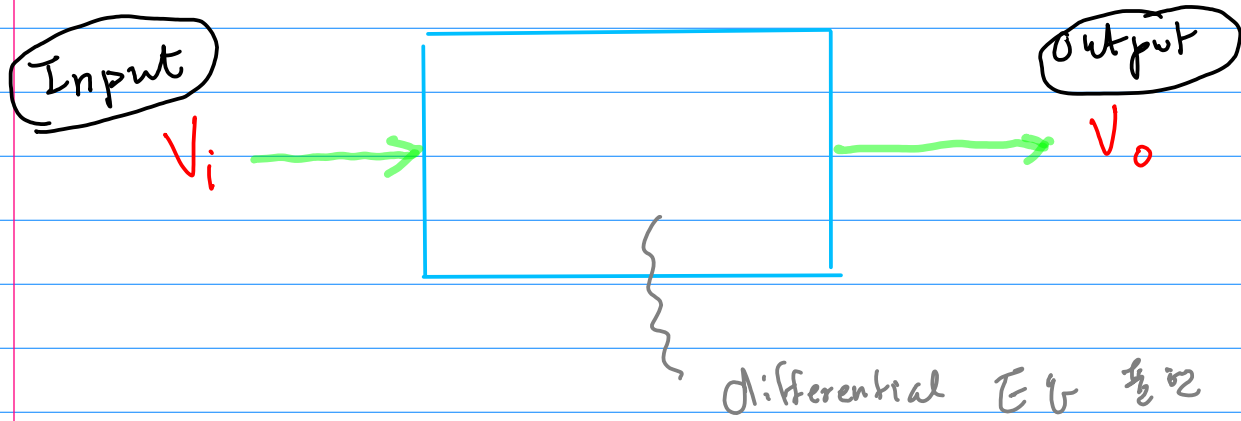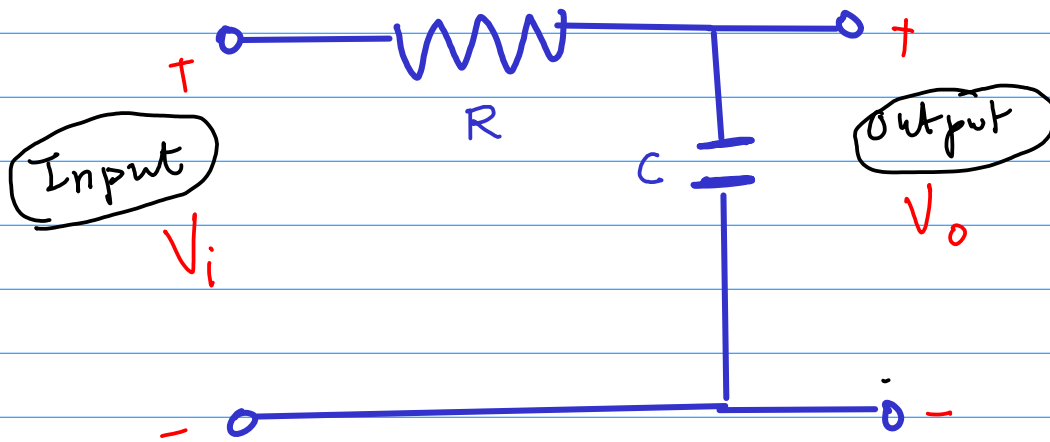

Low Pass Filter

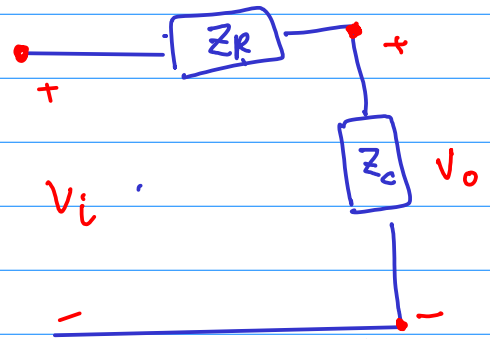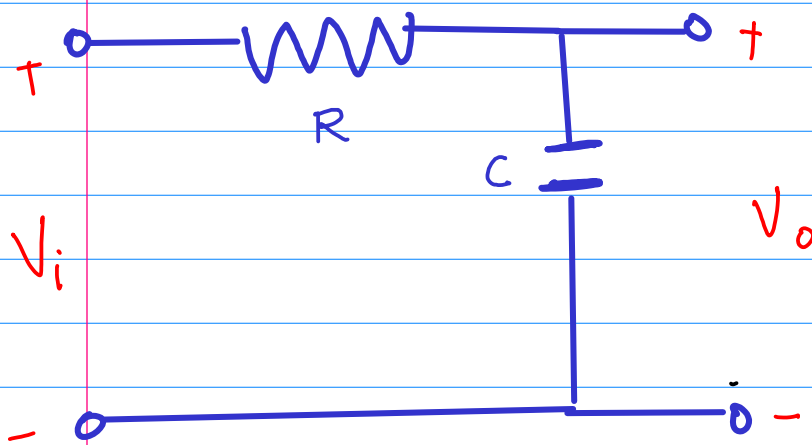

$$V_o = \frac{Z_C}{Z_R + Z_C} V_i = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} V_i$$


$$V_o = \frac{1}{j\omega RC + 1} V_i$$

$$\frac{V_o}{V_i}$$

$$z = x + iy = \boxed{r \cdot e^{i\theta}}$$

$$\left| \frac{1}{j\omega RC + 1} \right|^2 = \frac{1}{(j\omega RC + 1)(-j\omega RC + 1)} = \frac{1}{1 + (\omega RC)^2}$$

$$\left| \frac{1}{j\omega RC + 1} \right| = \frac{1}{\sqrt{1 + (\omega RC)^2}}$$

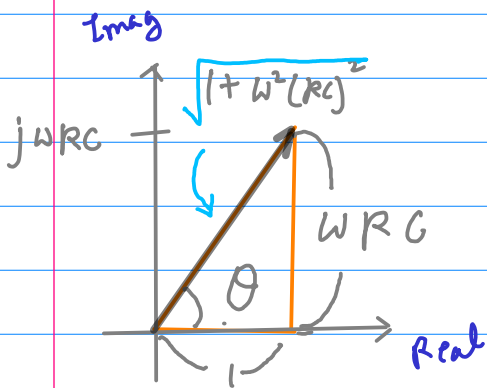

$$\tan \theta = \frac{\omega RC}{1}$$

$$\theta = \tan^{-1}(\omega RC)$$

$$\arg(\omega RC + 1) = \tan^{-1}(\omega RC)$$

$$\frac{1}{j\omega RC + 1} = \left| \frac{1}{j\omega RC + 1} \right| e^{j \arg\left(\frac{1}{j\omega RC + 1}\right)}$$

$$= \left| \frac{1}{j\omega RC + 1} \right| e^{-j \arg(\omega RC + 1)}$$

$$= \left| \frac{1}{j\omega RC + 1} \right| e^{-j \tan^{-1}(\omega RC)}$$

$$|z|^2 = z \cdot \bar{z}$$

$$z = (x + iy)$$

$$\bar{z} = (x - iy)$$

$$z \cdot \bar{z} = (x + iy)(x - iy)$$


$$= x^2 - (iy)^2$$

$$= x^2 - i^2 y^2$$

$$= x^2 + y^2$$

$$|z| = \sqrt{z \cdot \bar{z}} = \sqrt{x^2 + y^2}$$

$$= \left| \frac{1}{j\omega RC + 1} \right| \frac{1}{e^{j \arg(\omega RC + 1)}}$$

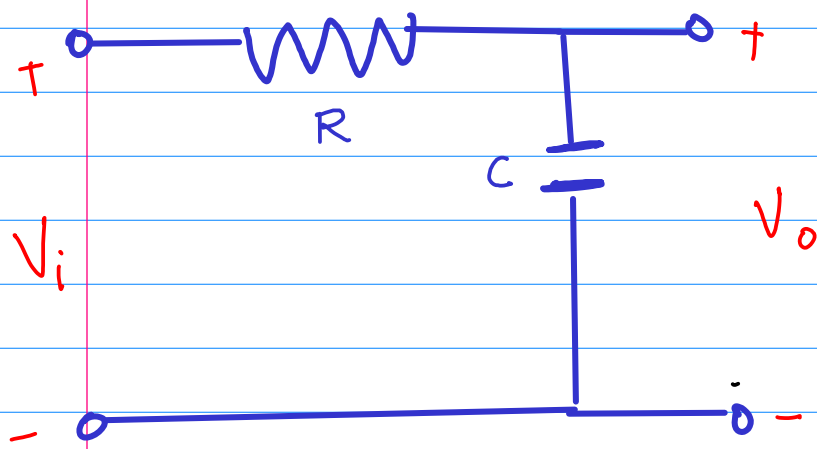

rotating phasor

$$V_o = \frac{1}{j\omega RC + 1} V_i$$

rotating phasor

$$\frac{V_o(j\omega)}{V_i(j\omega)} = \frac{1}{j\omega RC + 1} = H(j\omega)$$

unit less scaling factor
just a complex number for a given ω

$$H(j\omega) = |H(j\omega)| \cdot e^{j \text{ang}(H(j\omega))}$$

$$|H(j\omega)| = \left| \frac{1}{j\omega RC + 1} \right|$$


$$\text{ang}(H(j\omega)) = e^{-j \tan^{-1}(\omega RC)}$$

$$H(j\omega) = |H(j\omega)| \cdot e^{j \text{ang}(H(j\omega))}$$

$$\omega_0 = \frac{1}{RC} \quad \cdot \quad \frac{1}{\omega_0} = RC$$

$$|H(j\omega)| = \left| \frac{1}{j\omega RC + 1} \right| = \left| \frac{1}{j(\omega/\omega_0) + 1} \right|$$
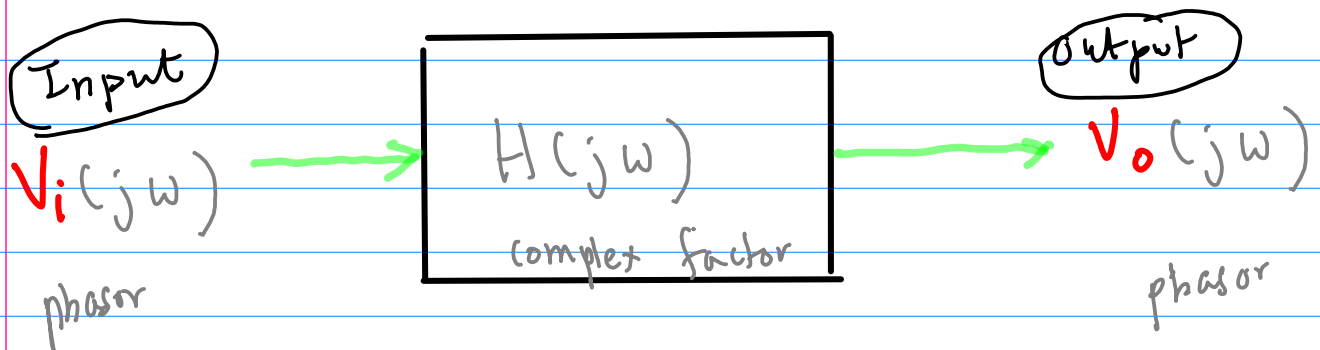
$$\text{ang}(H(j\omega)) = e^{-j \tan^{-1}(\omega RC)} = e^{-j \tan^{-1}(\omega/\omega_0)}$$



$$\begin{aligned} V_o(j\omega) &= H(j\omega) V_i(j\omega) \\ &= |H(j\omega)| e^{+j \text{ang}(H(j\omega))} \cdot |V_i(j\omega)| e^{+j \text{ang}(V_i(j\omega))} \\ &= |H(j\omega)| \cdot |V_i(j\omega)| e^{+j [\text{ang}(H(j\omega)) + \text{ang}(V_i(j\omega))]} \end{aligned}$$

$$|V_o(j\omega)| = V_o = |H| \cdot V_i$$

$$\text{ang}\{V_o(j\omega)\} = \phi_o = \text{ang}(H) + \text{ang}(V_i)$$

$$U_o = \frac{1}{j\omega RC + 1} U_i$$

$$\frac{1}{j\omega RC + 1} = \left| \frac{1}{j\omega RC + 1} \right| e^{-j \tan^{-1}(\omega RC)}$$

→ phasor

$$H(j\omega) = \frac{U_o}{U_i} = \left| \frac{1}{j\omega RC + 1} \right| e^{-j \tan^{-1}(\omega RC)}$$

Complex
scaling
factor

→ phasor

$$H(j\omega) = |H(j\omega)| e^{-j \arg(H(j\omega))}$$

$$|H(j\omega)| = \left| \frac{1}{j\omega RC + 1} \right| = \frac{1}{\sqrt{1 + \omega^2 RC^2}}$$

$$\arg(H(j\omega)) = -\tan^{-1}(\omega RC)$$

$$\omega_0 = \frac{1}{RC}$$

$$|H(j\omega)| = \frac{1}{\sqrt{1 + \omega^2 RC^2}} = \frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_0}\right)^2}}$$

$$\text{ang}(H(j\omega)) = -\tan^{-1}(\omega RC) = -\tan^{-1}\left(\frac{\omega}{\omega_0}\right)$$

$$|H(j\omega)| = \frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_0}\right)^2}}$$

$$\text{ang}(H(j\omega)) = -\tan^{-1}\left(\frac{\omega}{\omega_0}\right)$$

$$\omega \gg \omega_0 \quad \left(\frac{\omega}{\omega_0} \gg 1\right)$$



$$1 + \frac{\omega}{\omega_0} \approx \frac{\omega}{\omega_0}$$

$$|H(j\omega)| = \frac{1}{\left(\frac{\omega}{\omega_0}\right)}$$


$$\omega \ll \omega_0 \quad \left(\frac{\omega}{\omega_0} \ll 1\right)$$

$$1 + \frac{\omega}{\omega_0} \approx 1$$

$$|H(j\omega)| = \frac{1}{\sqrt{2}}$$

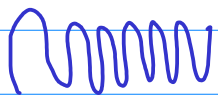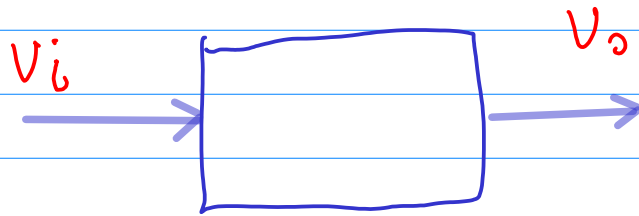

$|H(j\omega)|$

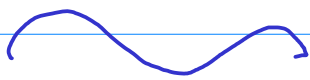

$|H(j\omega)|$






$$y_{ss}(t) = H(j\omega) \cdot A \cos(\omega t)$$

$$= A \cdot H(j\omega) \cos(\omega t)$$

$$x(t) = A \cos(\omega t)$$

$$\xi = j\omega$$


ω_1 ω_2 ω_3

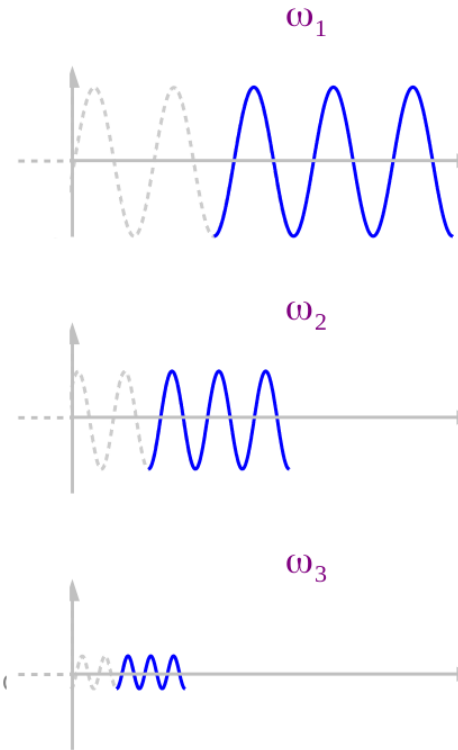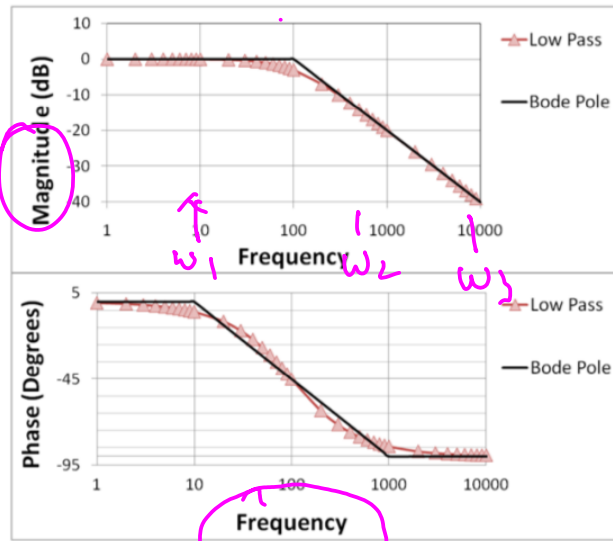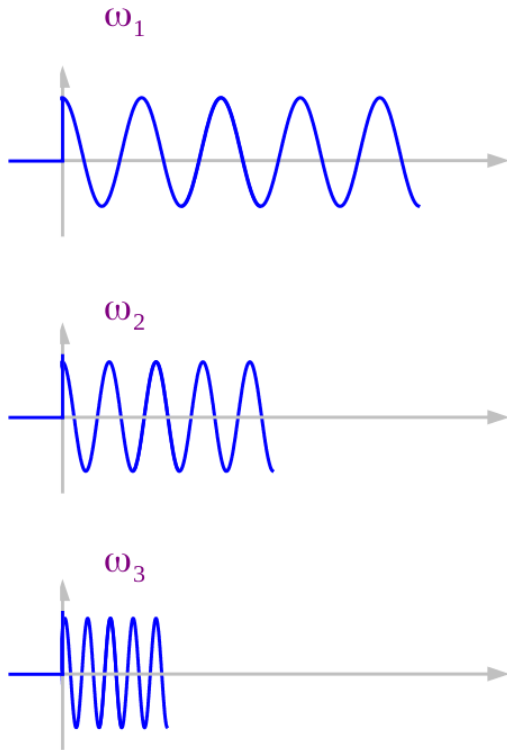

http://en.wikipedia.org/wiki/File:Bode_Low-Pass.PNG

Frequency


∩ ∩

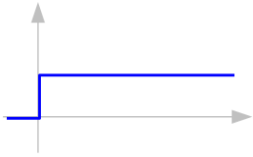

$$y_{ss}(t) = H(0) \cdot A e^{0t} = A \cdot H(0)$$



$$x(t) = A$$

$$\xi = 0$$

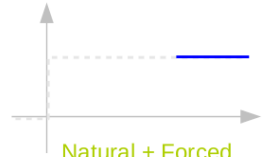

Natural + Forced response


transient response

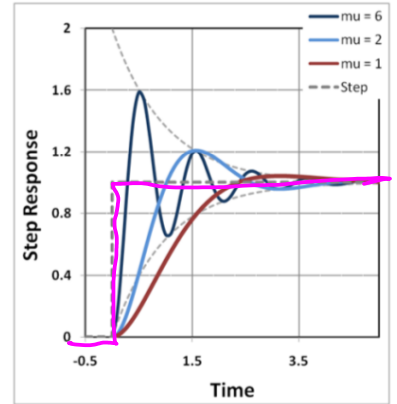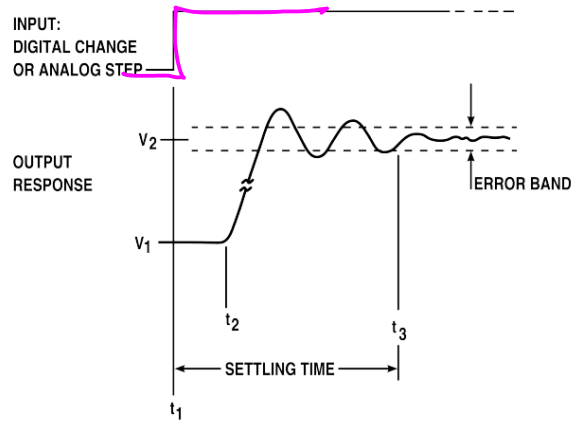

http://en.wikipedia.org/wiki/File:High_accuracy_settling_time_measurements_figure_1.png
http://en.wikipedia.org/wiki/File:Step_response_for_two-pole_feedback_amplifier.PNG


time response



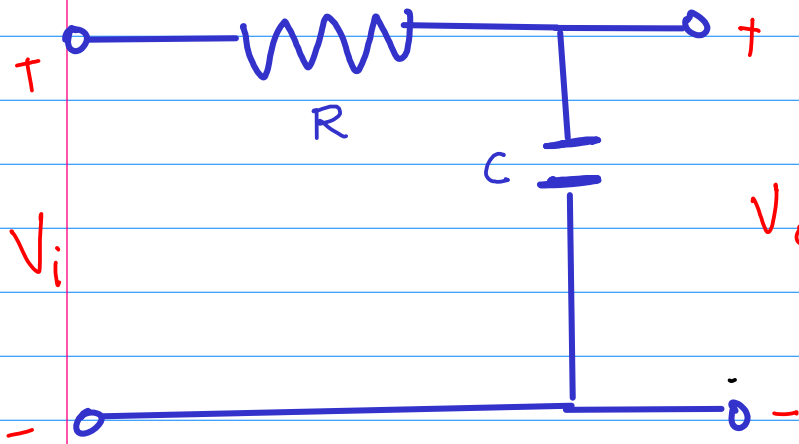

V_i

V_o Low Pass

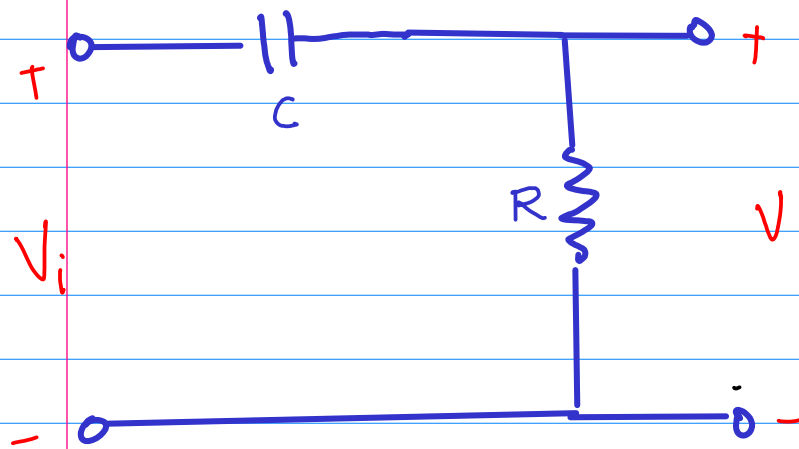

V_i

V_o High Pass

$$10 \angle 0 - 4.421 \angle -0.9852$$

$$10 - (4.421 \cos(-0.9852) + j4.421 \sin(-0.9852))$$

$$10 - 4.421 \cos(0.9852) + j4.421 \sin(0.9852)$$

$$7.556 + j 3.684$$