



BJT Device (H1) 201704021-2 Copyright (c) 2015 Young W. Lim. Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".

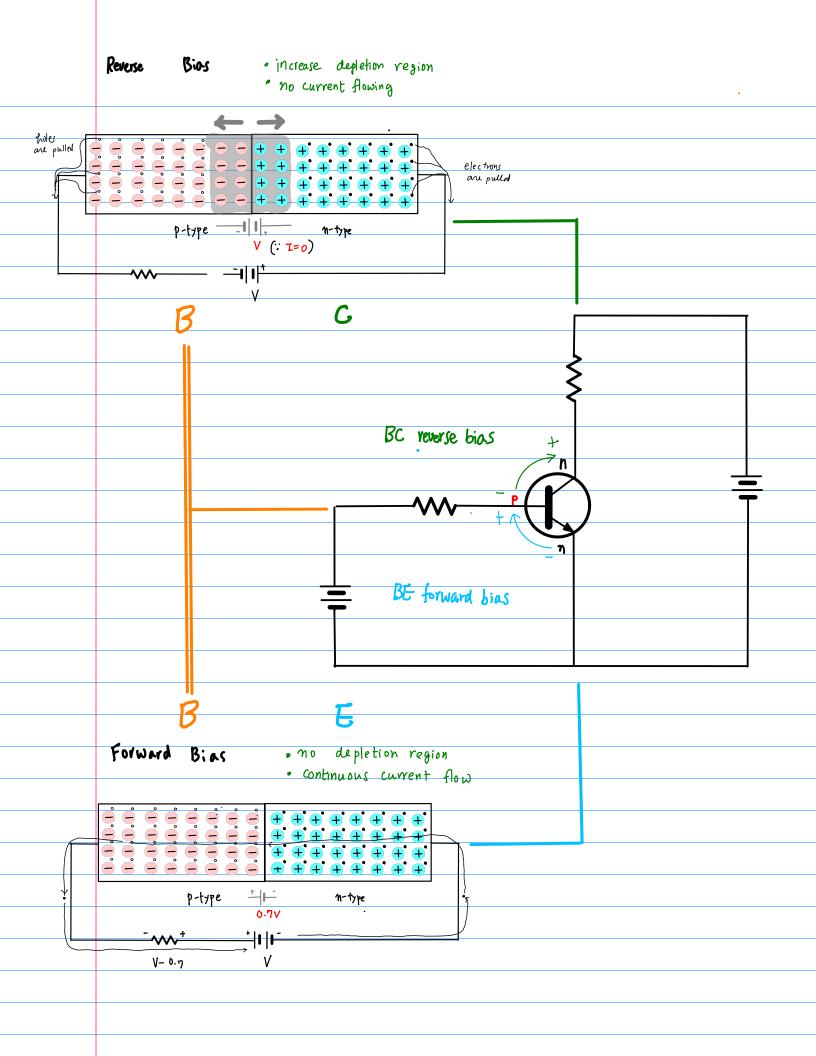

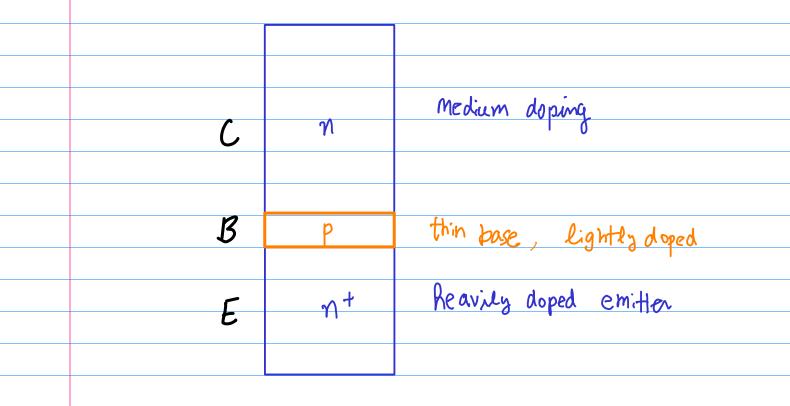

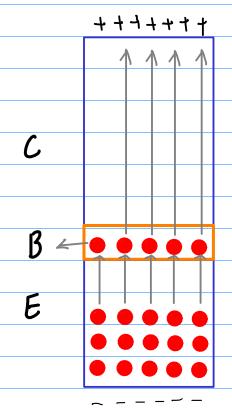



Trans + resistor

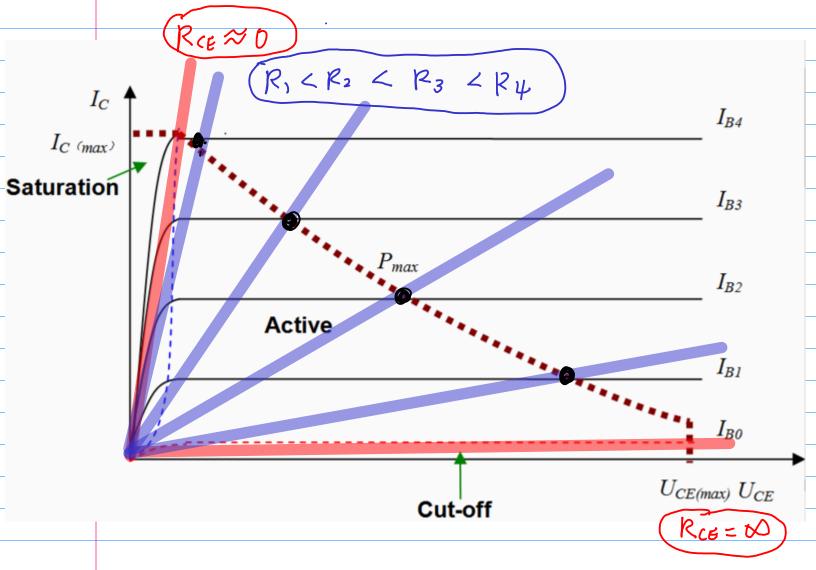

https://en.wikipedia.org/wiki

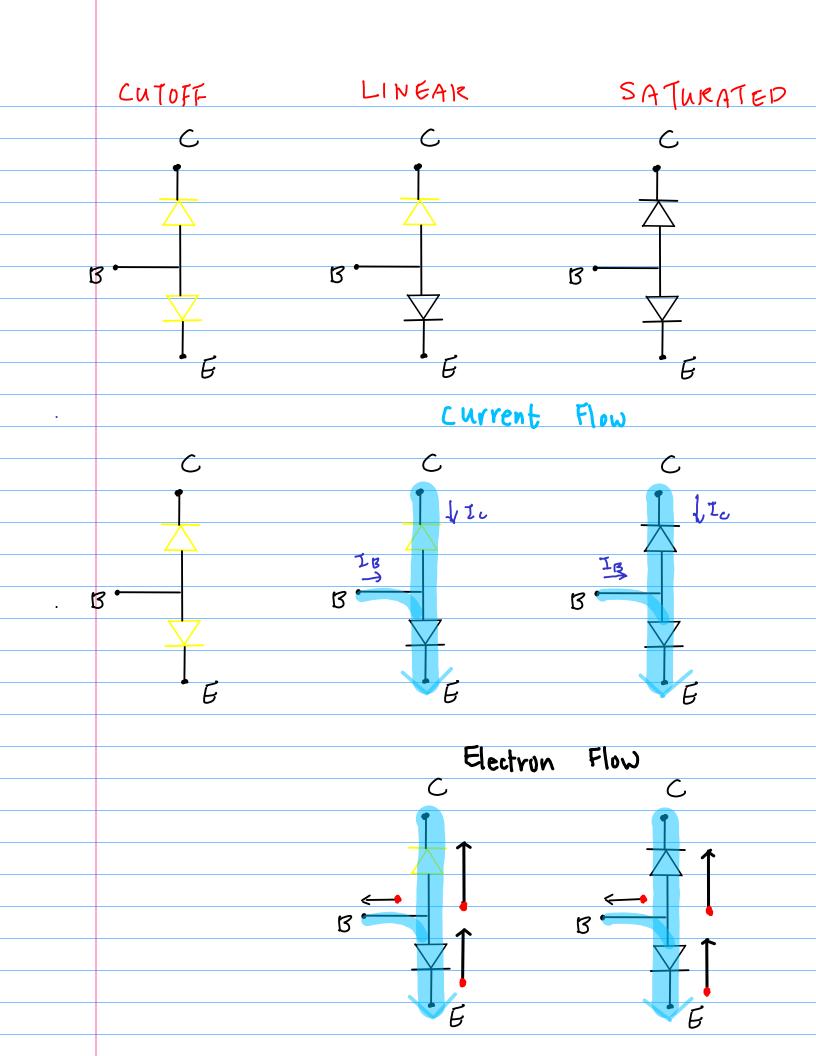
$$Slope = \frac{I_0}{\sqrt{c_6}} = \frac{1}{R_{CE}}$$



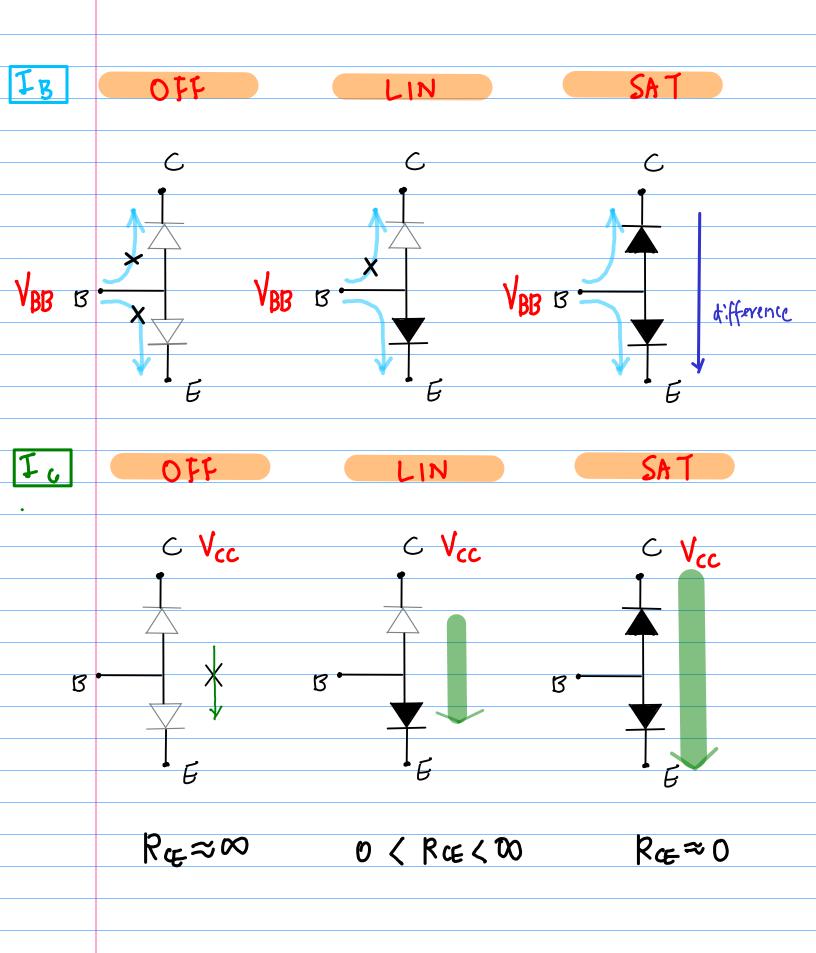


No Bias

Linear

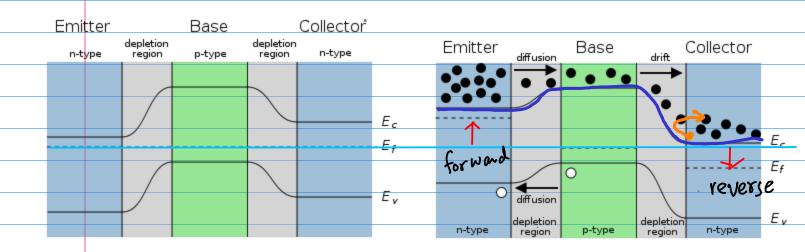

LINGAR

SATURATION

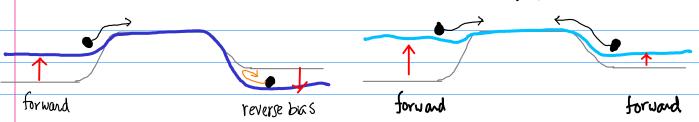

VCE 1

VEL


IBT

LB + fixed

IOT REL


Ic - fixed




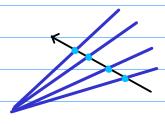

$$M = \frac{I_c}{V_{CE}} = \frac{1}{R_{CE}} \uparrow$$

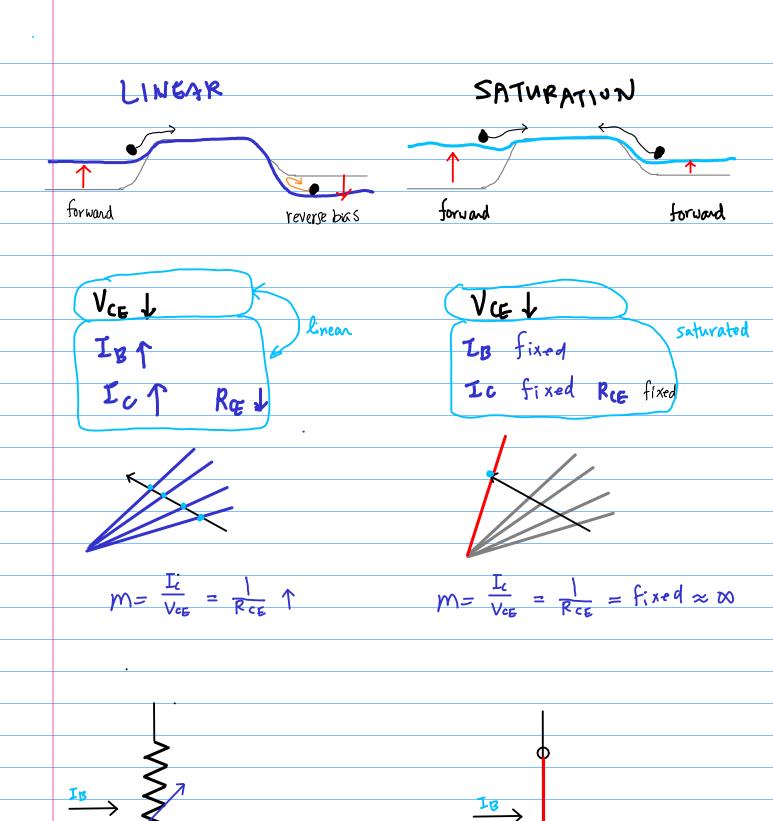
$$M = \frac{I_c}{V_{CE}} = \frac{1}{R_{CE}} = fixed \approx \infty$$



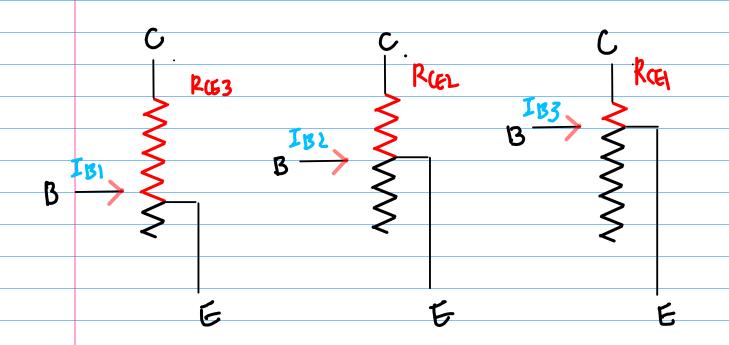



IBI. (IB2 (IB3

RCEL) RCE3

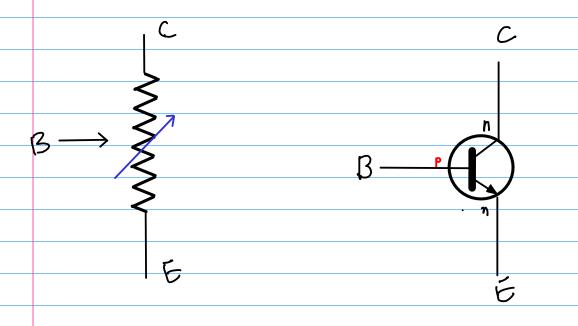


To increase IB

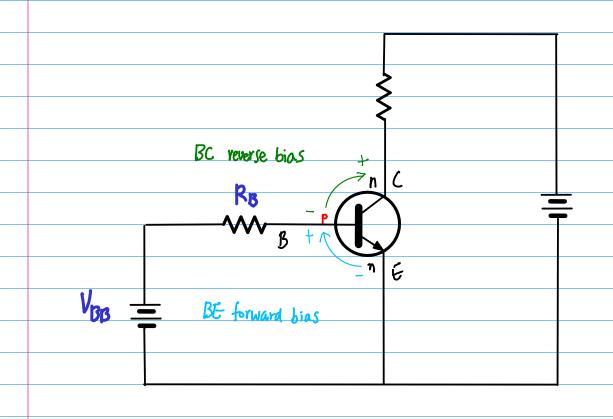

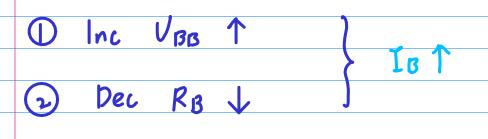

Current (ontrolled Device (Is)

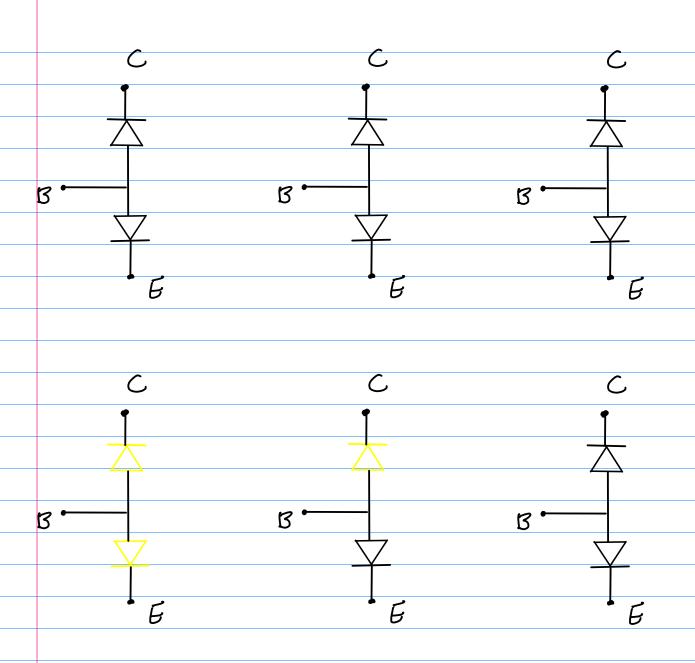

- D cut off
- 2 Active
- 3 Saturation

