

OP Amp (1A)

•
•

Copyright (c) 2015 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".

Please send corrections (or suggestions) to youngwlim@hotmail.com.


This document was produced by using OpenOffice and Octave.

741 op-amp



A μ A741 integrated circuit, one of the most successful operational amplifiers.

Type	Discrete circuit Integrated circuit
Invented	Karl D. Swartzel Jr.
First production	1941
Pin configuration	<ul style="list-style-type: none">• V+: non-inverting input• V-: inverting input• Vout: output• VS+: positive power supply• VS-: negative power supply

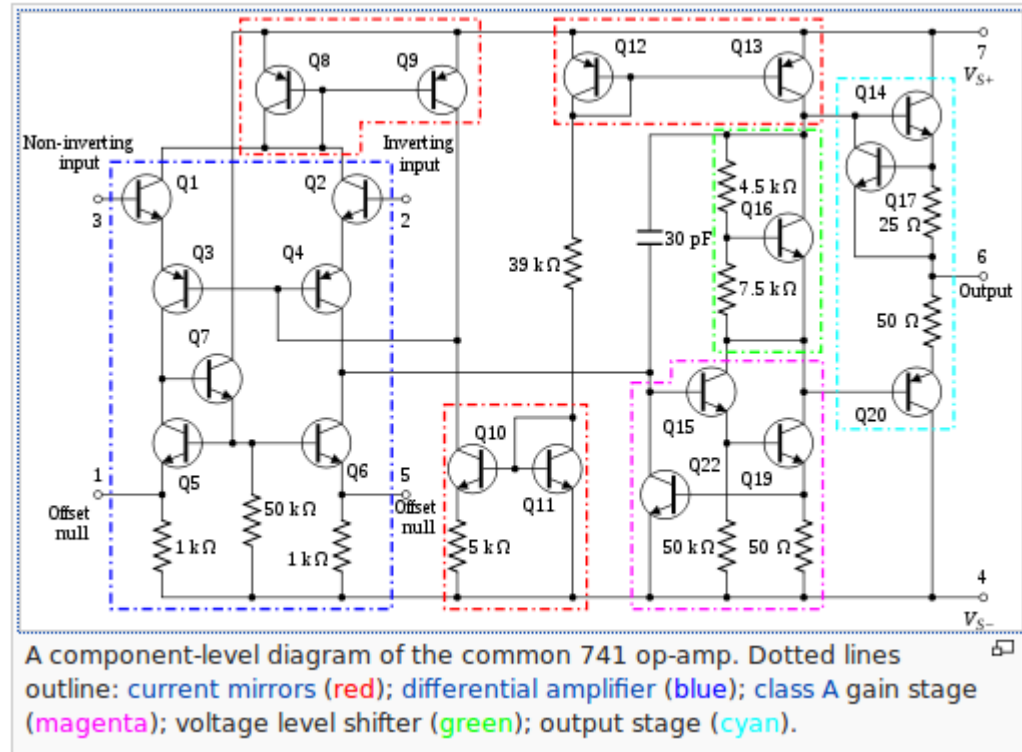


https://en.wikipedia.org/wiki/Operational_amplifier


Power Supply

The power supply pins (V_{S+} and V_{S-}) can be labeled in different ways (See *IC power supply pins*). Often these pins are left out of the diagram for clarity, and the power configuration is described or assumed from the circuit.

Electronic symbol

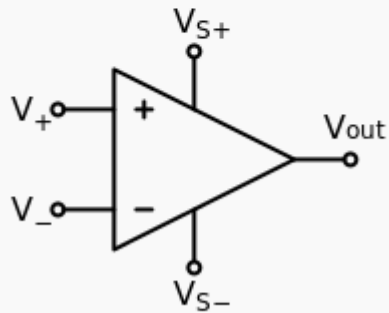


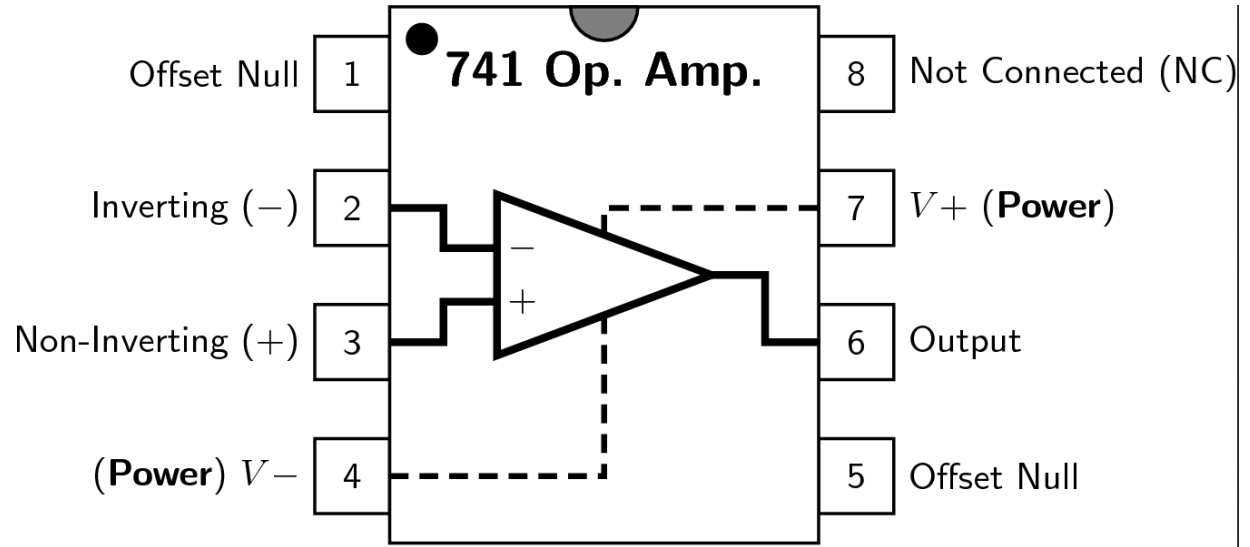Circuit diagram symbol for an op-amp.
Pins are labeled as listed above.



https://en.wikipedia.org/wiki/Operational_amplifier

Ideal OP-Amps

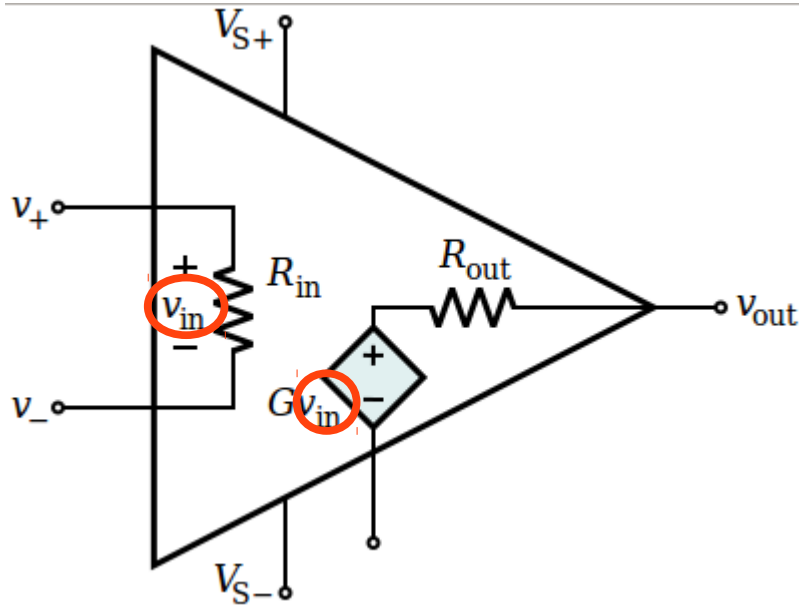

$$R_{in} = \infty$$

$$R_{out} = 0$$


- Infinite open-loop gain $G = v_{out} / v_{in}$
- Infinite input impedance R_{in}
- Zero input current
- Zero output impedance R_{out}

- Zero input offset voltage
- Zero noise
- Infinite voltage range available at the output
- Infinite bandwidth
with zero phase shift and infinite slew rate

- Infinite Common-mode rejection ratio (CMRR)
- Infinite Power supply rejection ratio.

https://en.wikipedia.org/wiki/Operational_amplifier

The Op-amp golden rule

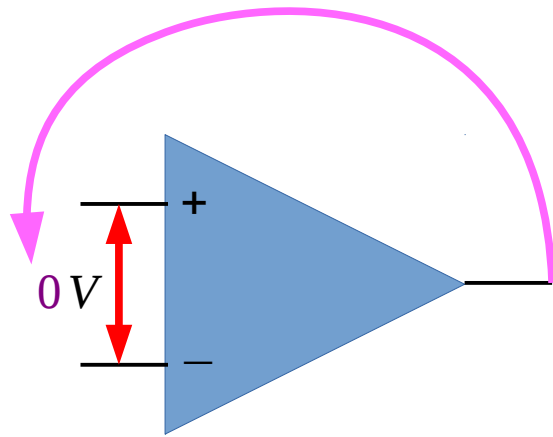


1. The Voltage Rule

The output attempts to do whatever is necessary to make the **voltage difference** between the inputs **zero**.


II. The Current Rule

The inputs draw no current.

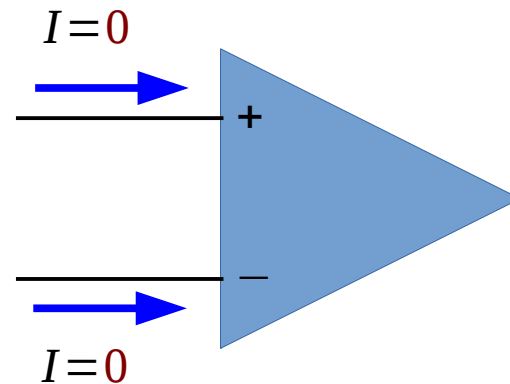

<http://hyperphysics.phy-astr.gsu.edu/hbase/electronic/opamp.html#c1>


Inverting Amplifier

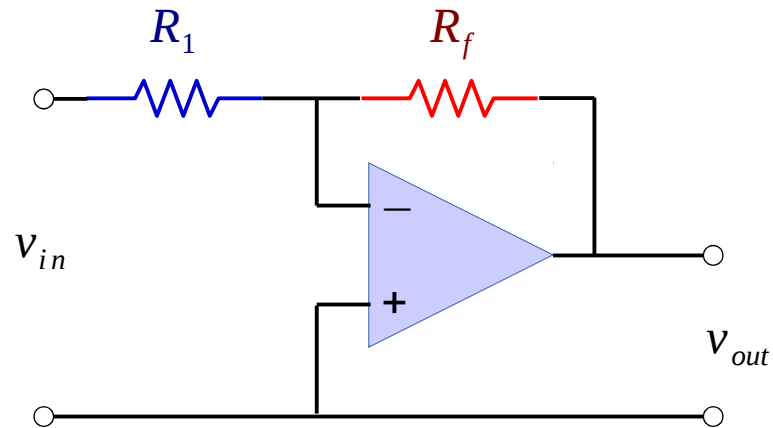

$$\frac{V_{out}}{V_{in}} = -\frac{R_f}{R_1}$$

<http://hyperphysics.phy-astr.gsu.edu/hbase/electronic/opampi.html#c1>


Non-Inverting Amplifier

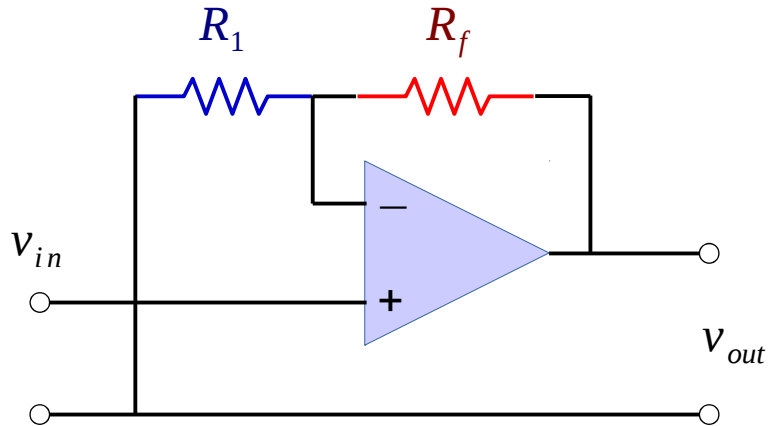

$$\frac{V_{out}}{V_{in}} = 1 + \frac{R_f}{R_1}$$

<http://hyperphysics.phy-astr.gsu.edu/hbase/electronic/opampi.html#c1>


Voltage Follower

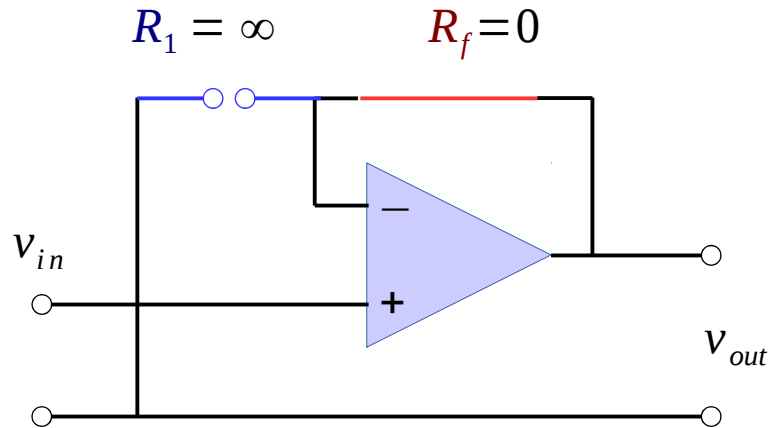

$$\frac{V_{out}}{V_{in}} = 1$$

<http://hyperphysics.phy-astr.gsu.edu/hbase/electronic/opampi.html#c1>


Voltage Follower

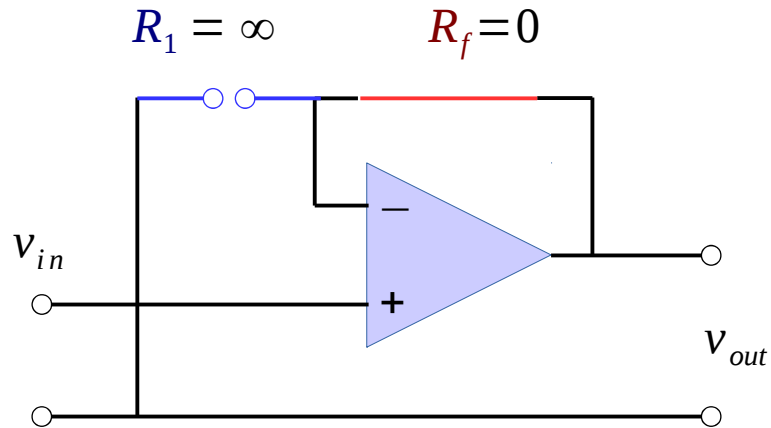

$$\frac{V_{out}}{V_{in}} = 1$$

<http://hyperphysics.phy-astr.gsu.edu/hbase/electronic/opampi.html#c1>


I → V Amplifier

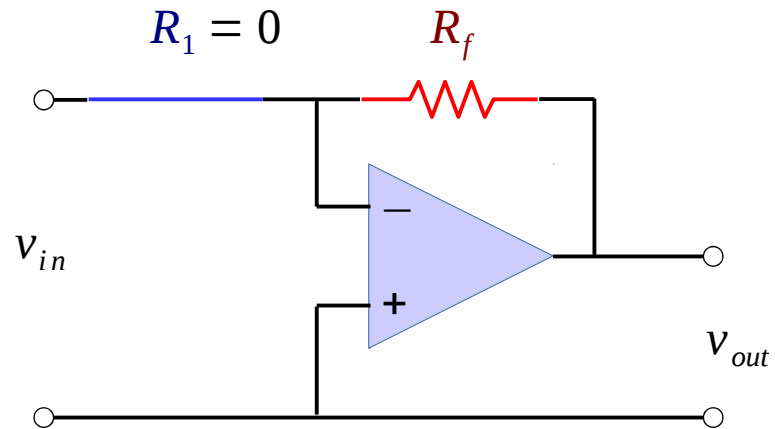

$$V_{out} = -i_{in} R_f$$

<http://hyperphysics.phy-astr.gsu.edu/hbase/electronic/opampi.html#c1>


V → I Amplifier

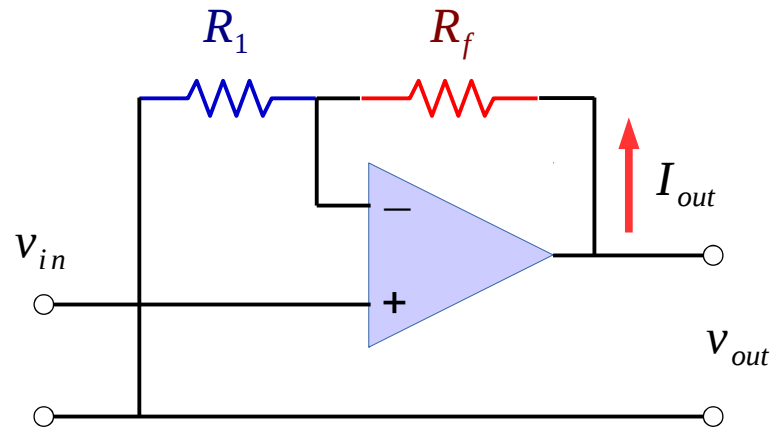

$$I_{out} = \frac{V_{in}}{R_1}$$


<http://hyperphysics.phy-astr.gsu.edu/hbase/electronic/opampi.html#c1>

Integrator

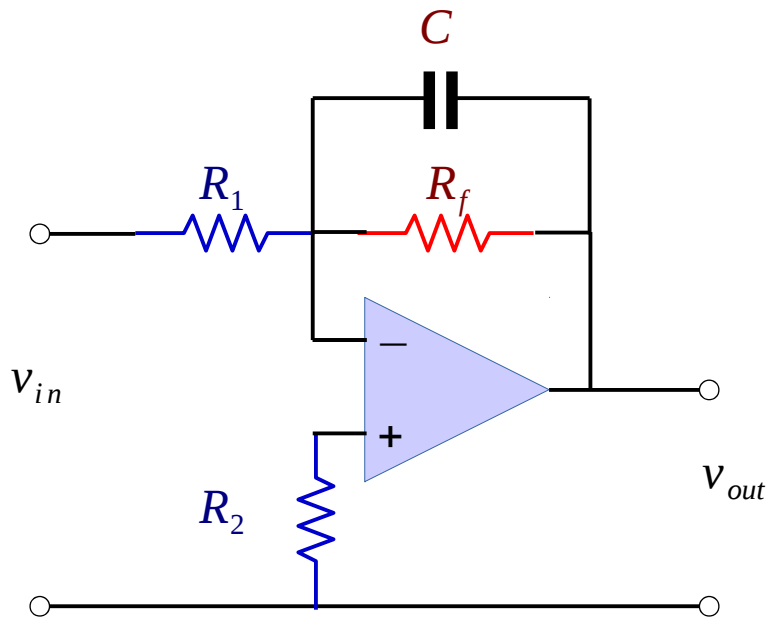


<http://hyperphysics.phy-astr.gsu.edu/hbase/electronic/opampi.html#c1>

Differentiator

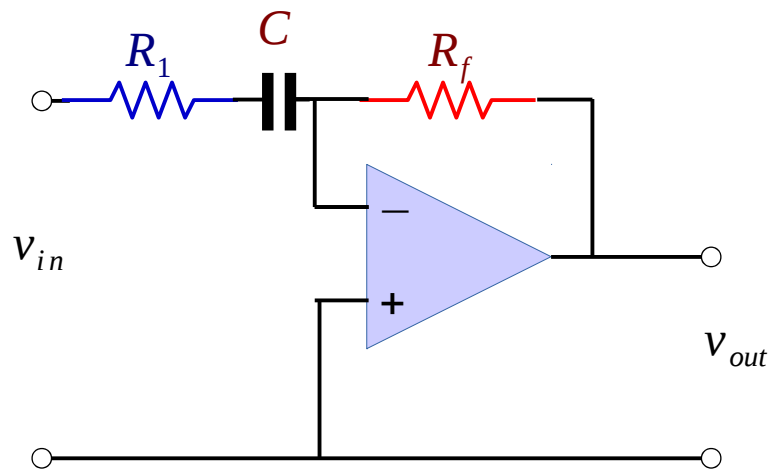

<http://hyperphysics.phy-astr.gsu.edu/hbase/electronic/opampi.html#c1>


Summing Amplifier

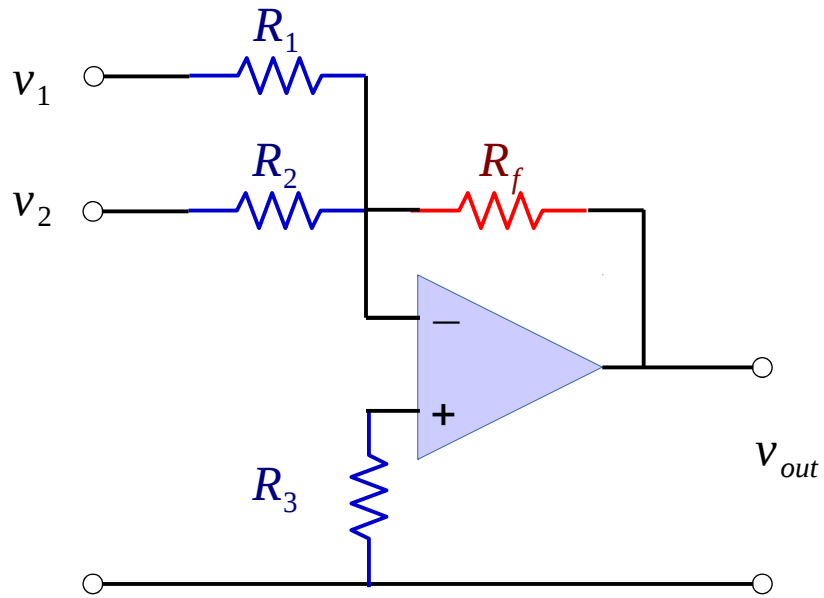

$$v_{out} = -[V_1 + V_2]$$

<http://hyperphysics.phy-astr.gsu.edu/hbase/electronic/opamp.html#c1>


Difference Amplifier

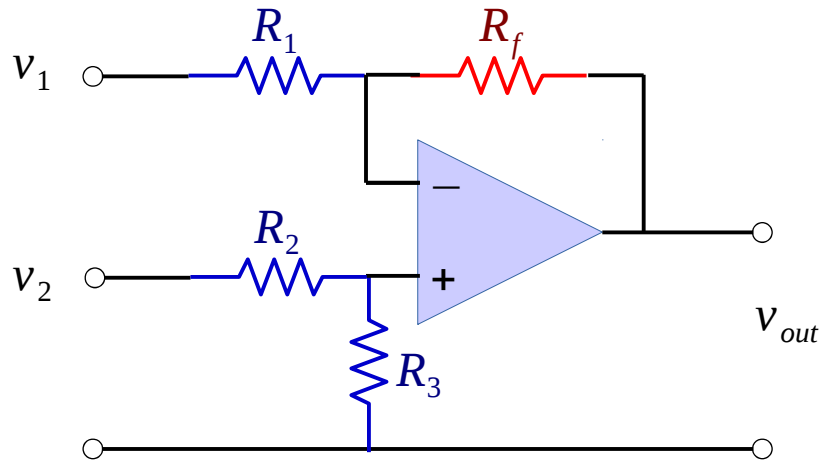

$$V_{out} = -[V_1 - V_2]$$

<http://hyperphysics.phy-astr.gsu.edu/hbase/electronic/opamp1.html#c1>

Differential Amplifier

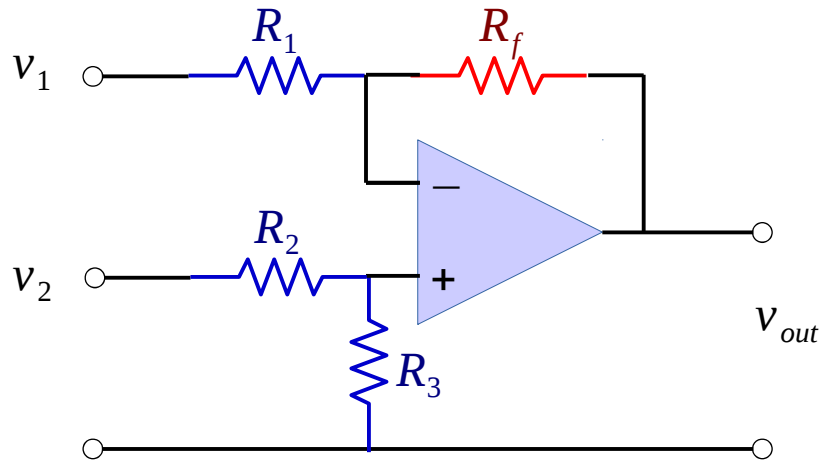

$$v_{out} = v_2 \frac{(R_f + R_1)}{(R_3 + R_2)} - v_1 \frac{R_f}{R_1}$$

<http://hyperphysics.phy-astr.gsu.edu/hbase/electronic/opamp.html#c1>

References

- [1] en.wikipedia.org
- [2] <http://hyperphysics.phy-astr.gsu.edu/>