

Truth Table (2A)

Copyright (c) 2011-2013 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".

Please send corrections (or suggestions) to youngwlim@hotmail.com.

This document was produced by using OpenOffice and Octave.


Truth Table and minterms (1)

x	y	z			
0	0	0	→	the case when x=0 and y=0 and z=0	↔ $\bar{x}\bar{y}\bar{z} = 1$
0	0	1	→	the case when x=0 and y=0 and z=1	↔ $\bar{x}\bar{y}z = 1$
0	1	0	→	the case when x=0 and y=1 and z=0	↔ $\bar{x}y\bar{z} = 1$
0	1	1	→	the case when x=0 and y=1 and z=1	↔ $\bar{x}yz = 1$
1	0	0	→	the case when x=1 and y=0 and z=0	↔ $x\bar{y}\bar{z} = 1$
1	0	1	→	the case when x=1 and y=0 and z=1	↔ $x\bar{y}z = 1$
1	1	0	→	the case when x=1 and y=1 and z=0	↔ $xy\bar{z} = 1$
1	1	1	→	the case when x=1 and y=1 and z=1	↔ $xyz = 1$

inputs

All possible combination of inputs

$$x\bar{y}z = 1 \quad \leftrightarrow$$

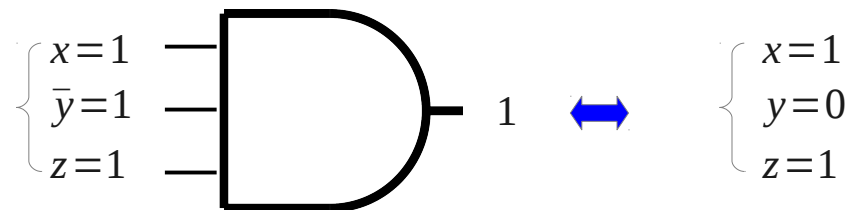

For the output of an **and** gate to be 1, all inputs must be 1

Truth Table and minterms (2)

	x	y	z
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
→ 5	1	0	1
6	1	1	0
7	1	1	1

index

inputs

All possible combination of inputs

the case when the minterm

the case when the minterm

the case when the minterm

the case when the minterm

the case when the minterm

the case when the minterm

the case when the minterm

the case when the minterm

$$m_0 = \bar{x}\bar{y}\bar{z} = 1$$

$$m_1 = \bar{x}\bar{y}z = 1$$

$$m_2 = \bar{x}y\bar{z} = 1$$


$$m_3 = \bar{x}yz = 1$$

$$m_4 = x\bar{y}\bar{z} = 1$$

$$m_5 = x\bar{y}z = 1$$

$$m_6 = xy\bar{z} = 1$$

$$m_7 = xyz = 1$$

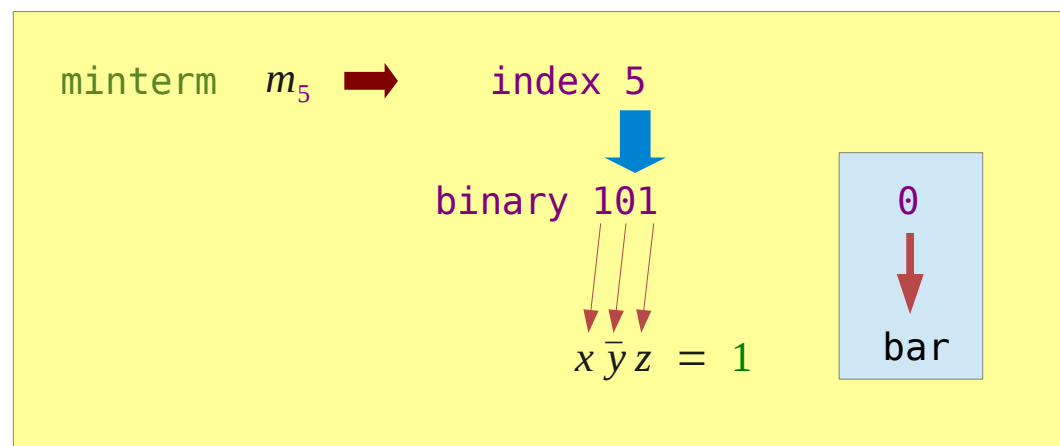


Truth Table and MAXterms (1)

x	y	z			
0	0	0	→	the case when x=0 and y=0 and z=0	↔ $x + y + z = 0$
0	0	1	→	the case when x=0 and y=0 and z=1	↔ $x + y + \bar{z} = 0$
0	1	0	→	the case when x=0 and y=1 and z=0	↔ $x + \bar{y} + z = 0$
0	1	1	→	the case when x=0 and y=1 and z=1	↔ $x + \bar{y} + \bar{z} = 0$
1	0	0	→	the case when x=1 and y=0 and z=0	↔ $\bar{x} + y + z = 0$
1	0	1	→	the case when x=1 and y=0 and z=1	↔ $\bar{x} + y + \bar{z} = 0$
1	1	0	→	the case when x=1 and y=1 and z=0	↔ $\bar{x} + \bar{y} + z = 0$
1	1	1	→	the case when x=1 and y=1 and z=1	↔ $\bar{x} + \bar{y} + \bar{z} = 0$

inputs

All possible combination of inputs
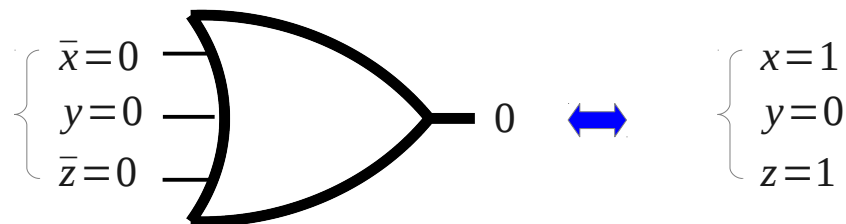
$$\bar{x} + y + \bar{z} = 0 \quad \leftrightarrow$$



For the output of an **or** gate to be 0, all inputs must be 0

Truth Table and MAXterms (2)

	x	y	z
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
→ 5	1	0	1
6	1	1	0
7	1	1	1

index

inputs

All possible combination of inputs

the case when the MAXterm
 the case when the MAXterm
 the case when the MAXterm
 the case when the MAXterm
 the case when the MAXterm
 the case when the MAXterm
 the case when the MAXterm
 the case when the MAXterm

$$M_0 = x + y + z = 0$$

$$M_1 = x + y + \bar{z} = 0$$

$$M_2 = x + \bar{y} + z = 0$$


$$M_3 = x + \bar{y} + \bar{z} = 0$$

$$M_4 = \bar{x} + y + z = 0$$


$$M_5 = \bar{x} + y + \bar{z} = 0$$

$$M_6 = \bar{x} + \bar{y} + z = 0$$
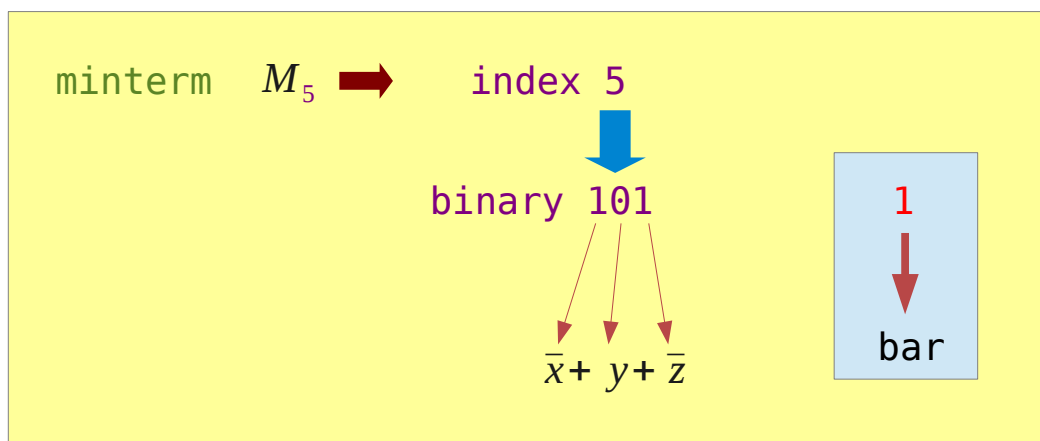
$$M_7 = \bar{x} + \bar{y} + \bar{z} = 0$$



Maxterm and minterm Conditions

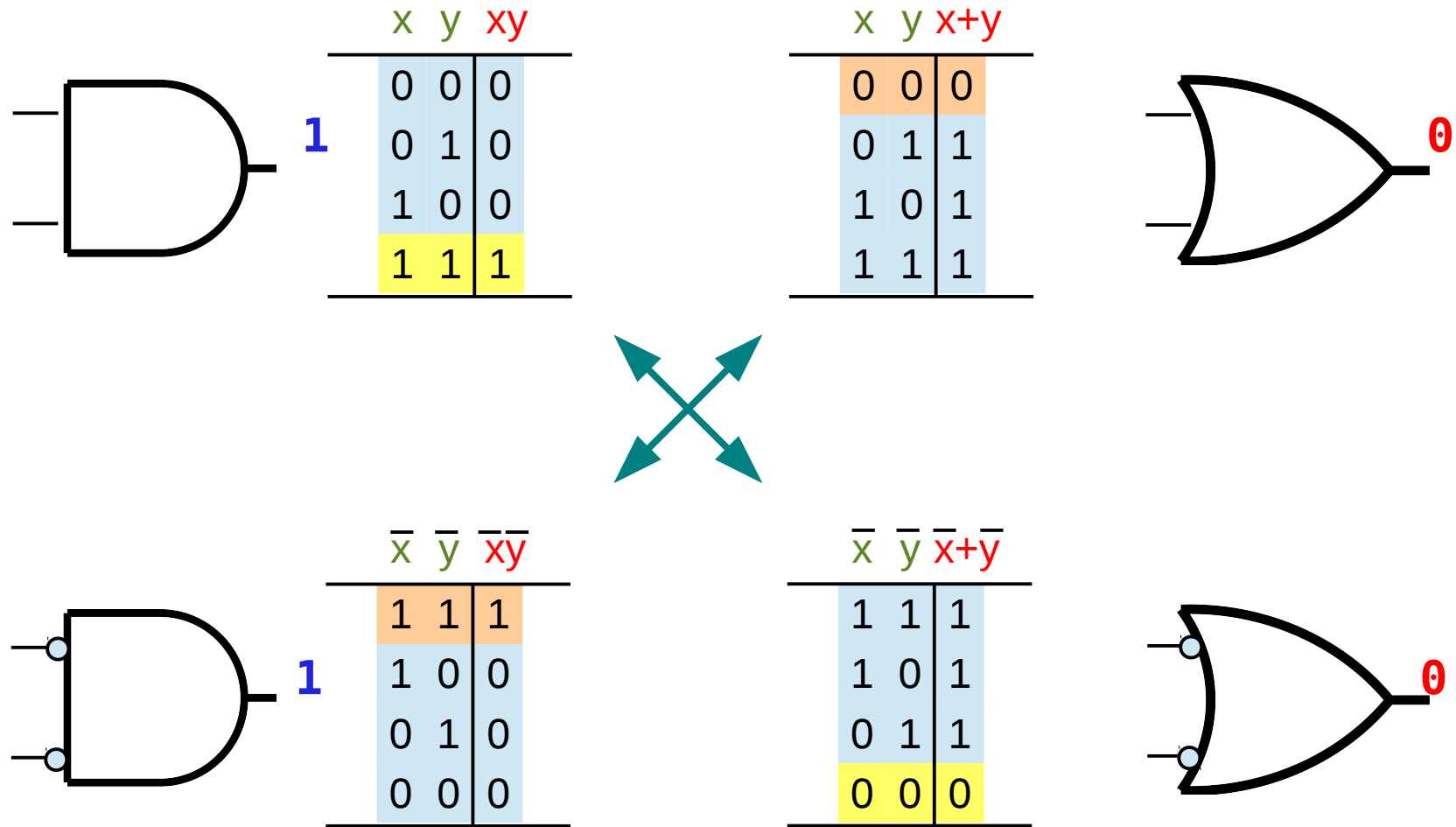

Boolean Function with minterms (1)

	x	y	z	F
0	0	0	0	0
→ 1	0	0	1	1
2	0	1	0	0
→ 3	0	1	1	1
→ 4	1	0	0	1
5	1	0	1	0
6	1	1	0	0
7	1	1	1	0

index



inputs output


All possible combination of inputs

The output F becomes 1, for one of the three following cases

(the case when $x=0$ and $y=0$ and $z=1$) ↔ $m_1 = \bar{x}\bar{y}z = 1$

or (the case when $x=0$ and $y=1$ and $z=1$) ↔ $m_3 = \bar{x}yz = 1$

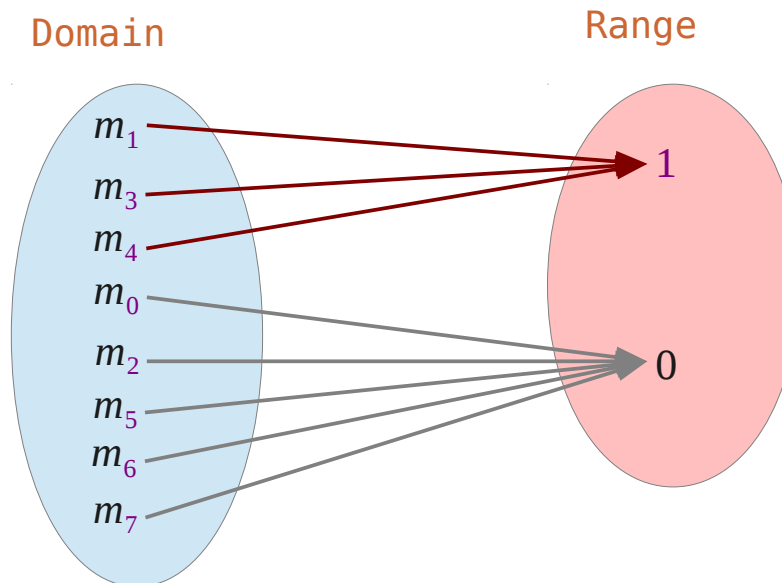or (the case when $x=1$ and $y=0$ and $z=0$) ↔ $m_4 = x\bar{y}\bar{z} = 1$



Boolean Function with minterms (2)

	x	y	z	F
0	0	0	0	0
→ 1	0	0	1	1
2	0	1	0	0
→ 3	0	1	1	1
→ 4	1	0	0	1
5	1	0	1	0
6	1	1	0	0
7	1	1	1	0

index } }
inputs output

All possible combination of inputs

The output F becomes 1,
 either $m_1=1$ or $m_3=1$ or $m_4=1$

$$m_1 + m_3 + m_4 = 1 \quad \Rightarrow \quad F = 1$$

$$\Leftrightarrow F = m_1 + m_3 + m_4$$

The output F becomes 0,
 either $m_0=1$ or $m_2=1$ or $m_5=1$ or $m_6=1$ or $m_7=1$

$$m_0 + m_2 + m_5 + m_6 + m_7 = 1 \quad \Rightarrow \quad F = 0$$

$$\Leftrightarrow \bar{F} = m_0 + m_2 + m_5 + m_6 + m_7$$

For the output of an **or** gate to be 1,
 at least one must be 1

Boolean Function with Maxterms (1)

	x	y	z	F
→ 0	0	0	0	0
1	0	0	1	1
→ 2	0	1	0	0
3	0	1	1	1
4	1	0	0	1
→ 5	1	0	1	0
→ 6	1	1	0	0
→ 7	1	1	1	0

The output F becomes 0,
for one of the five following cases

(the case when $x=0$ and $y=0$ and $z=0$) ↔ $x + y + z = 0$

or (the case when $x=0$ and $y=1$ and $z=0$) ↔ $x + \bar{y} + z = 0$


or (the case when $x=1$ and $y=0$ and $z=1$) ↔ $\bar{x} + y + \bar{z} = 0$

or (the case when $x=1$ and $y=1$ and $z=0$) ↔ $\bar{x} + \bar{y} + z = 0$

or (the case when $x=1$ and $y=1$ and $z=1$) ↔ $\bar{x} + \bar{y} + \bar{z} = 0$

index
inputs output

All possible
combination of inputs

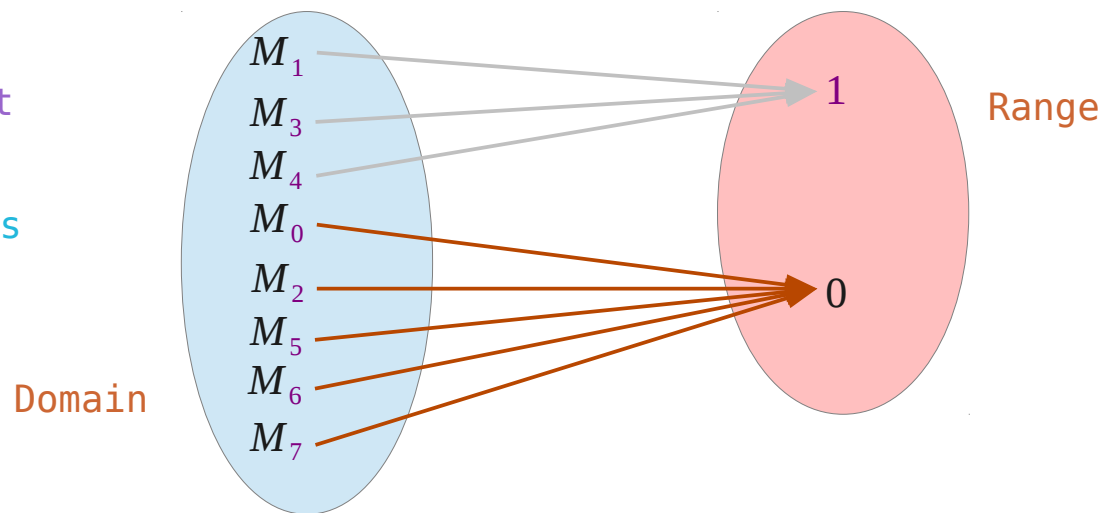

Boolean Function with Maxterms (2)

	x	y	z	F
→ 0	0	0	0	0
1	0	0	1	1
→ 2	0	1	0	0
3	0	1	1	1
4	1	0	0	1
→ 5	1	0	1	0
→ 6	1	1	0	0
→ 7	1	1	1	0

index } }
inputs output

All possible combination of inputs

The output F becomes 0,

either $M_0=0$ or $M_2=0$ or $M_5=0$ or $M_6=0$ or $M_7=0$

$$M_0 \cdot M_2 \cdot M_5 \cdot M_6 \cdot M_7 = 0 \quad \Rightarrow \quad F = 0$$

$$\Leftrightarrow F = M_0 \cdot M_2 \cdot M_5 \cdot M_6 \cdot M_7$$

The output F becomes 1,

either $M_1=0$ or $M_3=0$ or $M_4=0$

$$M_1 \cdot M_3 \cdot M_4 = 0 \quad \Rightarrow \quad F = 1$$

$$\Leftrightarrow \bar{F} = M_1 \cdot M_3 \cdot M_4$$

For the output of an **and** gate to be 0,
at least one input must be 0

Complimentary Relations

	x	y	z	F
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	1
4	1	0	0	1
5	1	0	1	0
6	1	1	0	0
7	1	1	1	0

index } }
inputs output

All possible
combination of inputs

$$m_i = \overline{M_i}$$

$$M_i = \overline{m_i}$$

$$F(x, y, z) = m_1 + m_3 + m_4$$

The output F becomes 1,

either $m_1=1$ or $m_3=1$ or $m_4=1$

For the output of an **or** gate to be 1,
at least one must be 1

$$\overline{F}(x, y, z) = m_0 + m_2 + m_5 + m_6 + m_7$$

$$\Leftrightarrow F(x, y, z) = \overline{m_0 + m_2 + m_5 + m_6 + m_7}$$

$$= \overline{m_0} \cdot \overline{m_2} \cdot \overline{m_5} \cdot \overline{m_6} \cdot \overline{m_7}$$

$$F(x, y, z) = M_0 \cdot M_2 \cdot M_5 \cdot M_6 \cdot M_7$$

The output F becomes 0,

either $M_0=0$ or $M_2=0$ or $M_5=0$ or $M_6=0$ or $M_7=0$

For the output of an **and** gate to be 0,
at least one input must be 0

Boolean Function Summary

	x	y	z	F
0	0	0	0	
1	0	0	1	1
2	0	1	0	
3	0	1	1	1
4	1	0	0	1
5	1	0	1	
6	1	1	0	
7	1	1	1	

The output F becomes 1,

for the cases

1) when $m_1=1$ or $m_3=1$ or $m_4=1$

$$F(x, y, z) = m_1 + m_3 + m_4 \Rightarrow F=1$$

2) when $M_1=0$ or $M_3=0$ or $M_4=0$

$$\bar{F}(x, y, z) = M_1 \cdot M_3 \cdot M_4 \Rightarrow F=1 (\bar{F}=0)$$

	x	y	z	F
0	0	0	0	0
1	0	0	1	
2	0	1	0	0
3	0	1	1	
4	1	0	0	
5	1	0	1	0
6	1	1	0	0
7	1	1	1	0

The output F becomes 0,

for the cases

1) when $m_0=1$ or $m_2=1$ or $m_5=1$ or $m_6=1$ or $m_7=1$

$$\bar{F}(x, y, z) = m_0 + m_2 + m_5 + m_6 + m_7 \Rightarrow F=0 (\bar{F}=1)$$

2) when $M_0=0$ or $M_2=0$ or $M_5=0$ or $M_6=0$ or $M_7=0$

$$F(x, y, z) = M_0 \cdot M_2 \cdot M_5 \cdot M_6 \cdot M_7 \Rightarrow F=0$$

Boolean Function Summary

	x	y	z	F
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	1
4	1	0	0	1
5	1	0	1	0
6	1	1	0	0
7	1	1	1	0

	x	y	z	F
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	1
4	1	0	0	1
5	1	0	1	0
6	1	1	0	0
7	1	1	1	0

$$F(x, y, z) = m_1 + m_3 + m_4 \quad \Rightarrow \quad F=1$$

$$F(x, y, z) = M_0 \cdot M_2 \cdot M_5 \cdot M_6 \cdot M_7 \quad \Rightarrow \quad F=0$$

$$\bar{F}(x, y, z) = m_0 + m_2 + m_5 + m_6 + m_7 \quad \Rightarrow \quad F=0 \quad (\bar{F}=1)$$

$$\bar{F}(x, y, z) = M_1 \cdot M_3 \cdot M_4 \quad \Rightarrow \quad F=1 \quad (\bar{F}=0)$$

Truth Table

References

[1] <http://en.wikipedia.org/>