

# BJT Amplifier

## Common Emitter Amp (H.11)

20170630

Copyright (c) 2016 - 2017 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".

# References

Based

[1] Floyd, Electronic Devices 7th ed


[2] Cook,

[2] [en.wikipedia.org](https://en.wikipedia.org)


**Common Base****Common Emitter****Common Collector**

$Z_{in}$	CB : low $r_e \parallel R_E \approx r_e$	CE : med $R_1 \parallel R_2 \parallel \beta r_e$	CC : high $R_1 \parallel R_2 \parallel \beta(r_e + R_E)$
$Z_{out}$	CB : high $R_C$	CE : med $R_C$	CC : low $(r_e + \frac{R_s}{\beta}) \parallel R_E = \frac{R_s}{\beta} \parallel R_E$
$A_v$	CB : high $\frac{R_C}{r_e}, \frac{R_C \parallel R_L}{r_e}$	CE : med $\frac{R_C}{r_e}, \frac{R_C \parallel R_L}{r_e}$	CC : unity $\frac{R_E}{(r_e + R_E)} \approx 1$
$A_i$	CB : unity	CE : med	CC : high

VDB

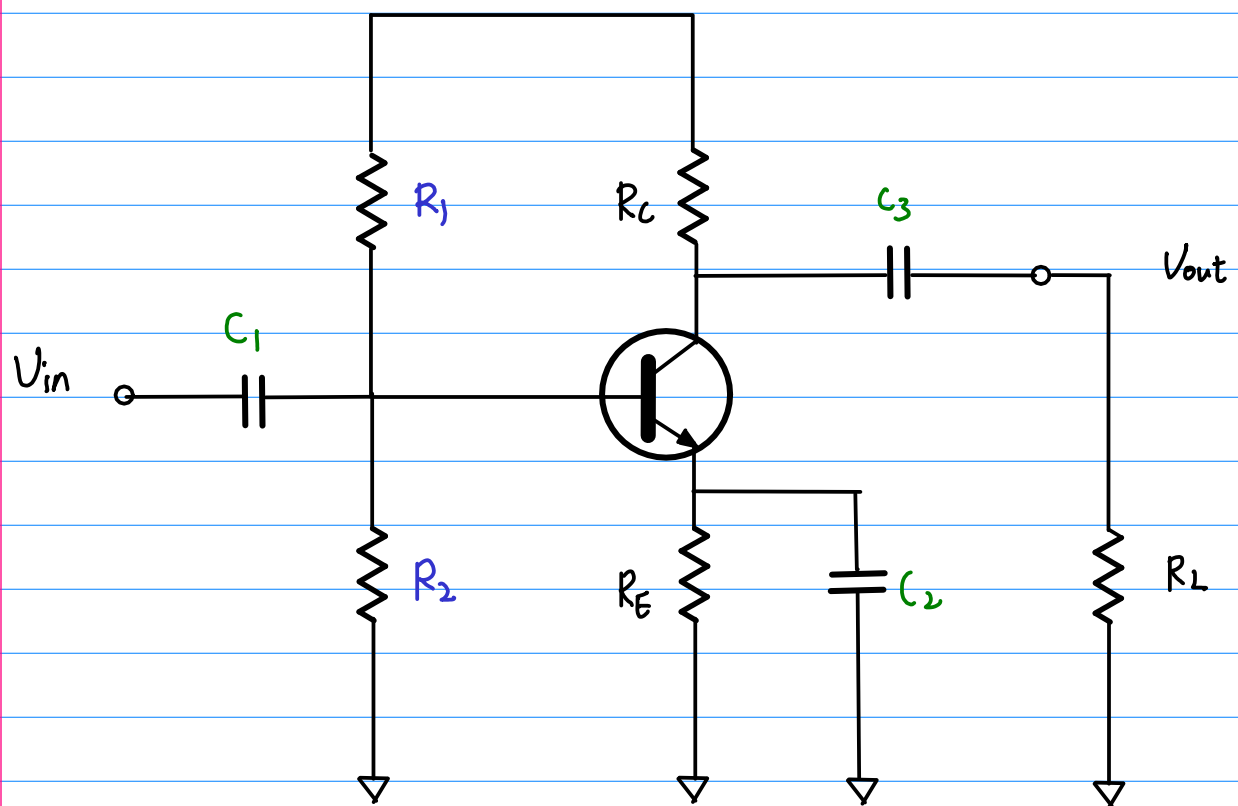


# Common Emitter Configuration

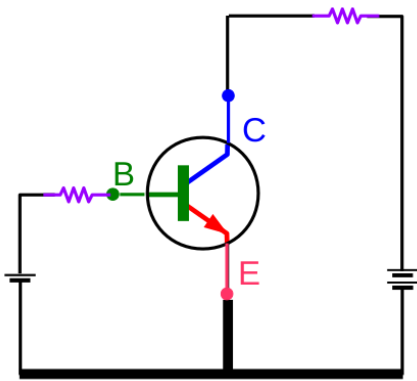


*Common Emitter*

**DC Bias**

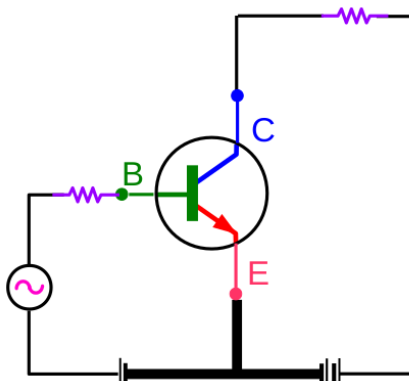



*Common Emitter*

**DC Bias + AC Signal**

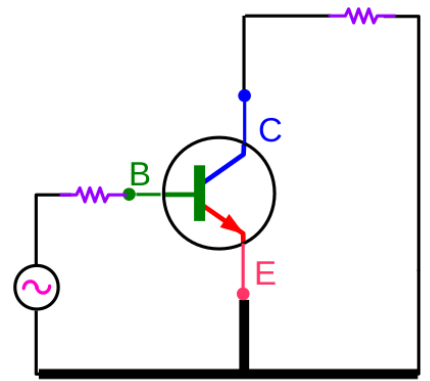


*Common Emitter*

**AC Signal**

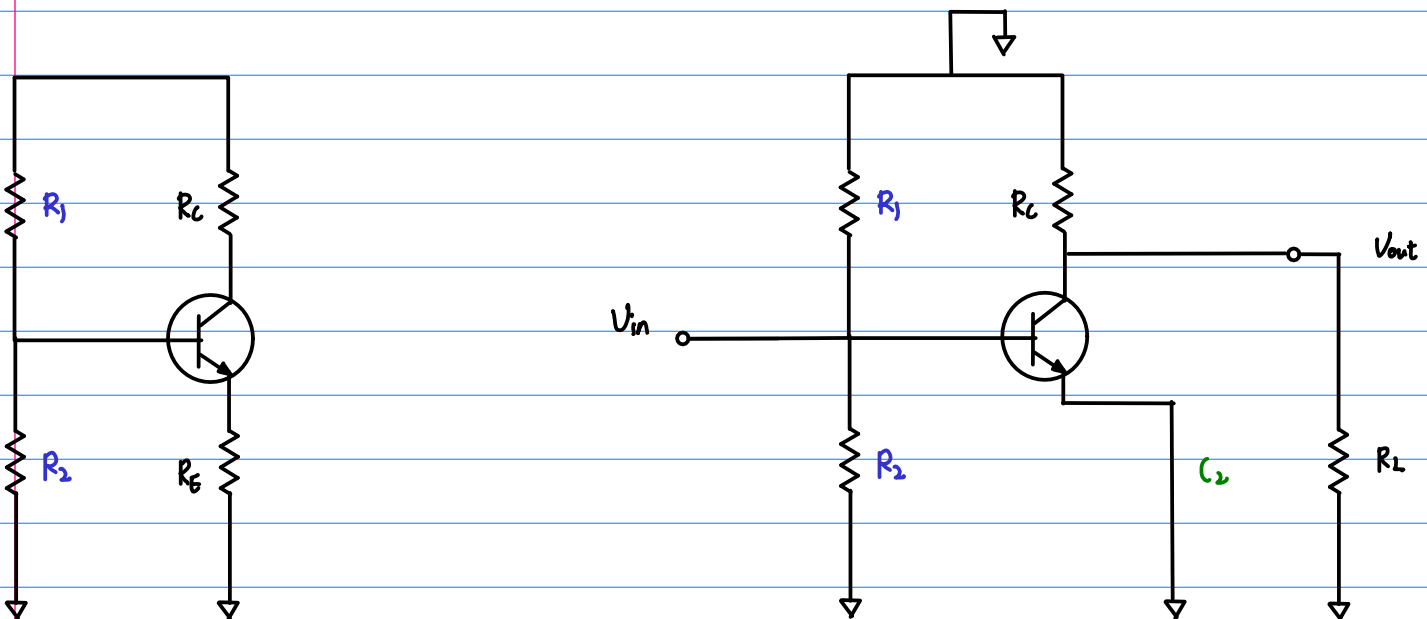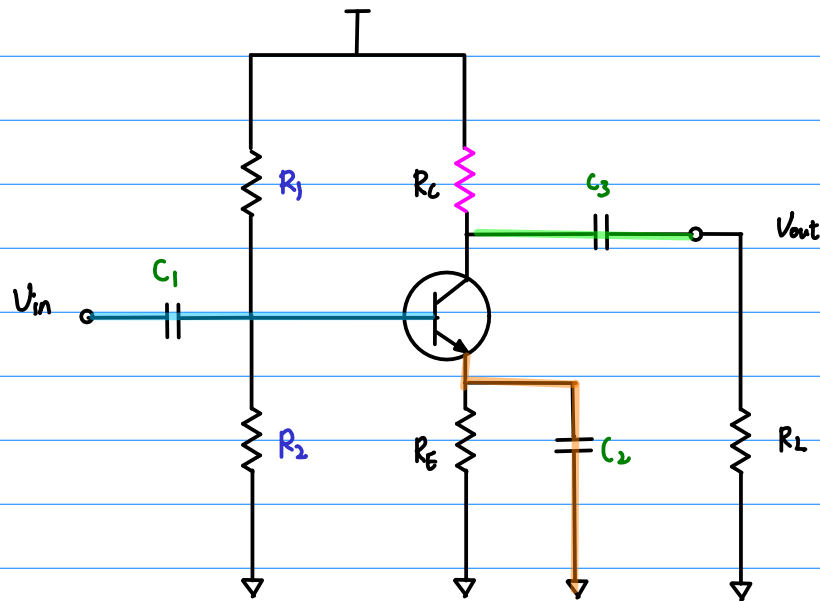

# DC Analysis

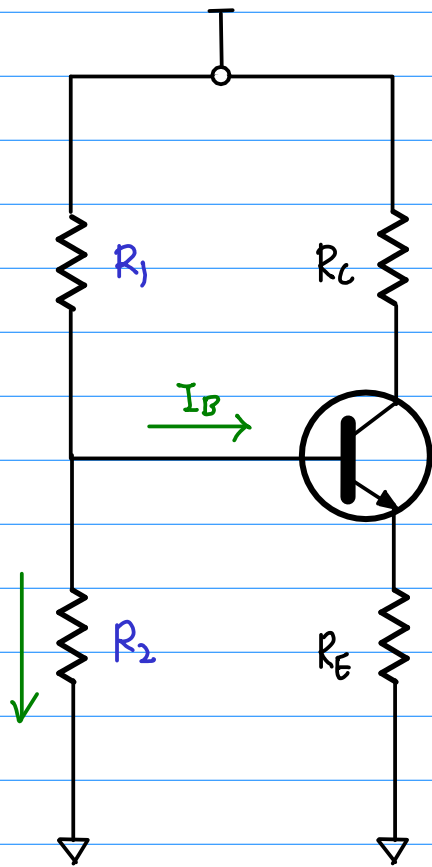

# AC Ground



$C_1, C_2, C_3$  - effectively short

their values are selected


$$\text{s.t. } X_C = \frac{1}{j\omega C} \approx 0 \Omega$$



at the signal frequency ( $\omega$ )



dc source



dc ground

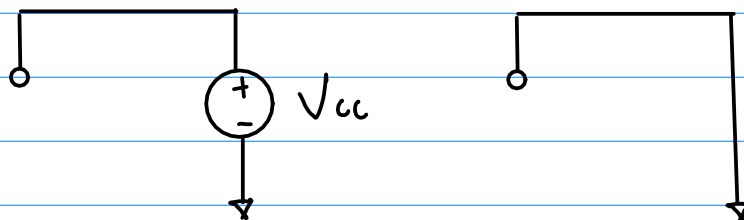

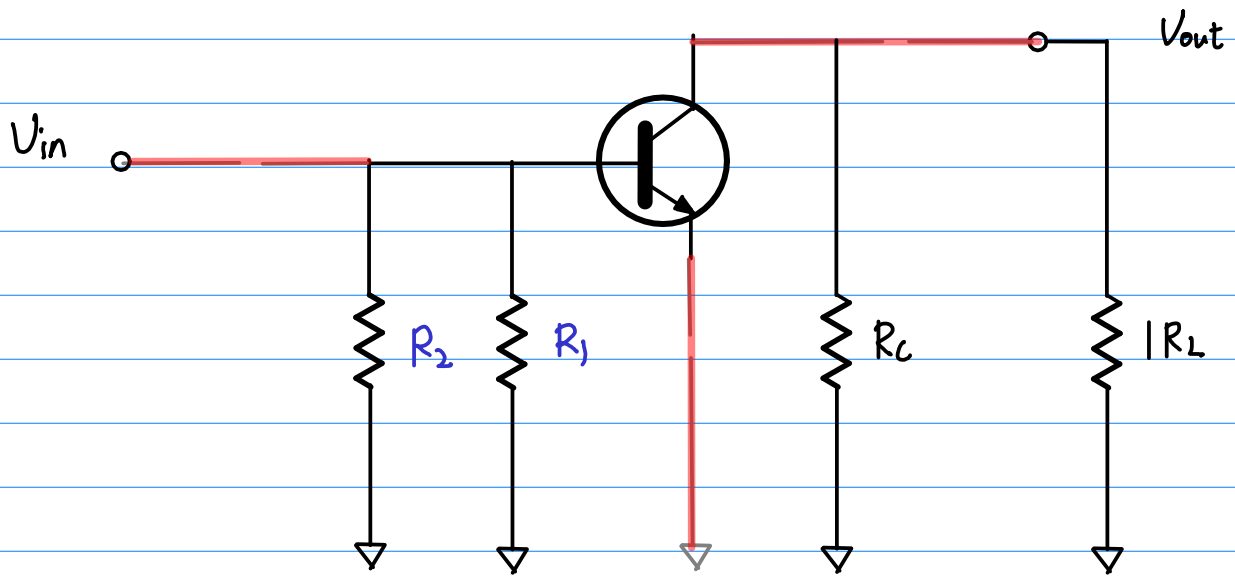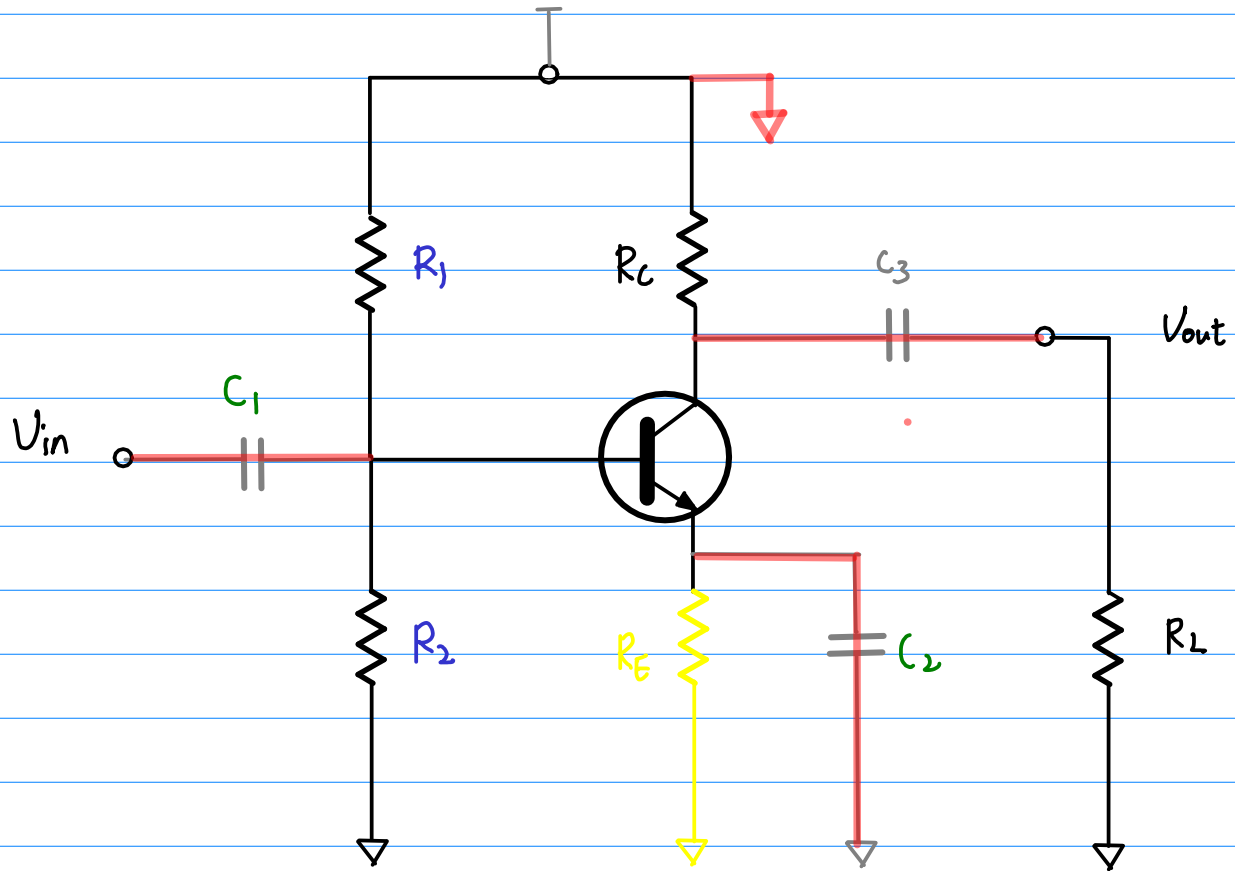






# AC Equivalent Circuit

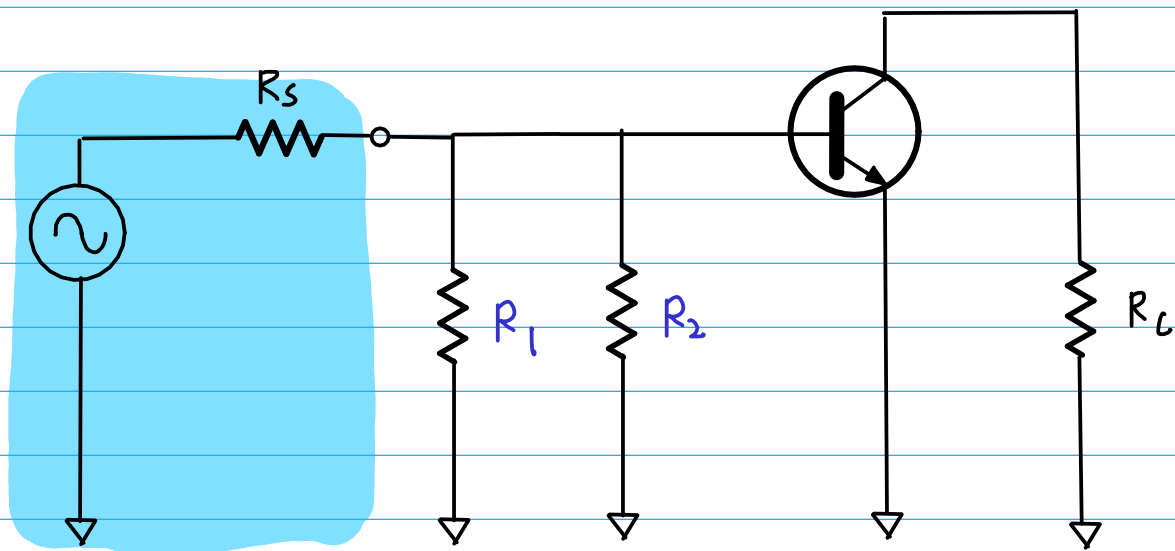
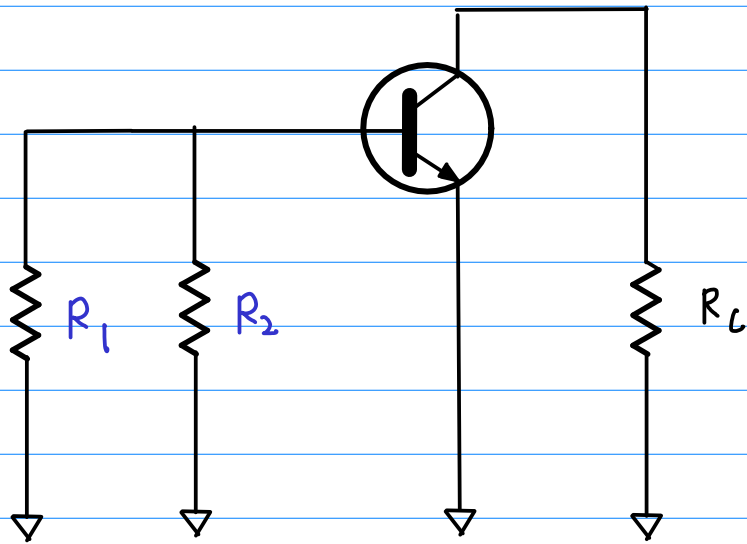


AC source




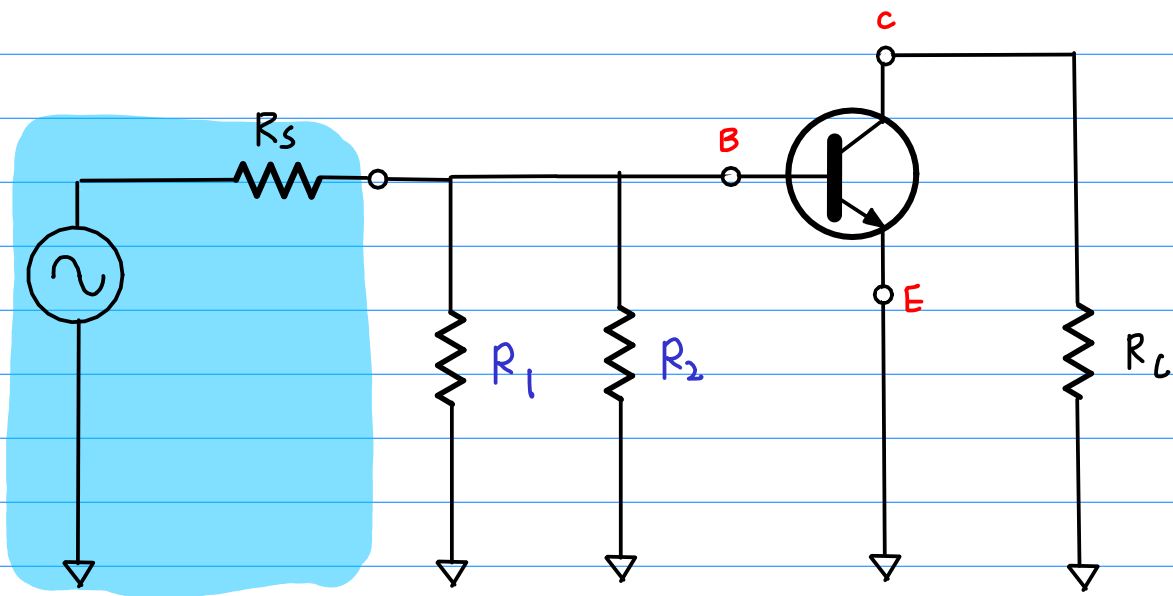


AC source

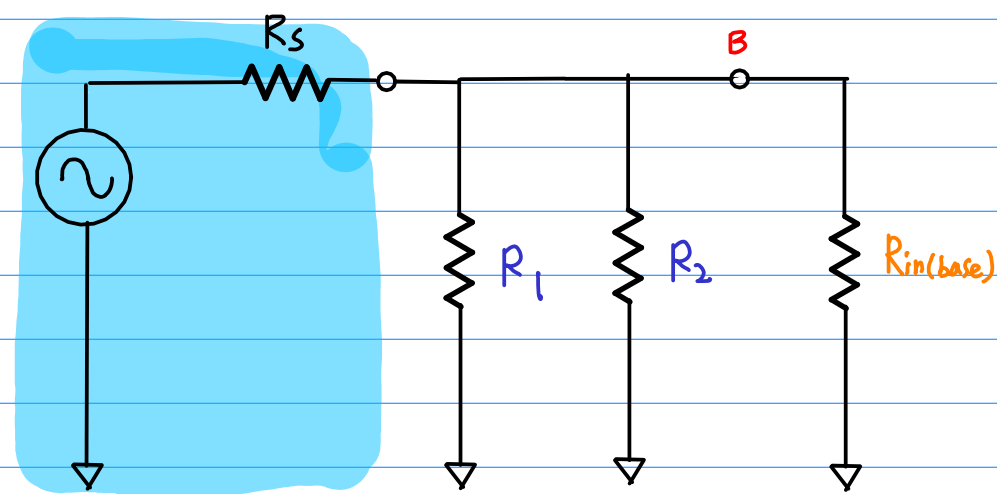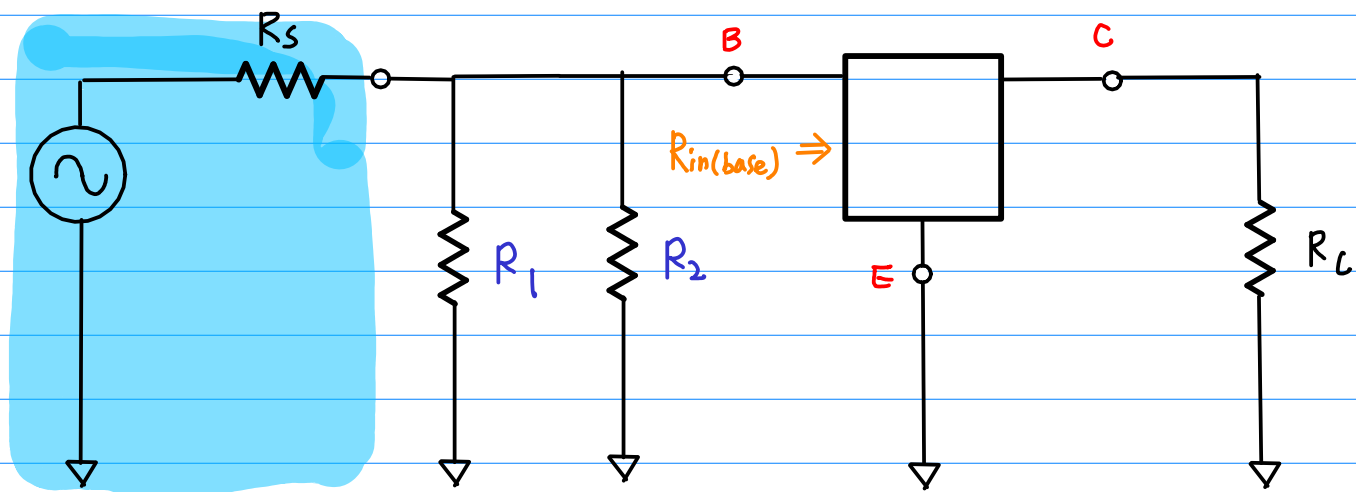


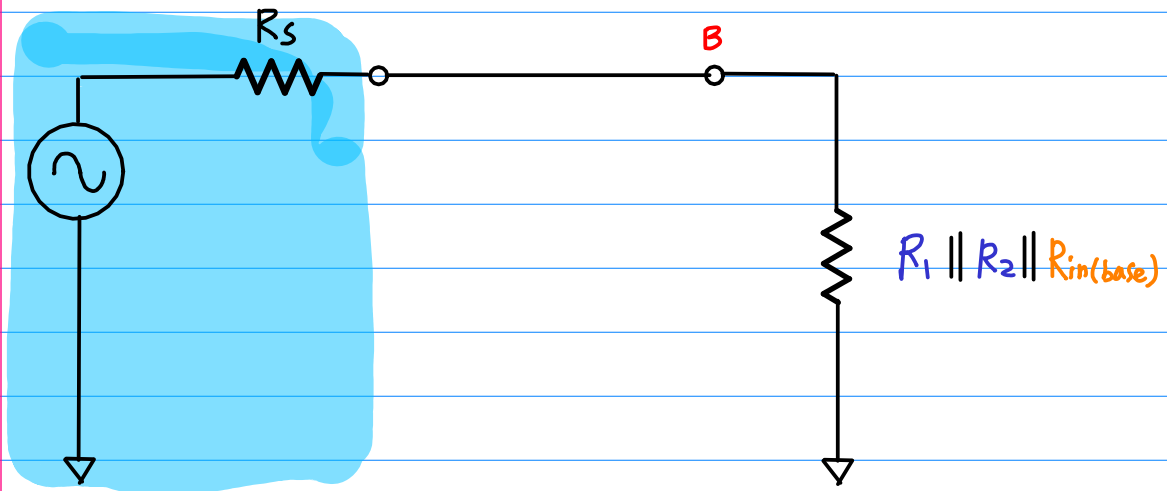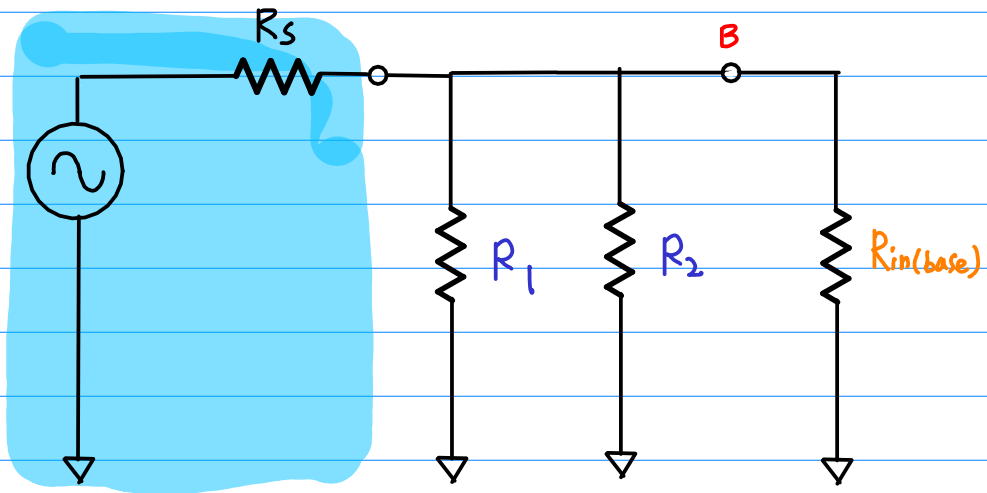


# Input Resistance

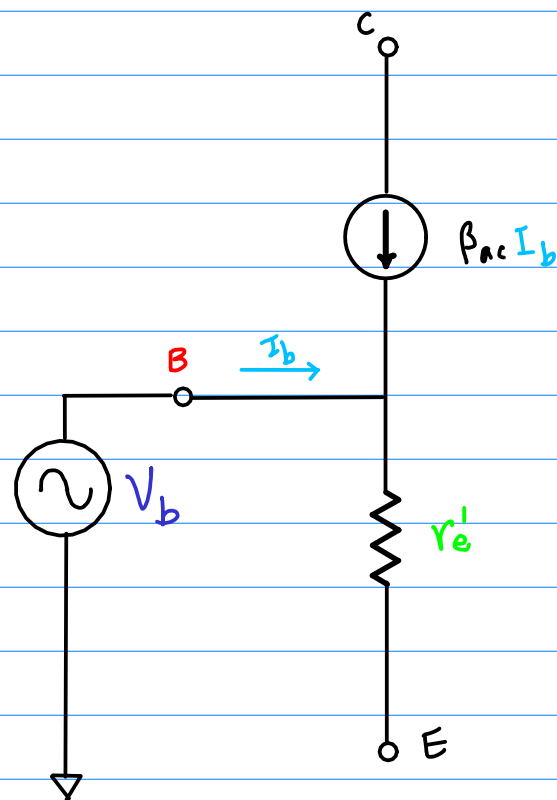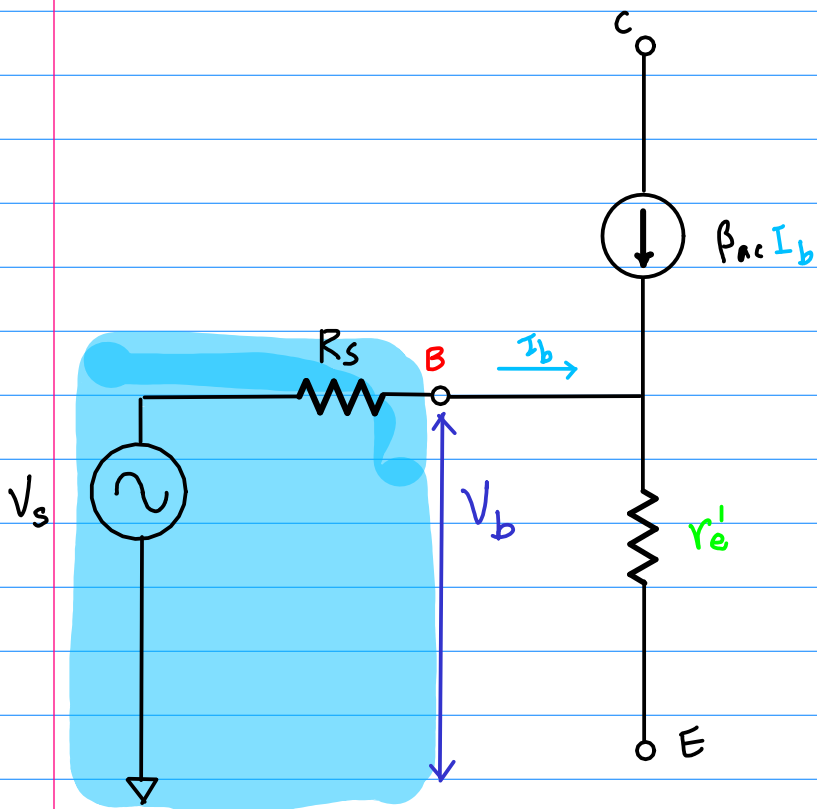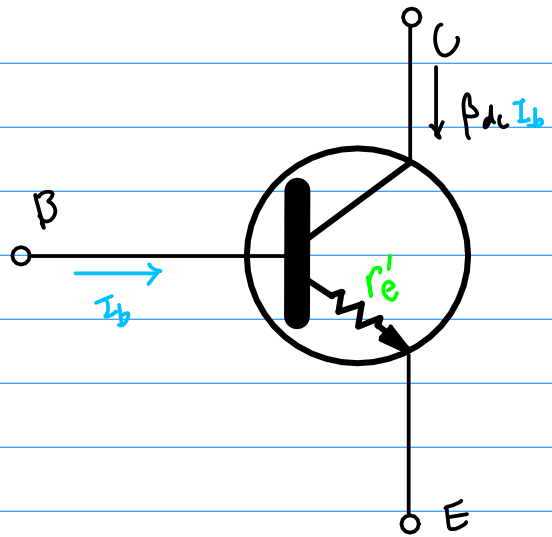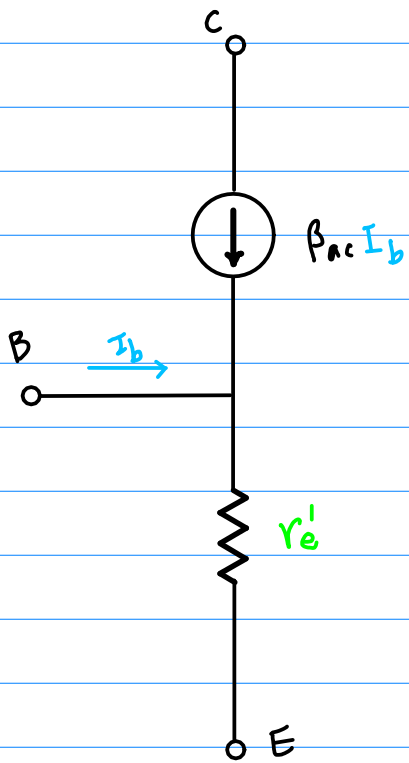



# Output Resistance

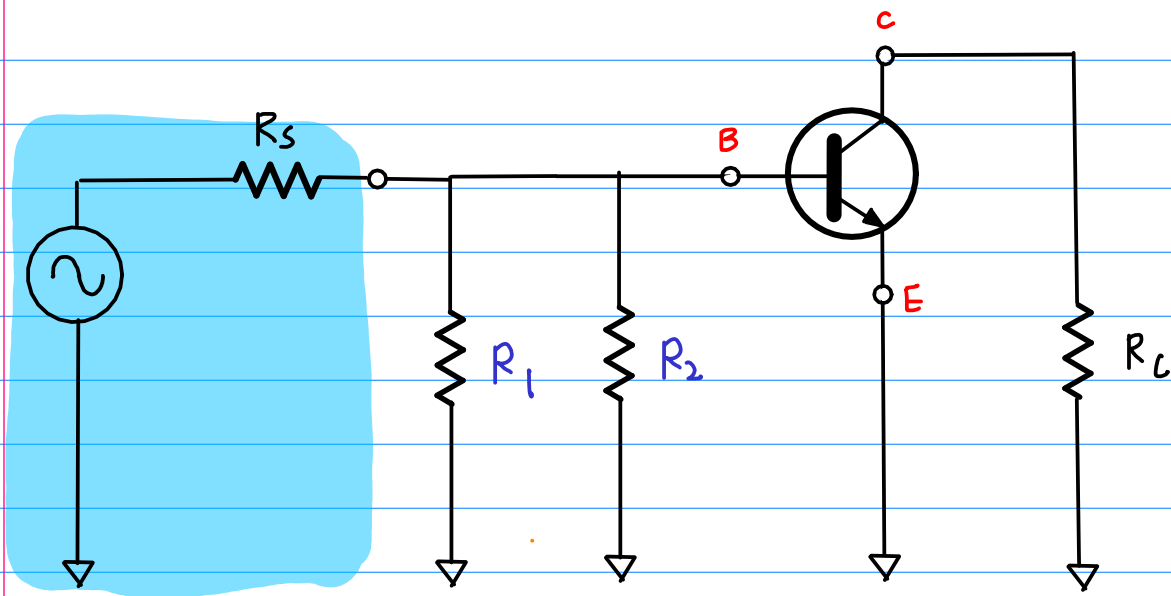


AC source

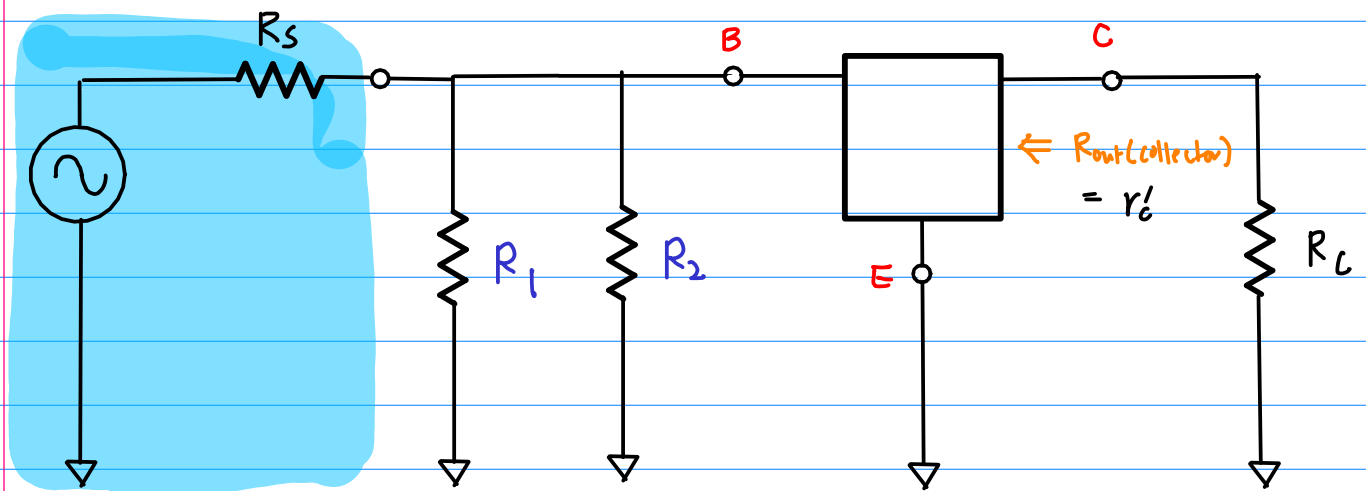
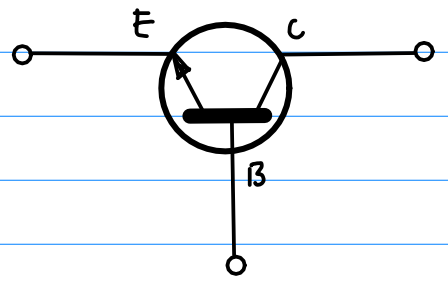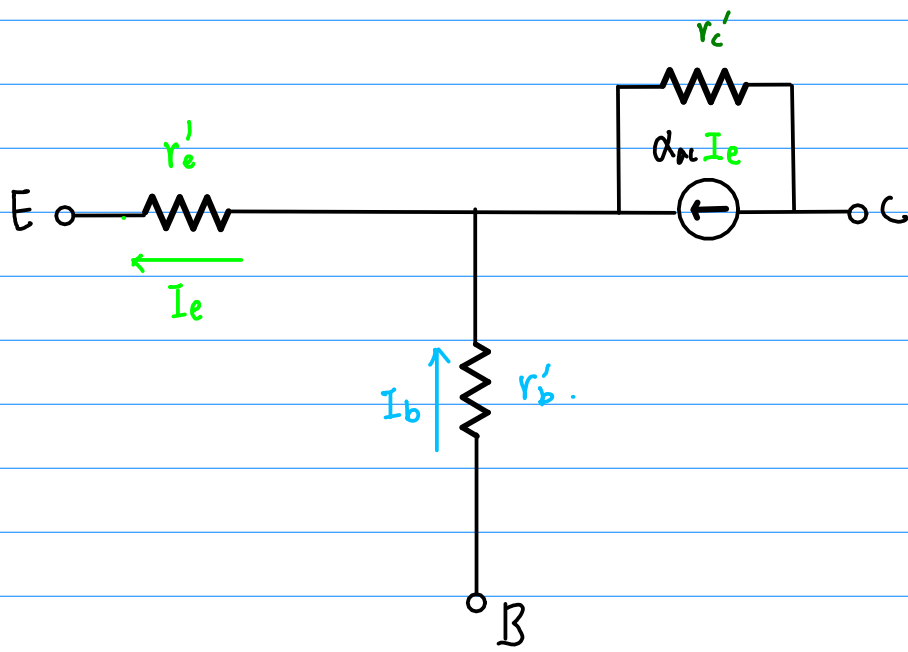
$$R_{out(collector)} = r'_c \parallel R_C \\ \approx R_C \quad (r'_c \gg R_C)$$




# Voltage Gain

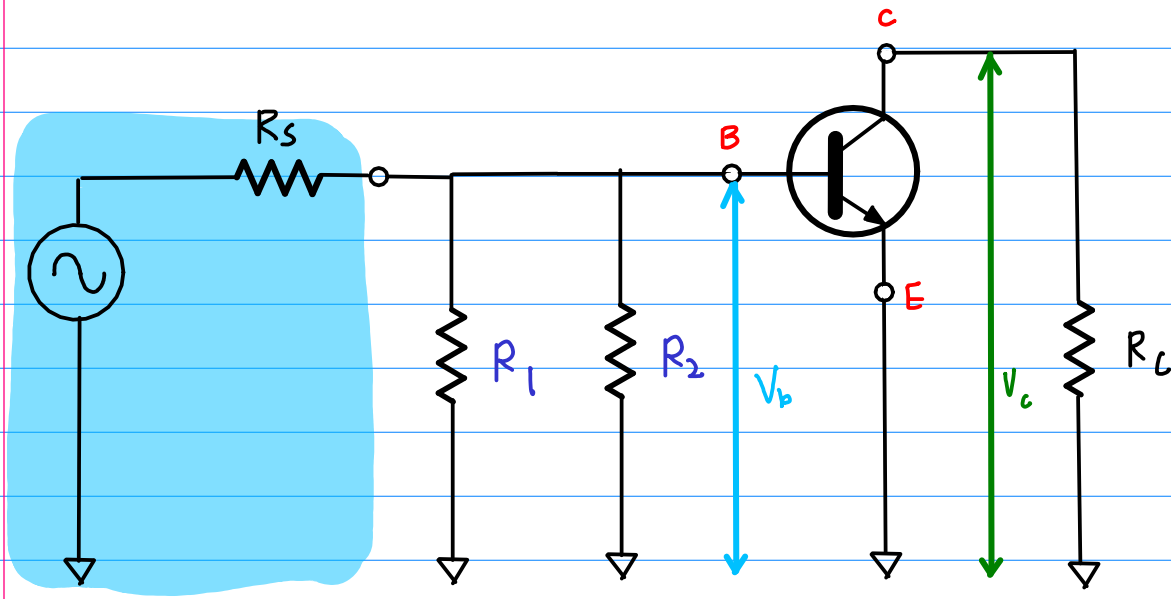


$$A_v = \frac{V_{out}}{V_{in}} = \frac{V_c}{V_b}$$
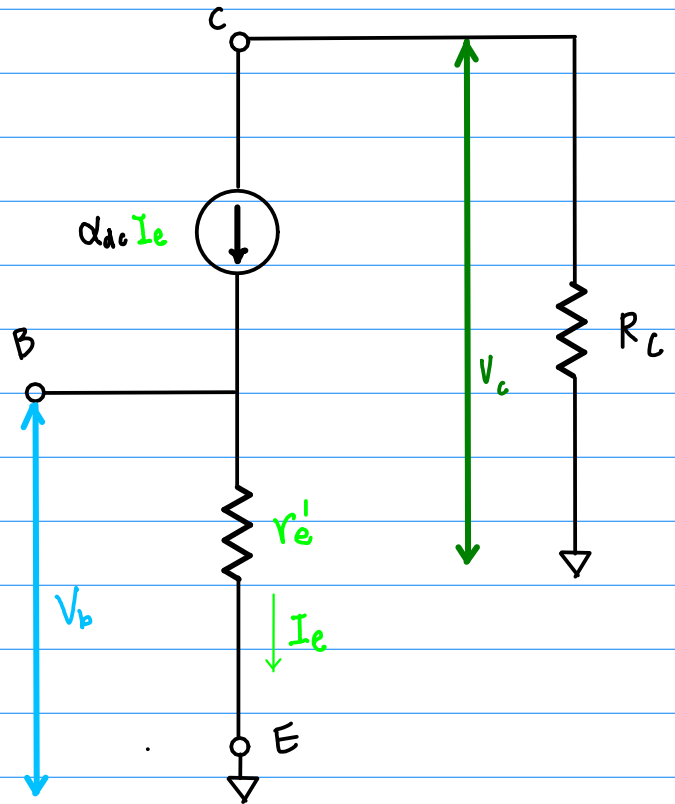
$$A_v = \frac{I_c R_C}{I_e r_e'} = \frac{R_C}{r_e'}$$



$$\text{Overall Gain } V_c/V_s = V_b/V_s \times V_c/V_b$$

attenuation  $V_b/V_s$

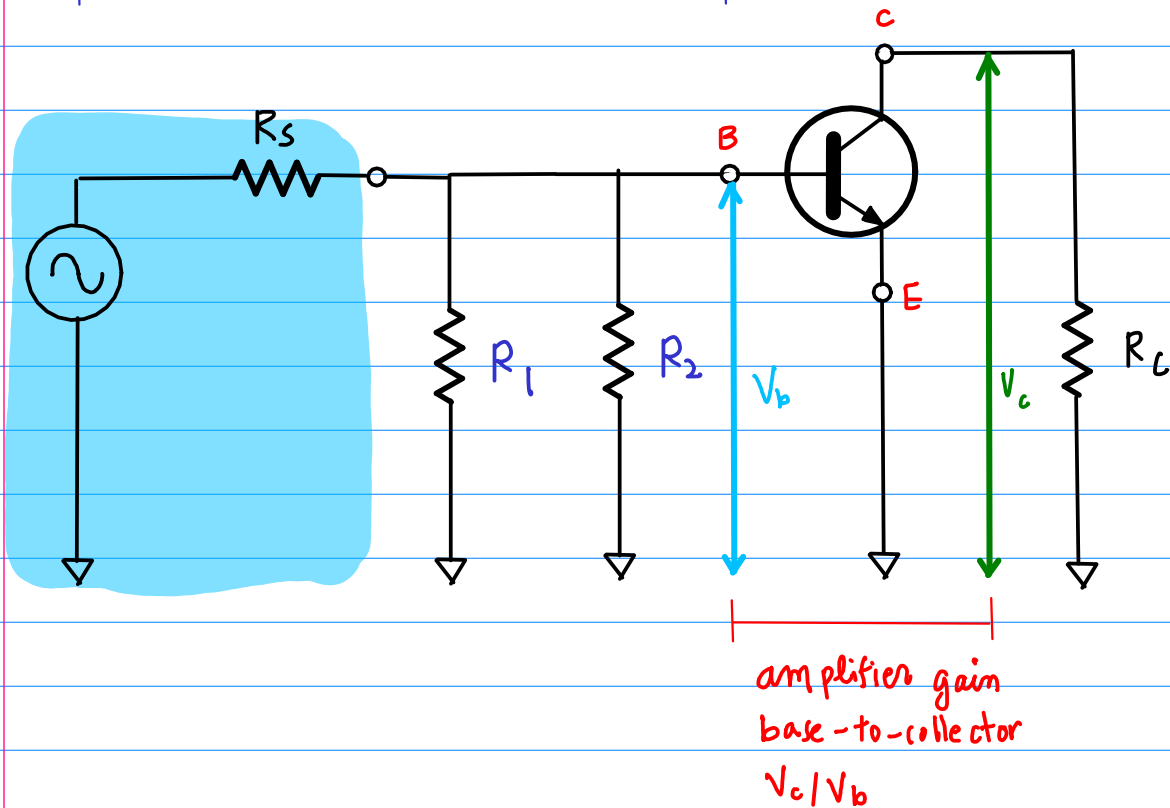


$$\text{Attenuation} = \frac{V_b}{V_s} = \frac{R_{in(tot)}}{R_s + R_{in(tot)}}$$

$$A'_v = \left( \frac{V_b}{V_s} \right) \cdot A_v = \frac{R_{in(tot)}}{R_s + R_{in(tot)}} \cdot \frac{R_c}{r_e'}$$



# Voltage Gain without Bypass Capacitor


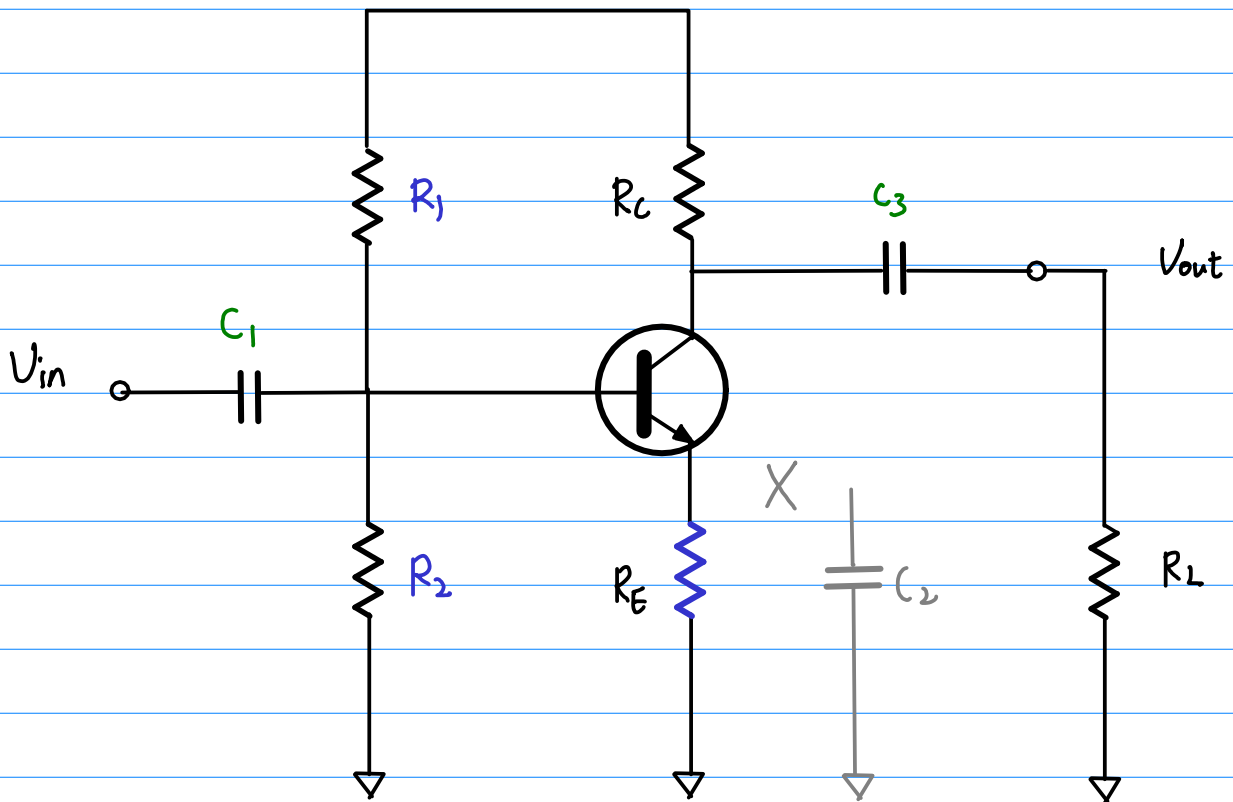



$$A_v = \frac{I_c R_c}{I_e r_e'} = \frac{R_c}{r_e'}$$

$$A_v = \frac{I_c R_c}{I_e (r_e' + R_E)} = \frac{R_c}{(r_e' + R_E)} \quad R_E \text{ decrease } A_v$$

$$A_v = \frac{I_c R_c}{I_e (r_e' + R_{E1})} = \frac{R_c}{(r_e' + R_{E1})} \approx \frac{R_c}{R_{E1}} \quad \text{swamping}$$


# Load Effect on the voltage Gain

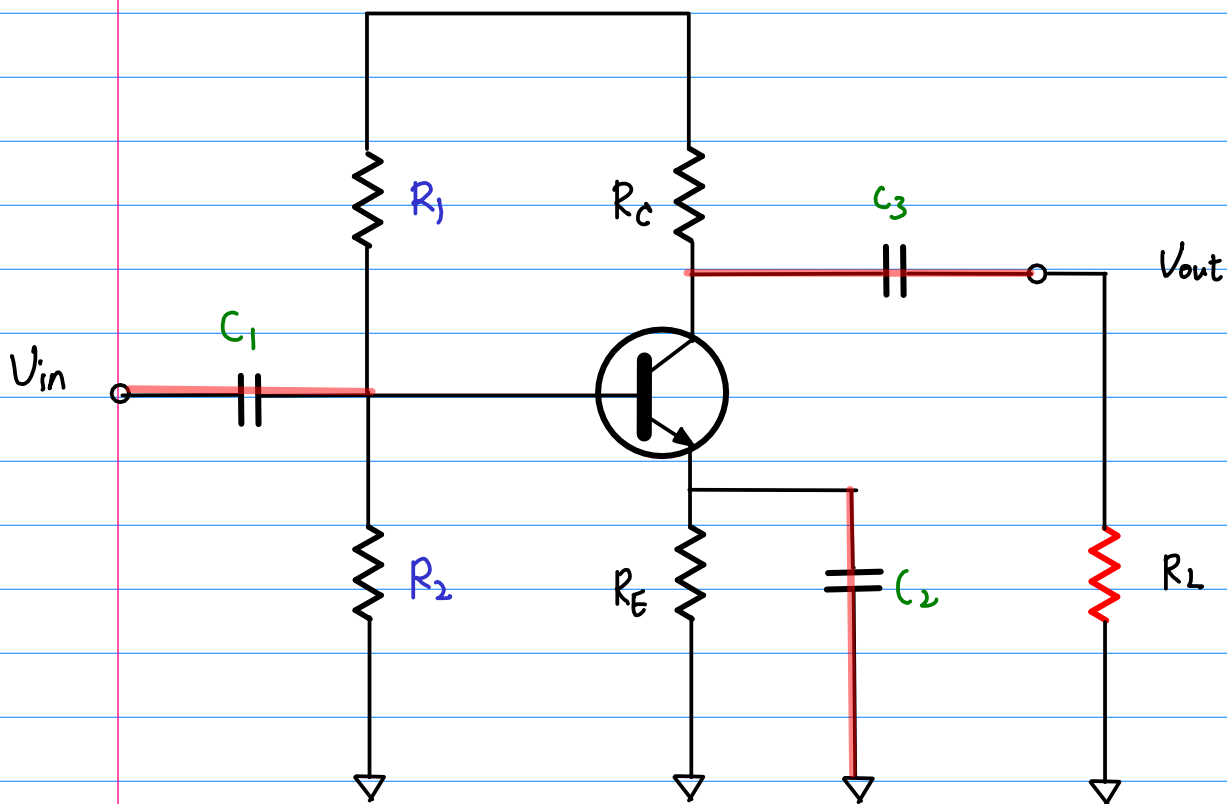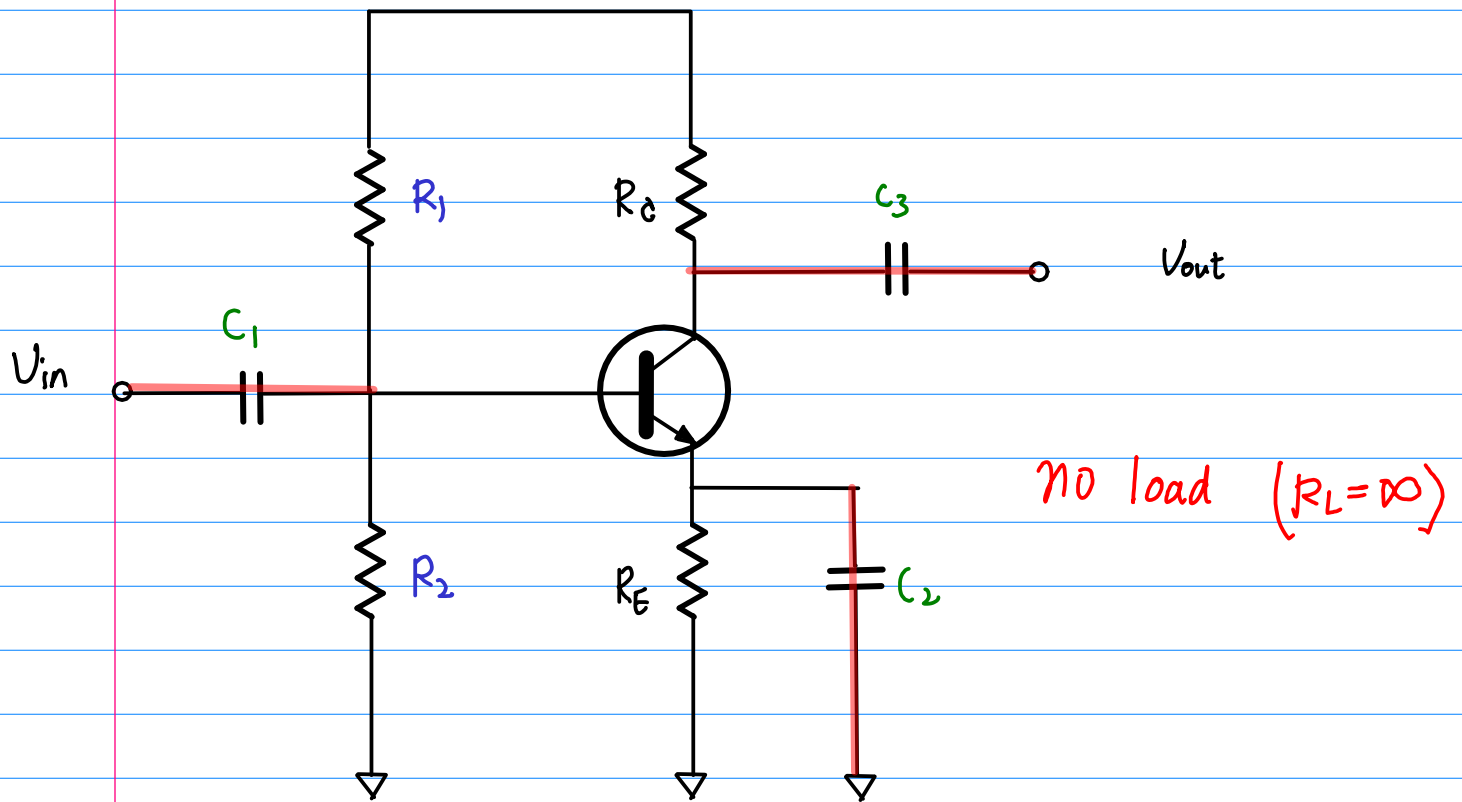

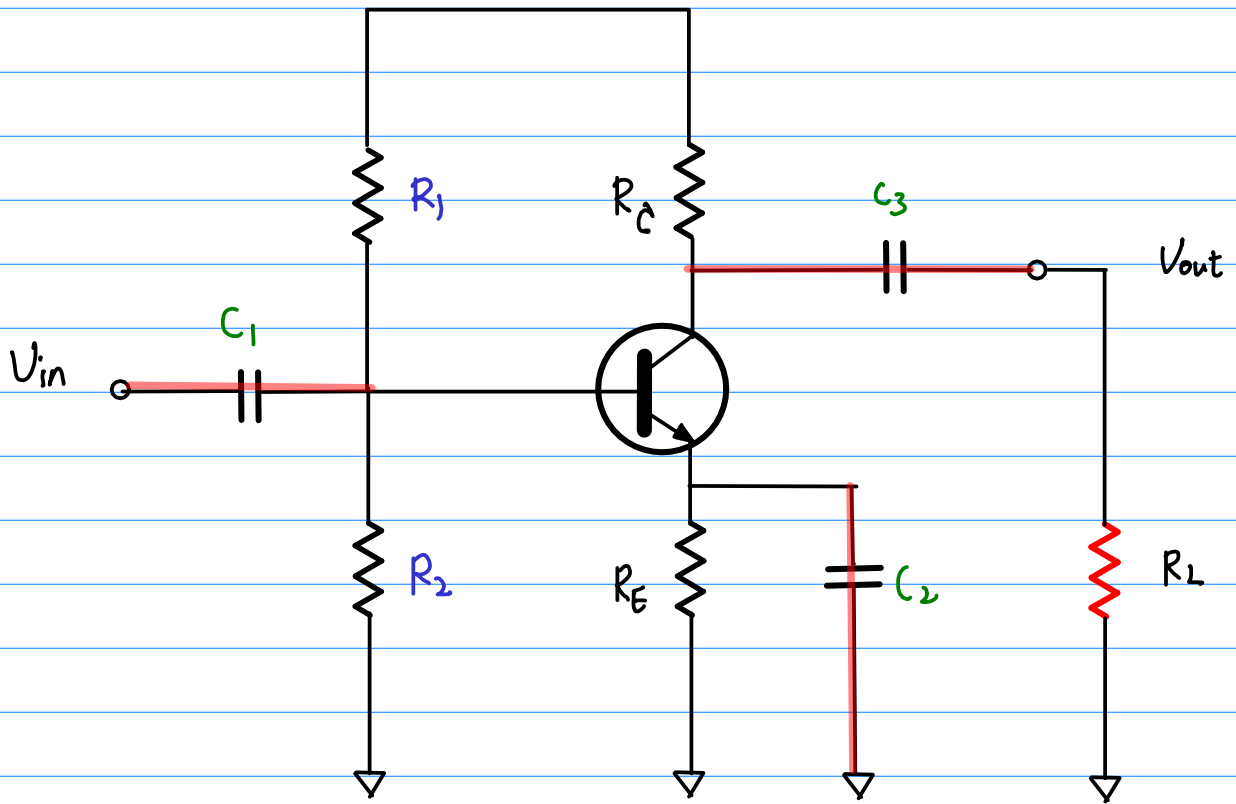

$$R_c = R_C \quad (\text{no load})$$
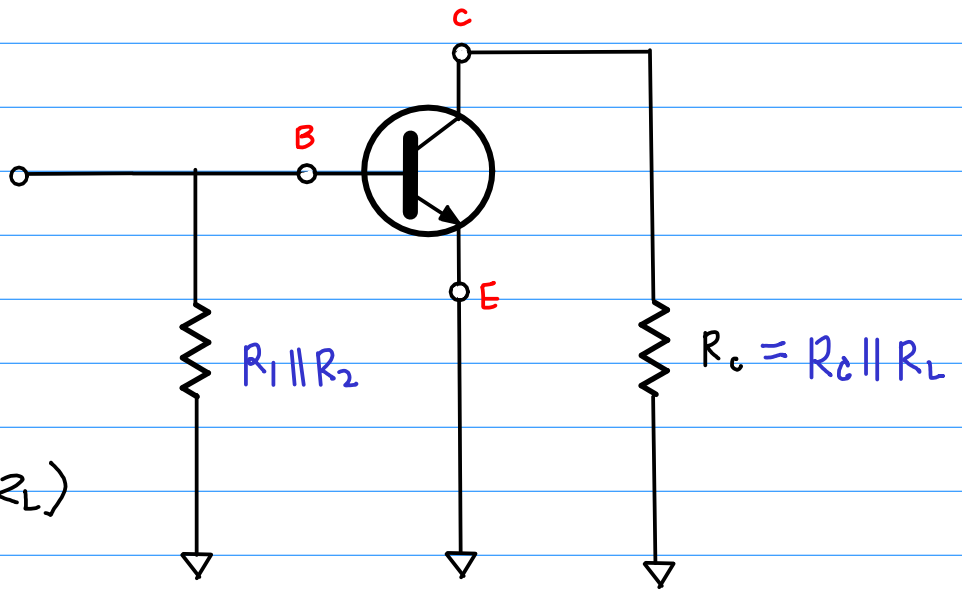
$$R_c = \frac{R_C R_L}{R_C + R_L} \quad (\text{with } R_L)$$



$$R_c = R_c \text{ (no load)}$$

$$A_v = \frac{R_c}{r_e'} = \frac{R_c}{r_e'}$$

$$R_c = \frac{R_c R_L}{R_c + R_L} \text{ (with } R_L)$$

$$A_v = \frac{R_c}{r_e'} = \frac{R_c}{r_e'} \frac{R_L}{R_c + R_L}$$

$$R_c \ll R_L \quad \frac{R_L}{R_c + R_L} = 1$$

$$R_c > R_L \quad \frac{R_L}{R_c + R_L} < 1 \quad A_v \downarrow$$

$$R_c = R_L \quad \frac{R_L}{R_c + R_L} = \frac{1}{2} \quad \frac{1}{2} A_v.$$

swamp (plural swamps)

A piece of wet, spongy land; low ground saturated with water; soft, wet ground which may have a growth of certain kinds of trees, but is unfit for agricultural or pastoral purposes.

A type of wetland that stretches for vast distances, and is home to many creatures who have adapted specifically to that environment.



To drench or fill with water.


The boat was swamped in the storm.

To overwhelm; to make too busy, or overrun the capacity of.


I have been swamped with paperwork ever since they started using the new system.

(figuratively) To plunge into difficulties and perils; to overwhelm; to ruin; to wreck.


# Swamped Amplifier

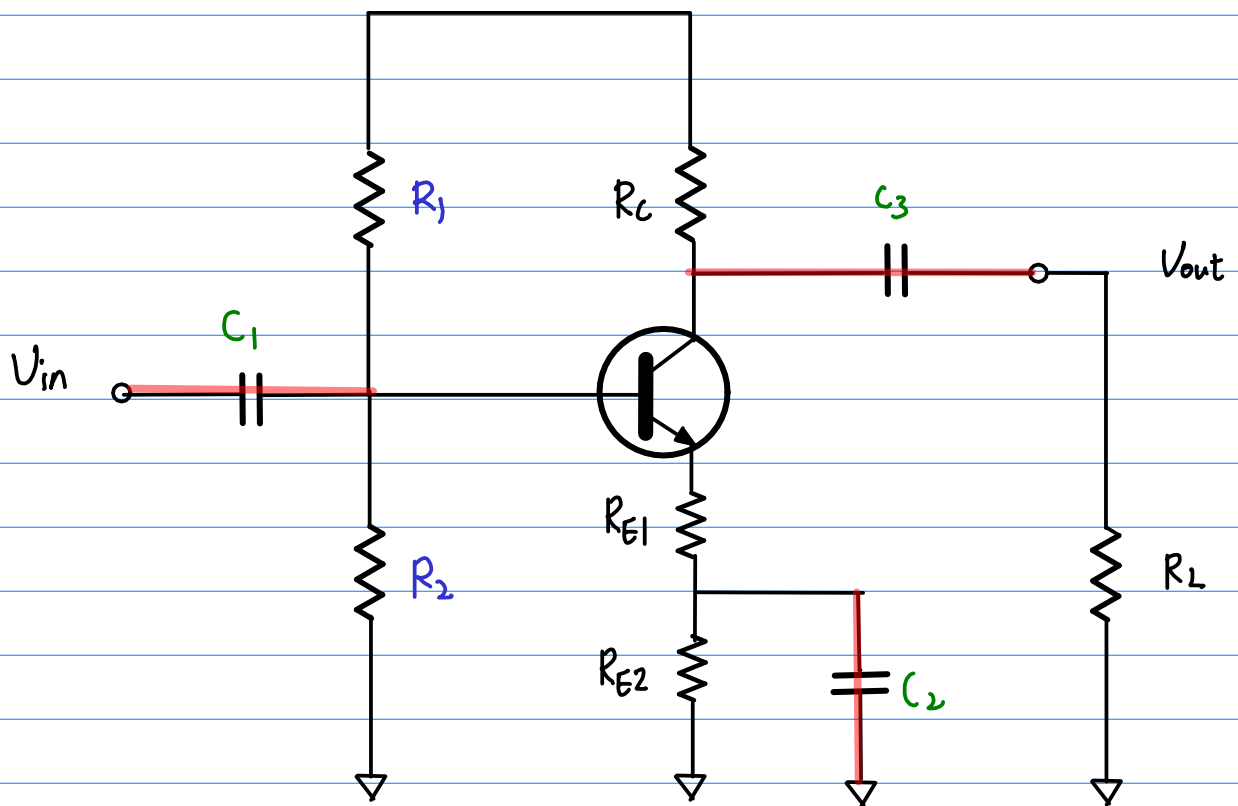

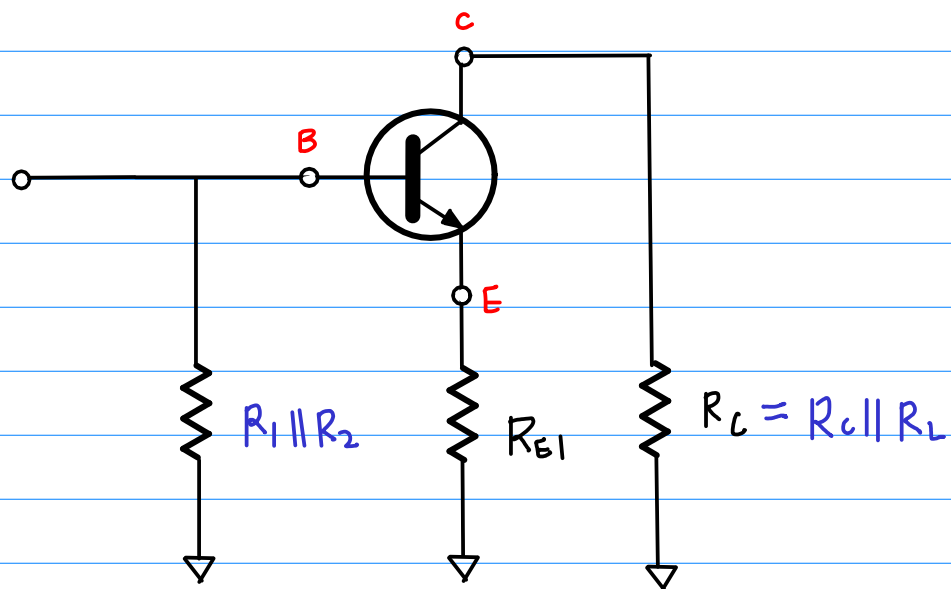
bypassed resistance to minimize the effect of  $r_e \Rightarrow$  gain stability





# AC Emitter Feedback

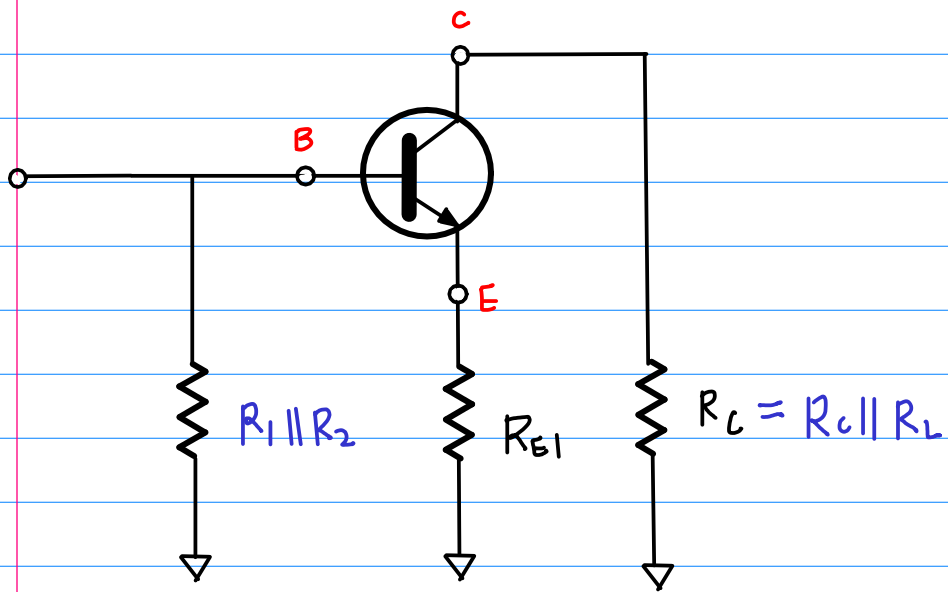

$R_{E1}$ : feedback resistor

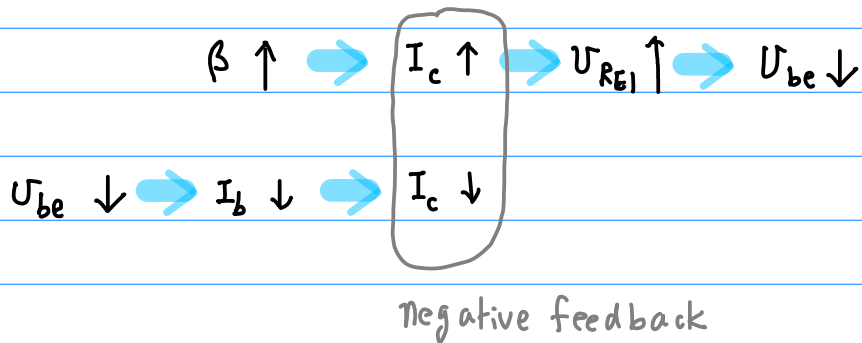


# Current Gain

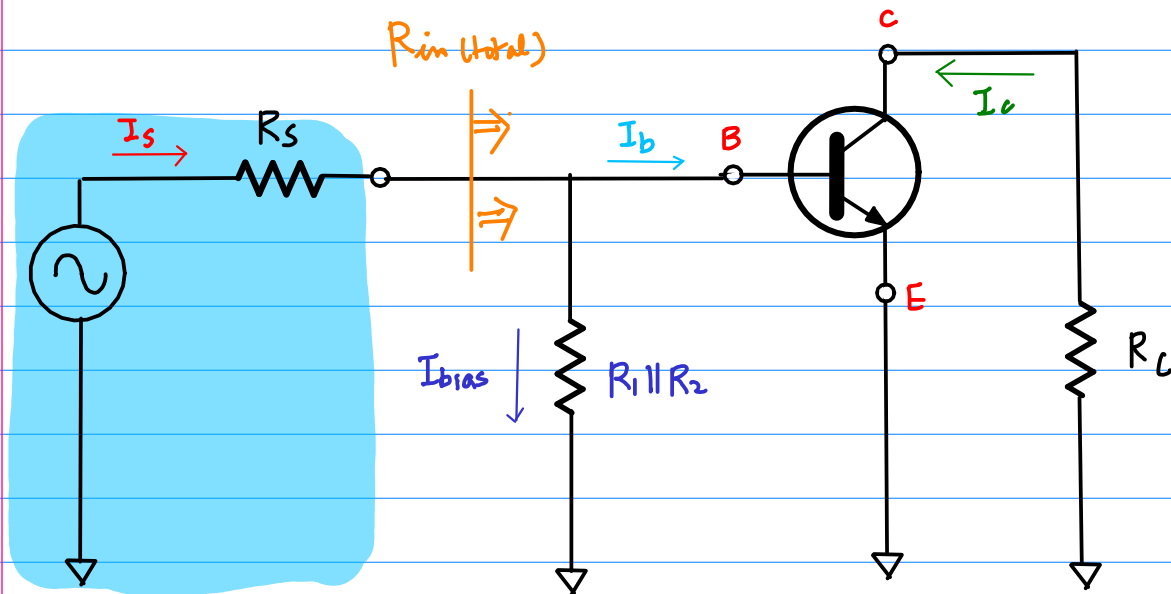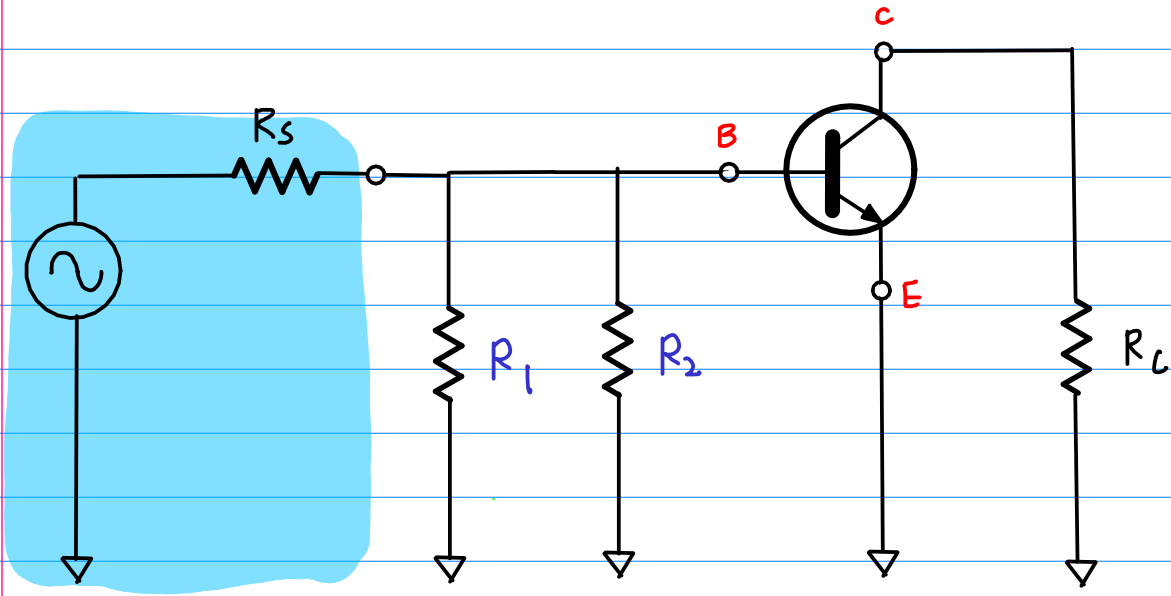



# dc resistance

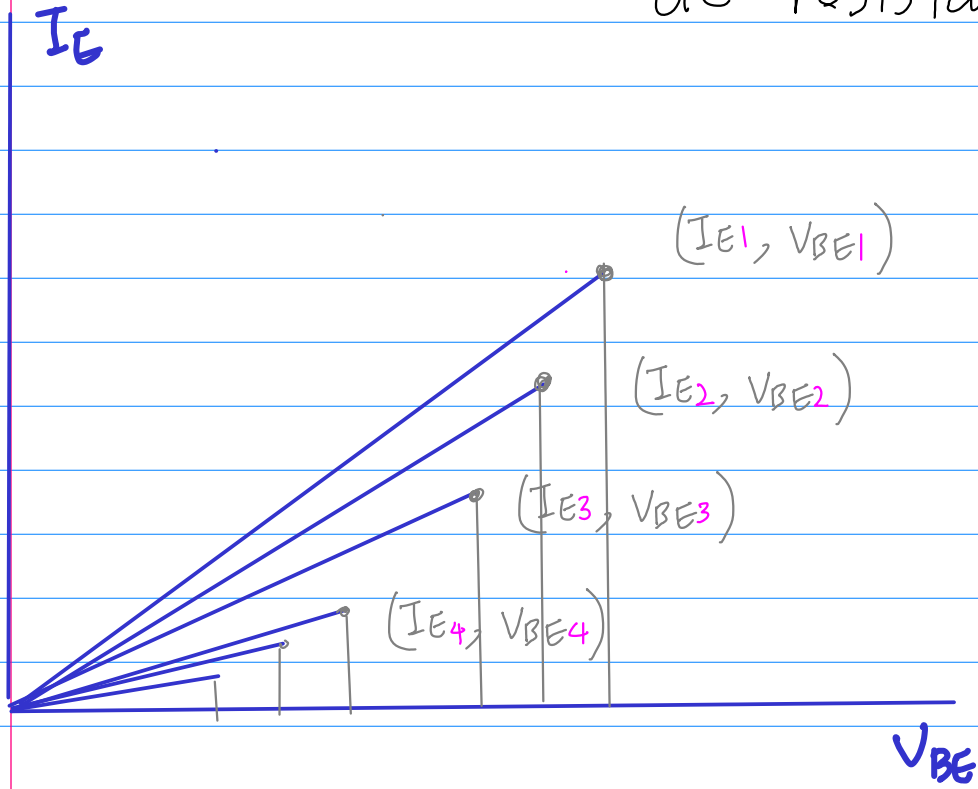

$$R = \frac{V_{BE1}}{I_{E1}}$$


$$R = \frac{V_{BE2}}{I_{E2}}$$

$$R = \frac{V_{BE3}}{I_{E3}}$$

$$R = \frac{V}{I}$$

ac resistance

$I_E$

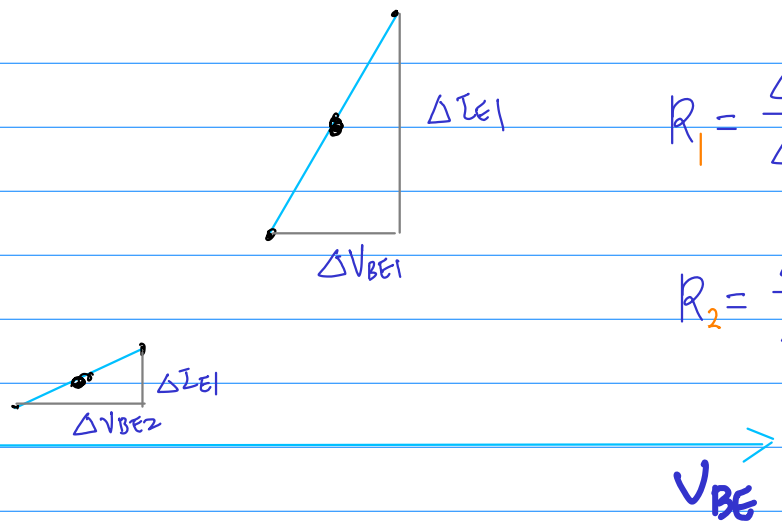

$$R_1 = \frac{\Delta V_{BE1}}{\Delta I_{E1}}$$

$$R_2 = \frac{\Delta V_{BE2}}{\Delta I_{E2}}$$


# ac resistance

$I_E$

large  $I_E$

large slope (small  $R$ )


$$r_e' = \frac{V_{be}}{i_e}$$

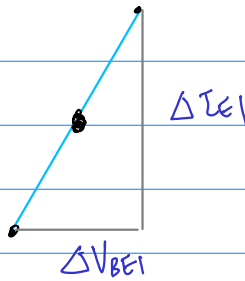

$$R_1 = \frac{\Delta V_{BE1}}{\Delta I_{E1}}$$

small  $I_E$

small slope (large  $R$ )

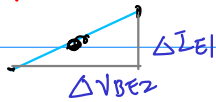

$$R_2 = \frac{\Delta V_{BE2}}{\Delta I_{E2}}$$

$V_{BE}$