

# Capacitor in an AC circuit

---


Copyright (c) 2011 – 2017 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".


Please send corrections (or suggestions) to [youngwlim@hotmail.com](mailto:youngwlim@hotmail.com).

This document was produced by using OpenOffice and Octave.


# Everchanging signal pairs

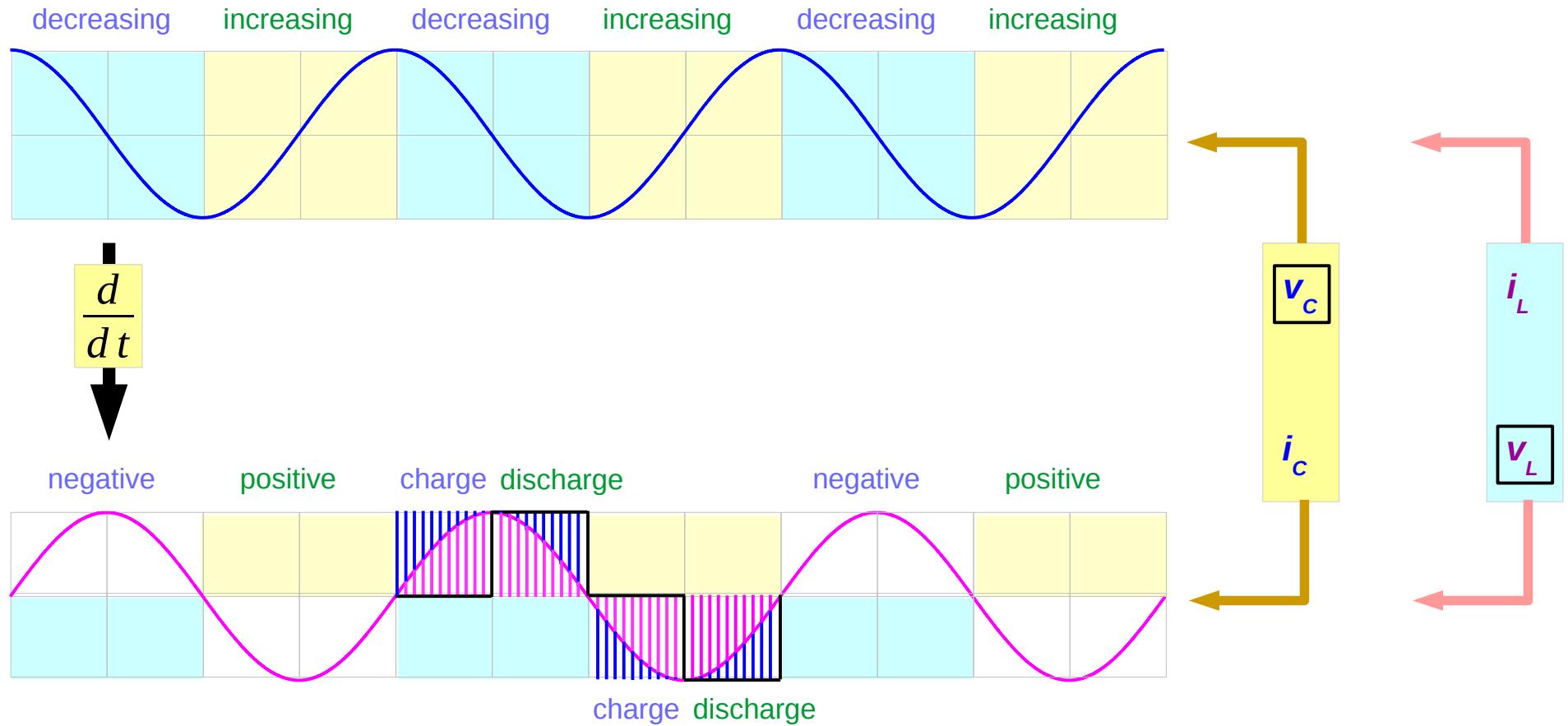



# Capacitor Current

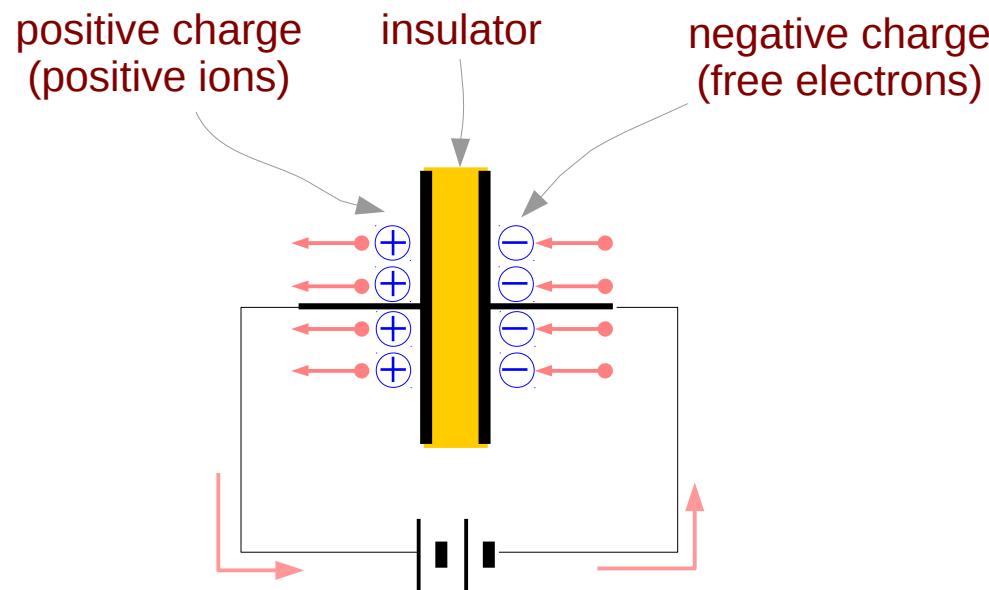




Think as electrons move to the left

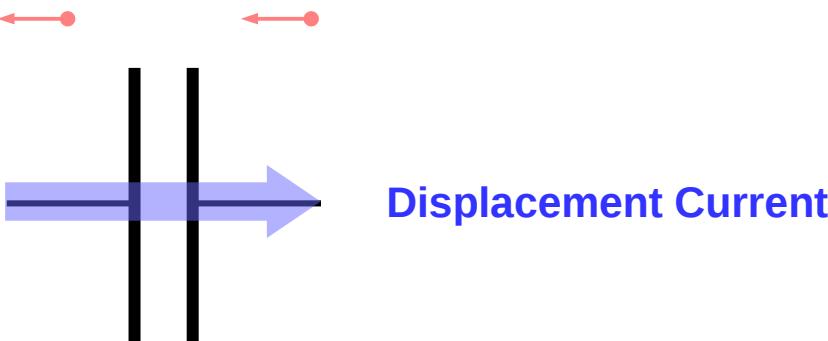

# Positive ions and free electrons

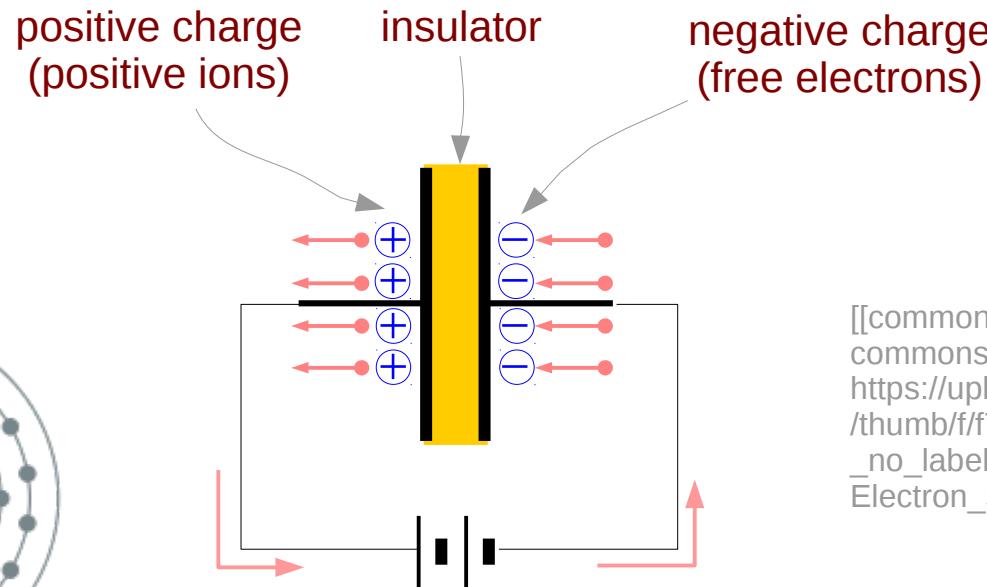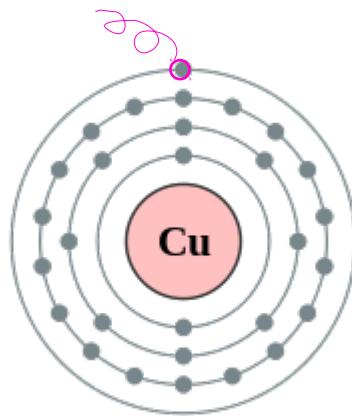

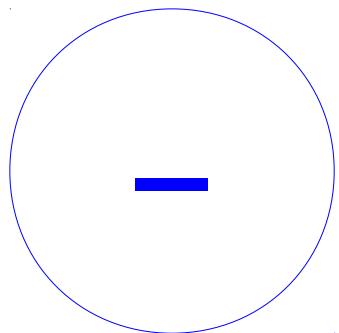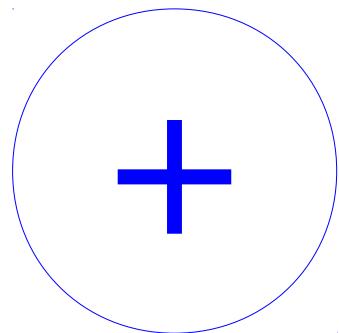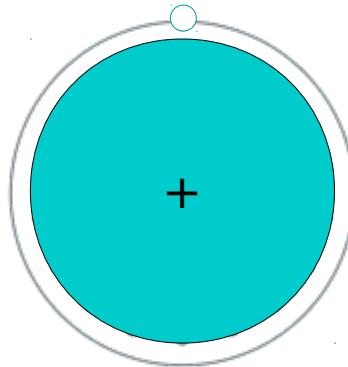
[[commons:User crap ]] (original work by commons:User:Greg Robson)  
[https://upload.wikimedia.org/wikipedia/commons/thumb/f/f7/Electron\\_shell\\_029\\_Copper\\_-\\_no\\_label.svg/200px-Electron\\_shell\\_029\\_Copper\\_-\\_no\\_label.svg.png](https://upload.wikimedia.org/wikipedia/commons/thumb/f/f7/Electron_shell_029_Copper_-_no_label.svg/200px-Electron_shell_029_Copper_-_no_label.svg.png)



# Three States



positive charge  
(positive ions)

**Positive Charged State**  
no current

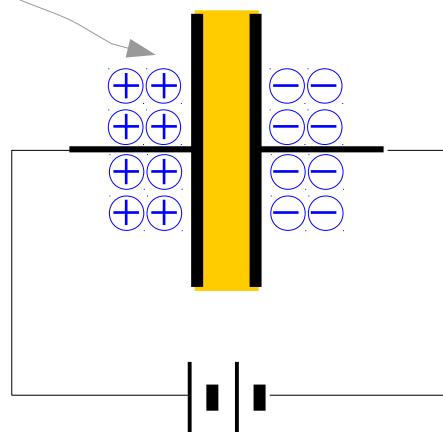

negative charge  
(free electrons)


**Negative Charged State**  
no current

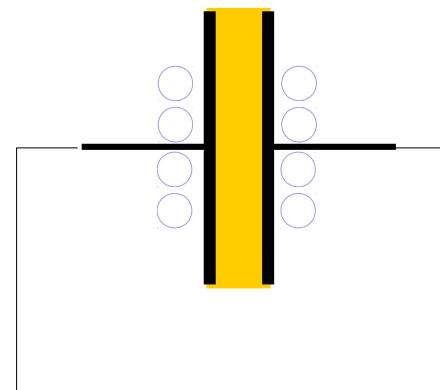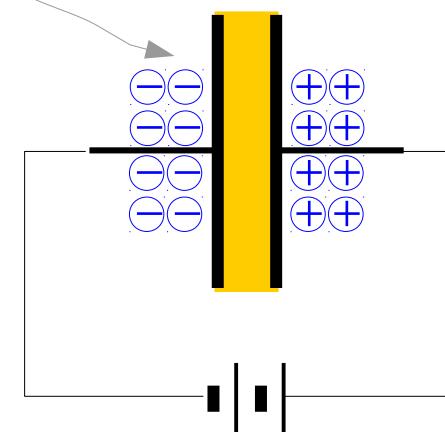


**Fully Discharged State**  
large current

# Inter-State Current Flowing

## Positive Charging

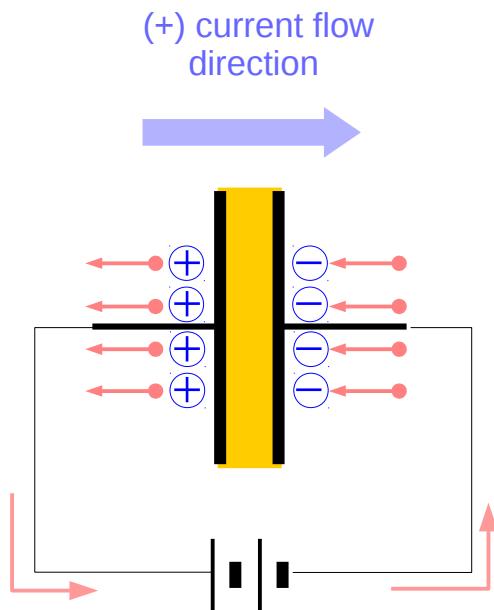


## Negative Charging

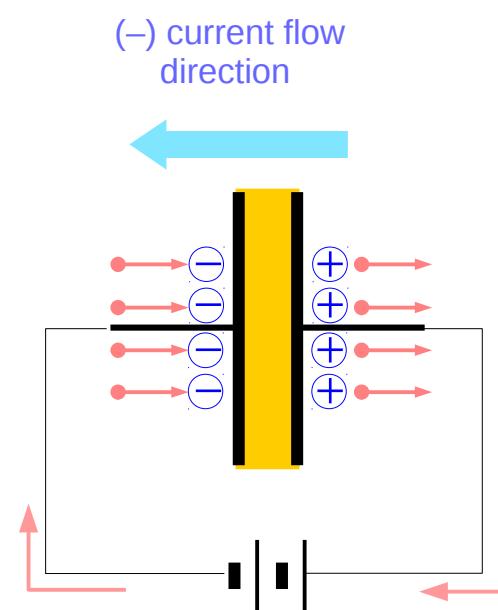


# Inter-State Current Flowing

Fully Discharged State

large current

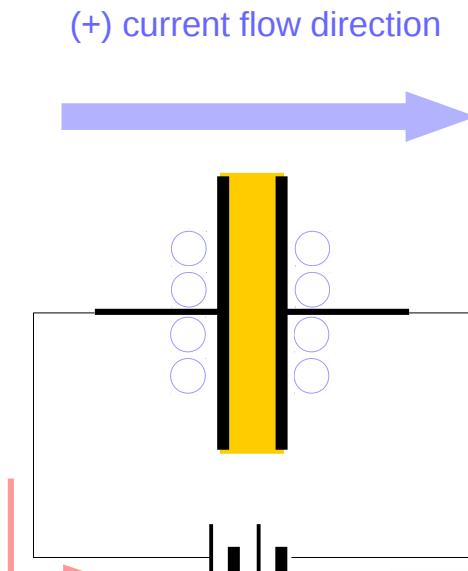


Positive Charging

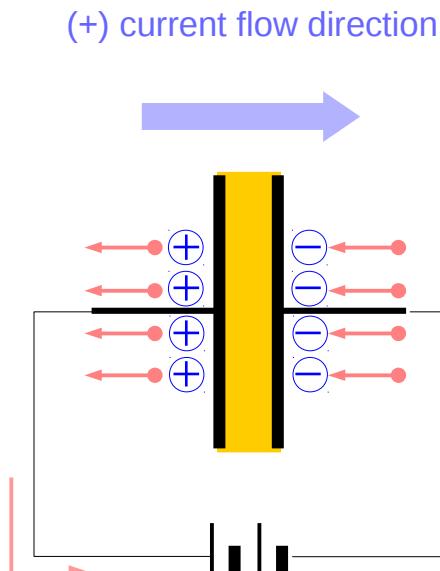

Positive Charged State

no current

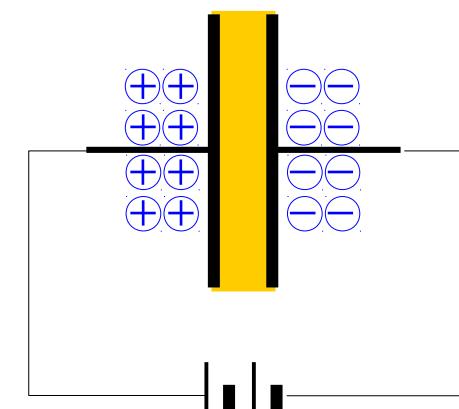


# Inter-State Current Flowing

Fully Discharged State


large current

(-) current flow direction

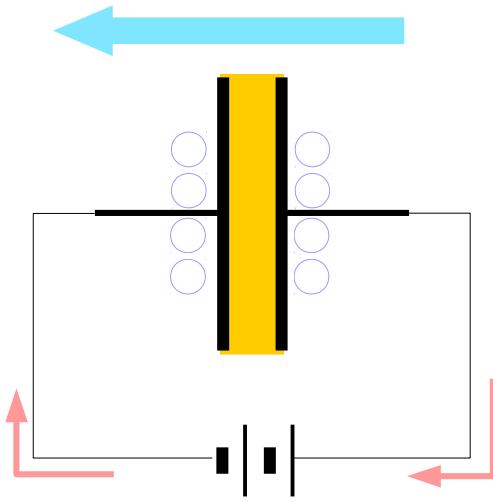


Positive Charging

(-) current flow direction

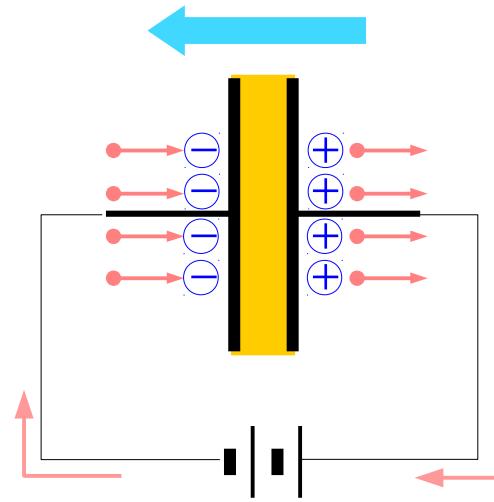

Positive Charged State

no current


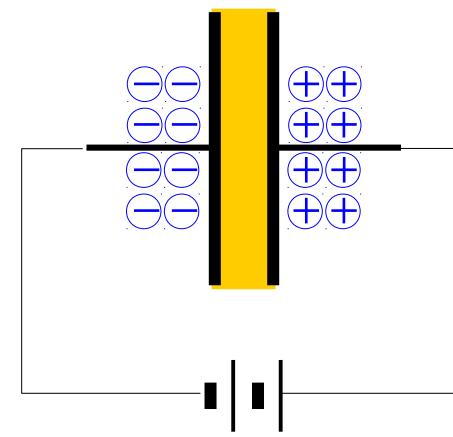


electron flow direction


electron flow direction

Crowded  
No more space



# An AC Voltage Source

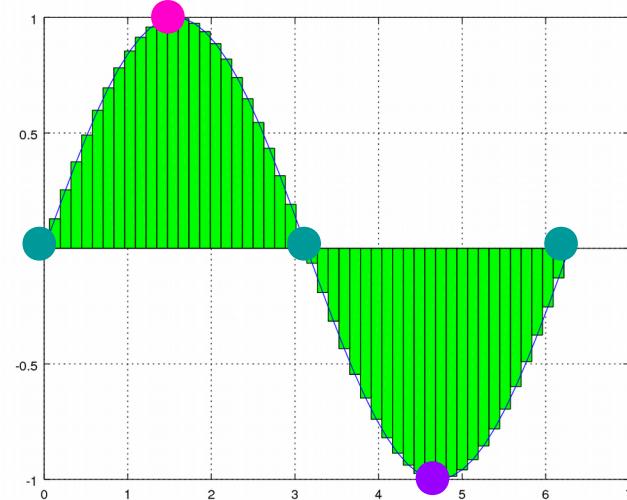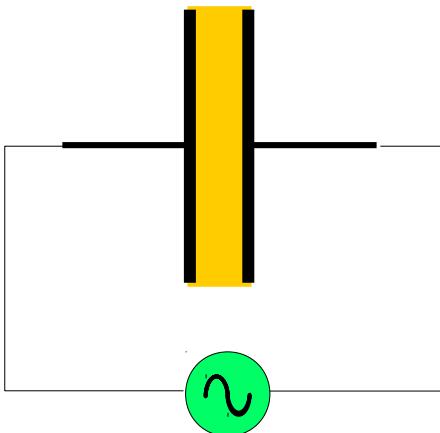



# Fully Charged and Fully Discharged

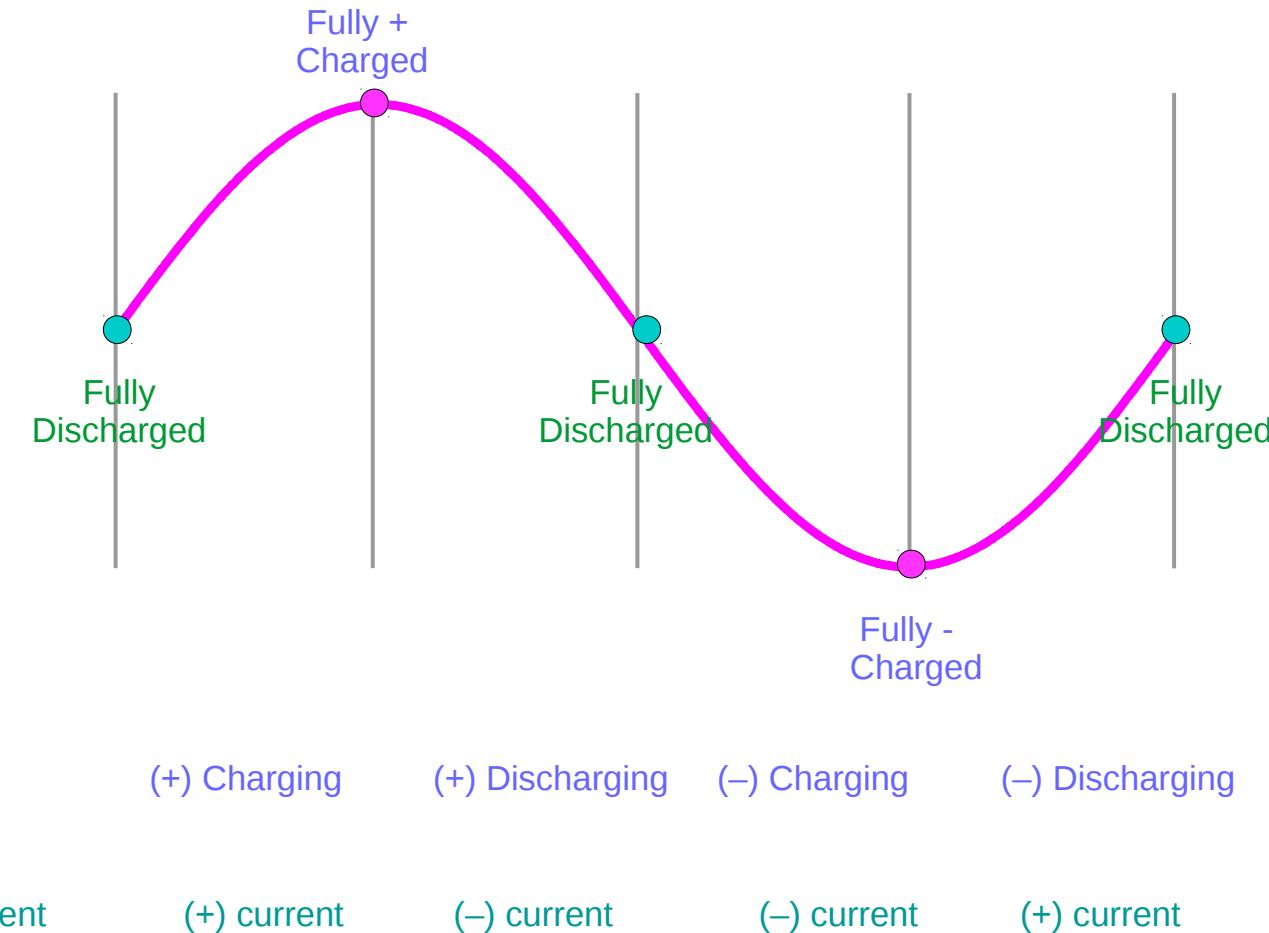


# A Cycle

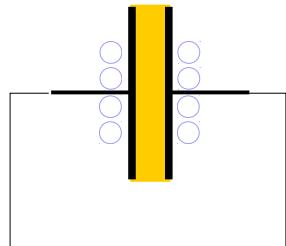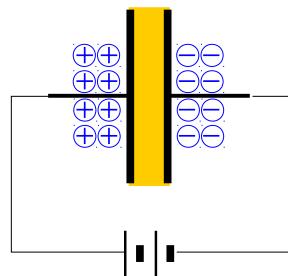



Fully Discharged State

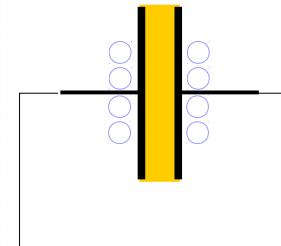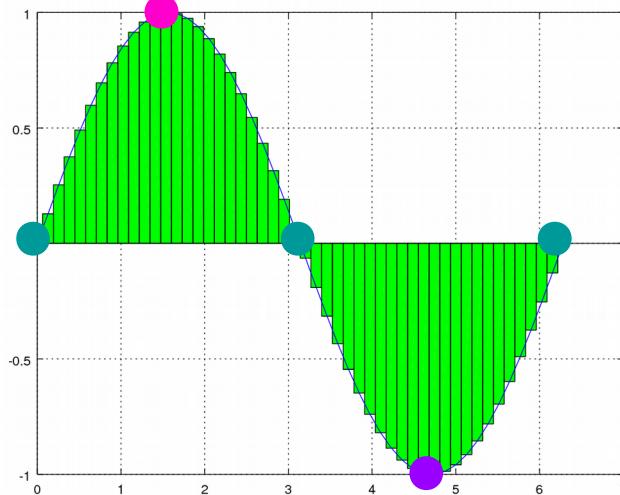



Fully Discharged State

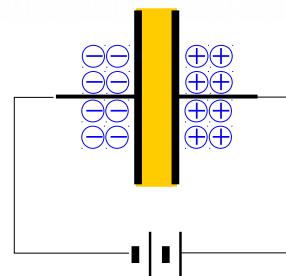


# State Transition Diagram

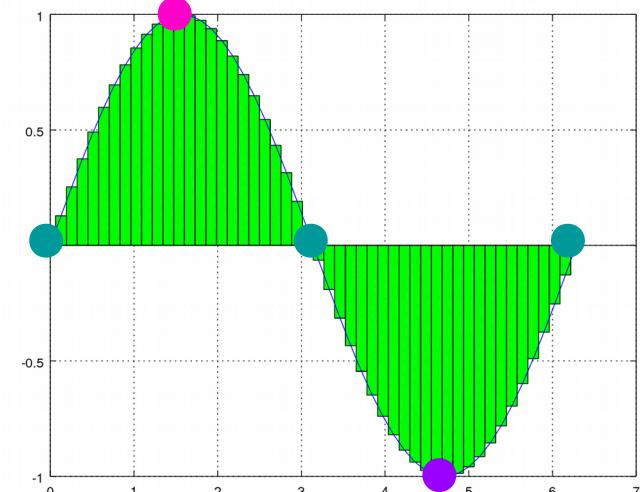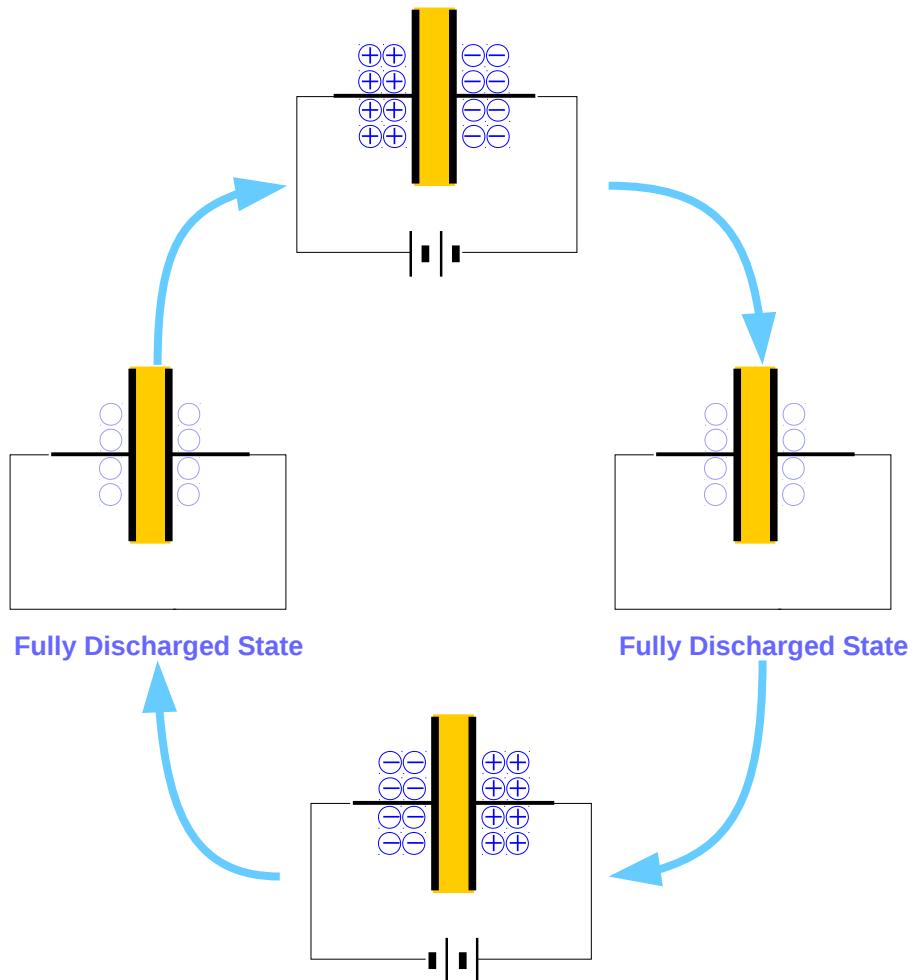

# Current Flow

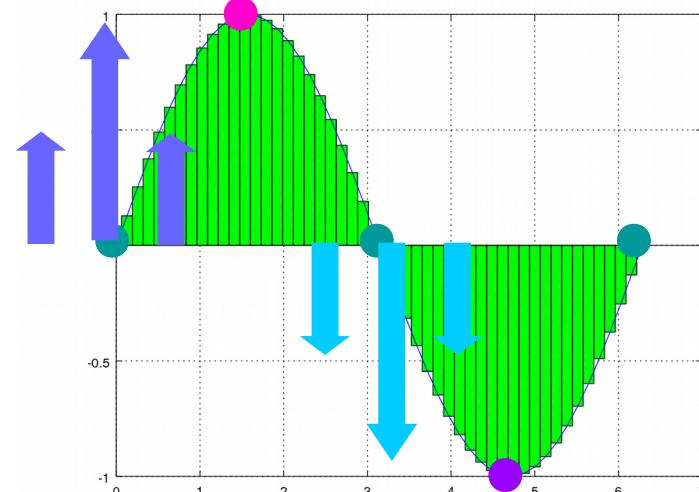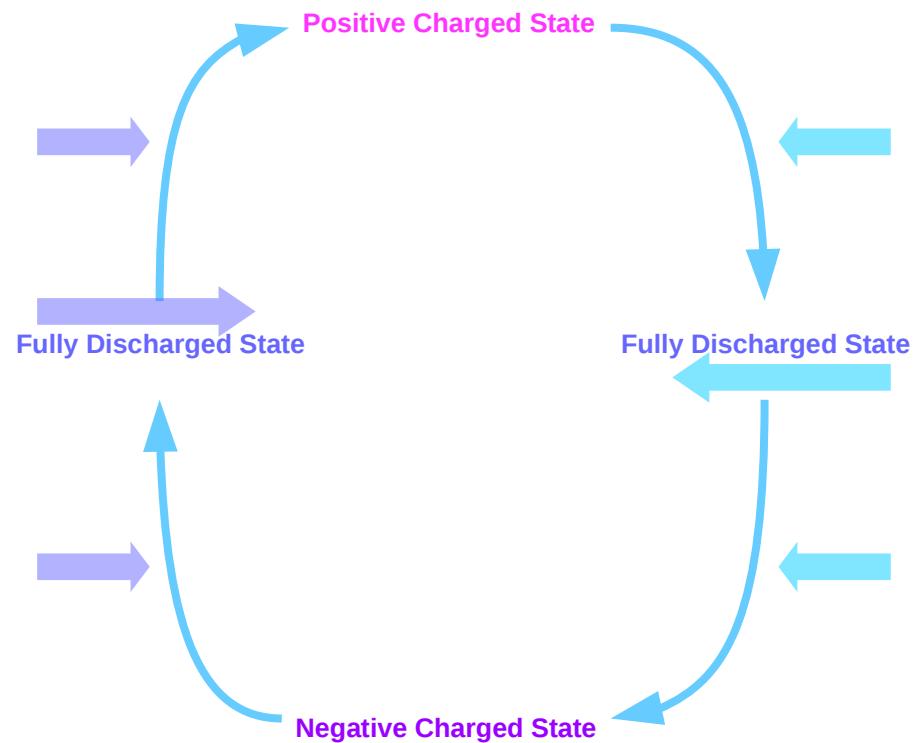

# Fully Charged and Fully Discharged

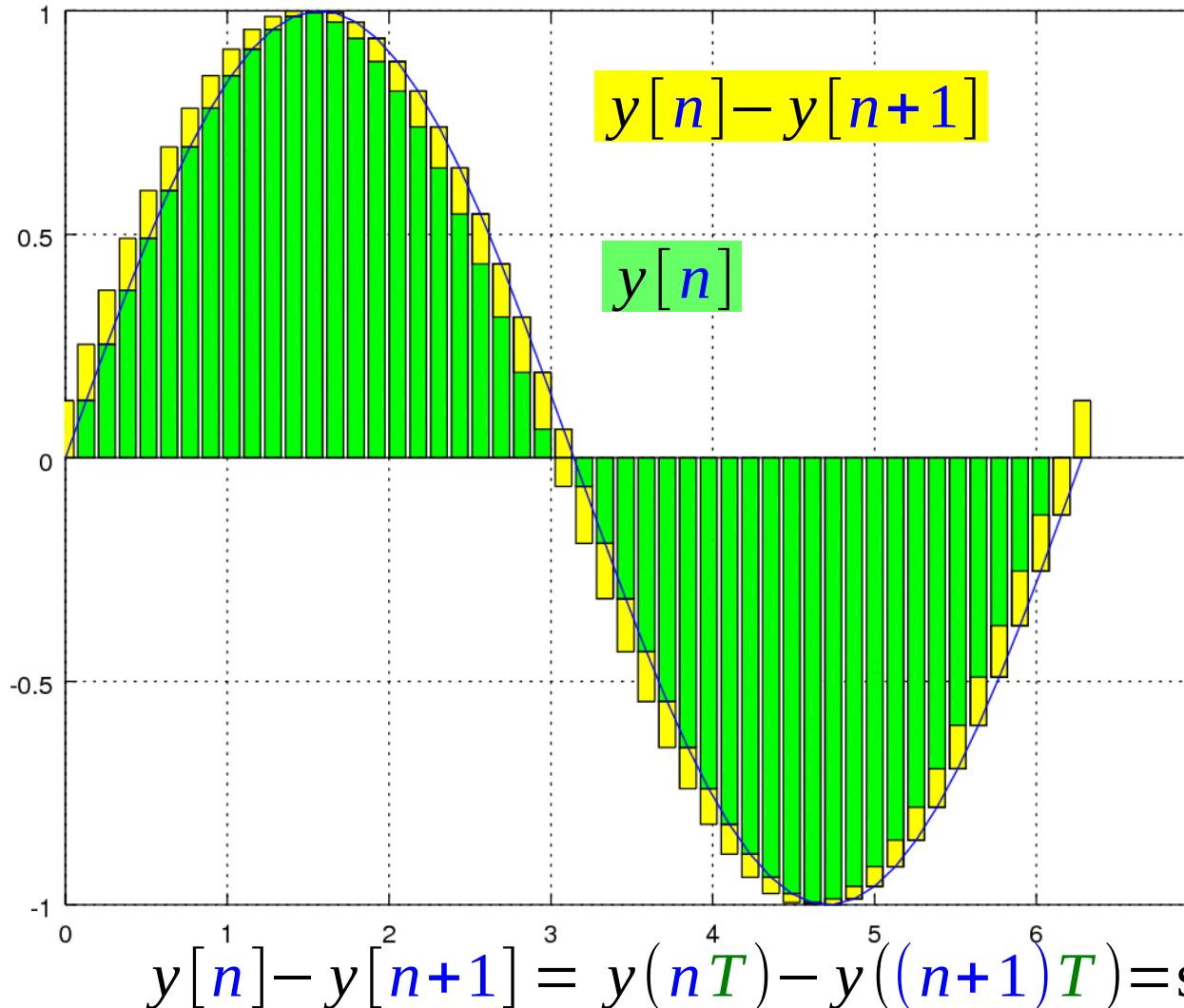


```
h = bar(t1, [y1' y2'],  
"stacked")  
set(h(1), "facecolor", "g");  
set(h(2), "facecolor", "y");  
hold on  
plot(t1, y1)  
axis([0 7 -1 1]);
```
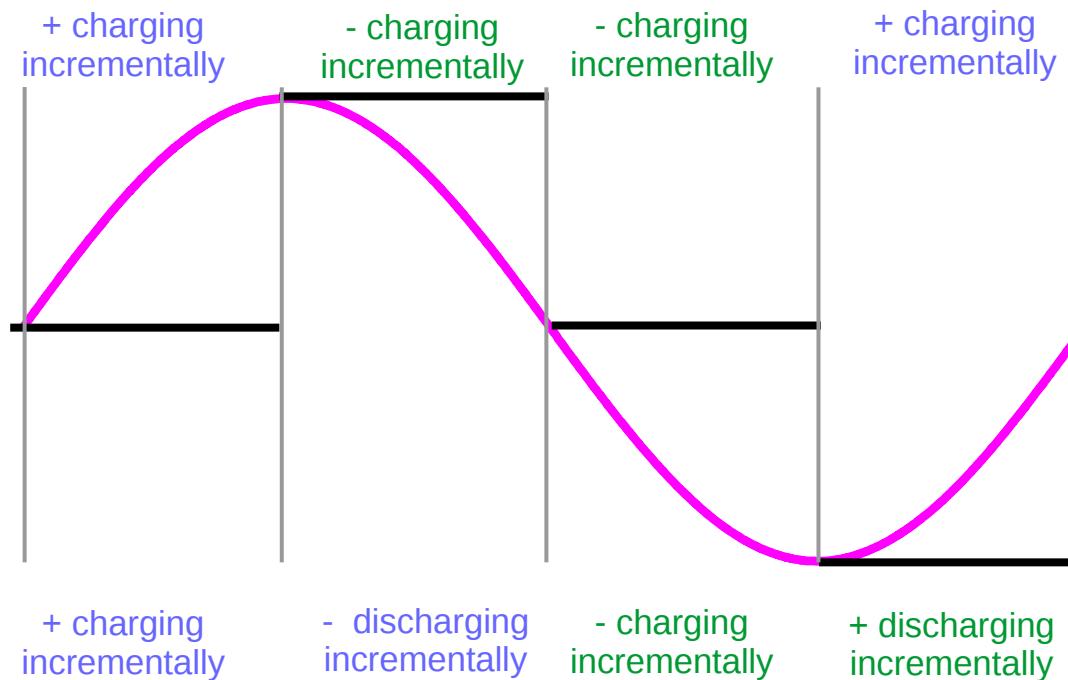
# Continuous Charging and Discharging Operations


Incremental Voltage Increment  $\rightarrow +$  Charging incrementally

Incremental Voltage Decrement  $\rightarrow -$  Charging incrementally



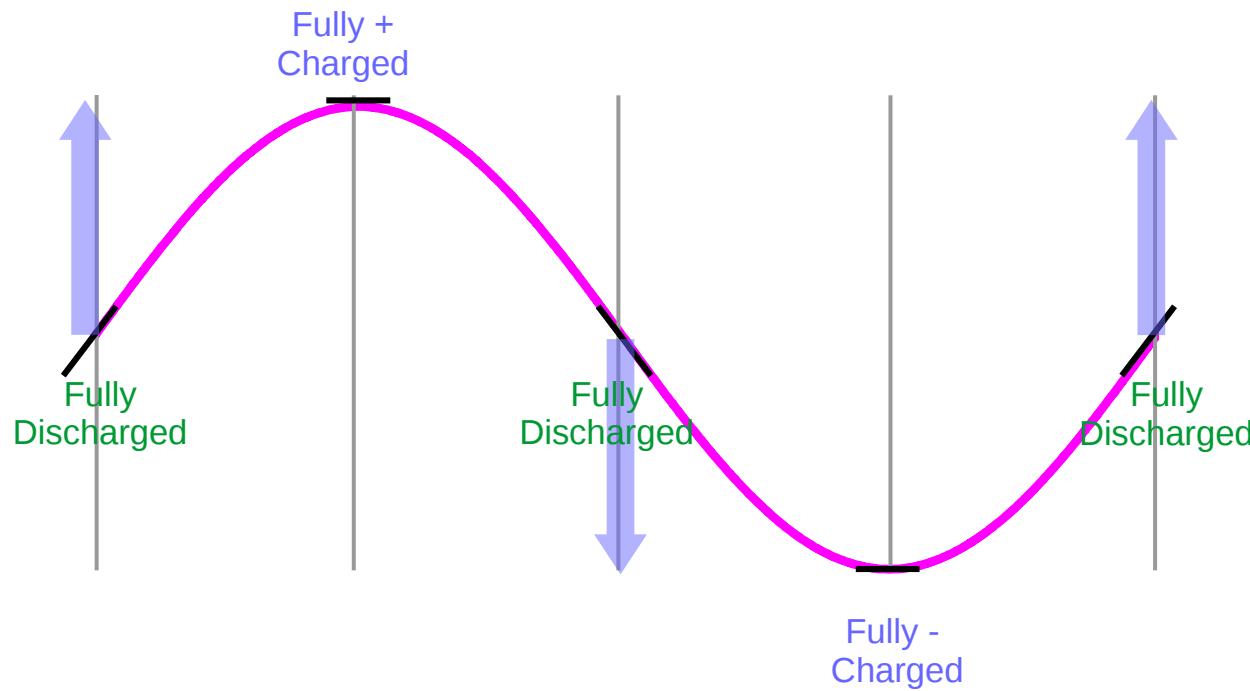
# Fully Discharged : Large Current

Incremental Voltage Increment → Continuous Charging  
Incremental Voltage Decrement → Continuous Discharging




# $y[n+1] - y[n]$

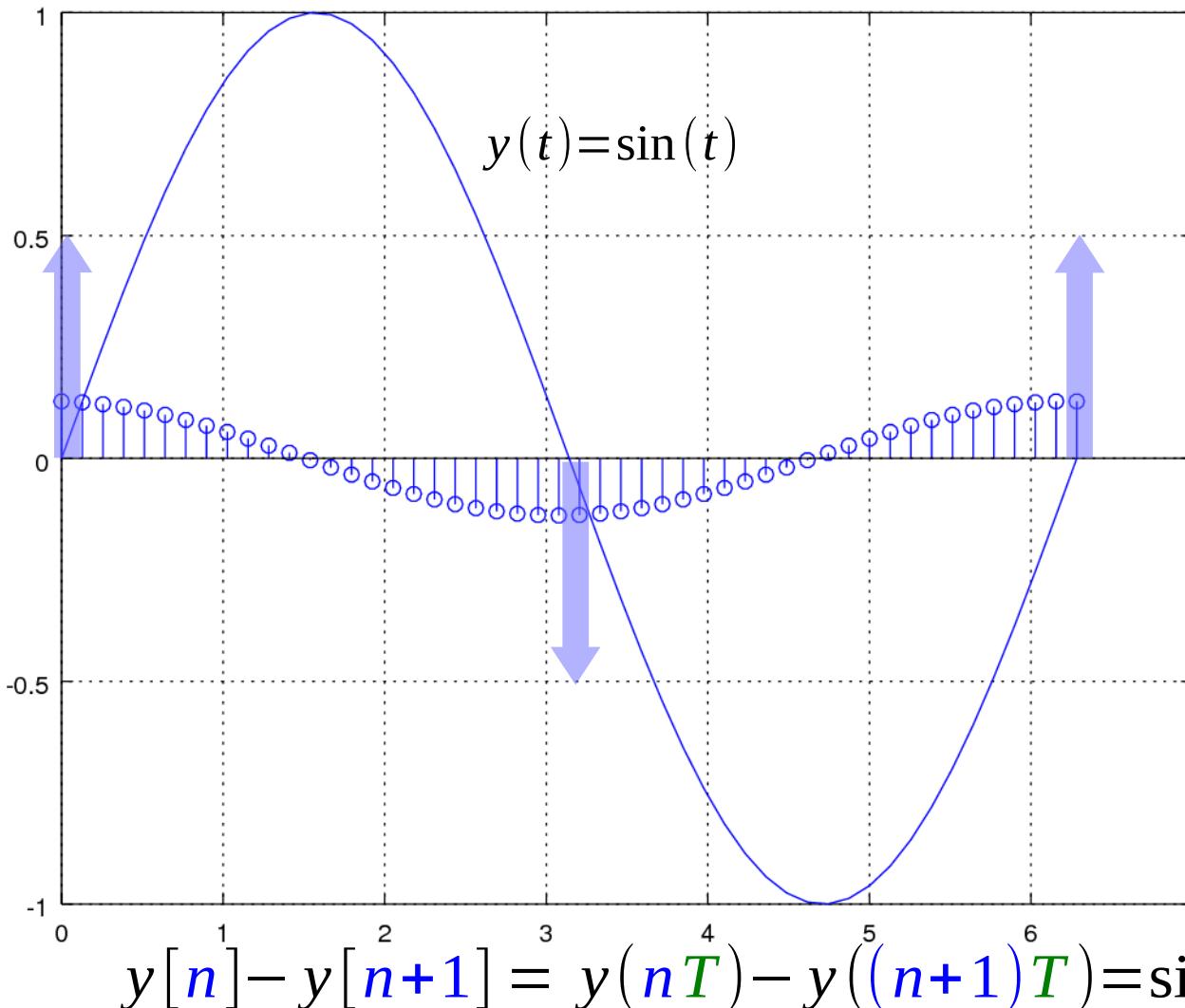


```
t = linspace(0, pi*2, 50);
t1 = t;
t2 = t + t(2);
y1 = sin(t1);
y2 = sin(t2) - sin(t1);
stem(t1, y2)
hold on
plot(t1, y1)
```

# Fully Charged and Fully Discharged

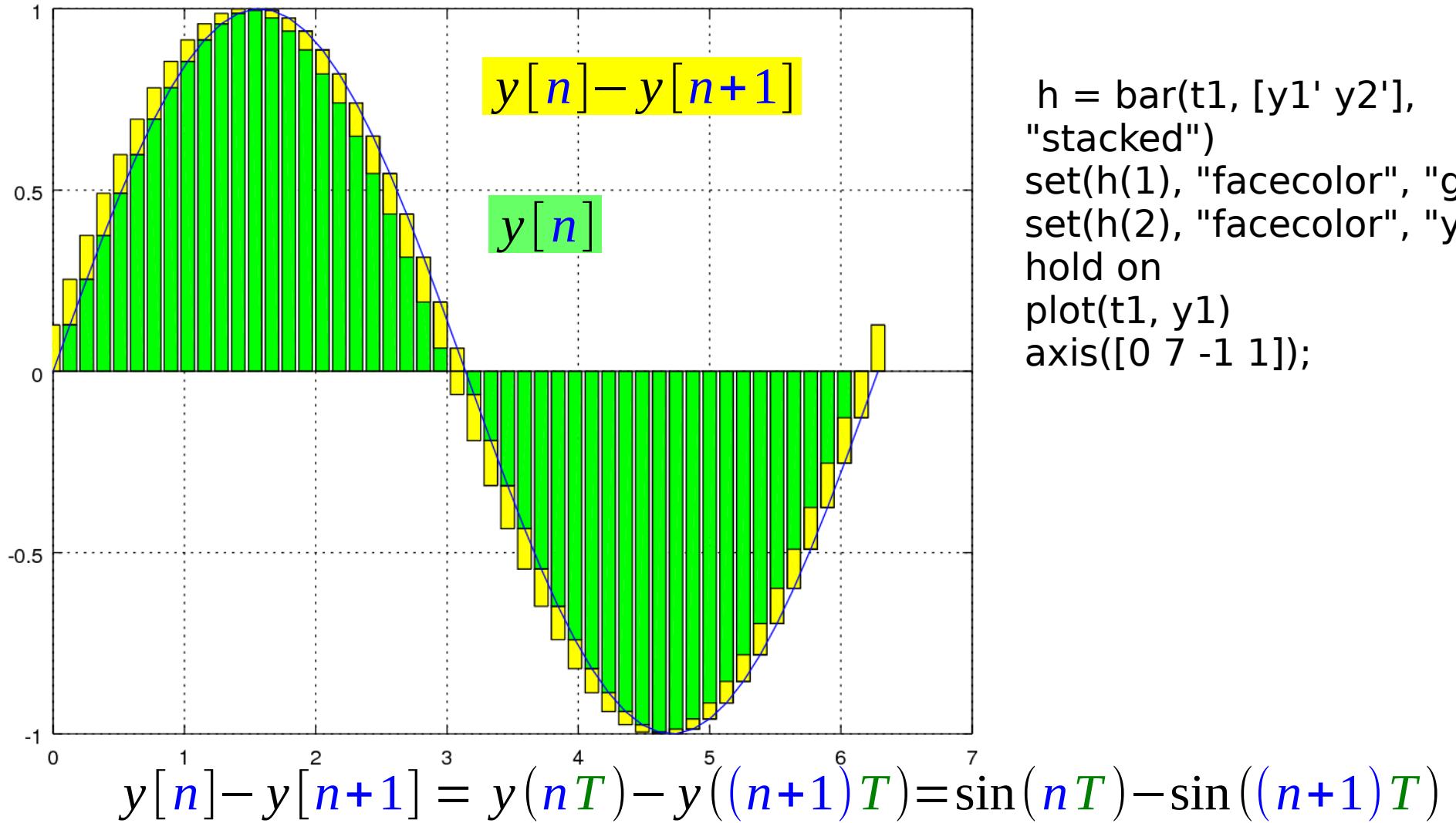

# Fully Charged and Fully Discharged

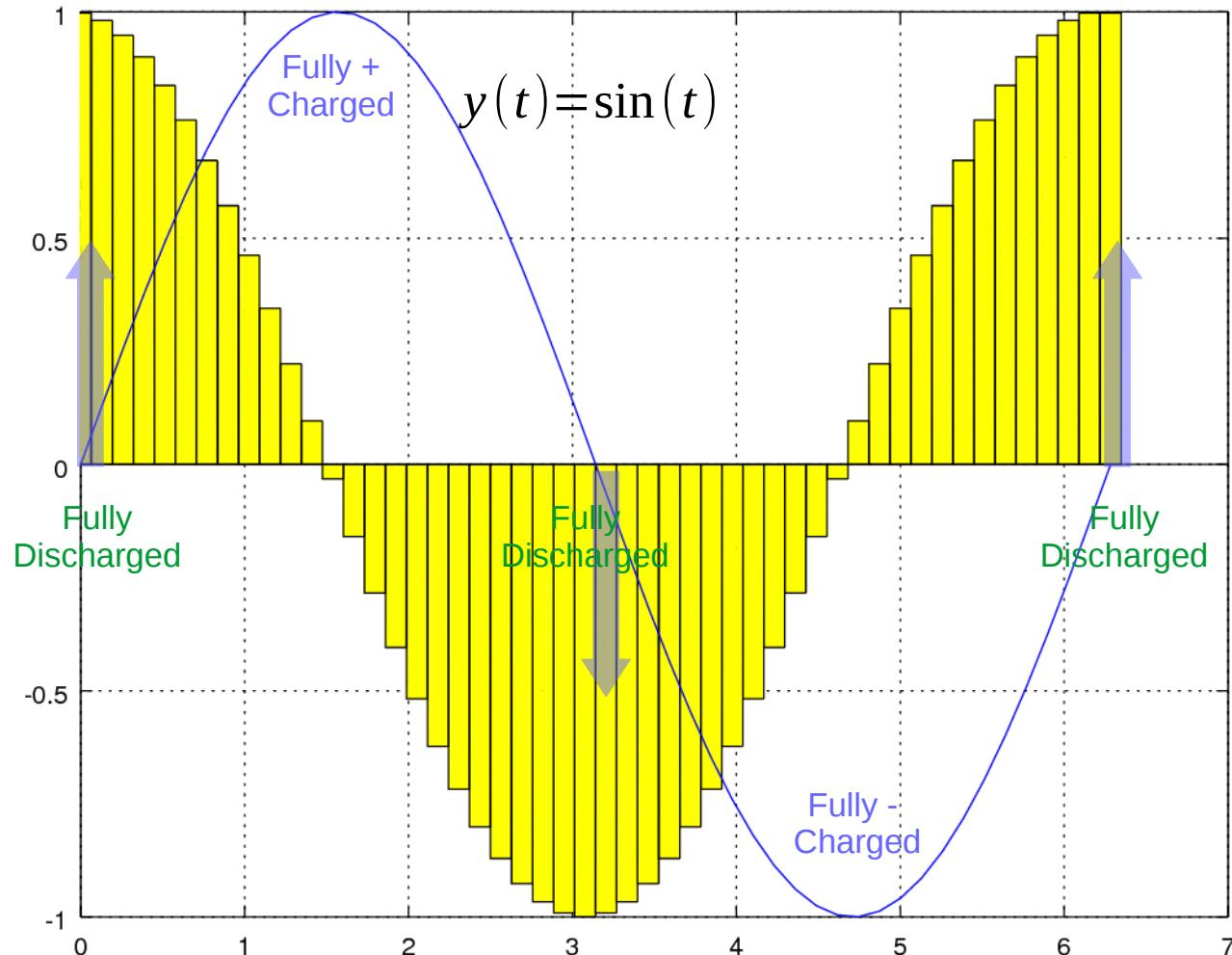


```
h = bar(t1, y2/t(2), "hist")
set(h(1), "facecolor", "y");
hold on
plot(t1, y1)
axis([0 7 -1 1]);
```

$$\frac{y[n] - y[n+1]}{T}$$


$$\propto \frac{dy}{dt}$$

# Fully Charged and Fully Discharged

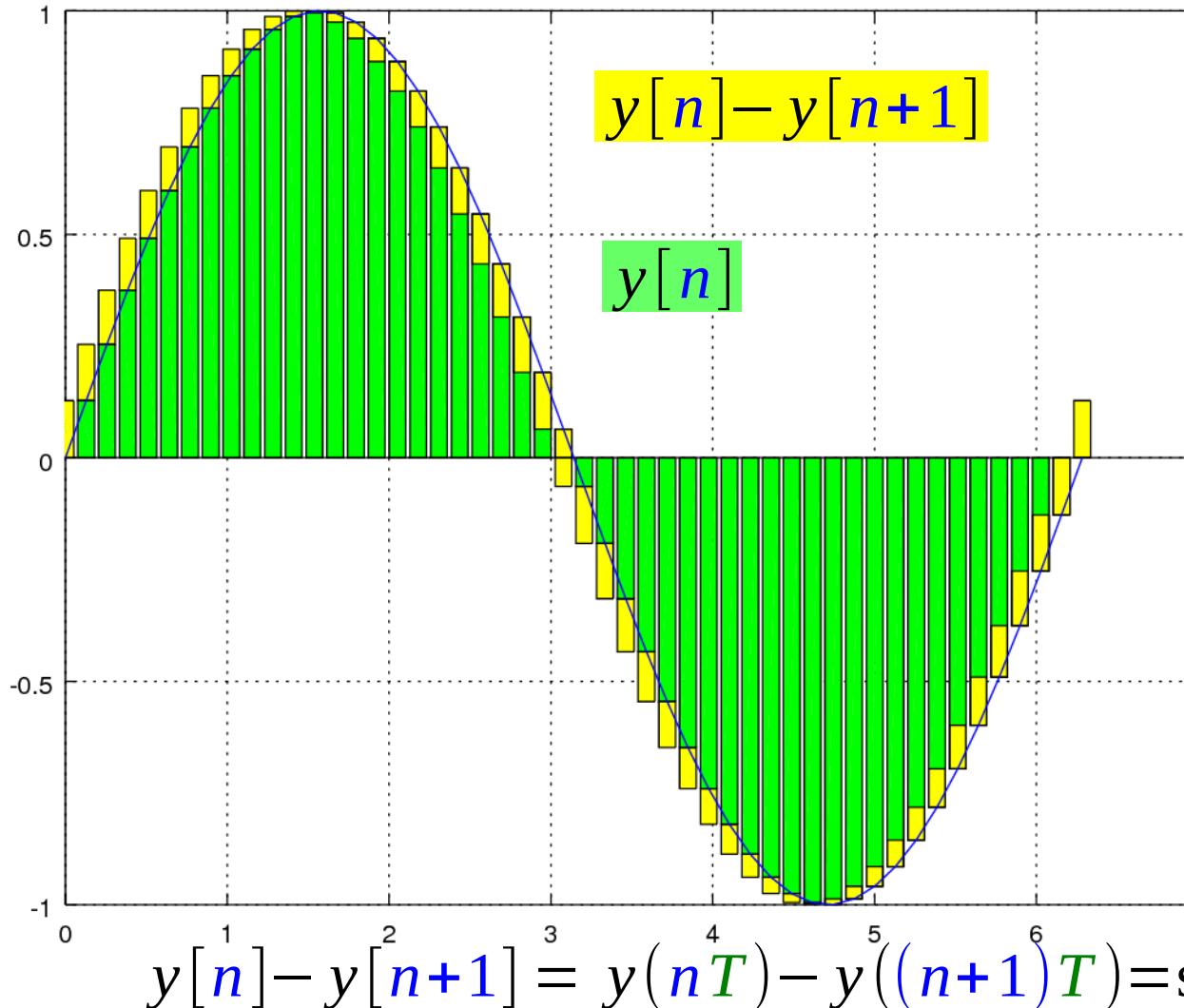


```
h = bar(t1, [y1' y2'],  
"stacked")  
set(h(1), "facecolor", "g");  
set(h(2), "facecolor", "y");  
hold on  
plot(t1, y1)  
axis([0 pi]);
```

# Everchanging signal pairs


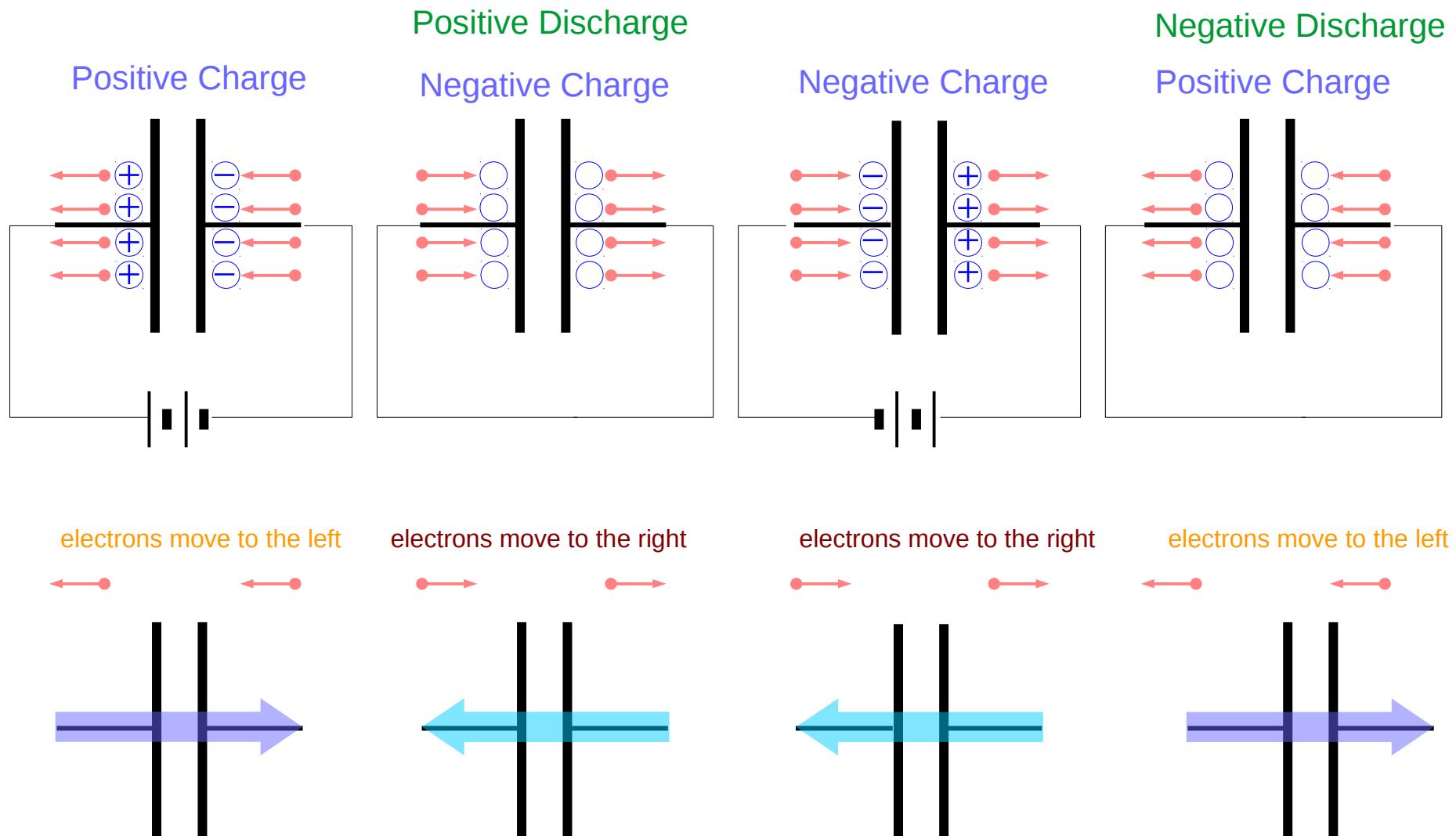


# Everchanging signal pairs

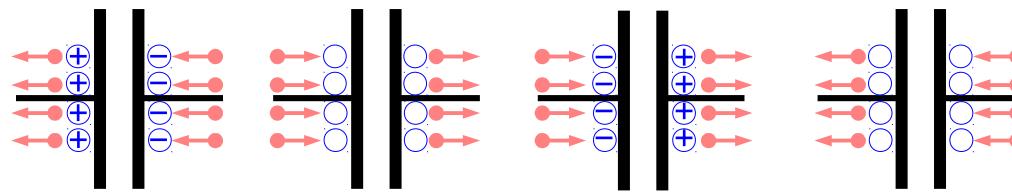


charge


discharge

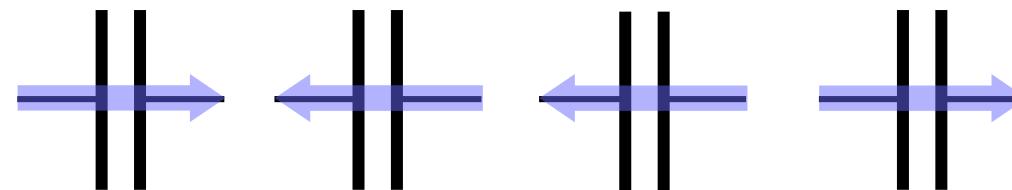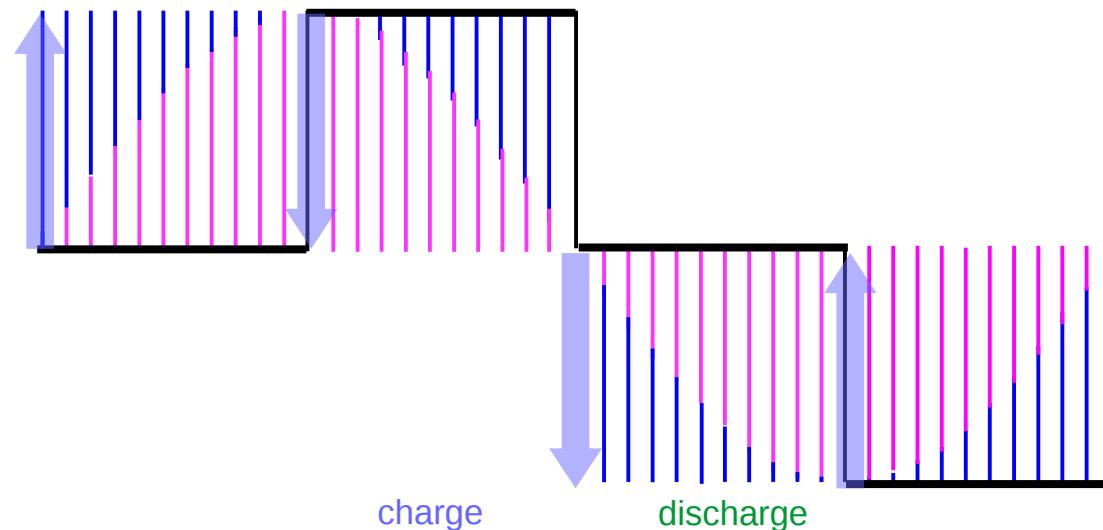


# Everchanging signal pairs

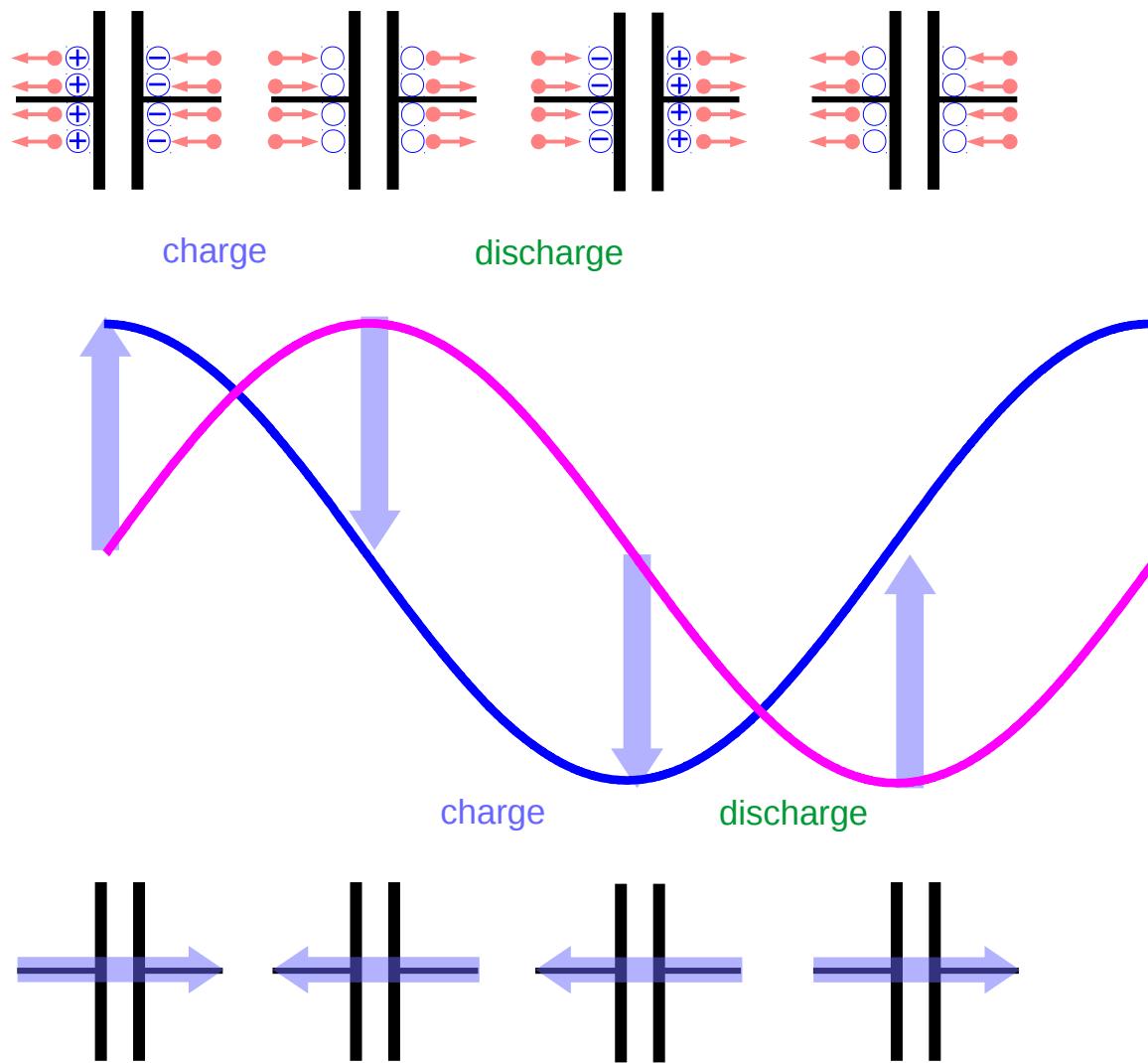

# Everchanging signal pairs

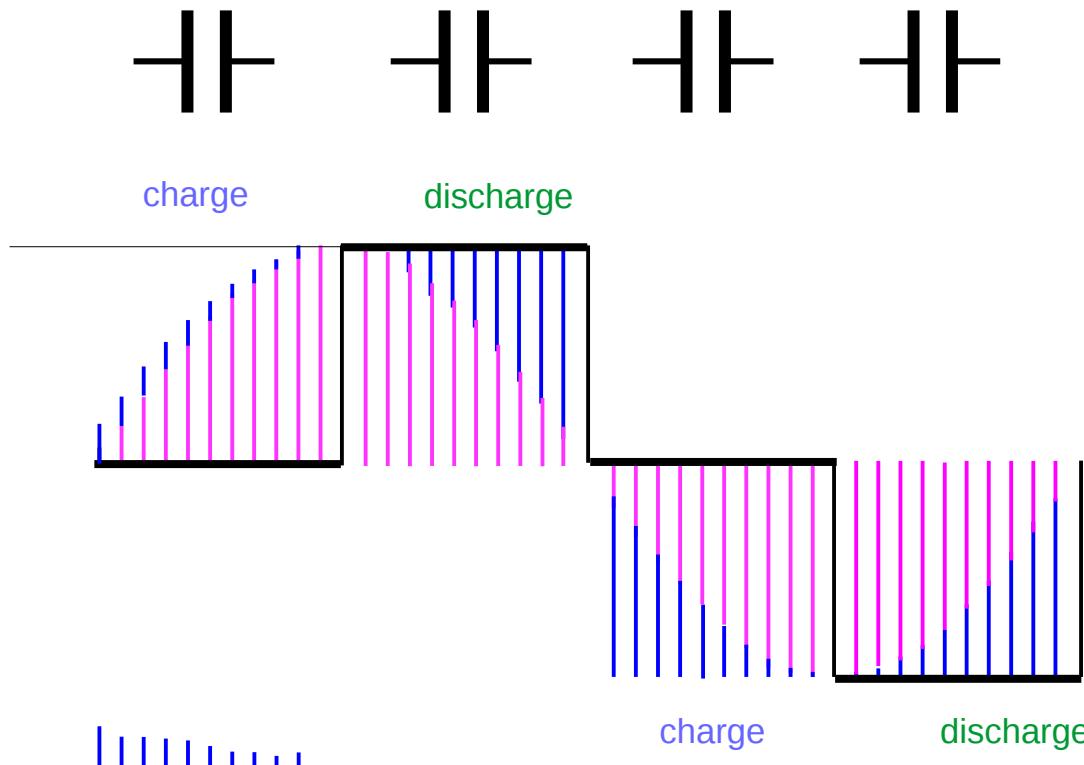


# Everchanging signal pairs

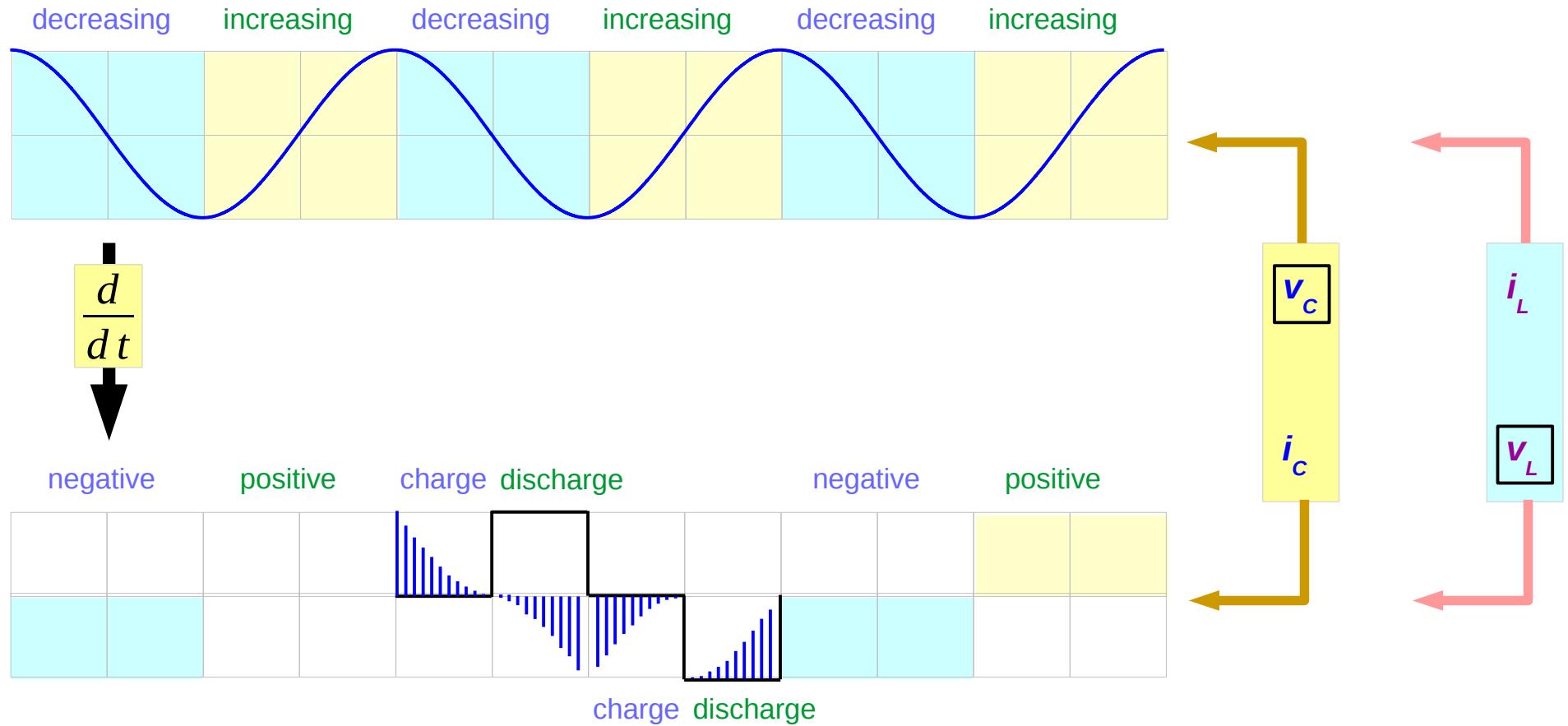

# $I$ leads $V$ by $90^\circ$

*Initial  
charge*

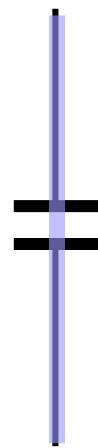


*SHORT*

$$V = 0$$

$I : \text{peak}$


*Full  
charge*

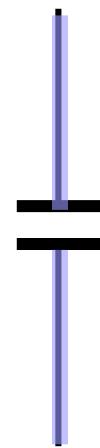

*OPEN*

$$I = 0$$

$V : \text{peak}$

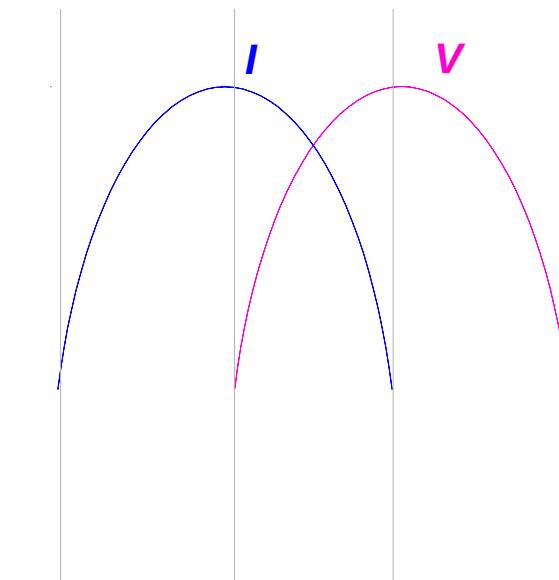

## **References**

- [1] <http://en.wikipedia.org/>
- [2] J.H. McClellan, et al., Signal Processing First, Pearson Prentice Hall, 2003