

CMOS Delay-9 (H.0) Interconnect Delay

20170121

Copyright (c) 2015 - 2016 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".

References


Some Figures from the following sites

[1] <http://pages.hmc.edu/harris/cmosvlsi/4e/index.html>
Weste & Harris Book Site

[2] en.wikipedia.org


Wire Geometry

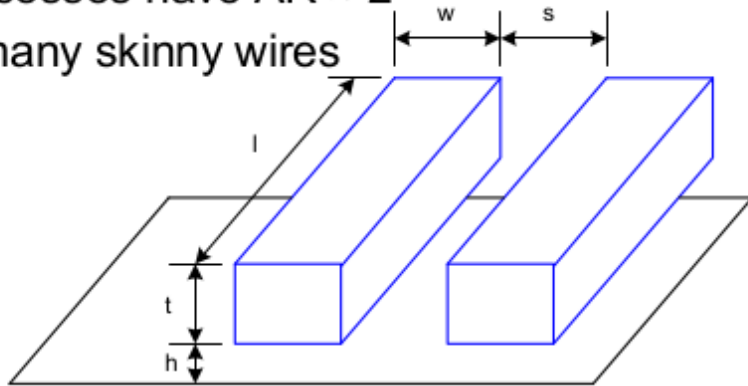- ❑ Pitch = $w + s$
- ❑ Aspect ratio: $AR = t/w$
 - Old processes had $AR \ll 1$
 - Modern processes have $AR \approx 2$
 - Pack in many skinny wires




Interconnect Modeling

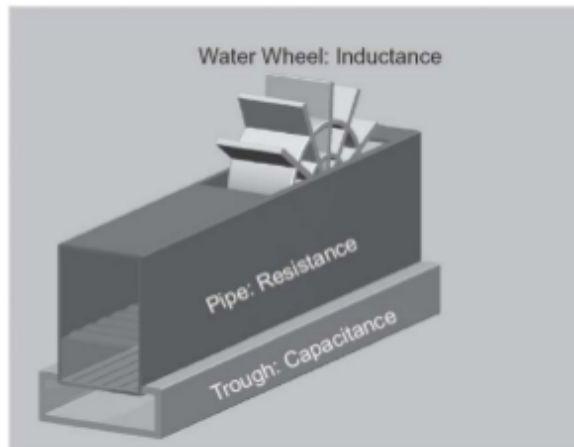- Current in a wire is analogous to current in a pipe
 - Resistance: narrow size impedes flow
 - Capacitance: trough under the leaky pipe must fill first
 - Inductance: paddle wheel inertia opposes changes in flow rate
 - Negligible for most wires



Lumped Element Models

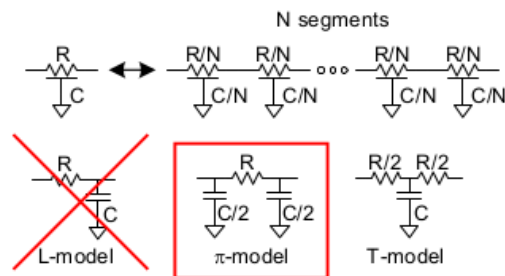- ❑ Wires are a distributed system
 - Approximate with lumped element models




- ❑ 3-segment π -model is accurate to 3% in simulation
- ❑ L-model needs 100 segments for same accuracy!
- ❑ Use single segment π -model for Elmore delay

Wire Resistance

□ $\rho = \text{resistivity } (\Omega \cdot \text{m})$


$R =$

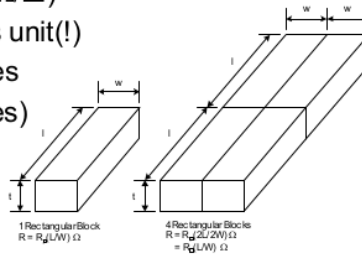- $R_{\square} = \text{sheet resistance } (\Omega/\square)$
 - \square is a dimensionless unit(!)
- Count number of squares
 - $R = R_{\square} * (\# \text{ of squares})$



Wire Capacitance

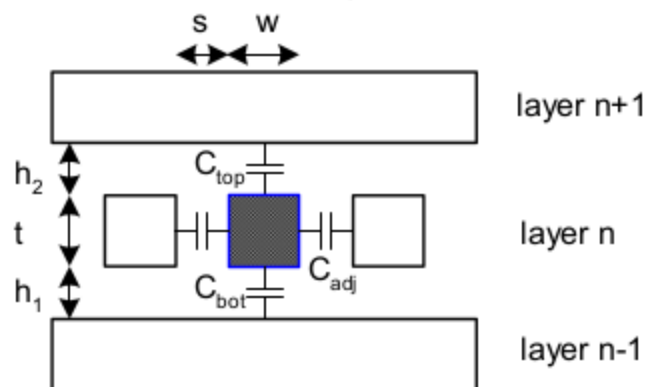- ❑ Wire has capacitance per unit length
 - To neighbors
 - To layers above and below
- ❑ $C_{\text{total}} = C_{\text{top}} + C_{\text{bot}} + 2C_{\text{adj}}$




Diffusion & Polysilicon

- ❑ Diffusion capacitance is very high (1-2 fF/ μm)
 - Comparable to gate capacitance
 - Diffusion also has high resistance
 - Avoid using diffusion *runners* for wires!
- ❑ Polysilicon has lower C but high R
 - Use for transistor gates
 - Occasionally for very short wires between gates

Wire RC Delay


- Estimate the delay of a 10x inverter driving a 2x inverter at the end of the 1 mm wire. Assume wire capacitance is $0.2 \text{ fF}/\mu\text{m}$ and that a unit-sized inverter has $R = 10 \text{ K}\Omega$ and $C = 0.1 \text{ fF}$.

- $t_{\text{od}} =$

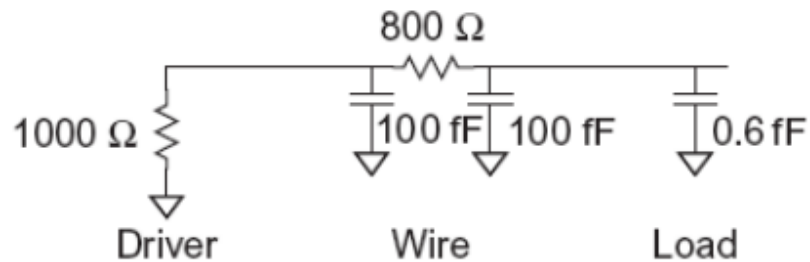


- * A Step tapered wire
- * A tree with sized segments
- * Varieties of wiring trees
- * Steiner Tree
- * Wire Sizing

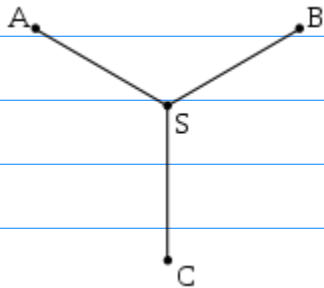https://en.wikipedia.org/wiki/Steiner_tree_problem



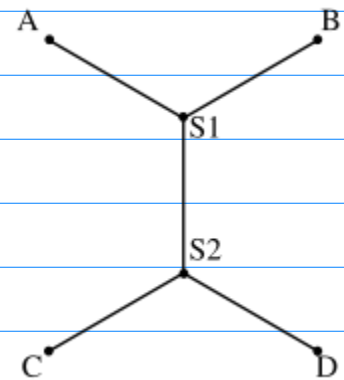Steiner tree for three points A, B, and C (note there are no direct connections between A, B, C). The Steiner point S is located at the Fermat point of the triangle ABC.



Solution for four points—there are two Steiner points, S1 and S2

The Steiner tree problem in graphs can be seen as a generalization of two other famous combinatorial optimization problems: the (non-negative) shortest path problem and the minimum spanning tree problem. If a Steiner tree problem in graphs contains exactly two terminals, it reduces to finding a shortest path. If, on the other hand, all vertices are terminals, the Steiner tree problem in graphs is equivalent to the minimum spanning tree.