

# BJT Characteristics (H.1)

20170110

Copyright (c) 2016 - 2017 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".



# References


Based



[1] Floyd, Electronic Devices 7th ed



[2] Cook,

[2] en.wikipedia.org

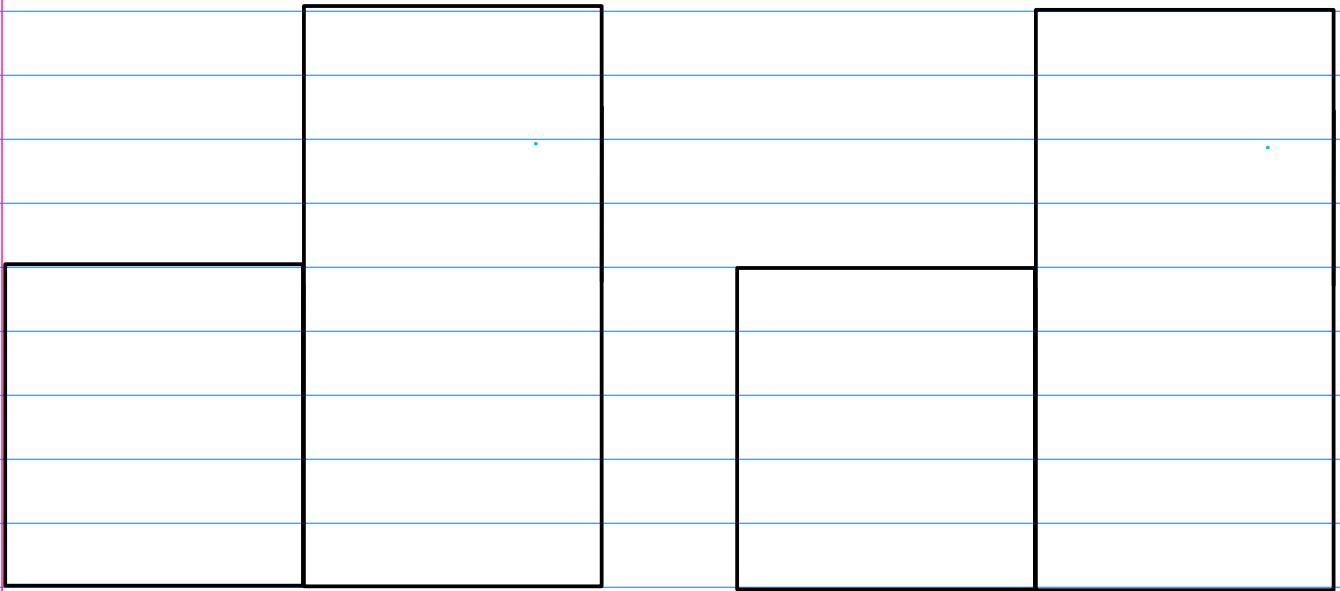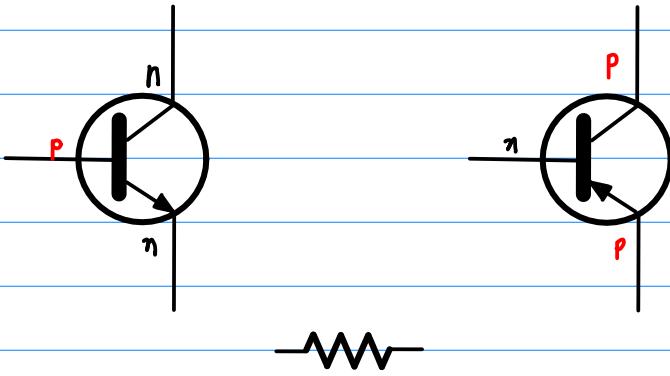

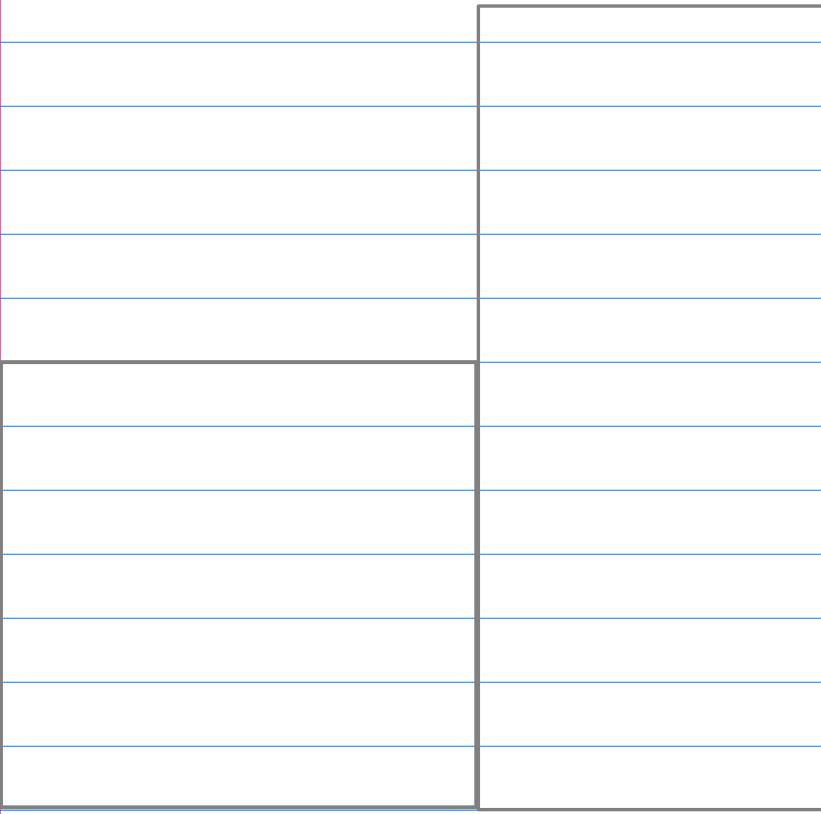

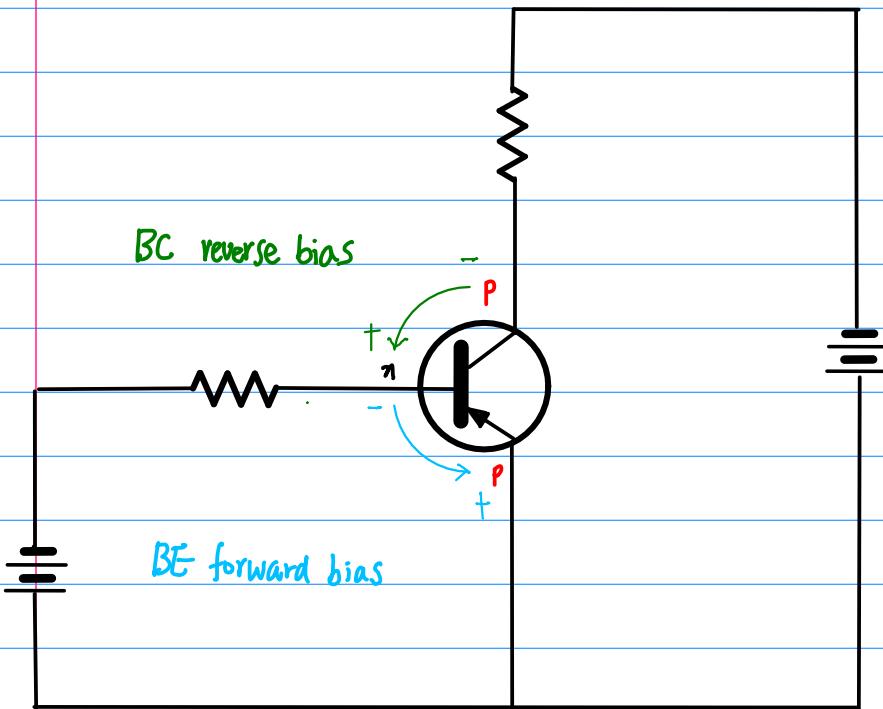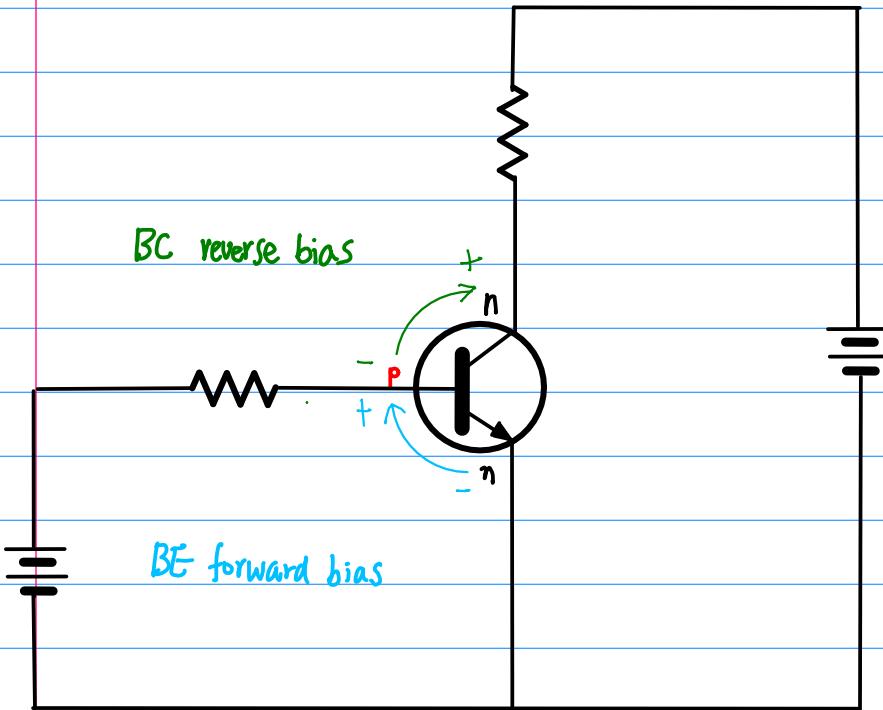

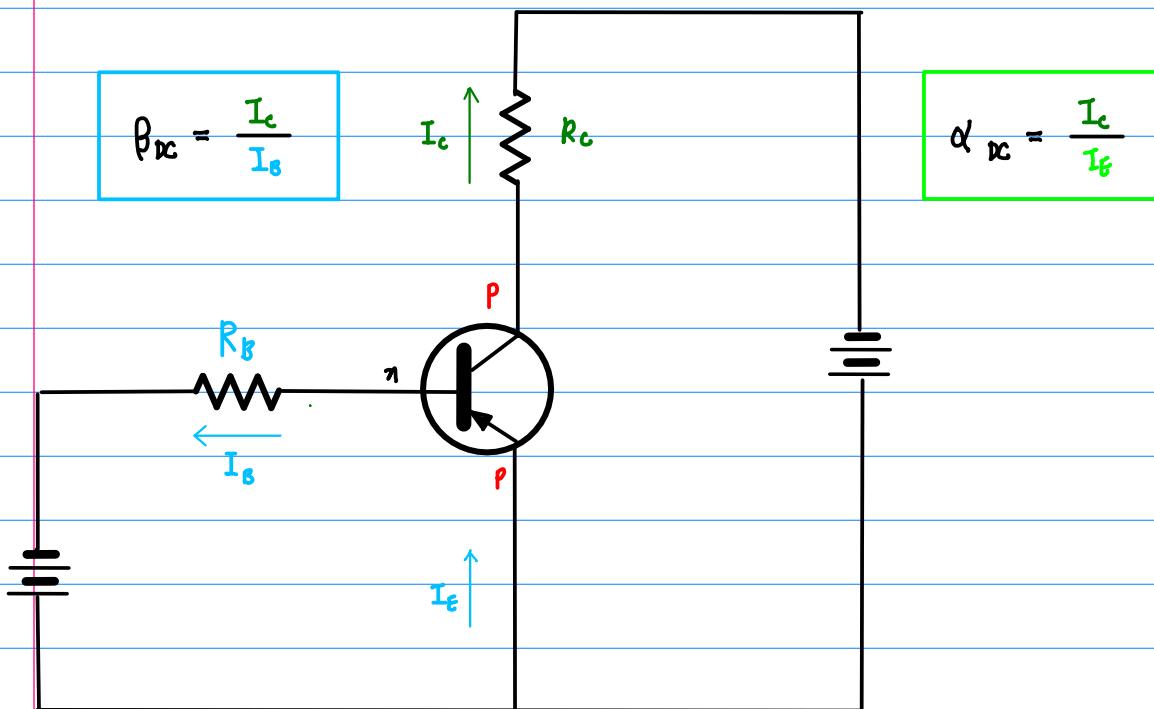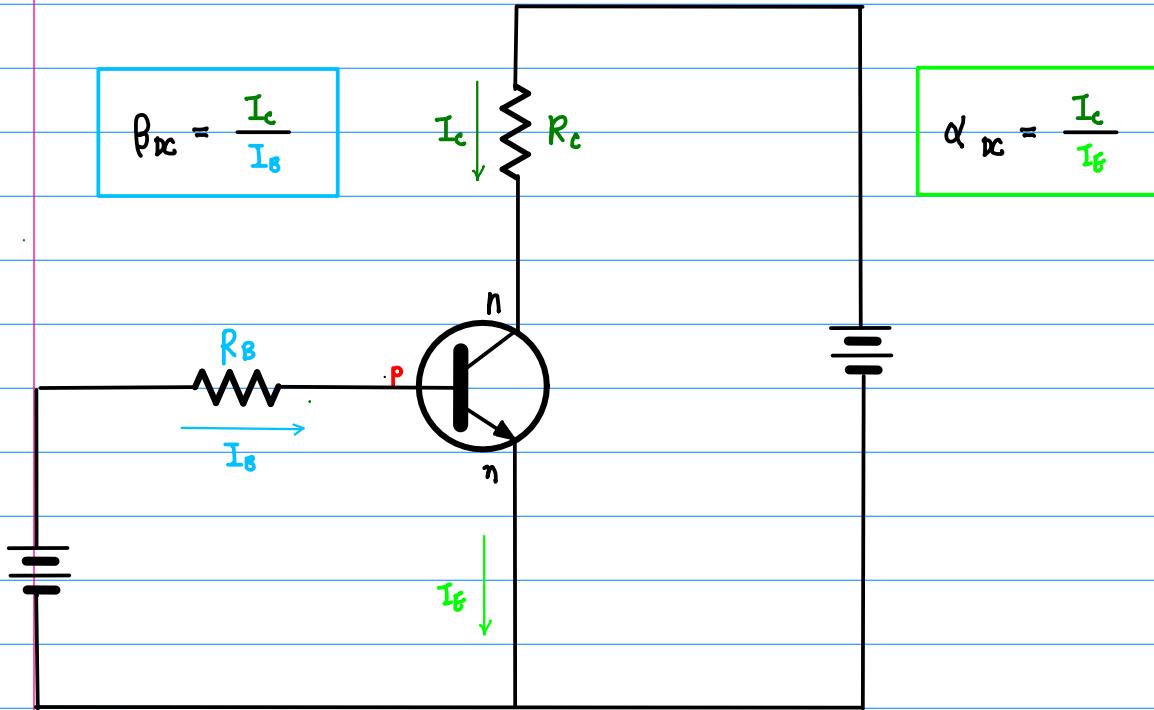



$$\beta_{DC} = \frac{I_C}{I_S}$$


20 ~ 200

$$h_{FE} = \beta_{DC}$$

$$\alpha_{DC} = \frac{I_C}{I_E}$$

0,95 ~ 0,99

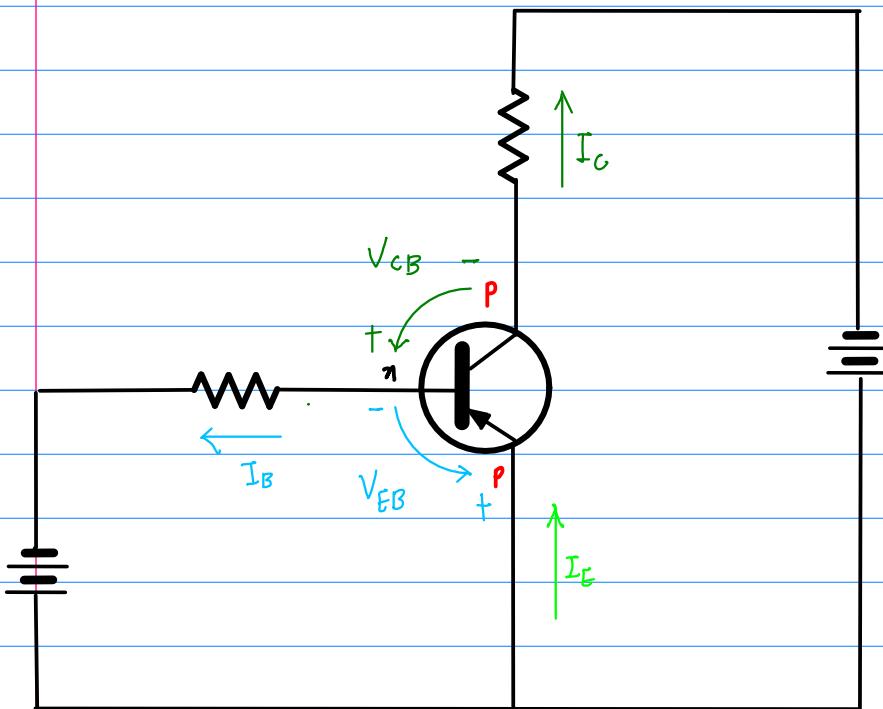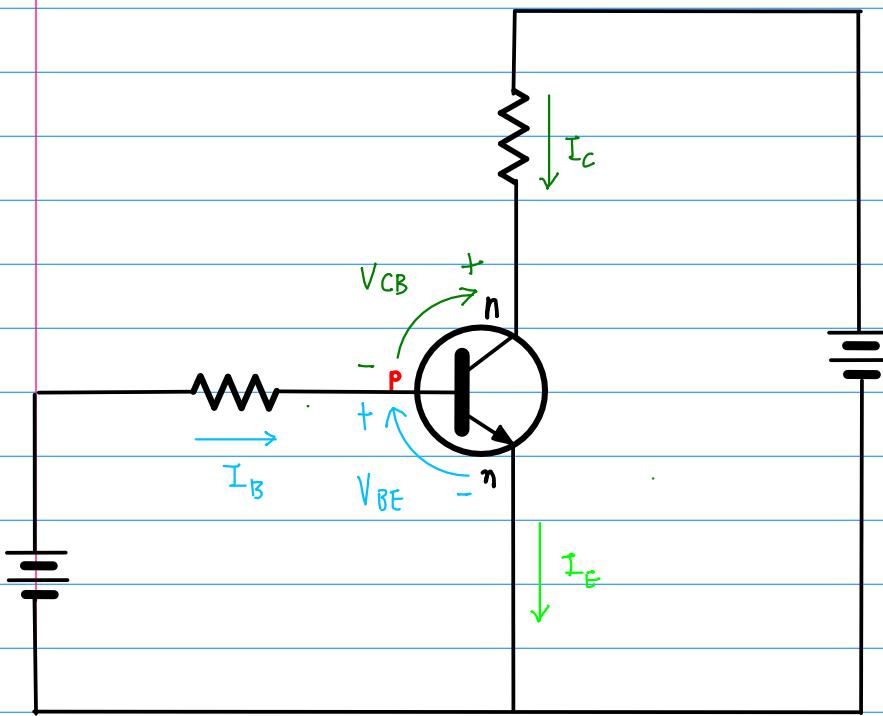

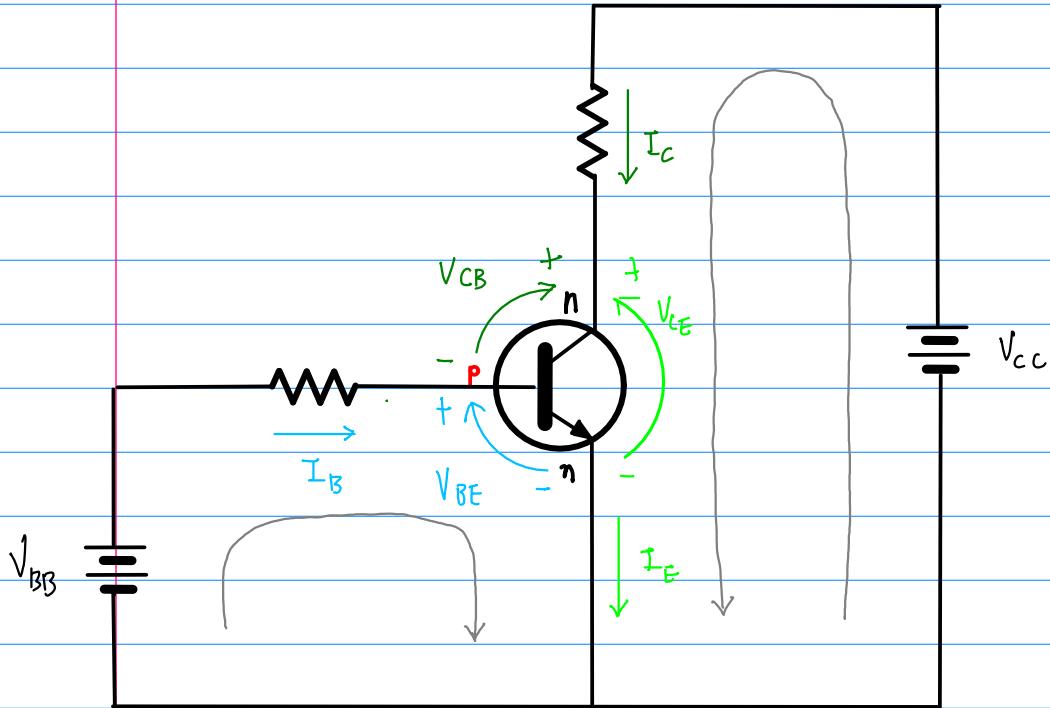



$$V_{BB} = I_B R_B + V_{BE}$$



$$V_{CC} = I_C R_C + V_{CE}$$

$$I_B = \frac{V_{BB} - V_{BE}}{R_B}$$



$$I_C = \frac{V_{CC} - V_{CE}}{R_C}$$

$$V_{CE} = V_{CC} - I_C R_C$$

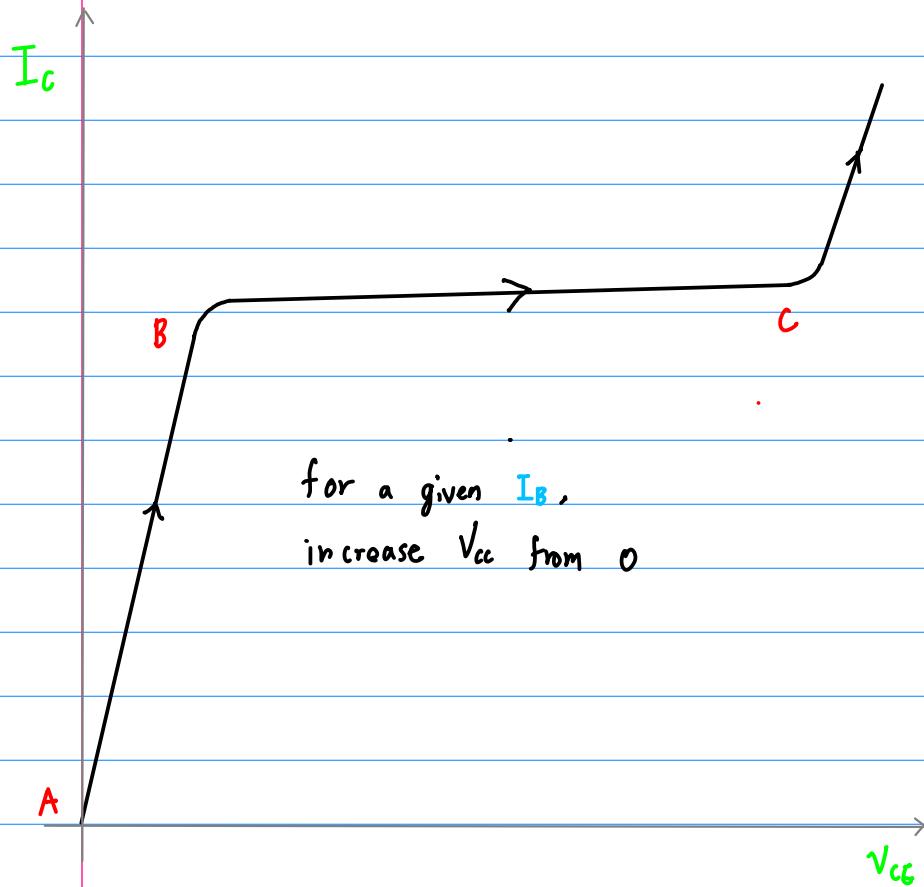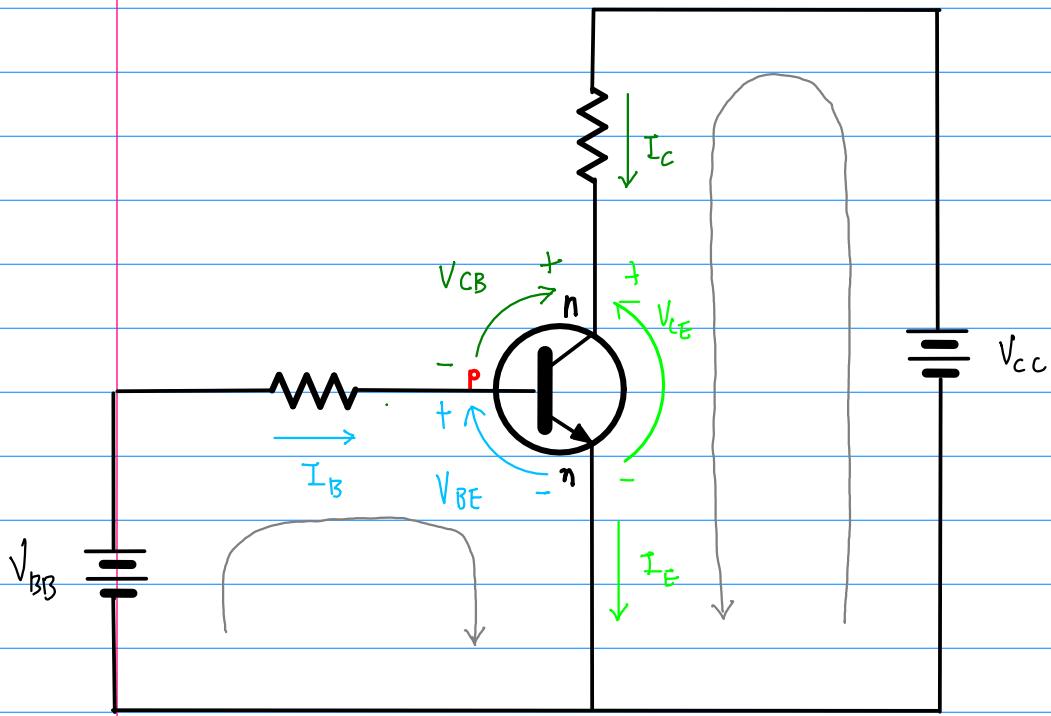

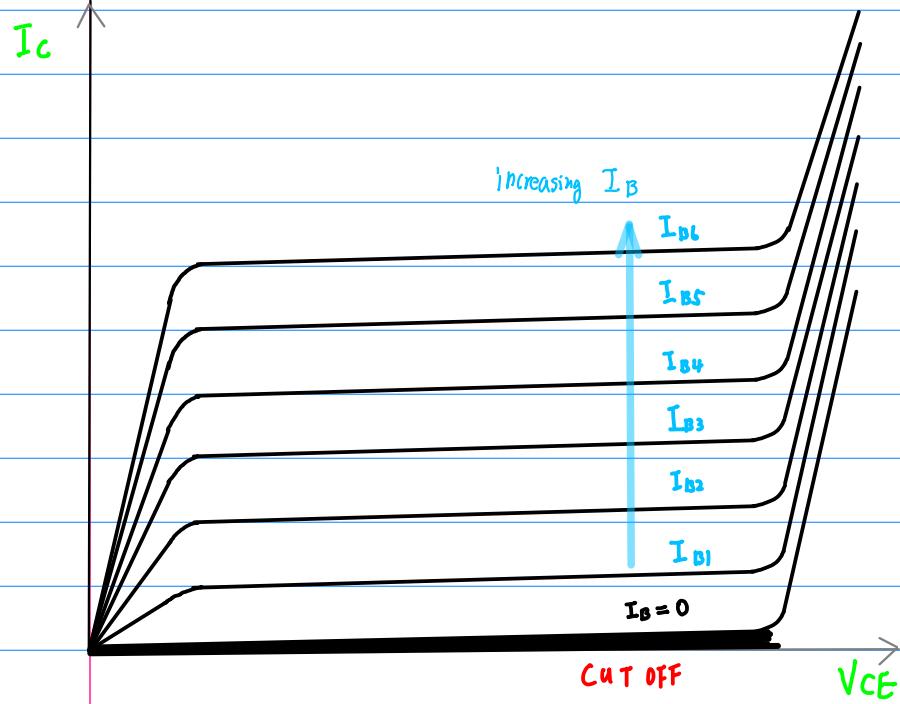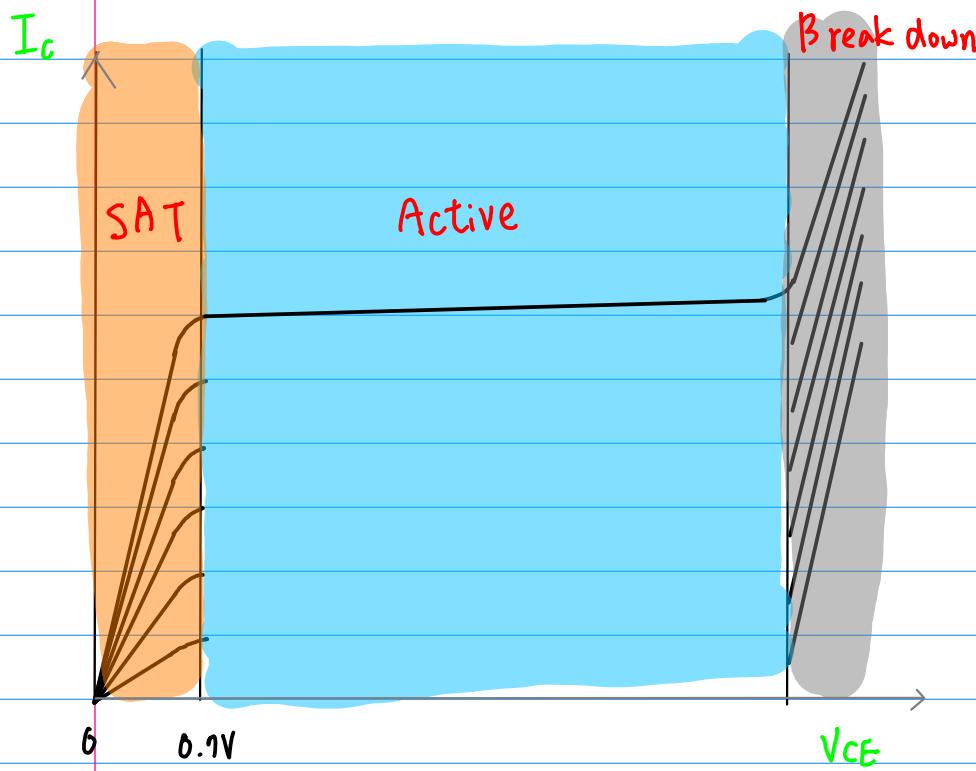

(A)

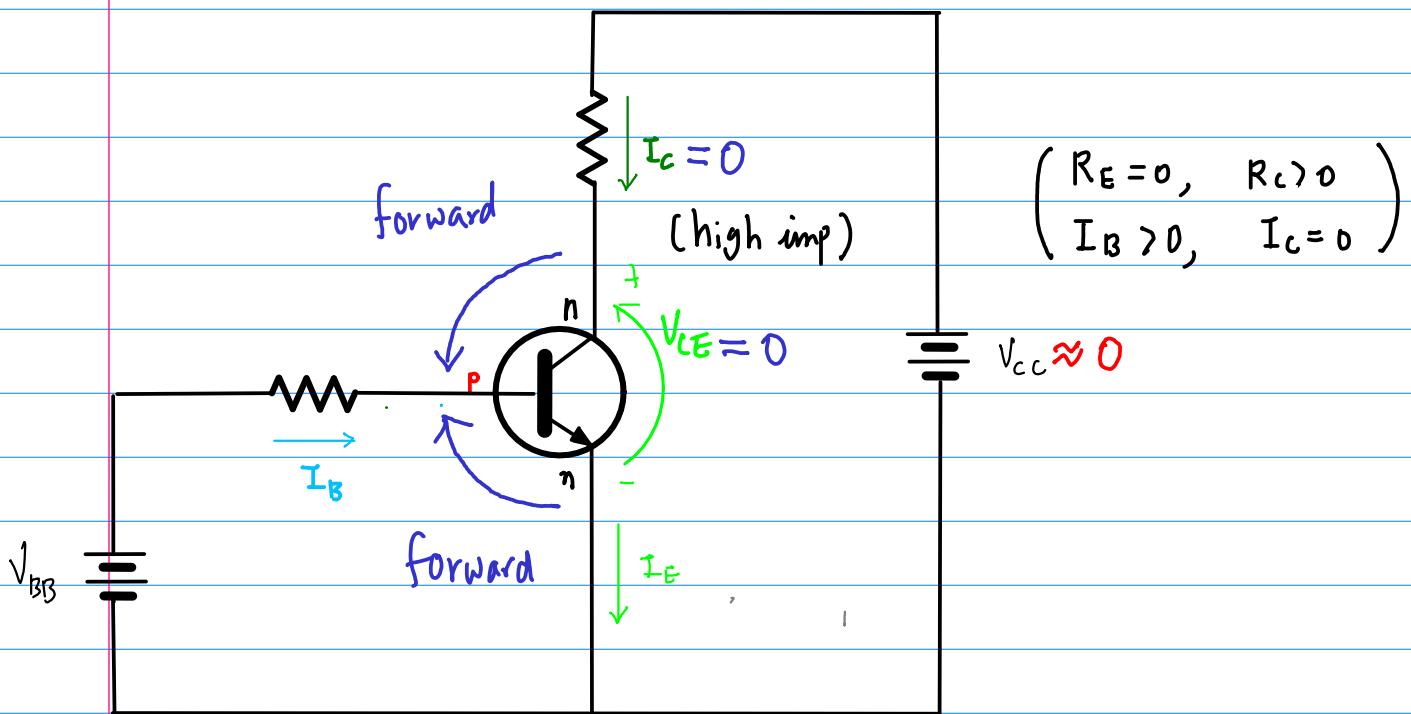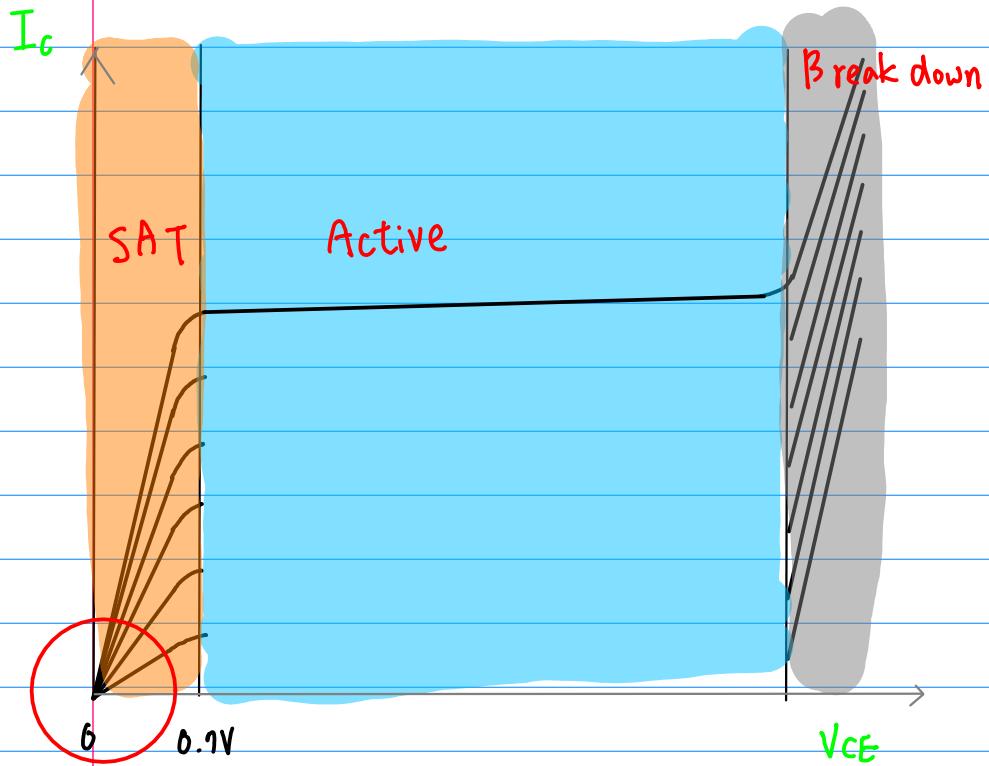


(A)

$$V_{CC} \approx 0$$







2 paths

B  $\rightarrow$  E
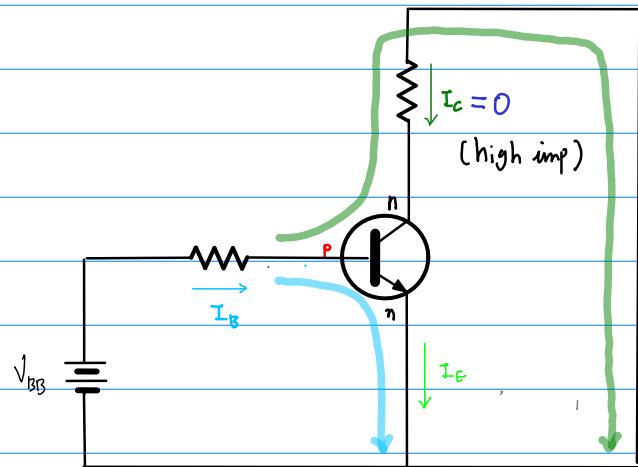
$$B \rightarrow C \quad (R_C) \rightarrow I_C = 0$$





(A-B)

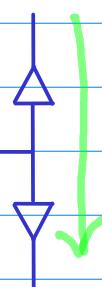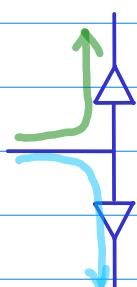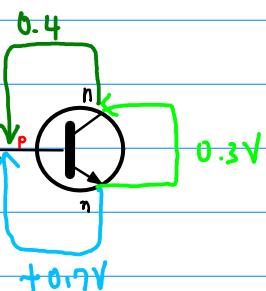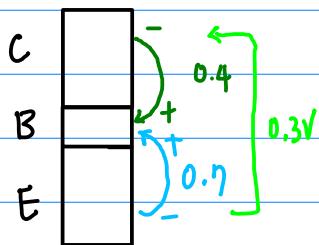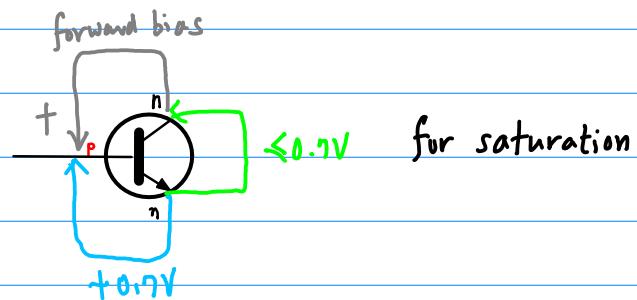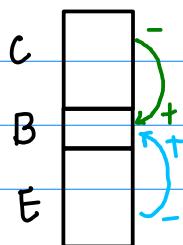

(B)-C

Active (Linear)

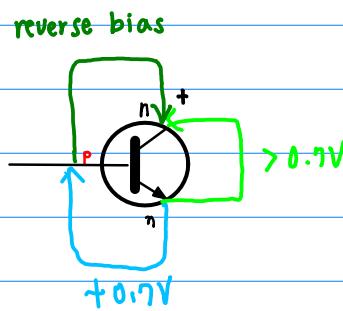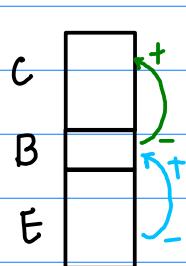

active (linear)

