

# Logic Families Dynamic-2 (H.2)

20151215

Copyright (c) 2015 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".

# References

Some Figures from the following sites

[1] <http://pages.hmc.edu/harris/cmosvlsi/4e/index.html>

Weste & Harris Book Site

[2] [en.wikipedia.org](http://en.wikipedia.org)

[3] Digital Integrated Circuits : A Design Perspective,

Jan M. Rabaey,

(<http://bwracs.eecs.berkeley.edu/Classes/lcBook/>)

[4] Digital Electronics and Design with VHDL

Pedroni

# Other MOS Architectures

## Static MOS

Pseudo-nMOS Logic

Transmission-gate Logic

BiCMOS Logic




## Dynamic MOS

Dynamic Logic



Domino Logic

C2MOS Logic

# Dynamic Logic

 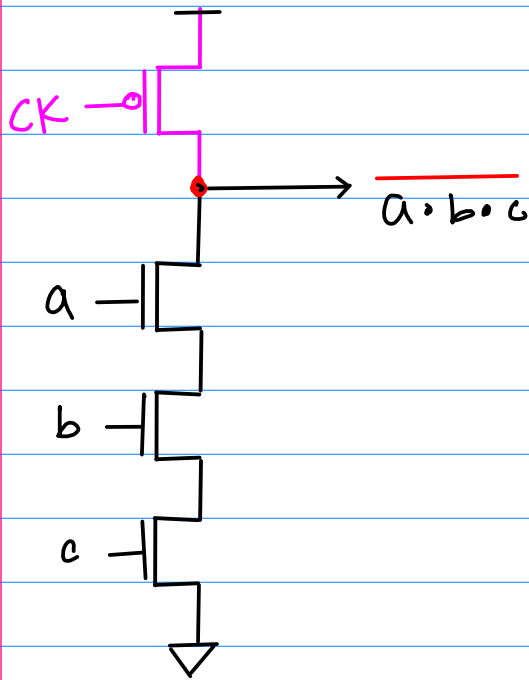 





a clocked strong pull-up pMOS

 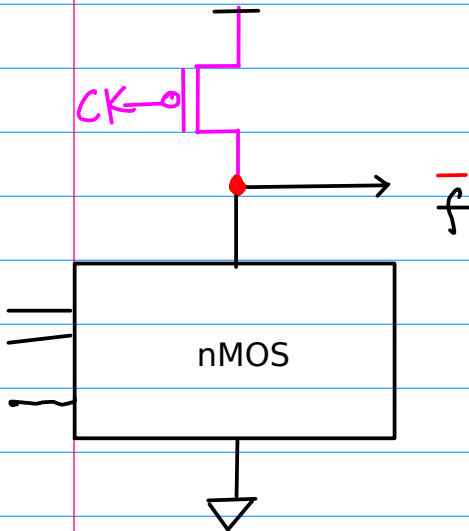

compared to pseudo-nMOS,

- smaller static power consumption  
pMOS ON only while clock=0
- faster rising time  
larger W/L, smaller R



# Footed Dynamic Logic

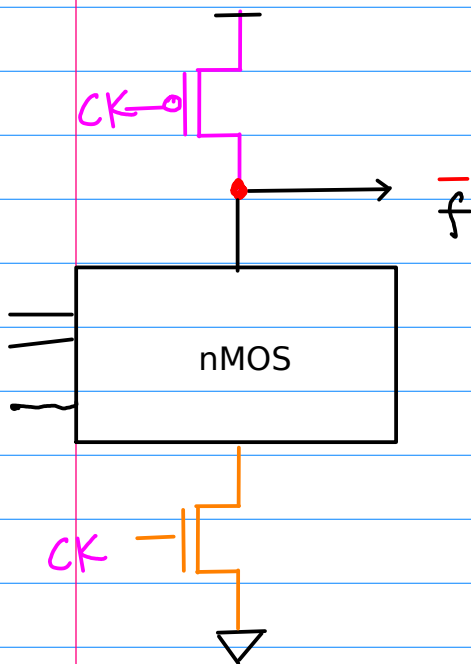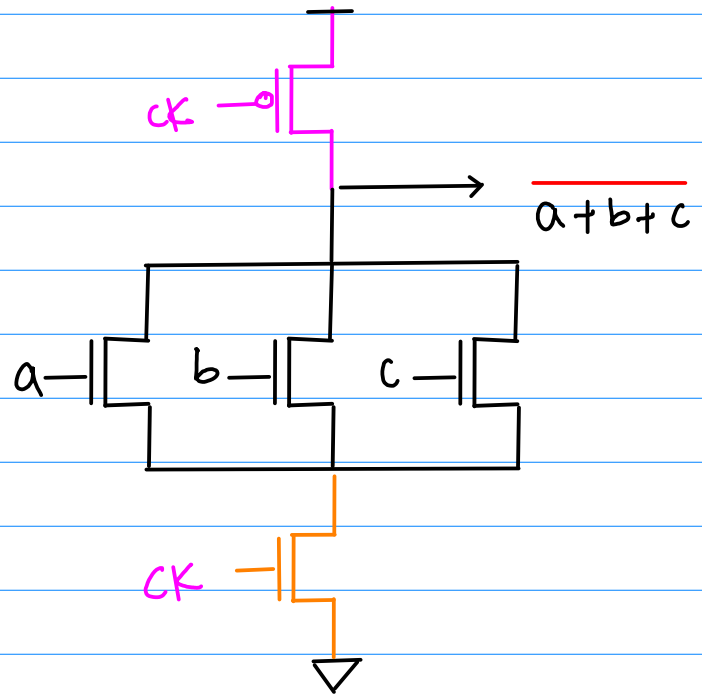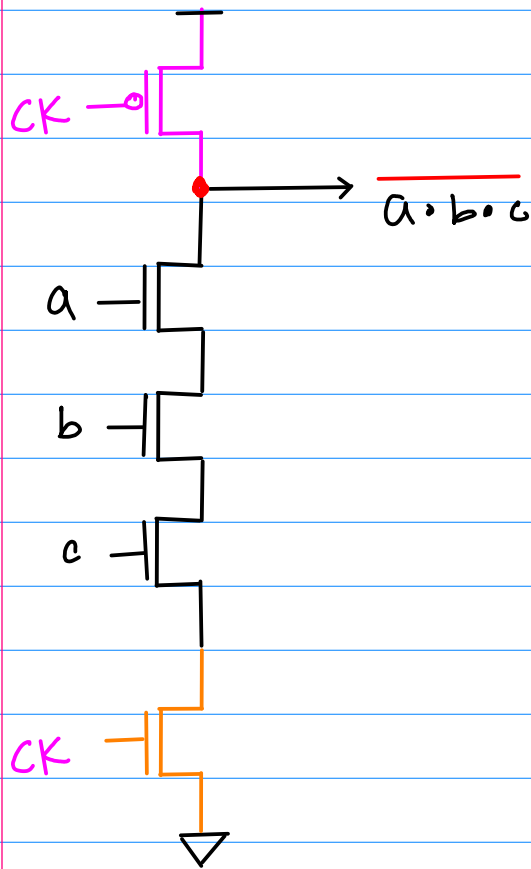 

both power supply connections clocked

more faster output transition  
nearly zero static power consumption

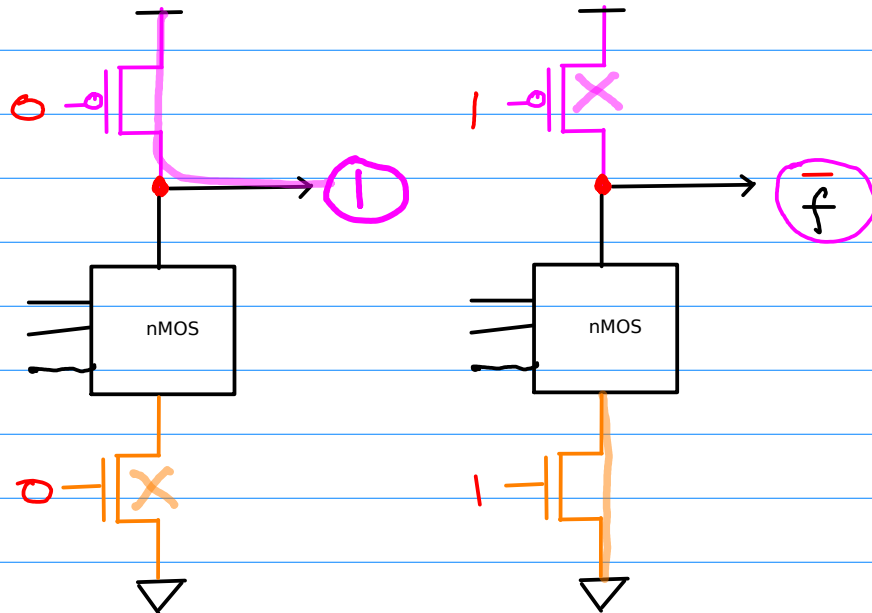 slightly more complex circuit  
heavy loaded clock



every output will be pulled up to  $V_{dd}$  during precharge

since these outputs feed the inputs of other logic gates

all inputs are assumed to be 'H' during precharge but no conditional discharge


precharge pMOS : On  
footed nMOS : Off

now every output that were forced to be held as 'H' during precharge, evaluates their real values, through conditional discharging according to their inputs

However, during evaluation phase, no pulling up is allowed.

So the allowed output transition is only 1  $\rightarrow$  0 (falling)

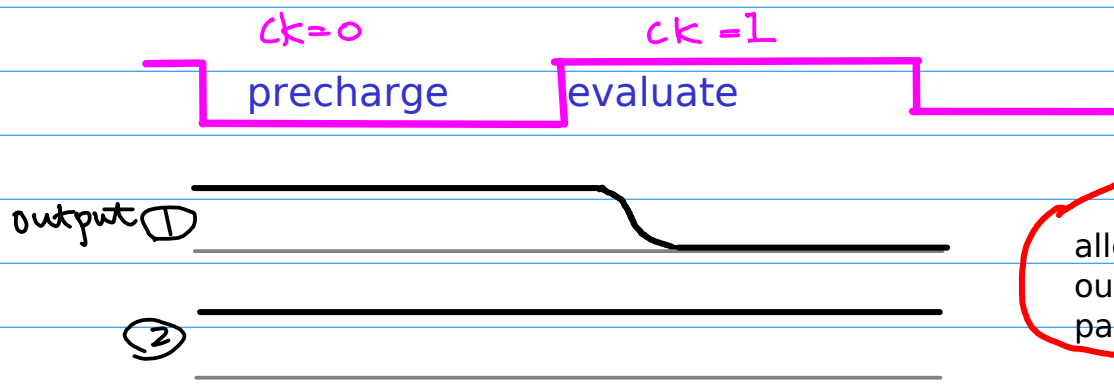
0  $\rightarrow$  1 transition is not possible



allowed output patterns

0 to 1 inputs are always OK

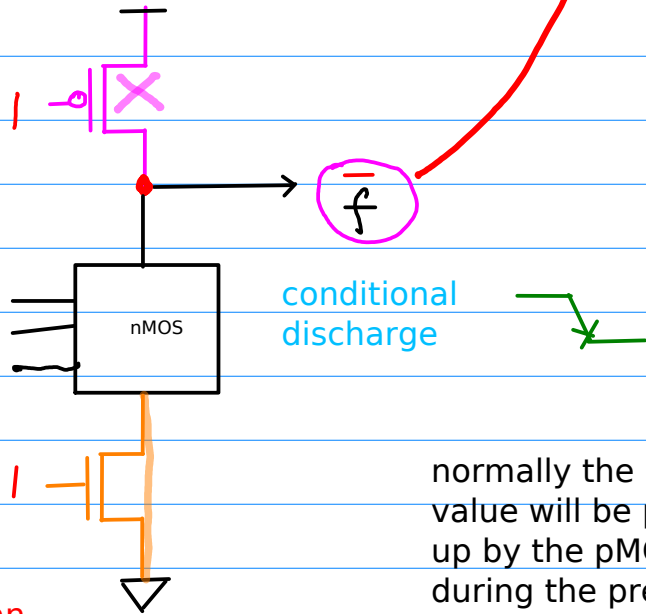some inputs turns on nMOS to be connected to the ground




1 to 0 inputs will turn off nMOS

sometimes this can make 0->1 output transition that is not allowed


normally the logic value will be pulled up by the pMOS during the precharge

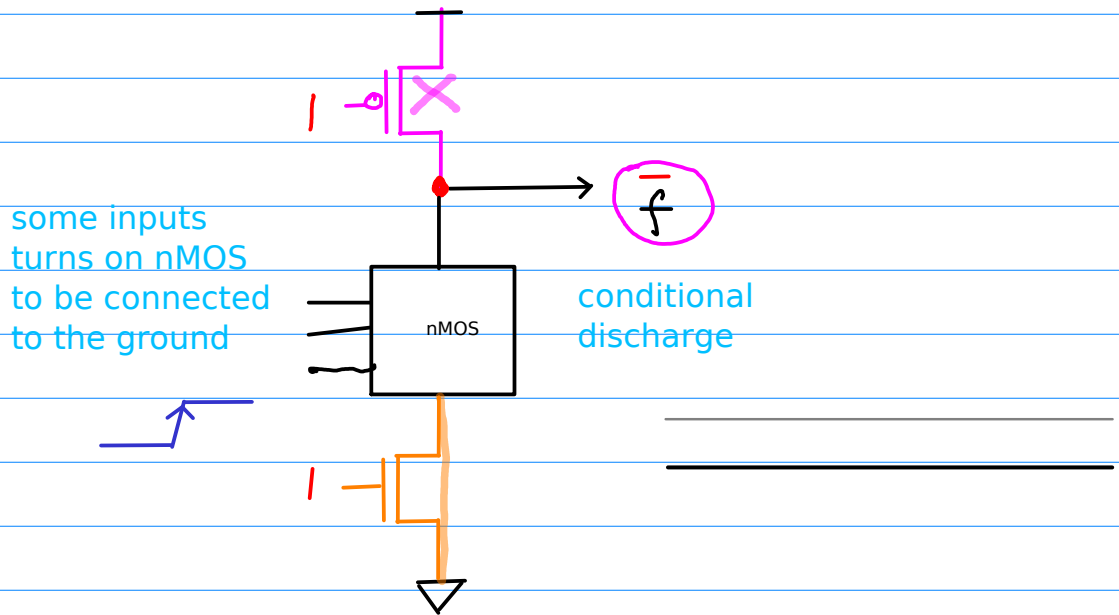but the evaluate phase of the Domino Logic, pMOS is always turned off, thus no pulling up possible




input transitions

output transitions

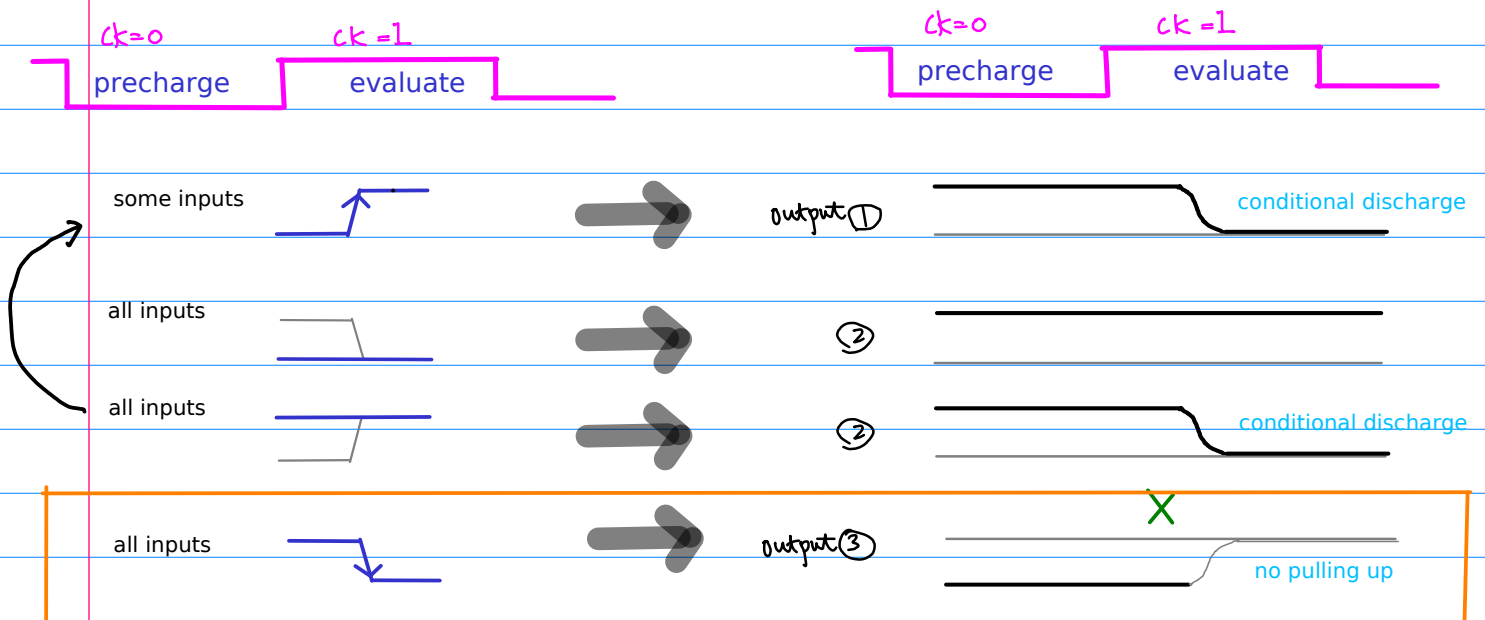







therefore, prevent the last case



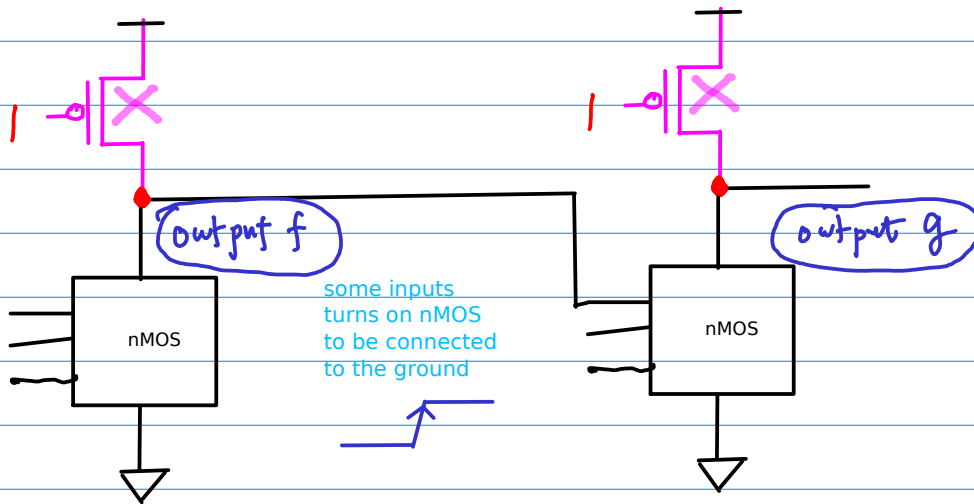

output f

output g

      


sometimes

impossible


not allowed output transition

impossible




conditional discharge

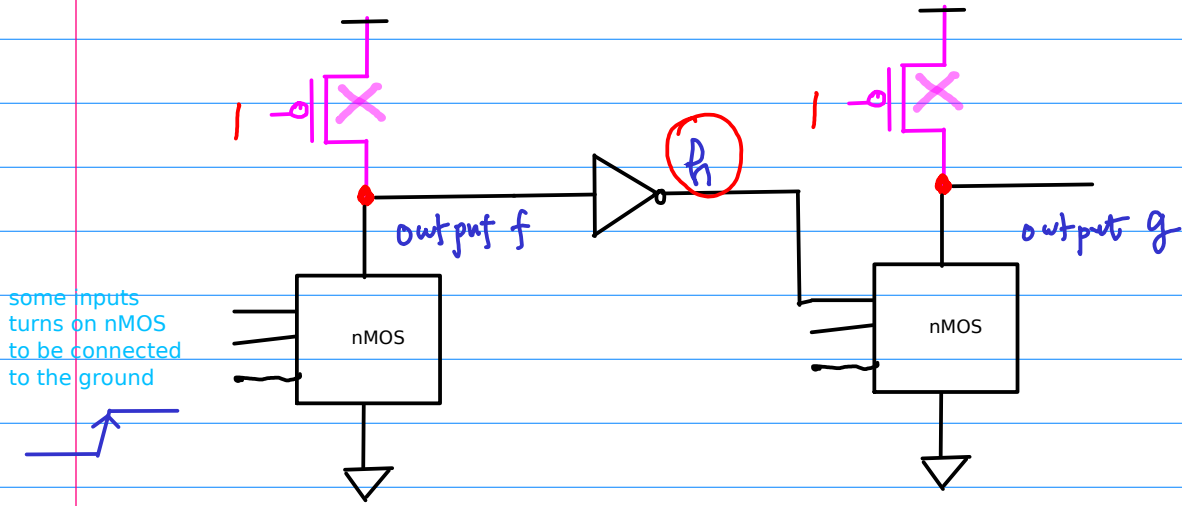

 some inputs turns on nMOS to be connected to the ground



all inputs

   


output  $h$

with INV

output  $g$



# Monotonicity Condition

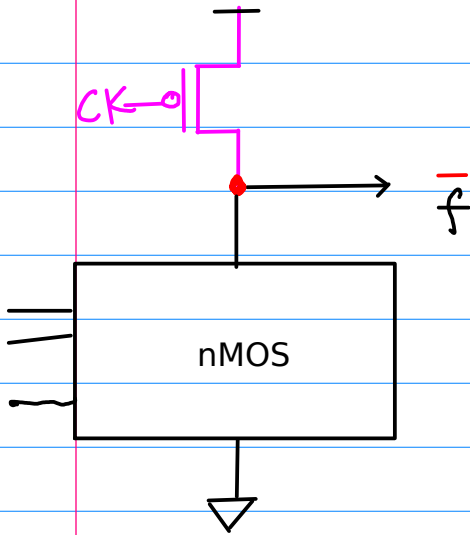

foot, unfoot

both dynamic logic has a problem when the output of the one gate must be connected to the input of another

-- use domino logic

  


## Domino Logic

Never allow input transition from H to L  
Then only the allowed output transitions will result

## Monotonicity Condition

the inputs are required to be monotonically rising


# Domino Logic

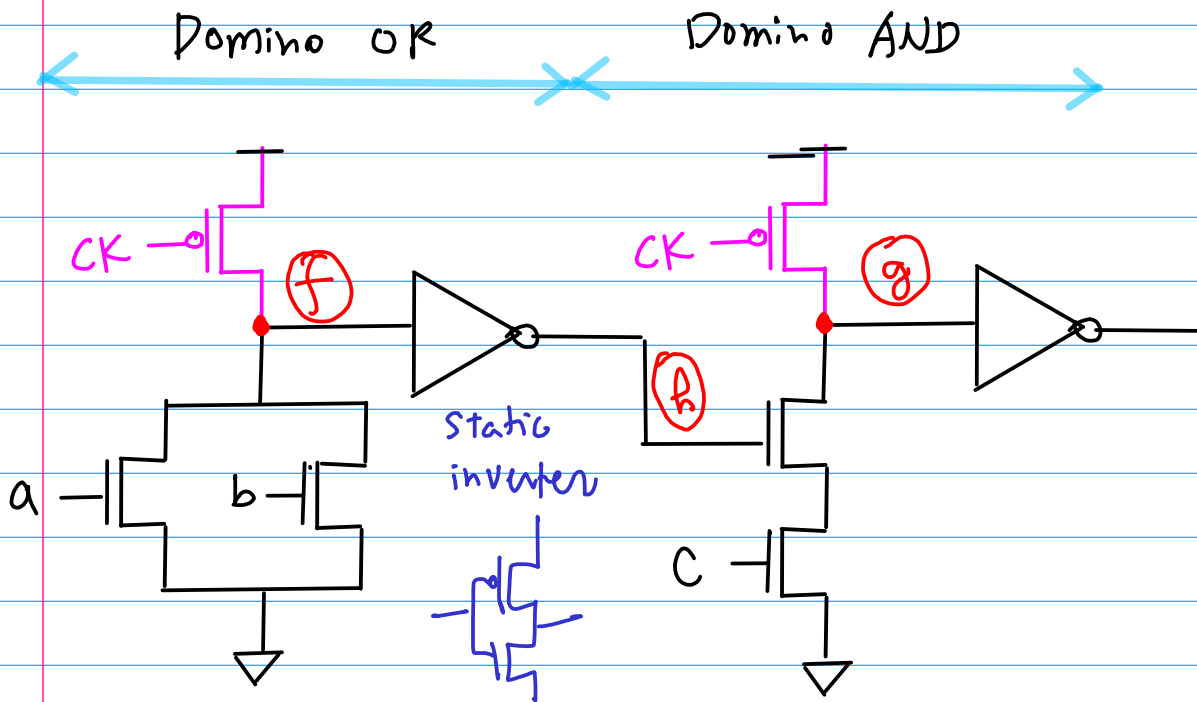


static inverters between dynamic stages

during precharge phase, the output becomes H by the pull-up transistor, and the inverter's output becomes L

 
this L stays or change to H during evaluation phase therefore, the undesirable H-to-L transition is avoided



# Pipeline

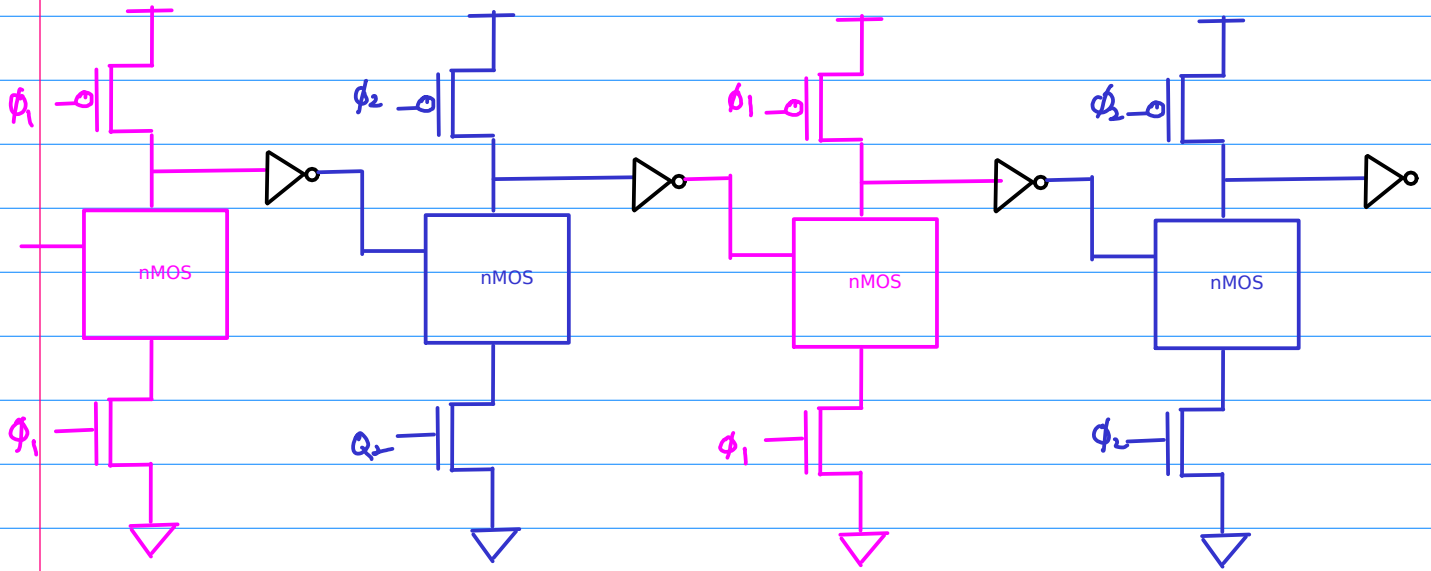


$\phi_1$  clock

 

$\phi_2$  clock


Without FF's & latches, a pipeline can be constructed

# Clocked CMOS Logic (C<sup>2</sup>MOS)

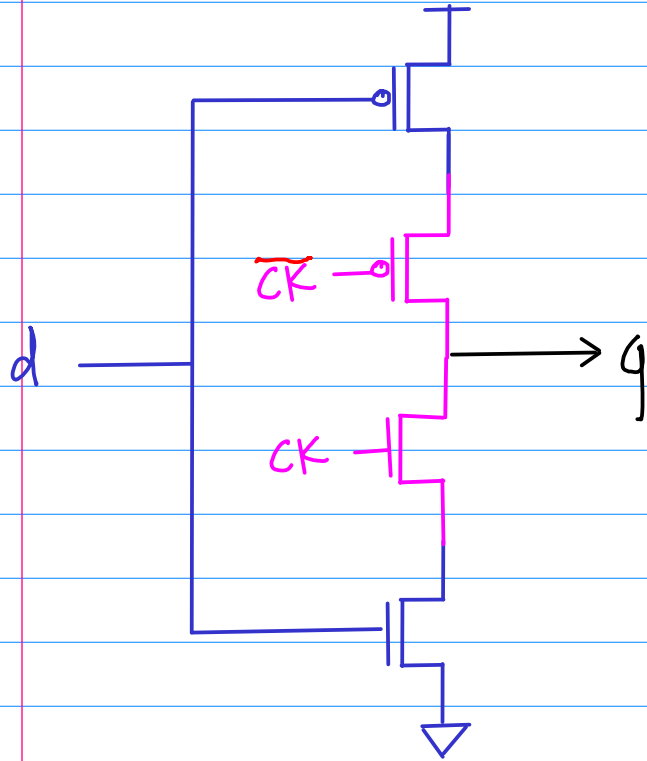


similar to the 3-state buffer

 output node cannot be shared with other circuits



$q = \bar{d}$   
transparent

 

$q = Z$  float  
opaque