

BJT Bias Operating Point (H.4)

20170117

Copyright (c) 2016 - 2017 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".



References

Based

[1] Floyd, Electronic Devices 7th ed



[2] Cook,


[2] en.wikipedia.org

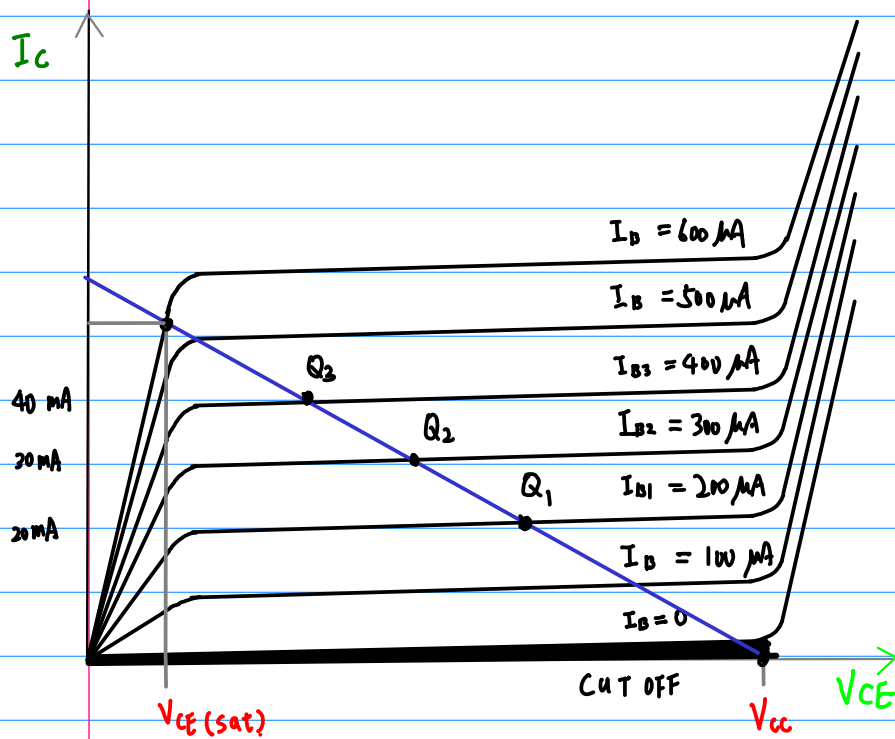
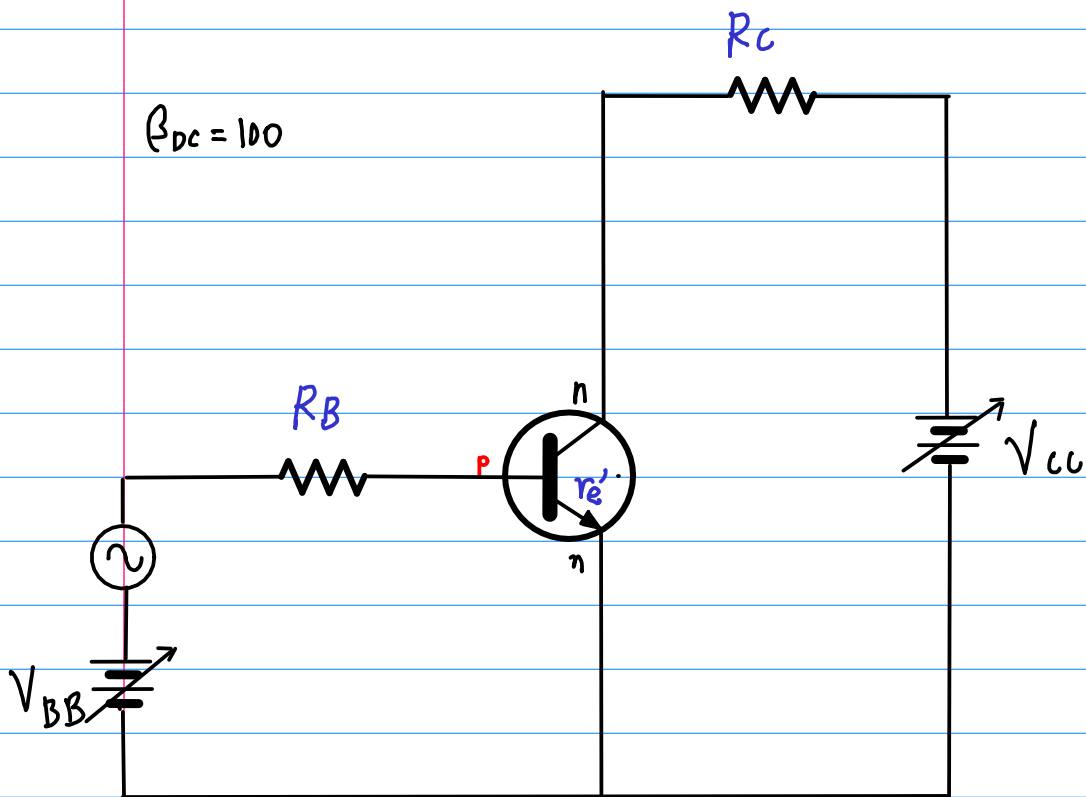




$\beta_{DC} = 100$


$I_{B3} = 400 \mu A$	$\rightarrow * 100 \rightarrow$	$I_{C3} = 40 mA$
$I_{B2} = 300 \mu A$	$\rightarrow * 100 \rightarrow$	$I_{C2} = 30 mA$
$I_{B1} = 200 \mu A$	$\rightarrow * 100 \rightarrow$	$I_{C1} = 20 mA$

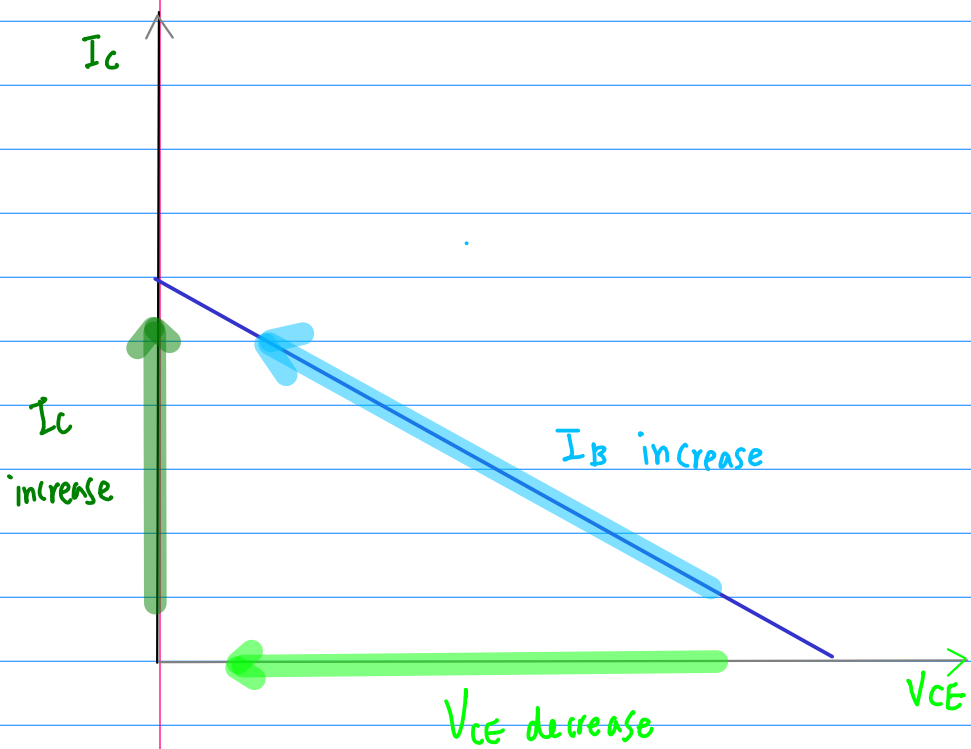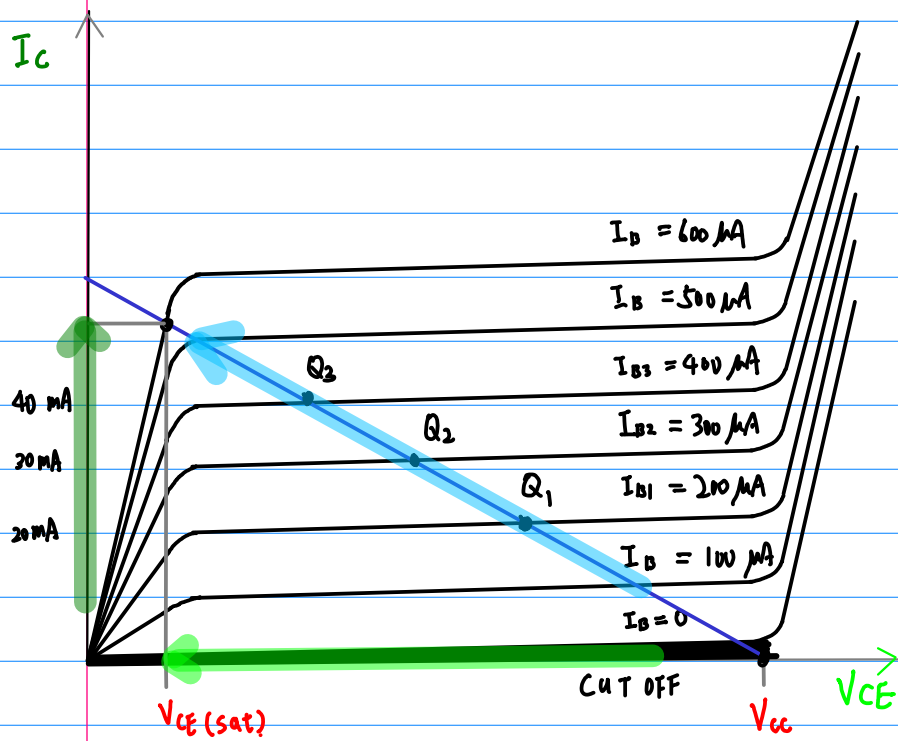


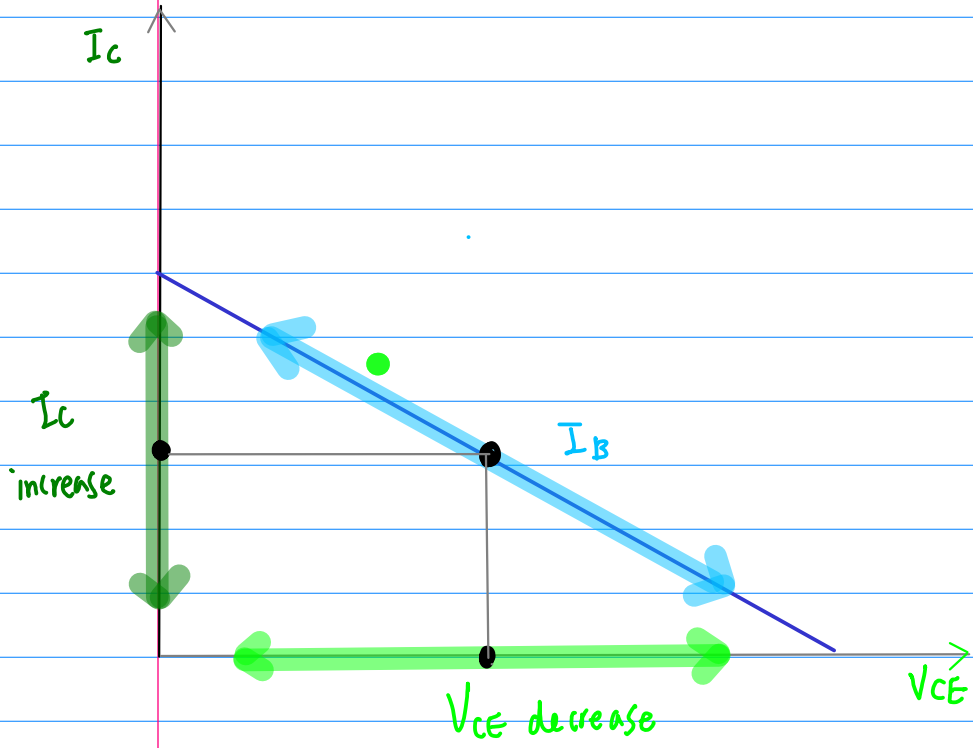

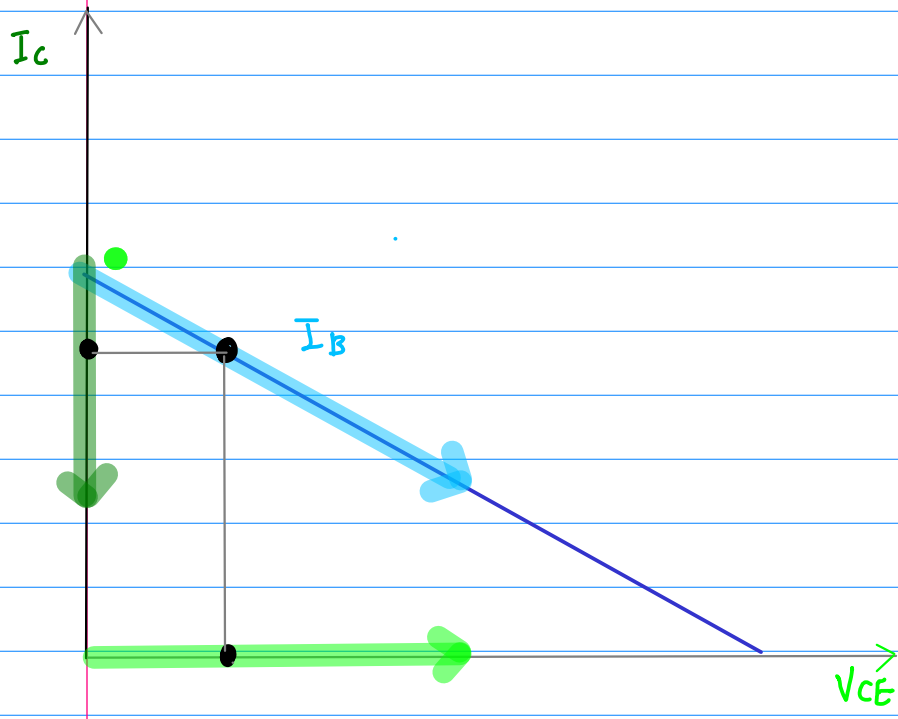
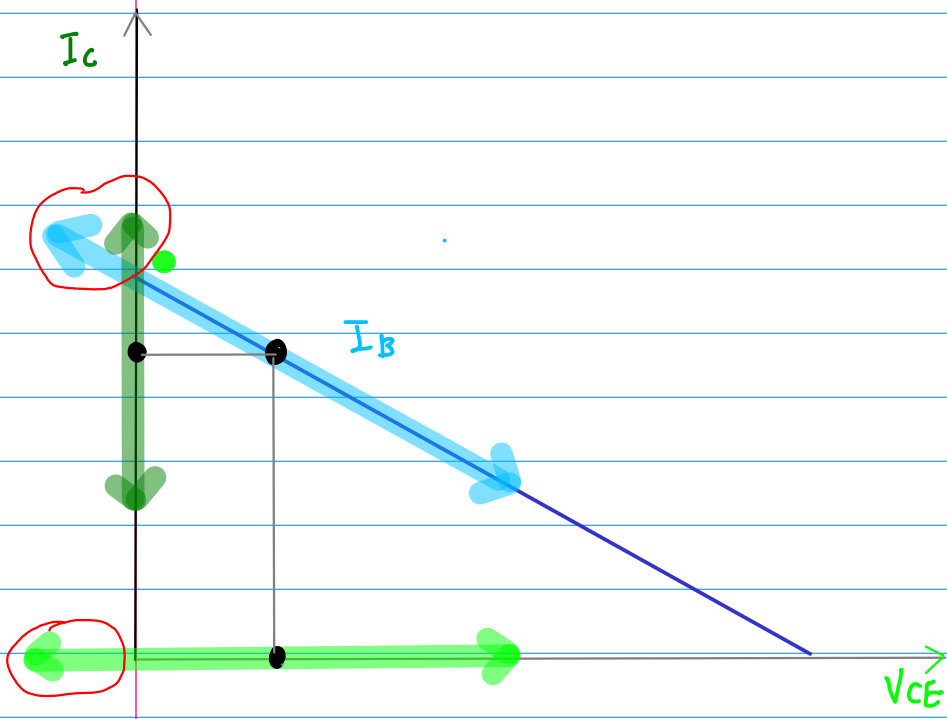


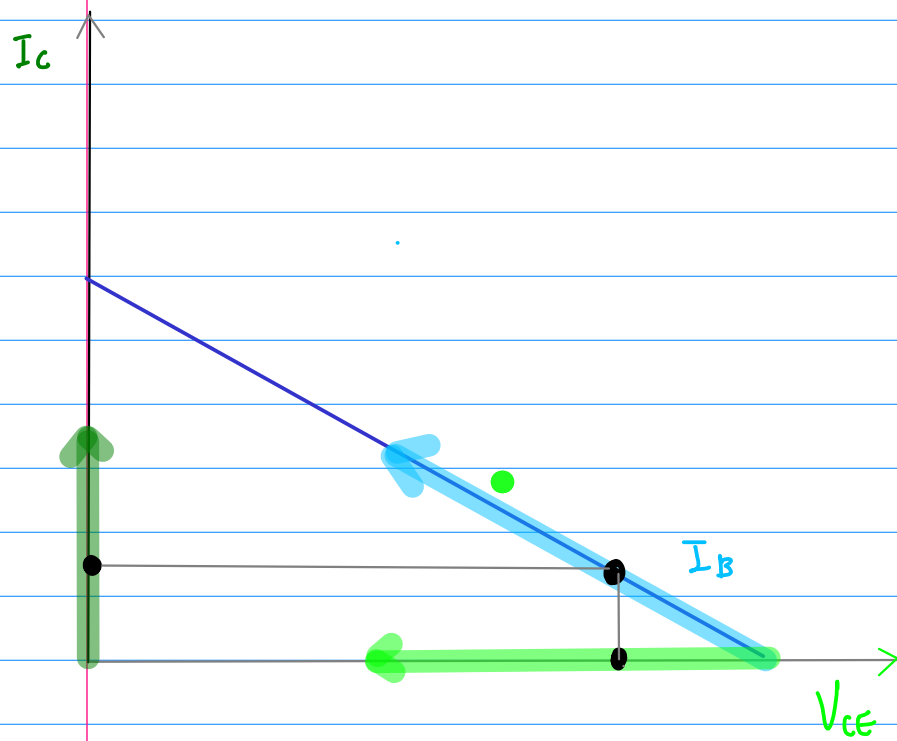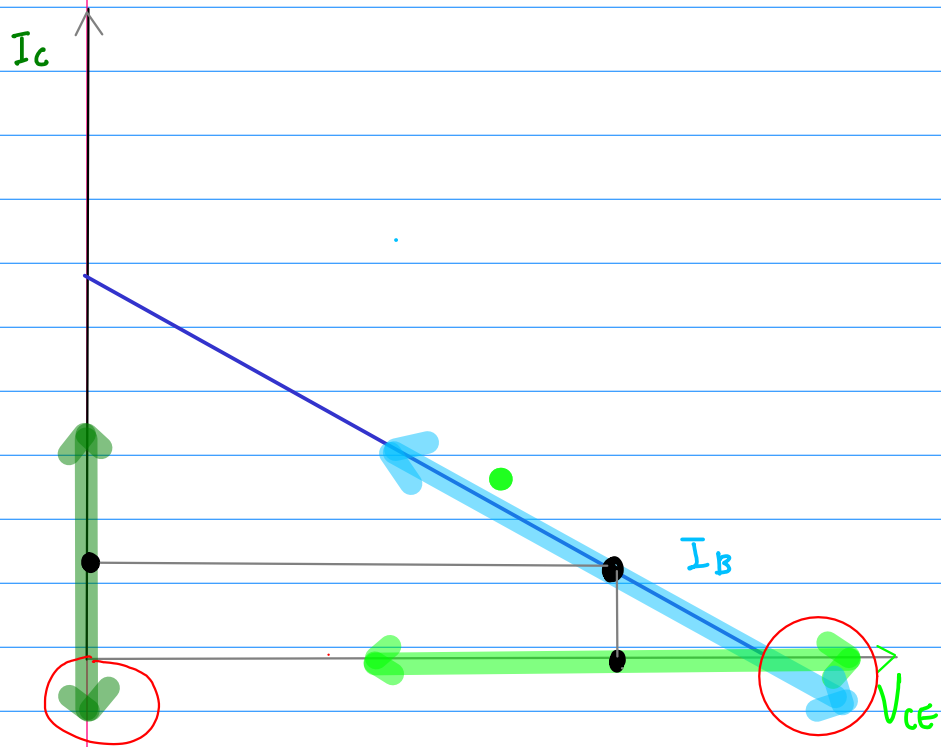

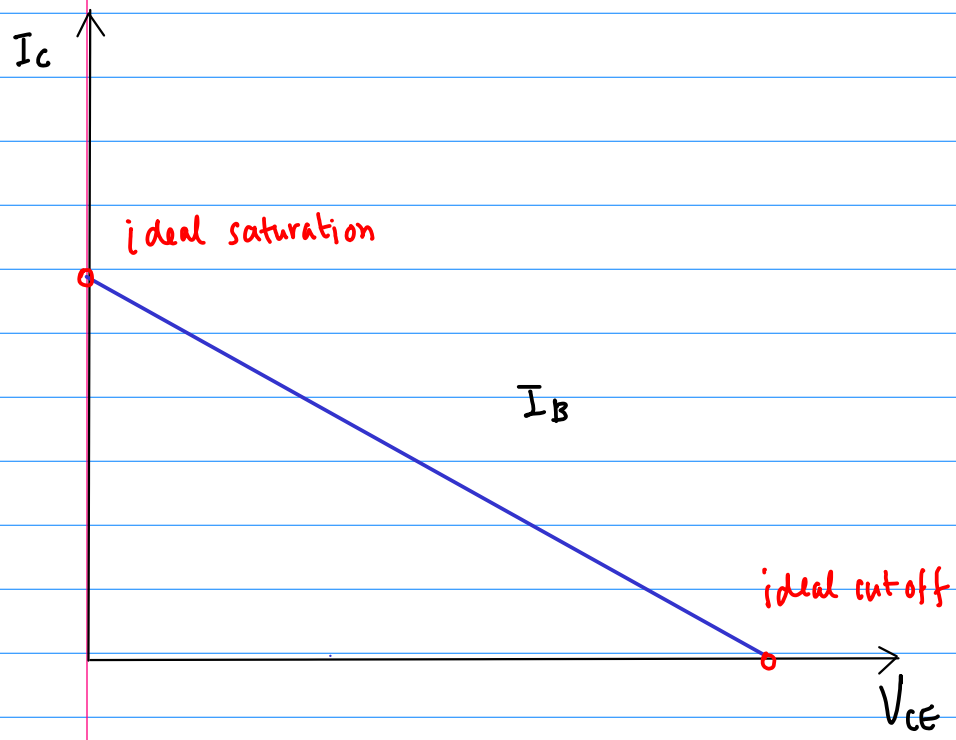

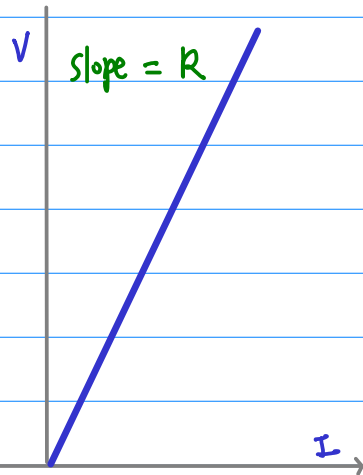


$$V = RI$$

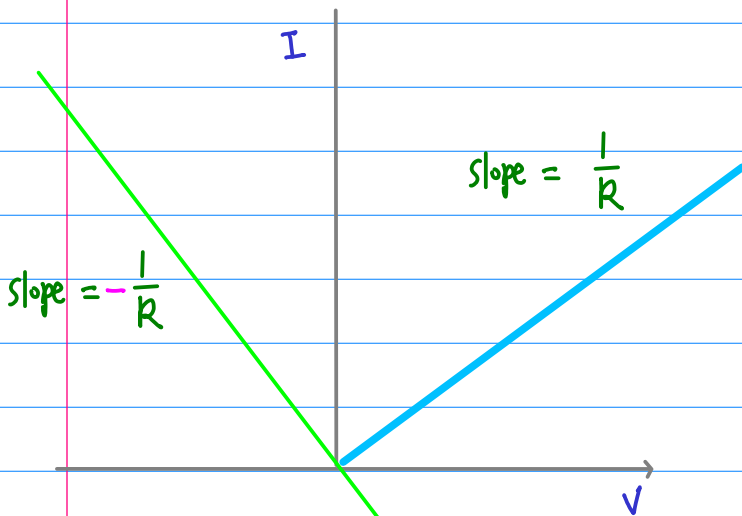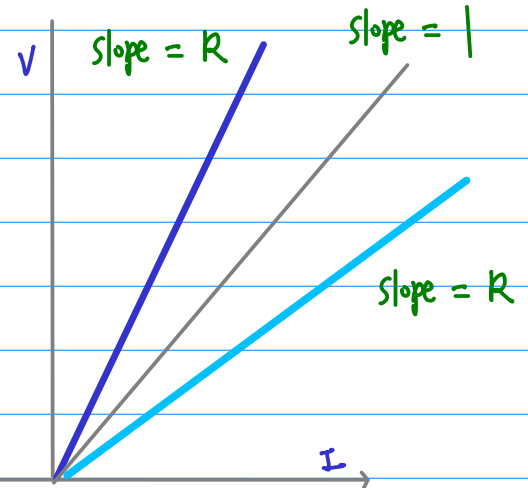

* Change axis $I \leftrightarrow V$

$$V = RI \rightarrow I = \frac{1}{R} V$$

* reflect along V-axis

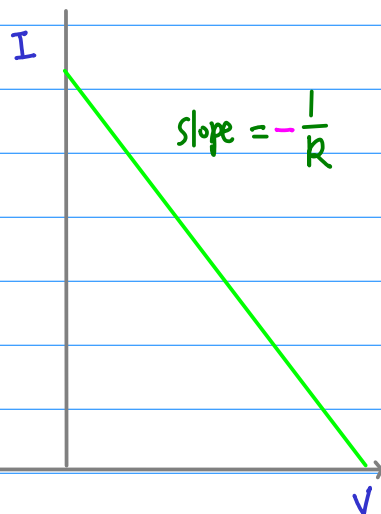


* shift to the right by V_{cc}

$$I = -\frac{1}{R} (V - V_{cc})$$

$$IR = -V + V_{cc}$$


$$V = V_{cc} - IR$$

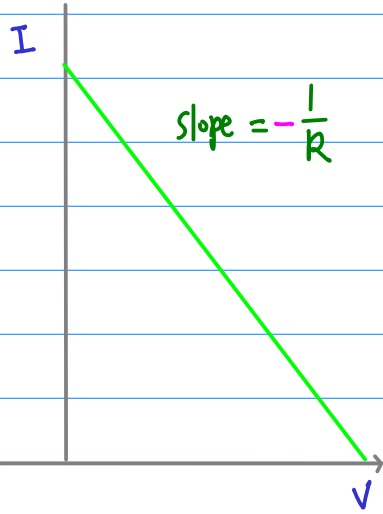


$$I = -\frac{1}{R} (V - V_{cc})$$


$$IR = -V + V_{cc}$$

$$V = V_{cc} - IR$$

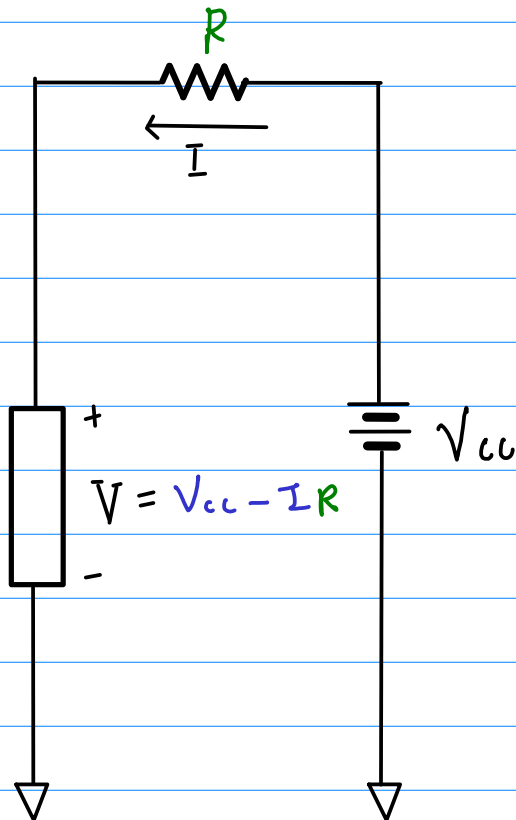

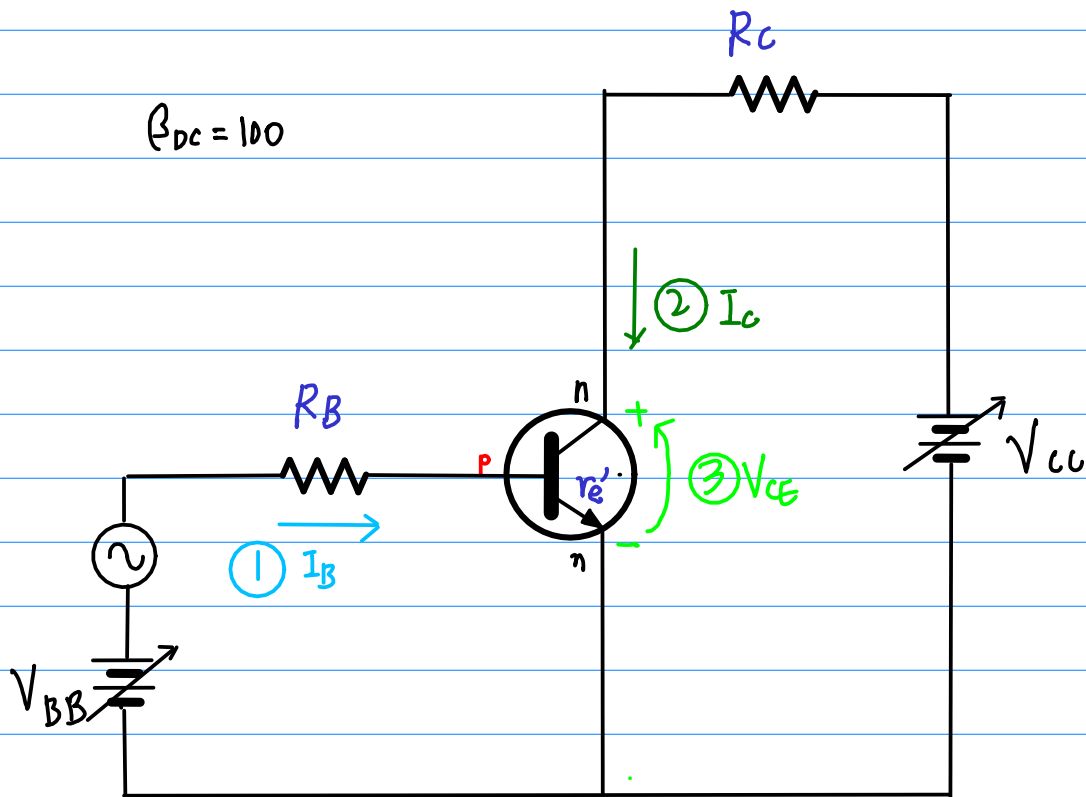
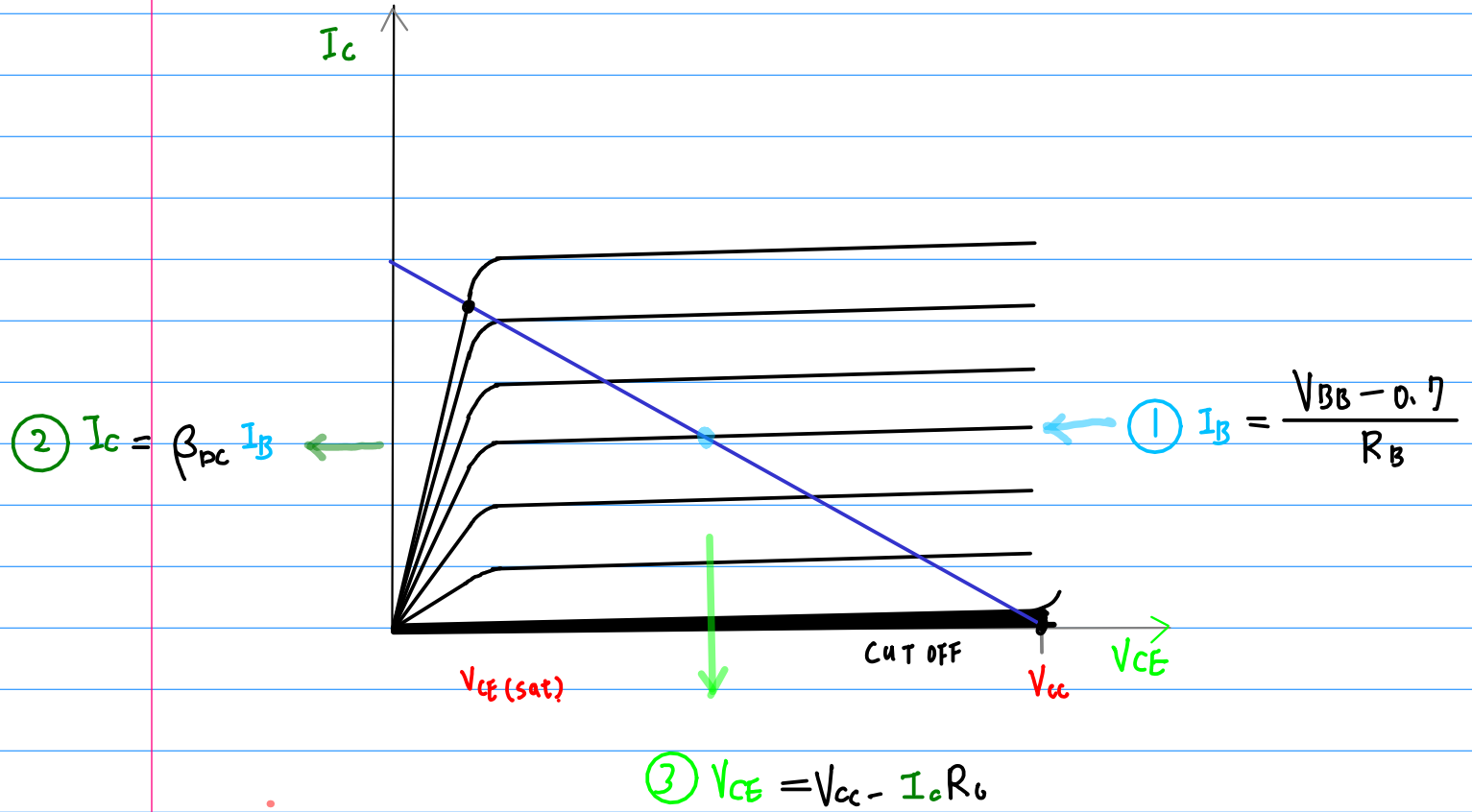
$$\textcircled{1} I_B = \frac{V_{BB} - 0.7}{R_B} \rightarrow \textcircled{2} I_C = \beta_{DC} I_B \rightarrow \textcircled{3} V_{CE} = V_{CC} - I_C R_C$$



① $I_B = \frac{V_{BB} - 0.7}{R_B}$ \rightarrow ② $I_c = \beta_{DC} I_B$ \rightarrow ③ $V_{ce} = V_{cc} - I_c R_o$

③ $V_{ce} = V_{cc} - I_c R_o$

$I_c = \frac{1}{R_o} \cdot (V_{ce} - V_{cc})$
 \downarrow y \uparrow x

