

# BJT Amplifier Overview (H.9)

20170512

Copyright (c) 2016 - 2017 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".


# References

Based

[1] Floyd, Electronic Devices 7th ed

[2] Cook,

[2] en.wikipedia.org

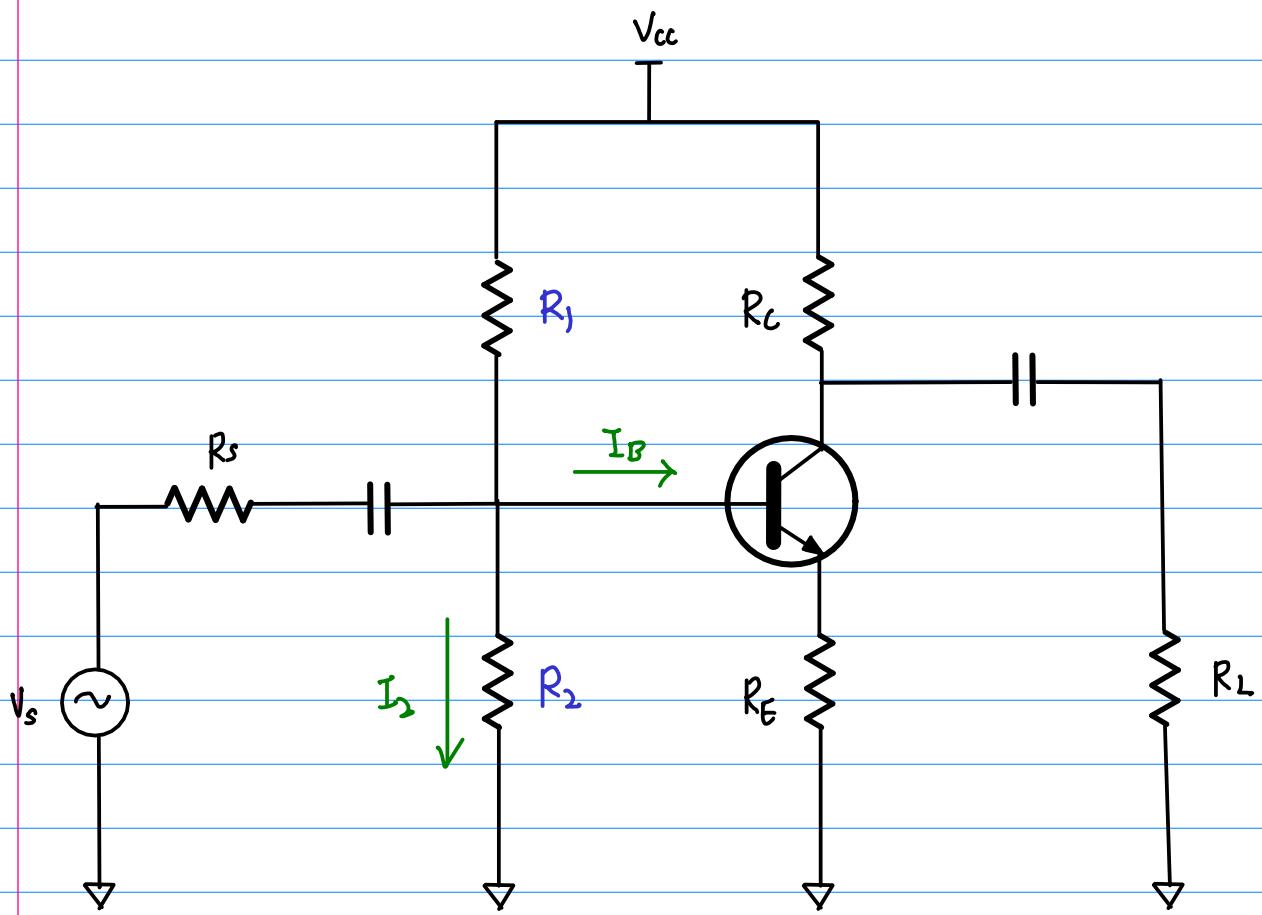

$I_c$  $I_c$  $I_E$  $I_e$  $I_B$  $I_b$  $V_{CE}$  $V_{ce}$ 

.

 $I_c$  $I_E$  $I_B$  $V_{CE}$ 

DC quantities

 $I_c$  $I_e$  $I_b$  $V_{ce}$ 


ac quantities (rms, peak, peak-to-peak)

 $i_c$  $i_e$  $i_b$  $v_{ce}$ 

instantaneous quantities

$$\left( \frac{1}{\beta_{DC}} + R_C \right) I_C = V_{CC} - V_{BE}$$
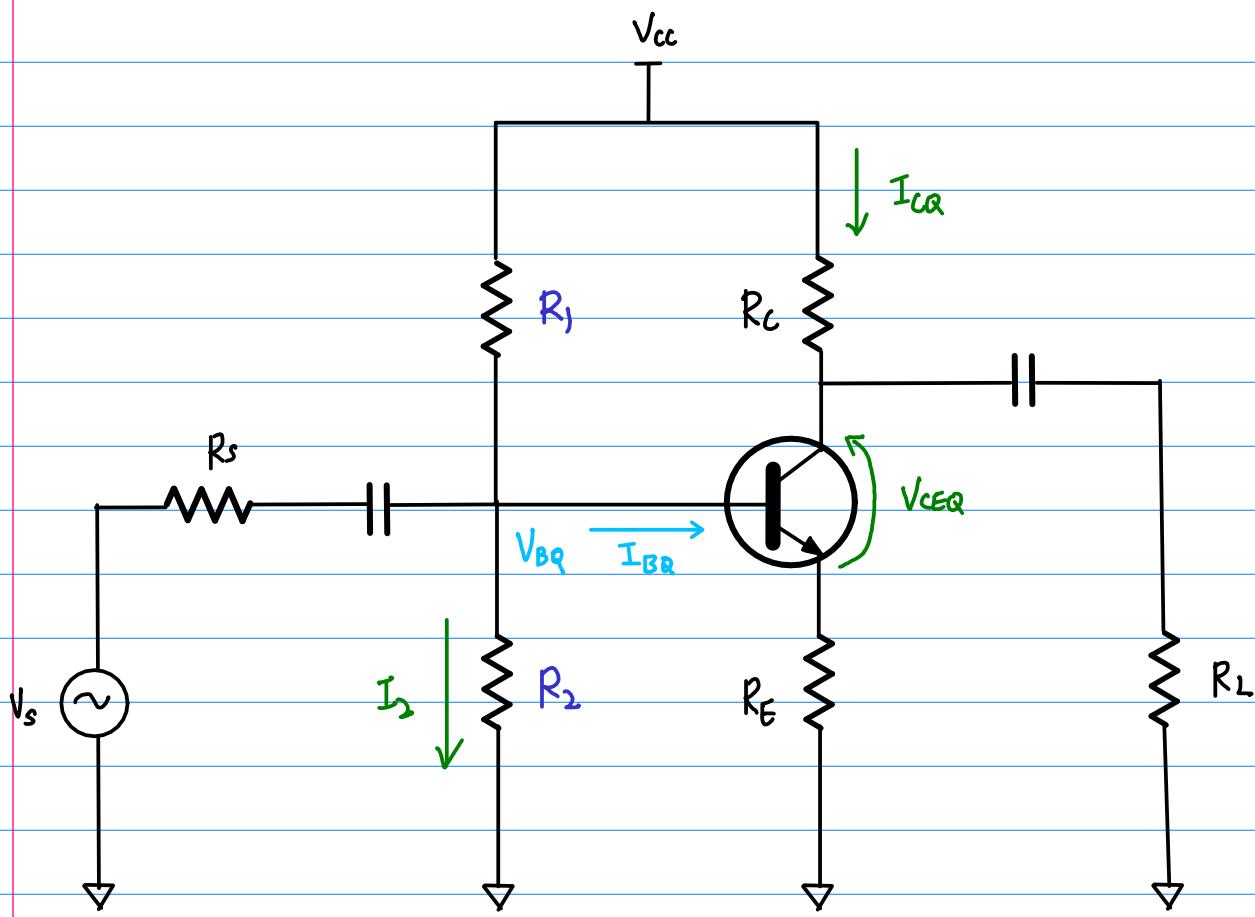
$$I_C = \frac{V_{CC} - V_{BE}}{R_C + R_B / \beta_{DC}}$$





$$V_{bQ} + V_b$$

$$I_B + I_b$$

$$V_{CEQ} + V_{ce}$$

$$I_{cQ} + I_c$$

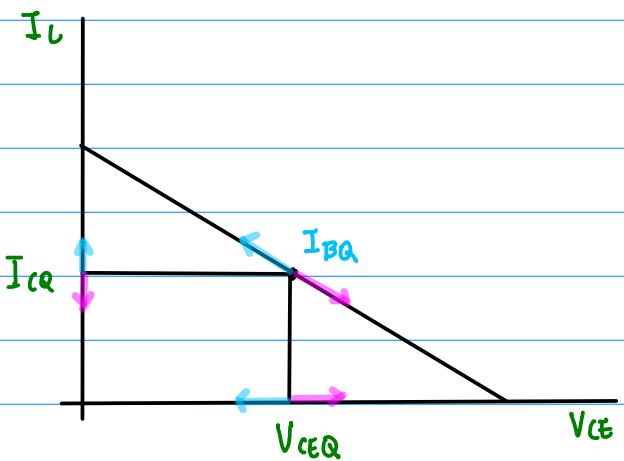
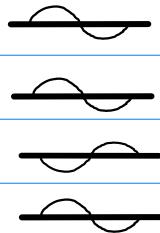





$$V_{BQ} \text{ ---} + V_b \text{ } \sim = V_{BQ} + V_b$$

$$I_B \text{ ---} + I_b \text{ } \sim = I_B + I_b$$


$$V_{CEQ} \text{ ---} + V_{ce} \text{ } \sim = V_{CEQ} + V_{ce}$$
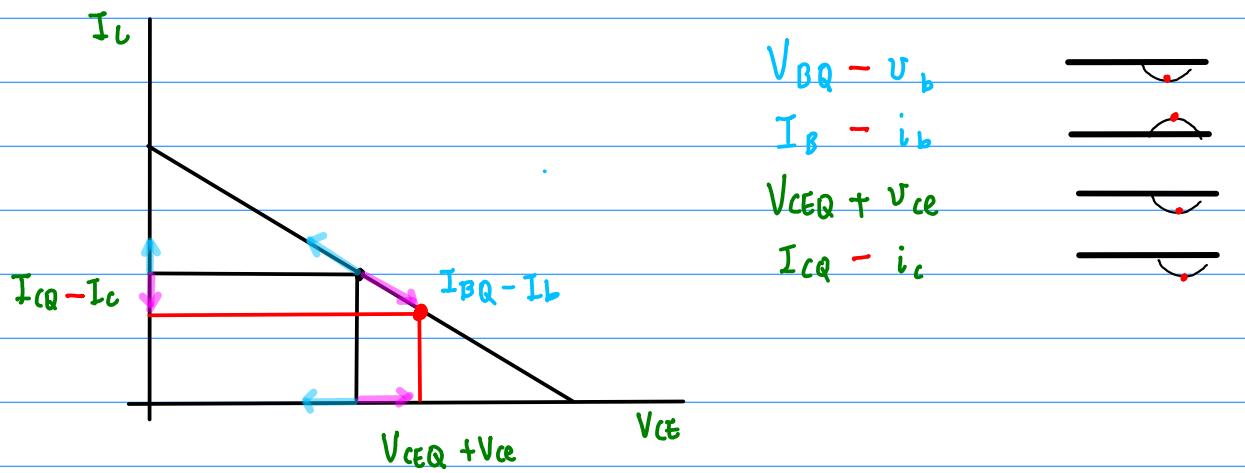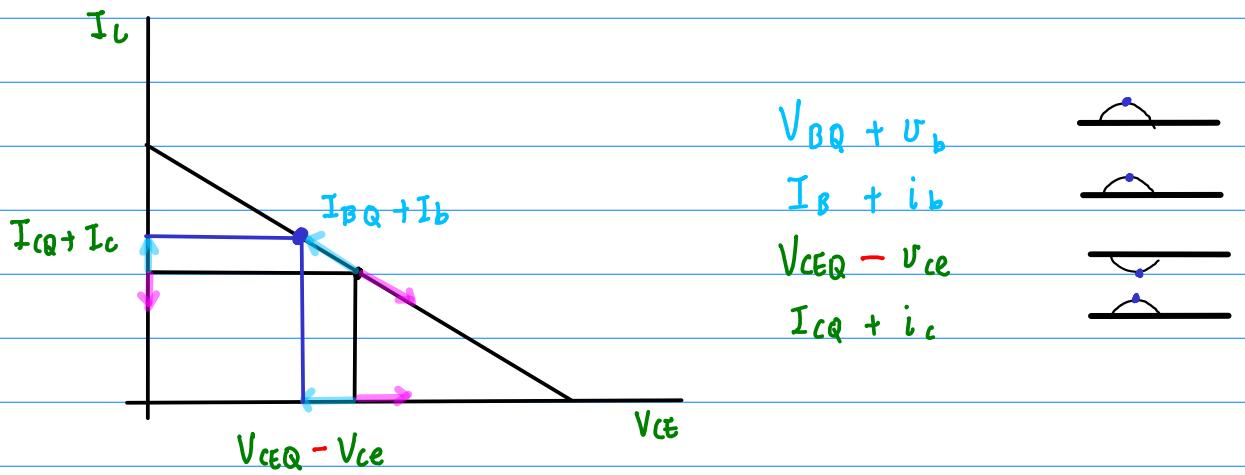
$$I_{CQ} \text{ ---} + I_c \text{ } \sim = I_{CQ} + I_c$$



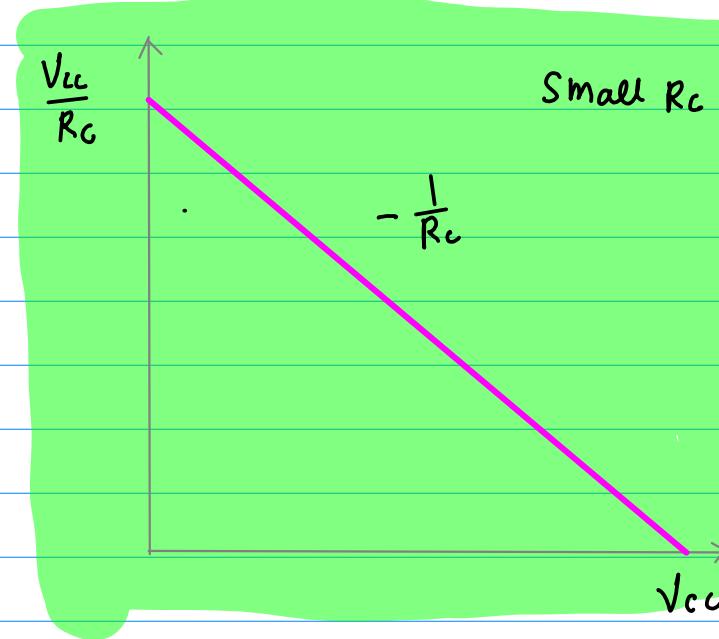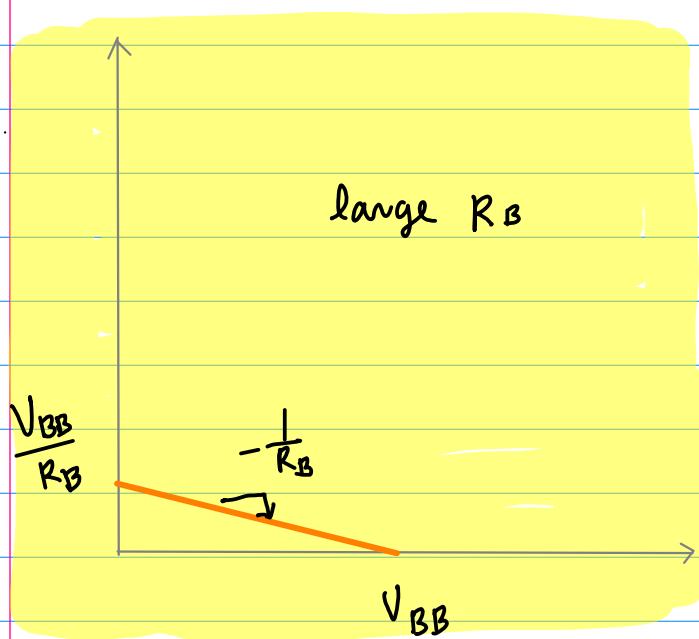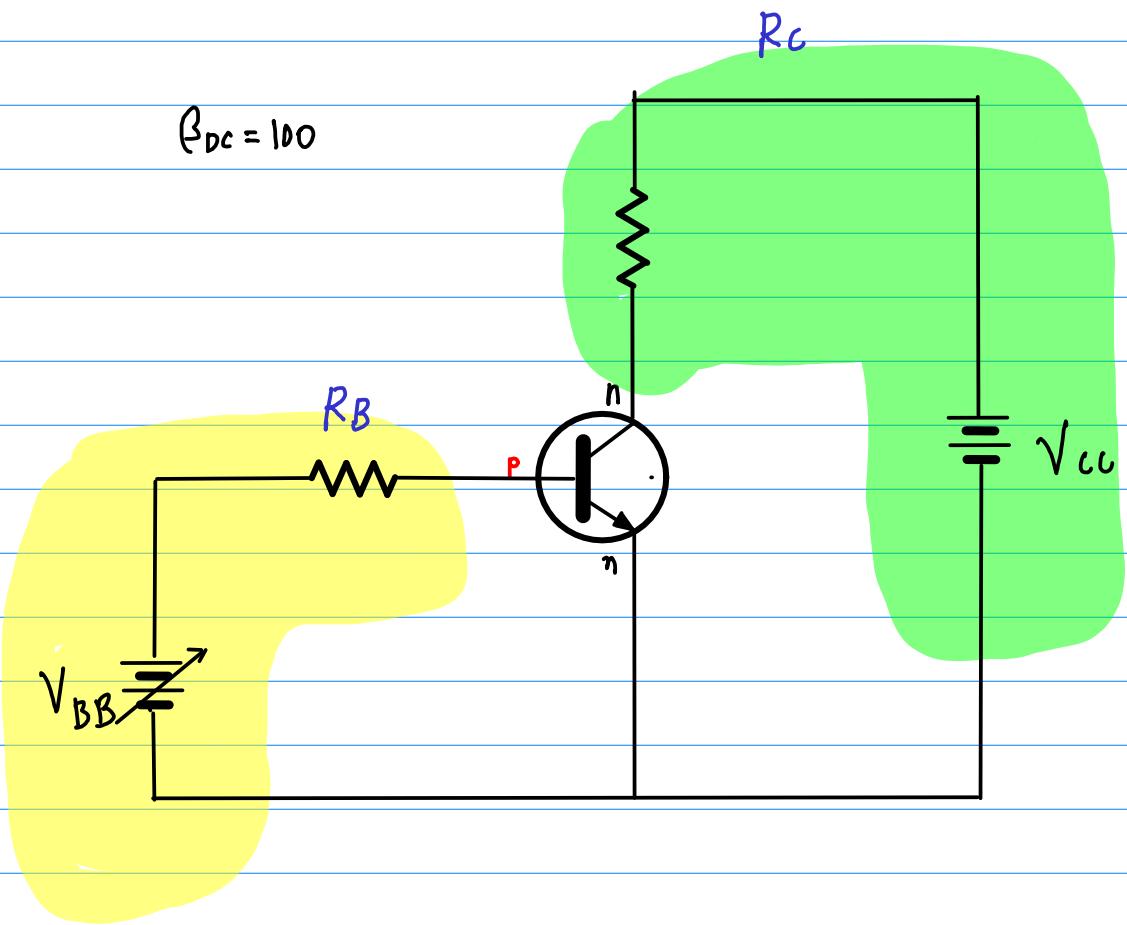$\mu A$

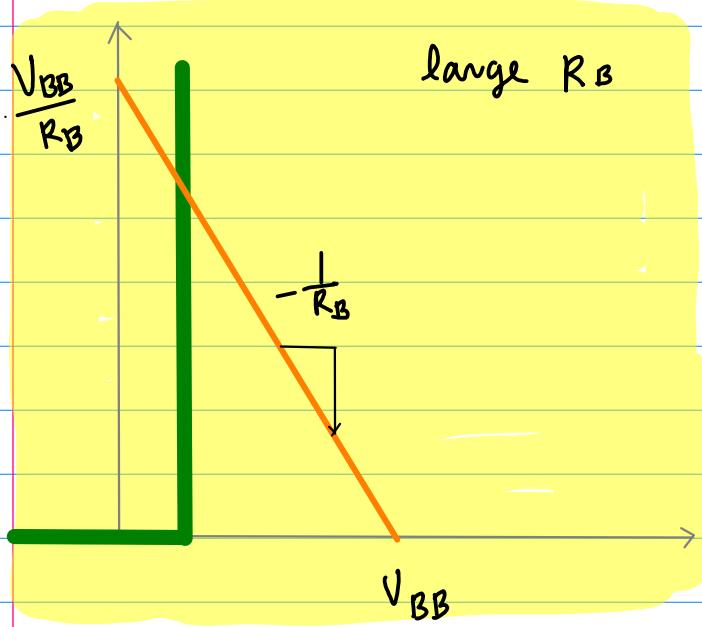

$mA$

