

# BJT Amplifier Equivalent Circuits (H.10)

20170126

Copyright (c) 2016 - 2017 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".

# References

Based

[1] Floyd, Electronic Devices 7th ed

[2] Cook,

[2] en.wikipedia.org



$\alpha_{ac}$  ac alpha ( $I_c / I_e$ )


$\beta_{ac}$  ac beta ( $I_c / I_b$ )

$r'_e$  ac emitter resistance

$r'_b$  ac base resistance

$r'_c$  ac collector resistance

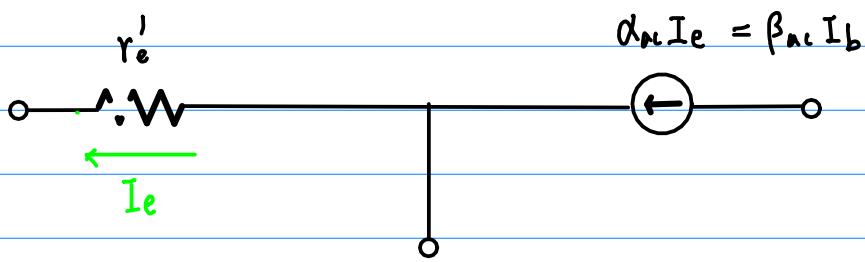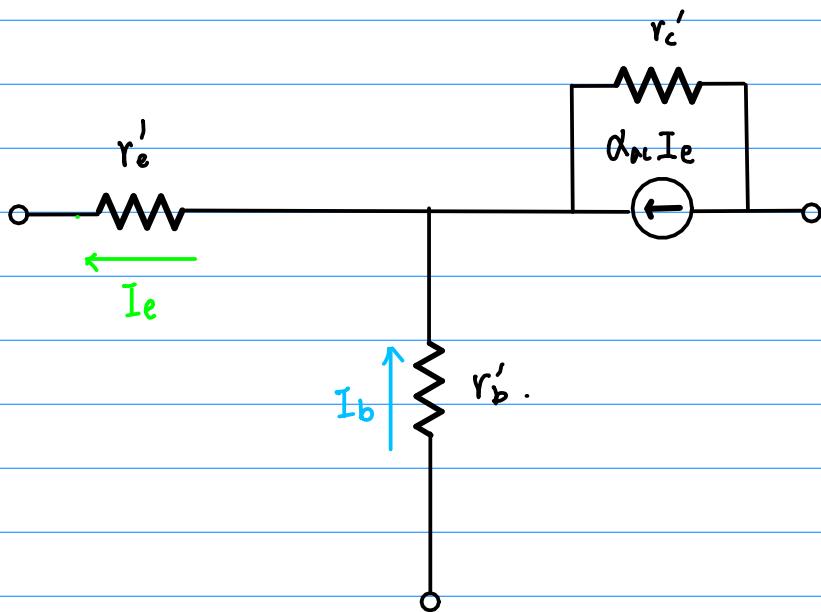

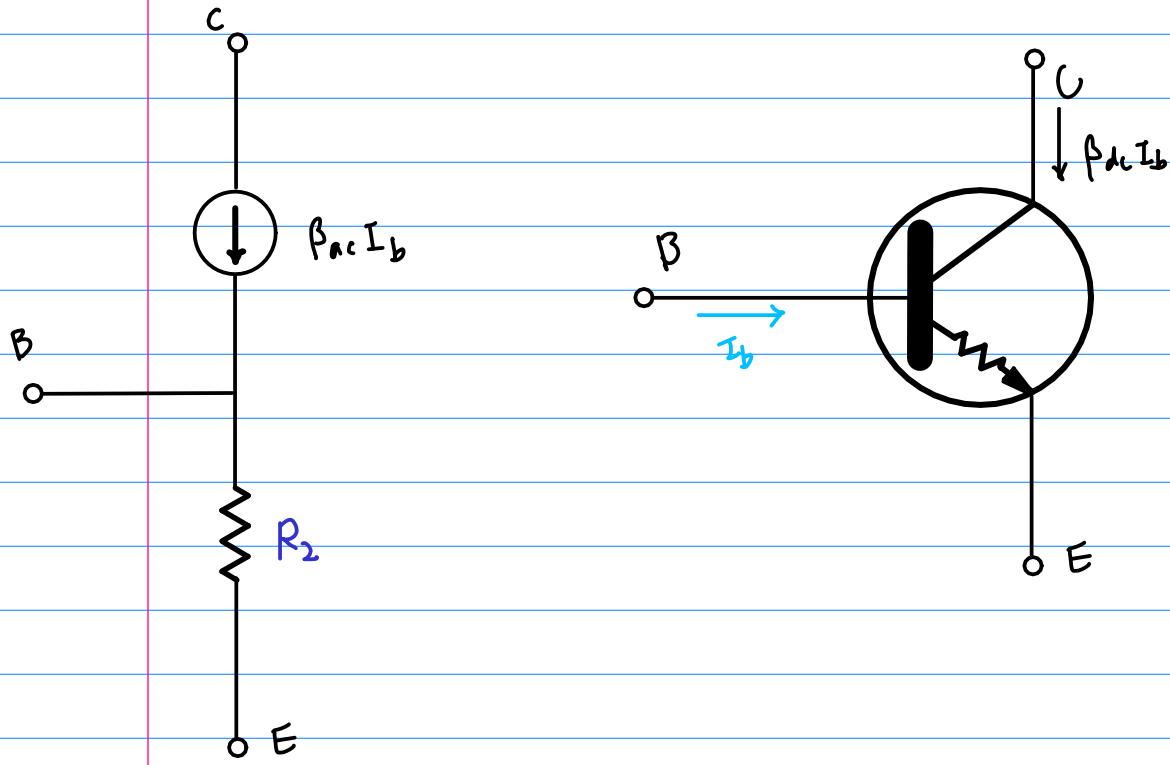

$$\begin{array}{lll}
 I_c & I_c & i_c \\
 I_E & I_e & i_e \\
 I_B & I_b & i_b \\
 V_{CE} & V_{ce} & v_{ce}
 \end{array}$$

$$\left( \frac{1}{\beta_{DC}} + R_C \right) I_C = V_{CC} - V_{BE}$$

$$I_C = \frac{V_{CC} - V_{BE}}{R_C + R_B / \beta_{DC}}$$

