BJT Topologies – Basic Bias

Copyright (c) 2012 – 2017 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".

Please send corrections (or suggestions) to youngwlim@hotmail.com.

This document was produced by using OpenOffice and Octave.

BJT Amplifier Topologies



Common Collector

BJT Topologies – Basic Bias

3

Common Emitter

Common Base Topology



Common Base

4

Current Flow

Common Base

Common Emitter Topology



Common Emitter

Current Flow



Common Emitter

Common Collector Topology



Common Collector

Current Flow



Common Collector

Forward bias (BE) & Reverse bias (CB)



7

BJT Topologies – Basic Bias

Bias for the Active Region



B2B Diodes

Active Region



Biasing B2B Diodes

Active Region



Polarities of Two voltage supplies

Active Region



BJT Topologies – Basic Bias

11

Two voltage supplies Bias

Active Region



BJT Topologies – Basic Bias

12

Controlling $V_{BE} \& V_{CB}$

Active Region

Common Base





Common Emitter

Common Collector



Direct Control



Voltage of **B** from E



Voltage of C from **B**

Indirect Control



Indirect Control



Slope Controlling Resistors

Active Region



BJT Topologies – Basic Bias

Two Voltage Sources

Active Region



Basic Bias

CE & CC Comparison

Active Region



BJT Topologies – Basic Bias

Bias for the Saturation Region



Large I_c & Small V_{CE}

Saturation Region



BJT Topologies – Basic Bias

18

B2B Diodes

Saturation Region



Voltage Supply Polarities

Saturation Region



BJT Topologies – Basic Bias

20

Two Voltage Sources

Saturation Region



CE & CC Comparison

Basic Bias

Saturation Region



07/14/2017

BJT Topologies – Basic Bias

Active and Saturation Regions (1)



BJT Topologies – Basic Bias

Active and Saturation Regions (2)



Basic Bias

25

Active and Saturation Regions (3)



Basic Bias

26

Active and Saturation Regions (4)



Basic Bias

BJT Topologies – Basic Bias



Common Base (1)





Common Base (2)



BJT Topologies – Basic Bias

30

Common Emitter (1)

Electron Flow



Common Emitter

Current Flow



Common Emitter

Common Emitter (2)

Electron Flow



Common Emitter



Current Flow



Common Collector (1)

Electron Flow



Common Collector

Current Flow



Common Collector

Common Collector (2)





Common Collector



Current Flow



BJT Bias



Common Base



Common Emitter



Common Collector







BJT Topologies – Basic Bias

Common Emitter (2)





BJT Topologies – Basic Bias

36

References

- [1] http://en.wikipedia.org/
- [2] J.H. McClellan, et al., Signal Processing First, Pearson Prentice Hall, 2003