

RC Circuit


Copyright (c) 2011 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".

Please send corrections (or suggestions) to youngwlim@hotmail.com.

This document was produced by using OpenOffice and Octave.





Charge

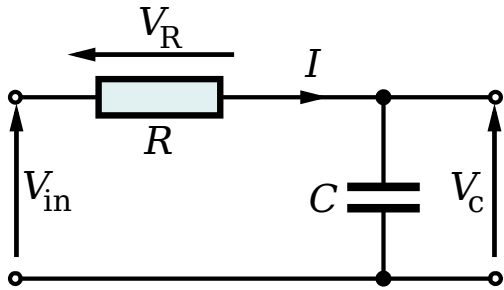


$$i_c = C \cdot \frac{d v_c}{d t}$$

unyielding voltage

current jump

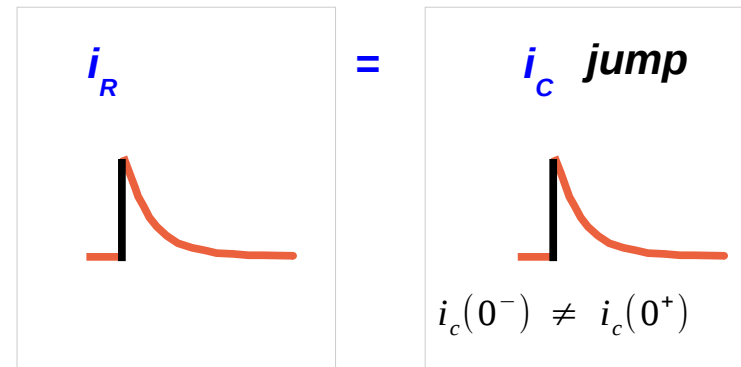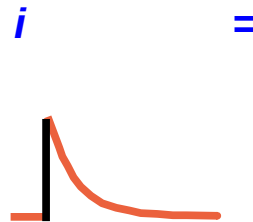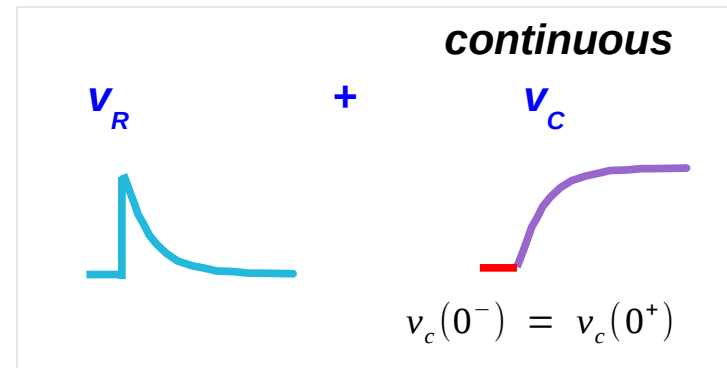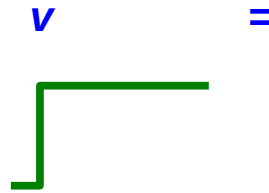





Discharge

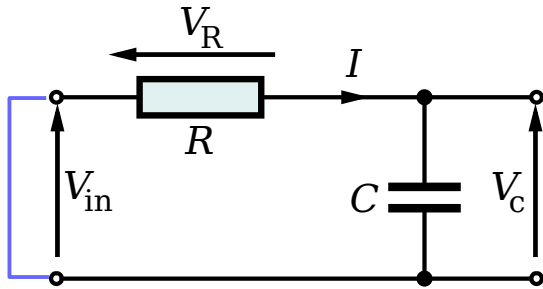


$$i_c = C \cdot \frac{dv_c}{dt}$$

unyielding voltage

current jump

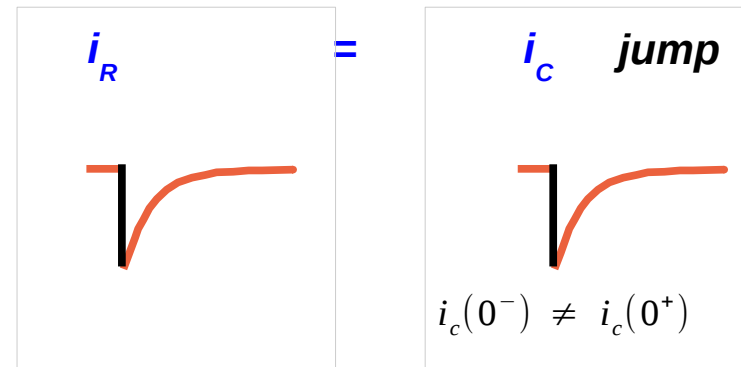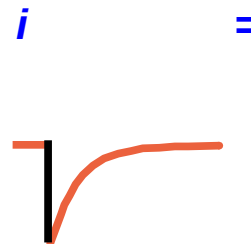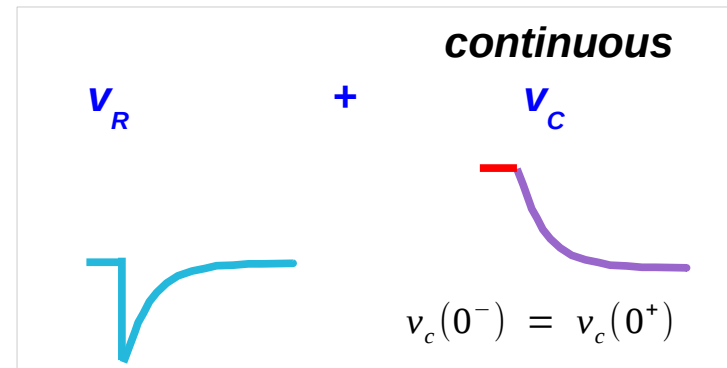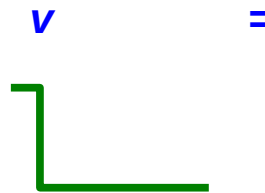

Differential Equation (1)

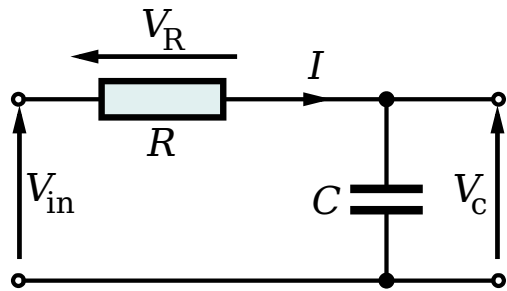

$$RC \cdot \frac{dv_c}{dt} + v_c = V_s \quad t \geq 0^+ \quad v_c(0^+) = v_c(0^-) = V_0$$

$$\frac{dv_c}{dt} + \frac{1}{RC} v_c = \frac{1}{RC} V_s$$

$$\frac{dv_c}{dt} + \frac{1}{RC} v_c = 0$$

$$\frac{dv_c}{dt} = -\frac{1}{RC} v_c$$

$$\frac{dv_c}{v_c} = -\frac{1}{RC} dt$$

$$\ln v_c = -\int \frac{1}{RC} dt + C$$

$$v_c = A e^{-\int \frac{1}{RC} dt}$$

$$v_c = A e^{-\frac{t}{RC}}$$

$$\frac{dv_c}{dt} e^{\frac{t}{RC}} + \frac{1}{RC} v_c e^{\frac{t}{RC}} = \frac{V_s}{RC} e^{\frac{t}{RC}}$$

$$\frac{d}{dt} \left(v_c e^{\frac{t}{RC}} \right) = \frac{V_s}{RC} e^{\frac{t}{RC}}$$


$$\left(v_c e^{\frac{t}{RC}} \right) = c + \int \frac{V_s}{RC} e^{\frac{t}{RC}} dt = c + V_s e^{\frac{t}{RC}}$$

$$v_c(t) = c e^{-\frac{t}{RC}} + V_s$$

$$v_c(0) = c + V_s = V_0$$

$$v_c(t) = (V_0 - V_s) e^{-\frac{t}{RC}} + V_s$$

Differential Equation (2)

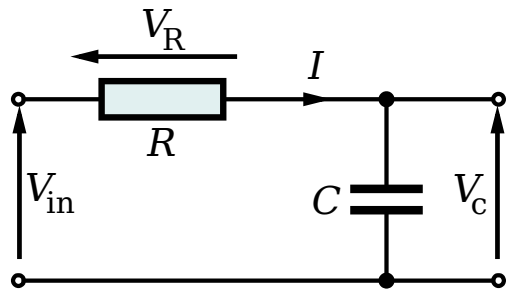

$$RC \cdot \frac{dv_c}{dt} + v_c = V_s \quad t \geq 0^+ \quad v_c(0^+) = v_c(0^-) = V_0$$

$$\frac{dv_c}{dt} + \frac{1}{RC} v_c = \frac{1}{RC} V_s$$

$$\frac{dv_c}{dt} + \frac{1}{RC} v_c = 0$$

assume $v_c = A e^{st}$

$$\frac{d}{dt}(A e^{st}) + \frac{1}{RC} A e^{st} = 0$$

$$\left(s + \frac{1}{RC}\right) A e^{st} = 0$$

$$s = -\frac{1}{RC}$$

$$v_c = A e^{-\frac{t}{RC}}$$

homogeneous solution

$$\frac{dv_c}{dt} + \frac{1}{RC} v_c = \frac{V_s}{RC}$$

assume $v_c = c$

$$\frac{d}{dt}(c) + \frac{1}{RC} c = \frac{V_s}{RC}$$

$$v_c = V_s$$

particular solution


$$v_c(t) = V_s + A e^{-\frac{t}{RC}}$$

$$v_c(0) = A + V_s = V_0$$

$$v_c(t) = (V_0 - V_s) e^{-\frac{t}{RC}} + V_s$$

complete solution

Differential Equation (3)

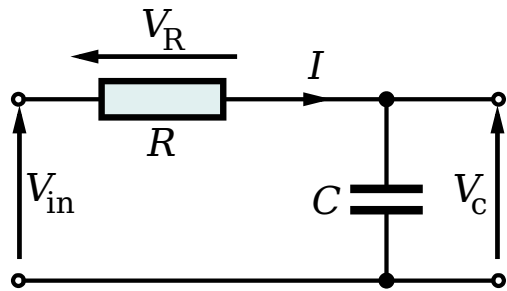

$$Ri + \frac{1}{C} \int_{-\infty}^t i d\tau = V_s \quad t \geq 0^+ \quad v_c(0^+) = v_c(0^-) = V_0$$

$$i = C \frac{dv_c}{dt} \quad RC \cdot \frac{dv_c}{dt} + v_c = V_s$$

$$(RC D + 1)v_c = V_s \quad (RC\lambda + 1) = 0 \quad \lambda = -\frac{1}{RC} \quad v_{c0} = A e^{-\frac{t}{RC}}$$

$$v_{c0}(0) = A = V_0 \quad v_{c0} = V_0 e^{-\frac{t}{RC}} \quad \text{zero-input response}$$

$$RC \cdot \dot{h}(t) + h(t) = \delta(t)$$

assume $v_c = c$


$$\frac{d}{dt}(c) + \frac{1}{RC}c = \frac{V_s}{RC} \quad v_c = V_s$$

particular solution

$$v_c(t) = V_s + A e^{-\frac{t}{RC}} \quad v_c(t) = (V_0 - V_s) e^{-\frac{t}{RC}} + V_s$$



complete solution

Pulse

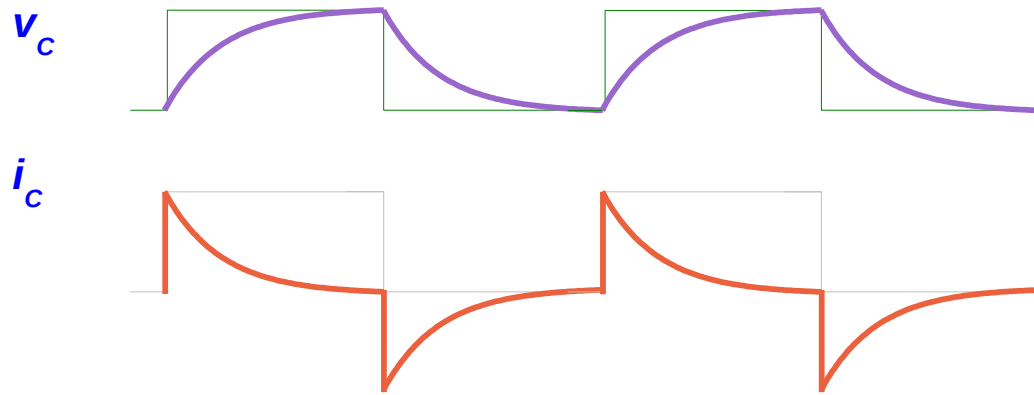

$$i_c = C \frac{dv_c}{dt}$$

ω ↑ i_c ↑ X_c ↓

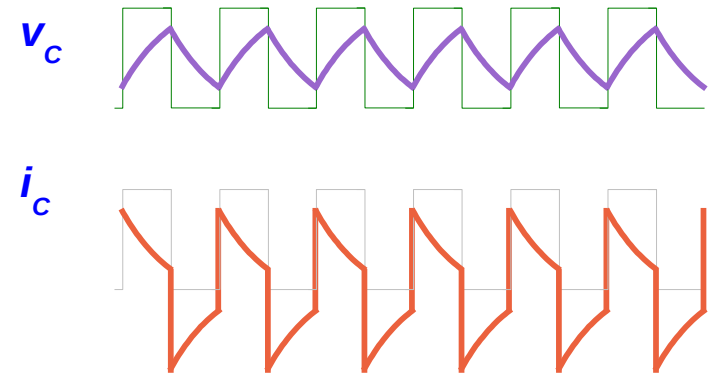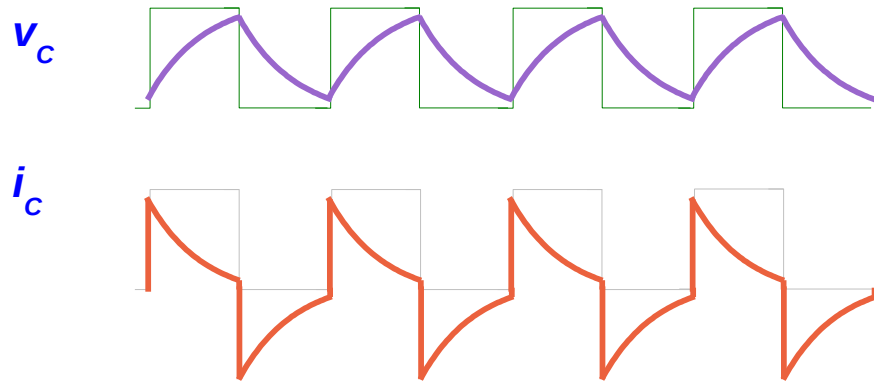

Phase Lags and Leads

References

[1] <http://en.wikipedia.org/>

[2] J.H. McClellan, et al., Signal Processing First, Pearson Prentice Hall, 2003