BJT Amplifier Configurations

Young Won Lim 05/23/2017 Copyright (c) 2012 - 2017 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".

Please send corrections (or suggestions) to youngwlim@hotmail.com.

This document was produced by using OpenOffice and Octave.

Young Won Lim 05/23/2017

BJT Amplifier Configurations



BJT Bias

BJT Configuration Properties



BJT Configuration Properties





Common Base



Common Emitter

6



Common Collector

RF Applications

Widely used

Emitter Follower Buffer to Low Impedance Load

BJT Bias

DC Bias + AC Small Signal



7

AC Equivalent Circuits



Common Base



Common Emitter



Common Collector

Voltage Gain



Common Base





9



Common Collector

BJT Bias

Storing Magnetic Energy V_+



References

- [1] http://en.wikipedia.org/
- [2] J.H. McClellan, et al., Signal Processing First, Pearson Prentice Hall, 2003