

BJT Amplifier Power Amp Overview(H.21)

20170616-2

Copyright (c) 2016 - 2017 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".


References

Based

[1] Floyd, Electronic Devices 7th ed

[2] Cook,

[2] en.wikipedia.org

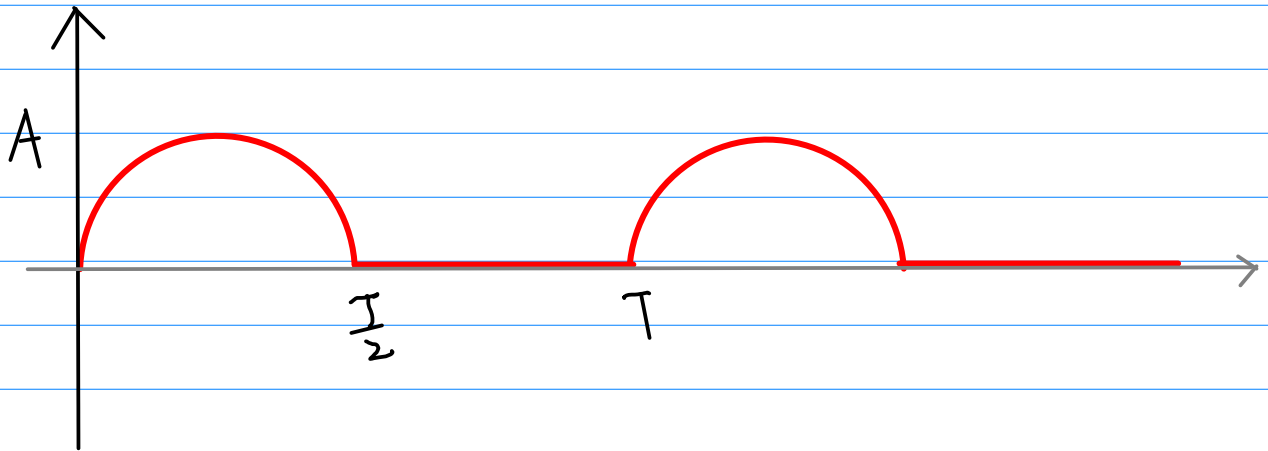

$$\omega_0 = \frac{2\pi}{T}$$

$$f(t) = \frac{A}{\pi} + \frac{A}{2} \sin \omega_0 t - \frac{2A}{\pi} \sum_{n=1}^{\infty} \frac{\cos(2n\omega_0 t)}{4n^2 - 1}$$

<http://www.calpoly.edu/~fowen/me318/FourierSeriesTable.pdf>

$$b_k = \begin{cases} \frac{1}{2} & k=1 \\ 0 & k>1 \end{cases} \quad - \frac{2}{\pi} \sum_{k=\text{even}} \frac{\cos(k\omega_0 t)}{(k^2 - 1)}$$

$$a_k = \begin{cases} \frac{-2}{\pi(k^2 - 1)} & k \text{ even} \\ 0 & k \text{ odd} \end{cases} \quad \frac{2}{\pi} \sum_{n=1}^{\infty} \frac{\cos(2n\omega_0 t)}{(4n^2 - 1)}$$

$k = \text{even}$

$$f(t) = \frac{2}{\pi} + \frac{1}{2} \sin \omega_0 t - \frac{2}{\pi} \sum_{n=1}^{\infty} \frac{\cos(2n\omega_0 t)}{4n^2 - 1} \quad \omega_0 = 2\pi$$

```
(%i1) f1(t) := 1 / %pi;
```

```
(%o1) f1(t) := 1 / pi
```

```
(%i2) w : 2 * %pi;
```


```
(%o2) 2 pi
```


```
(%i3) f2(t) := (1/2) * sin(w*t);
```


```
(%o3) f2(t) := sin(wt) / 2
```

```
(%i5) f3(t, n) := - 2 / (%pi * (4*n^2-1)) * cos(2*n*w*t);
```

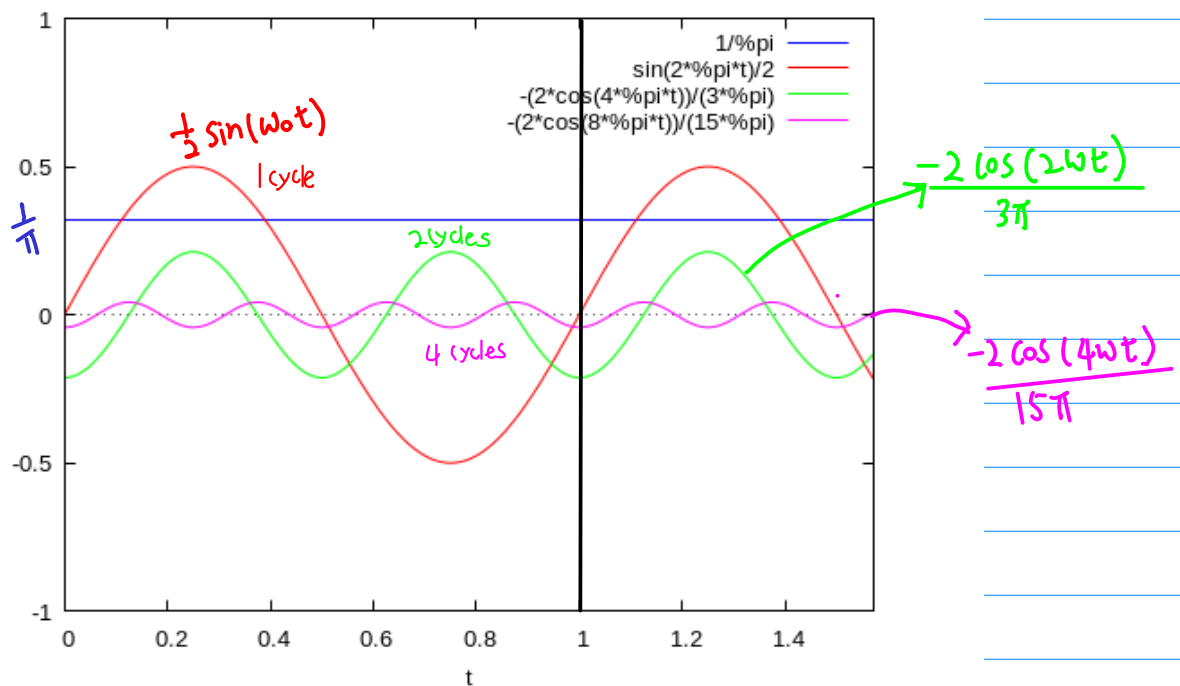
```
(%o5) f3(t, n) := -2 cos(2nw t) / (pi(4n^2-1))
```



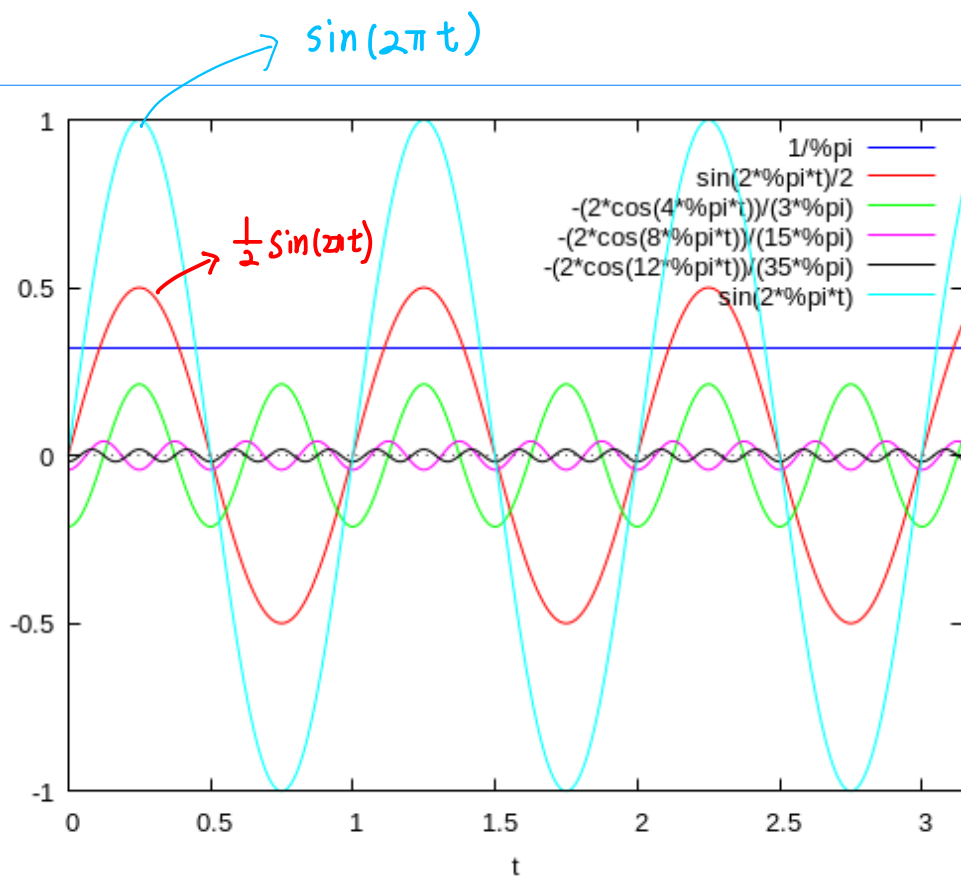

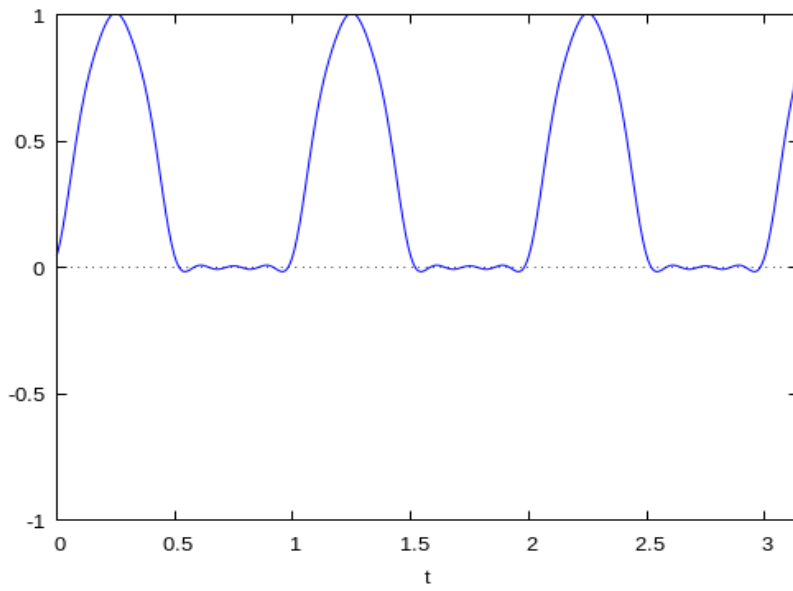

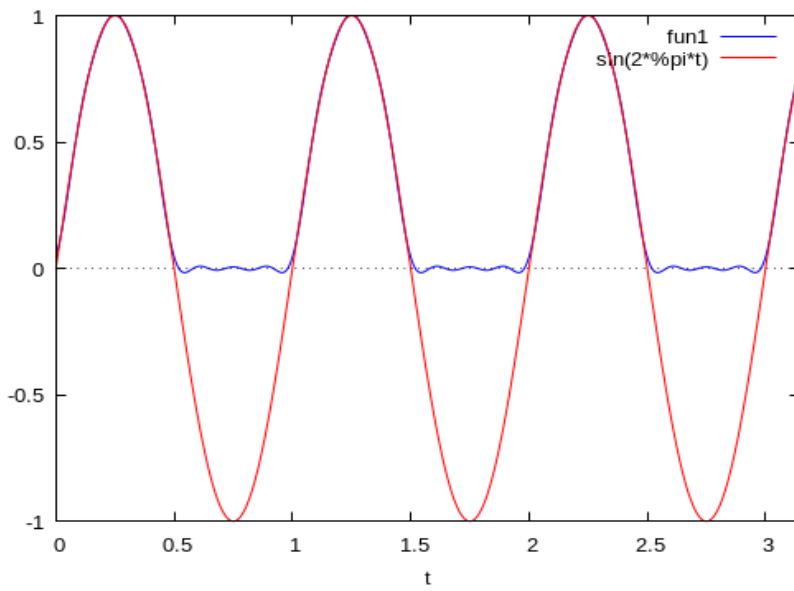$\frac{1}{\pi} + \frac{1}{2} \sin(2\pi t)$ f_0
 $-\frac{1}{3\pi} \cdot 2 \cos(4\pi t)$ $2f_0$
 $-\frac{1}{15\pi} \cdot 2 \cos(8\pi t)$ $4f_0$
 $-\frac{1}{35\pi} \cdot 2 \cos(12\pi t)$ $6f_0$



$$\begin{aligned}
 a_0 &= \frac{1}{T} \int_0^{T/2} \sin\left(\frac{2\pi t}{T}\right) dt \\
 &= \frac{1}{T} \frac{T}{2\pi} \left[-\cos\left(\frac{2\pi t}{T}\right) \right]_0^{T/2} \\
 &= \frac{1}{\pi}
 \end{aligned}$$



$$\begin{aligned}
 b_k &= \frac{2}{T} \int_0^{T/2} \sin\left(\frac{2\pi t}{T}\right) \sin\left(\frac{2\pi k t}{T}\right) dt \\
 &= \frac{1}{T} \int_0^{T/2} \left(\cos\left(\frac{2\pi(k-1)t}{T}\right) - \cos\left(\frac{2\pi(k+1)t}{T}\right) \right) dt
 \end{aligned}$$

$$k=1 \quad \frac{1}{T} \int_0^{T/2} \left(1 - \cos\left(\frac{2\pi t}{T}\right) \right) dt = \frac{1}{2}$$


$$k=2 \quad \frac{1}{T} \int_0^{T/2} \left(\cos\left(\frac{2\pi t}{T}\right) - \cos\left(\frac{2\pi \cdot 3t}{T}\right) \right) dt = 0$$

$$b_k = \begin{cases} \frac{1}{2} & k=1 \\ 0 & k > 1 \end{cases}$$

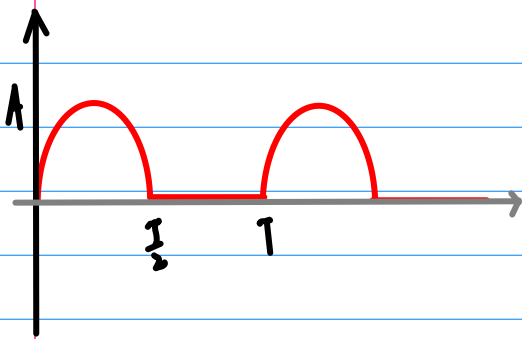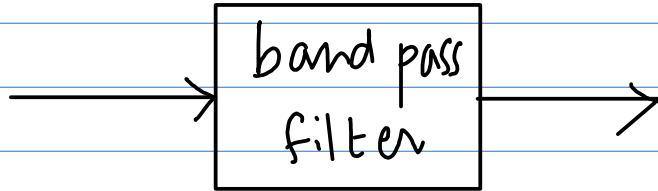
$$a_k = \begin{cases} \frac{-2}{\pi(k^2-1)} & k \text{ even} \\ 0 & k \text{ odd} \end{cases}$$




$$\omega_0 = 2\pi f_0$$

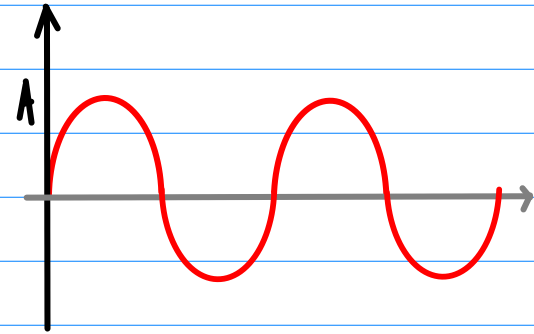


$$\omega_0 = 2\pi f_0$$

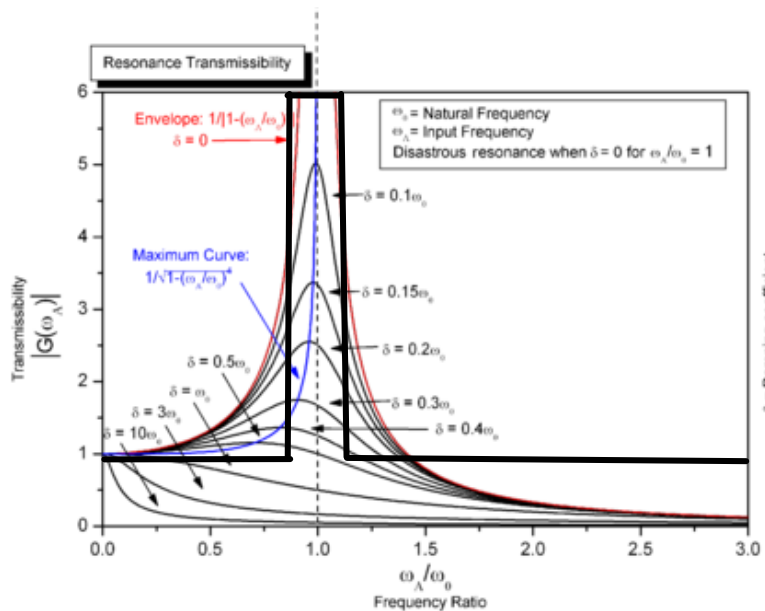
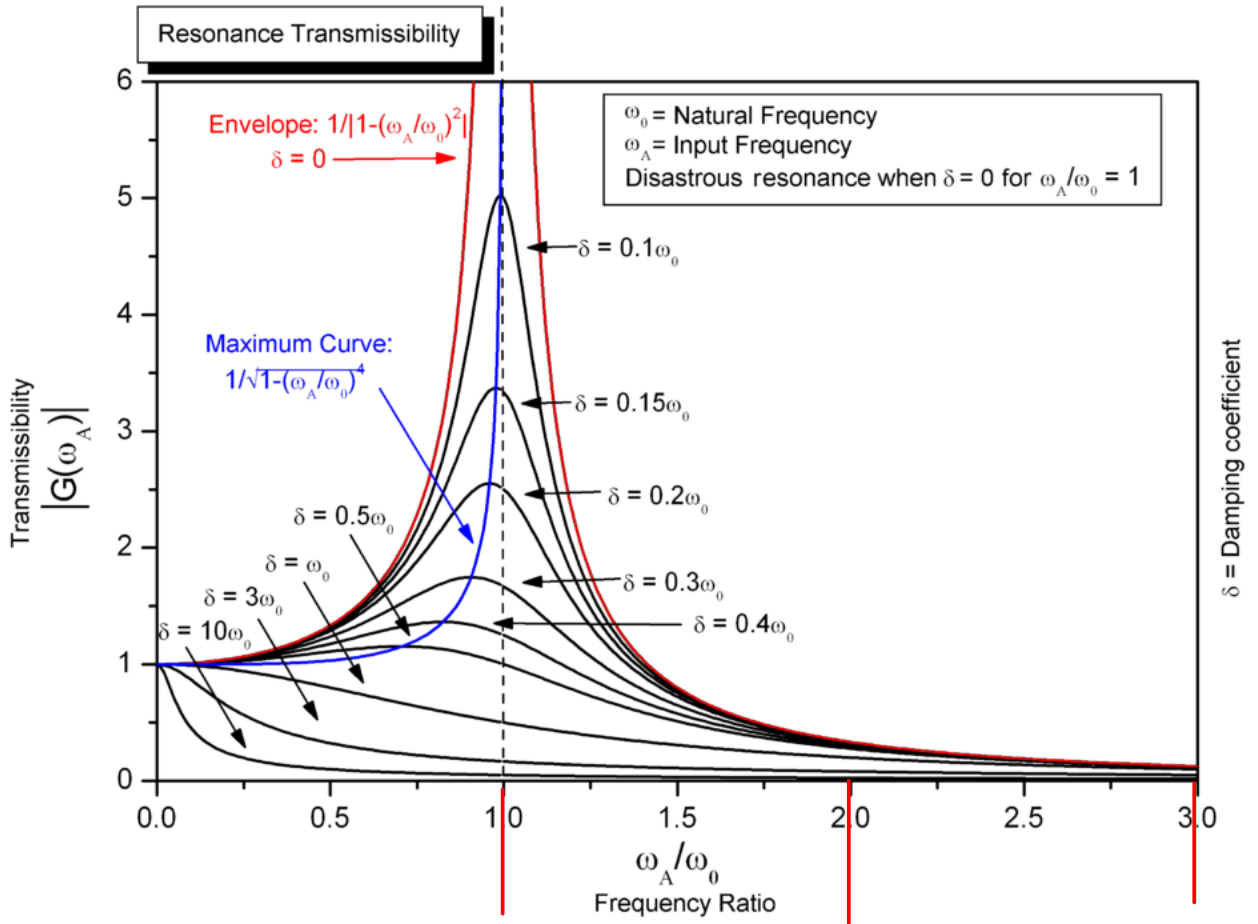
<https://en.wikipedia.org/wiki/Resonance>








harmonics are suppressed

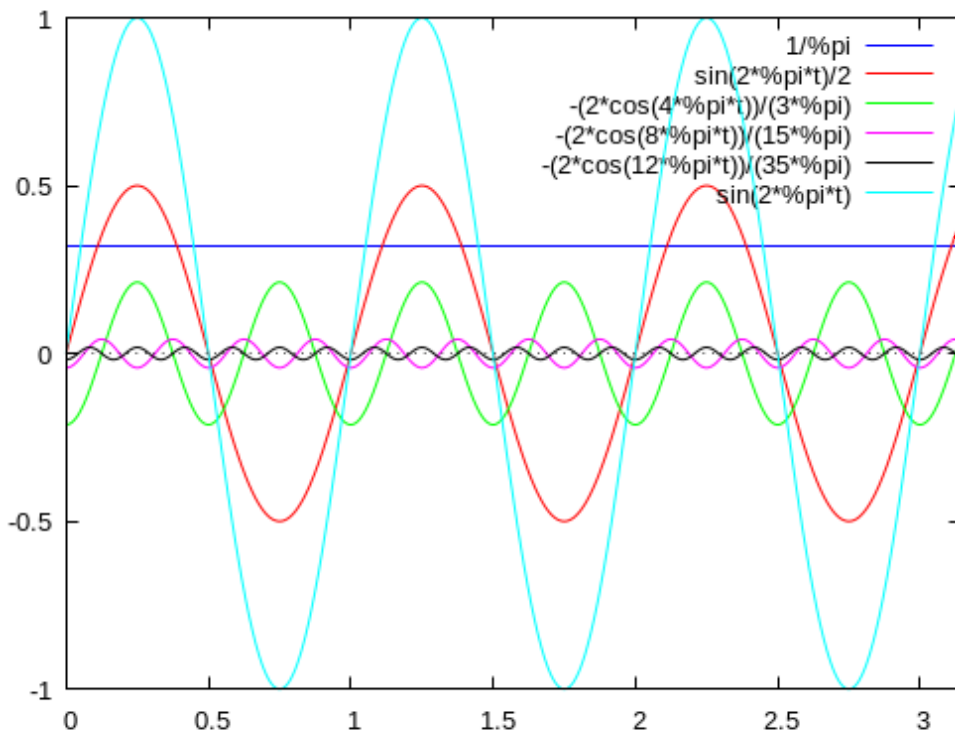

only this one

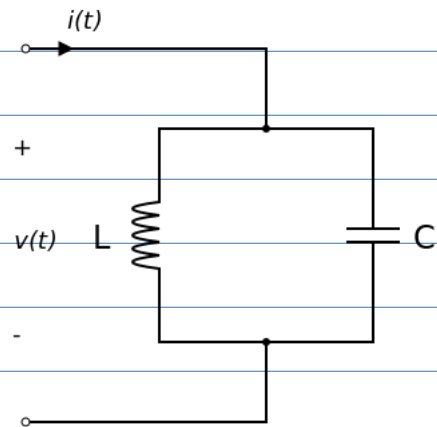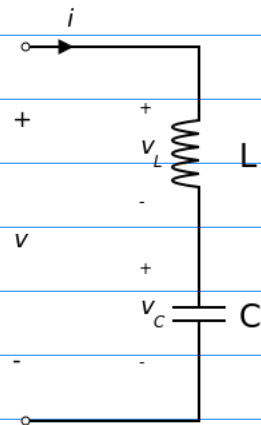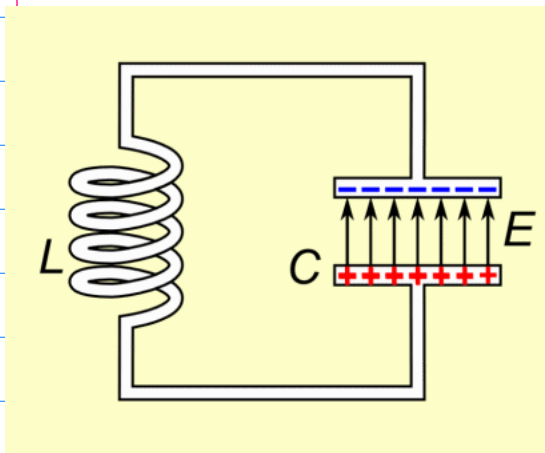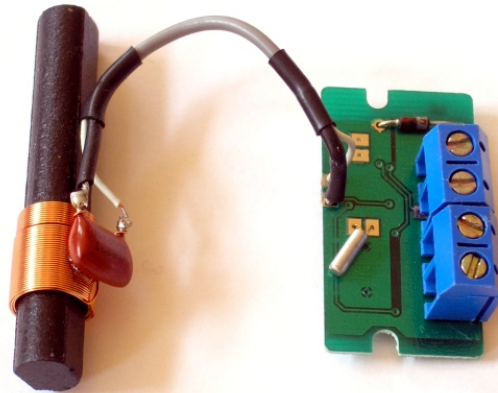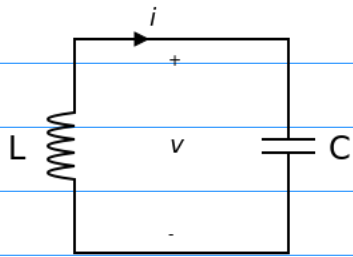https://en.wikipedia.org/wiki/LC_circuit#/media/File:Low_cost_DCF77_receiver.jpg



voltage amplifier : increase the amplitude of a signal

gain 100 150 mV --> 15 V

possible across $R_L = 1\text{K}\Omega$

not possible across $R_L = 10\ \Omega$

cannot provide excess current

current amplifier : increase the current of a signal

gain 100 10 μA --> 1 mA

possible at low output voltage 100 mV

not possible at high output voltage 10 V

these voltage & current amplifier

not have sufficient POWER ($V * I$)

small transistors

very tiny junction areas

cannot draw large amounts of power

without overheating

Power Transistors

can handle more than 1 A of collector current

larger current

higher voltage

low output resistance --> large current

good junction insulation --> high voltage

large collector/base junction --> quick heat dissipation

Power Amplifier Classes


Class A, B, AB, C, D, E, F, G, H

Class A, B, AB, C
the way the amplifier are biased
the Q point position


Class C - oscillator circuits

Class D ~ H - switch mode, rapid switch, low power

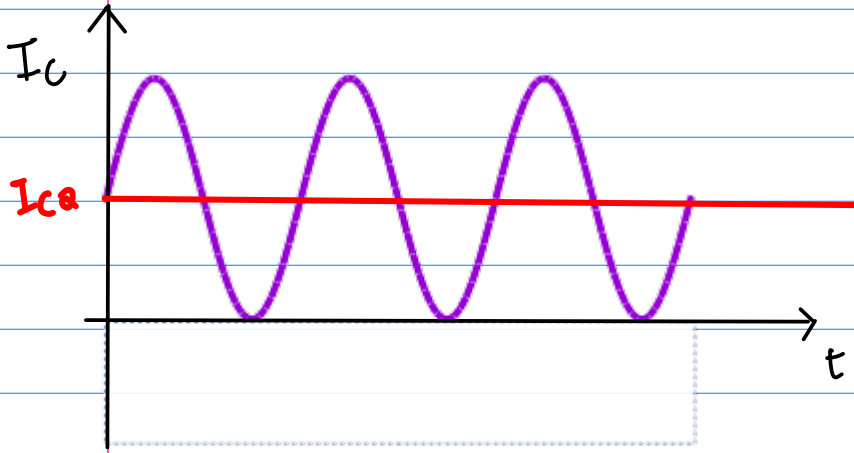
<http://learnabout-electronics.org/Amplifiers/amplifiers50.php>




Class A

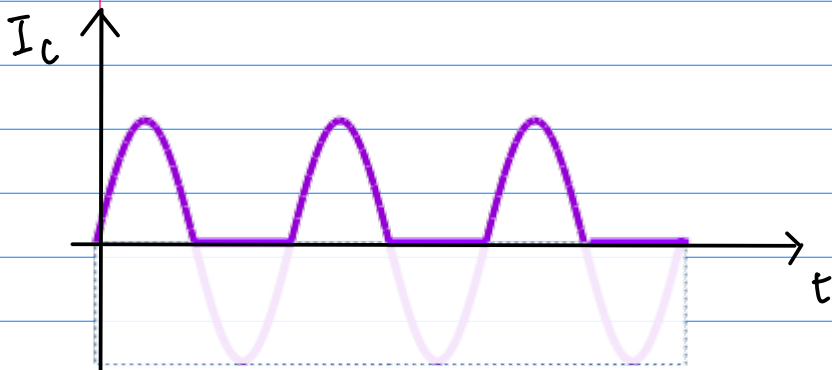

Class B

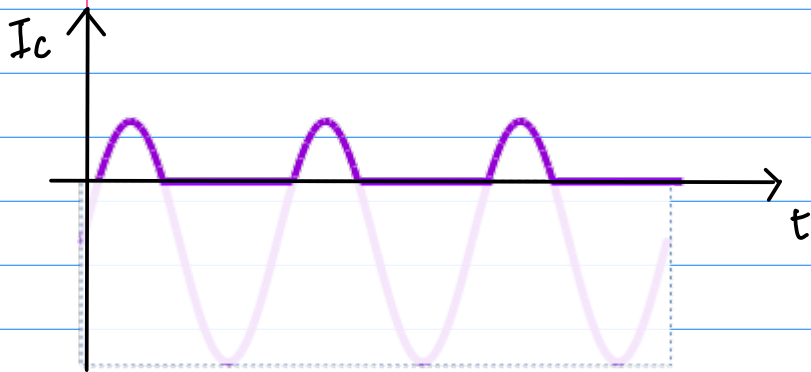

Class C

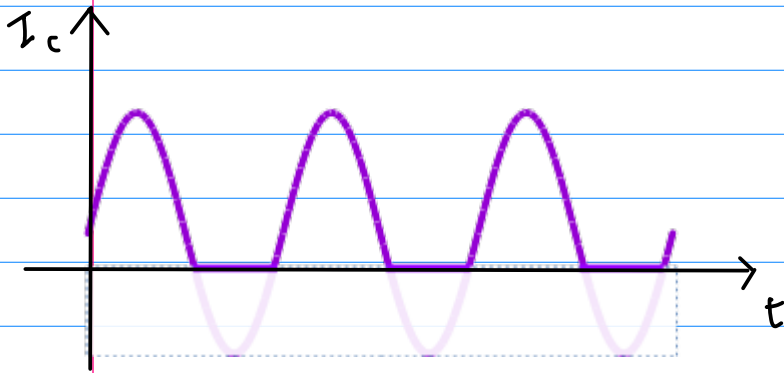

Class AB

Class A

common emitter amplifier

many applications

free from distortion

poor efficiency

outside the region between 0 ~ 0.6V

non-linear input characteristic region

produce the output power 50% theoretically

25~30% practically

compared with the DC power consumption

standing bias current

during the whole waveform cycle

even when no input signal is present

standing bias current (quiescent current)

is sufficient to make the collector voltage fall

to half the supply voltage

power $P = I_c * V_{cc}/2$ is being dissipated

whether any signal is present or not

with substantially less than 50%

of the power consumed from the supply

going into the signal power supplied to the loudspeaker

the wasted power is simply produced as heat,

main in the output transistors

not practical

for example,

an amplifier used to produce 200W to a large loudspeaker

would need a 400W amplifier producing at its most efficient

200W of the wasted heat that must be dissipated

by very large transistors and even larger heat-sinks

if overheating is to be avoided

Class B

no standing bias current
the quiescent current is zero
transistor conducts for only half of each cycle

increases efficiency compared with class A
theoretically 80%
practically 50~60%

a good power gain
as much of the energy consumed from the power supply
going into the load as possible

reasonable linearity (lack of distortion) as possible

RF power amplifiers using class B

* a tuned circuit
resonating at the signal frequency
the resonating effect fills in the missing half cycles
only suitable at RF (relatively high frequency)
for low frequency application,
L and C must be made bulky (costly)

* a push-pull circuit
filling the missing half cycle
2 identical but anti phase signals from a phase splitter
are fed to the bases of a pair of power transistor
each transistor conducts only for either positive or negative
half cycle.
the two half cycles are re-combined to produce
a complete sine wave.

- + very low standing bias current
- + negligible power consumption without signal
- + can be used for much more powerful outputs than class A
- + more efficient than class A

- creates crossover distortion
- supply current changes with signal, stabilized supply may be needed
- more distortion than class A

<http://learnabout-electronics.org/Amplifiers/amplifiers50.php>

Class AB Power Amplifiers

less efficient than class B
small quiescent current flowing
just above cut off
minimize crossover distortion

as each cycle of the waveform crosses zero volts,
both transistors are conducting momentarily
and the bias in the characteristic of each one cancels out

a complementary matched pair of transistors
in emitter follower mode, gives cheaper construction
no phase splitter is needed

opposite npn and pnp pair

each transistor will conduct on opposite half cycles
the low output impedance of the emitter follower
eliminates the need for an impedance matching
output transformer

matching of current gain and temperature characteristics of
complementary (nnp/pnp) transistors is more difficult
than with just the single transistor type in class B operation

<http://learnabout-electronics.org/Amplifiers/amplifiers50.php>

Class C Bias

the bias point is placed well below cut-off
the transistor is cut-off for most of the cycle




much improved efficiency to the amplifier
very heavy distortion

not suitable for audio amplifiers

commonly used in high frequency sine wave oscillators
and certain types of RF amplifiers
where the pulses of current produced at the amplifier output
can be converted to complete sine waves of a particular
frequency by the use of LCR resonant circuits
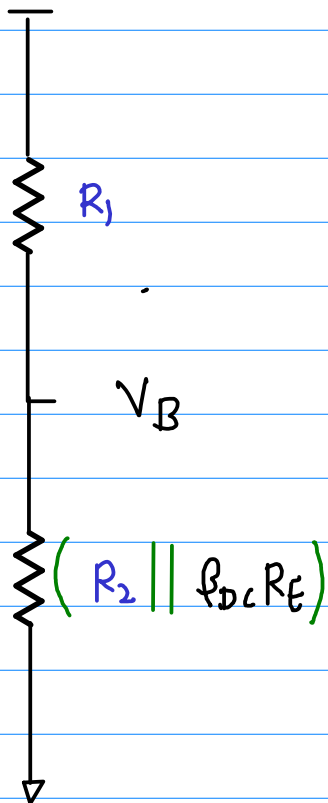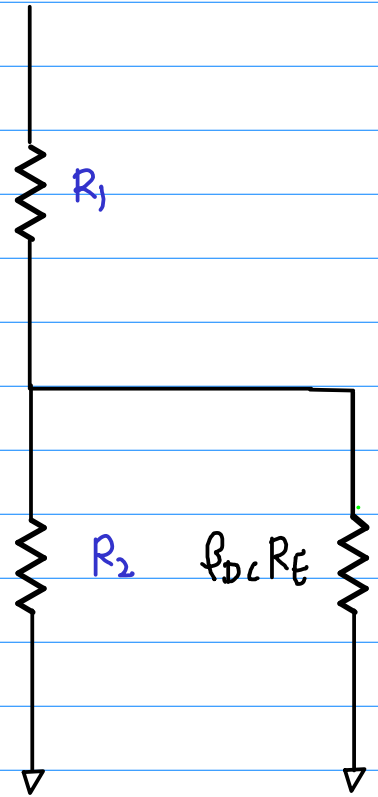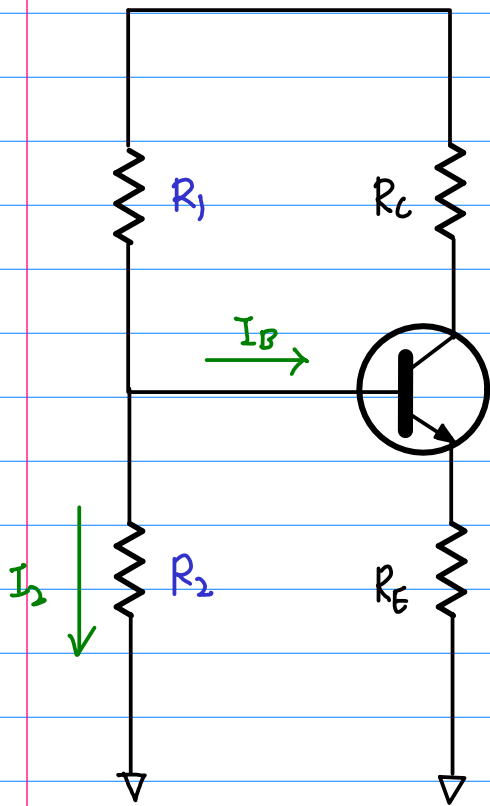
<http://learnabout-electronics.org/Amplifiers/amplifiers50.php>






$$V_B = \frac{(R_2 \parallel \beta_{DC} R_E)}{R_1 + (R_2 \parallel \beta_{DC} R_E)} \cdot V_{CC}$$

$$\approx \frac{R_2}{R_1 + R_2} \cdot V_{CC}$$
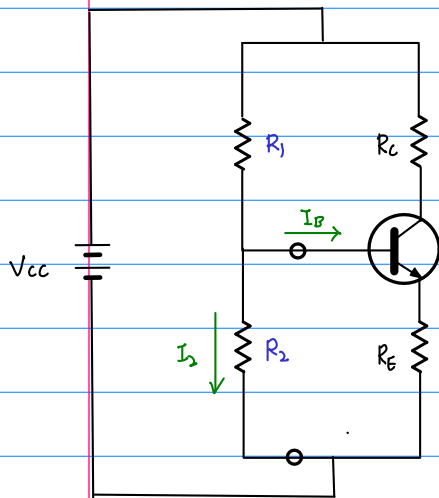
$$R_2 \ll \beta_{DC} R_E \quad (R_2 \parallel \beta_{DC} R_E) \approx R_2$$



$$R_{TH} = R_1 \parallel R_2$$

$$V_{TH} = \frac{R_2 V_{CC}}{R_1 + R_2}$$


$$\frac{1}{200+1} = \frac{1}{200}$$

$$I_E = (\beta + 1) I_B = 201 \cdot I_B$$

$$I_C = \beta I_B = 200 \cdot I_B$$

$$I_E \cong I_C$$

$$\frac{1}{201} \cong \frac{1}{200}$$

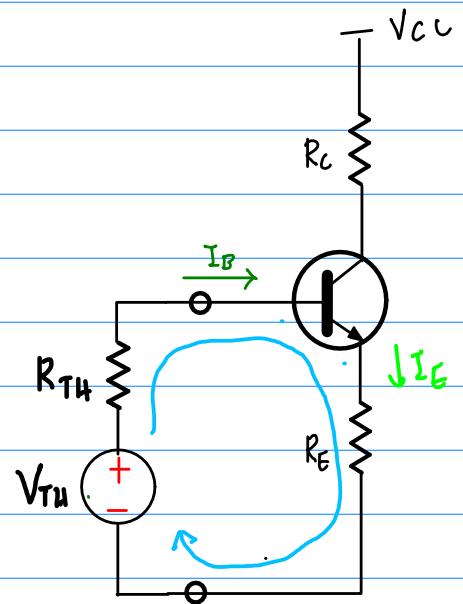

$$V_{TH} = I_B R_{TH} + V_{BE} + I_E R_E$$

$$I_E = (\beta + 1) I_B$$

$$V_{TH} - V_{BE} = I_B R_{TH} + (\beta + 1) I_B R_E$$




$$I_B = \frac{V_{TH} - V_{BE}}{R_{TH} + (\beta + 1) R_E}$$



$$I_E = (\beta + 1) \frac{V_{TH} - V_{BE}}{R_{TH} + (\beta + 1) R_E}$$


$$= \frac{(\beta + 1)}{(\beta + 1)} \frac{V_{TH} - V_{BE}}{\left(\frac{R_{TH}}{(\beta + 1)} + R_E \right)}$$

$$= \frac{V_{TH} - V_{BE}}{R_E + \frac{R_{TH}}{(\beta + 1)}}$$
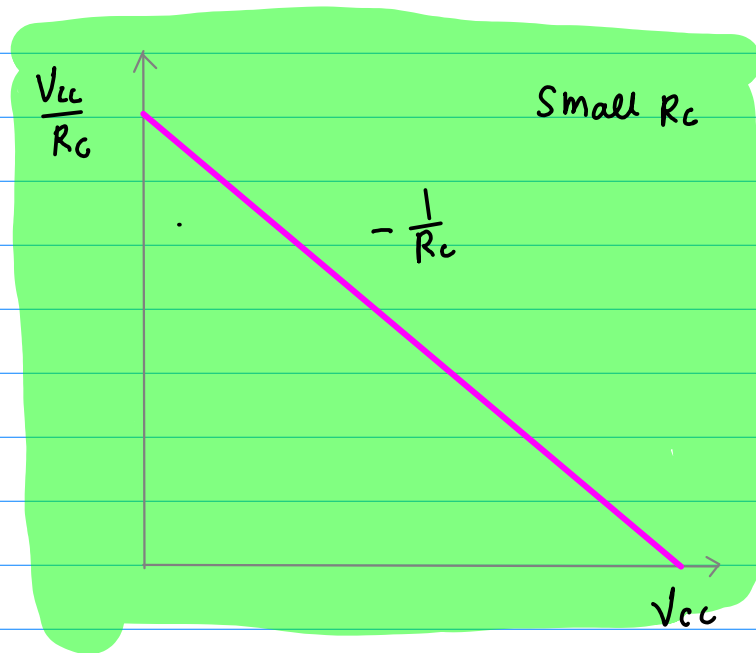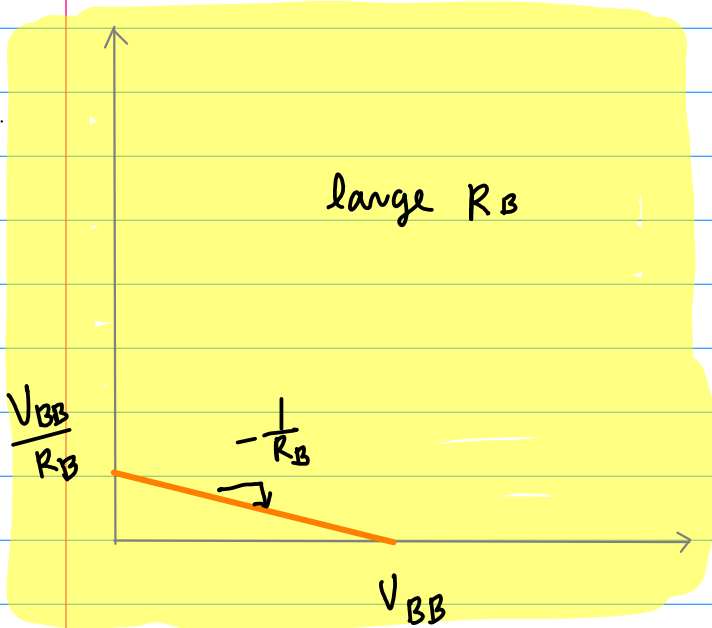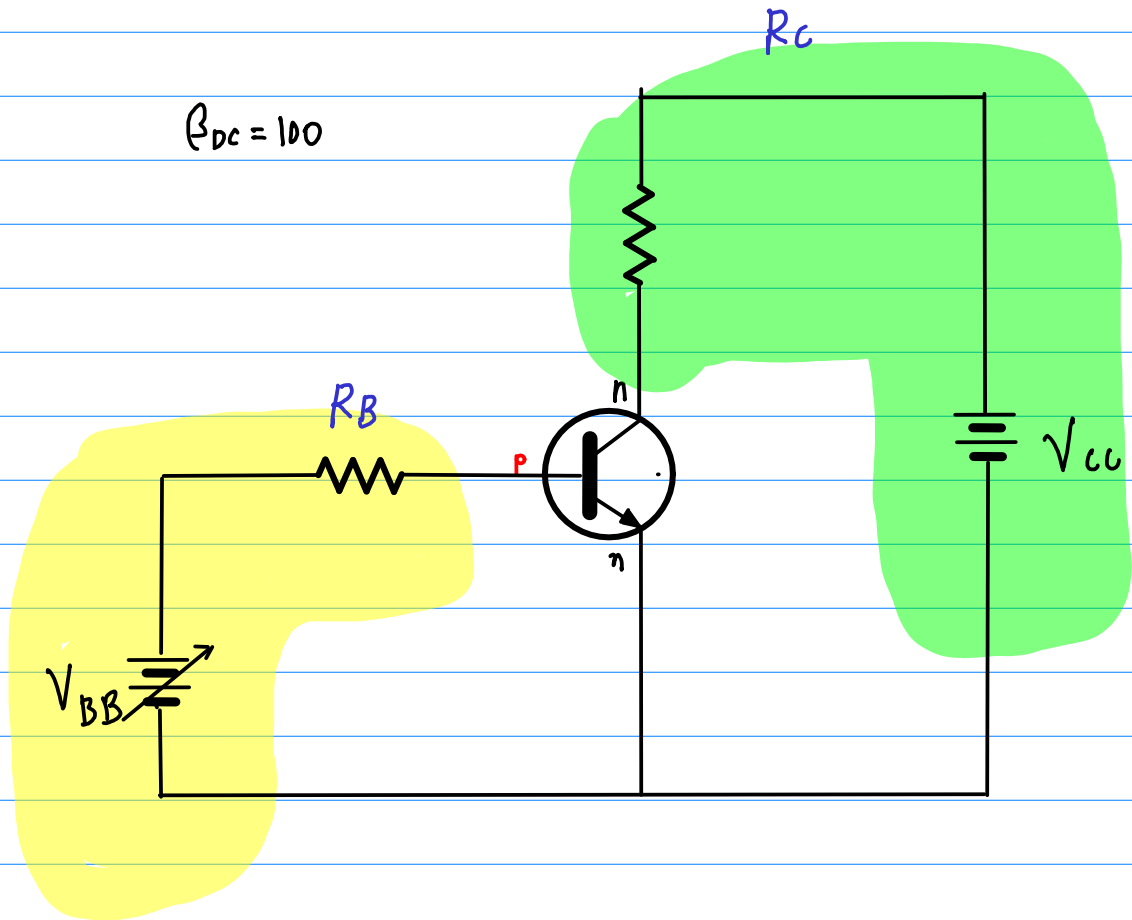
$$\cong \frac{V_{TH} - V_{BE}}{R_E + \frac{R_{TH}}{\beta}}$$



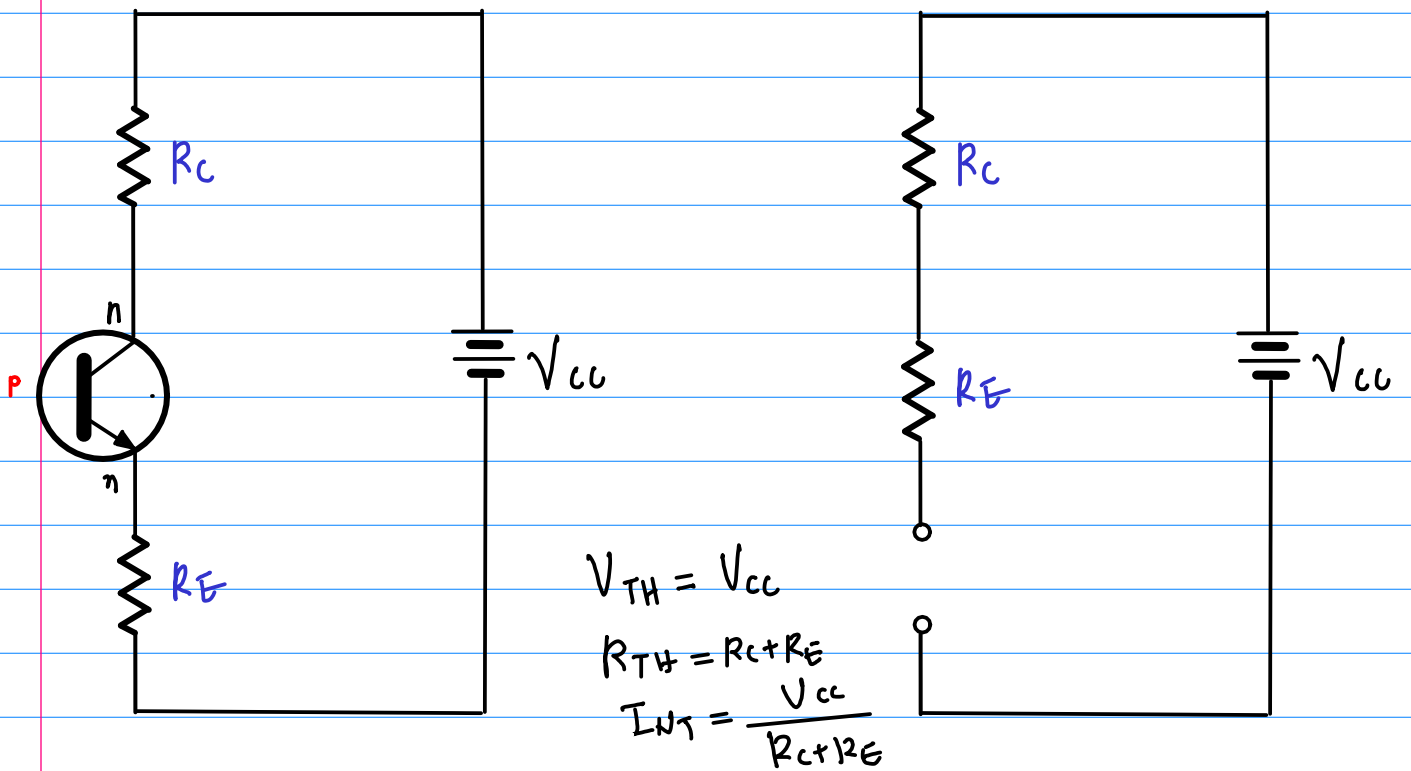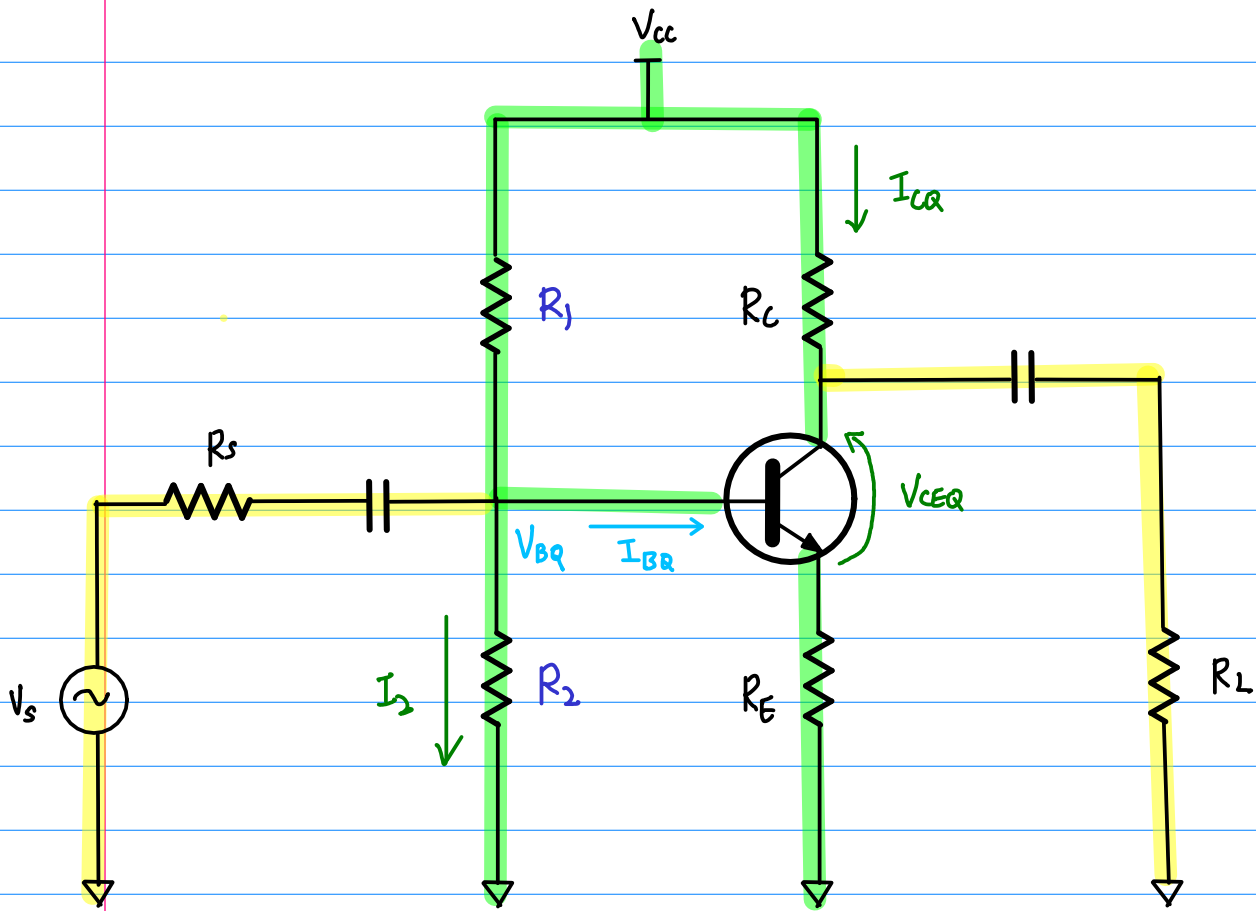

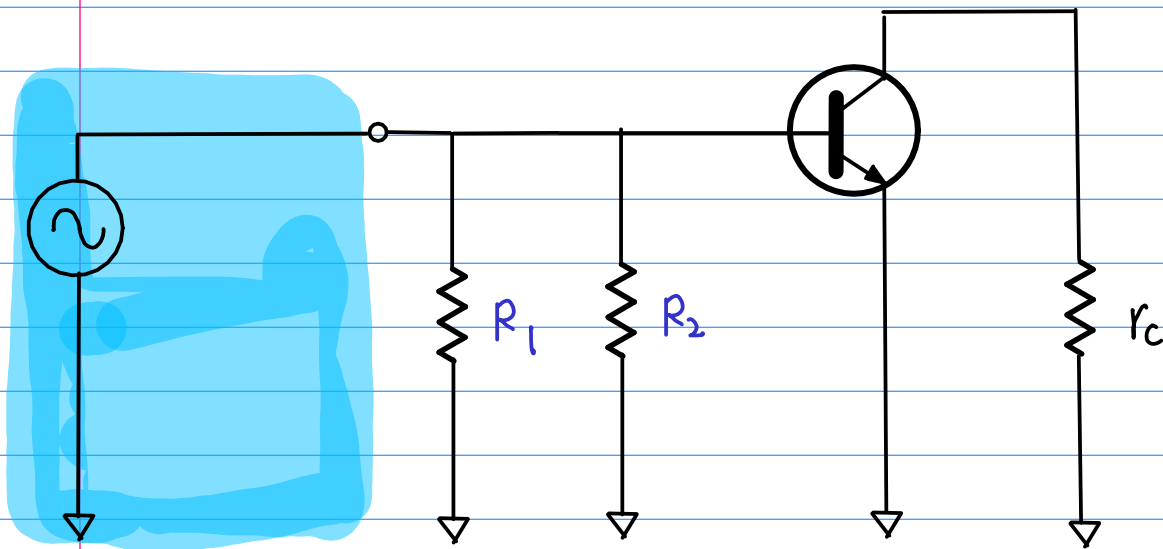

ac source

$$V_{ce} + i_c r_c = 0 \quad \Rightarrow \quad i_c = -\frac{V_{ce}}{r_c}$$

$$i_c = \Delta I_c = I_c - I_{cQ} \quad \Rightarrow \quad I_c = i_c + I_{cQ}$$

$$V_{ce} = \Delta V_{ce} = V_{ce} - V_{ceQ}$$

$$I_c = I_{cQ} - \frac{1}{r_c} (V_{ce} - V_{ceQ})$$

$$= I_{cQ} + \frac{V_{ceQ}}{r_c} - \frac{V_{ce}}{r_c}$$

$$\text{SAT } V_{ce} = 0 \quad \Rightarrow \quad I_{c(\text{SAT})} = I_{cQ} + \frac{V_{ceQ}}{r_c}$$

$$\begin{aligned} \text{OFF } I_c = 0 \quad \Rightarrow \quad V_{ce(\text{OFF})} &= V_{ceQ} + \Delta V_{ce} = V_{ceQ} + (\Delta I_c) r_c \\ &= V_{ceQ} + (I_{cQ} - I_c) r_c \\ &= V_{ceQ} + I_{cQ} r_c \end{aligned}$$

$i_{c(sat)}$ = ac saturation current

I_{CQ} = DC collector current



V_{CEQ} = DC collector-emitter voltage

r_c = ac resistance seen by the collector.

$$i_c = \Delta I_c = I_c - I_{CQ} \Rightarrow I_c = i_c + I_{CQ}$$

$$V_{ce} = \Delta V_{CE} = V_{CE} - V_{CEQ}$$

$$i_c = \Delta I_c = I_c - I_{CQ}$$

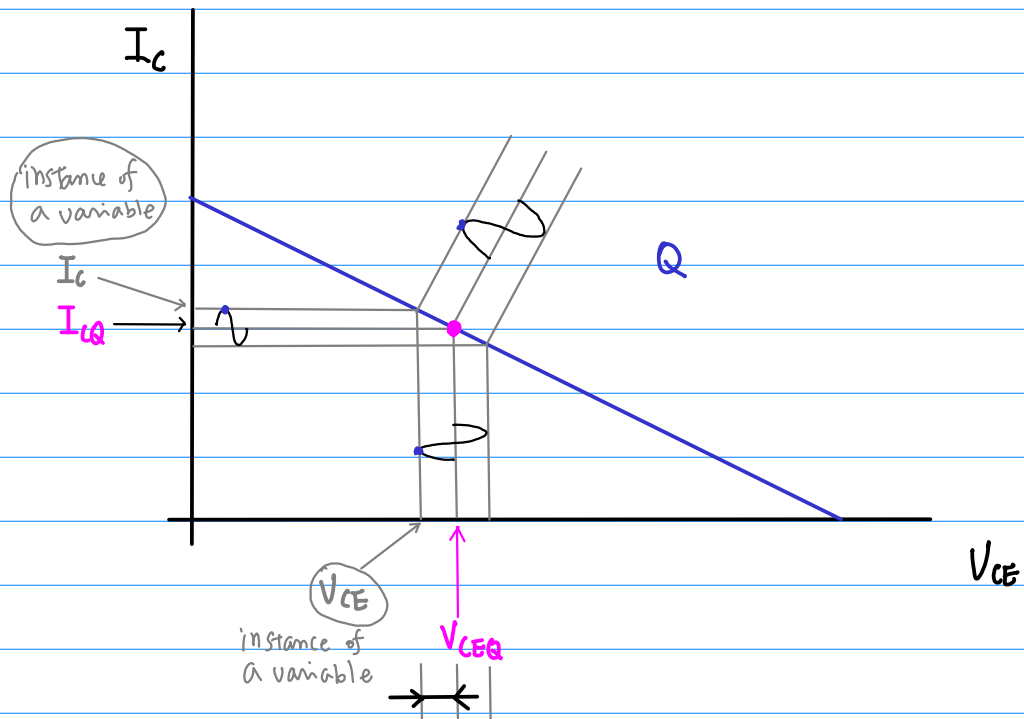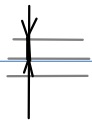

$$V_{ce} = \Delta V_{CE} = V_{CE} - V_{CEQ}$$

$$V_{ce} + i_c r_c = 0 \quad \Rightarrow \quad i_c = -\frac{V_{ce}}{r_c}$$


$$i_c = \Delta I_c = I_c - I_{cQ} \quad \Rightarrow \quad I_c = i_c + I_{cQ}$$

$$V_{ce} = \Delta V_{ce} = V_{ce} - V_{ceQ}$$

$$\begin{aligned} I_c &= i_c + I_{cQ} \\ i_c &= -\frac{V_{ce}}{r_c} \\ V_{ce} &= V_{ce} - V_{ceQ} \end{aligned}$$


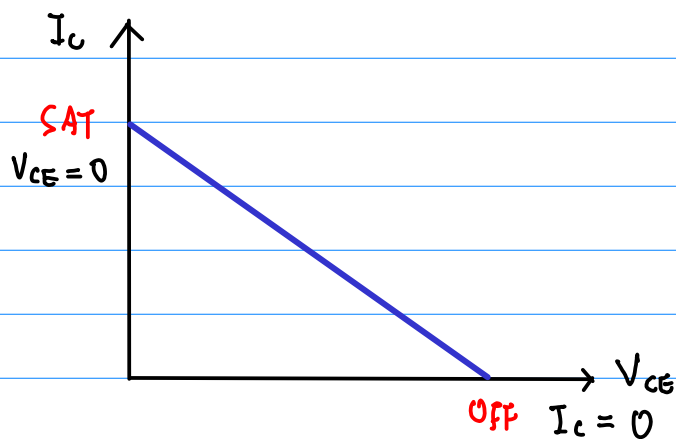
$$\begin{aligned} I_c &= I_{cQ} - \frac{1}{r_c} (V_{ce} - V_{ceQ}) \\ &= I_{cQ} + \frac{V_{ceQ}}{r_c} - \frac{V_{ce}}{r_c} \end{aligned}$$




$$\text{SAT } V_{ce} = 0 \Rightarrow I_{c(\text{SAT})} = I_{cQ} + \frac{V_{ceQ}}{r_c}$$



$$\begin{aligned} \text{OFF } I_c = 0 \Rightarrow V_{ce(\text{OFF})} &= V_{ceQ} + \Delta V_{ce} = V_{ceQ} + (-\Delta I_c) r_c \\ &= V_{ceQ} + (I_{cQ} - I_c) r_c \\ &= V_{ceQ} + I_{cQ} r_c \end{aligned}$$

$I_{c(\text{SAT})}$ instead of $i_{c(\text{SAT})}$

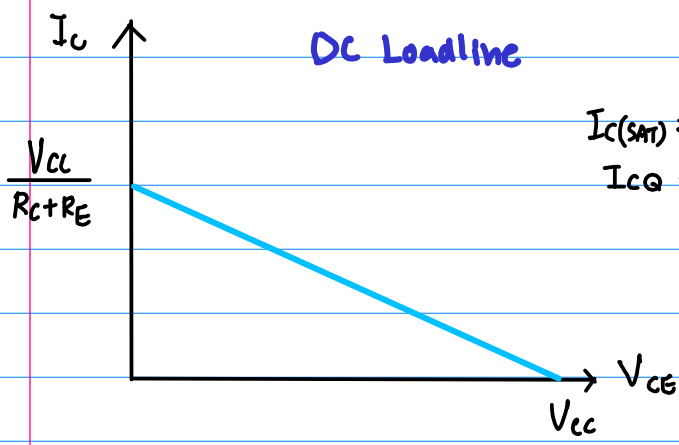$V_{ce(\text{OFF})}$ instead of $v_{ce(\text{OFF})}$


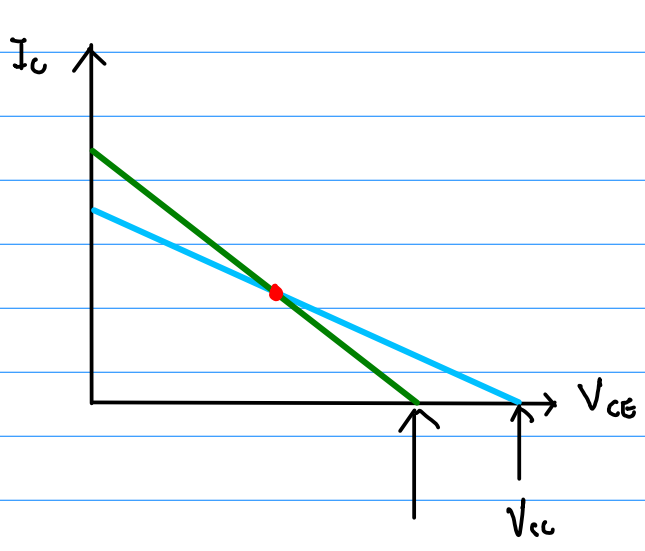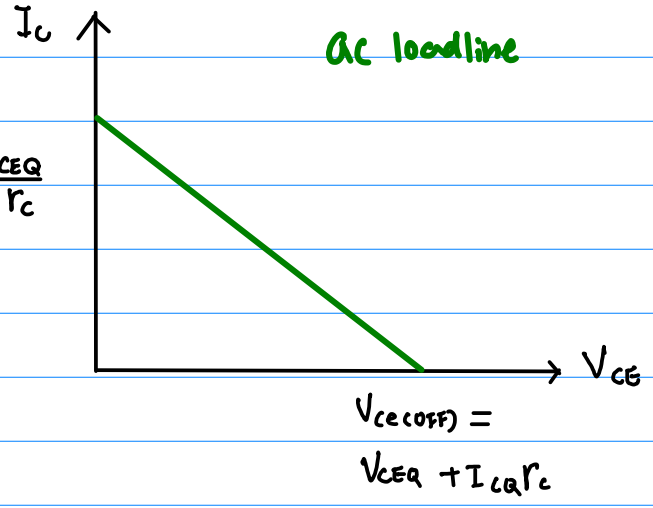
$$I_c(\text{sat}) = I_{cQ} + \frac{V_{CEQ}}{r_c}$$



Maximum Peak to Peak

$$MPP < V_{cc}$$