# Variable Block Adder (1C)

•

•


Copyright (c) 2024 - 2010 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".

Please send corrections (or suggestions) to youngwlim@hotmail.com.

This document was produced by using OpenOffice and Octave.

#### Carry Skip Adder

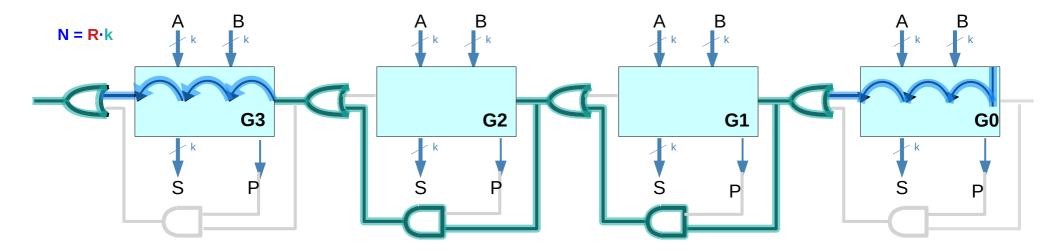

Fixed block size = k bits

$$(k-1) \Delta_{rca} \qquad (R-2) \Delta_{SKIP} \qquad (k-1) \Delta_{rca} \qquad (k-1) t \qquad (k-1) t$$

Variable block size =  $x_i$  bits for the i-th group


$$(x_i - 1) t$$

$$(m-2)T$$

$$(x_j - 1) t$$

t denote the time required for a carry signal to ripple across a bit T denote the time required for the signal to skip over a group of bits m denotes the optimal number of groups for an n-bit carry chain


#### Carry Skip Adder – fixed block size

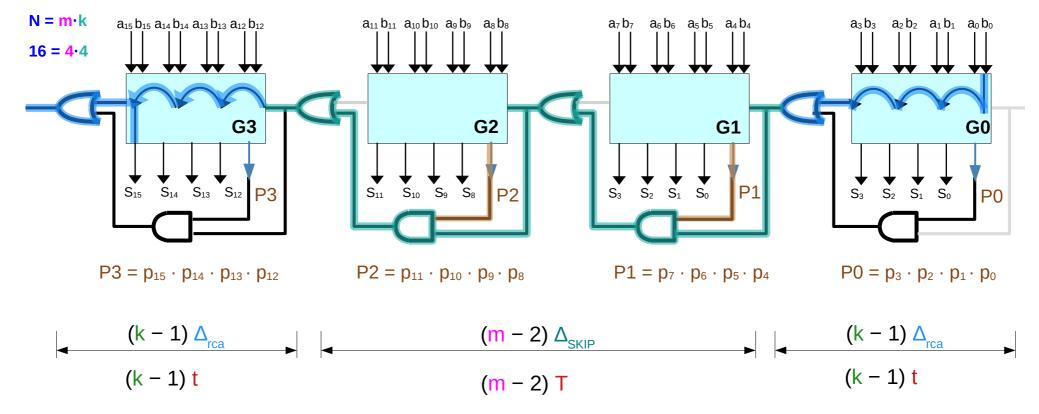


*t* denote the time required for a carry signal to ripple across a bit *T* denote the time required for the signal to skip over a group of bits *m* denotes the optimal number of groups for an n-bit carry chain

Fixed Block Size  $\Rightarrow$  delay(P3) = delay(P2) = delay(P1) = delay(P0) = Fixed Delay

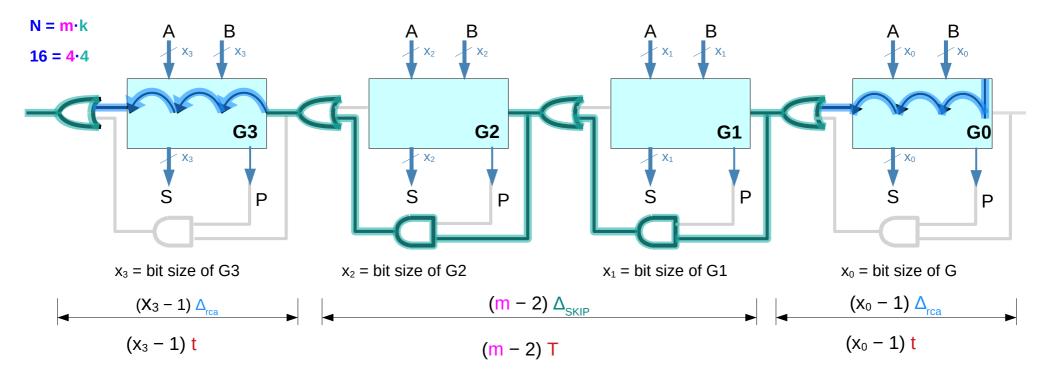
### Carry Skip Adder – maximum carry delay (3)



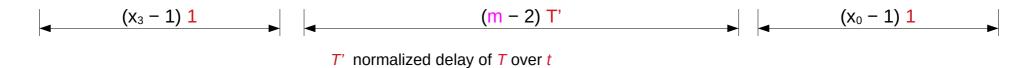*t* denote the time required for a carry signal to ripple across a bit *T* denote the time required for the signal to skip over a group of bits *m* denotes the optimal number of groups for an n-bit carry chain



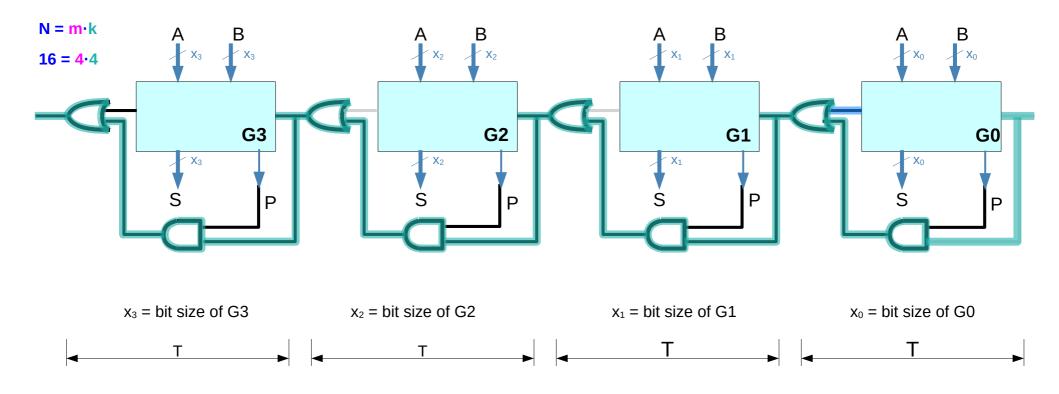
### Carry Skip Adder – maximum carry delay (3)




**Carry Skip Delays** 
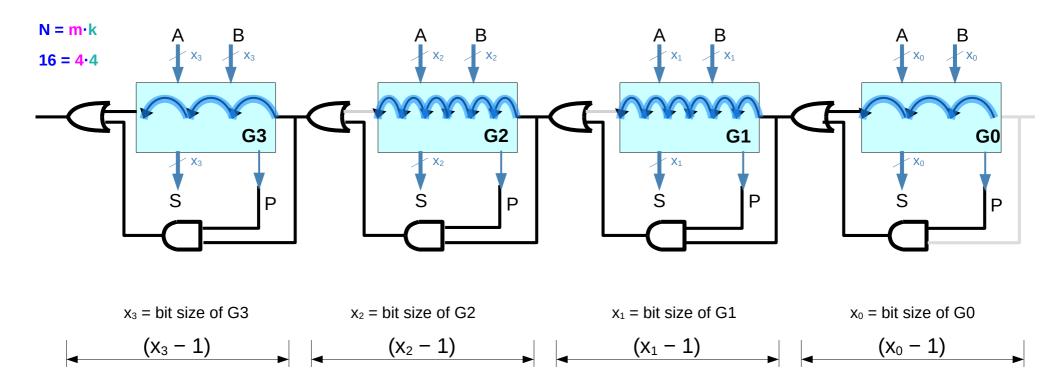
### Carry Skip Adder – maximum carry delay (3)




**Carry Ripple delays** 


#### Skip path delays and ripple delays

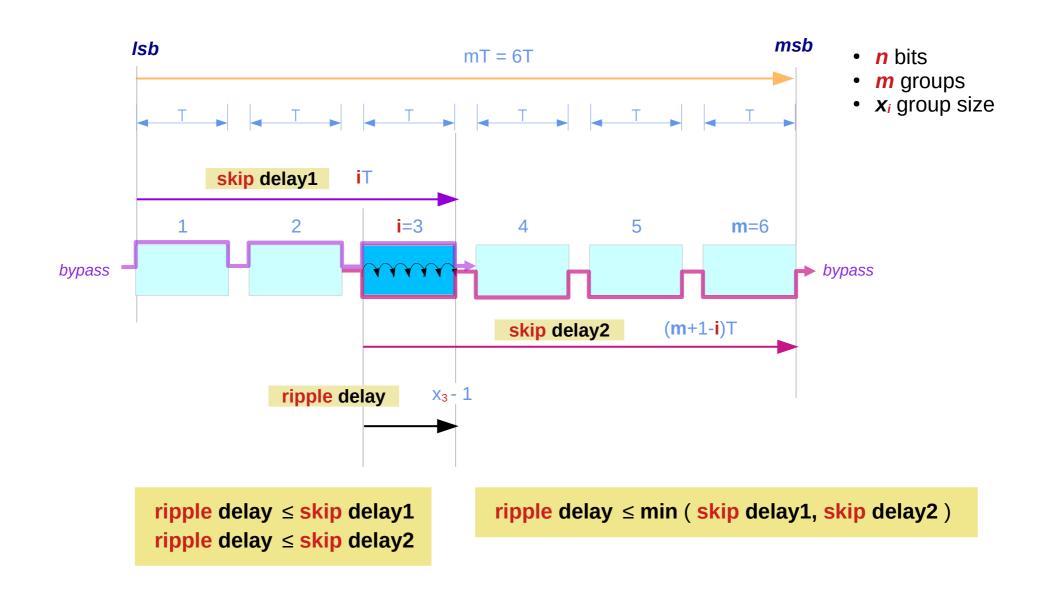


#### **Overlapping Delay Paths**

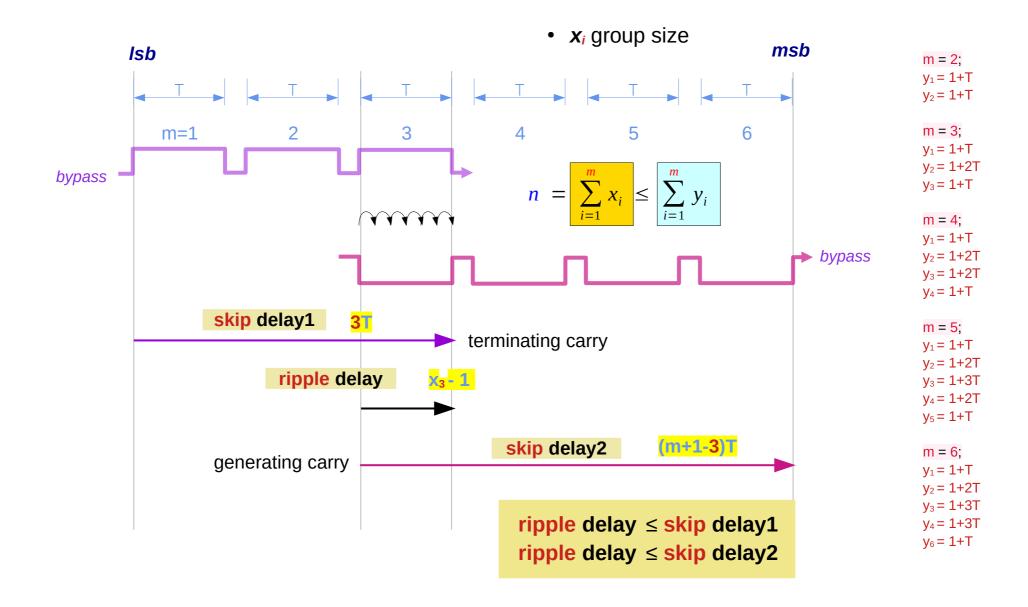


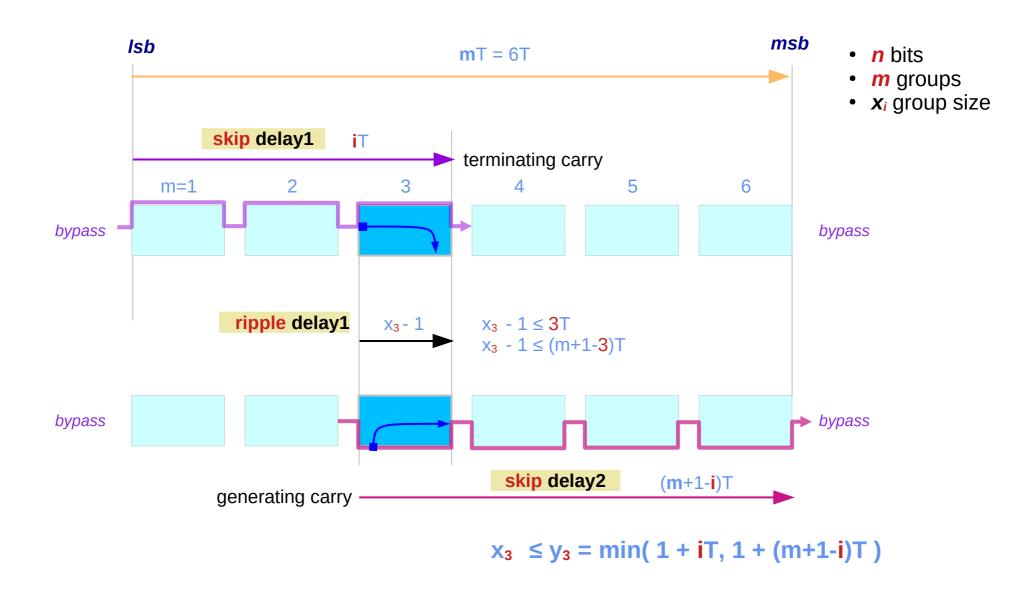
### Minimum skip path delay $(\mathbf{y}_i - \mathbf{1})$ of the $\mathbf{i}^{th}$ group



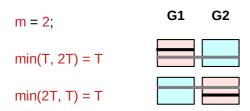
### Minimum skip path delay of the *i*<sup>th</sup> group (1)



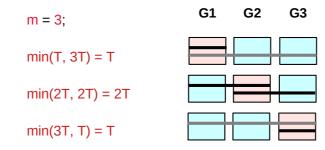

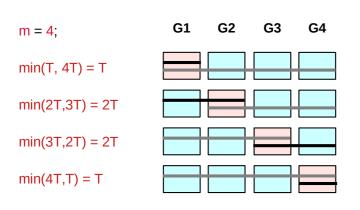


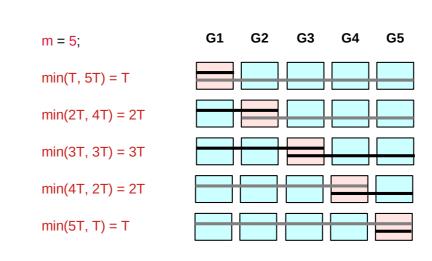

$$y_i = 1 + min\{iT, (m+1-i)T\}$$

$$y_i = min\{1+iT, 1+(m+1-i)T\}, i = 1,...,m$$
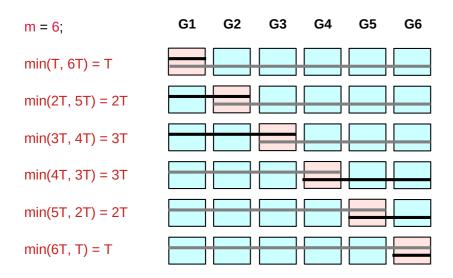
### Minimum skip path delay of the *i*<sup>th</sup> group (2)





$$y_i = 1 + min\{iT, (m+1-i)T\}$$





$$y_i = min\{1+iT, 1+(m+1-i)T\}, i = 1,...,m$$
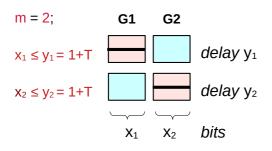
## The $i^{th}$ group has $x_i$ bits for a given m (1)



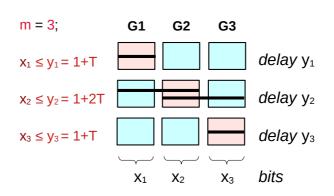

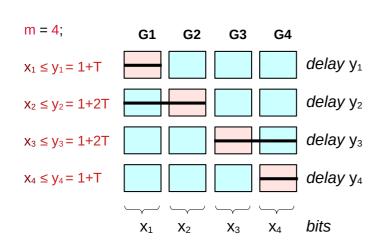

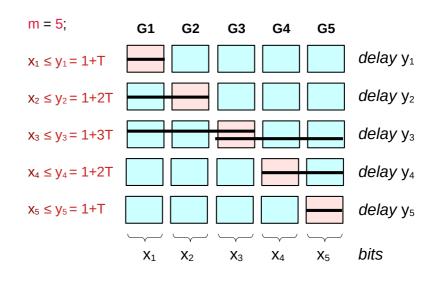


$$x_i - 1 \le min(iT, (m+1-i)T)$$



$$x_i \le y_i = \min(1 + iT, 1 + (m+1-i)T)$$
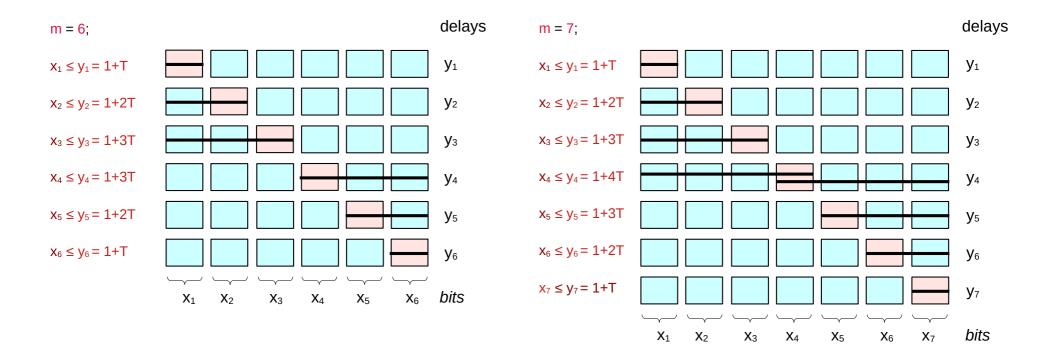
## The $i^{th}$ group has $x_i$ bits for a given m (2)




$$x_i - 1 \le \min(iT, (m+1-i)T)$$



$$x_i \le y_i = \min(1 + iT, 1 + (m+1-i)T)$$
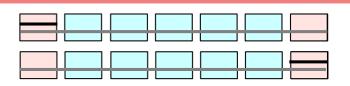
### Symmetric histograms of $y_i$ 's

$$y_1 = min\{1+1\cdot T, 1+(m+1-1)T\} = 1+T$$
 $y_m = min\{1+m\cdot T, 1+(m+1-m)T\} = 1+T$ 
 $x_1 \le y_1 = 1+T \text{ (bits)}$ 
 $x_m \le y_m = 1+T \text{ (bits)}$ 





$$y_{2} = min\{1+2\cdot T, 1+(m+1-2)T\} = 1+2T$$

$$y_{m-1} = min\{1+(m-1)\cdot T, 1+(m+1-(m-1))T\} = 1+2T$$

$$x_{2} \le y_{2} = 1+2T \quad (bits)$$
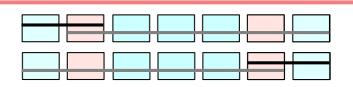
$$x_{m-1} \le y_{m-1} = 1+2T \quad (bits)$$



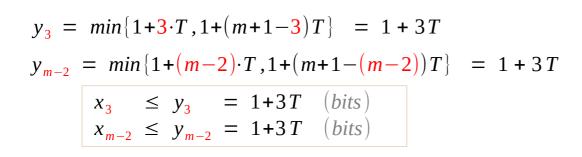



#### Procedure

(I) Let m be the smallest positive integer

$$n \leq \sum_{i=1}^{m} y_i \qquad i = 1, ..., m$$

$$i = 1, ..., m$$

(II) Let

$$y_{i} = min\{1+iT,1+(m+1-i)T\}$$

(III) Let  $x_i$ , i = 1, ..., m

starting with the first row, row by row

$$n = \sum_{i=1}^{m} x_i \le \sum_{i=1}^{m} y_i$$

Variable block size =  $x_i$  bits for the i-th group

the scheme (i), (ii), (iii) gives the max propagation time mT

Oklobdzija: High-Speed VLSI arithmetic units: adders and multipliers

#### find the smallest m

$$n \leq \sum_{i=1}^{m} y_i = \sum_{i=1}^{m} \min\{1+iT, 1+(m+1-i)T\}$$

$$m = 2;$$
  
while  $(y_1 + \dots + y_m < n)$   $m = m+1;$ 

### Determining *m* the number of groups (1)


#### **Method 1** – using a histogram

Let *m* be the <u>smallest</u> positive integer such that

$$n \leq \sum_{i=1}^{m} y_i$$

$$m = 2;$$
  
while  $(y_1+\dots+y_m < n)$   $m = m+1;$ 
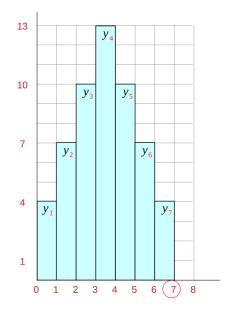
$$y_i = min\{1+iT, 1+(m+1-i)T\}, i = 1,...,m$$



```
\begin{array}{lll} m=2; & T=3 \\ y_1=\min \left\{1+T,\, 1+2T\right\} & = 1+T=4 \\ y_2=\min \left\{1+2T,\, 1+T\right\} & = 1+T=4 \\ \end{array}
\begin{array}{lll} m=3; & T=3 \\ y_1=\min \left\{1+T,\, 1+3T\right\} & = 1+T=4 \\ y_2=\min \left\{1+2T,\, 1+2T\right\} & = 1+2T=7 \\ y_3=\min \left\{1+3T,\, 1+T\right\} & = 1+T=4 \\ \end{array}
\begin{array}{lll} m=4; & T=3 \\ y_1=\min \left\{1+T,\, 1+4T\right\} & = 1+T=4 \\ \end{array}
\begin{array}{lll} y_2=\min \left\{1+T,\, 1+4T\right\} & = 1+T=4 \\ \end{array}
y_2=\min \left\{1+T,\, 1+T\right\} & = 1+T=4 \\ \end{array}
y_3=\min \left\{1+T,\, 1+T\right\} & = 1+T=7 \\ y_4=\min \left\{1+T,\, 1+T\right\} & = 1+T=4 \\ \end{array}
```

```
\begin{array}{lll} m=7; & T=3 \\ y_1=\min \left\{1+T, & 1+7T\right\} & = & 1+T=4 \\ y_2=\min \left\{1+2T, & 1+6T\right\} & = & 1+2T=7 \\ y_3=\min \left\{1+3T, & 1+5T\right\} & = & 1+3T=10 \\ y_4=\min \left\{1+4T, & 1+4T\right\} & = & 1+4T=13 \\ y_5=\min \left\{1+5T, & 1+3T\right\} & = & 1+3T=10 \\ y_6=\min \left\{1+6T, & 1+2T\right\} & = & 1+2T=7 \\ y_7=\min \left\{1+7T, & 1+1T\right\} & = & 1+T=4 \end{array}
```

```
4+4 = 8

4+7+4 = 15

4+7+7+4 = 22

4+7+10+7+4 = 32

4+7+10+10+7+4 = 42

4+7+10+13+10+7+4 = 55
```

#### Determining *m* the number of groups (2)


Method 1 – using a histogram


Let *m* be the <u>smallest</u> positive integer such that

$$n \leq \sum_{i=1}^{m} y_i$$

$$m = 2;$$
  
while  $(y_1 + \dots + y_m < n)$   $m = m+1;$ 
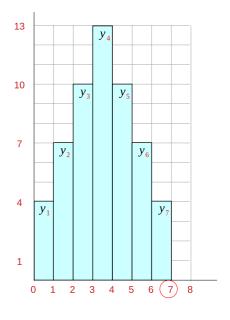
$$y_i = min\{1+iT, 1+(m+1-i)T\}, i = 1,...,m$$




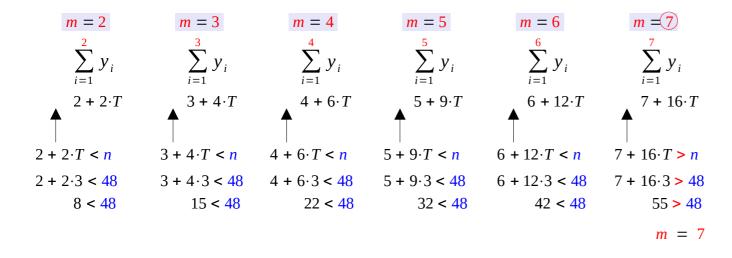



$$\begin{array}{c}
n = 48 \\
T = 3
\end{array}$$


$$m = 7$$

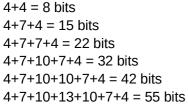
#### **n** the number of bits, **m** the number of groups




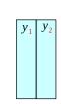

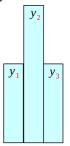


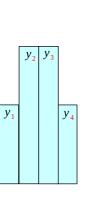


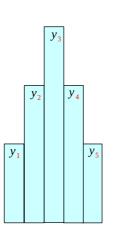


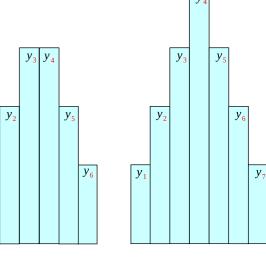

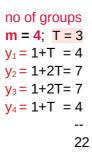
no of groups
m = 2; $T = 3$
$y_1 = 1 + T = 4$
$y_2 = 1 + T = 4$
8



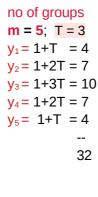

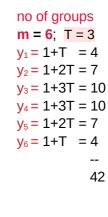

 $y_1$ 

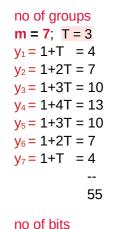

no of bits  $n \le 8$ 


no of bits 8 < n ≤ 15 no of bits 15 < n ≤ 22


no of bits 22 < n ≤ 32 no of bits 32 < n ≤ 42


m=48 m=7


 $42 < n \le 55$ 
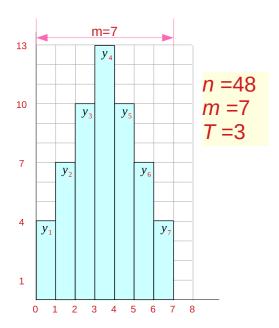
#### Determining $x_i$ the group size of the $i^{th}$ group



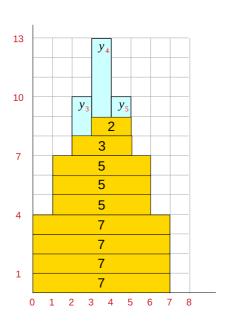

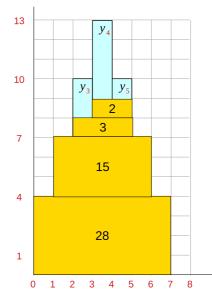

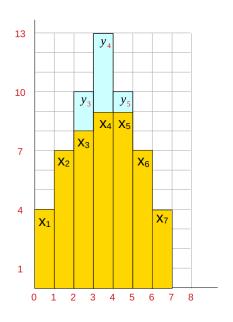


7	7
7	14
7	21
7	28
5	33
5	38
5	43
3	46
2	48


$$x_1 = 4 \le y_1 = 4$$
  
 $x_2 = 7 \le y_2 = 7$   
 $x_3 = 8 < y_3 = 10$   
 $x_4 = 9 < y_4 = 13$   
 $x_5 = 9 < y_5 = 10$   
 $x_6 = 7 \le y_6 = 7$   
 $x_7 = 4 \le y_7 = 4$ 

m = 7 groups
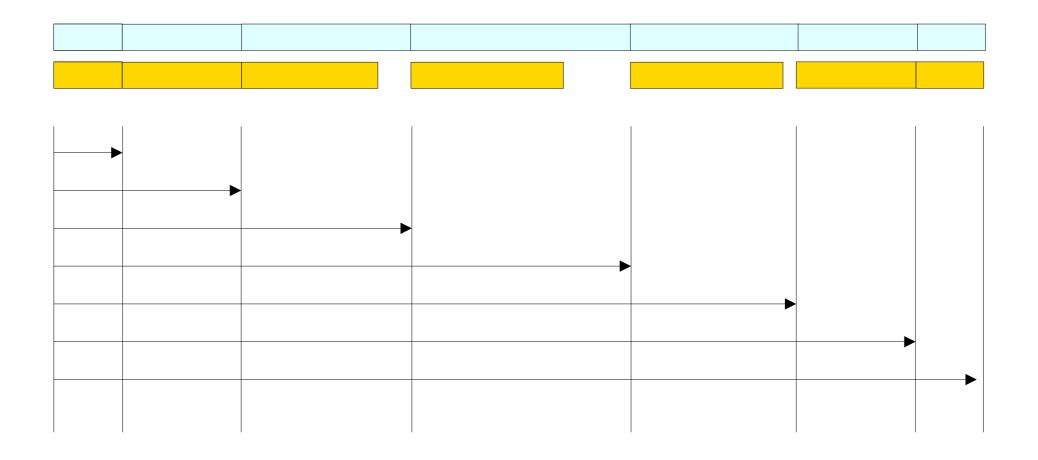
### Determining $x_i$ the group size of the i<sup>th</sup> group


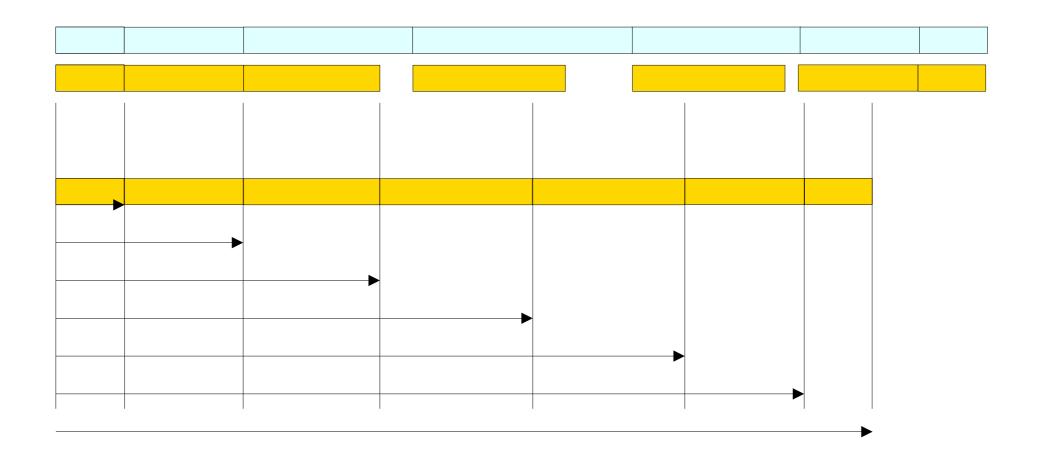
### Determining $x_i$ the group size of the i<sup>th</sup> group



#### Procedure

(I) Let m be the smallest positive integer such that

$$n \le m + \frac{1}{2}mT + \frac{1}{4}m^2T + (1 - (-1)^m)\frac{1}{8}T = \sum_{i=1}^m y_i$$
•  $m = 7$  groups
•  $i$ -th group has  $x_i$  bits (size)
• constant skip delay  $T = T(x)$ 

- total n = 48 bits
- m = 7 groups
- constant skip delay  $T = T(x_i) = 3$

(II) Let

$$y_i = min\{1+iT, 1+(m+1-i)T\}, i = 1,...,m$$

and construct a histogram whose *i-th* column has height *y*, for example, for T=3, and n=48, we have m=7

(III) It is easily verified that the area of the histogram in (II) is

$$\sum_{i=1}^{m} y_{i} = \left[ m + \frac{1}{2} m T + \frac{1}{4} m^{2} T + (1 - (-1)^{m}) \frac{1}{8} T \right] \ge n$$

so these are at least *n* unit squares in the histogram starting with the first row, shade in *n* of the squares, row by row Let  $x_i$  denote the number of shaded squares in column i of the histogram,

$$y_i = \sum_{i=1}^m x_i \le \sum_{i=1}^m y_i$$

i = 1, ..., m

#### Procedure - determining *m* the number of groups


Method 1 – using a histogram

Let  $\frac{m}{m}$  be the <u>smallest</u> positive integer such that

$$n \leq \sum_{i=1}^{m} y_i$$

$$m = 2$$
;  
while  $(y_1+\dots+y_m < n)$   $m = m+1$ ;

$$y_i = min\{1+iT,1+(m+1-i)T\}, i = 1,...,m$$

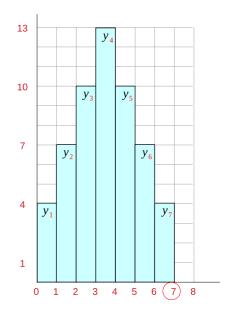


Method 2 – using a closed formula

Let *m* be the <u>smallest</u> positive integer such that
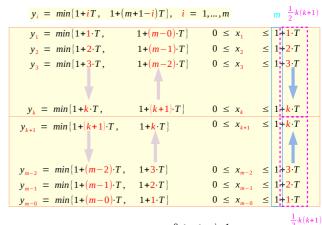
$$n \le m + \frac{1}{2}mT + \frac{1}{4}m^2T + (1 - (-1)^m)\frac{1}{8}T$$





$$0 \le x_i \le y_i, i = 1, \dots, m$$


#### Processing - determining $x_i$ the group size of the i<sup>th</sup> group


construct a histogram whose i-th column has height  $y_i$ 


so these  $y_i$ 's are <u>at least n unit squares</u> in the histogram, starting with the first row, shade in n of the squares, <u>row by row</u>

let  $\frac{x_i}{x_i}$  denote the number of shaded squares in column i of the histogram,

$$i = 1, ..., m$$

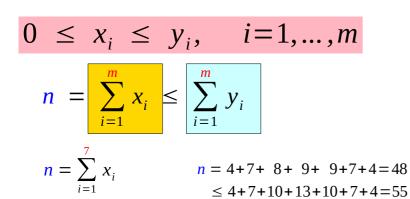

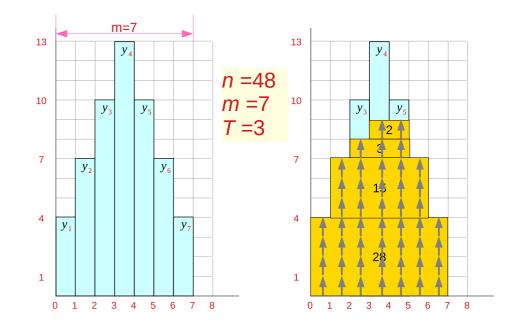

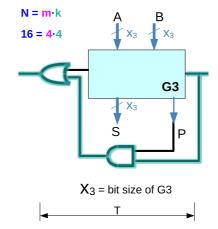

$$m = 7;$$
  $T = 3$ 
 $x_1 = 4 \le y_1 = 4$ 
 $x_2 = 7 \le y_2 = 7$ 
 $x_3 = 8 < y_3 = 10$ 
 $x_4 = 9 < y_4 = 13$ 
 $x_5 = 9 < y_5 = 10$ 
 $x_6 = 7 \le y_6 = 7$ 
 $x_7 = 4 \le y_7 = 4$ 

#### Maximum Propagation Time P<sub>max</sub>

#### find the smallest *m*


$$n \leq \sum_{i=1}^{m} y_i = \sum_{i=1}^{m} \min\{1+iT, 1+(m+1-i)T\}$$


$$m = 2$$
;  
while  $(y_1 + \dots + y_m < n)$   $m = m+1$ ;

the scheme (i), (ii), (iii) gives the max propagation time mT




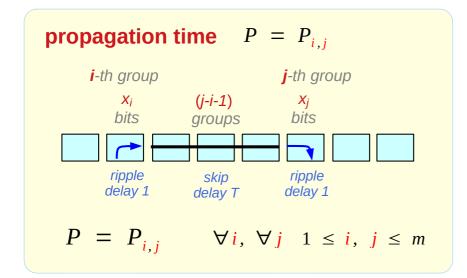propagation time of a carry signal  $\leq mT$ the maximum propagation time = mT



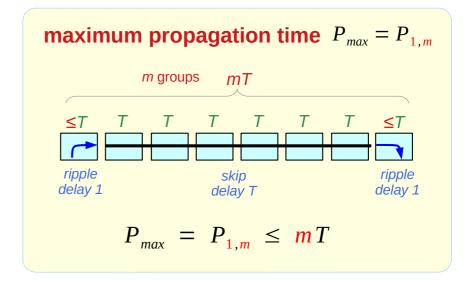

#### Maximum propagation time P

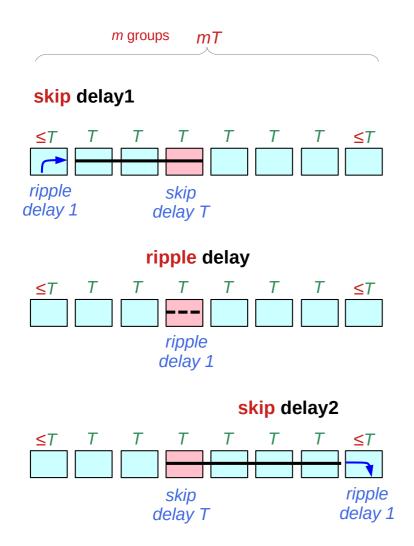

Oklobdzija: High-Speed VLSI arithmetic units: adders and multipliers

the scheme (i), (ii), (iii) gives the max prop time mT

```
skip delay1iTgenerating carryripple delayx_i - 1skip delay2(m+1-i)Tterminating carry
```

```
 \begin{cases} x_i \text{-} \ 1 \leq iT \\ x_i \text{-} \ 1 \leq (m+1-i)T \end{cases}   \begin{cases} x_i \leq 1 + iT \\ x_i \leq 1 + (m+1-i)T \end{cases}   x_i \leq \min \left\{ 1 + iT, \ 1 + (m+1-i)T \right\} = y_i   X_i \leq y_i
```

#### Maximum propagation time P


$$y_i = min\{1+iT, 1+(m+1-i)T\}, i = 1,...,m$$

the scheme (i), (ii), (iii) gives the max prop time *mT* 

$$y_1 = min\{1+1\cdot T, 1+(m+1-1)T\} = 1+T$$
  
 $y_m = min\{1+m\cdot T, 1+(m+1-m)T\} = 1+T$ 

$$x_1 \le y_1 = 1 + T$$

$$x_m \le y_m = 1 + T$$

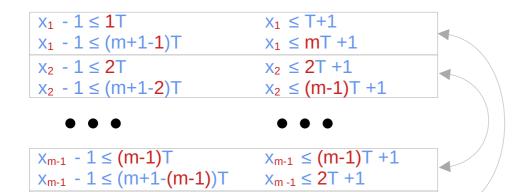


 $x_m - 1 \le mT$ 

 $x_m - 1 \le T$ 

Oklobdzija: High-Speed VLSI arithmetic units: adders and multipliers

#### maximum propagation time

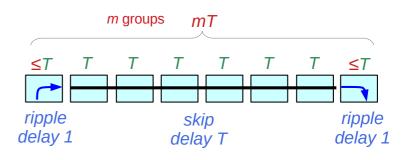

$$P_{max} = P_{1,m} \leq mT$$

$$P = P_{i,j} \leq mT$$

 $x_m - 1 \le mT$ 

 $x_{m} - 1 \le (m+1-m)T$ 

#### Maximum propagation time P

**Lemma 1** When the bits of a carry skip adder are grouped according to the scheme (i)-(iii), the maximum propagation time of a carry signal is *mT* 


the scheme (i), (ii), (iii) gives the max prop time *mT* 

The carry generated at the  $2^{nd}$  bit position and terminating at the  $(n-1)^{th}$  bit position clearly has propagation time mT.

We must show that *any other* carry signal has propagation time  $\underline{smaller}$  than or equal to  $\underline{mT}$ 

propagation time of a carry signal  $\leq mT$ the maximum propagation time = mT

#### maximum propagation time

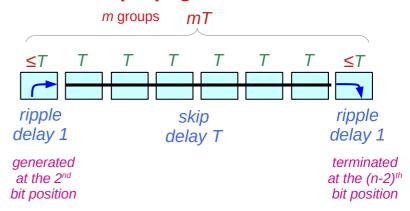

$$P_{max} = P_{1,m} \leq mT$$

#### Delay range of a carry signal

**Lemma 2** Let *D* denote the maximum delay of a carry signal in a *n* bit carry skip adder with group sizes chosen optimally. Then


• r groups

$$(m-1)T \leq D \leq mT$$

Since we have exhibited a <u>division</u> of the carry chain into groups In such a way that the <u>maximum delay</u> of a carry signal is mT We clearly have  $D \leq mT$ 

the maximum delay = D the optimal group size = m

$$(m-1)T \leq D \leq mT$$

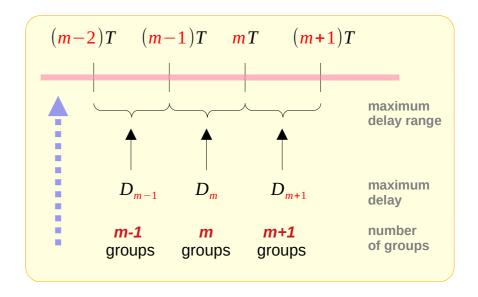

#### Maximum delay and optimal group size

the maximum propagation time  $\infty$  the number of groups

 $D \propto m$ 

- <u>not</u> an optimal optimal division
  - larger number of groups →
  - larger delays →

- when group size m is <u>not optimal</u> then there is an <u>optimal</u> group size = r
  - the maximum delay with the group size m  $D_m = mT$
  - the maximum delay with the group size r  $D_r = rT$
  - r must be smaller than m  $r \le m$

$$D_r < D_m$$

$$\rightarrow rT < mT$$


$$\rightarrow r < m$$

### Maximum delay of a carry signal

$$(m-1)T \leq D \leq mT$$

Assume there are **r** groups the propagation delay of P: any carry signal path  $\leq mT$ then 2 cases: even r, odd r the max of P D: for each of these 2 cases the upper bound of D prove mT - D < T + 1 $\longrightarrow$   $mT - D \leq T$  $diff(mT, D) \leq T$  $\longrightarrow$   $(m-1)T \leq D$ diff  $(mT, max P) \leq T$ the lower bound of D  $(m-1)T \leq D$ 
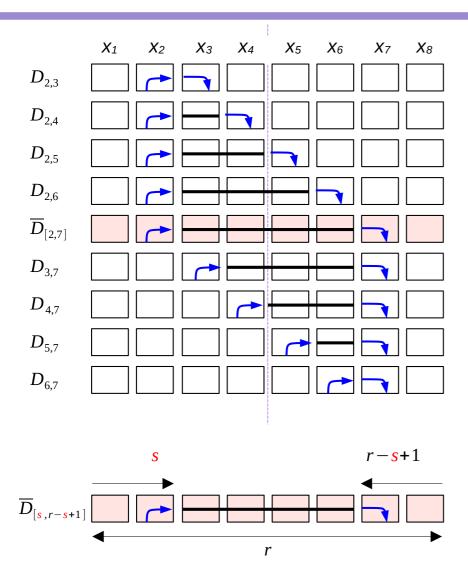
### Maximum delays of carry signals (r = 2k)



Oklobdzija: High-Speed VLSI arithmetic units: adders and multipliers


 $\overline{D}_{[2,7]}$  = the maximum delay of carry signals  $\leq \overline{D}$  generated in the i-th group and terminated in the j-th group such that  $2 \leq i, j \leq 7$ 

$$\overline{D}_{[2,7]} = \max \left\{ \begin{bmatrix} D_{2,3}, & D_{2,4}, & D_{2,5}, & D_{2,6}, \\ & D_{2,7}, & \\ D_{3,7}, & D_{4,7}, & D_{5,7}, & D_{6,7} \end{bmatrix} \right\}$$


 $\overline{D}_{[s,r-s+1]}$  = the maximum delay of carry signals generated in the i-th group and terminated in the j-th group such that  $s \le i, j \le r-s+1$ 

$$\overline{D}_{[2,7]} = \overline{D}_{[2,8-2+1]} = \overline{D}_{[s,8-s+1]} \leftarrow s = 2$$
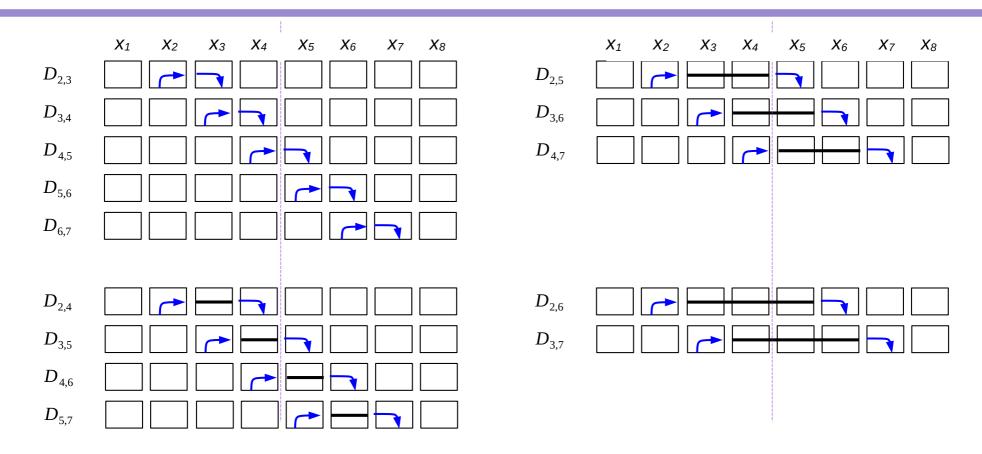
### Maximum delays of carry signals (r = 2k)


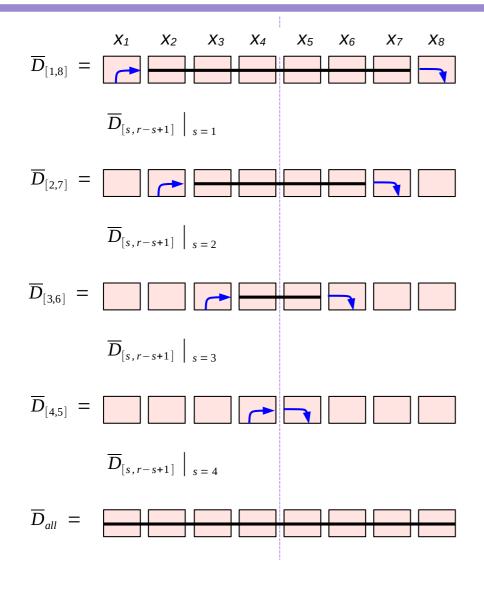
### Maximum delays of carry signals (r = 2k)



Oklobdzija: High-Speed VLSI arithmetic units: adders and multipliers

$$\overline{D}_{[1,8]} =$$
The maximum delay of carry signals  $\leq D$  generated in the i-th group or terminated in the j-th group such that  $1 \leq i, j \leq 8$ 

$$\overline{D}_{[2,7]} =$$
The maximum delay of carry signals  $\leq D$  generated in the i-th group or terminated in the j-th group such that  $2 \leq i$ ,  $j \leq 7$ 

$$\overline{D}_{[3,6]} =$$
 The maximum delay of carry signals  $\leq D$  generated in the i-th group or terminated in the j-th group such that  $3 \leq i, j \leq 6$ 


$$\overline{D}_{[4,5]} =$$
 The maximum delay of carry signals  $\leq D$  generated in the i-th group or terminated in the j-th group such that  $4 \leq i, j \leq 5$ 

$$\overline{D}_{all} = All \, skip \, delay$$

 $\leq D$ 

$$D = max\{\overline{D}_{[1,8]}, \overline{D}_{[2,7]}, \overline{D}_{[3,6]}, \overline{D}_{[4,5]}\}$$
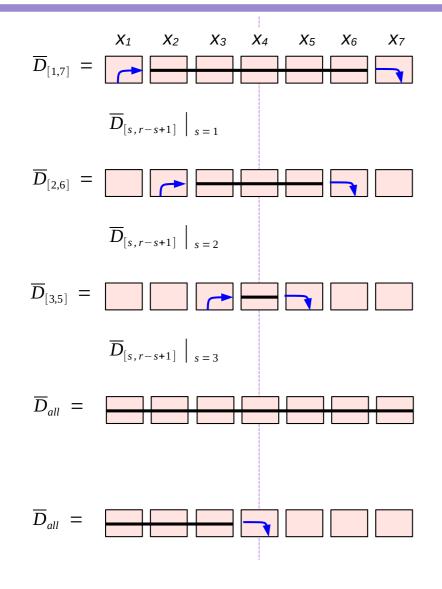
#### Maximum delays of carry signals (r = 2k+1)



Oklobdzija: High-Speed VLSI arithmetic units: adders and multipliers

$$\overline{D}_{[1,7]} =$$
The maximum delay of carry signals  $\leq D$  generated in the i-th group or terminated in the j-th group such that  $1 \leq i, j \leq 8$ 

$$\overline{D}_{[2,6]} =$$
The maximum delay of carry signals  $\leq D$  generated in the i-th group or terminated in the j-th group such that  $2 \leq i, j \leq 7$ 

$$\overline{D}_{[3,65]} =$$
 The maximum delay of carry signals  $\leq D$  generated in the i-th group or terminated in the j-th group such that  $3 \leq i, j \leq 6$ 

$$\overline{D}_{all} = All \, skip \, delay$$

$$\widetilde{D}_{all}$$
 = Comparable to all skip delay

$${f D}=\max\{\overline{D}_{[1,8]},\ \overline{D}_{[2,7]},\ \overline{D}_{[3,6]},\ \overline{D}_{[4,5]}\}$$
 Max delay of all carry signals

 $\leq D$ 

# Maximum delays of carry signals (r = 2k)

$$D = \max_{s=1}^{r/2} \overline{D}_{[s,r-s+1]}$$

$$= \max_{s=1}^{k} \overline{D}_{[s,2k+1-s]}$$

$$= \max_{s=1}^{4} \overline{D}_{[s,9-s]}$$


Max delay of all carry signals

 $\overline{D}_{[1,r]} \leq D$   $\overline{D}_{[2,r-1]} \leq D$   $\vdots \qquad \vdots$   $\overline{D}_{[k,k+1]} \leq D$   $\overline{D}_{all} \leq D$   $(m-1)T \leq D$ 

Oklobdzija: High-Speed VLSI arithmetic units: adders and multipliers

Lower bound of D
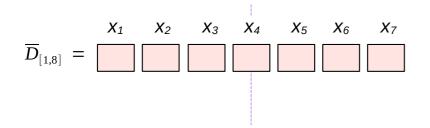
#### Maximum delays of carry signals (r = 2k+1)




$$\mathbf{D} = \max_{s=1}^{floor(r/2)} \overline{D}_{[s,r-s+1]}$$

$$= \max_{s=1}^{k} \overline{D}_{[s,2k+2-s]}$$


$$= \max_{s=1}^{3} \overline{D}_{[s,8-s]}$$

Max delay of all carry signals

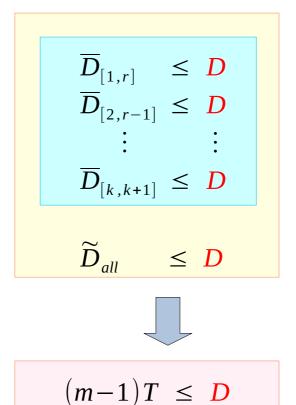


Lower bound of D
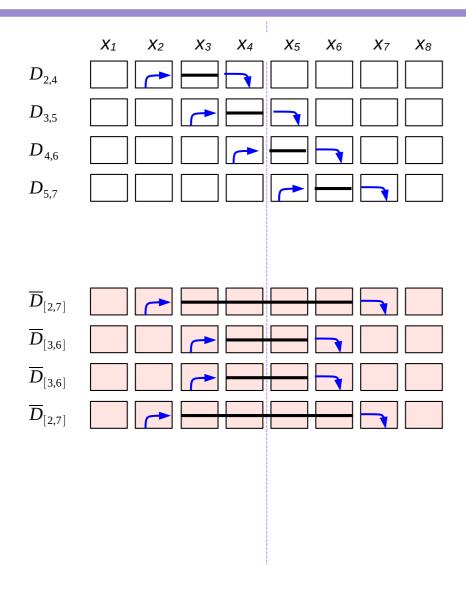
#### Example delays of carry signals (r = 2k) (1)


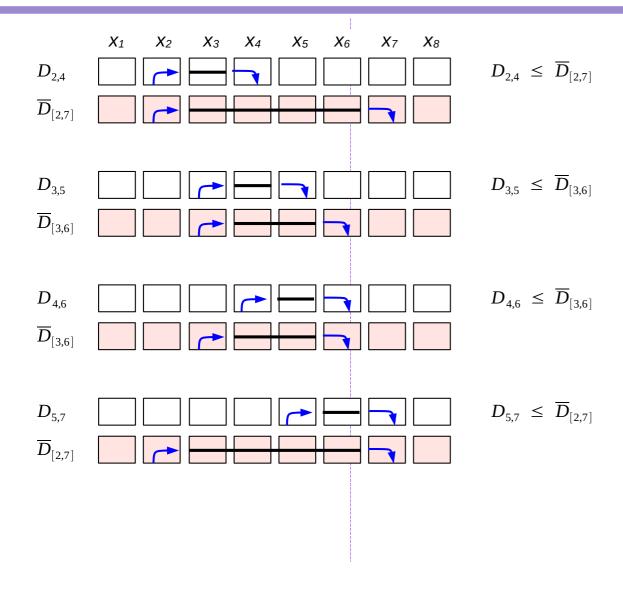
# Example delays of carry signals (r = 2k) (2)



#### **Theorem 1**

The scheme 2(i) - 2(iii) given above for dividing the bits of a carry skip adder into groups is optimal for  $2 \le T \le 7$ 

dividing the bits into groups by the scheme 2(i) - 2(iii) gives m groups

propagation time of a carry signal  $\leq mT$  the maximum propagation time = mT

the maximum delay = Dthe optimal group size = m

$$(m-1)T \leq D \leq mT$$

Oklobdzija: High-Speed VLSI arithmetic units: adders and multipliers

(I) Let m be the smallest positive integer such that

$$n \le m + \frac{1}{2}mT + \frac{1}{4}m^2T + (1 - (-1)^m)\frac{1}{8}T$$

(II) Let 
$$y_i = min\{1+iT, 1+(m+1-i)T\},\ i = 1,...,m$$

and construct a histogram whose *i-th* column has height  $y_i$ 

(III) the area of the histogram in (II) is

$$m + \frac{1}{2}mT + \frac{1}{4}m^2T + (1-(-1)^m)\frac{1}{8}T \ge n$$

so these are <u>at least n unit squares</u> in the histogram starting with the first row, shade in n of the squares, <u>row by row</u>
Let  $x_i$  denote the number of shaded squares in column i of the histogram,

$$i = 1, ..., m$$

#### **Assume**

- the scheme by 2(i) 2(iii) (m groups) is not optimal
- let D be the maximum delay corresponding to an optimal division of the bits into groups
- there are *r* groups in the optimal division.

Since a carry in signal to the least significant bit group can skip over each group

we have  $rT \le D \le mT$  so  $r \le m$ 

if m is <u>not</u> optimal, <u>but</u> r is then  $mT \ge rT$  (smaller delay rT) thus  $m \ge r$  (smaller r exists)

Oklobdzija: High-Speed VLSI arithmetic units: adders and multipliers

#### **m** groups

- <u>not</u> optimal division
- -D = maximum delay
- -mT skip delay

#### r groups

- optimal division
- *rT* skip delay

skip delay  $rT \le D \le mT$ 

 $r \leq m$ 

D = max delay is assumedTo be greater than all skipdelay rT of the optimal division

If the optimal division gives *m* groups

$$m$$
 groups  $mT$  (m-1) groups  $mT$ 

Normally, by 2(i) - 2(iii) (m groups) is optimal and its maximum delay D is less than all skip delay mT

$$D \leq mT$$

To prove this, first, negate that

- m is not by the optimal division, but r is
- D is greater than all skip delay of the optimal division

$$D \leq mT$$

$$(m-1)T \leq D$$

- when optimal group size = m the maximum delay  $D_m \le mT$
- when optimal group size = (m-1)the maximum delay  $D_{m-1} \le (m-1)T$

D = maximum delay

$$rT \le D \le mT$$

$$r \le m$$
  $\longrightarrow$   $r < (m-1)$ 

```
rT \le D \le mT so r \le m
```

Optimal division : r groups  $D' \leq all \ skip \ delay \ rT \ (r \ groups)$ 

Non-optimal division : m groups  $D \le all \ skip \ delay \ mT \ (m \ groups)$ too many partitions  $m \ r \le m$ 

Assume max delay D is greater than all skip delay rT of the optimal division

if m is <u>not</u> optimal, <u>but</u> r is then  $mT \ge rT$  (smaller delay rT) thus  $m \ge r$  (smaller r exists)

D is max delay for m groups D' is max delay for r groups then  $D' \le rT \le D \le mT$ 

Oklobdzija: High-Speed VLSI arithmetic units: adders and multipliers

D = maximum delay $rT \le D \le mT$ 

 $r \le m$   $\longrightarrow$  r < (m-1)

we have  $rT \le D \le mT$  so  $r \le m$ 

If 
$$r = m$$
  
then  $D = mT$   $\longrightarrow$   $D = rT$   $rT = D$   
If  $r = m-1$ ,  $(r < m)$   
 $D \ge (m-1)T$   $\longrightarrow$   $D \ge (m-1)T = rT$   $rT \le D$   
if  $r < m-1$ ,  $(r < m)$   
 $D \ge (m-1)T$   $\longrightarrow$   $D \ge (m-1)T > rT$   $rT < D$ 

we have  $rT \le D \le mT$  so  $r \le m$ 

If r = m then D = mT and the **theorem** holds by **lemma** 1

When the bits of a carry skip adder are grouped according to the scheme (i)-(iii), the maximum propagation time of a carry signal is mT

 $(m-1)T \le D \le mT$ 

Oklobdzija: High-Speed VLSI arithmetic units: adders and multipliers

**Lemma 1** When the bits of a carry skip adder are grouped according to the scheme (i)-(iii), the maximum propagation time of a carry signal is mT

**Theorem 1** The scheme 2(i) - 2(iii) given above for dividing the bits of a carry skip adder into groups is optimal for  $2 \le T \le 7$ 

(5) 
$$r=2k$$
  $X = 4-T^2$   $mT-D \le T + \frac{-8(T/n)+4}{\sqrt{4(T/n)+8(T/n^2)} + \sqrt{4(T/n)+4/n^2}}$   $r=2k+1$   $X = 4$ 

$$mT-D \le T + \frac{(T-2)^2/n}{\sqrt{4(T/n)+4(T/n^2)} + \sqrt{4(T/n)+(T/n)^2+4/n^2}}$$

*m* groups – not optimal division *r* groups – optimal division

D = maximum delay

 $rT \le D \le mT$ 

 $r \leq m$ 

```
If r = m-1, (r < m)

m and r have different parities and

it follows from (5)

that mT - D \le T for 2 \le T \le 7
```

so that 
$$D \ge (m-1)T$$
  
since  $r = m-1$ ,  
 $D \ge (m-1)T = rT$   $rT \le D$ 

This means that a signal which skips over each of the r groups (rT) has delay less than the maximum D.

$$rT \le D \le mT$$

*m* is <u>not</u> optimal division *r* is optimal division

Oklobdzija: High-Speed VLSI arithmetic units: adders and multipliers

**Lemma 1** When the bits of a carry skip adder are grouped according to the scheme (i)-(iii), the maximum propagation time of a carry signal is mT

**Theorem 1** The scheme 2(i) - 2(iii) given above for dividing the bits of a carry skip adder into groups is optimal for  $2 \le T \le 7$ 

(5) 
$$r=2k$$
  $X = 4-T^2$ 

$$mT-D \le T + \frac{-8(T/n)+4}{\sqrt{4(T/n)+8(T/n^2)} + \sqrt{4(T/n)+4/n^2}}$$

$$r=2k+1 \qquad X = 4$$

$$mT-D \le T + \frac{(T-2)^2/n}{\sqrt{4(T/n)+4(T/n^2)} + \sqrt{4(T/n)+(T/n)^2+4/n^2}}$$

*m* groups – not optimal division *r* groups – optimal division

D = maximum delay

 $rT \le D \le mT$ 

 $r \leq m$ 

```
Similarly,
if r < m-1, (r < m)
(m-1)T \le D
since r < m-1,
rT < (m-1)T \le D
```

so that a signal which skips over each group has delay rT < D.

```
rT < D \le mT
```


*m* is <u>not</u> optimal division *r* is optimal division

*m* groups – not optimal division *r* groups – optimal division

*D* = maximum delay

 $rT \le D \le mT$ 

 $r \leq m$ 

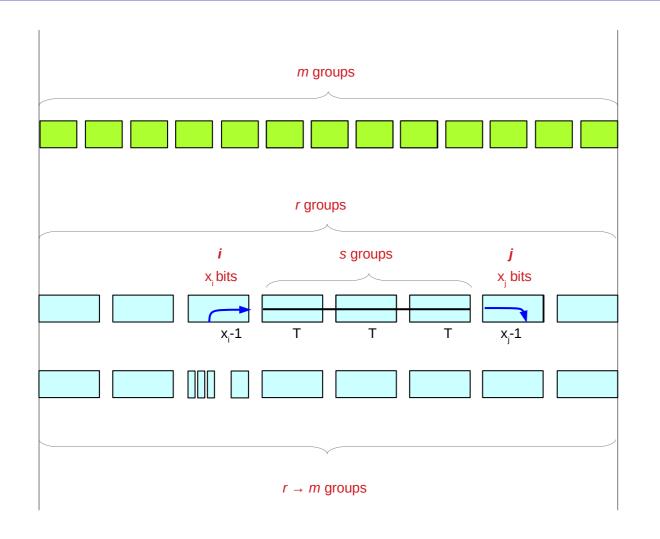

*m* groups – not optimal division *r* groups – optimal division

D = maximum delay

 $rT \le D \le mT$ 

 $r \leq m$ 

if **m** is <u>not</u> optimal, <u>but</u> **r** is


$$(((r +1) +1) +1) \dots \longrightarrow m$$
 contradiction!  $r$  must be  $m$ 

It follows that a signal with delay D

must <u>start</u> in a group *i*, <u>ripple</u> to the <u>end</u> of group *i*,

then skip over s < r groups and

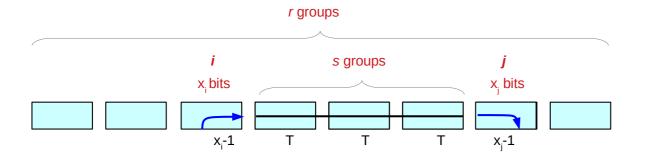either <u>terminate</u>, or <u>ripple</u> through the first few bits of a group j > i.



Oklobdzija: High-Speed VLSI arithmetic units: adders and multipliers

*m* groups – not optimal division *r* groups – optimal division


*D* = maximum delay

 $rT \le D \le mT$ 


 $r \leq m$ 

Let  $x_i$  and  $x_j$  denote the lengths of the *i-th* and *j-th* groups respectively.

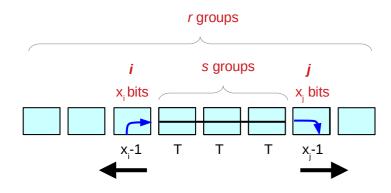Assume that i is chosen as <u>small</u> as possible and j as <u>large</u> as possible. (longer path)



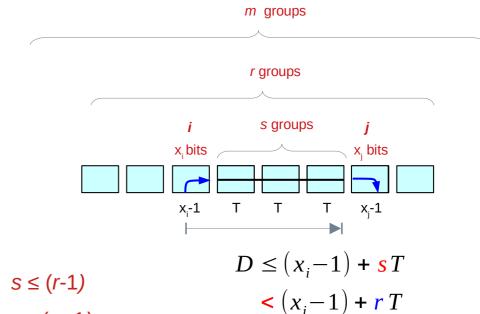A signal <u>originating</u> in group i, <u>rippling</u> to the end of this group i and then skipping over the next s group has delay  $(x_i - 1) + sT$ 



$$D \leq (x_i - 1) + sT$$

$$\leq (x_i - 1) + (r - 1)T$$

$$\leq (x_i - 1) + (m - 2)T.$$

$$s < r \text{ groups} \implies s \leq (r - 1)$$

$$r < m \text{ groups} \implies r \leq (m - 1)$$

$$s < r < m$$
  
 $s \le (r-1) < (m-1)$   
 $s \le (r-1) \le (m-2)$ 

Oklobdzija: High-Speed VLSI arithmetic units: adders and multipliers

if **m** is <u>not</u> optimal, <u>but</u> **r** is

 $<(x_i-1)+mT.$ 

$$\begin{split} D & \leq (x_i - 1) + {}_{S}T \\ & \leq (x_i - 1) + (r - 1)T \\ & \leq (x_i - 1) + (m - 2)T \end{split}$$

$$(m-1)T \le D$$
  
 $D \le (x_i-1) + (m-2)T$ 

$$(m-1)T \le D \le (x_i-1) + (m-2)T$$

$$(m-1)T \le (x_i-1) + (m-2)T$$

$$T \le (x_i - 1)$$

$$T + 1 \le x_i$$


Since  $D \ge (m-1)T$ this implies that  $x_i \ge T+1$ 

Divide group i into two groups such that the group containing the msb has size T.

Since the *i*-th group is the first group in which a signal having maximum delay can <u>originate</u>,

this subdivision does <u>not</u> <u>increase</u> the delay of any carry signal of maximum delay

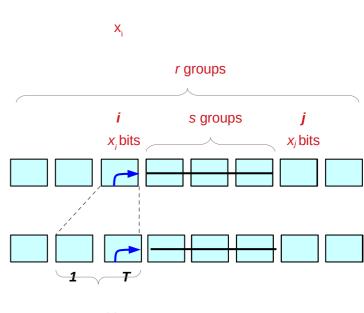However, it increases the <u>number</u> of groups by 1



 $x_i \ge T+1$  bits size

T+1 bits

$$\begin{split} D &\leq (x_i - 1) + sT & (m - 1)T < D \\ &\leq (x_i - 1) + (r - 1)T & D < (x_i - 1) + (m - 2)T \\ &\leq (x_i - 1) + (m - 2)T. & x_i \geq (T + 1) \end{split}$$


Suppose now that a carry signal <u>originates</u> in a group i, <u>ripples</u> to its end, <u>skips</u> over  $s \le r-2$  groups and finally <u>ripples</u> through the first few bits of a group j and terminates.

#### We then have

$$D \le (x_i - 1) + sT + (x_j - 1)$$
  
$$\le x_i + x_j - 2 + (m - 3)T$$

So that either  $x_i \ge T+1$  or  $x_i \ge T+1$ 
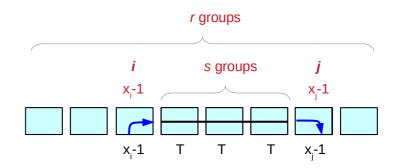
$$s < r$$
 groups  $s < r$  groups  $s \le (r-1)$  groups  $s \le (r-2)$  groups  $r < m$  groups  $r \le (m-1)$  groups  $r \le (m-2)$  groups




$$s < r < m$$

$$s \le (r-1) < (m-1)$$

$$s \le (r-1) \le (m-2)$$

$$s \le (r-2) \le (m-3)$$

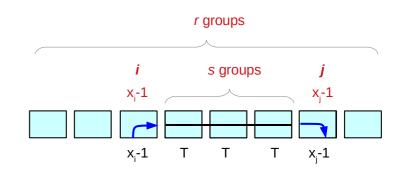

$$D \leq (x_{i}-1) + sT + (x_{j}-1)$$

$$\leq x_{i} + x_{j} - 2 + (r-2)T$$

$$\leq x_{i} + x_{j} - 2 + (m-3)T$$

$$(m-1)T < D$$
 $D < (x_i-1) + (m-2)T \iff x_i \ge (T+1)$ 
 $D < (x_j-1) + (m-2)T \iff x_j \ge (T+1)$ 

So that either  $x_i \ge T+1$  or  $x_j \ge T+1$ 

Oklobdzija: High-Speed VLSI arithmetic units: adders and multipliers


 $s \leq (r-2)$ 

So that either  $x_i \ge T+1$  or  $x_i \ge T+1$ 

This means that we can subdivide one of the groups i, j without increasing D not both of them

Continuing in this way, we can always increase the number *r* of group in an optimal division of a carry chain by 1 without increasing D if r < m

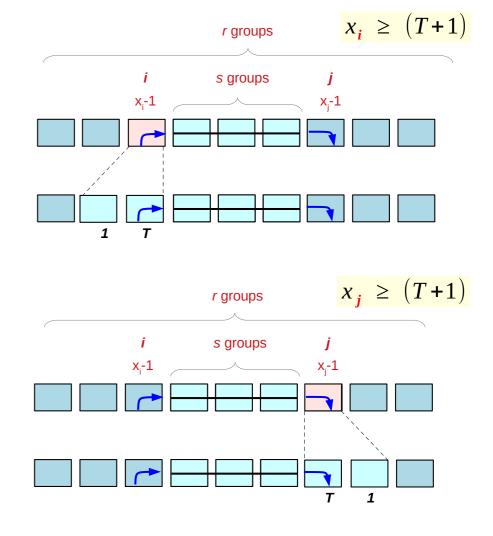This means that we can arrive at an optimal division of the carry chain into *m* groups.




Oklobdzija: High-Speed VLSI arithmetic units: adders and multipliers

6/19/24

$$x_i \geq (T+1) > (T+2) \cdots$$

$$x_i \geq (T+1)$$

$$x_i \geq (T+2)$$

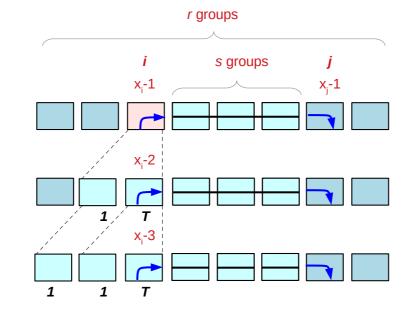

$$D \le (x_i - 1) + sT$$

$$\le (x_i - 1) + (r - 1)T$$


$$\le (x_i - 1) + (m - 2)T$$

$$(m-1)T \le D \le (x_i-1) + (m-2)T$$

if m is <u>not</u> optimal, <u>but</u> r is

$$(((r +1) +1) +1) \dots \longrightarrow m$$

contradiction! m must be r

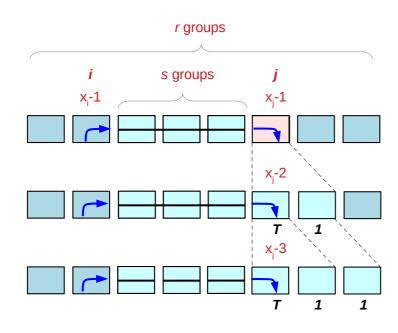

if m is <u>not</u> optimal, <u>but</u> r is

$$(((r +1) +1) +1) \dots \longrightarrow m$$

$$x_{i} \geq (T+1) > (T+2) \cdots$$

$$x_i \geq (T+1)$$


$$x_i \geq (T+2)$$


$$D \le (x_i - 1) + sT$$

$$\le (x_i - 1) + (r - 1)T$$

$$\le (x_i - 1) + (m - 2)T$$

$$(m-1)T \le D \le (x_i-1) + (m-2)T$$

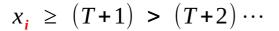


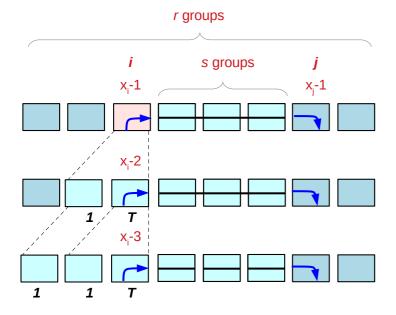

if m is <u>not</u> optimal, <u>but</u> r is  $(((r +1) +1) +1) \dots \longrightarrow m$ contradiction! m must be r

Oklobdzija: High-Speed VLSI arithmetic units: adders and multipliers

$$x_j \geq (T+1) > (T+2) \cdots$$

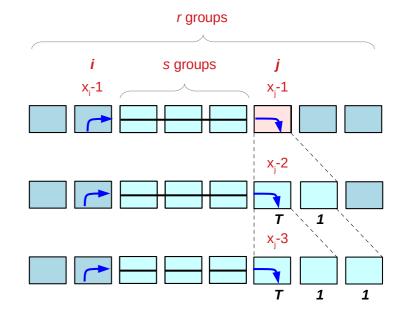

if m is <u>not</u> optimal, <u>but</u> r is  $(((r +1) +1) +1) ... \longrightarrow m$ contradiction! m must be r

Normally, by 2(i) - 2(iii) (m groups) is optimal and its maximum delay D is less than all skip delay mT

 $D \leq mT$ 

To prove this, first, negate that

- m is <u>not</u> by the optimal division, but r is
- D is greater than all skip delay of the optimal division

#### **Assume**

- the scheme by 2(i) 2(iii)
   (*m* groups) is not optimal
- let D be the maximum delay corresponding to an optimal division
- there are r groups in the optimal division.

$$(...(((r+1)+1)+1) ... +1) \rightarrow m : optimal$$

if **m** is <u>not</u> optimal, <u>but</u> **r** is

$$(((r +1) +1) +1) \dots \longrightarrow m$$

contradiction! m must be r

We must then have  $D \ge mT$  which, together with **Lemma 2**, Implies D = mT

This completes the proof of the theorem

*m* groups – not optimal division *r* groups – optimal division

D = maximum delay

rT < D < mT

 $r \leq m$ 

Oklobdzija: High-Speed VLSI arithmetic units: adders and multipliers

#### Lemma 2

Let *D* denote the maximum delay of a carry signal in a *n* bit carry skip adder with group sizes chosen optimally.

$$(m-1)T \leq D \leq mT$$

#### Theorem 1

The scheme 2(i) - 2(iii) given above for dividing the bits of a carry skip adder into groups is optimal for  $2 \le T \le 7$