

BJT Amplifier

Common Emitter Amp (H.11)

20170207

Copyright (c) 2016 - 2017 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".


References

Based


[1] Floyd, Electronic Devices 7th ed

[2] Cook,

[2] en.wikipedia.org

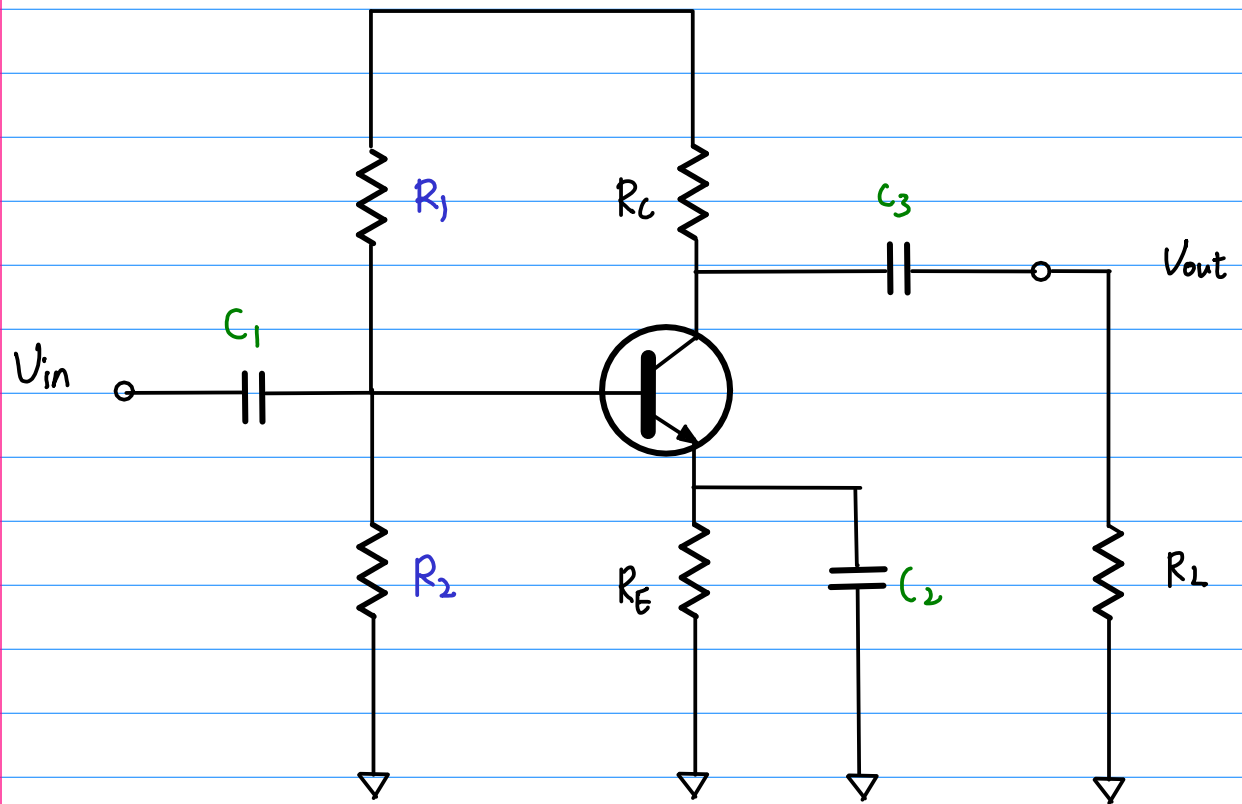

DC Analysis

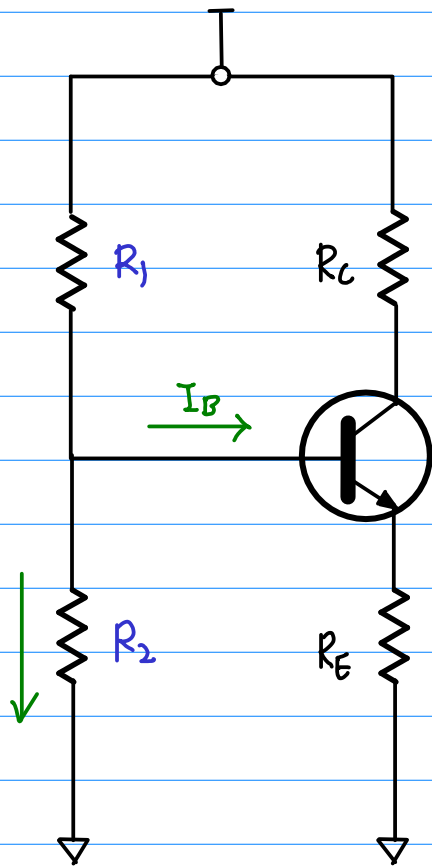

AC Ground



C_1, C_2, C_3 - effectively short

their values are selected



$$\text{s.t. } X_C = \frac{1}{j\omega C} \approx 0 \Omega$$

at the signal frequency (ω)





dc source


dc ground

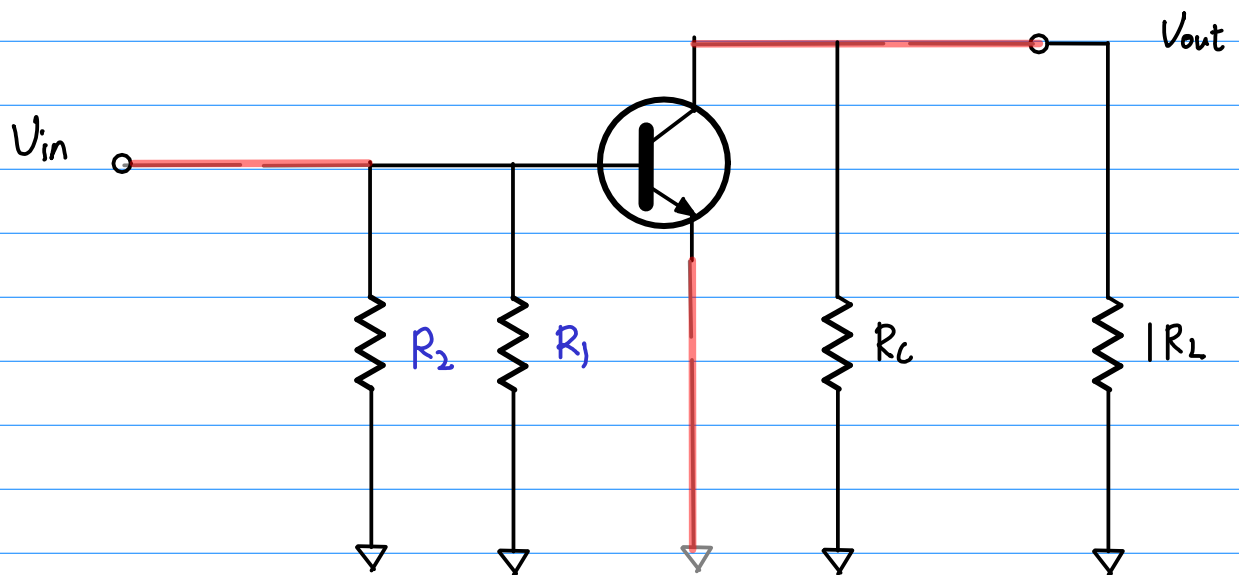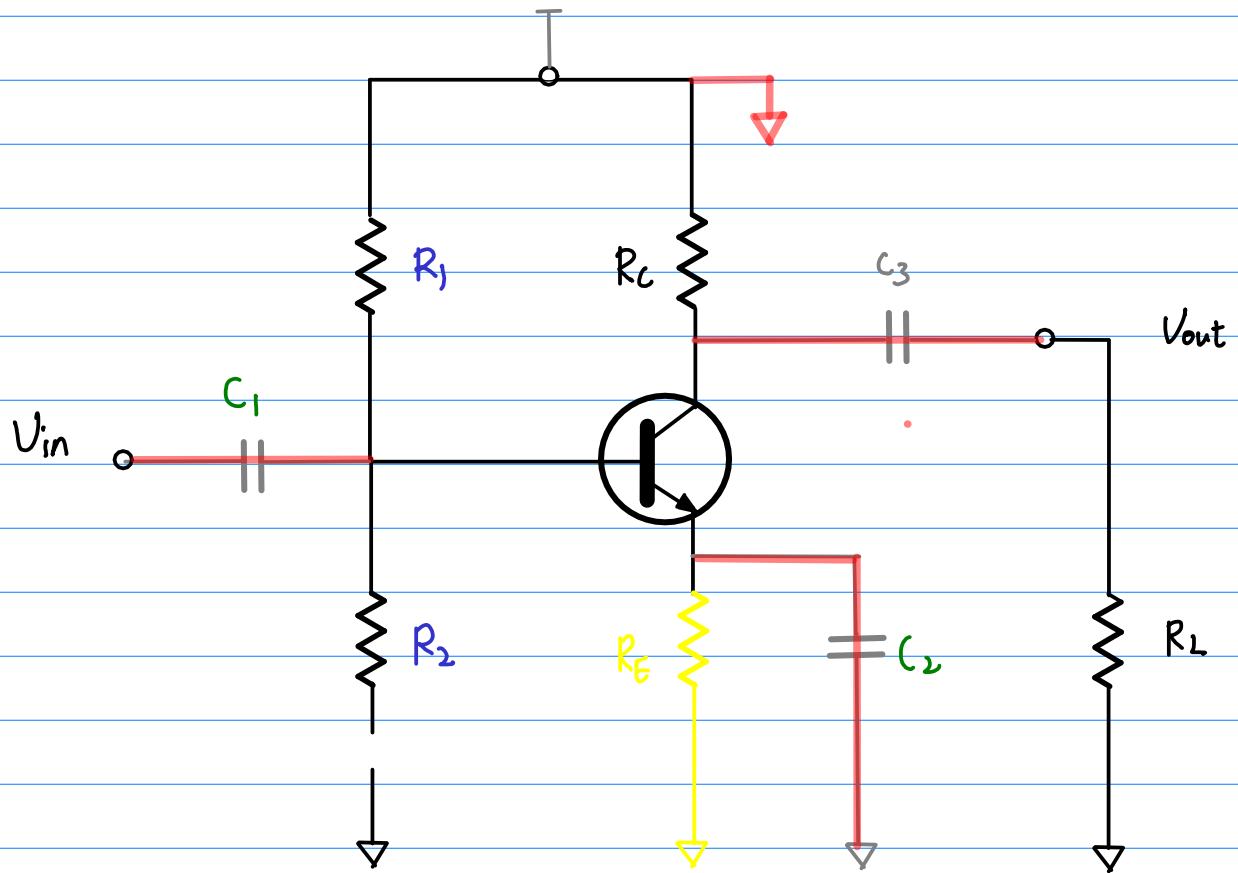



AC Equivalent Circuit

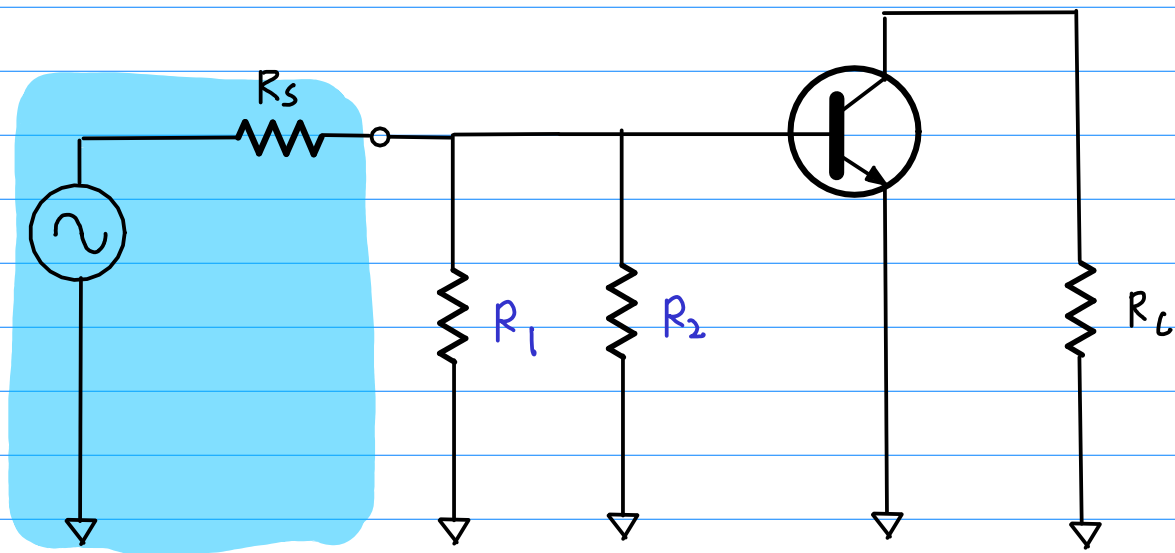
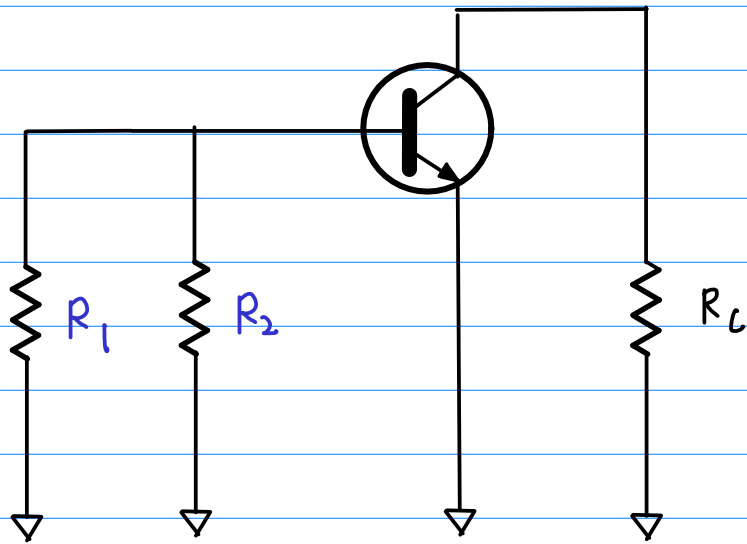


AC source




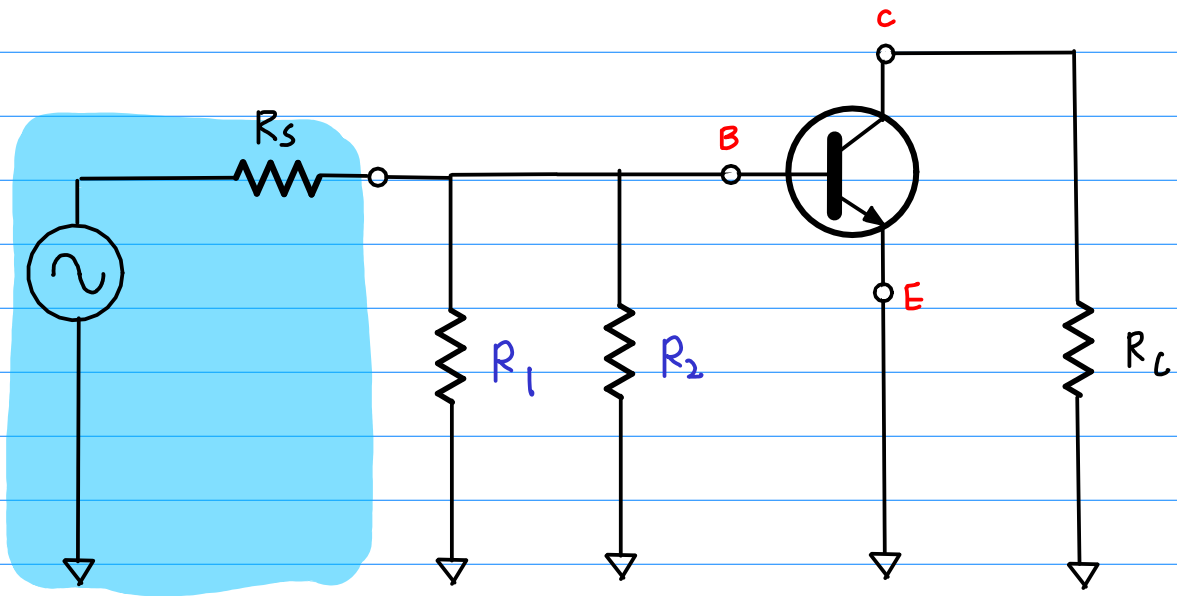


AC source

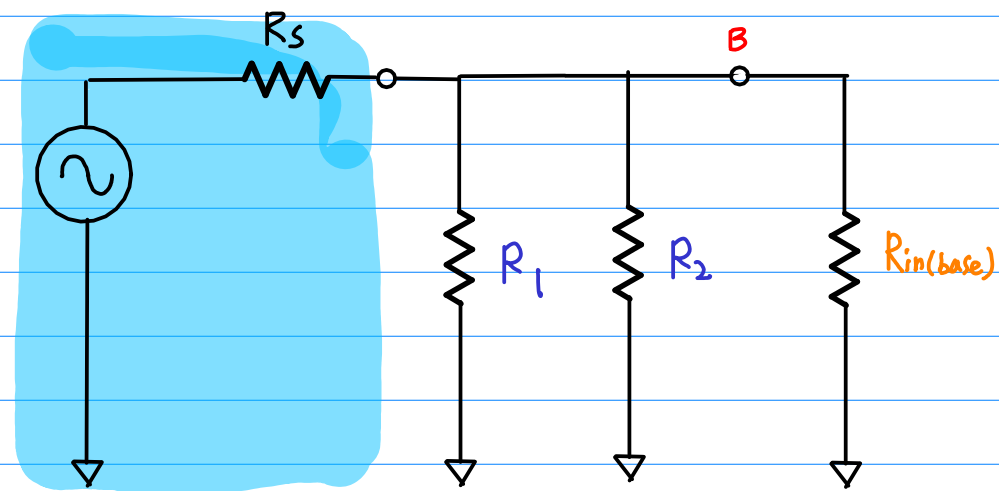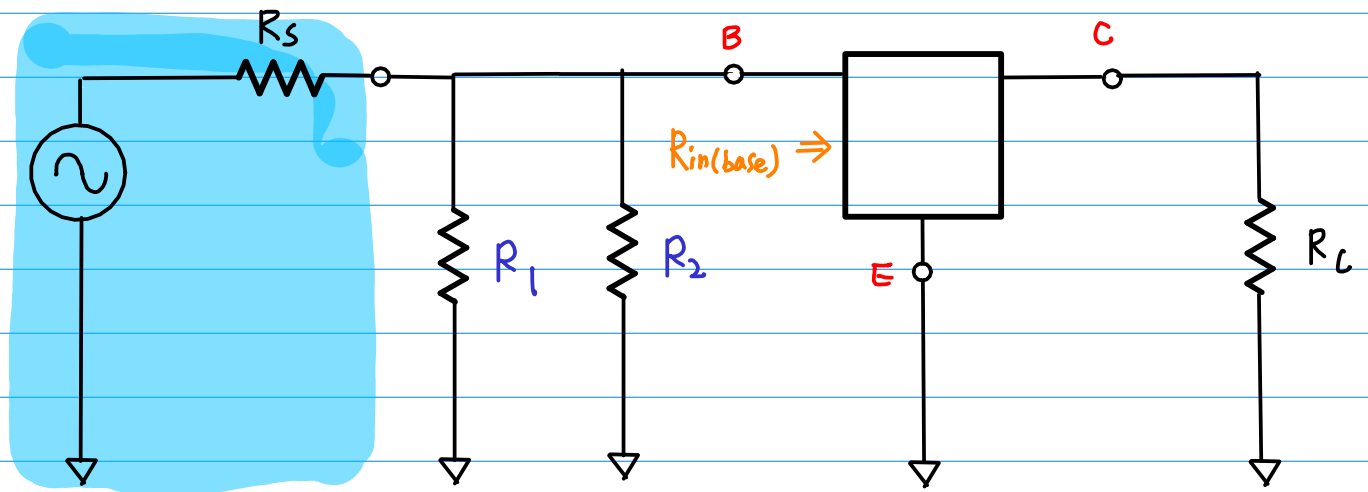


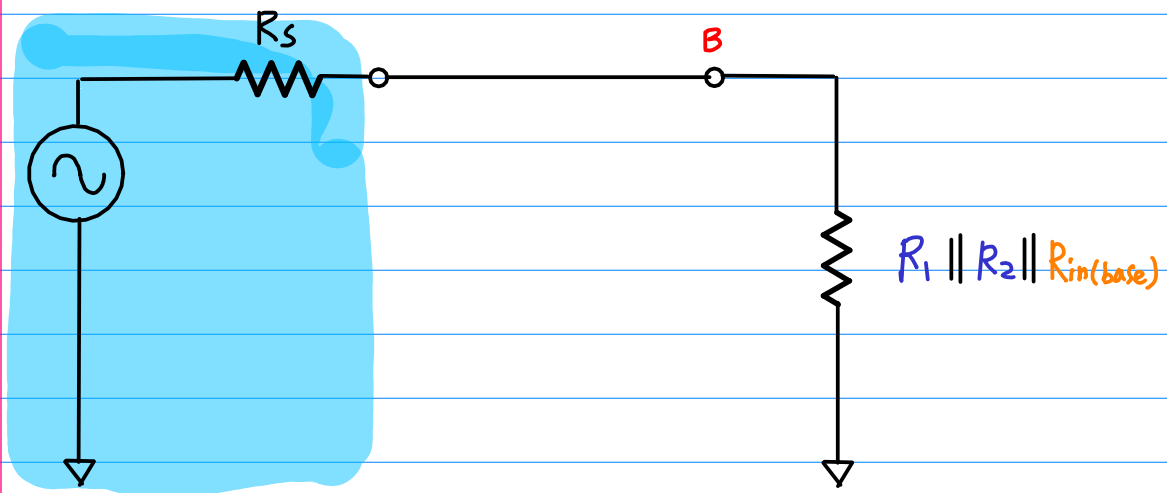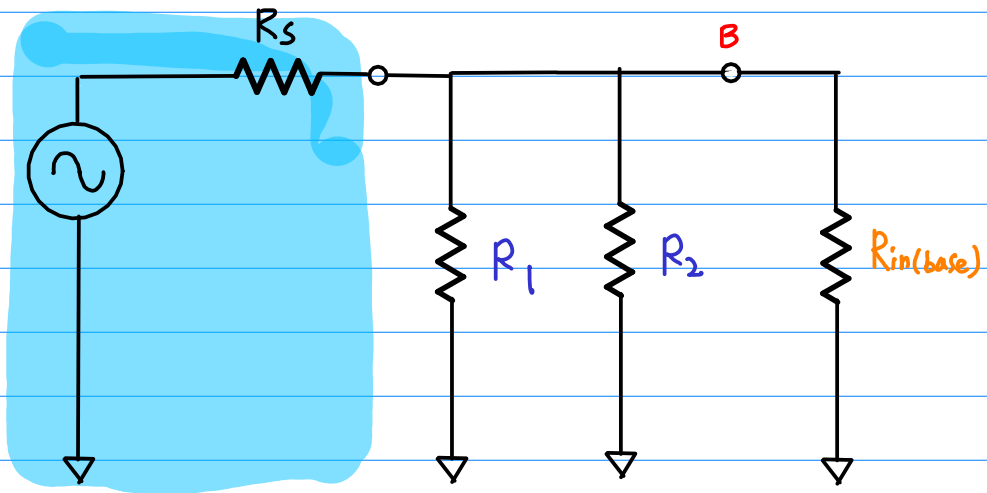


Input Resistance

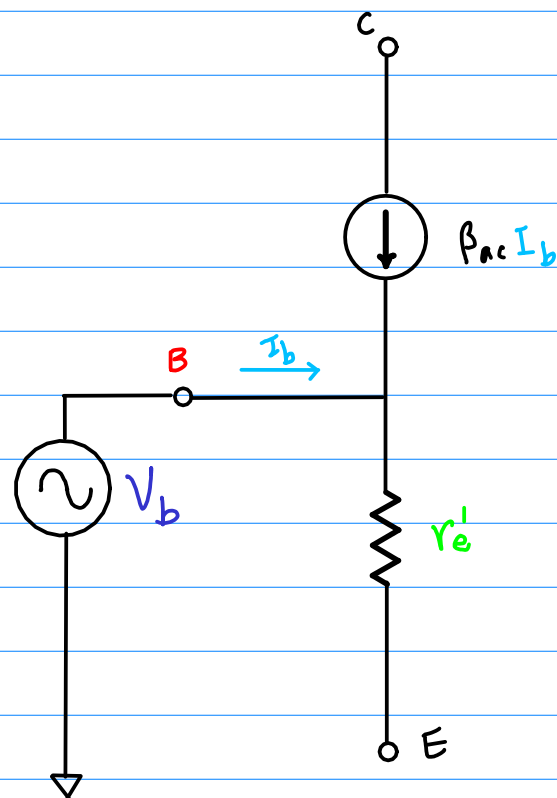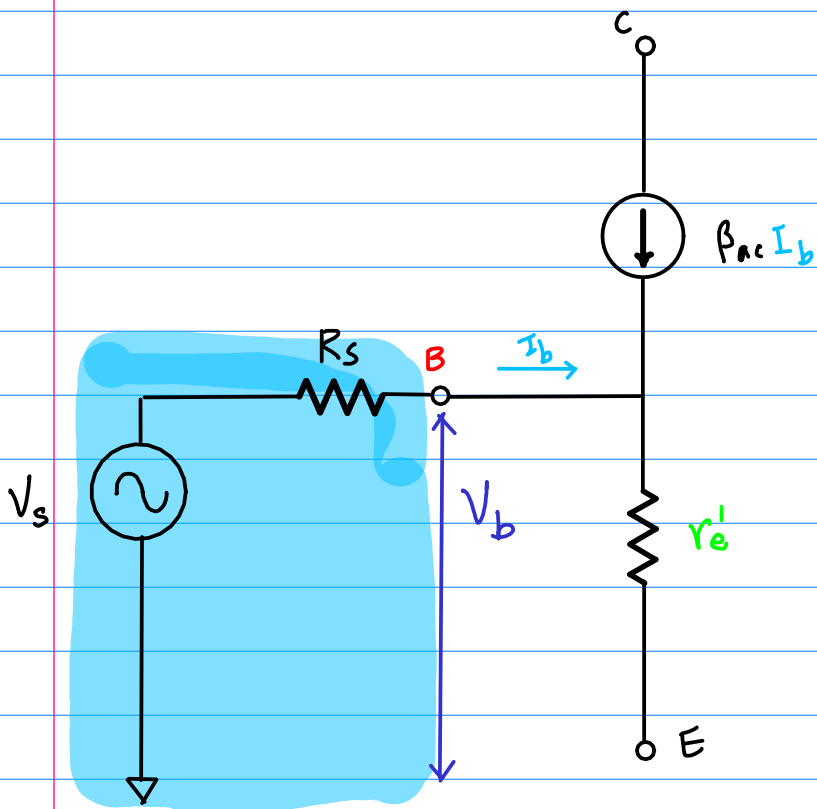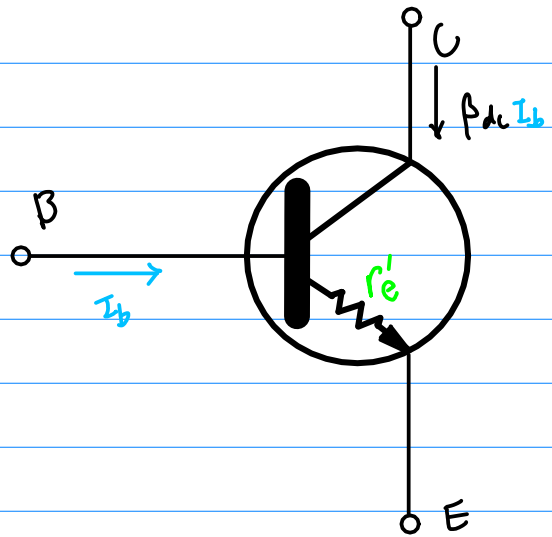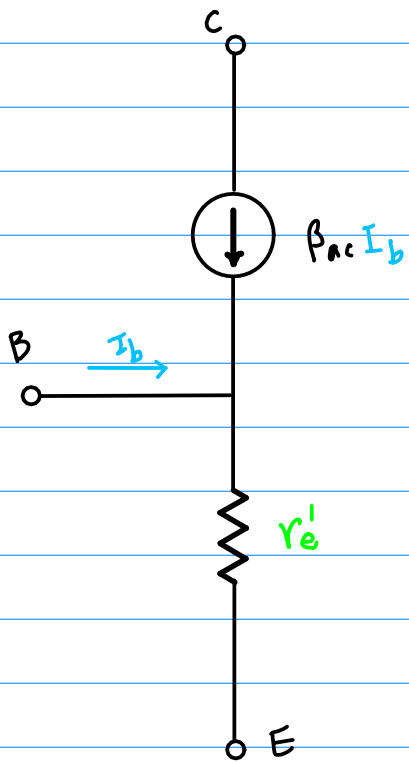



Output Resistance

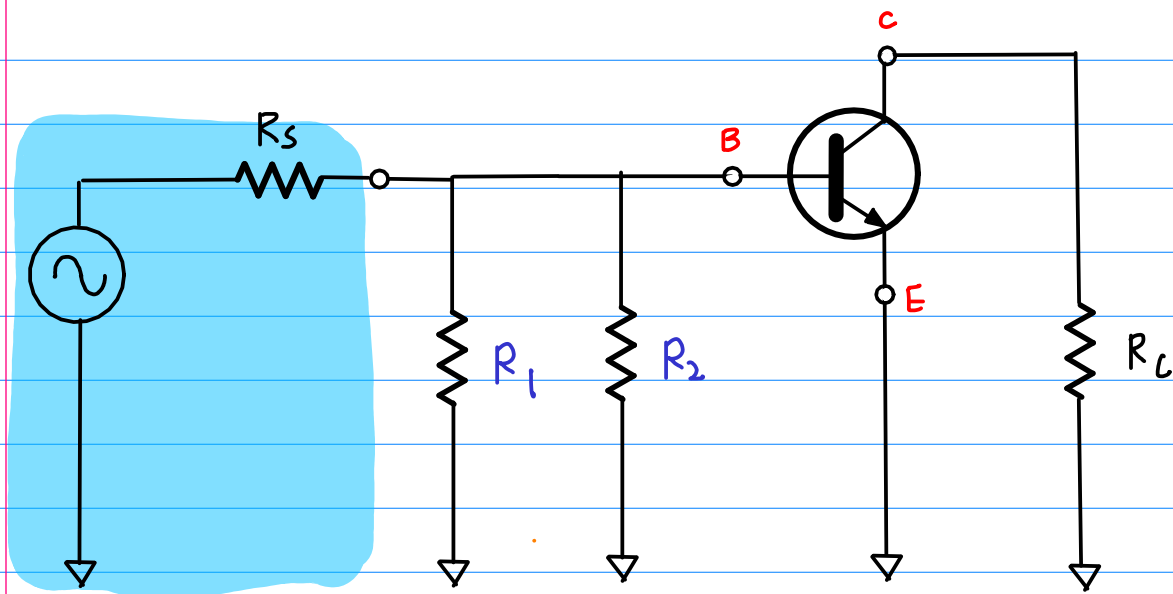



AC source

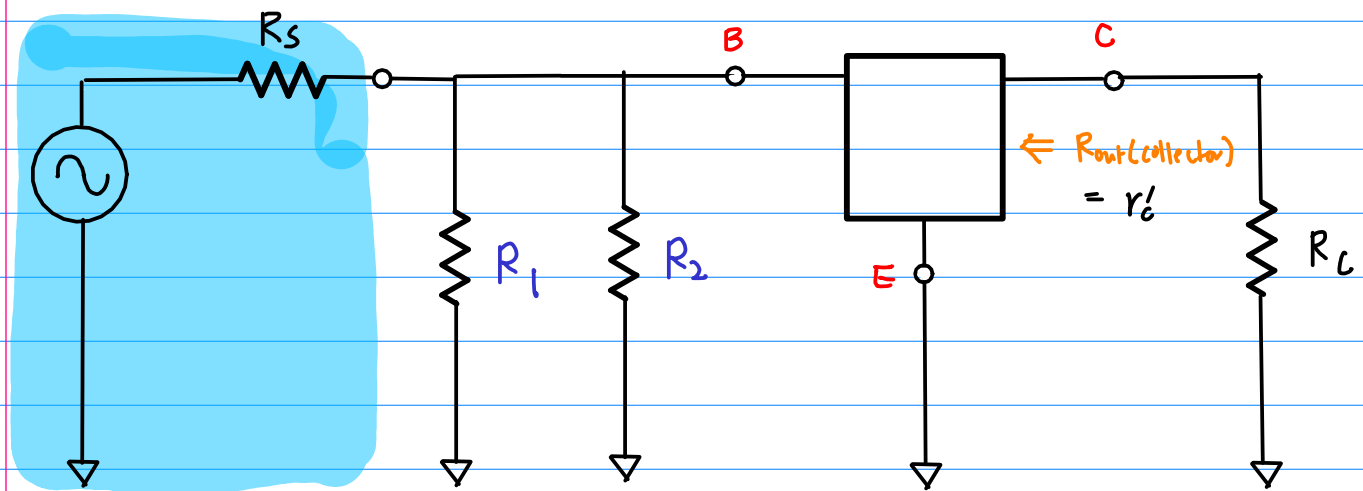
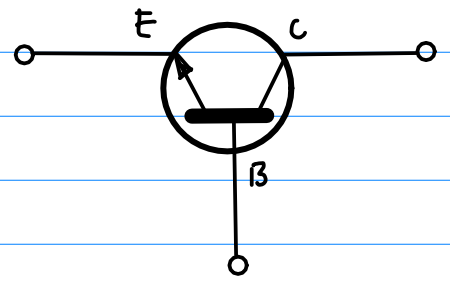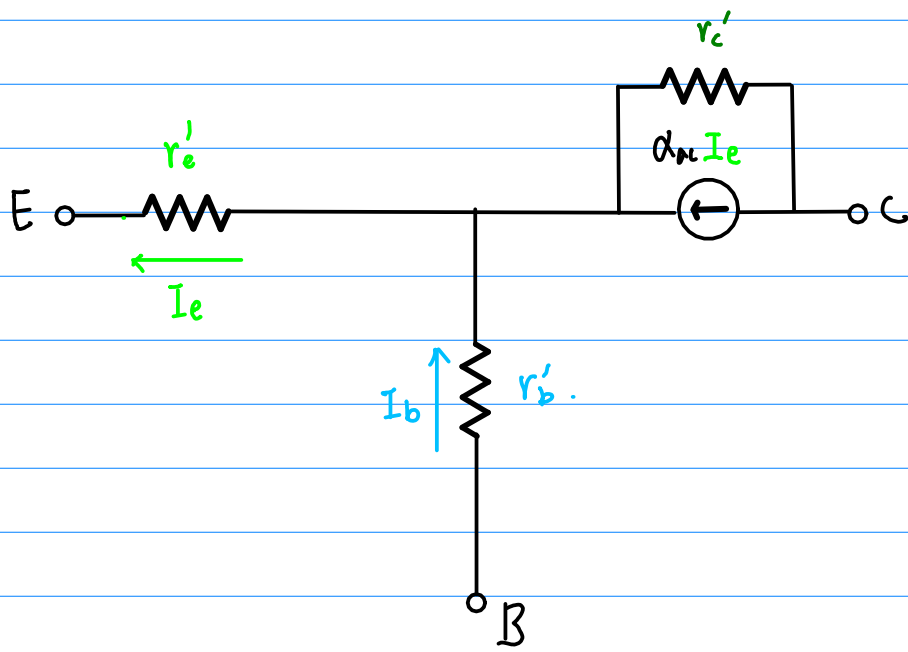
$$R_{out}(\text{collector}) = r'_c \parallel R_C \\ \approx R_C \quad (r'_c \gg R_C)$$




Voltage Gain

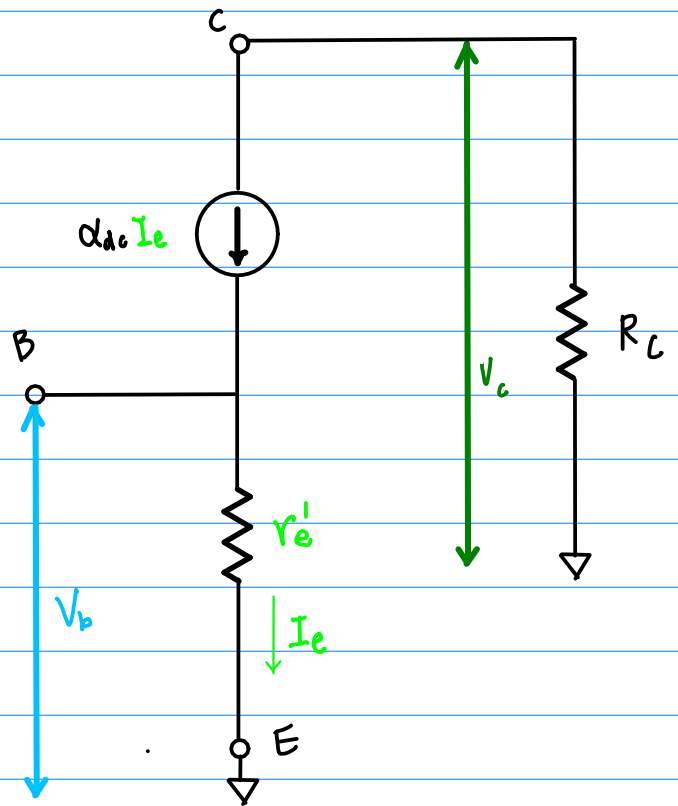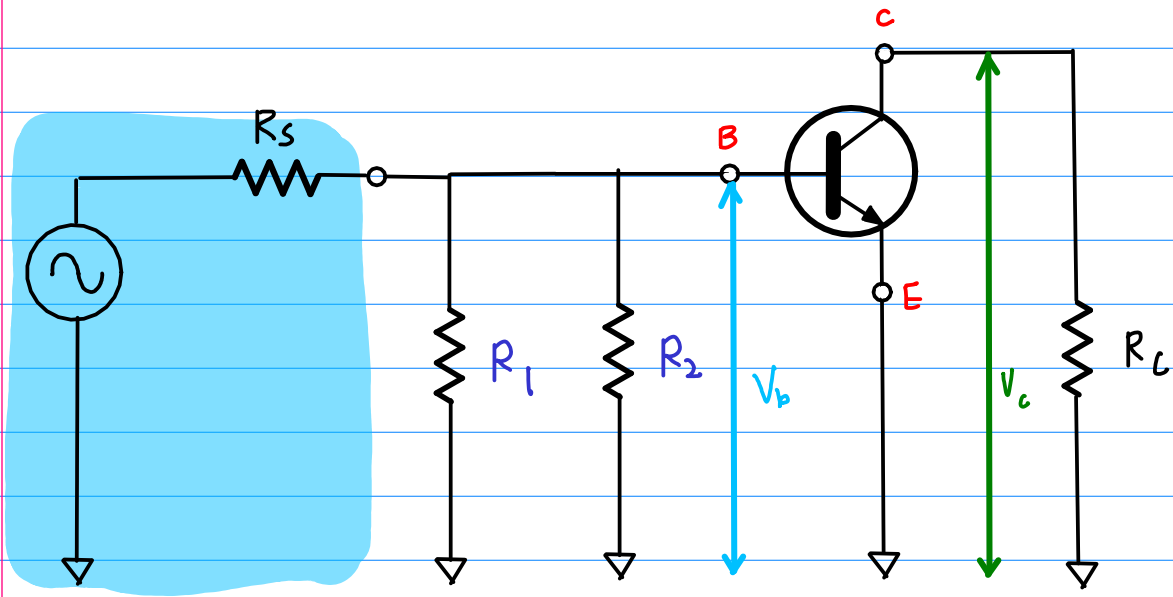



Overall Gain $V_c/V_s = V_b/V_s \times V_c/V_b$


attenuation V_b/V_s

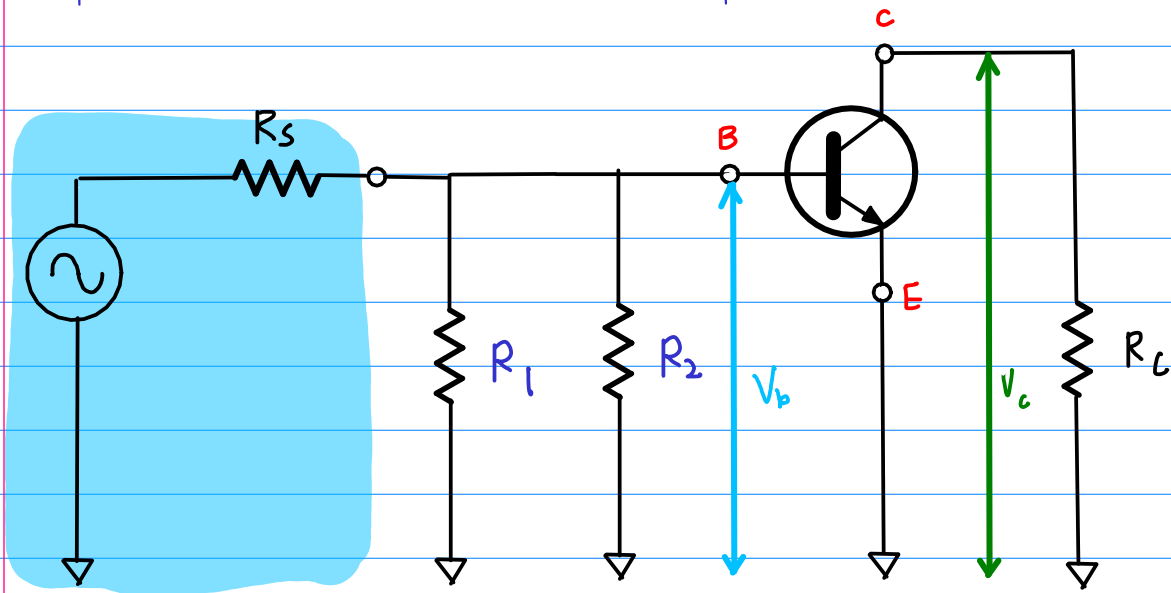


amplifier gain
base-to-collector
 V_c/V_b

Load Effect on the voltage Gain

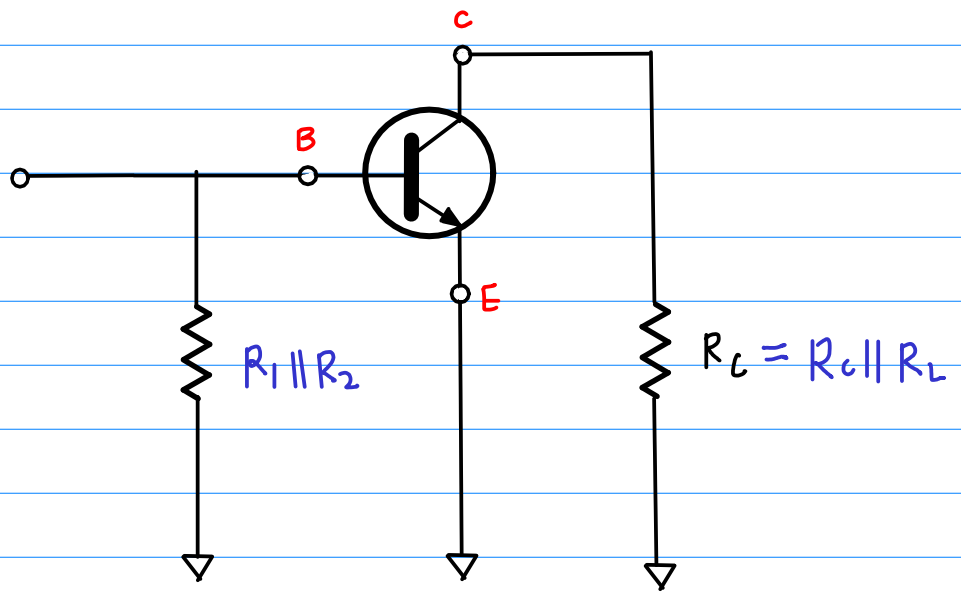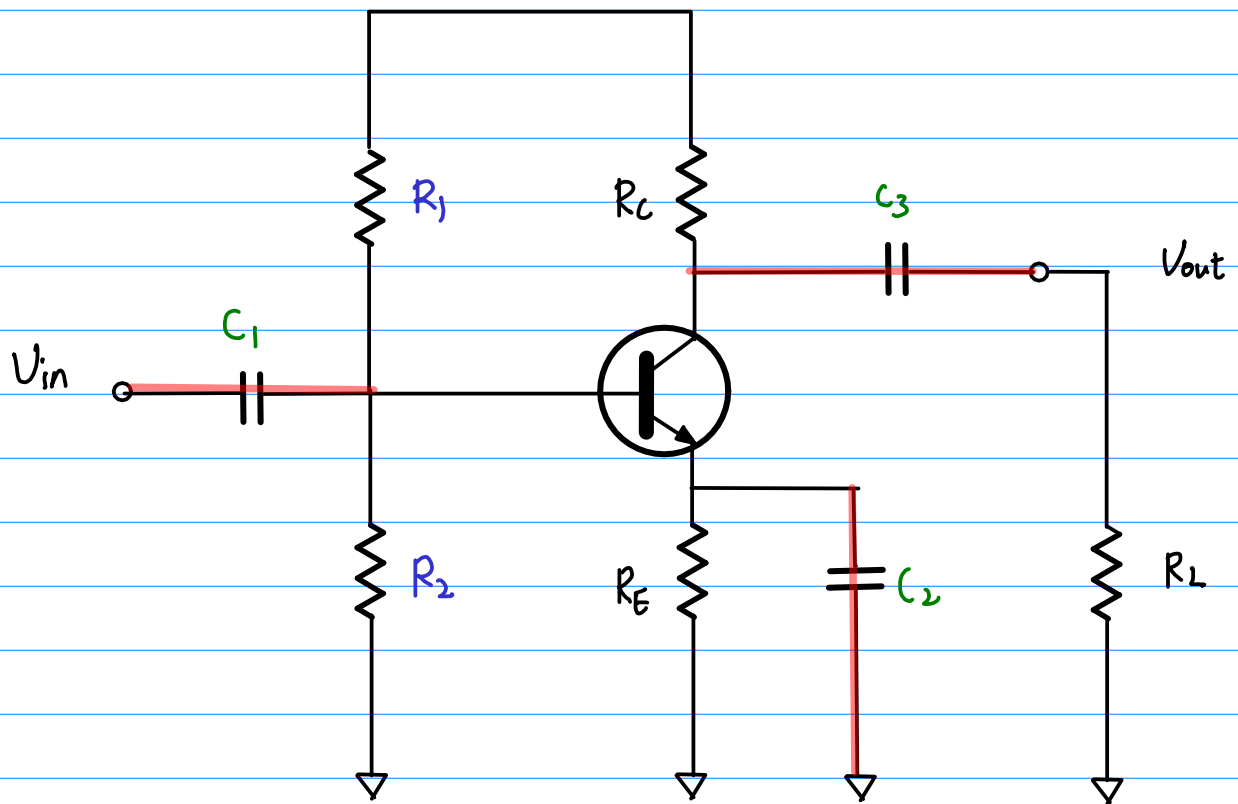

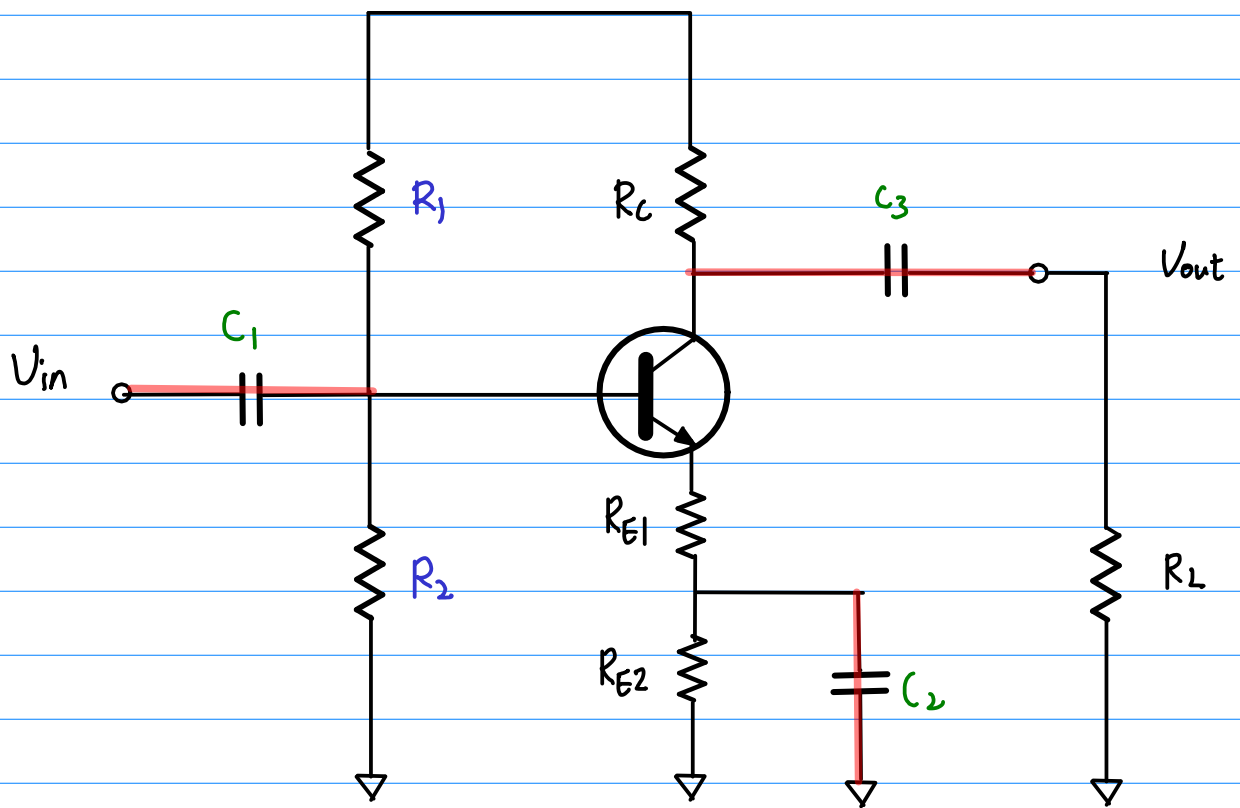

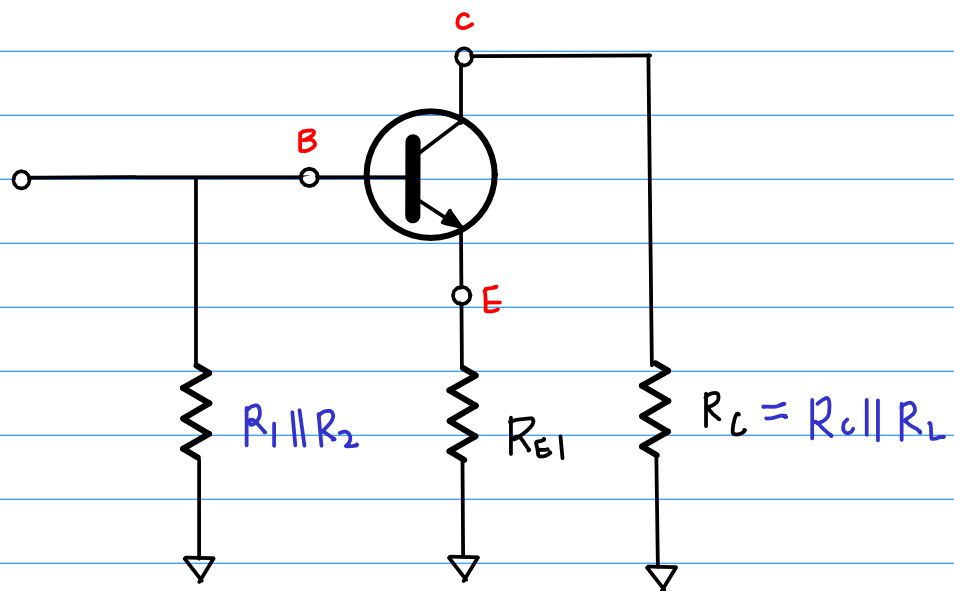bypassed resistance to minimize the effect of $r_e \Rightarrow$ gain stability



Current Gain

