

Tapped Delay

Copyright (c) 2024 - 2019 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".

Please send corrections (or suggestions) to youngwlim@hotmail.com.

This document was produced by using LibreOffice.

Based on

Introduction to Signal Processing

S. J. Ofranidis


The necessities in DSP C Programming

FIR Filter (A.pdf) 20191114

D Flip Flop

Considering the widely used
Edge triggered
D-type Flip Flops

Register

 


Tapped Delay
(1A)

Types of Timing Diagrams


a timing diagram without delays

 https://en.wikiversity.org/wiki/The_necessities_in_Digital_Design



no delay (ideal case)

a timing diagram with delays


 


input delay

output delay $Clk \rightarrow Q$

Setup & Hold Time (1)

 
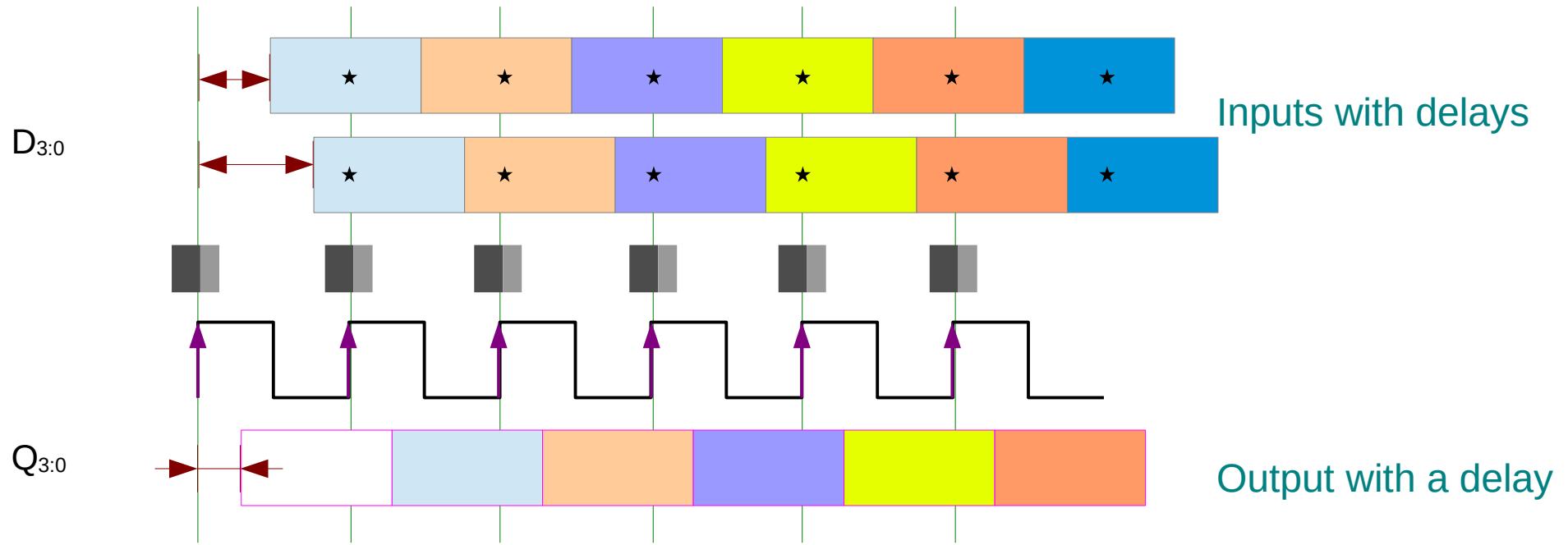
https://en.wikiversity.org/wiki/The_necessities_in_Digital_Design




Master-Slave D FlipFlop – Rising Edge

https://en.wikiversity.org/wiki/The_necessities_in_Digital_Design

Master D Latch

  


Slave D Latch

 


Master-Slave D FlipFlop – Rising Edge

 https://en.wikiversity.org/wiki/The_necessities_in_Digital_Design



Master D Latch

 


Slave D Latch

Using inverted clocks enable
(1) and (2) to be executed sequentially


Master-Slave D FlipFlop – Rising Edge Sampling

https://en.wikiversity.org/wiki/The_necessities_in_Digital_Design

Master D Latch

 

Slave D Latch

 


(1) the current input
 $x(n)$ gets stored
in the master latch

(2) the current content
 $w1(n)$ is clocked out
to the output $y(n)$


Master-Slave D FlipFlop – open and hold

https://en.wikiversity.org/wiki/The_necessities_in_Digital_Design

Master D Latch

 


Master D Latch

 


Slave D Latch

Slave D Latch

Master-Slave D FlipFlop – ideal timing

 


Typical Timing

 


Ideal Timing

Master-Slave D FlipFlop – DSP C model

 


Hardware model

 

DSP C model

Master-Slave D FlipFlop – DSP C model

 

DSP C model

(1) $w1(n) = x(n-1)$

WR $w1(n)$

Input

(2) $y(n) = w1(n)$

RD $w1(n)$

Internal State

No RAW (read after write) hazard

but we must simulate the parallel hardware by a sequential code


at time n ,
use only $x(n)$ and $y(n)$

Output

Master-Slave D FlipFlop – DSP C model

at the time n

RAW (read after write)

 

Input

$$(2) \quad y(n) = w1(n)$$

RD $w1(n)$

Internal State

$$(1) \quad w1(n) = x(n)$$

WR $w1(n)$

No **RAW** (read after write) hazard

Output

$$y(n) = w1(n)$$

$$w1(n) = x(n)$$

$$\overline{w1(n+1) = w1(n)}$$

$$y(n+1) = w1(n+1)$$

$$w1(n+1) = x(n+1)$$


$$\overline{w1(n+2) = w1(n+1)}$$

$$y(n+2) = w1(n+2)$$

$$w1(n+2) = x(n+2)$$

DSP C model

Simultaneous RD and WR actions

 

current content	$w1(n)$	$= x(n-1)$
next content	$w1(n+1)$	$= x(n)$

at time n

$$\begin{aligned}y(n) &= w1(n) \\w1(n+1) &= x(n)\end{aligned}$$

at time $n+1$

$$\begin{aligned}y(n+1) &= w1(n+1) \\w1(n+2) &= x(n+1)\end{aligned}$$

read internal state

update internal state


at time n ,

- 1) the content of the register $w1(n)$
becomes the output $y(n)$
- 2) the input $x(n)$ is saved and
becomes the new content $w1(n+1)$

RD access of $w1(n) = x(n-1)$

WR access of $w1(n+1) = x(n)$

 Current content $w1(n)$ and current input $x(n)$





current content	$w1(n)$	$= x(n-1)$
next content	$w1(n+1)$	$= x(n)$


a register holding the previous input sample $x(n-1)$

  - (1) the current content $x(n-1)$ is clocked out to the output
- (2) the current input $x(n)$ gets stored in the register



It will be held for one sampling instant and become the output at the next time $n+1$



 Current content $w1(n)$ and current input $x(n)$




current content	$w1(n)$	$= x(n-1)$
next content	$w1(n+1)$	$= x(n)$

  

*simulate a clocked hardware
ignoring delay constraints in hardware*

zero-delay simulation

Delay element modeling

 

$w1(n) \rightarrow y(n)$	$y(n) = w1(n)$ (1) RD old $w1$
$x(n) \rightarrow w1(n+1)$	$w1(n+1) = x(n)$ (2) WR new $w1$

The content of the delay register at time n as the **internal state** of the filter by

internal state at time n

$$w1(n) = x(n-1)$$

internal state at time $n+1$


$$w1(n+1) = x(n)$$

output at time n

$$y(n) = w1(n)$$

RD before WR

WAR (Write after Read) Access

 

simulate a clocked hardware ignoring delay constraints in hardware


zero-delay simulation

WAR (Write after Read)

$y(n) = w1(n)$	(1) RD	old w1
$w1(n+1) = x(n)$	(2) WR	new w1
$y(n+1) = w1(n+1)$	(1) RD	old w1
$w1(n+2) = x(n+1)$	(2) WR	new w1


$w1(n+1) = x(n)$	(2) WR	new w1
$y(n) = w1(n)$	(1) RD	old w1
$w1(n+2) = x(n+1)$	(2) WR	new w1
$y(n+1) = w1(n+1)$	(1) RD	old w1

WAR (Write after Read) Violation

 


DSP C model

Single Delay

 

 
$$y(n) = w1(n) \quad (1) \text{ RD} \quad \xrightarrow{\text{blue arrow}}$$
$$w1(n+1) = x(n) \quad (2) \text{ WR} \quad \xrightarrow{\text{yellow arrow}}$$




n	$x(n)$	$w1(n)$	$y(n)$
0	x_0	0	0
1	x_1	x_0	x_0
2	x_2	x_1	x_1
3	x_3	x_2	x_2
4	x_4	x_3	x_3

Double Delay


 

 
$$\begin{aligned} y(n) &= w2(n) \\ w2(n+1) &= w1(n) \\ w1(n+1) &= x(n) \end{aligned}$$



n	x(n)	w1(n)	w2(n)	y(n)
0	x0	0	0	0
1	x1	x0	0	0
2	x2	x1	x0	x0
3	x3	x2	x1	x1
4	x4	x3	x2	x2


Triple Delay

  

n	$x(n)$	$w1(n)$	$w2(n)$	$w3(n)$	$y(n)$
0	x_0	0	0	0	0
1	x_1	x_0	0	0	0
2	x_2	x_1	x_0	0	0
3	x_3	x_2	x_1	x_0	x_0
4	x_4	x_3	x_2	x_1	x_1

$$\begin{aligned}
 y(n) &= w3(n) \\
 w3(n+1) &= w2(n) \\
 w2(n+1) &= w1(n) \\
 w1(n+1) &= x(n)
 \end{aligned}$$

Single Delay – IO Equations

 

single delay

$y(n) = w1(n)$	output
$w1(n+1) = x(n)$	input


double delay

$y(n) = w2(n)$	output
$w2(n+1) = w1(n)$	
$w1(n+1) = x(n)$	input

triple delay

$y(n) = w3(n)$	output
$w3(n+1) = w2(n)$	
$w2(n+1) = w1(n)$	
$w1(n+1) = x(n)$	input

Double Delay – IO Equations

 

$$y_1(n) = w_1(n)$$

$$w_1(n+1) = x(n)$$

$$y(n) = w_2(n)$$

$$w_2(n+1) = y_1(n)$$

$$y_1(n) = w_1(n)$$

$$w_2(n+1) = y_1(n)$$

$$\underline{w_2(n+1) = w_1(n)}$$

$$y(n) = w_2(n)$$


$$w_2(n+1) = w_1(n)$$

$$w_1(n+1) = x(n)$$

output

input

Triple Delay – IO Equations

 

$$y_1(n) = w_1(n)$$

$$w_1(n+1) = x(n)$$

$$y_2(n) = w_2(n)$$

$$w_2(n+1) = y_1(n)$$

$$y(n) = w_3(n)$$

$$w_3(n+1) = y_2(n)$$

$$y_1(n) = w_1(n)$$

$$w_2(n+1) = y_1(n)$$

$$\underline{w_2(n+1) = w_1(n)}$$

$$y_2(n) = w_2(n)$$

$$w_3(n+1) = y_2(n)$$

$$\underline{w_3(n+1) = w_2(n)}$$

$$y(n) = w_3(n)$$

$$w_3(n+1) = w_2(n)$$

$$w_2(n+1) = w_1(n)$$


$$\underline{w_1(n+1) = x(n)}$$

output

input


Delay C Model

Timing Chart

 


$$\begin{aligned} y(n) &= w2(n) \\ w2(n+1) &= w1(n) \\ w1(n+1) &= x(n) \end{aligned}$$

Register Transfer

 

DSP C Model for simulation

 

$$\begin{aligned} y &= w2 \\ w2 &= w1 \\ w1 &= x \end{aligned}$$


$$\begin{aligned} y[n] &= w[2] \\ w[0] &= x[n] \\ w[2] &= w[1] \\ w[1] &= w[0] \end{aligned}$$

IO Equations for the Triple Delay (1)

$y(n) = w_2(n)$
 $w_0(n) = x(n)$
 $w_2(n+1) = w_1(n)$
 $w_1(n+1) = w_2(n)$

$D = 2, 1$


 
$y[n] = w[2]$ // get the output
 $w[0] = x[n]$ // put the input
 $w[2] = w[1]$ // shift
 $w[1] = w[0]$ // shift



delay.c

```
/* delay.c - delay by D time samples */  
/* w[0] = input, w[D] = output */
```

  
```
void delay(int D, double *w)  
{  
    int i;  
  
    for (i=D; i>=1; i--)  
        w[i] = w[i-1];  
  
    // reverse-order updating  
}
```



Using the delay function

```
double *w;  
w = (double *) calloc(D+1, sizeof(double)); // (D+1)-dimensional
```
 
```
for (n = 0; n < Ntot; n++) {  
    y[n] = w[D];           // (1) write output  
    w[0] = x[n];           // (2) read input  
    delay(D, w);         // (3) update delay line  
}
```



Delay Functions

$$y(n) = w_1(n)$$

$$w_1(n+1) = x(n)$$

$$y(n) = w_2(n)$$

$$w_2(n+1) = w_1(n)$$

$$w_1(n+1) = x(n)$$

$$y(n) = w_3(n)$$

$$w_3(n+1) = w_2(n)$$

$$w_2(n+1) = w_1(n)$$

$$w_1(n+1) = x(n)$$

$$y(n) = w_D(n)$$

$$w_0(n) = x(n)$$

$$w_i(n+1) = w_{i-1}(n),$$

$$i = D, D-1, \dots, 2, 1$$


time index : n

memory location : W_i

memory index : i

$$w_i(n+1) = w_{i-1}(n)$$

 the current value at w_{i-1}
will become
the next value at w_i




Holding a delayed input sequence

$$w_0(n) = x(n)$$


$$w_1(n) = x(n-1) = w_0(n-1)$$

$$w_2(n) = x(n-2) = w_1(n-1)$$

$$w_3(n) = x(n-3) = w_2(n-1)$$

 

Single Delay (1)

 

$$[x_0, x_1, x_2, x_3, \dots] \rightarrow [0, x_0, x_1, x_2, x_3, \dots]$$

for each input sample x do:

$$y := w_1$$

$$w_1 := x$$

$$w_1(n) = x(n-1) \quad (\text{internal state at time } n)$$

$$w_1(n+1) = x(n) \quad (\text{internal state at time } n+1)$$

$$y(n) = w_1(n) \quad n \quad x(n) \quad w_1(n) \quad y(n)$$

$$w_1(n+1) = x(n) \quad 0 \quad x_0 \quad 0 \quad 0$$

$$1 \quad x_1 \quad x_0 \quad x_0$$


$$y(n+1) = w_1(n+1) \quad 2 \quad x_2 \quad x_1 \quad x_1$$

$$w_1(n+2) = x(n+1) \quad 3 \quad x_3 \quad x_2 \quad x_2$$

$$4 \quad x_4 \quad x_3 \quad x_3$$

$$w_1(0) = 0$$

Double Delay (1)

 

$$\begin{aligned} w_2(n) &= w_1(n-1) &= x((n-1)-1) &= x(n-2) \\ w_1(n) &= x(n-1) \end{aligned}$$


$[x_0, x_1, x_2, x_3, \dots] \rightarrow [0, x_0, x_1, x_2, x_3, \dots]$

for each input sample x do:

$y := w_2$
$w_2 := w_1$
$w_1 := x$

$w_2(n+1) = w_1(n)$	n	$x(n)$	$w_1(n)$	$w_2(n)$	$y(n)$
$w_1(n+1) = x(n)$	0	x_0	0	0	0
	1	x_1	x_0	0	0
$y(n) = w_2(n)$	2	x_2	x_1	x_0	x_0
$w_2(n+1) = w_1(n)$	3	x_3	x_2	x_1	x_1
$w_1(n+1) = x(n)$	4	x_4	x_3	x_2	x_2
$w_1(0) = 0$					

Triple Delay (1)

 

$[x_0, x_1, x_2, x_3, \dots] \rightarrow [0, x_0, x_1, x_2, x_3, \dots]$

for each input sample x do:

$y := w_3$
$w_3 := w_2$
$w_2 := w_1$
$w_1 := x$

$$w_3(n) = w_2(n-1) = w_1(n-2) = x(n-3)$$

$$w_2(n) = w_1(n-1)$$

$$w_1(n) = x(n-1)$$

$$w_3(n+1) = w_2(n) \quad n \quad x(n) \quad w_1(n) \quad w_2(n) \quad y(n)$$

$$w_2(n+1) = w_1(n) \quad 0 \quad x_0 \quad 0 \quad 0 \quad 0$$

$$w_1(n+1) = x(n) \quad 1 \quad x_1 \quad x_0 \quad 0 \quad 0$$

$$2 \quad x_2 \quad x_1 \quad x_0 \quad x_0$$


$$y(n) = w_3(n) \quad 3 \quad x_3 \quad x_2 \quad x_1 \quad x_1$$

$$w_3(n+1) = w_2(n) \quad 4 \quad x_4 \quad x_3 \quad x_2 \quad x_2$$

$$w_2(n+1) = w_1(n)$$

$$w_1(n+1) = x(n)$$

D Unit Delay (1)

 

$$w_i(n) = w_{i-1}(n-1) \quad \text{for } i = 1, 2, \dots, D$$

$$w_3(n+1) = w_2(n)$$

$$w_2(n+1) = w_1(n)$$

$$w_1(n+1) = x(n)$$

$$y(n) = w_D(n)$$

$$w_0(n) = x(n)$$

$$w_i(n+1) = w_{i-1}(n)$$

$$i = D, D-1, \dots, 2, 1$$

$[x_0, x_1, x_2, x_3, \dots] \rightarrow [0, x_0, x_1, x_2, x_3, \dots]$

for each input sample x do:

$$y := w_D$$

$$w_0 := x$$

$$w_0 := x$$

for $i = D, D-1, \dots, 1$ do:

$$w_i := w_{i-1}$$

for each input sample w_0 do:

for $i = D, D-1, \dots, 1$ do:

$$w_i := w_{i-1}$$

$$n \quad x(n) \quad w_1(n) \quad w_2(n) \quad y(n)$$

$$0 \quad x_0 \quad 0 \quad 0 \quad 0$$

$$1 \quad x_1 \quad x_0 \quad 0 \quad 0$$

$$2 \quad x_2 \quad x_1 \quad x_0 \quad x_0$$

$$3 \quad x_3 \quad x_2 \quad x_1 \quad x_1$$

$$4 \quad x_4 \quad x_3 \quad x_2 \quad x_2$$

D Unit Delay (1)

```
/* delay.c - delay by D time samples */  
void delay(int D, double *w)      w[0] = input, w[D] = output  
{  
    int i;  
  
    for (i=D; i>=1; i--)          reverse-order updating  
        w[i] = w[i-1];  
}
```

dot

```
/* dot.c - dot product of two length-(M+1) vectors */
double dot(int M, double *h, double *w)      Usage: y = dot(M, h, w);
{                                              h = filter vector, w = state vector
    int i;
    double y;

    for (y=0, i=0; i<=M; i++)                  M = filter order
        y += h[i] * w[i];                      compute dot product

    return y;
}
```

$$y = h_0 w_0 + h_1 w_1 + \dots + h_M w_M = [h_0, h_1, \dots, h_M] \begin{bmatrix} w_0 \\ w_1 \\ \vdots \\ w_M \end{bmatrix} = \mathbf{h}^T \mathbf{w}$$

Direct Form

Considering the widely used
Edge triggered
D-type Flip Flops

$$H(z) = \frac{N(z)}{D(z)} = \frac{b_0 + b_1 z^{-1} + b_2 z^{-2}}{1 + a_1 z^{-1} + a_2 z^{-2}}$$

$$y_n = -a_1 y_{n-1} - a_2 y_{n-2} + b_0 x_n + b_1 x_{n-1} + b_2 x_{n-2}$$

References

- [1] S. J. Ofranidis , Introduction to Signal Processing