

CORDIC Background (2B)

- FPGA Architecture
-

Copyright (c) 2010, 2011 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".


Please send corrections (or suggestions) to youngwlim@hotmail.com.

This document was produced by using OpenOffice and Octave.

CORDIC Background

1.A survey of CORDIC algorithms for FPGAs, Ray Andraka,
www.andraka.com/cordic.htm

Bit-Parallel CORDIC: Structure

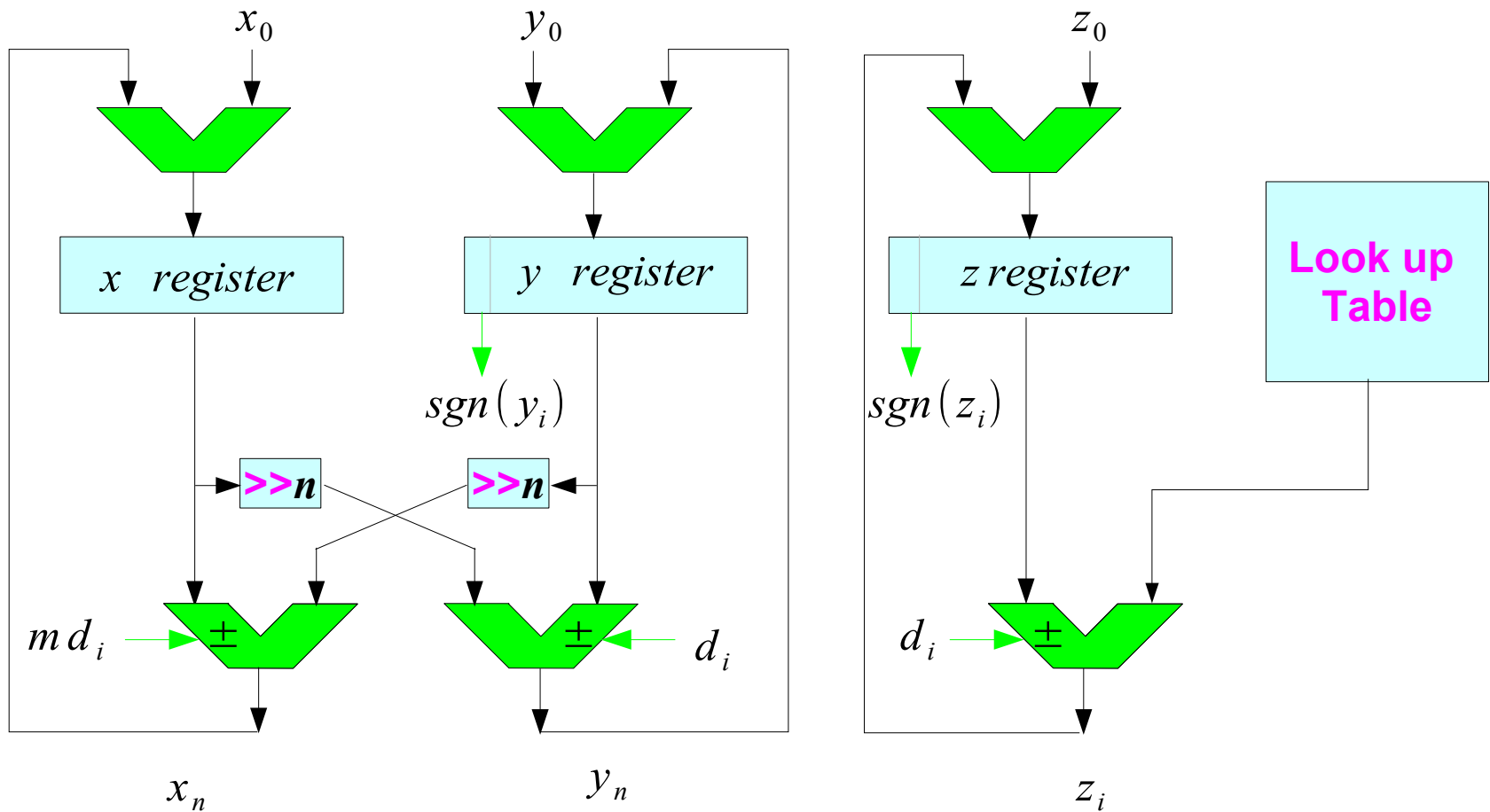

Bit-Parallel CORDIC: Decision Function

Decision Function d_i

In rotation mode

$$\begin{aligned}x_{i+1} &= x_i - y_i \cdot d_i \cdot 2^{-i} \\y_{i+1} &= y_i + x_i \cdot d_i \cdot 2^{-i} \\z_{i+1} &= z_i - d_i \cdot \tan^{-1}(2^{-i})\end{aligned}$$

$$\begin{aligned}d_i &= -1 \quad \text{if } z_i < 0 \\d_i &= +1 \quad \text{otherwise}\end{aligned}$$

sign of z register

In vectoring mode

$$\begin{aligned}x_{i+1} &= x_i - y_i \cdot d_i \cdot 2^{-i} \\y_{i+1} &= y_i + x_i \cdot d_i \cdot 2^{-i} \\z_{i+1} &= z_i - d_i \cdot \tan^{-1}(2^{-i})\end{aligned}$$

$$\begin{aligned}d_i &= +1 \quad \text{if } y_i < 0 \\d_i &= -1 \quad \text{otherwise}\end{aligned}$$

sign of y register

Bit-Parallel CORDIC: Characteristics

N iteration (clock cycles)

Variable Shifters

Adder- Subtractors

the amount of shift

the address of ROM LUT

the proper elementary angle

to z add/ subtractor

Bit-parallel variable shifter

Not good for FPGA


High Fan-in

→ several layers of logic

→ many cells to be traversed

- Slow design
- Large Area

Bit-Serial CORDIC: Structure

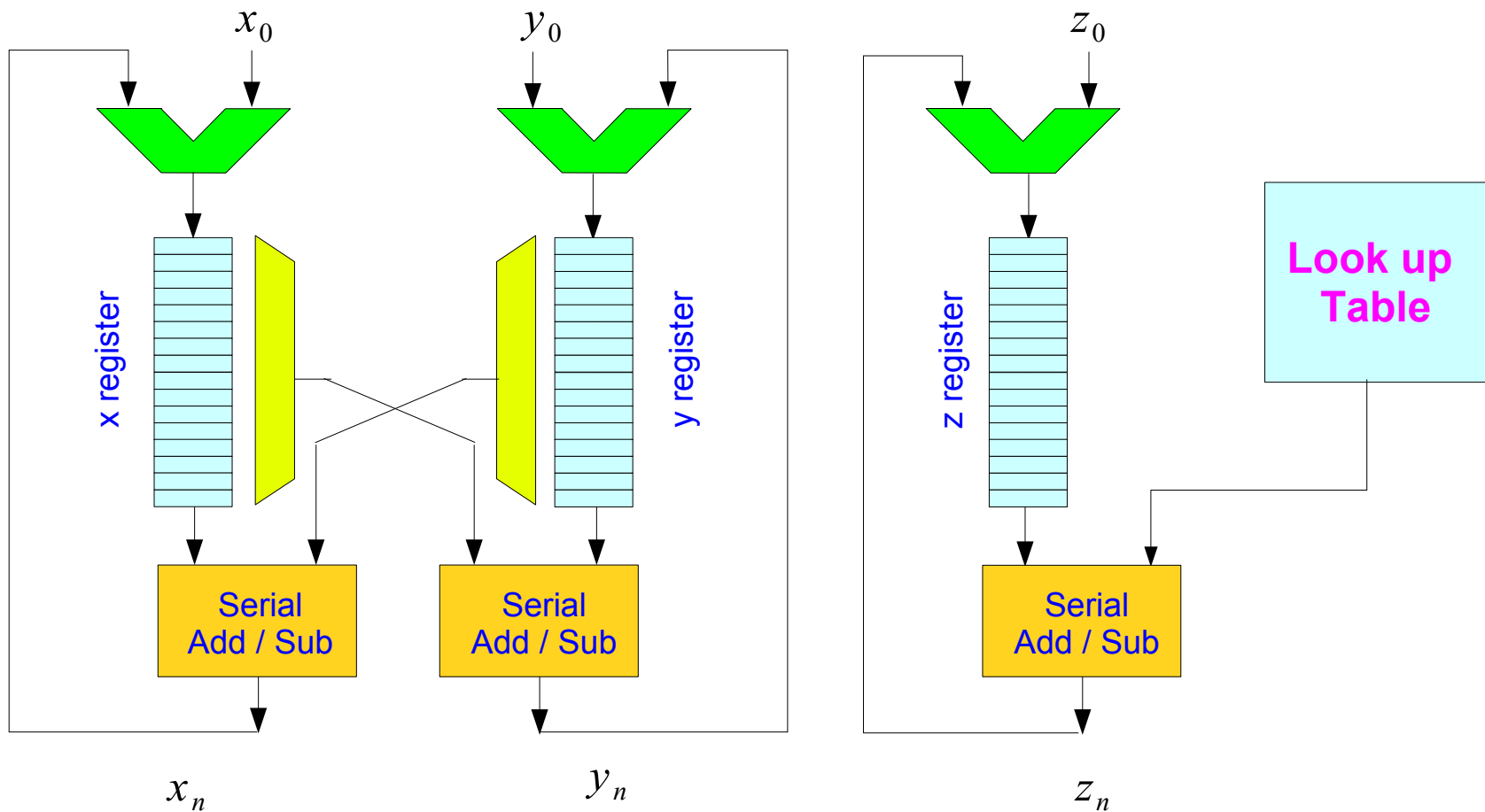

Bit-Serial CORDIC: Characteristics

Compact design

Simple interconnection →

Higher clock rate – up to the max rate of the FPGA

w : word width

w clocks per each iteration

3 bit-serial adder-subtractors

3 shifter registers

Shift tap multiplexers →

 Multiplexer tree: wiring problem

 Tri-state bus: ?

 Still simple interconn & logic

1 serial ROM

No shifting – using bit delays

During the n th iteration,

the result is read from the serial adders

While the next initialization data is shifted into the registers

Bit-Serial CORDIC: Shifter Register Implementation

Xilinx 4000E

Shift register

implemented in the CLB RAM

16x1 RAM emulates shift register

By incrementing read/write address
after each access

Dual port –


simultaneous reading 2 locations

By properly sequencing the 2nd address

→ shift tap multiplexer realized

w/o using actual multiplexer

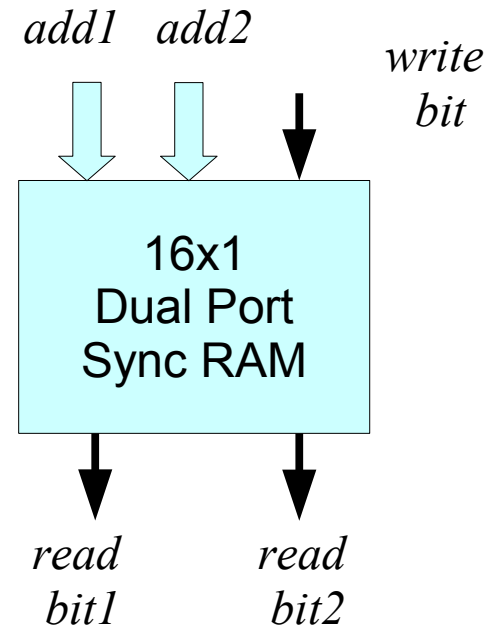→ upto 16 bit word length, 1 CLB is enough




Bit-Serial CORDIC: ROM

Serial ROM


1 CLB is required for every 2 iteration

16-bit, 8 iteration CORDIC

16x8 ROM

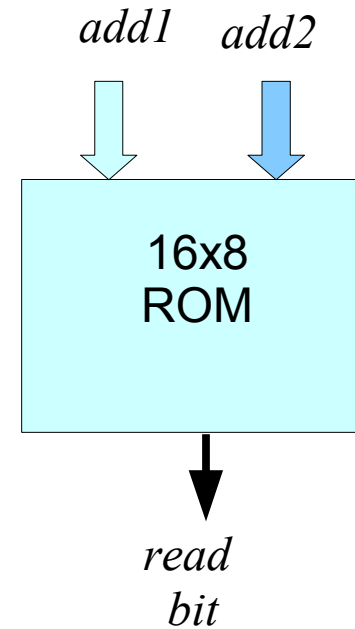

Loop Unrolled CORDIC: Structure

 

Loop Unrolled CORDIC: Characteristics

design

Sims

Unified CORDIC Iteration Eq

References

- [1] <http://en.wikipedia.org/>
- [2] CORDIC FAQ, www.dspguru.com
- [3] R. Andraka, A survey of CORDIC algorithms for FPGA based computers
- [4] J. S. Walther, A Unified Algorithm for Elementary Functions