Subsystems: Adder (3G)

Transistor Level Design

Copyright (c) 2011-2016 Young W. Lim.
Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".
Please send corrections (or suggestions) to youngwlim@hotmail.com.
This document was produced by using OpenOffice and Octave.

Subsystem Examples

Adders

Multipliers


Memories


Clock

PLL

DLL

I/O

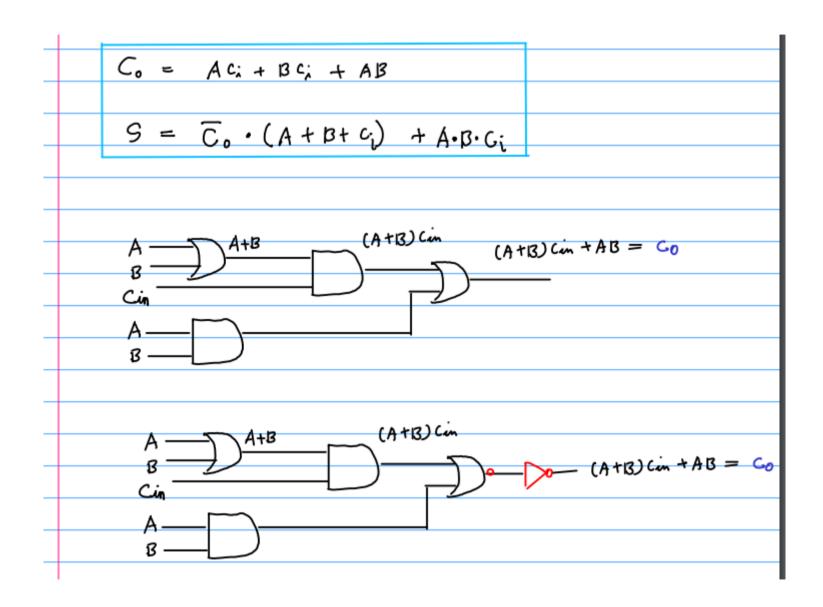

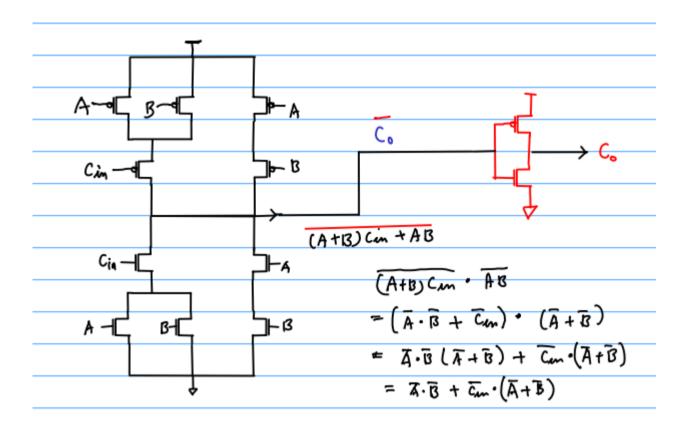


$$C_{o} = Ac_{i} + Bc_{i} + AB$$


$$G = \overline{C}_{o} \cdot (A + B + c_{i}) + A \cdot B \cdot C_{i}$$

$$A \longrightarrow C_{o}$$

$$C \longrightarrow \overline{S}$$

$$C \longrightarrow \overline{S}$$

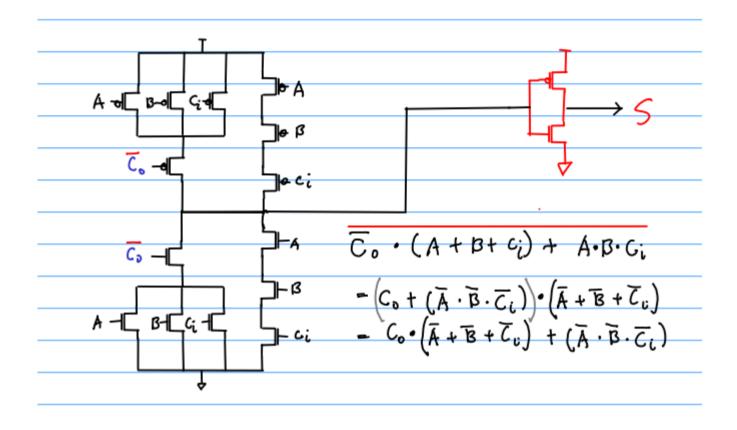

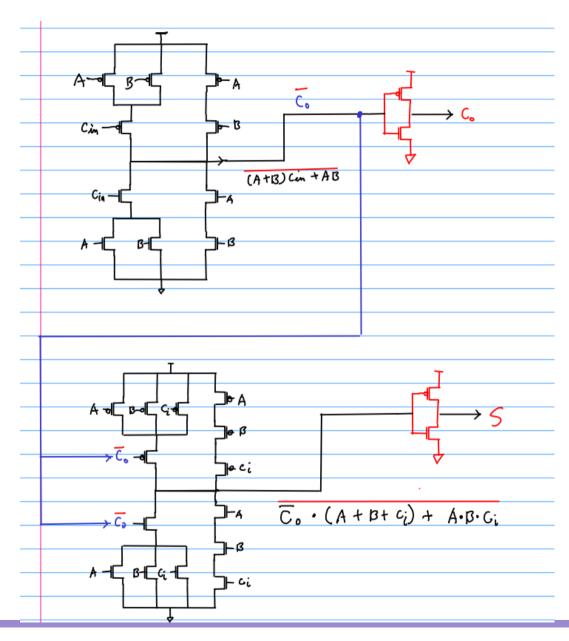

References

- [1] http://en.wikipedia.org/
- [2] http://www.allaboutcircuits.com/
- [3] W. Wolf, "Modern VLSI Design: Systems on Silicon
- [4] N. Weste, D. Harris, "CMOS VLSI Design: A Circuits and Systems Perspective"
- [5] J. P. Uyemura, "Introduction to VLSI Circuits and Systems"
- [6] https://en.wikiversity.org/wiki/The_necessities_in_SOC_Design
- [7] https://en.wikiversity.org/wiki/The_necessities_in_Digital_Design
- [8] https://en.wikiversity.org/wiki/The_necessities_in_Computer_Design
- [9] https://en.wikiversity.org/wiki/The_necessities_in_Computer_Architecture
- [10] https://en.wikiversity.org/wiki/The_necessities_in_Computer_Organization