

BJT Bias Base Bias (H.6)

20170425

Copyright (c) 2016 - 2017 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".

References


Based

[1] Floyd, Electronic Devices 7th ed

[2] Cook,

[2] en.wikipedia.org

Base Bias


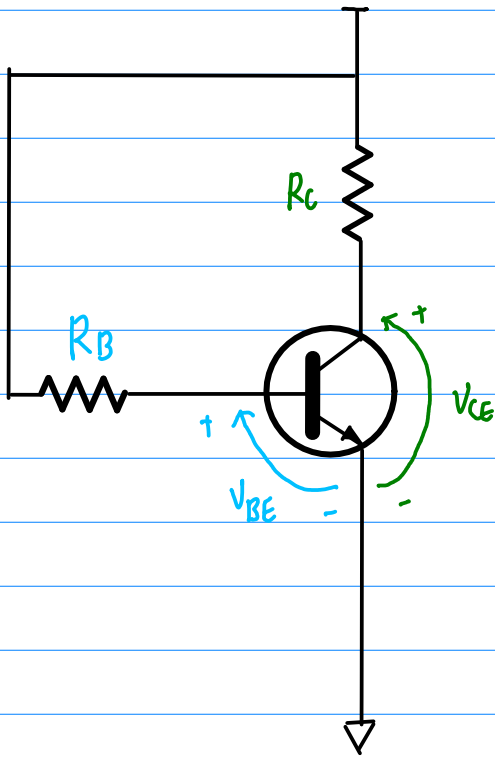




Q point values $I_C \cong I_E$



$$I_C = \beta_{DC} \left(\frac{V_{CC} - V_{BE}}{R_B} \right)$$

$$V_{CE} = V_{CC} - I_C R_C$$

Transistor Approximation

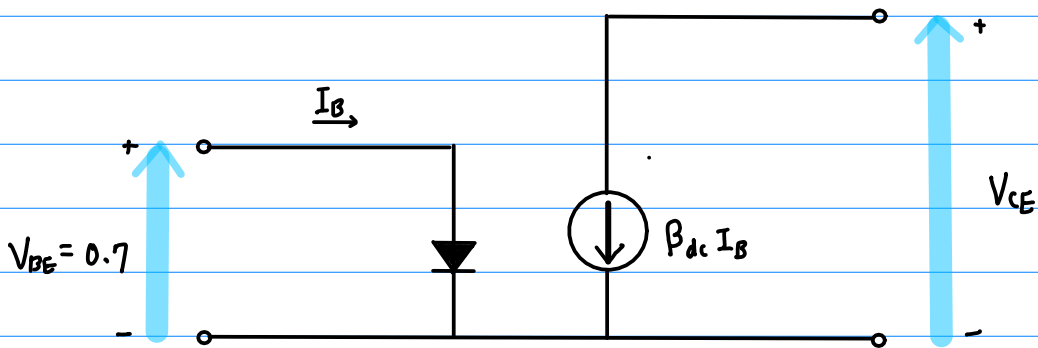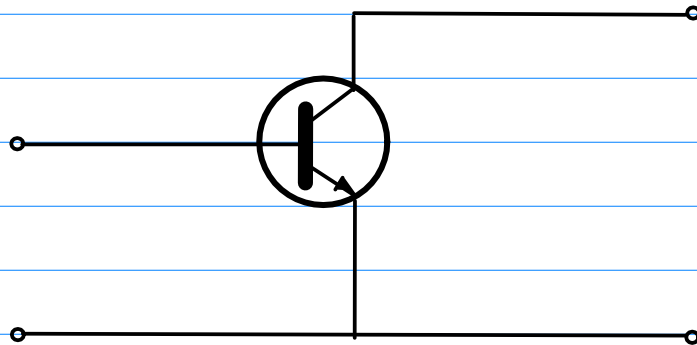

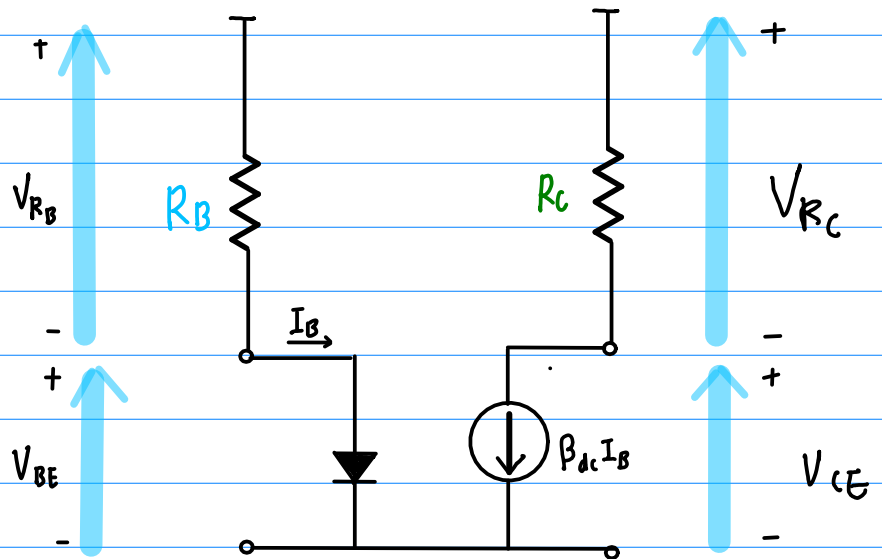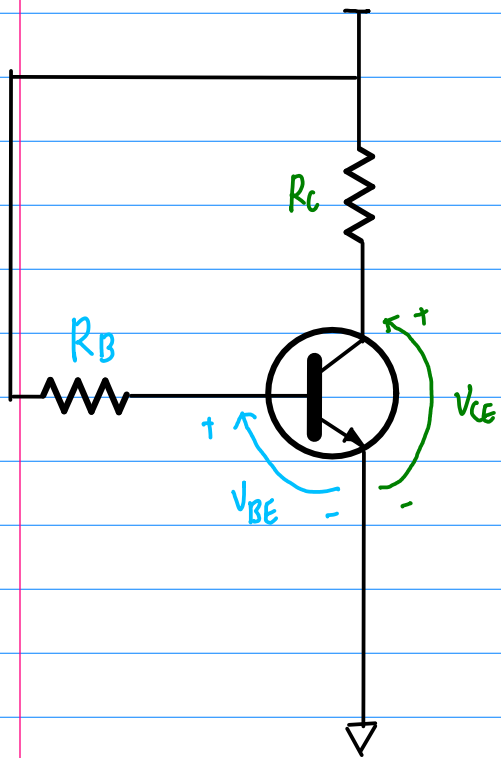

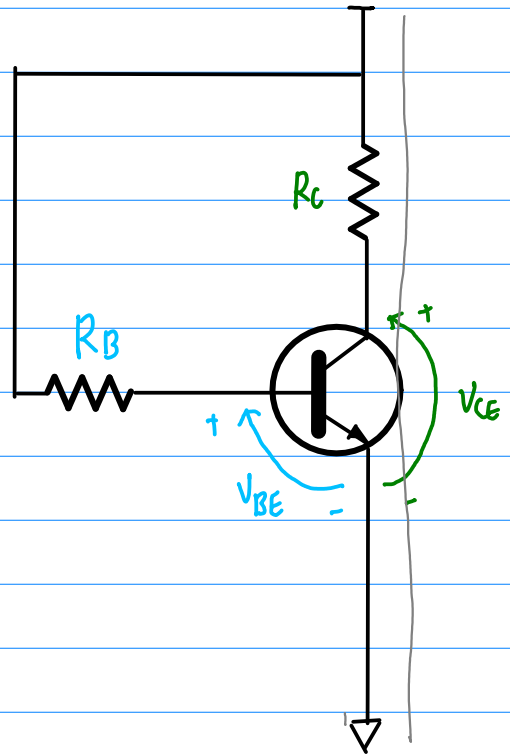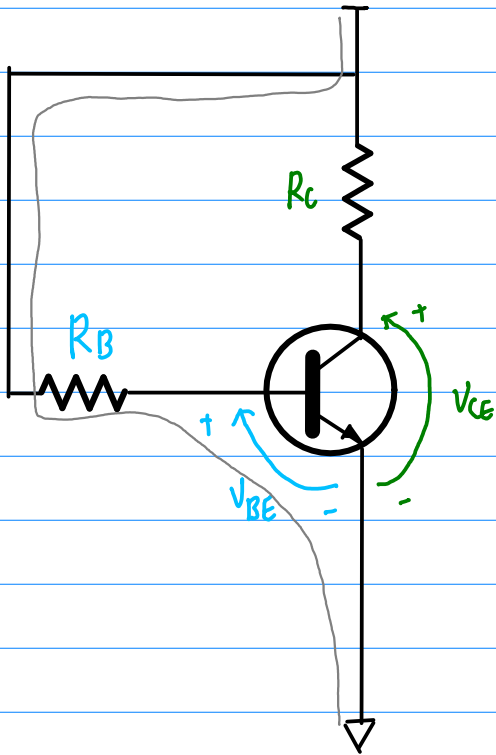

$$V_{CC} - V_{R_B} - V_{BE} = 0$$

$$V_{CC} - I_B R_B - V_{BE} = 0$$


$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

$$V_{CC} - I_C R_C - V_{CE} = 0$$


$$V_{CE} = V_{CC} - I_C R_C$$

$$I_C = \beta_{DC} I_B = \beta_{DC} \left(\frac{V_{CC} - V_{BE}}{R_B} \right)$$

Base Bias

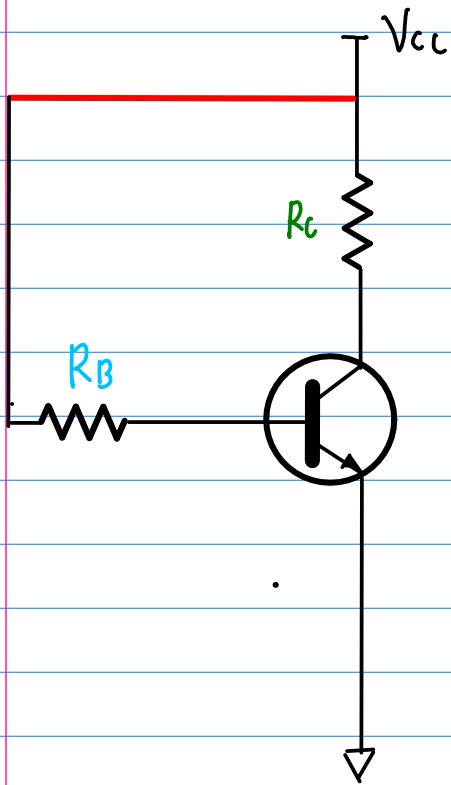

Collector Feedback Bias

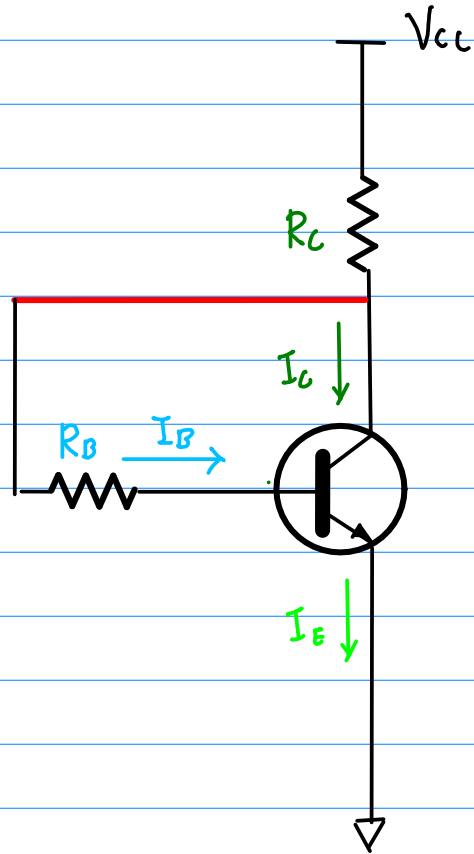

Emitter Bias

