

Tiny CPU Overview


Copyright (c) 2014 - 2016 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".

Please send corrections (or suggestions) to youngwlim@hotmail.com.



This document was produced by using OpenOffice and Octave.

Gated D Latch


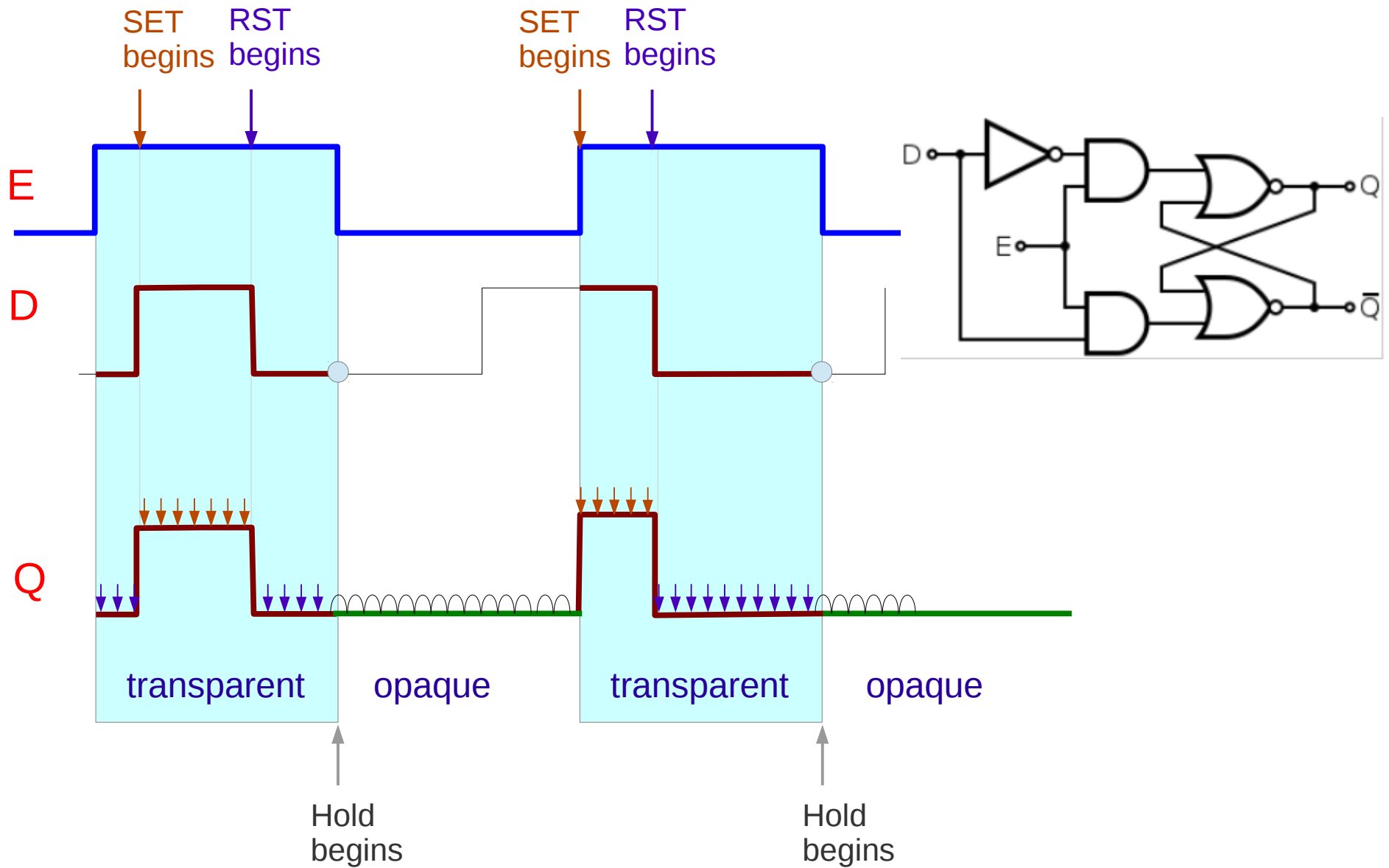


Edge Triggered D FlipFlop (2)


Master D Latch

  

Slave D Latch


 
 


Edge Triggered D F/F

 

Master-Slave D FlipFlop – Falling Edge


Master D Latch

   



Slave D Latch

Master-Slave D FlipFlop – Rising Edge

Master D Latch

 



Slave D Latch

  

D Latch & D FlipFlop



Level Sensitive D Latch

CK=1 transparent
CK=0 opaque

  


Edge Sensitive D FlipFlop

CK=1 → 0 transparent
else opaque

  


Data Path

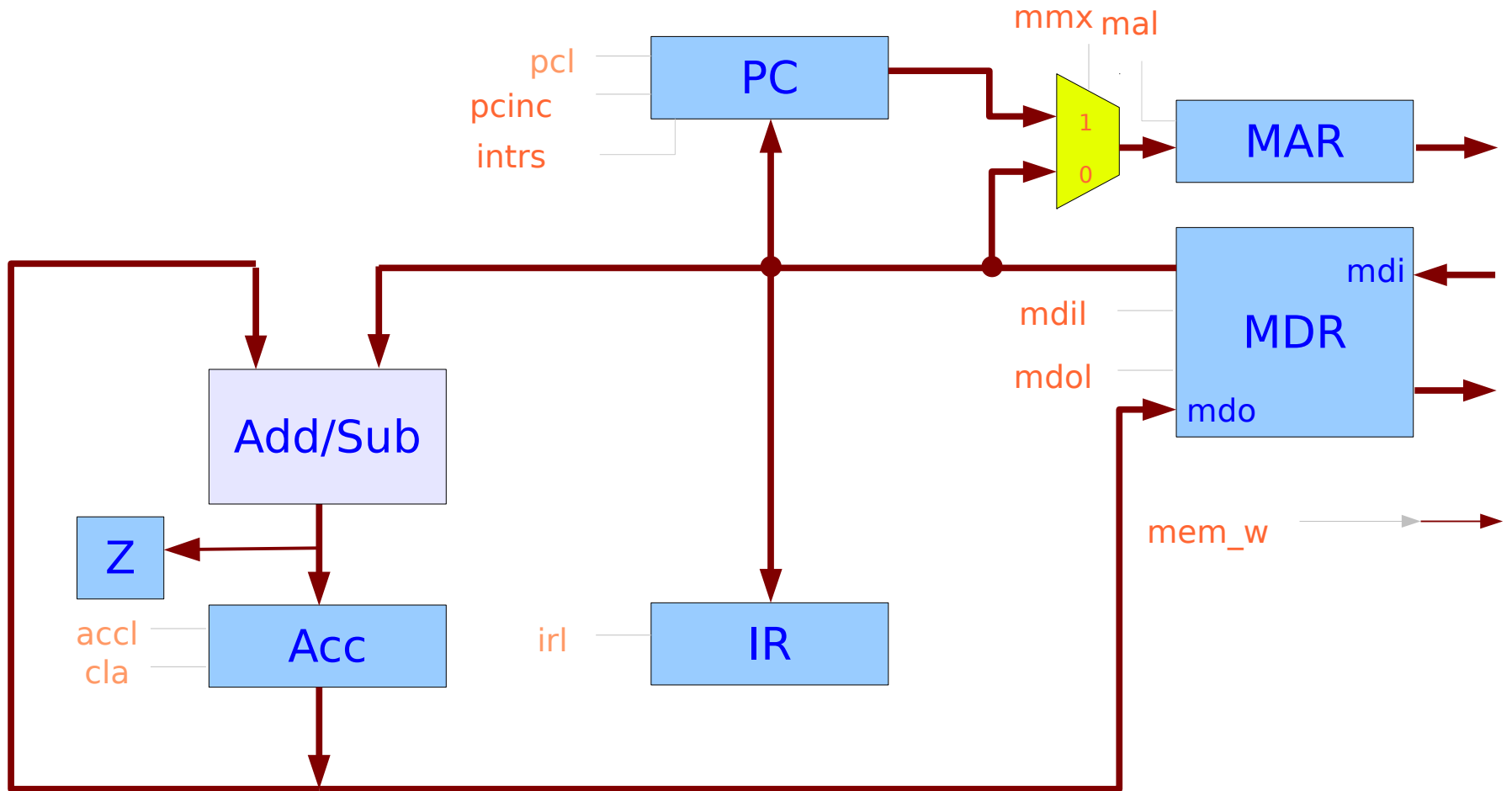



Based on <http://www.ele.uri.edu/Courses/ele306/f01/Tinydoc.pdf>

CPU and MEM

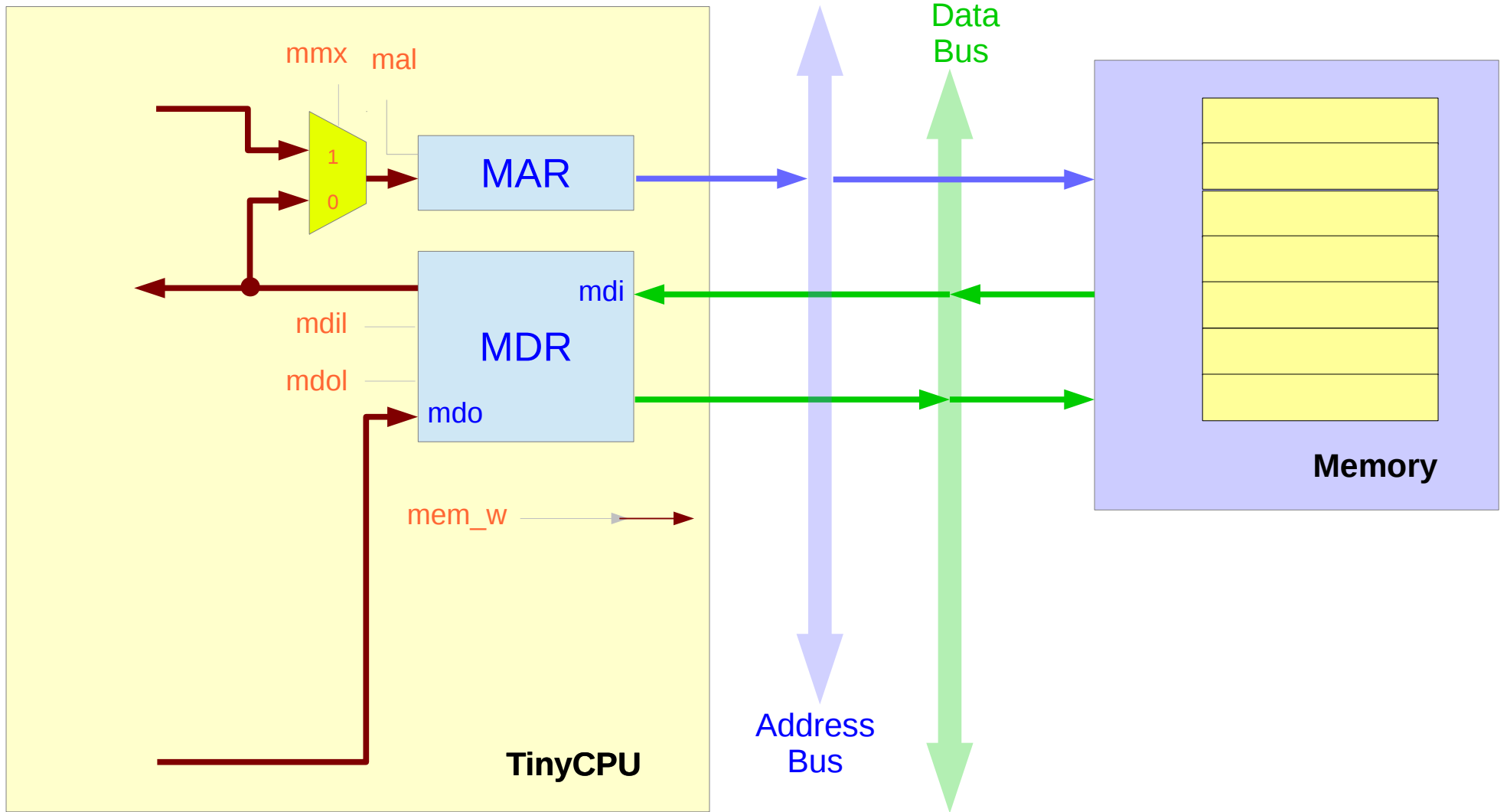



Based on <http://www.ele.uri.edu/Courses/ele306/f01/Tinydoc.pdf>

Memory Data Register


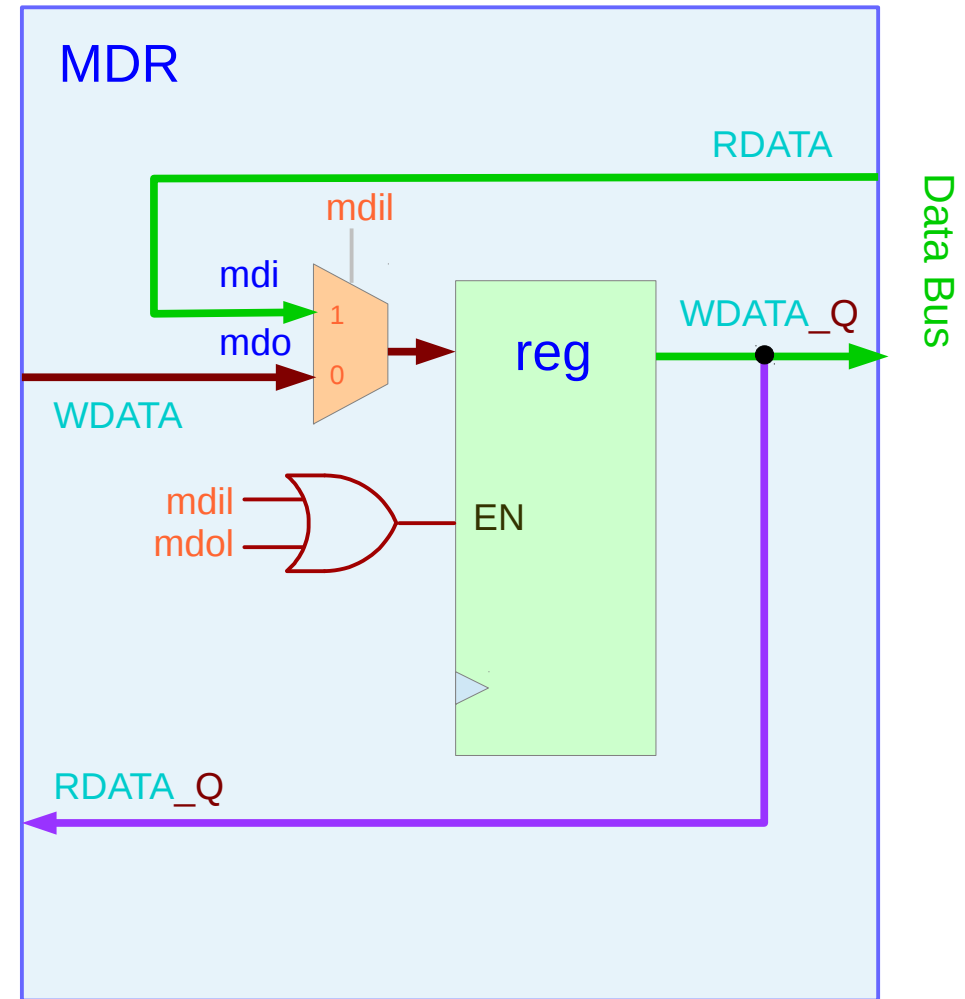
 


Based on <http://www.ele.uri.edu/Courses/ele306/f01/Tinydoc.pdf>





Memory Access Operations

  

Memory Write Cycle – Synchronous

  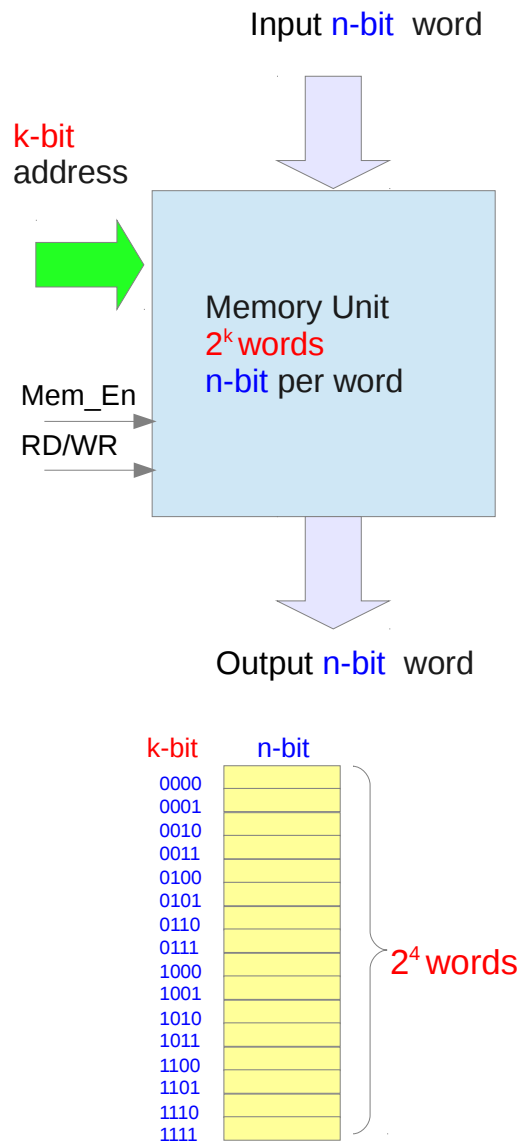

Memory Read Cycle - Asynchronous

    

Waveform Viewer Timing (1)

* timing figures without delay (Ideal case)


RTL functional simulation

* timing figures with delay


Gate level simulation
with SDF annotation

Waveform Viewer Timing (2)

Sync WRITE

 


Sync READ

 

Waveform Viewer Timing (3)

Sync READ


Async READ

 

unintended
write cycle!

MEM_RD :
One cycle ahead

Instruction Set Architecture

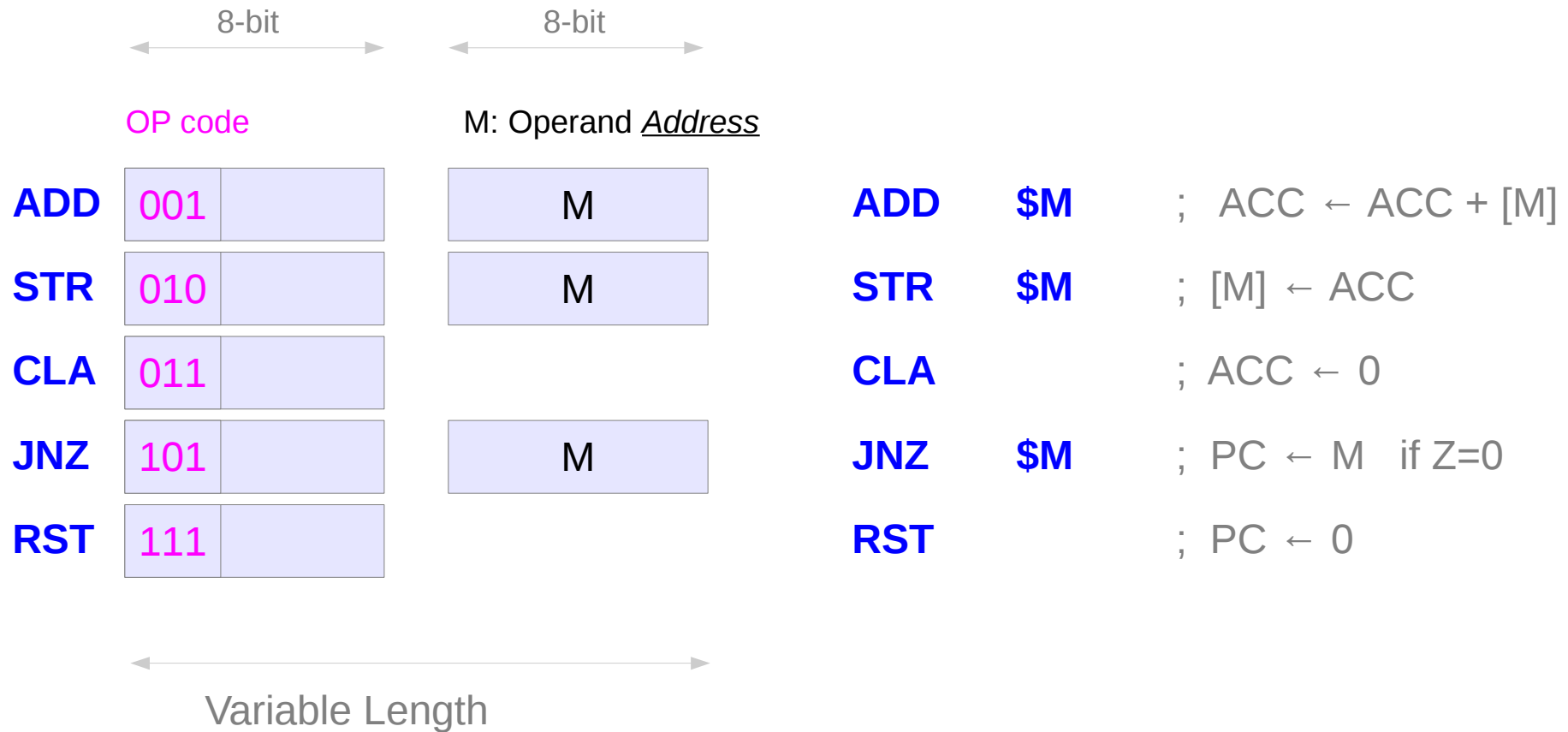

Based on <http://www.ele.uri.edu/Courses/ele306/f01/Tinydoc.pdf>

Instruction Cycles

common cycles

c1 MAR \leftarrow PC; MEM_RD;
c2 MDR \leftarrow MEM; PC \leftarrow PC+1;
c3 IR \leftarrow MDR

ADD specific cycles

c4 MAR \leftarrow PC; MEM_RD
c5 MDR \leftarrow MEM; PC \leftarrow PC+1
c6 MAR \leftarrow MDR; MEM_RD
c7 MDR \leftarrow MEM;
c8 ACC \leftarrow ACC + MDR;

CLA specific cycles

c4 ACC \leftarrow "00"

RST specific cycles

c4 PC \leftarrow "00"

Opcode_RD
Operand_RD

STR specific cycles


c4 MAR \leftarrow PC; MEM_RD
c5 MDR \leftarrow MEM; PC \leftarrow PC + 1
c6 MAR \leftarrow MDR; MDR \leftarrow ACC
c7 MEM_WR;

JNZ specific cycles

c4 MAR \leftarrow PC; MEM_RD;
c5 MDR \leftarrow MEM; PC \leftarrow PC + 1
c6 If (Z=='0') PC \leftarrow MDR;


Based on <http://www.ele.uri.edu/Courses/ele306/f01/Tinydoc.pdf>

Clock Cycle Counts

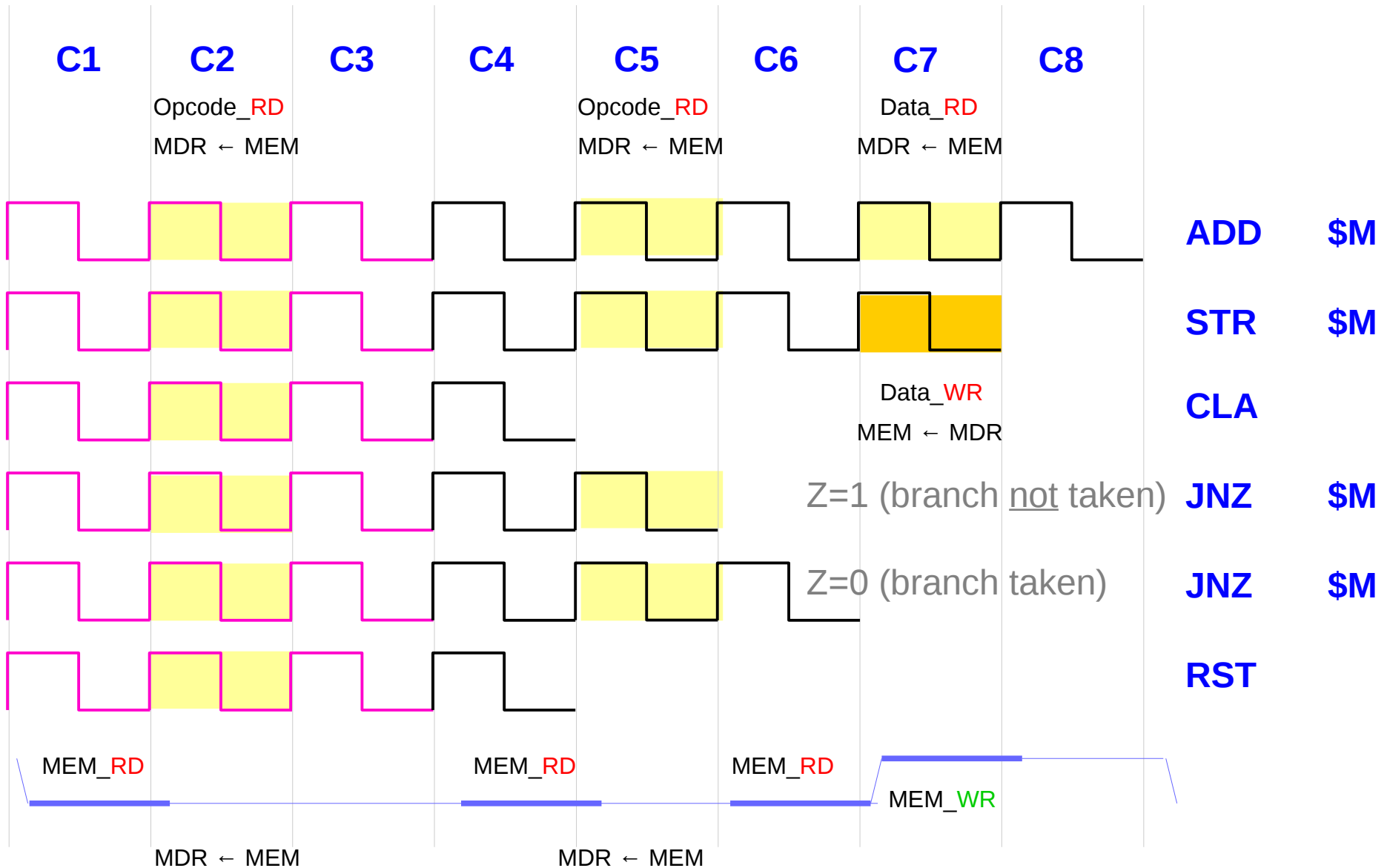

Based on <http://www.ele.uri.edu/Courses/ele306/f01/Tinydoc.pdf>

IF (S1,S2,S3)

 


S1 MAR \leftarrow PC; MEM_RD;
 S2 MDR \leftarrow MEM; PC \leftarrow PC+1;
 S3 IR \leftarrow MDR

	IR[7:5]
ADD	001
STR	010
CLA	011
JNZ	101
RST	111


Based on <http://www.ele.uri.edu/Courses/ele306/f01/Tinydoc.pdf>

ADD (S4,S5,S6,S7,S8)

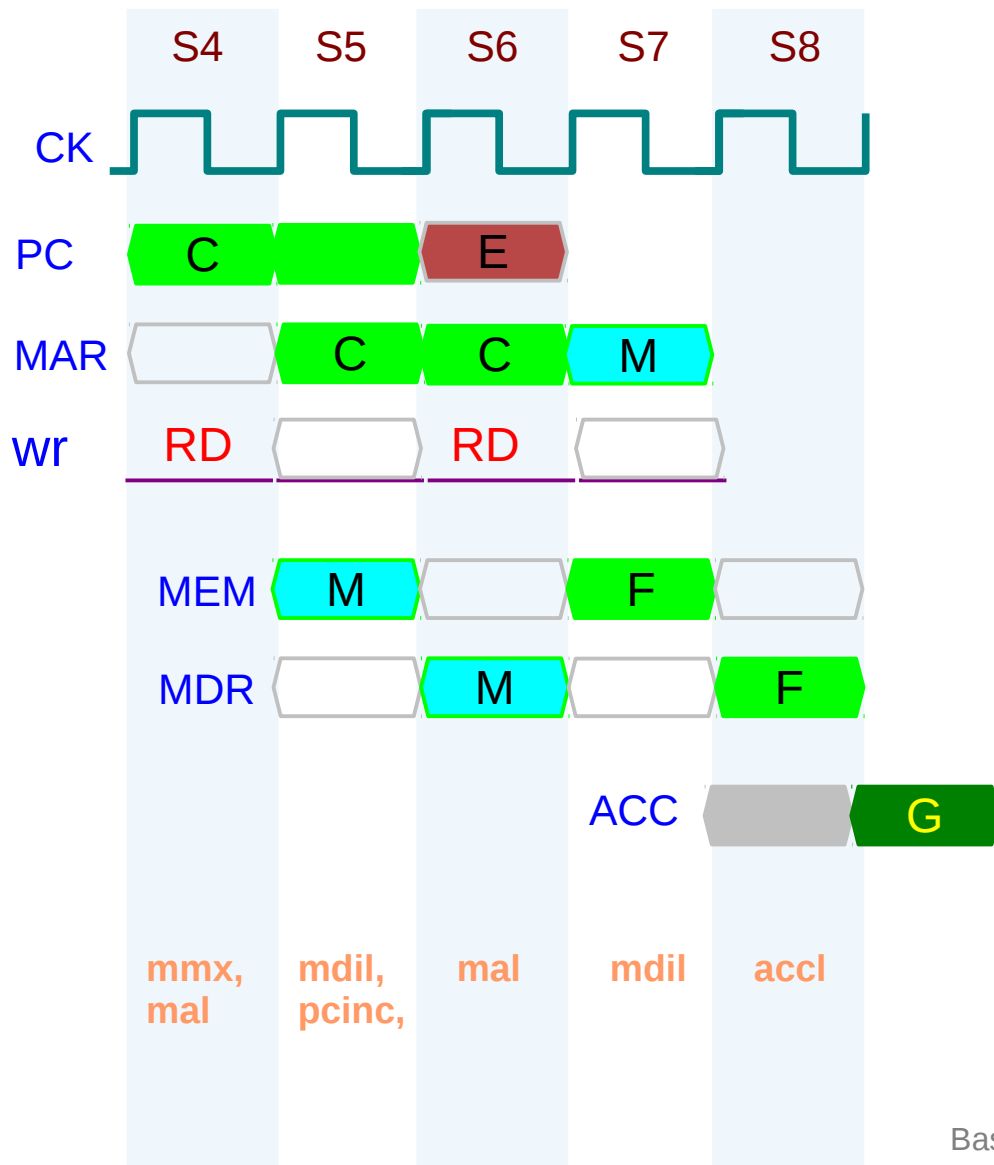


S4 MAR ← PC; MEM_RD
 S5 MDR ← MEM; PC ← PC+1
 S6 MAR ← MDR; MEM_RD
 S7 MDR ← MEM;
 S8 ACC ← ACC + MDR;

ADD \$M ; ACC ← ACC + [M]

 


Based on <http://www.ele.uri.edu/Courses/ele306/f01/Tinydoc.pdf>

STR (S4,S5,S6,S7)

 


S4 MAR ← PC; MEM_RD
 S5 MDR ← MEM; PC ← PC + 1
 S6 MAR ← MDR; MDR ← ACC
 S7 MEM_WR;

STR \$M ; [M] ← ACC

 

Based on <http://www.ele.uri.edu/Courses/ele306/f01/Tinydoc.pdf>

CLA (S4)

 


S4 ACC ← "00"

CLA ; ACC ← 0

PC 011


Based on <http://www.ele.uri.edu/Courses/ele306/f01/Tinydoc.pdf>

JNZ (S4,S5,S6)

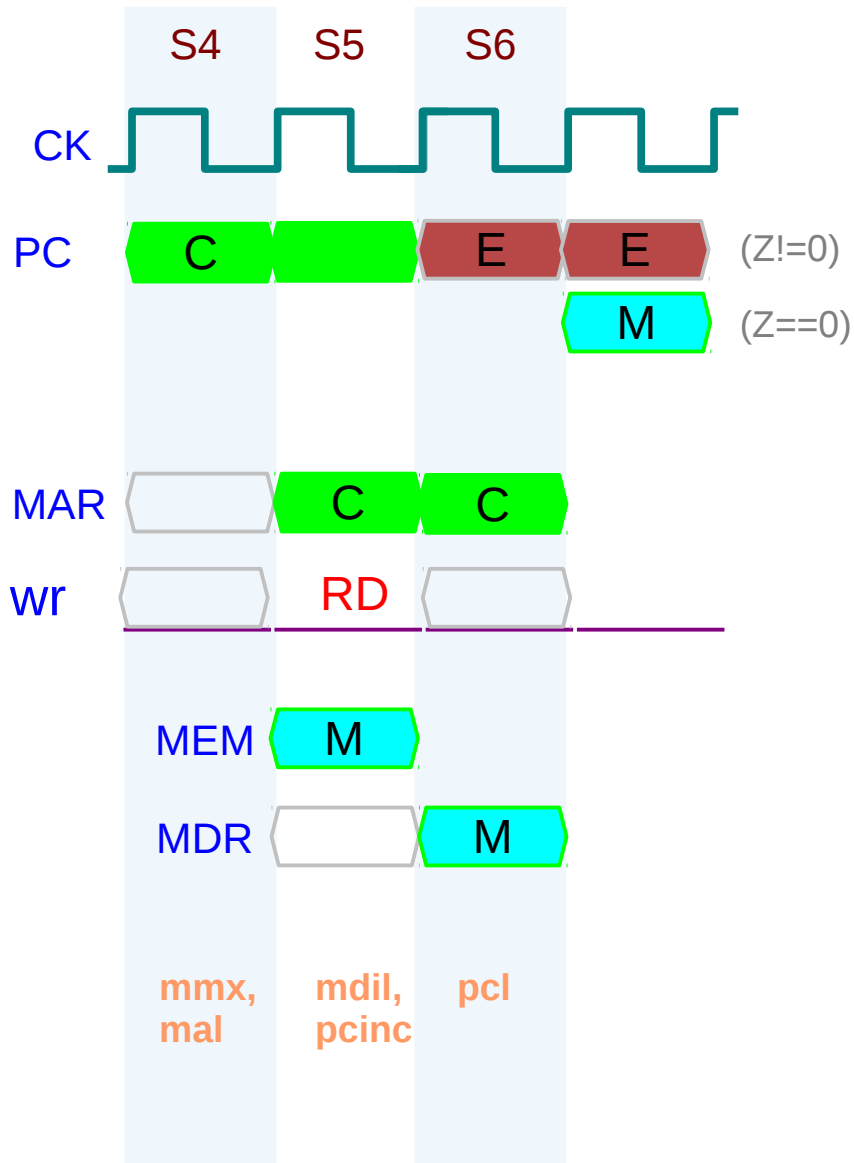


S4 MAR \leftarrow PC; MEM_RD;
 S5 MDR \leftarrow MEM; PC \leftarrow PC + 1
 S6 If (Z=='0') PC \leftarrow MDR;

JNZ \$M ; PC \leftarrow [M] if Z=0

 

Based on <http://www.ele.uri.edu/Courses/ele306/f01/Tinydoc.pdf>

RST (S4)

 


S4 PC ← "00";

RST ; PC ← 0




Based on <http://www.ele.uri.edu/Courses/ele306/f01/Tinydoc.pdf>

FSM I

 


Instruction Decoder

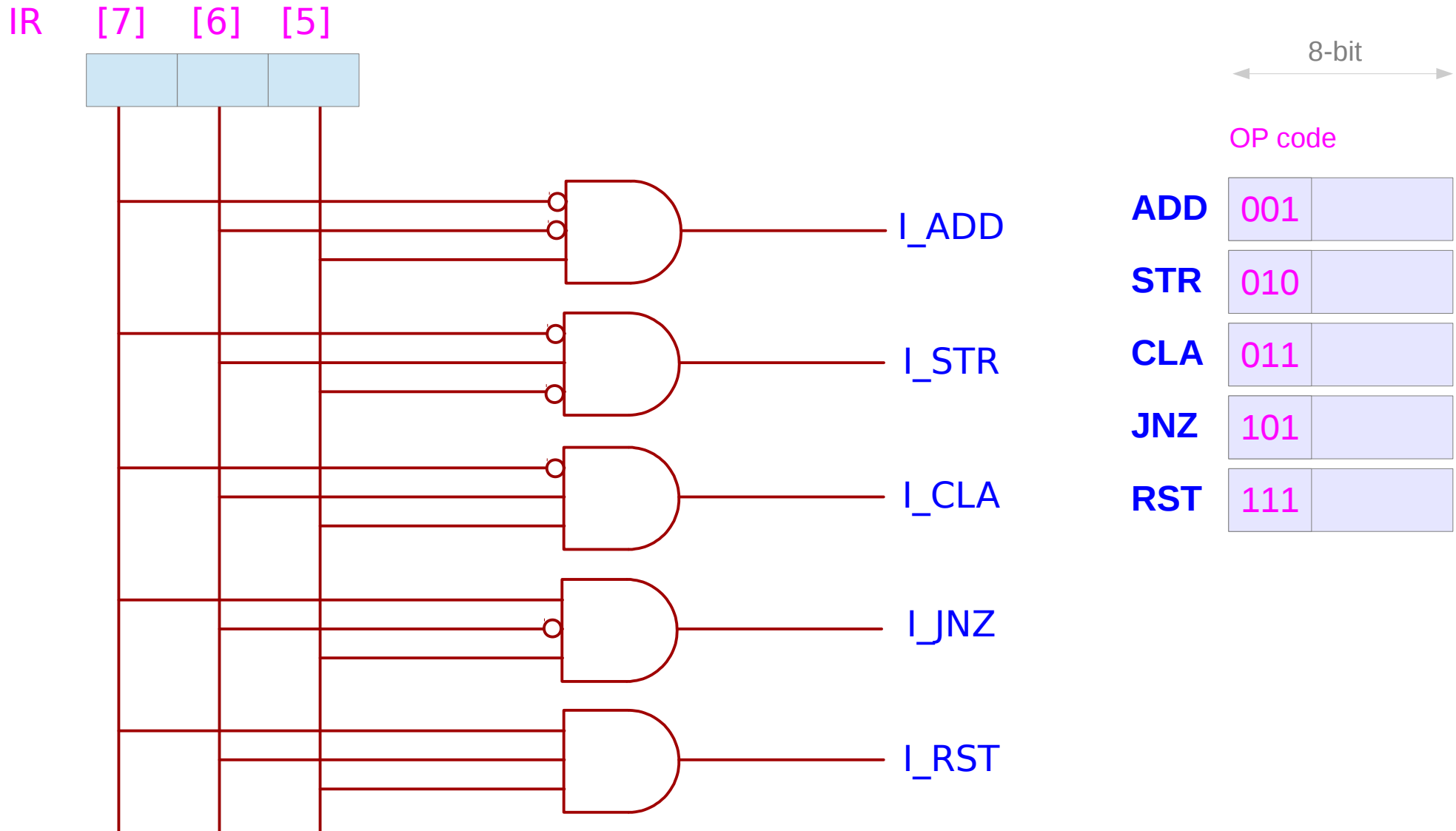


Based on <http://www.ele.uri.edu/Courses/ele306/f01/Tinydoc.pdf>

FSM II

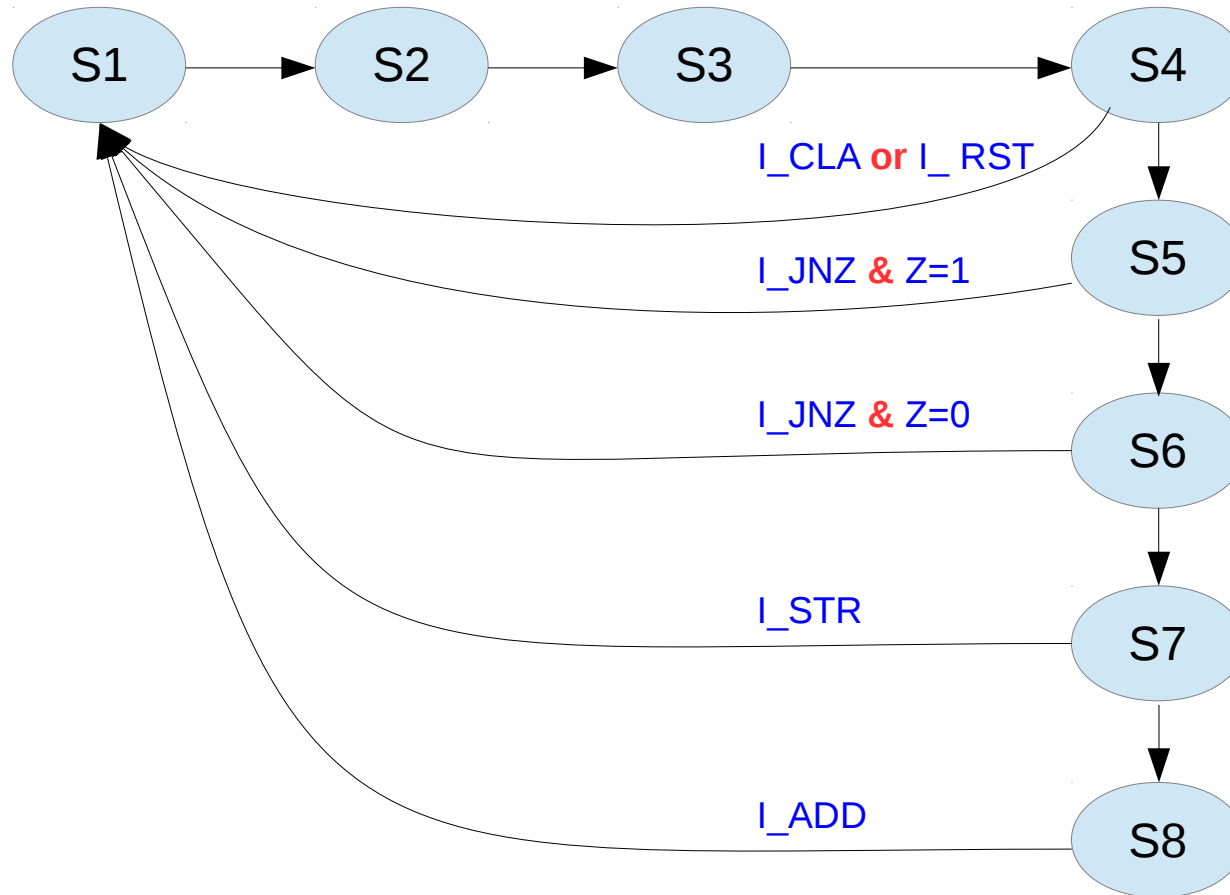


Based on <http://www.ele.uri.edu/Courses/ele306/f01/Tinydoc.pdf>

Control Signal - IF

 


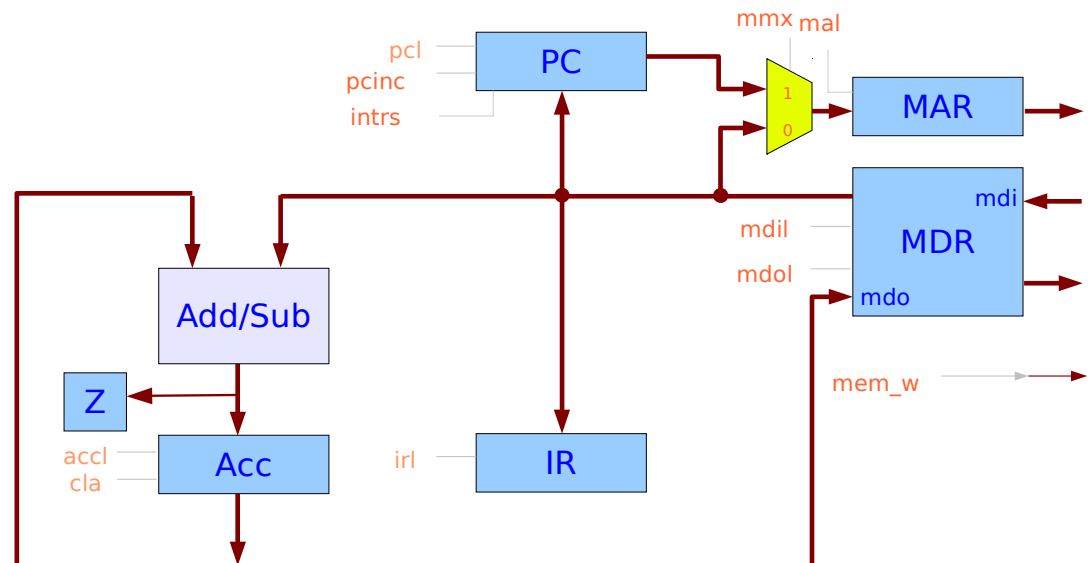S1 MAR \leftarrow PC; MEM_RD;
S2 MDR \leftarrow MEM; PC \leftarrow PC+1;
S3 IR \leftarrow MDR




Based on <http://www.ele.uri.edu/Courses/ele306/f01/Tinydoc.pdf>

Control Signal - ADD

 


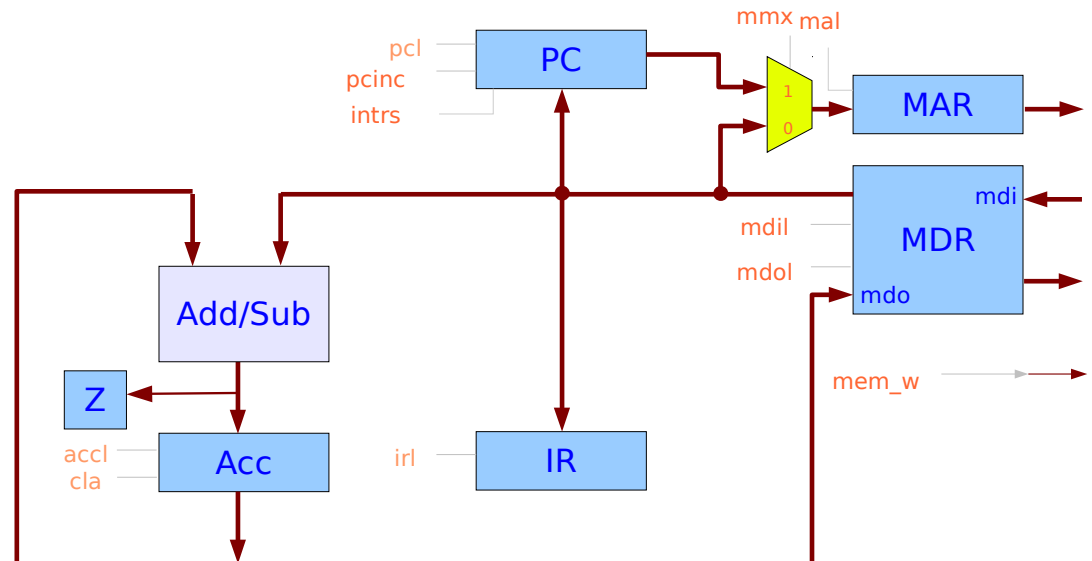S4 MAR \leftarrow PC; MEM_RD
 S5 MDR \leftarrow MEM; PC \leftarrow PC+1
 S6 MAR \leftarrow MDR; MEM_RD
 S7 MDR \leftarrow MEM;
 S8 ACC \leftarrow ACC + MDR;




Based on <http://www.ele.uri.edu/Courses/ele306/f01/Tinydoc.pdf>

Control Signal - STR

 

 S4 MAR \leftarrow PC; MEM_RD
S5 MDR \leftarrow MEM; PC \leftarrow PC + 1
S6 MAR \leftarrow MDR; MDR \leftarrow ACC
S7 MEM_WR;




Based on <http://www.ele.uri.edu/Courses/ele306/f01/Tinydoc.pdf>

Control Signal - CLA

S4 CLA


cla

S4 ACC ← "00"

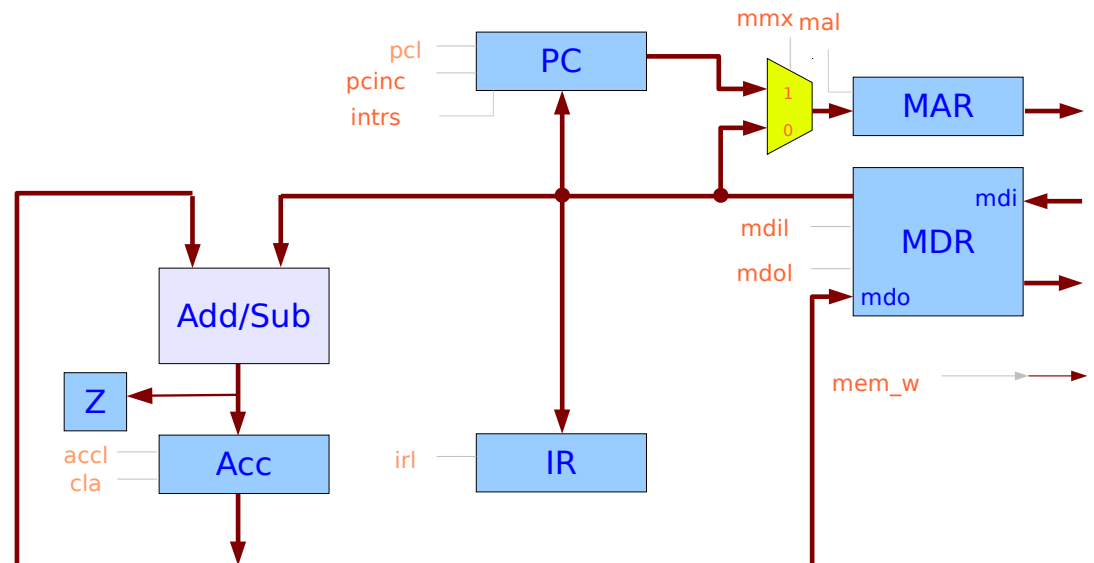


Based on <http://www.ele.uri.edu/Courses/ele306/f01/Tinydoc.pdf>

Control Signal - JNZ

 

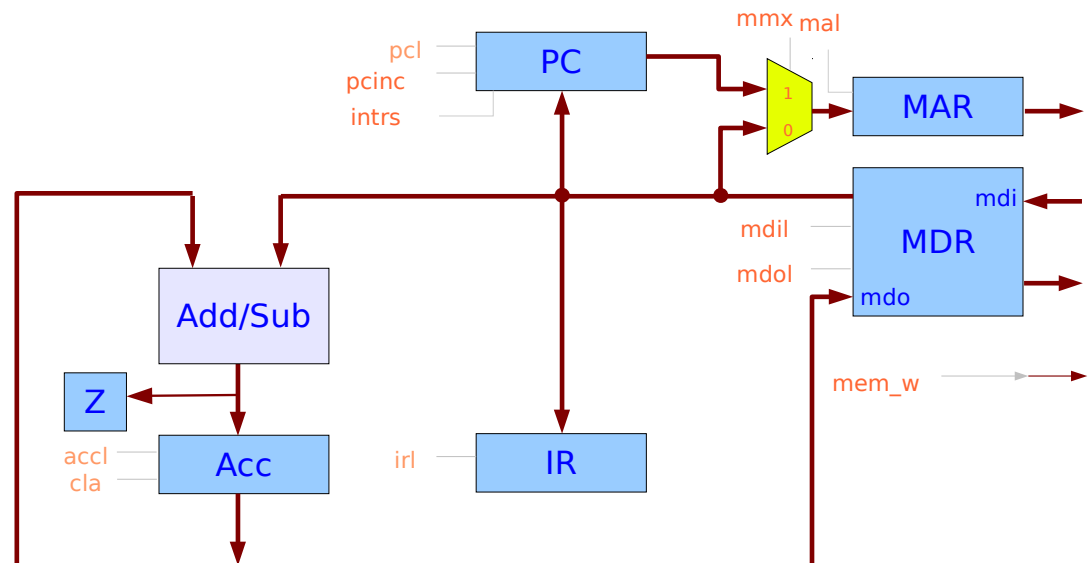S4 MAR \leftarrow PC; MEM_RD;
 S5 MDR \leftarrow MEM; PC \leftarrow PC + 1
 S6 If (Z=='0') PC \leftarrow MDR;




Based on <http://www.ele.uri.edu/Courses/ele306/f01/Tinydoc.pdf>

Control Signal - RST

S4_{RST}

intrs

S4 PC ← "00"

 

Based on <http://www.ele.uri.edu/Courses/ele306/f01/Tinydoc.pdf>

Addr. Machine Codes

00	60		CLA						;Clear Acc and then adding the operand is
01	20	78	ADD	\$ONE					;equivalent to move the operand to Acc
03	40	FF	STR	\$FF					
05	A0	01	JNZ	\$01					
06	E0		RST						
78	01	ONE:	DAT	0000	0001				;Constant 1

References

- [1] <http://en.wikipedia.org/>
- [2] https://en.wikiversity.org/wiki/The_necessities_in_SOC_Design
- [3] https://en.wikiversity.org/wiki/The_necessities_in_Digital_Design
- [4] https://en.wikiversity.org/wiki/The_necessities_in_Computer_Design
- [5] https://en.wikiversity.org/wiki/The_necessities_in_Computer_Architecture
- [6] https://en.wikiversity.org/wiki/The_necessities_in_Computer_Organization
- [7] https://en.wikiversity.org/wiki/Understanding_Embedded_Software
- [8] Digital Systems, Hill, Peterson, 1987
- [9] <http://en.wikipedia.org/>
- [10] <http://www.ele.uri.edu/Courses/ele306/f01/Tinydoc.pdf>