

Finite State Machine (A3)



Copyright (c) 2011-2013 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".



Please send corrections (or suggestions) to youngwlim@hotmail.com.

This document was produced by using OpenOffice and Octave.



FF Timing (Ideal)

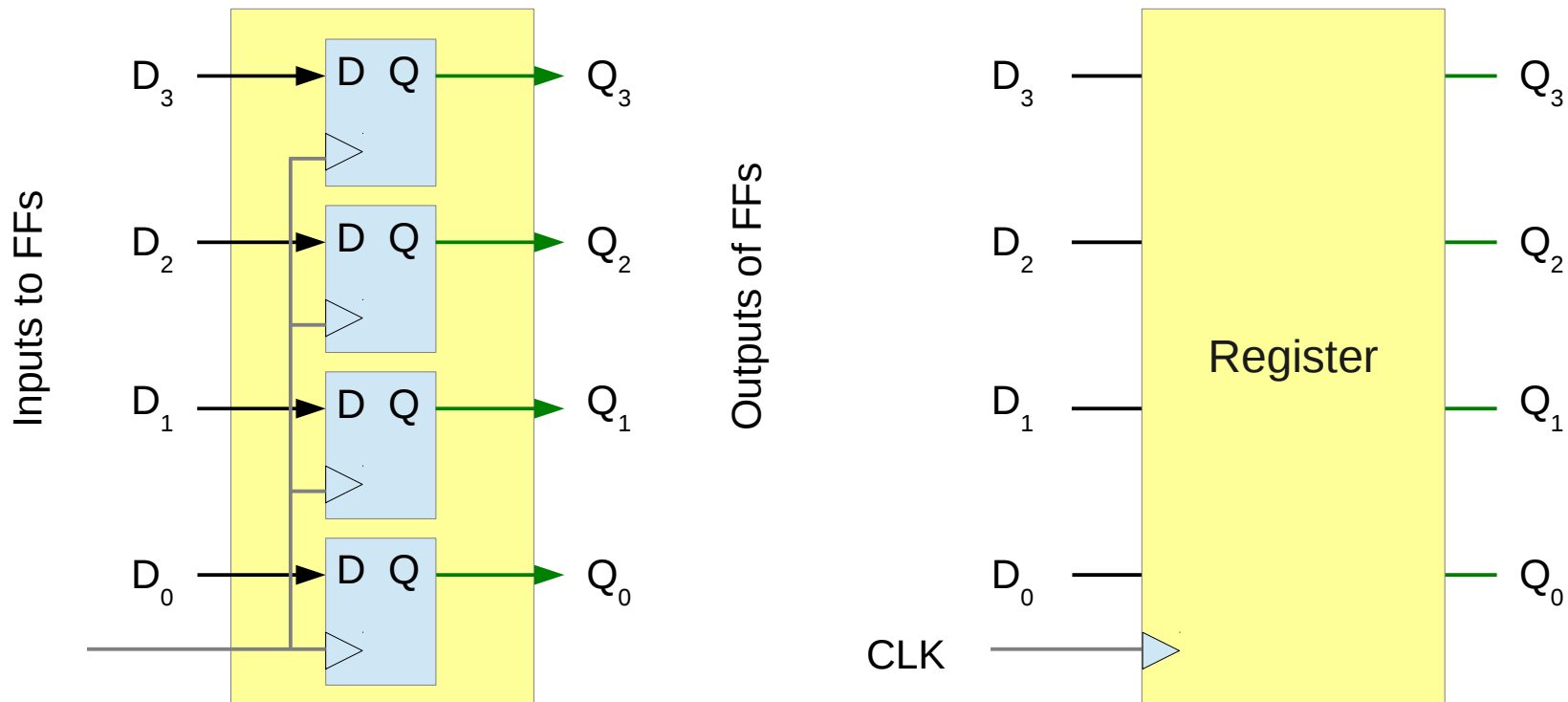 



Sequence of States

  

When NextSt becomes CurrSt

  

Finding FF Inputs

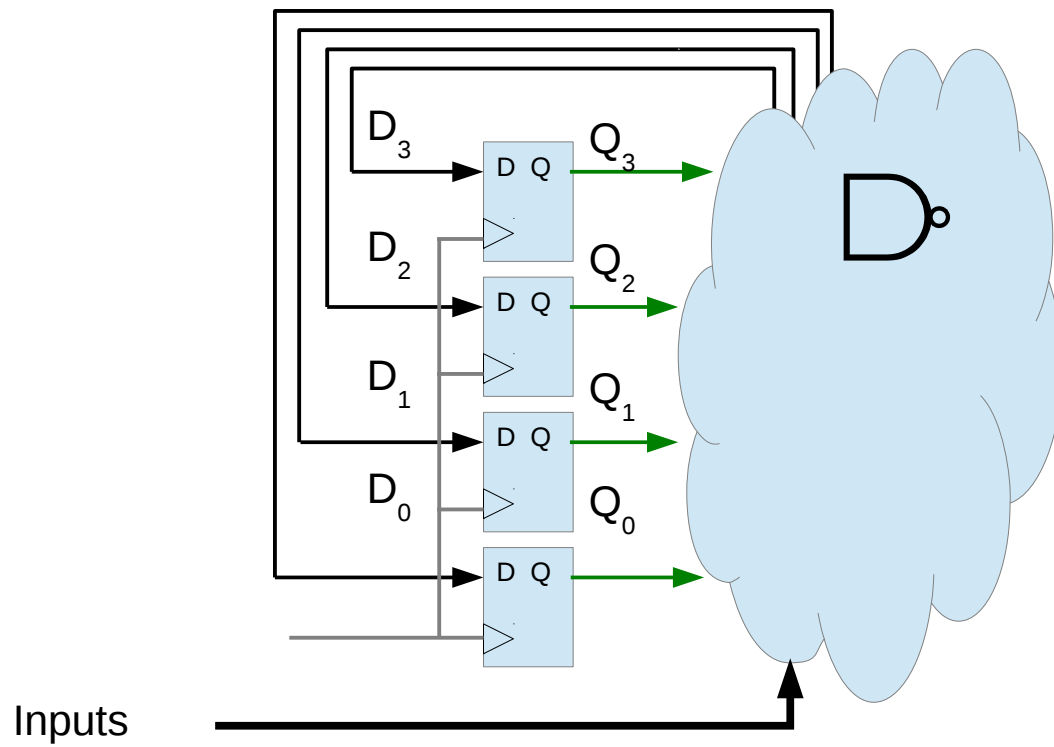 


During the t^{th} clock edge period,

Compute the next state $Q(t+1)$ using the current state $Q(t)$ and other external inputs


Place it to FF inputs

After the next clock edge, $(t+1)^{\text{th}}$, the **computed** next state $Q(t+1)$ becomes the current state

Method of Finding FF Inputs

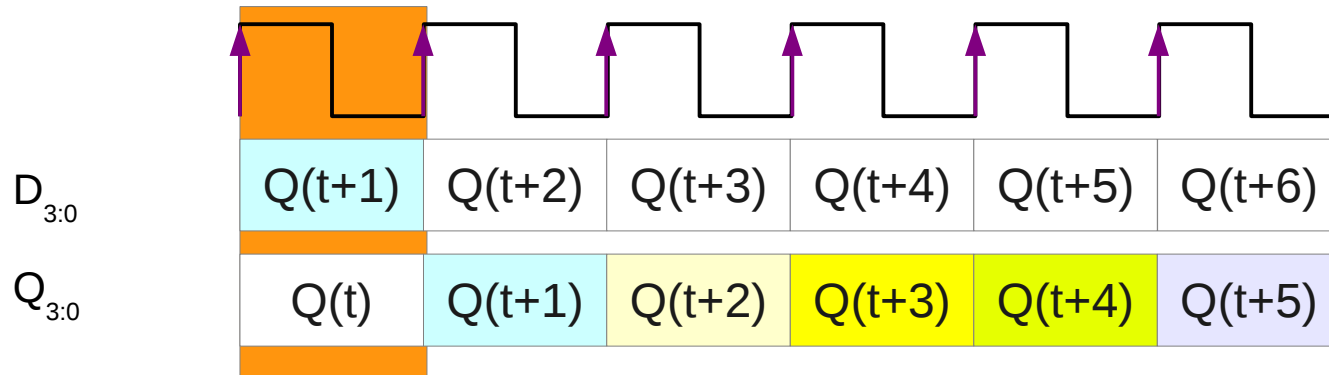

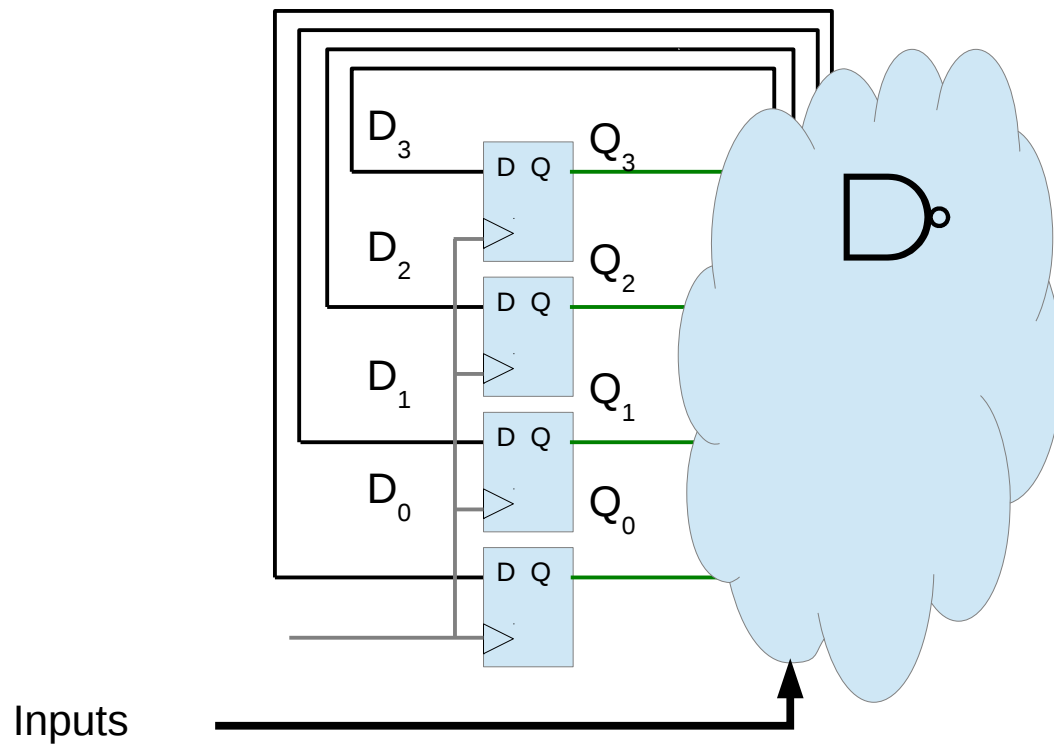
Find the **boolean functions** D_3, D_2, D_1, D_0 in terms of Q_3, Q_2, Q_1, Q_0 , and external inputs for all possible cases.





Truth Table and K-map

Q_3	Q_2	Q_1	Q_0	I	D_3

State Transition

 


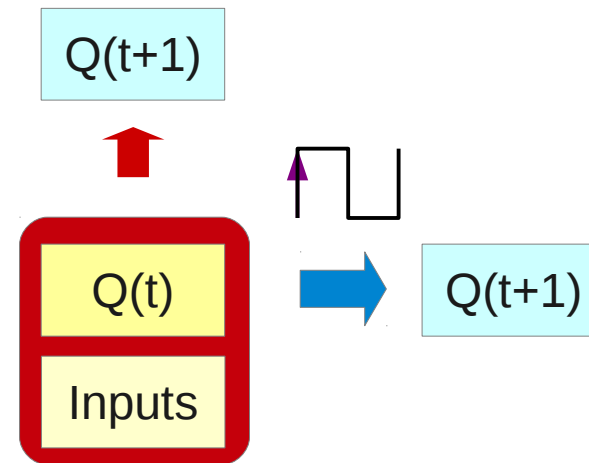 Compute the next state using the current state and external inputs in the current clock cycle




After the next clock edge, the computed next state (FF Inputs) becomes the current state (FF Outputs)

Moore FSM




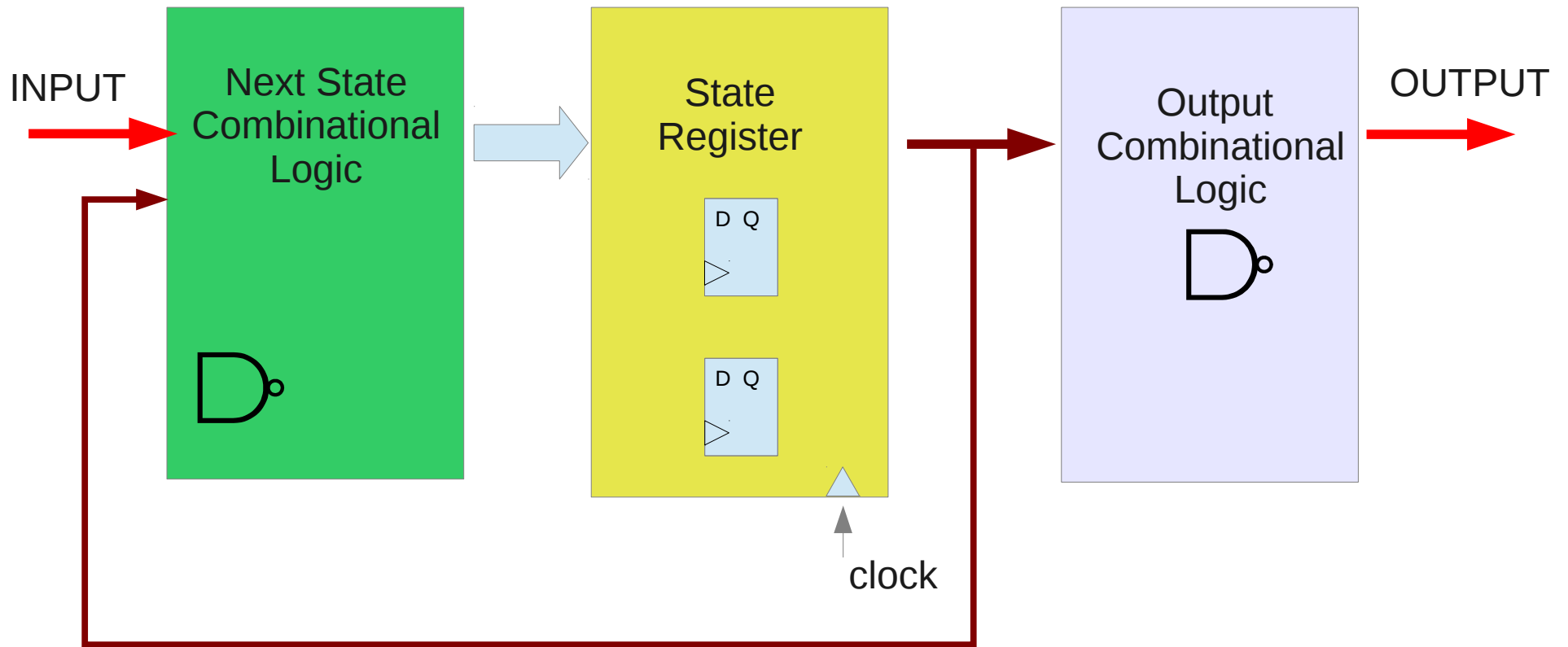


Mealy Machine

 

Register Timing

NOR-based SR Latch

    

FSM (3B)

12

Young Won Lim
10/30/13

References

- [1] <http://en.wikipedia.org/>
- [2] M. M. Mano, C. R. Kime, "Logic and Computer Design Fundamentals", 4th ed.
- [3] D.M. Harris, S. L. Harris, "Digital Design and Computer Architecture"