

# Carry Skip Adder (5A)

---

•  
•

Copyright (c) 2024 – 2013 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".


[https://en.wikipedia.org/wiki/AND\\_gate](https://en.wikipedia.org/wiki/AND_gate)  
[https://en.wikipedia.org/wiki/OR\\_gate](https://en.wikipedia.org/wiki/OR_gate)  
[https://en.wikipedia.org/wiki/XOR\\_gate](https://en.wikipedia.org/wiki/XOR_gate)  
[https://en.wikipedia.org/wiki/NAND\\_gate](https://en.wikipedia.org/wiki/NAND_gate)

Please send corrections (or suggestions) to [youngwlim@hotmail.com](mailto:youngwlim@hotmail.com).

This document was produced by using OpenOffice and Octave.


# Carry Kill, Propagate, Generate conditions (1)

X	Y		
0	0	K	Kill ( $=\bar{P}\bar{G}$ )
0	1	P	Propagate
1	0	P	Propagate
1	1	G	Generate

 


<https://electronics.stackexchange.com/questions/21251/critical-path-for-carry-skip-adder>
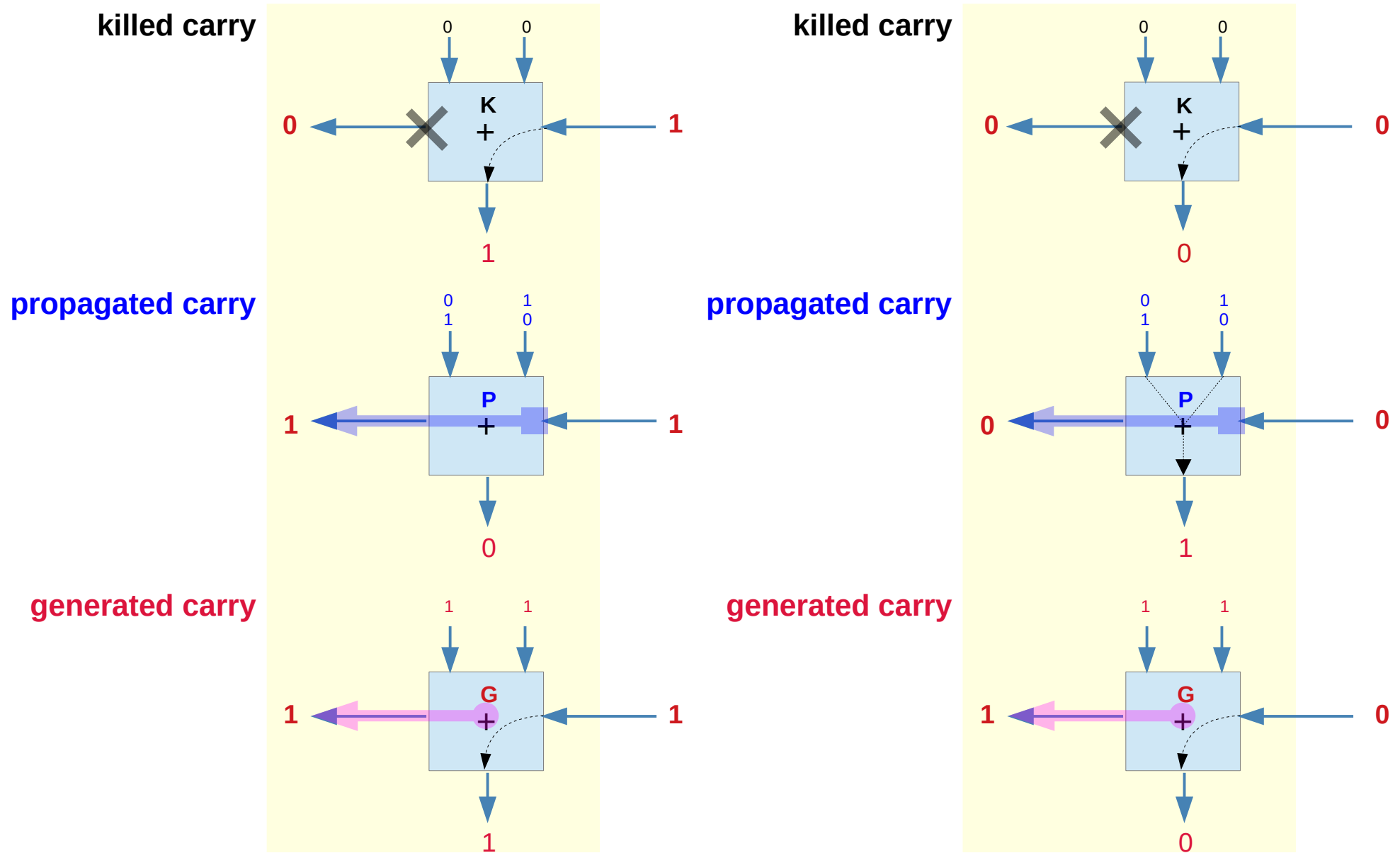
# Carry Kill, Propagate, Generate conditions (2)



# K, P, and G conditions in a 2-bit adder (1)

X	Y		
0	0	K	Kill ( $=\bar{P}G$ )
0	1	P	Propagate
1	0	P	Propagate
1	1	G	Generate

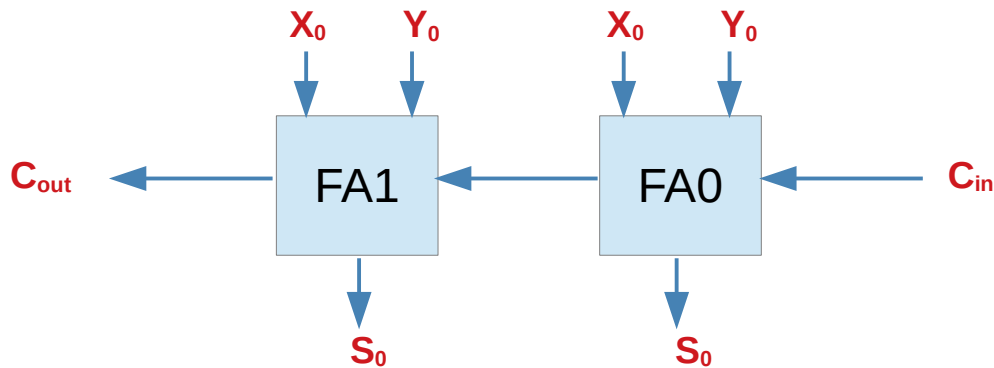

Unless the two FA's are in **propagate** mode, the transition of  $C_{in}$  does not affect the transition of  $C_{out}$


Critical path – all FA's in **propagate** mode

Broken paths for any FA in other mode  
- kill mode, **generate** mode

<https://electronics.stackexchange.com/questions/21251/critical-path-for-carry-skip-adder>


# K, P, and G conditions in a 2-bit adder (2)

X	Y		
0	0	K	Kill ( $=\bar{P}G$ )
0	1	P	Propagate
1	0	P	Propagate
1	1	G	Generate

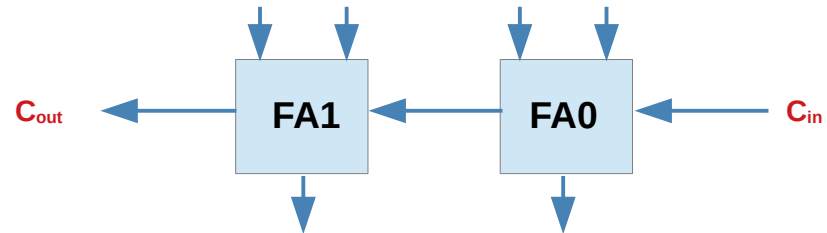


K	K	0
K	K	1
K	P	0
K	P	1
K	G	0
K	G	1
P	K	0
P	K	1
P	P	0
P	P	1
P	G	0
P	G	1
G	K	0
G	K	1
G	P	0
G	P	1
G	G	0
G	G	1
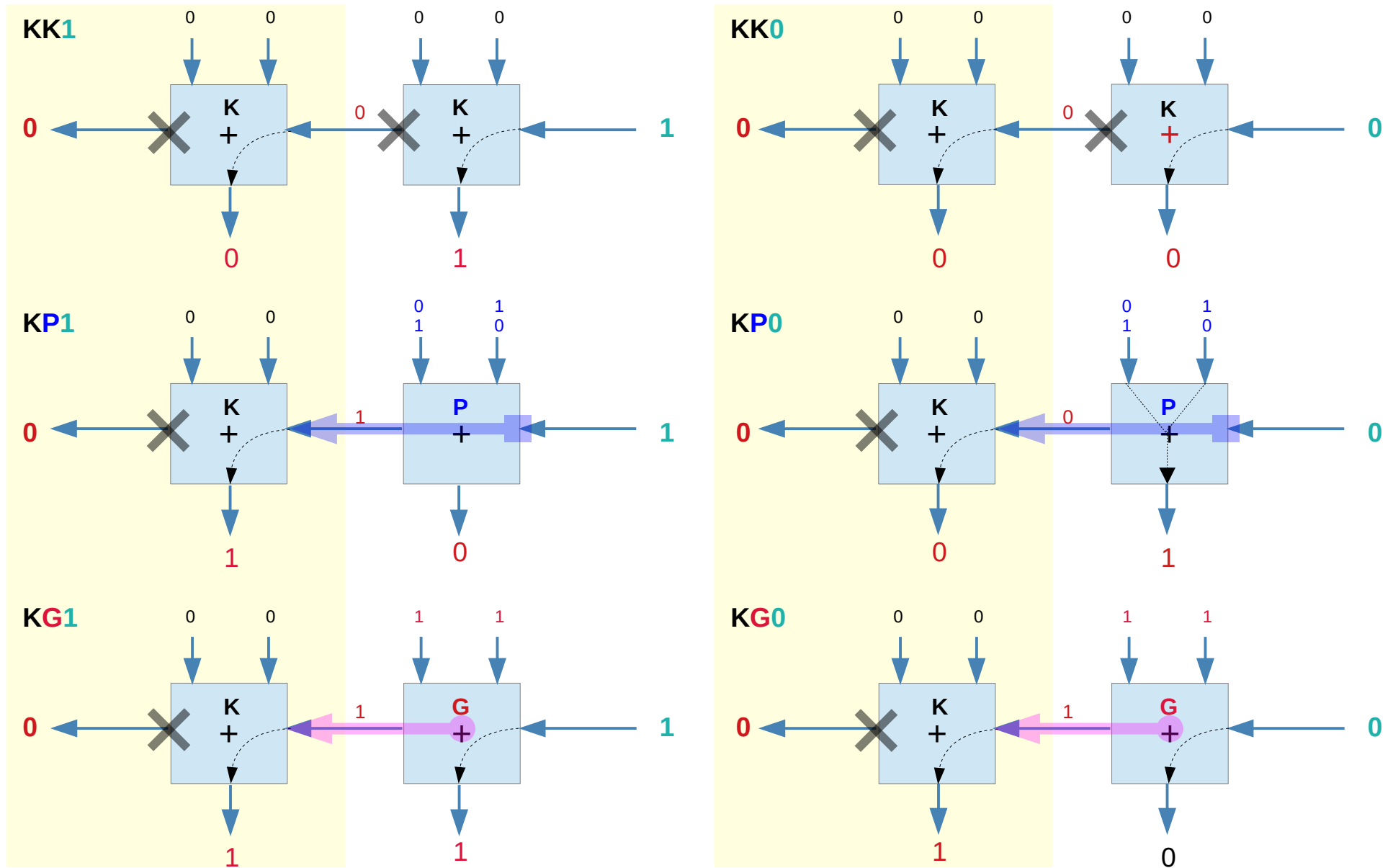
# 1. Cases when **FA1** is in the **K** mode



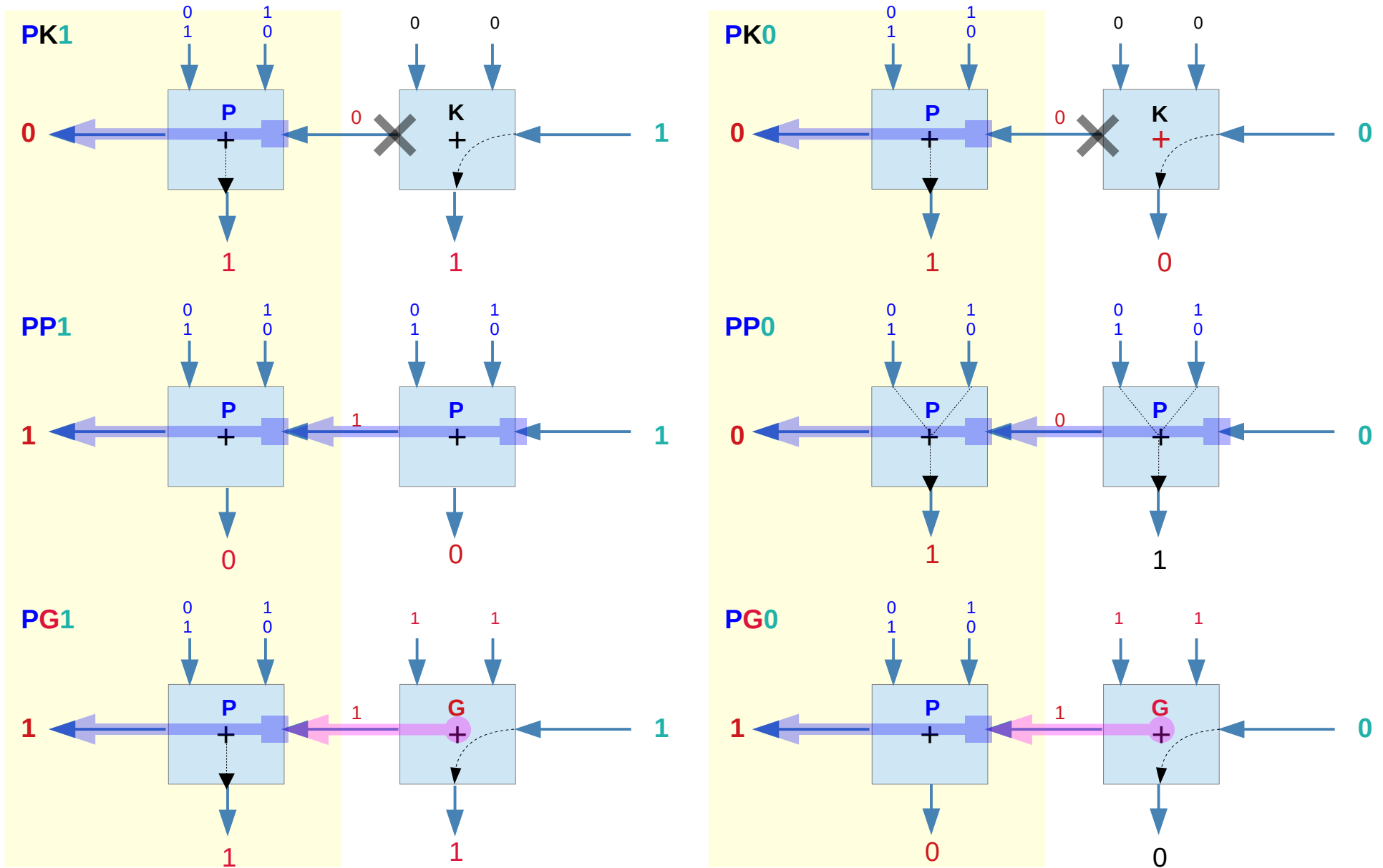
## 2. Cases when **FA1** is in the **P** mode







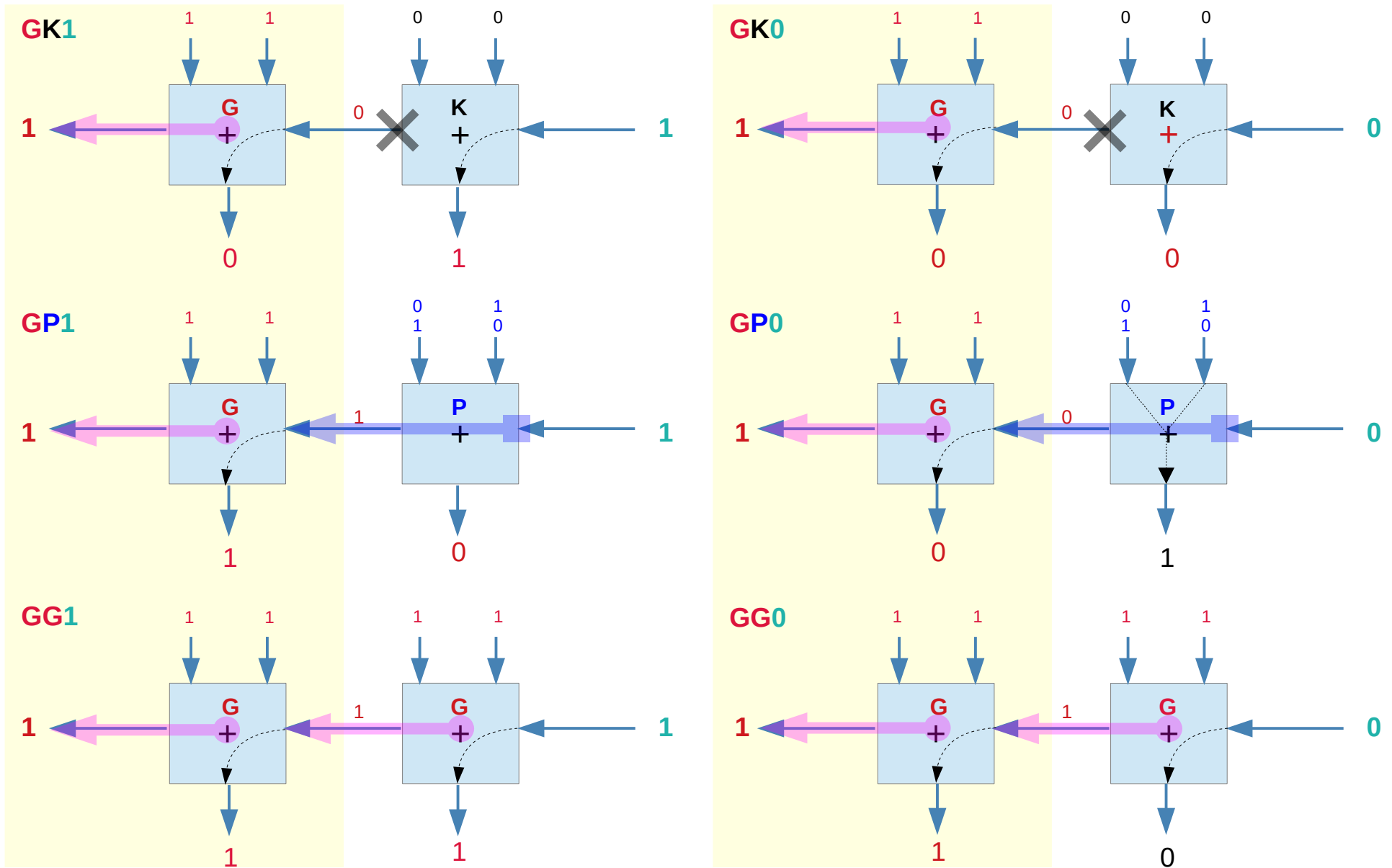
### 3. Cases when **FA1** is in the **G** mode




# Cases for $C_{out} = 1$

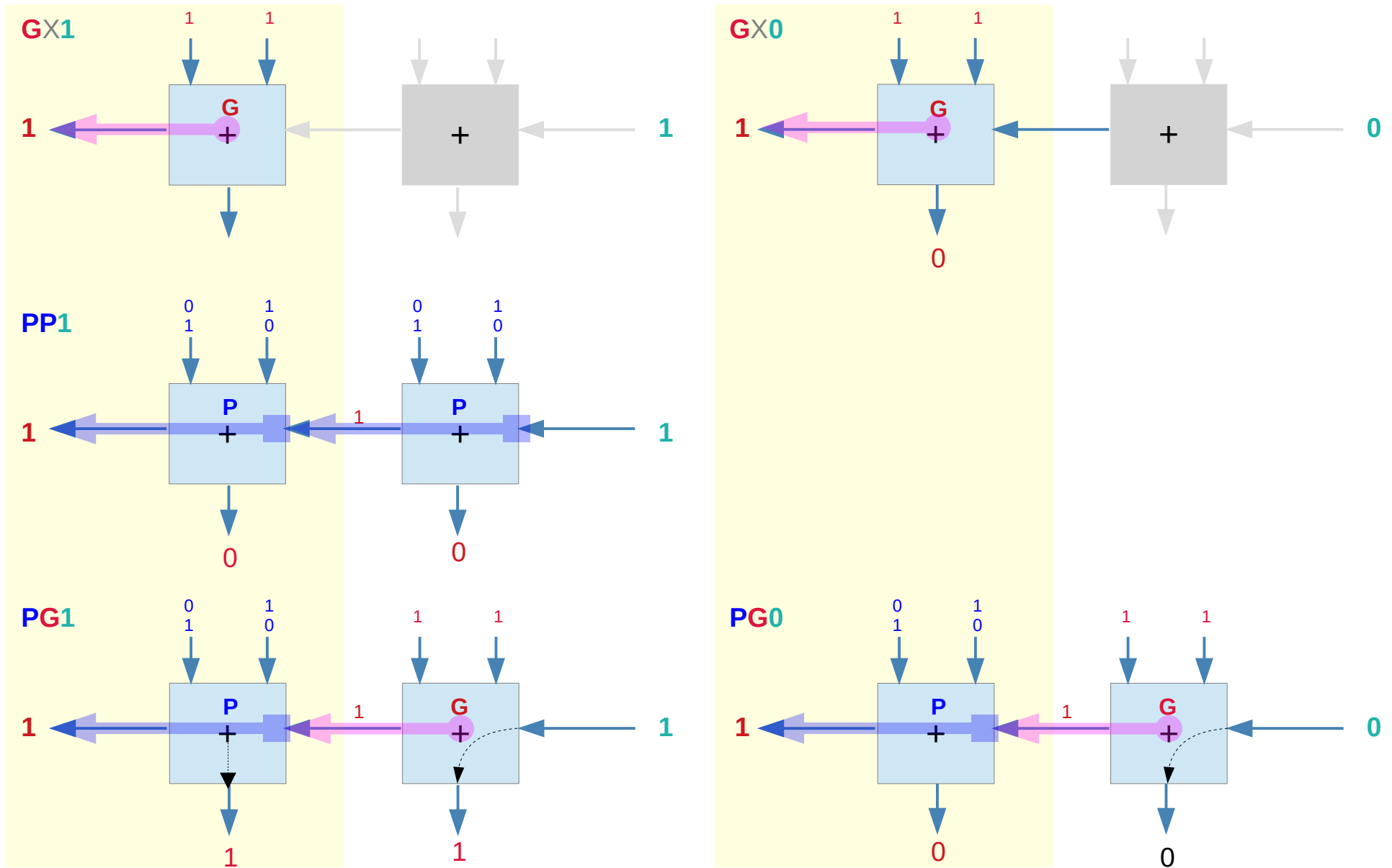

# Cases for $C_{out} = 0$

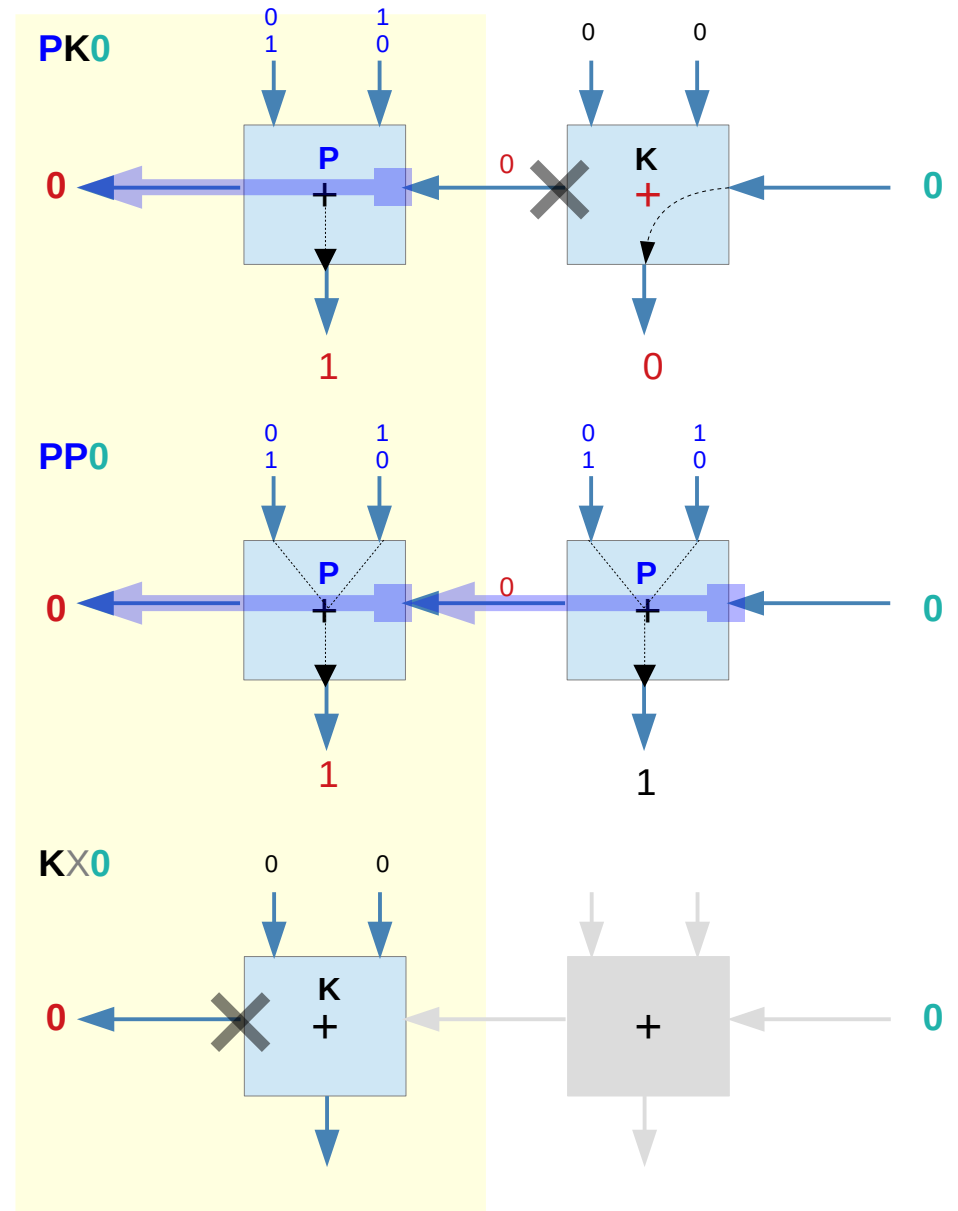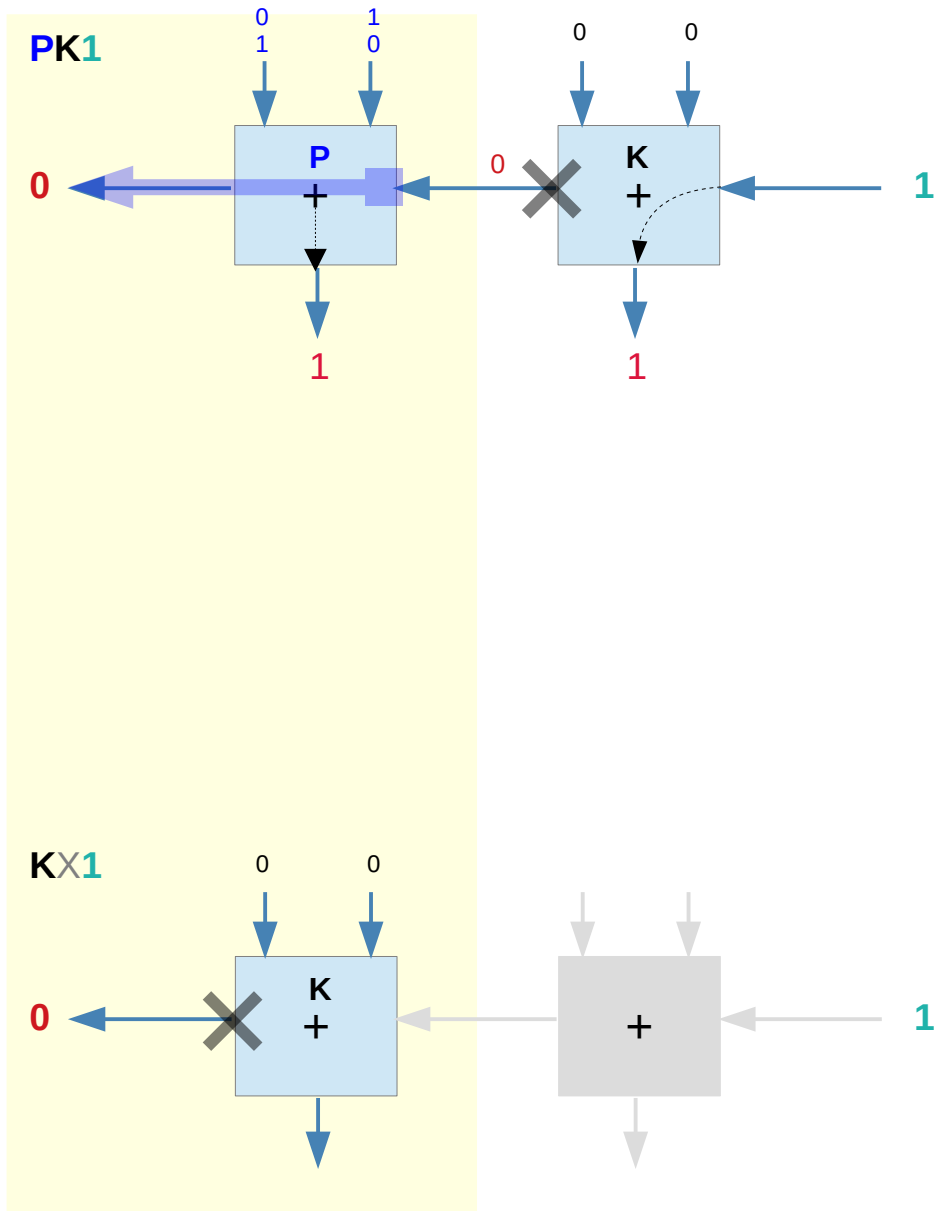


# FA with P & G

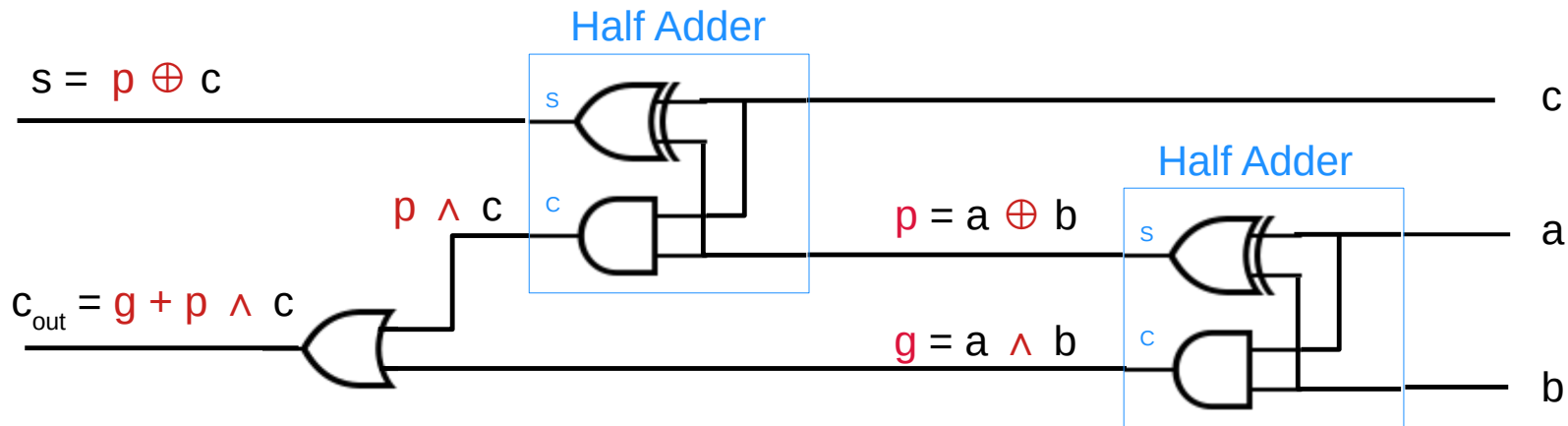

Half Adder  
 $S = a \oplus b$   
 $C = a \wedge b$

a	b	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

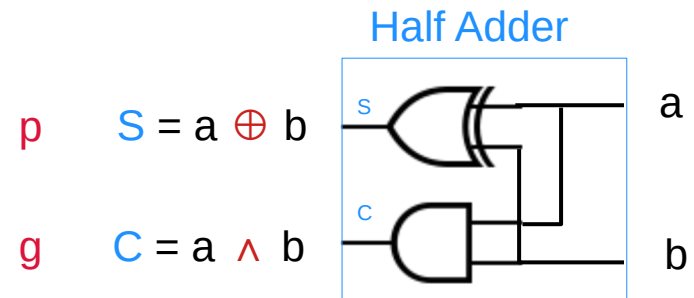

Full adder with additional generate and propagate signals.

[https://en.wikipedia.org/wiki/Carry-skip\\_adder](https://en.wikipedia.org/wiki/Carry-skip_adder)

# Ripple Carry Adder


$$p_i = a_i \oplus b_i$$

$$g_i = a_i \wedge b_i$$

$$\begin{aligned} c_1 &= g_0 + p_0 \wedge c_0 \\ c_2 &= g_1 + p_1 \wedge c_1 \\ c_3 &= g_2 + p_2 \wedge c_2 \\ c_4 &= g_3 + p_3 \wedge c_3 \end{aligned}$$


generated carry

propagated carry

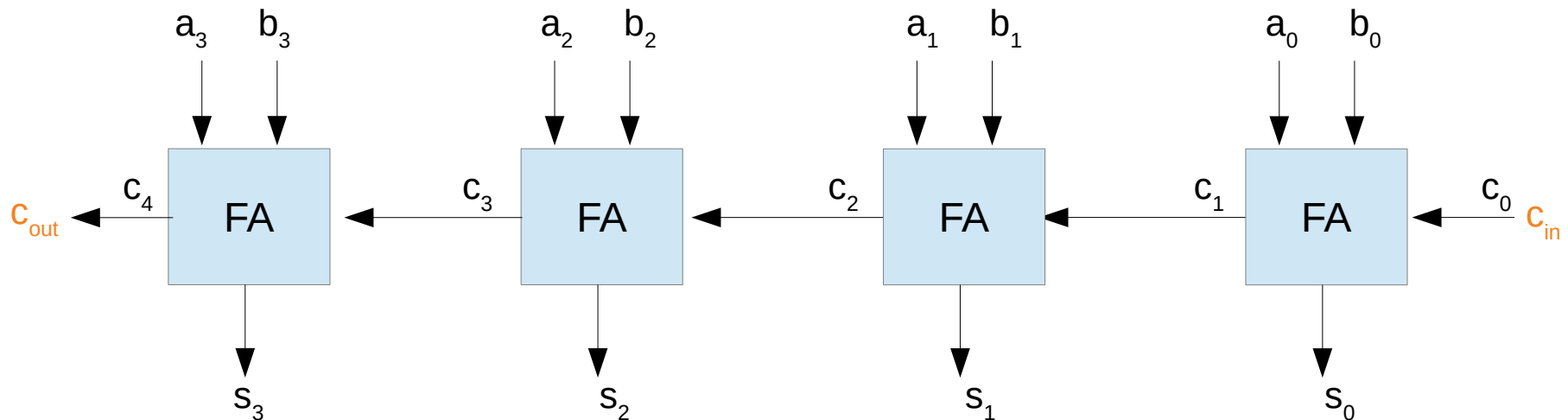

[https://en.wikipedia.org/wiki/Carry-skip\\_adder](https://en.wikipedia.org/wiki/Carry-skip_adder)

# 4-bit Full Adder with P and G

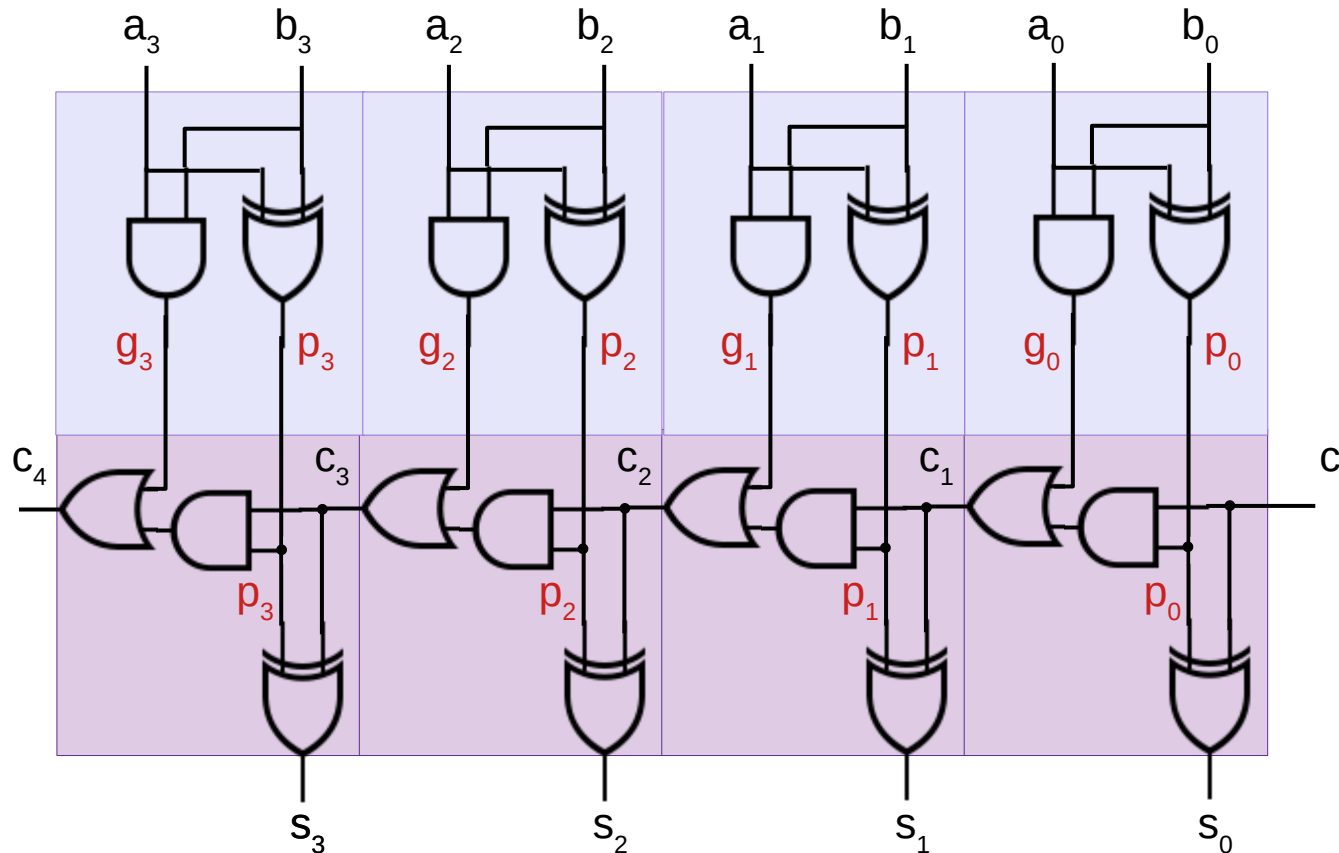

**Half Adder**

$$p_i = a_i \oplus b_i$$

$$g_i = a_i \wedge b_i$$


**Half Adder**

$$c_{i+1} = g_i + p_i \wedge c_i$$

$$s_i = p_i \oplus c_i$$


<https://upload.wikimedia.org/wikiversity/en/1/18/RCA.Note.H.1.20151215.pdf>

# C<sub>0</sub> propagation condition

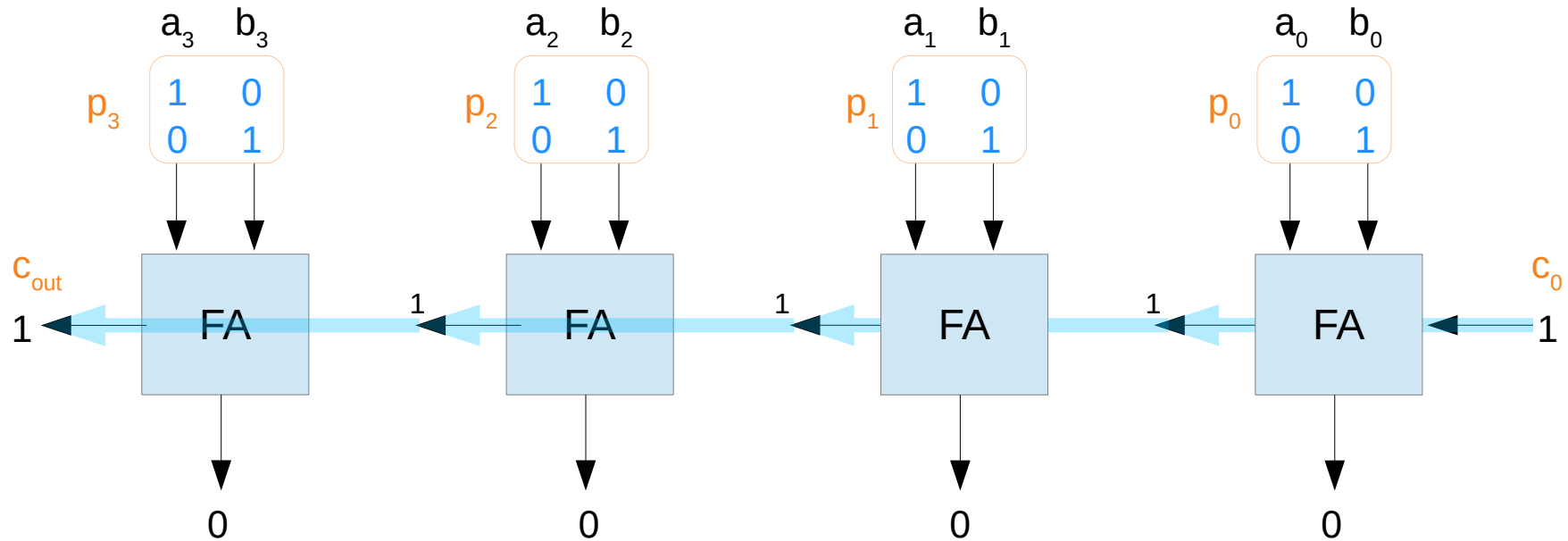


$c_0$  can be propagated to  $c_{out}$  only when  $s = 1$
 
$$\begin{aligned}
 s &= p_3 \wedge p_2 \wedge p_1 \wedge p_0 = p_{[3:0]} \\
 &= (a_3 \oplus b_3) \\
 &\quad \wedge (a_2 \oplus b_2) \\
 &\quad \wedge (a_1 \oplus b_1) \\
 &\quad \wedge (a_0 \oplus b_0)
 \end{aligned}$$



[https://en.wikipedia.org/wiki/Carry-skip\\_adder](https://en.wikipedia.org/wiki/Carry-skip_adder)

# Carry Skip Adder

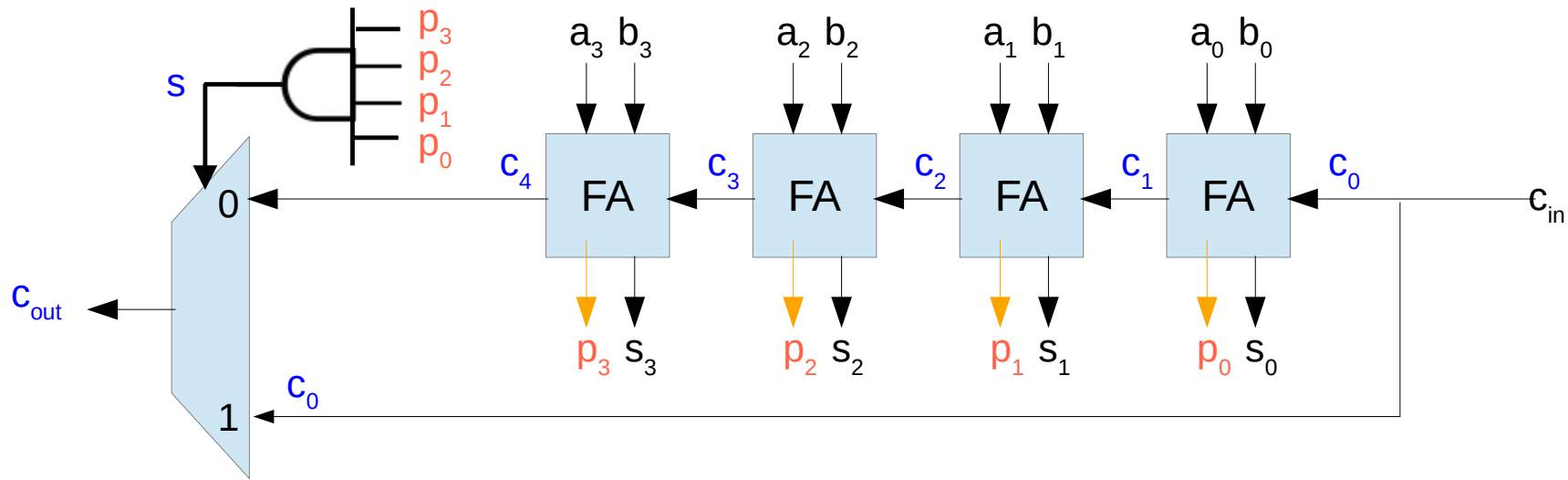

The n-bit Carry Skip Adder consists of

a n-bit **carry-ripple-chain**,  
a n-input **AND-gate** and  
one **multiplexer**.

a multiplexer switches  
either the last carry-bit  $c_n$  or the carry-in  $c_0$   
to the carry-out signal  $c_{out}$

$$s = p_3 \wedge p_2 \wedge p_1 \wedge p_0 = p_{[3:0]}$$



when  $s = 1$ ,  $c_{out} \leftarrow c_0$

otherwise, internally generated carries  
can be propagated to  $c_{out} \leftarrow c_4$

[https://en.wikipedia.org/wiki/Carry-skip\\_adder](https://en.wikipedia.org/wiki/Carry-skip_adder)



# Carry Skip Adder

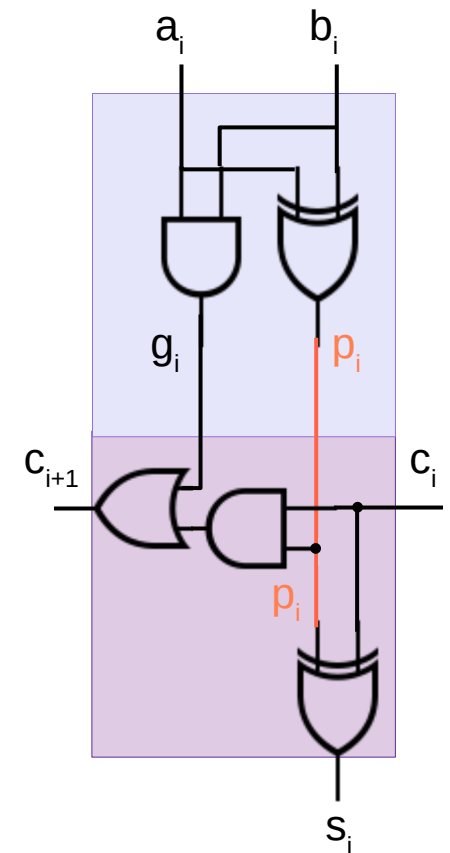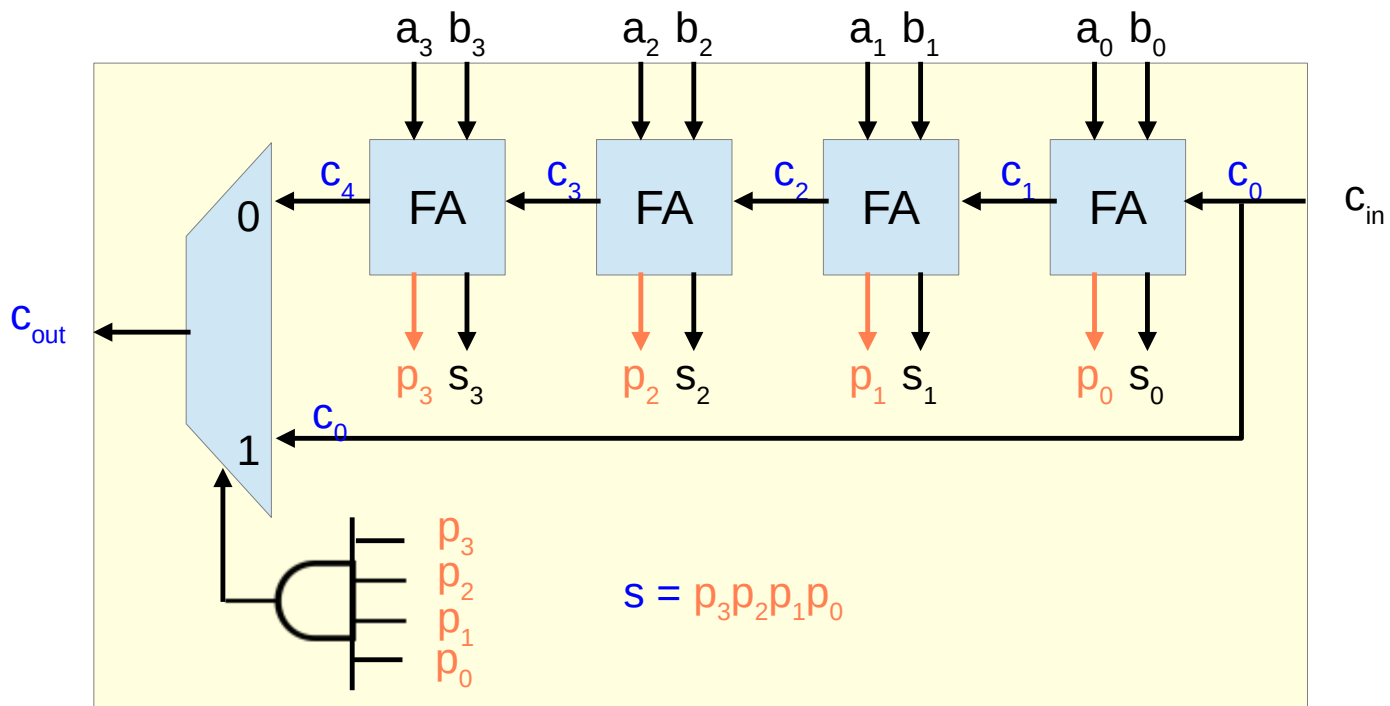


[https://en.wikipedia.org/wiki/Carry-skip\\_adder](https://en.wikipedia.org/wiki/Carry-skip_adder)

# Carry Skip Adder

The **critical path** of a Carry Skip Adder begins at the first full adder, passes through all adders and ends at the sum bit  $s_{n-1}$

Since a single *n-bit* Carry Skip Adder has no real speed benefit compared to a *n-bit* Ripple Carry Adder

$$T_{CSA}(n) = T_{RCA}(n)$$

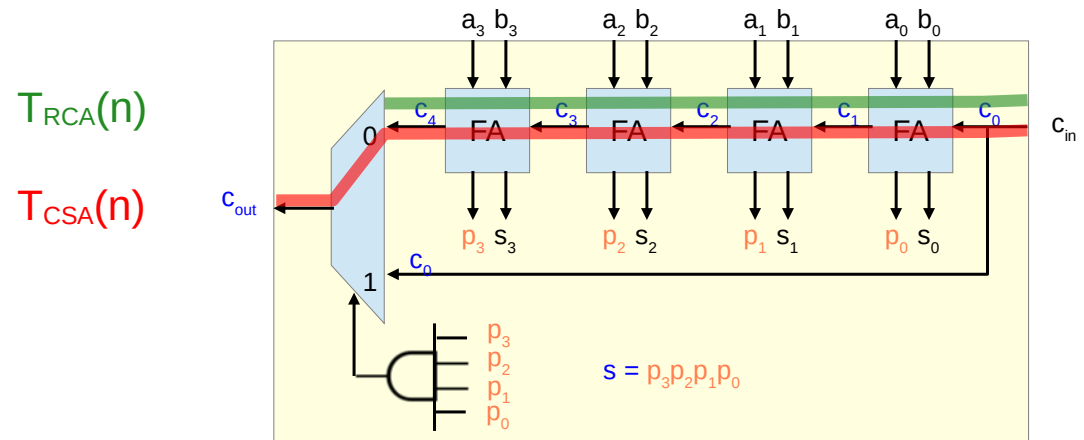

[https://en.wikipedia.org/wiki/Carry-skip\\_adder](https://en.wikipedia.org/wiki/Carry-skip_adder)

# Carry Skip Adder

the skip logic consists of a **k-input** AND gate and one MUX



$$T_{SK1} = T_{AND}(k) + T_{MUX}$$

$$T_{SK2} = T_{MUX}$$

delay path through the AND gate

delay path from the ripple carry

... the critical path

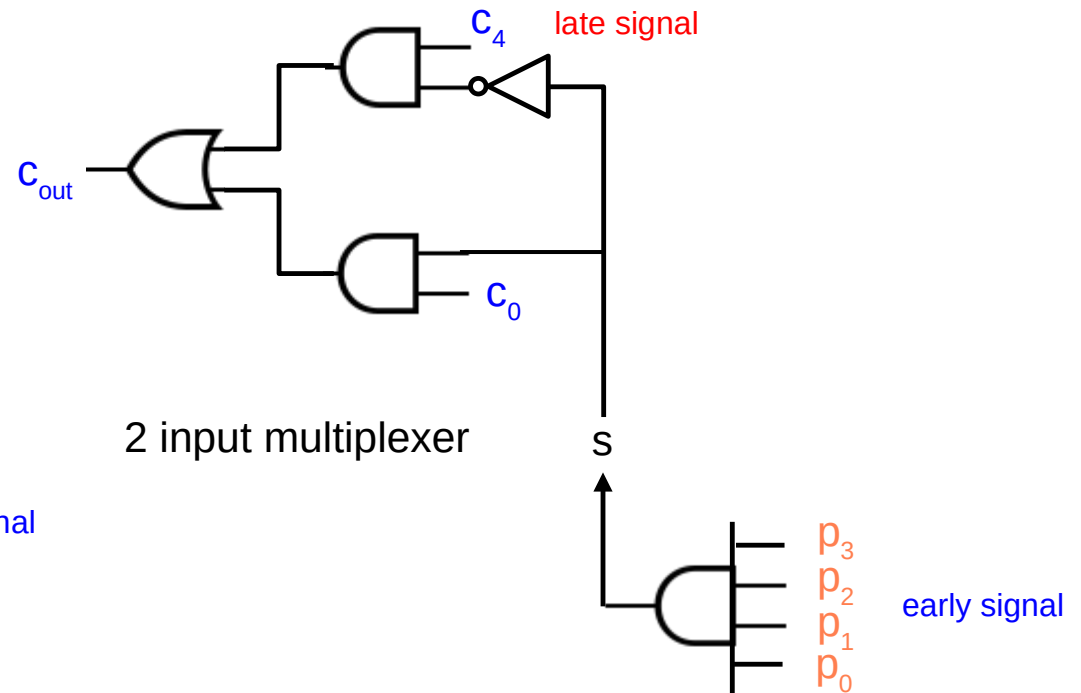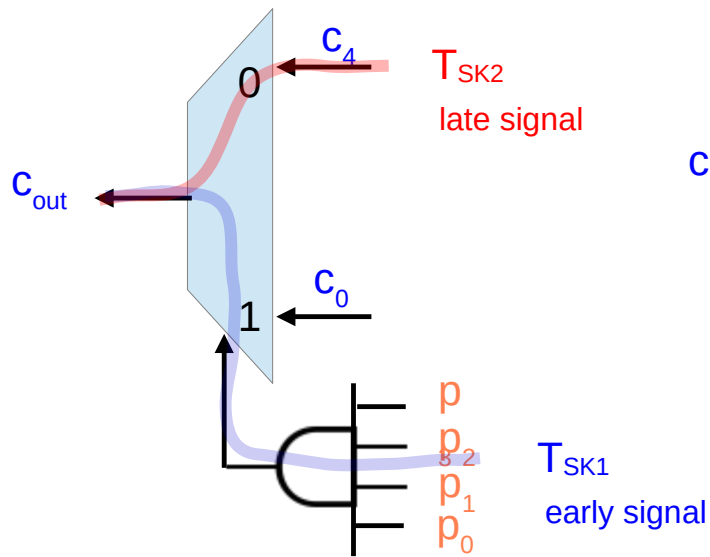

[https://en.wikipedia.org/wiki/Carry-skip\\_adder](https://en.wikipedia.org/wiki/Carry-skip_adder)

# Carry Skip Adder

As the **propagate** signals are computed in parallel and are early available,



$$p_i = a_i \oplus b_i$$

The critical path in a Carry Skip Adder consists of ripple carry path and mux path for ripple carry ( $T_{SK2}$ )

the **critical path** for the skip logic in a Carry Skip Adder consists of the delay imposed by the multiplexer (conditional skip)

$T_{CSK}$  skip logic delay in the critical path

$$T_{CSK} = T_{SK2} = T_{MUX} = 2D$$

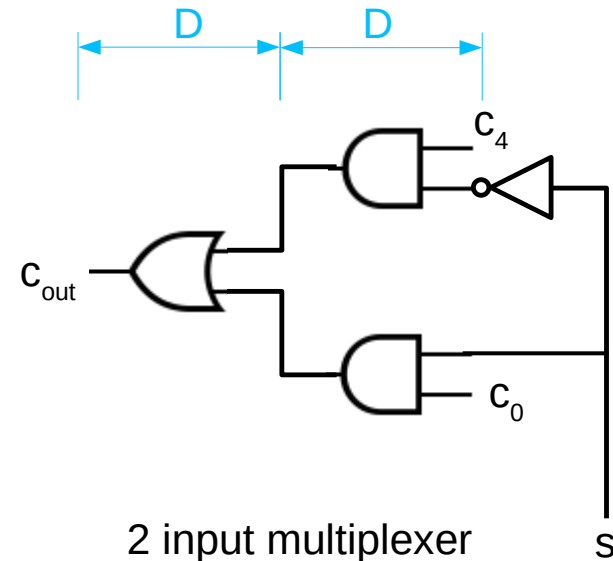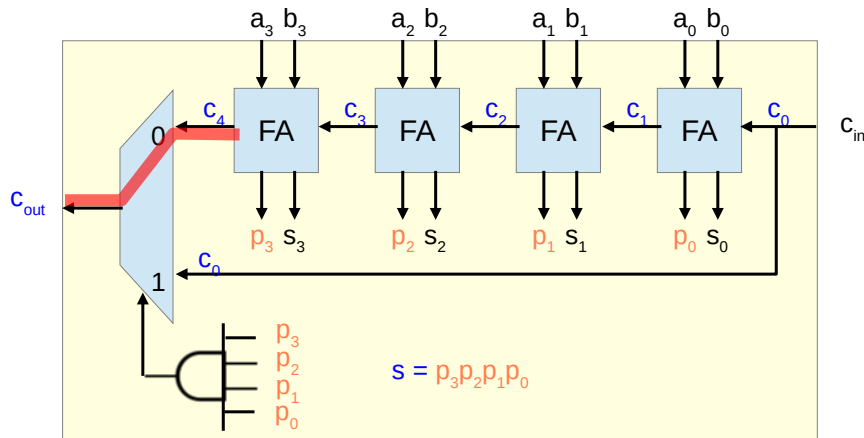

[https://en.wikipedia.org/wiki/Carry-skip\\_adder](https://en.wikipedia.org/wiki/Carry-skip_adder)

# Block Carry Skip Adder

Block carry skip adders are composed of a number of carry skip adders

There are two types of block carry skip adders

The two operands  $A = (a_{n-1}, a_{n-2}, \dots, a_1, a_0)$  and  $B = (b_{n-1}, b_{n-2}, \dots, b_1, b_0)$  are split in  $k$  blocks of  $(m_k, m_{k-1}, \dots, m_2, m_1)$  bits

- Why are **block** carry skip adders used
- Should the **block size** be constant or variable?
- Fixed **block size** vs. variable **block size**



Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

# Fixed-size Block Carry Skip Adder

Carry Skip Adders are chained to reduce the overall critical path,  
(Block Carry Skip Adders)

Fixed size block Carry Skip Adders (FCSA) split the  $n$  bits of the input bits  
into blocks of  $k$  bits each, resulting in  $R = n / k$  blocks.

**Fixed-size block CSA  
(FCSA)**

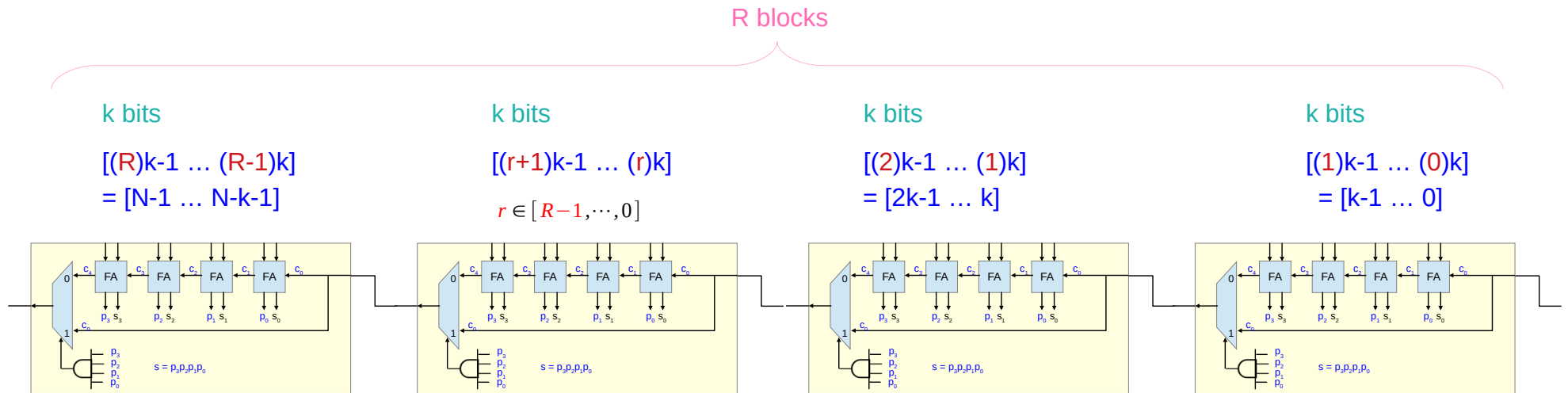 

# Carry Skip Adder

the critical path

the longest carry path must be

- generate in the first block
- terminated in the last block
- propagated in the blocks between the first and the last

X	Y		
0	0	K	Kill ( $=\overline{PG}$ )
0	1	P	Propagate
1	0	P	Propagate
1	1	G	Generate

Fixed-size block CSA  
(FCSA)

R groups

k bits

$$n = R \cdot k$$


the last block

carry terminated in  
the last FA

(R-2) blocks

the first block

carry generated in  
the first FA

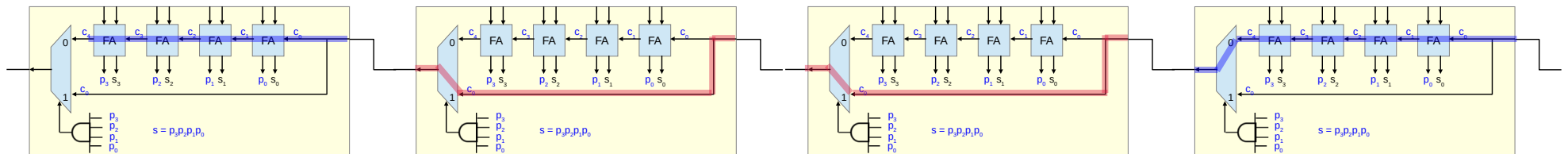

[https://en.wikipedia.org/wiki/Carry-skip\\_adder](https://en.wikipedia.org/wiki/Carry-skip_adder)

# Carry Skip Adder

The critical path consists of


- the ripple path and the skip element of the first block  
 $T_{CRA(k)} + T_{CSK}$
- the skip paths that are enclosed between the first and the last block  
 $(R-2)T_{CSK}$
- finally the ripple path of the last block  
 $T_{CRA(k)}$

Fixed-size block CSA  
(FCSA)

R groups

k bits


$$n = R \cdot k$$

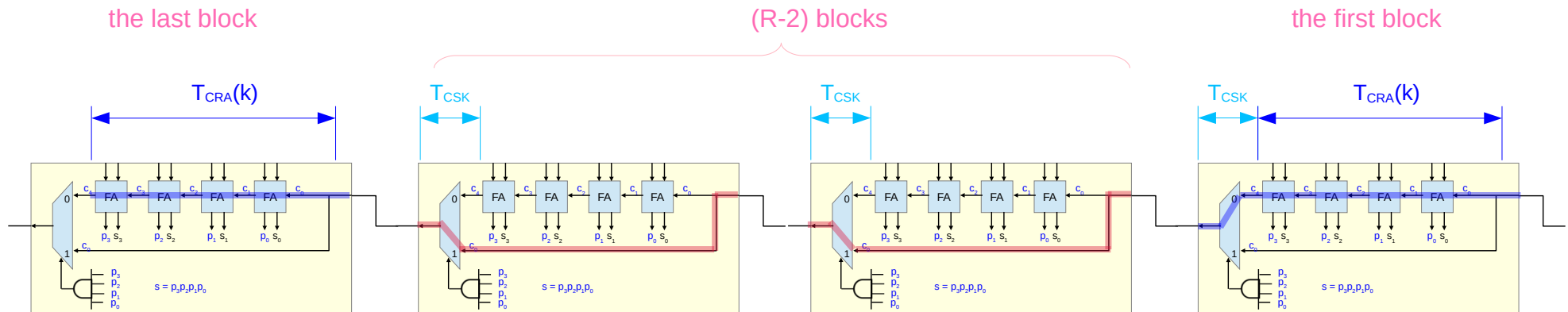

[https://en.wikipedia.org/wiki/Carry-skip\\_adder](https://en.wikipedia.org/wiki/Carry-skip_adder)



# 4-bit Full Adder with P and G

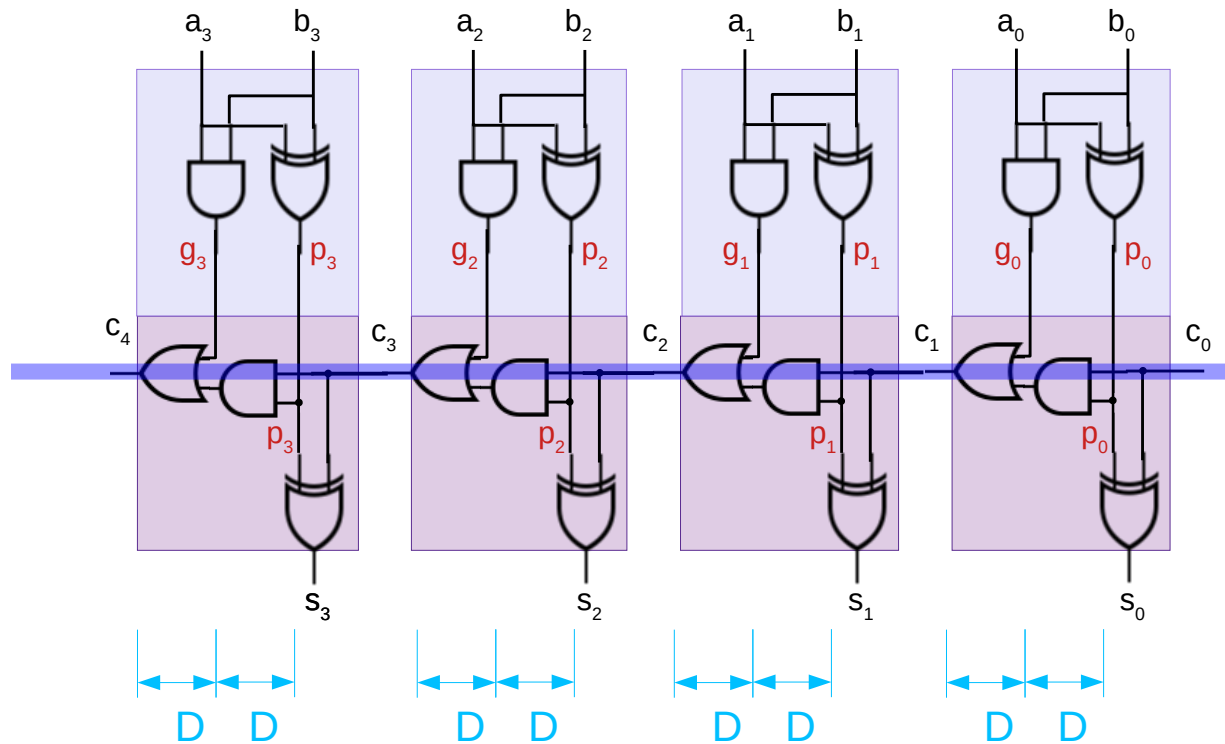

k bits

$$T_{CRA}(k) = 2D \cdot k$$

<https://upload.wikimedia.org/wikiversity/en/1/18/RCA.Note.H.1.20151215.pdf>

# Critical Path Delay

## Fixed-size block CSA (FCSA)

The critical path consists of

- the ripple path and the skip element of the first block  $T_{CRA}(k) + T_{CSK}$
- the skip paths that are enclosed between the first and the last block  $(R-2)T_{CSK}$
- finally the ripple path of the last block  $T_{CRA}(k)$

$$\begin{aligned}T_{FCSA}(n) &= T_{CRA}(k) + T_{CSK} + (R-2)T_{CSK} + T_{CRA}(k) \\ &= k2D + 2D + (R-2)2D + k2D \\ &= k2D + 2D + (R-1)2D - 2D + k2D \\ &= k2D + (R-1)2D + k2D \\ &= 2k2D + (R-1)2D \\ &= (2k+R)2D \\ &= (2k+n/k)2D\end{aligned}$$

$$\begin{aligned}&= k2D + 3D + (R-1)2D + (k+2)2D \\ &= 3D + k2D + R2D - 2D + k2D + 4D \\ &= (2k+R)2D + 5D\end{aligned}$$

R groups

k bits

$$n = R \cdot k$$

# Optimal block size k

$$\begin{aligned}T_{\text{FCSA}}(n) &= T_{\text{CRA}}(k) + T_{\text{CSK}} + (R-2)T_{\text{CSK}} + T_{\text{CRA}}(k) \\ &= (2k+R)2D \\ &= (2k+n/k)2D\end{aligned}$$

The optimal block size k for a given adder width n

$$dT_{\text{FCSA}}(n) / dk = 0 \qquad \frac{dT_{\text{FCSA}}(n)}{dk} = 0$$

$$(2-n(1/k^2)) = 0$$

$$2 = n/k^2$$

$$k^2 = n / 2$$

$$k = \text{sqrt}(n/2)$$

$$5.6 = \text{sqrt}(64/2) \qquad n = 64\text{bits} \rightarrow k = 6$$

$$4 = \text{sqrt}(32/2) \qquad n = 32\text{bits} \rightarrow k = 4$$

[https://en.wikipedia.org/wiki/Carry-skip\\_adder](https://en.wikipedia.org/wiki/Carry-skip_adder)

Fixed-size block CSA  
(FCSA)

R groups

k bits


$$n = R \cdot k$$

# Examples of Optimal Block Sizes

$$T_{FCSA,opt}(n) = \left(2k + \frac{n}{k}\right)2D$$

$$T_{FCSA}(32) = (2k + 32/k)2D$$

(2k+32/k)

 

$$4 = \text{sqrt}(32/2) \quad k_{opt} = \sqrt{\frac{n}{2}}$$


n = 32bits  
→ k = 4

[https://en.wikipedia.org/wiki/Carry-skip\\_adder](https://en.wikipedia.org/wiki/Carry-skip_adder)

$$T_{FCSA,opt}(n) = \left(2k + \frac{n}{k}\right)2D$$

$$T_{FCSA}(64) = (2k + 64/k)2D$$

(2k+64/k)

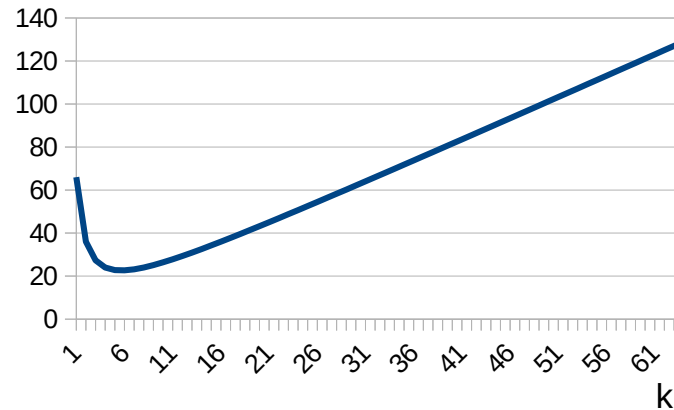

$$5.6 = \text{sqrt}(64/2) \quad k_{opt} = \sqrt{\frac{n}{2}}$$

n = 64bits  
→ k = 6

Fixed-size block CSA  
(FCSA)

R groups

k bits

$$n = R \cdot k$$

# Asymptotic Analysis

$$T_{\text{FCSA}}(n) = (2k+n/k)2D$$

The optimal block size  $k$  for a given adder width  $n$

$$k = \sqrt{n/2}$$

$$\begin{aligned} T_{\text{FCSA, opt}}(n) &= (2\sqrt{n/2} + n/\sqrt{n/2})2D \\ &= (\sqrt{2n} + \sqrt{n^2 / n / 2}) 2D \\ &= (\sqrt{2n} + \sqrt{2n})2D \\ &= (2\sqrt{2n})2D \end{aligned}$$

$$\begin{aligned} T_{\text{FCSA, opt}}(n) &= \left(2\sqrt{n/2} + \frac{n}{\sqrt{n/2}}\right) 2D \\ &= (2\sqrt{2n}) 2D \quad \text{when } k_{\text{opt}} = \sqrt{\frac{n}{2}} \end{aligned}$$

[https://en.wikipedia.org/wiki/Carry-skip\\_adder](https://en.wikipedia.org/wiki/Carry-skip_adder)

Fixed-size block CSA  
(FCSA)


$R$  groups

$k$  bits

$$n = R \cdot k$$


$$T_{\text{CRA}}(n) = 2D \cdot n$$
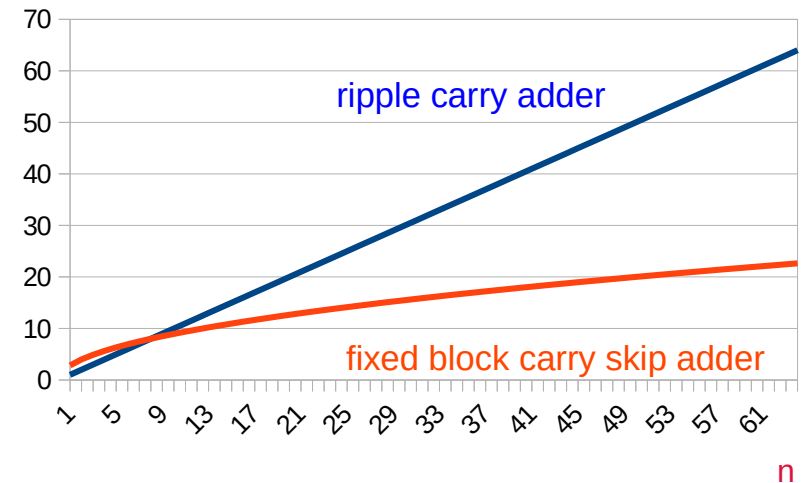
$$T_{\text{FCSA, opt}}(n) = 2D \cdot (2\sqrt{2n})$$



 
# Critical Carry Path (1)

For longest carry path, if any block generates a carry, that carry will propagate through the remaining 3 FA's of the block



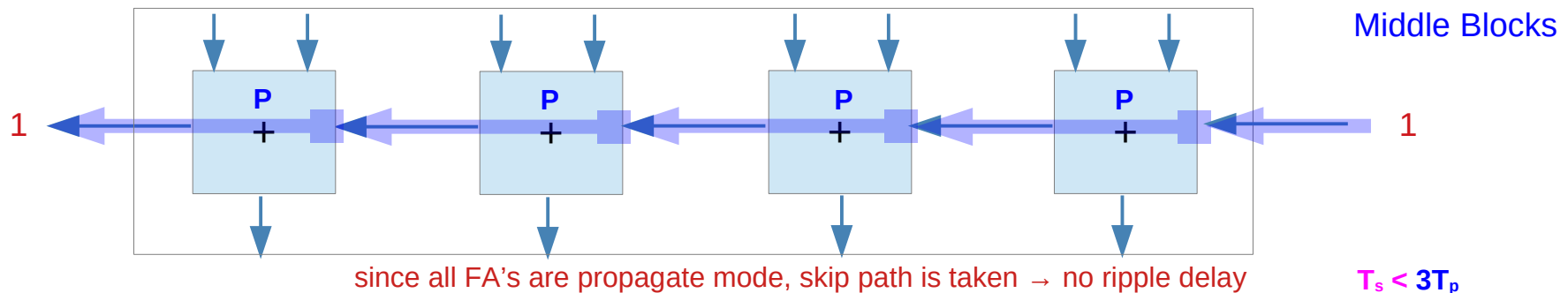
and then through the carry skip gates to the final block,



More Fast Adders, Ivor Page, University of Texas at Dallas

 
# Critical Carry Path (2)

At the final block, it may have to propagate through 3 FA's to reach the most significant adder



More Fast Adders, Ivor Page, University of Texas at Dallas


# Critical Carry Path (3)

 

More Fast Adders, Ivor Page, University of Texas at Dallas



# Critical Carry Path (4)

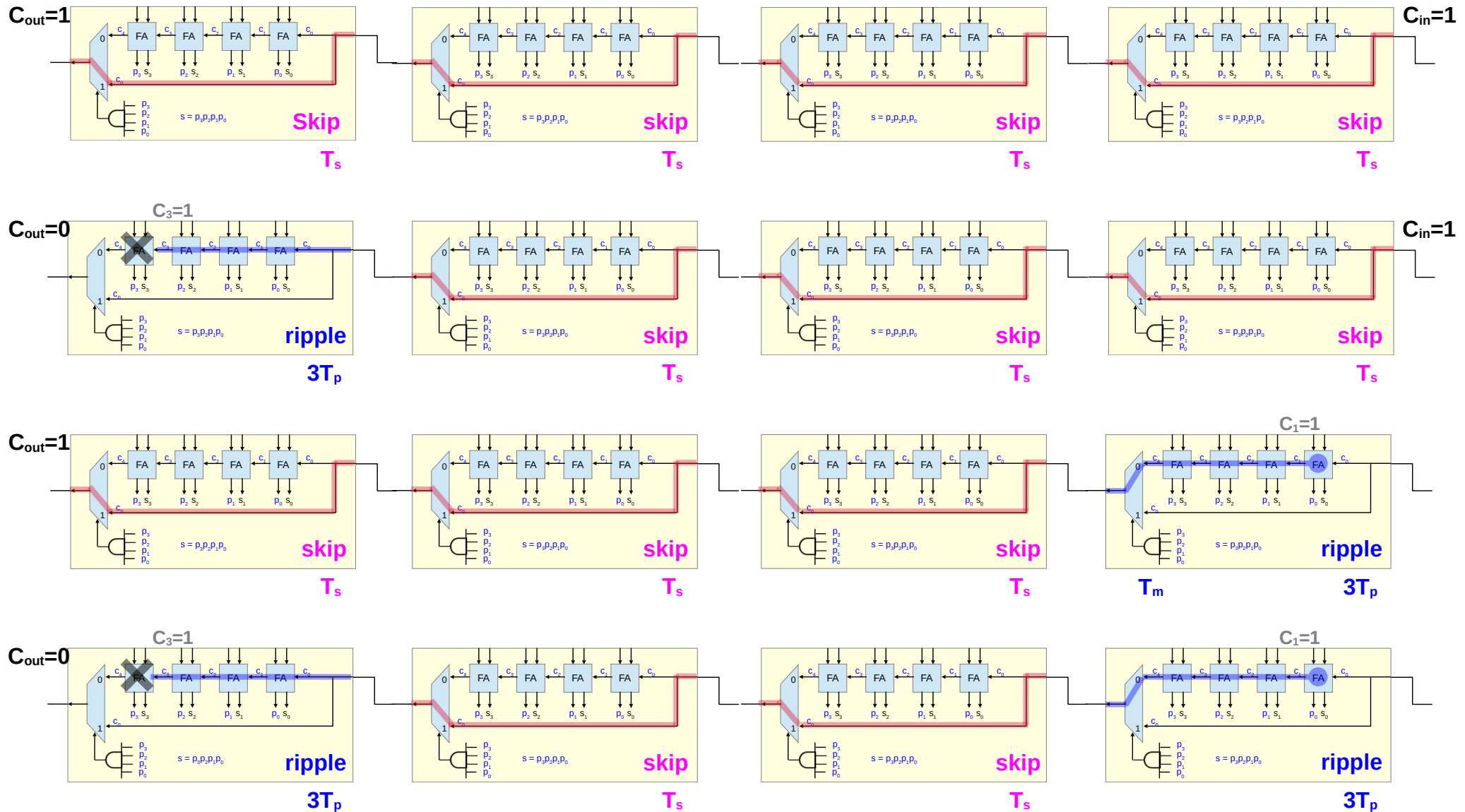

# Carry Skip Adder

## Fixed-size block CSA (FCSA)


The longest delay path from  $c_1$  to  $c_{n-1}$

begins with a carry generated in **FA0** in the least significant **block 0**, propagates through **FA3** in that block, then through the skip element (MUX can be replaced with OR gate), then through carry skip units of  $(R-2)$  blocks, and then through  $fa_0, fa_1, fa_2$  in the most significant **block  $(R-1)$** , to the  $c_{n-1}$  signal

R groups

k bits

$$n = R \cdot k$$

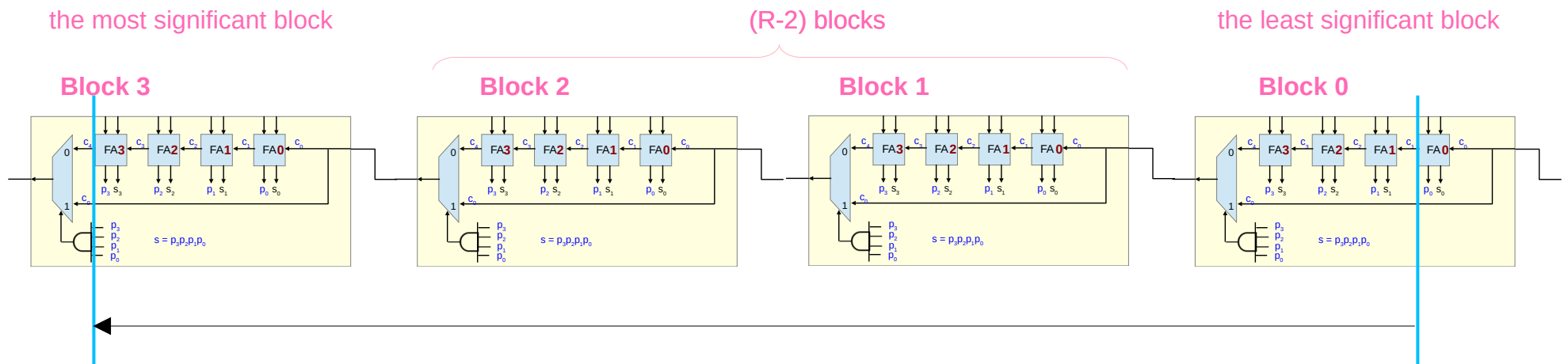

More Fast Adders, Ivor Page, University of Texas at Dallas

# Carry Skip Adder

The longest delay path from  $c_1$  to  $c_{n-1}$

$$(k-1)T_p + D + (n/k-2)T_s + (k-1)T_p$$

$T_p$  is the time to propagate a carry through one stage of the full adder (from  $c_i$  to  $c_{i+1}$ )

$T_s$  is the delay through one carry-skip stage

Fixed-size block CSA (FCSA)

R groups


k bits

$$n = R \cdot k$$


More Fast Adders, Ivor Page, University of Texas at Dallas
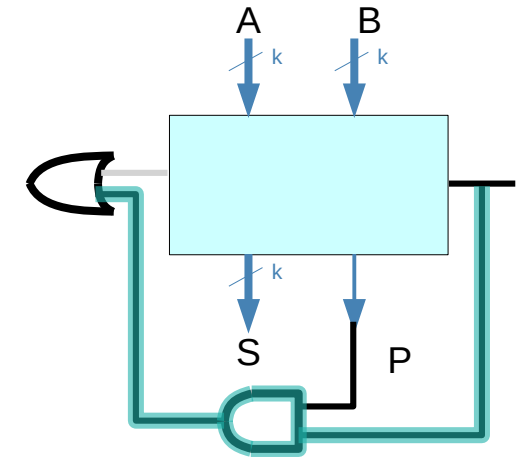
# Carry Skip Adder

A carry signal entering a certain block can be propagated past the block without waiting for the signal to propagate through the 4 individual stages of the block



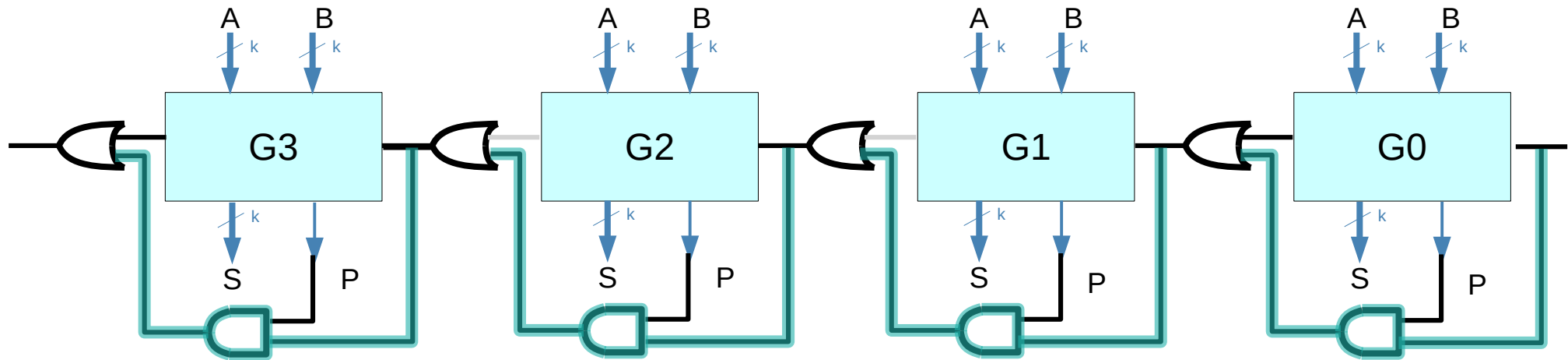If all  $n/4$  blocks propagate, a carry entering the least significant stage will pass to the most significant carry-out in time  $n/4$  times the delay through the carry-skip unit





More Fast Adders, Ivor Page, University of Texas at Dallas

# Carry Skip Adder


Ripple through  $k-1$  bits

$$(k-1) \Delta_{rca}$$

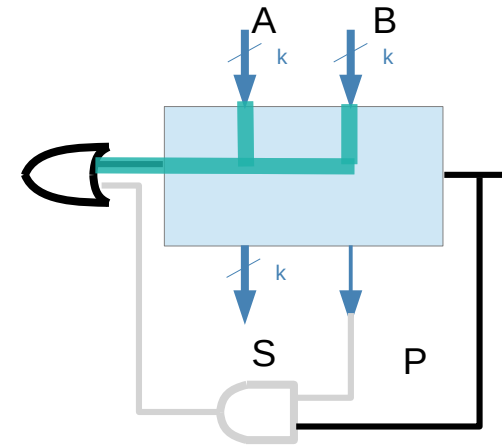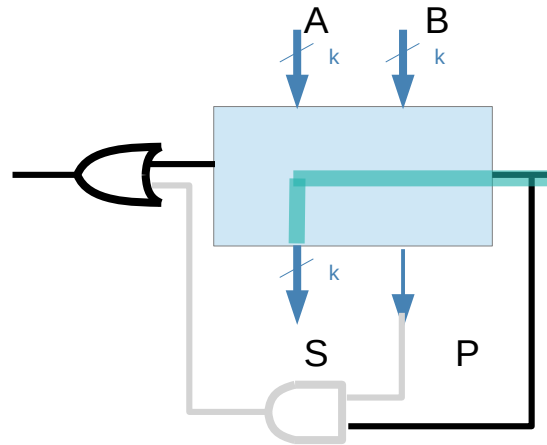

Skip carry

$$\Delta_{SKIP}$$

 

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

# Carry Skip Adder

The maximal delay  $\Delta$  of a Carry Skip Adder is encountered when **carry** is generated in the **least-significant bit** position,

- rippling through  $k-1$  bit positions,
- skipping over  $R-2 = N/k-2$  groups in the middle,
- rippling to the  $k-1$  bits of most significant group and
- being assimilated in the  $N$ -th bit position to produce the sum  $S_N$  :

$$\begin{aligned}\Delta_{\text{CSA}} &= (k - 1) \Delta_{\text{rca}} + (R - 2) \Delta_{\text{SKIP}} + (k - 1) \Delta_{\text{rca}} \\ &= 2 (k - 1) \Delta_{\text{rca}} + (R - 2) \Delta_{\text{SKIP}} \\ &= 2 (k - 1) \Delta_{\text{rca}} + (N/k - 2) \Delta_{\text{SKIP}}\end{aligned}$$

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers


# Carry Skip Adder

$$\begin{aligned}\Delta_{\text{CSA}} &= (k - 1) \Delta_{\text{rca}} + (R - 2) \Delta_{\text{SKIP}} + (k - 1) \Delta_{\text{rca}} \\ &= 2(k - 1) \Delta_{\text{rca}} + (R - 2) \Delta_{\text{SKIP}} \\ &= 2(k - 1) \Delta_{\text{rca}} + (N/k - 2) \Delta_{\text{SKIP}}\end{aligned}$$

Carry Skip Adder is faster than RCA at the expense of a few relatively simple modifications.



The delay is still linearly dependent on the size of the adder  $N$ , however this linear dependence is reduced by a factor of  $1/k$

$$N = R \cdot k$$

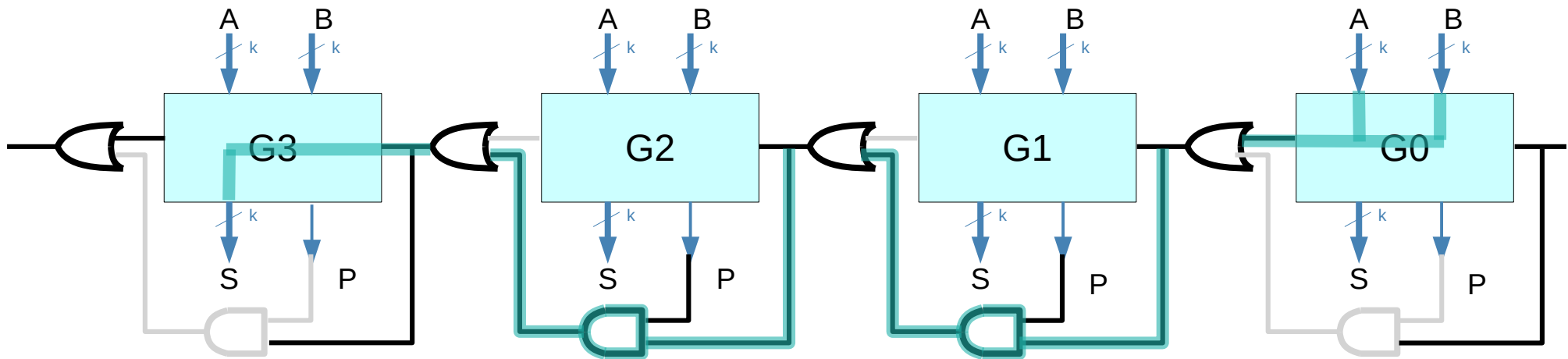

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

# Design C (9) – When Cout1 = 1

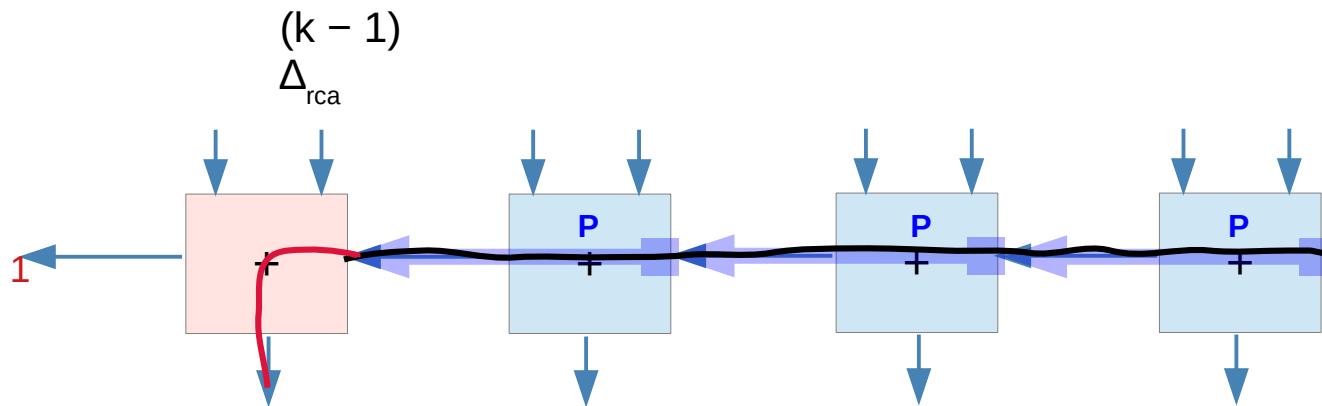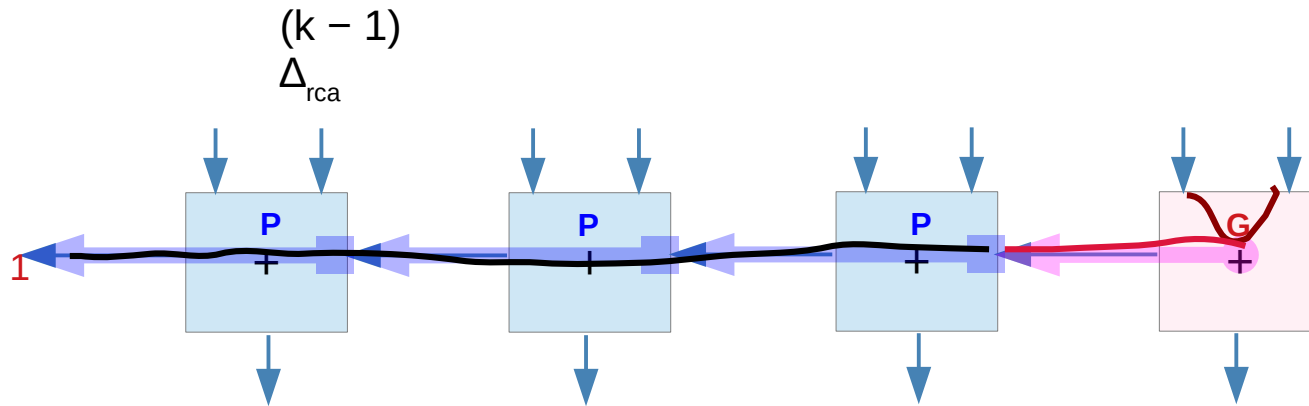

High Performance Carry Chains for FPGAs, S. Hauck, M. M. Hosler, T. W. Fry



# Carry Skip Adder

---

If an arbitrary block generated a carry by itself,  
The carry will always propagate to the next block  
However, if the second block generates a carry itself,  
Or kill the carry, then that is the end of the critical path

If the second block propagates the carry, then we see  
The advantage of the CSA architecture

<https://electronics.stackexchange.com/questions/21251/critical-path-for-carry-skip-adder>

<https://electronics.stackexchange.com/questions/21251/critical-path-for-carry-skip-adder>

# Variable size Block Carry Skip Adder

The performance can be improved, ie.  
all carries propagated quickly  
by varying the **block sizes**

Accordingly the **initial blocks** of the adder are  
made smaller so as to quickly detect **carry generates**  
that must be propagated the furthers,  
the **middle blocks** are made larger  
because they are not the problem case,  
and then the **most significant blocks** are again  
made smaller so that the late arriving carry inputs  
can be processed quickly

<https://electronics.stackexchange.com/questions/21251/critical-path-for-carry-skip-adder>

---

## References

- [1] [en.wikipedia.org](https://en.wikipedia.org)
- [2] Parhami, “Computer Arithmetic Algorithms and Hardware Designs”