

# d\_cp2.14

The LaTeX code that creates this quiz is released to the Public Domain  
Attribution for each question is documented in the Appendix

Tuesday 30<sup>th</sup> October, 2018




Latex markup at

<https://en.wikiversity.org/wiki/special:permalink/1892308>

## Contents

		<b>2.1</b>	.....	4	<b>2.5</b>	.....	20
<b>1 Quiz</b>	<b>2</b>	<b>2.2</b>	.....	8	<b>2.6</b>	.....	25
		<b>2.3</b>	.....	11			
<b>2 Renditions</b>	<b>4</b>	<b>2.4</b>	.....	15	<b>3 Attribution</b>		<b>29</b>

# 1 Quiz

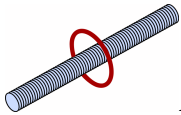


- A long solenoid has a length 0.75 meters, radius 3.1 cm, and 500 turns. It surrounds coil of radius 5.9 meters and 10 turns. If the current in the solenoid is changing at a rate of 200 A/s, what is the emf induced in the surrounding coil?<sup>1</sup>

A. 1.445E-02 V  
**B. 1.589E-02 V**  
 C. 1.748E-02 V  
 D. 1.923E-02 V  
 E. 2.115E-02 V
- An induced emf of 2.0V is measured across a coil of 50 closely wound turns while the current through it increases uniformly from 0.0 to 5.0A in 0.1s. What is the self-inductance of the coil?<sup>2</sup>


A. 3.306E-02 H  
 B. 3.636E-02 H  
**C. 4.000E-02 H**  
 D. 4.400E-02 H  
 E. 4.840E-02 H
- A washer has an inner diameter of 2.5 cm and an outer diameter of 4.5 cm. The thickness is  $h = Cr^{-n}$  where  $r$  is measured in cm,  $C = 3.5mm$ , and  $n = 2.7$ . What is the volume of the washer?<sup>3</sup>

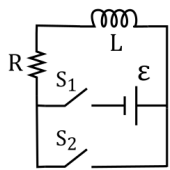A. 6.191E-01 cm<sup>3</sup>  
 B. 6.810E-01 cm<sup>3</sup>  
 C. 7.491E-01 cm<sup>3</sup>  
 D. 8.240E-01 cm<sup>3</sup>  
**E. 9.065E-01 cm<sup>3</sup>**



- Suppose switch  $S_1$  is suddenly closed at time  $t=0$  in the figure shown. What is the current at  $t = 2.0$  s if  $\epsilon = 2.0$  V ,  $R = 4.0 \Omega$  , and  $L = 4.0$  H?<sup>4</sup>

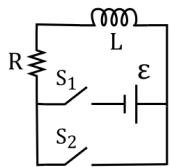A. 3.603E-01 V  
**B. 4.323E-01 V**  
 C. 5.188E-01 V  
 D. 6.226E-01 V  
 E. 7.471E-01 V



- Suppose switch  $S_1$  in the figure shown was closed and remained closed long enough to achieve steady state. At  $t=0$   $S_1$  is opened as  $S_2$  is closed. How long will it take for the energy stored in the inductor to be reduced to 1.0





- A.  $-1.730\text{E}+00\text{ s}$
- B.  $-1.903\text{E}+00\text{ s}$
- C.  $-2.093\text{E}+00\text{ s}$
- D.  $-2.303\text{E}+00\text{ s}$**
- E.  $-2.533\text{E}+00\text{ s}$


6. In an LC circuit, the self-inductance is  $0.02\text{ H}$  and the capacitance is  $8.000\text{E}-06\text{ F}$ . At  $t=0$  all the energy is stored in the capacitor, which has a charge of  $1.200\text{E}-05\text{ C}$ . How long does it take for the capacitor to become completely discharged?<sup>5</sup>

- A.  $6.283\text{E}-04\text{ s}$**
- B.  $6.912\text{E}-04\text{ s}$
- C.  $7.603\text{E}-04\text{ s}$
- D.  $8.363\text{E}-04\text{ s}$
- E.  $9.199\text{E}-04\text{ s}$


## 2 Renditions

### 2.1

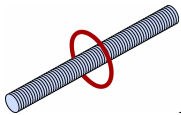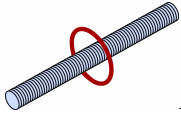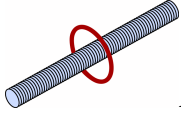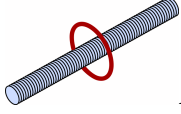
1.  A long solenoid has a length 0.714 meters, radius 4.95 cm, and 578 turns. It surrounds coil of radius 8.72 meters and 16turns. If the current in the solenoid is changing at a rate of 248 A/s, what is the emf induced in the surrounding coil?
- A. 6.667E-02 V
  - B. 7.334E-02 V
  - C. 8.067E-02 V
  - D. 8.874E-02 V
  - E. 9.762E-02 V**
2.  A long solenoid has a length 0.841 meters, radius 3.81 cm, and 516 turns. It surrounds coil of radius 9.2 meters and 11turns. If the current in the solenoid is changing at a rate of 190 A/s, what is the emf induced in the surrounding coil?
- A. 1.735E-02 V
  - B. 1.908E-02 V
  - C. 2.099E-02 V
  - D. 2.309E-02 V**
  - E. 2.540E-02 V
3.  A long solenoid has a length 0.605 meters, radius 4.26 cm, and 597 turns. It surrounds coil of radius 9.08 meters and 12turns. If the current in the solenoid is changing at a rate of 250 A/s, what is the emf induced in the surrounding coil?
- A. 4.551E-02 V
  - B. 5.006E-02 V
  - C. 5.507E-02 V
  - D. 6.057E-02 V
  - E. 6.663E-02 V**
4.  A long solenoid has a length 0.822 meters, radius 4.37 cm, and 515 turns. It surrounds coil of radius 6.12 meters and 14turns. If the current in the solenoid is changing at a rate of 118 A/s, what is the emf induced in the surrounding coil?
- A. 2.229E-02 V
  - B. 2.451E-02 V**
  - C. 2.697E-02 V
  - D. 2.966E-02 V
  - E. 3.263E-02 V

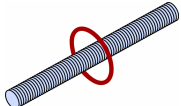- 
5. A long solenoid has a length 0.777 meters, radius 3.45 cm, and 557 turns. It surrounds coil of radius 6.01 meters and 10turns. If the current in the solenoid is changing at a rate of 184 A/s, what is the emf induced in the surrounding coil?


- A. 1.463E-02 V
- B. 1.609E-02 V
- C. 1.770E-02 V
- D. 1.947E-02 V**
- E. 2.142E-02 V

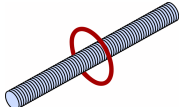- 
6. A long solenoid has a length 0.567 meters, radius 3.35 cm, and 555 turns. It surrounds coil of radius 5.73 meters and 9turns. If the current in the solenoid is changing at a rate of 281 A/s, what is the emf induced in the surrounding coil?


- A. 3.446E-02 V**
- B. 3.790E-02 V
- C. 4.169E-02 V
- D. 4.586E-02 V
- E. 5.045E-02 V

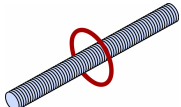- 
7. A long solenoid has a length 0.794 meters, radius 4.45 cm, and 568 turns. It surrounds coil of radius 6.81 meters and 9turns. If the current in the solenoid is changing at a rate of 246 A/s, what is the emf induced in the surrounding coil?


- A. 3.890E-02 V**
- B. 4.279E-02 V
- C. 4.707E-02 V
- D. 5.177E-02 V
- E. 5.695E-02 V

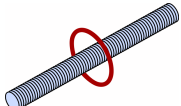- 
8. A long solenoid has a length 0.864 meters, radius 3.37 cm, and 522 turns. It surrounds coil of radius 7.87 meters and 13turns. If the current in the solenoid is changing at a rate of 290 A/s, what is the emf induced in the surrounding coil?

- A. 2.917E-02 V
- B. 3.208E-02 V**
- C. 3.529E-02 V
- D. 3.882E-02 V
- E. 4.270E-02 V

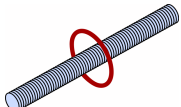
- 
9. A long solenoid has a length 0.974 meters, radius 4.72 cm, and 587 turns. It surrounds coil of radius 8.65 meters and 17turns. If the current in the solenoid is changing at a rate of 146 A/s, what is the emf induced in the surrounding coil?

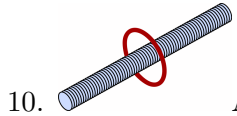- A. 2.823E-02 V
- B. 3.105E-02 V
- C. 3.416E-02 V
- D. 3.757E-02 V
- E. 4.133E-02 V**




10. A long solenoid has a length 0.896 meters, radius 4.28 cm, and 550 turns. It surrounds coil of radius 6.65 meters and 9 turns. If the current in the solenoid is changing at a rate of 204 A/s, what is the emf induced in the surrounding coil?

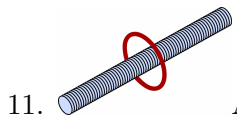- A. 2.328E-02 V
- B. 2.560E-02 V**
- C. 2.817E-02 V
- D. 3.098E-02 V
- E. 3.408E-02 V




11. A long solenoid has a length 0.89 meters, radius 3.01 cm, and 505 turns. It surrounds coil of radius 8.65 meters and 18 turns. If the current in the solenoid is changing at a rate of 279 A/s, what is the emf induced in the surrounding coil?

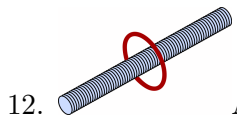- A. 2.646E-02 V
- B. 2.911E-02 V
- C. 3.202E-02 V**
- D. 3.522E-02 V
- E. 3.874E-02 V



12. A long solenoid has a length 0.784 meters, radius 3.57 cm, and 553 turns. It surrounds coil of radius 9.49 meters and 16 turns. If the current in the solenoid is changing at a rate of 276 A/s, what is the emf induced in the surrounding coil?

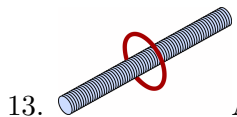- A. 4.476E-02 V
- B. 4.924E-02 V**
- C. 5.416E-02 V
- D. 5.958E-02 V
- E. 6.553E-02 V




13. A long solenoid has a length 0.923 meters, radius 4.08 cm, and 579 turns. It surrounds coil of radius 6.86 meters and 14 turns. If the current in the solenoid is changing at a rate of 139 A/s, what is the emf induced in the surrounding coil?

- A. 1.894E-02 V
- B. 2.083E-02 V
- C. 2.291E-02 V

**D. 2.520E-02 V**

E. 2.772E-02 V

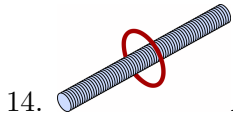

14. A long solenoid has a length 0.634 meters, radius 3.04 cm, and 522 turns. It surrounds coil of radius 9.17 meters and 9 turns. If the current in the solenoid is changing at a rate of 283 A/s, what is the emf induced in the surrounding coil?


A. 1.986E-02 V

B. 2.185E-02 V

**C. 2.404E-02 V**

D. 2.644E-02 V

E. 2.908E-02 V

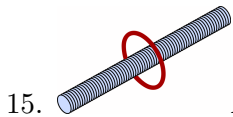

15. A long solenoid has a length 0.559 meters, radius 4.6 cm, and 515 turns. It surrounds coil of radius 9.72 meters and 17 turns. If the current in the solenoid is changing at a rate of 189 A/s, what is the emf induced in the surrounding coil?


A. 7.062E-02 V

**B. 7.768E-02 V**

C. 8.545E-02 V

D. 9.400E-02 V

E. 1.034E-01 V

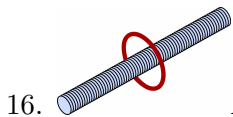

16. A long solenoid has a length 0.759 meters, radius 4.51 cm, and 542 turns. It surrounds coil of radius 9.59 meters and 13 turns. If the current in the solenoid is changing at a rate of 272 A/s, what is the emf induced in the surrounding coil?


A. 5.791E-02 V

**B. 6.370E-02 V**

C. 7.007E-02 V

D. 7.708E-02 V

E. 8.478E-02 V

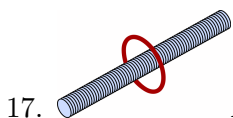

17. A long solenoid has a length 0.703 meters, radius 4.03 cm, and 542 turns. It surrounds coil of radius 6.58 meters and 9 turns. If the current in the solenoid is changing at a rate of 208 A/s, what is the emf induced in the surrounding coil?


A. 2.643E-02 V

**B. 2.907E-02 V**

C. 3.198E-02 V


D. 3.518E-02 V

E. 3.869E-02 V

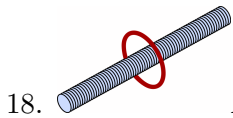

18. A long solenoid has a length 0.805 meters, radius 4.24 cm, and 536 turns. It surrounds coil of radius 8.5 meters and 16 turns. If the current in the solenoid is changing at a rate of 278 A/s, what is the emf induced in the surrounding coil?

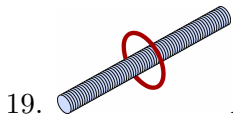- A. **6.604E-02 V**
- B. 7.264E-02 V
- C. 7.990E-02 V
- D. 8.789E-02 V
- E. 9.668E-02 V



19. A long solenoid has a length 0.667 meters, radius 4.41 cm, and 517 turns. It surrounds coil of radius 9.18 meters and 9 turns. If the current in the solenoid is changing at a rate of 296 A/s, what is the emf induced in the surrounding coil?

- A. 4.116E-02 V
- B. 4.528E-02 V
- C. **4.981E-02 V**
- D. 5.479E-02 V
- E. 6.027E-02 V

## 2.2

1. An induced emf of 4.82V is measured across a coil of 73 closely wound turns while the current through it increases uniformly from 0.0 to 4.61A in 0.934s. What is the self-inductance of the coil?
  - A. 7.337E-01 H
  - B. 8.071E-01 H
  - C. 8.878E-01 H
  - D. **9.765E-01 H**
  - E. 1.074E+00 H
2. An induced emf of 5.33V is measured across a coil of 77 closely wound turns while the current through it increases uniformly from 0.0 to 6.57A in 0.648s. What is the self-inductance of the coil?
  - A. 4.779E-01 H
  - B. **5.257E-01 H**
  - C. 5.783E-01 H
  - D. 6.361E-01 H
  - E. 6.997E-01 H
3. An induced emf of 1.7V is measured across a coil of 81 closely wound turns while the current through it increases uniformly from 0.0 to 7.07A in 0.174s. What is the self-inductance of the coil?
  - A. 3.458E-02 H
  - B. 3.804E-02 H
  - C. **4.184E-02 H**
  - D. 4.602E-02 H



- E.  $5.062\text{E-}02\text{ H}$
4. An induced emf of  $5.08\text{V}$  is measured across a coil of 78 closely wound turns while the current through it increases uniformly from  $0.0$  to  $5.07\text{A}$  in  $0.681\text{s}$ . What is the self-inductance of the coil?
- A.  $4.660\text{E-}01\text{ H}$   
B.  $5.127\text{E-}01\text{ H}$   
C.  $5.639\text{E-}01\text{ H}$   
D.  $6.203\text{E-}01\text{ H}$   
**E.  $6.823\text{E-}01\text{ H}$**
5. An induced emf of  $8.76\text{V}$  is measured across a coil of 62 closely wound turns while the current through it increases uniformly from  $0.0$  to  $5.59\text{A}$  in  $0.611\text{s}$ . What is the self-inductance of the coil?
- A.  $7.913\text{E-}01\text{ H}$   
B.  $8.704\text{E-}01\text{ H}$   
**C.  $9.575\text{E-}01\text{ H}$**   
D.  $1.053\text{E+}00\text{ H}$   
E.  $1.159\text{E+}00\text{ H}$
6. An induced emf of  $4.02\text{V}$  is measured across a coil of 85 closely wound turns while the current through it increases uniformly from  $0.0$  to  $3.53\text{A}$  in  $0.438\text{s}$ . What is the self-inductance of the coil?
- A.  $4.535\text{E-}01\text{ H}$   
**B.  $4.988\text{E-}01\text{ H}$**   
C.  $5.487\text{E-}01\text{ H}$   
D.  $6.035\text{E-}01\text{ H}$   
E.  $6.639\text{E-}01\text{ H}$
7. An induced emf of  $6.75\text{V}$  is measured across a coil of 79 closely wound turns while the current through it increases uniformly from  $0.0$  to  $7.76\text{A}$  in  $0.115\text{s}$ . What is the self-inductance of the coil?
- A.  $9.094\text{E-}02\text{ H}$   
**B.  $1.000\text{E-}01\text{ H}$**   
C.  $1.100\text{E-}01\text{ H}$   
D.  $1.210\text{E-}01\text{ H}$   
E.  $1.331\text{E-}01\text{ H}$
8. An induced emf of  $1.92\text{V}$  is measured across a coil of 74 closely wound turns while the current through it increases uniformly from  $0.0$  to  $6.38\text{A}$  in  $0.69\text{s}$ . What is the self-inductance of the coil?
- A.  $1.560\text{E-}01\text{ H}$   
B.  $1.716\text{E-}01\text{ H}$   
C.  $1.888\text{E-}01\text{ H}$   
**D.  $2.076\text{E-}01\text{ H}$**   
E.  $2.284\text{E-}01\text{ H}$
9. An induced emf of  $5.4\text{V}$  is measured across a coil of 95 closely wound turns while the current through it increases uniformly from  $0.0$  to  $7.03\text{A}$  in  $0.713\text{s}$ . What is the self-inductance of the coil?
- A.  $5.477\text{E-}01\text{ H}$**   
B.  $6.024\text{E-}01\text{ H}$

- C. 6.627E-01 H  
D. 7.290E-01 H  
E. 8.019E-01 H
10. An induced emf of 6.78V is measured across a coil of 58 closely wound turns while the current through it increases uniformly from 0.0 to 3.98A in 0.726s. What is the self-inductance of the coil?  
A. 1.022E+00 H  
B. 1.124E+00 H  
**C. 1.237E+00 H**  
D. 1.360E+00 H  
E. 1.496E+00 H
11. An induced emf of 4.7V is measured across a coil of 52 closely wound turns while the current through it increases uniformly from 0.0 to 3.08A in 0.961s. What is the self-inductance of the coil?  
A. 1.102E+00 H  
B. 1.212E+00 H  
C. 1.333E+00 H  
**D. 1.466E+00 H**  
E. 1.613E+00 H
12. An induced emf of 7.87V is measured across a coil of 66 closely wound turns while the current through it increases uniformly from 0.0 to 7.05A in 0.781s. What is the self-inductance of the coil?  
A. 7.926E-01 H  
**B. 8.718E-01 H**  
C. 9.590E-01 H  
D. 1.055E+00 H  
E. 1.160E+00 H
13. An induced emf of 6.29V is measured across a coil of 85 closely wound turns while the current through it increases uniformly from 0.0 to 2.15A in 0.913s. What is the self-inductance of the coil?  
A. 2.428E+00 H  
**B. 2.671E+00 H**  
C. 2.938E+00 H  
D. 3.232E+00 H  
E. 3.555E+00 H
14. An induced emf of 4.13V is measured across a coil of 70 closely wound turns while the current through it increases uniformly from 0.0 to 2.63A in 0.133s. What is the self-inductance of the coil?  
A. 1.726E-01 H  
B. 1.899E-01 H  
**C. 2.089E-01 H**  
D. 2.297E-01 H  
E. 2.527E-01 H
15. An induced emf of 7.48V is measured across a coil of 95 closely wound turns while the current through it increases uniformly from 0.0 to 5.33A in 0.304s. What is the self-inductance of the coil?

- A. 2.914E-01 H
- B. 3.205E-01 H
- C. 3.526E-01 H
- D. 3.878E-01 H
- E. 4.266E-01 H**

16. An induced emf of 3.78V is measured across a coil of 99 closely wound turns while the current through it increases uniformly from 0.0 to 6.36A in 0.821s. What is the self-inductance of the coil?

- A. 4.033E-01 H
- B. 4.436E-01 H
- C. 4.880E-01 H**
- D. 5.367E-01 H
- E. 5.904E-01 H

17. An induced emf of 2.9V is measured across a coil of 51 closely wound turns while the current through it increases uniformly from 0.0 to 6.89A in 0.806s. What is the self-inductance of the coil?

- A. 2.549E-01 H
- B. 2.804E-01 H
- C. 3.084E-01 H
- D. 3.392E-01 H**
- E. 3.732E-01 H

18. An induced emf of 7.94V is measured across a coil of 94 closely wound turns while the current through it increases uniformly from 0.0 to 5.65A in 0.478s. What is the self-inductance of the coil?

- A. 5.047E-01 H
- B. 5.552E-01 H
- C. 6.107E-01 H
- D. 6.717E-01 H**
- E. 7.389E-01 H

19. An induced emf of 1.86V is measured across a coil of 59 closely wound turns while the current through it increases uniformly from 0.0 to 2.58A in 0.89s. What is the self-inductance of the coil?

- A. 4.821E-01 H
- B. 5.303E-01 H
- C. 5.833E-01 H
- D. 6.416E-01 H**
- E. 7.058E-01 H

### 2.3

1. A washer has an inner diameter of 2.57 cm and an outer diameter of 4.14 cm. The thickness is  $h = Cr^{-n}$  where  $r$  is measured in cm,  $C = 4.33\text{mm}$ , and  $n = 2.42$ . What is the volume of the washer?

- A. 7.226E-01 cm<sup>3</sup>
- B. 7.949E-01 cm<sup>3</sup>
- C. 8.744E-01 cm<sup>3</sup>
- D. 9.618E-01 cm<sup>3</sup>

**E. 1.058E+00 cm<sup>3</sup>**

2. A washer has an inner diameter of 2.37 cm and an outer diameter of 4.84 cm. The thickness is  $h = Cr^{-n}$  where  $r$  is measured in cm,  $C = 4.67mm$ , and  $n = 2.56$ . What is the volume of the washer?

**A. 1.570E+00 cm<sup>3</sup>**

B. 1.727E+00 cm<sup>3</sup>

C. 1.900E+00 cm<sup>3</sup>

D. 2.090E+00 cm<sup>3</sup>

E. 2.299E+00 cm<sup>3</sup>

3. A washer has an inner diameter of 2.3 cm and an outer diameter of 4.44 cm. The thickness is  $h = Cr^{-n}$  where  $r$  is measured in cm,  $C = 4.31mm$ , and  $n = 2.66$ . What is the volume of the washer?

A. 1.089E+00 cm<sup>3</sup>

B. 1.198E+00 cm<sup>3</sup>

**C. 1.318E+00 cm<sup>3</sup>**

D. 1.449E+00 cm<sup>3</sup>

E. 1.594E+00 cm<sup>3</sup>

4. A washer has an inner diameter of 2.62 cm and an outer diameter of 4.79 cm. The thickness is  $h = Cr^{-n}$  where  $r$  is measured in cm,  $C = 4.08mm$ , and  $n = 2.68$ . What is the volume of the washer?

**A. 1.056E+00 cm<sup>3</sup>**

B. 1.161E+00 cm<sup>3</sup>

C. 1.278E+00 cm<sup>3</sup>

D. 1.405E+00 cm<sup>3</sup>

E. 1.546E+00 cm<sup>3</sup>

5. A washer has an inner diameter of 2.38 cm and an outer diameter of 4.83 cm. The thickness is  $h = Cr^{-n}$  where  $r$  is measured in cm,  $C = 3.92mm$ , and  $n = 2.68$ . What is the volume of the washer?

A. 1.118E+00 cm<sup>3</sup>

**B. 1.229E+00 cm<sup>3</sup>**

C. 1.352E+00 cm<sup>3</sup>

D. 1.487E+00 cm<sup>3</sup>

E. 1.636E+00 cm<sup>3</sup>

6. A washer has an inner diameter of 2.36 cm and an outer diameter of 4.5 cm. The thickness is  $h = Cr^{-n}$  where  $r$  is measured in cm,  $C = 3.28mm$ , and  $n = 2.4$ . What is the volume of the washer?

**A. 1.097E+00 cm<sup>3</sup>**

B. 1.207E+00 cm<sup>3</sup>

C. 1.328E+00 cm<sup>3</sup>

D. 1.460E+00 cm<sup>3</sup>

E. 1.606E+00 cm<sup>3</sup>

7. A washer has an inner diameter of 2.2 cm and an outer diameter of 4.11 cm. The thickness is  $h = Cr^{-n}$  where  $r$  is measured in cm,  $C = 3.23mm$ , and  $n = 2.74$ . What is the volume of the washer?

A. 7.110E-01 cm<sup>3</sup>

B. 7.821E-01 cm<sup>3</sup>

- C. 8.603E-01 cm<sup>3</sup>
- D. 9.463E-01 cm<sup>3</sup>**
- E. 1.041E+00 cm<sup>3</sup>

8. A washer has an inner diameter of 2.23 cm and an outer diameter of 4.85 cm. The thickness is  $h = Cr^{-n}$  where  $r$  is measured in cm,  $C = 3.7mm$ , and  $n = 2.76$ . What is the volume of the washer?

- A. 1.038E+00 cm<sup>3</sup>
- B. 1.142E+00 cm<sup>3</sup>
- C. 1.256E+00 cm<sup>3</sup>**
- D. 1.381E+00 cm<sup>3</sup>
- E. 1.520E+00 cm<sup>3</sup>

9. A washer has an inner diameter of 2.6 cm and an outer diameter of 4.17 cm. The thickness is  $h = Cr^{-n}$  where  $r$  is measured in cm,  $C = 4.38mm$ , and  $n = 2.62$ . What is the volume of the washer?

- A. 7.196E-01 cm<sup>3</sup>
- B. 7.916E-01 cm<sup>3</sup>
- C. 8.707E-01 cm<sup>3</sup>
- D. 9.578E-01 cm<sup>3</sup>**
- E. 1.054E+00 cm<sup>3</sup>

10. A washer has an inner diameter of 2.16 cm and an outer diameter of 4.82 cm. The thickness is  $h = Cr^{-n}$  where  $r$  is measured in cm,  $C = 4.22mm$ , and  $n = 2.8$ . What is the volume of the washer?

- A. 1.342E+00 cm<sup>3</sup>
- B. 1.477E+00 cm<sup>3</sup>**
- C. 1.624E+00 cm<sup>3</sup>
- D. 1.787E+00 cm<sup>3</sup>
- E. 1.965E+00 cm<sup>3</sup>

11. A washer has an inner diameter of 2.12 cm and an outer diameter of 4.47 cm. The thickness is  $h = Cr^{-n}$  where  $r$  is measured in cm,  $C = 4.7mm$ , and  $n = 2.72$ . What is the volume of the washer?

- A. 1.228E+00 cm<sup>3</sup>
- B. 1.351E+00 cm<sup>3</sup>
- C. 1.486E+00 cm<sup>3</sup>
- D. 1.634E+00 cm<sup>3</sup>**
- E. 1.798E+00 cm<sup>3</sup>

12. A washer has an inner diameter of 2.21 cm and an outer diameter of 4.5 cm. The thickness is  $h = Cr^{-n}$  where  $r$  is measured in cm,  $C = 4.29mm$ , and  $n = 2.62$ . What is the volume of the washer?

- A. 1.325E+00 cm<sup>3</sup>
- B. 1.457E+00 cm<sup>3</sup>**
- C. 1.603E+00 cm<sup>3</sup>
- D. 1.763E+00 cm<sup>3</sup>
- E. 1.939E+00 cm<sup>3</sup>

13. A washer has an inner diameter of 2.23 cm and an outer diameter of 4.18 cm. The thickness is  $h = Cr^{-n}$  where  $r$  is measured in cm,  $C = 4.42mm$ , and  $n = 2.62$ . What is the volume of the washer?

- A. 1.351E+00 cm<sup>3</sup>**
- B. 1.486E+00 cm<sup>3</sup>
- C. 1.635E+00 cm<sup>3</sup>
- D. 1.798E+00 cm<sup>3</sup>
- E. 1.978E+00 cm<sup>3</sup>

14. A washer has an inner diameter of 2.75 cm and an outer diameter of 4.87 cm. The thickness is  $h = Cr^{-n}$  where  $r$  is measured in cm,  $C = 4.39mm$ , and  $n = 2.55$ . What is the volume of the washer?

- A. 7.754E-01 cm<sup>3</sup>
- B. 8.530E-01 cm<sup>3</sup>
- C. 9.383E-01 cm<sup>3</sup>
- D. 1.032E+00 cm<sup>3</sup>
- E. 1.135E+00 cm<sup>3</sup>**

15. A washer has an inner diameter of 2.46 cm and an outer diameter of 4.24 cm. The thickness is  $h = Cr^{-n}$  where  $r$  is measured in cm,  $C = 4.32mm$ , and  $n = 2.63$ . What is the volume of the washer?

- A. 7.499E-01 cm<sup>3</sup>
- B. 8.249E-01 cm<sup>3</sup>
- C. 9.074E-01 cm<sup>3</sup>
- D. 9.982E-01 cm<sup>3</sup>
- E. 1.098E+00 cm<sup>3</sup>**

16. A washer has an inner diameter of 2.74 cm and an outer diameter of 4.71 cm. The thickness is  $h = Cr^{-n}$  where  $r$  is measured in cm,  $C = 3.9mm$ , and  $n = 2.85$ . What is the volume of the washer?

- A. 8.141E-01 cm<sup>3</sup>**
- B. 8.955E-01 cm<sup>3</sup>
- C. 9.850E-01 cm<sup>3</sup>
- D. 1.084E+00 cm<sup>3</sup>
- E. 1.192E+00 cm<sup>3</sup>

17. A washer has an inner diameter of 2.42 cm and an outer diameter of 4.53 cm. The thickness is  $h = Cr^{-n}$  where  $r$  is measured in cm,  $C = 4.47mm$ , and  $n = 2.8$ . What is the volume of the washer?

- A. 8.932E-01 cm<sup>3</sup>
- B. 9.825E-01 cm<sup>3</sup>
- C. 1.081E+00 cm<sup>3</sup>
- D. 1.189E+00 cm<sup>3</sup>**
- E. 1.308E+00 cm<sup>3</sup>


18. A washer has an inner diameter of 2.31 cm and an outer diameter of 4.19 cm. The thickness is  $h = Cr^{-n}$  where  $r$  is measured in cm,  $C = 4.14mm$ , and  $n = 2.86$ . What is the volume of the washer?

- A. 1.071E+00 cm<sup>3</sup>**
- B. 1.178E+00 cm<sup>3</sup>
- C. 1.296E+00 cm<sup>3</sup>
- D. 1.425E+00 cm<sup>3</sup>
- E. 1.568E+00 cm<sup>3</sup>

19. A washer has an inner diameter of 2.75 cm and an outer diameter of 4.62 cm. The thickness is  $h = Cr^{-n}$  where  $r$  is measured in cm,  $C = 3.66\text{mm}$ , and  $n = 2.61$ . What is the volume of the washer?


- A. 6.960E-01 cm<sup>3</sup>
- B. 7.656E-01 cm<sup>3</sup>
- C. 8.421E-01 cm<sup>3</sup>**
- D. 9.264E-01 cm<sup>3</sup>
- E. 1.019E+00 cm<sup>3</sup>

2.4

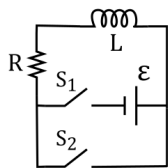


1. Suppose switch  $S_1$  is suddenly closed at time  $t=0$  in the figure shown. What is the current at  $t = 1.98\text{ s}$  if  $\epsilon = 5.75\text{ V}$ ,  $R = 8.07\ \Omega$ , and  $L = 2.84\text{ H}$ ?

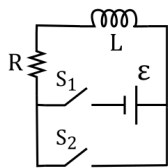- A. 4.109E-01 V
- B. 4.930E-01 V
- C. 5.917E-01 V
- D. 7.100E-01 V**
- E. 8.520E-01 V




2. Suppose switch  $S_1$  is suddenly closed at time  $t=0$  in the figure shown. What is the current at  $t = 5.67\text{ s}$  if  $\epsilon = 5.58\text{ V}$ ,  $R = 3.81\ \Omega$ , and  $L = 3.85\text{ H}$ ?

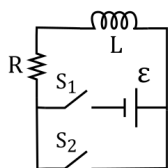- A. 7.037E-01 V
- B. 8.444E-01 V
- C. 1.013E+00 V
- D. 1.216E+00 V
- E. 1.459E+00 V**




3. Suppose switch  $S_1$  is suddenly closed at time  $t=0$  in the figure shown. What is the current at  $t = 0.919\text{ s}$  if  $\epsilon = 6.65\text{ V}$ ,  $R = 6.34\ \Omega$ , and  $L = 1.14\text{ H}$ ?

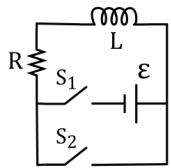- A. 6.033E-01 V
- B. 7.240E-01 V
- C. 8.688E-01 V
- D. 1.043E+00 V**
- E. 1.251E+00 V




4. Suppose switch  $S_1$  is suddenly closed at time  $t=0$  in the figure shown. What is the current at  $t=13.6$  s if  $\epsilon=6.56$  V,  $R=2.44\ \Omega$ , and  $L=8.76$  H?

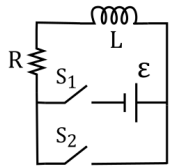- A. **2.627E+00 V**
- B. 3.153E+00 V
- C. 3.783E+00 V
- D. 4.540E+00 V
- E. 5.448E+00 V




5. Suppose switch  $S_1$  is suddenly closed at time  $t=0$  in the figure shown. What is the current at  $t=6.01$  s if  $\epsilon=5.75$  V,  $R=5.73\ \Omega$ , and  $L=7.46$  H?

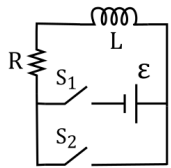- A. **9.936E-01 V**
- B. 1.192E+00 V
- C. 1.431E+00 V
- D. 1.717E+00 V
- E. 2.060E+00 V



6. Suppose switch  $S_1$  is suddenly closed at time  $t=0$  in the figure shown. What is the current at  $t=1.95$  s if  $\epsilon=8.33$  V,  $R=6.96\ \Omega$ , and  $L=2.66$  H?

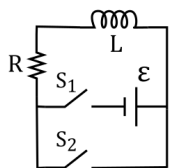
- A. 5.736E-01 V
- B. 6.884E-01 V
- C. 8.260E-01 V
- D. 9.912E-01 V
- E. **1.189E+00 V**



7. Suppose switch  $S_1$  is suddenly closed at time  $t=0$  in the figure shown. What is the current at  $t=2.47$  s if  $\epsilon=7.04$  V,  $R=7.69\ \Omega$ , and  $L=5.78$  H?

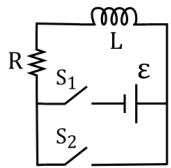
- A. 4.249E-01 V
- B. 5.099E-01 V
- C. 6.118E-01 V
- D. 7.342E-01 V
- E. **8.810E-01 V**






8. Suppose switch  $S_1$  is suddenly closed at time  $t=0$  in the figure shown. What is the current at  $t=5.9\text{ s}$  if  $\epsilon=7.85\text{ V}$ ,  $R=6.89\ \Omega$ , and  $L=7.36\text{ H}$ ?

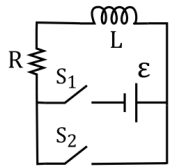- A. 6.567E-01 V
- B. 7.880E-01 V
- C. 9.456E-01 V
- D. 1.135E+00 V**
- E. 1.362E+00 V




9. Suppose switch  $S_1$  is suddenly closed at time  $t=0$  in the figure shown. What is the current at  $t=1.0\text{ s}$  if  $\epsilon=4.14\text{ V}$ ,  $R=7.92\ \Omega$ , and  $L=2.26\text{ H}$ ?

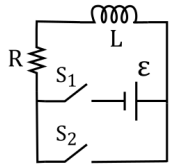- A. 3.523E-01 V
- B. 4.227E-01 V
- C. 5.073E-01 V**
- D. 6.087E-01 V
- E. 7.304E-01 V




10. Suppose switch  $S_1$  is suddenly closed at time  $t=0$  in the figure shown. What is the current at  $t=3.56\text{ s}$  if  $\epsilon=6.14\text{ V}$ ,  $R=7.96\ \Omega$ , and  $L=6.65\text{ H}$ ?

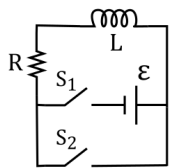- A. 5.281E-01 V
- B. 6.337E-01 V
- C. 7.605E-01 V**
- D. 9.126E-01 V
- E. 1.095E+00 V




11. Suppose switch  $S_1$  is suddenly closed at time  $t=0$  in the figure shown. What is the current at  $t=3.8\text{ s}$  if  $\epsilon=3.36\text{ V}$ ,  $R=5.2\ \Omega$ , and  $L=3.37\text{ H}$ ?

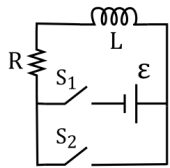- A. 5.369E-01 V
- B. 6.443E-01 V**
- C. 7.732E-01 V
- D. 9.278E-01 V
- E. 1.113E+00 V




12. Suppose switch  $S_1$  is suddenly closed at time  $t=0$  in the figure shown. What is the current at  $t=6.88$  s if  $\epsilon=2.58$  V ,  $R=5.69\ \Omega$  , and  $L=6.94$  H?

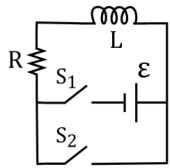- A. **4.518E-01 V**
- B. 5.422E-01 V
- C. 6.506E-01 V
- D. 7.807E-01 V
- E. 9.369E-01 V




13. Suppose switch  $S_1$  is suddenly closed at time  $t=0$  in the figure shown. What is the current at  $t=7.72$  s if  $\epsilon=2.79$  V ,  $R=1.56\ \Omega$  , and  $L=3.16$  H?

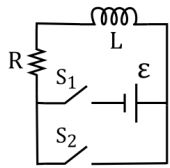- A. 1.214E+00 V
- B. 1.457E+00 V
- C. **1.749E+00 V**
- D. 2.099E+00 V
- E. 2.518E+00 V




14. Suppose switch  $S_1$  is suddenly closed at time  $t=0$  in the figure shown. What is the current at  $t=3.96$  s if  $\epsilon=4.92$  V ,  $R=5.02\ \Omega$  , and  $L=5.0$  H?

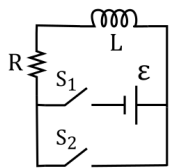- A. **9.618E-01 V**
- B. 1.154E+00 V
- C. 1.385E+00 V
- D. 1.662E+00 V
- E. 1.994E+00 V




15. Suppose switch  $S_1$  is suddenly closed at time  $t=0$  in the figure shown. What is the current at  $t=20.1$  s if  $\epsilon=5.77$  V ,  $R=1.38\ \Omega$  , and  $L=5.45$  H?

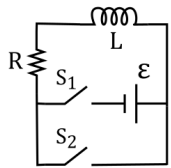- A. 3.463E+00 V
- B. **4.156E+00 V**
- C. 4.987E+00 V
- D. 5.984E+00 V
- E. 7.181E+00 V




16. Suppose switch  $S_1$  is suddenly closed at time  $t=0$  in the figure shown. What is the current at  $t = 2.53$  s if  $\epsilon = 6.14$  V ,  $R = 4.22 \Omega$  , and  $L = 1.91$  H?

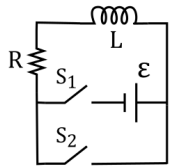- A. 1.007E+00 V
- B. 1.208E+00 V
- C. 1.450E+00 V**
- D. 1.739E+00 V
- E. 2.087E+00 V




17. Suppose switch  $S_1$  is suddenly closed at time  $t=0$  in the figure shown. What is the current at  $t = 0.741$  s if  $\epsilon = 7.36$  V ,  $R = 5.33 \Omega$  , and  $L = 1.27$  H?

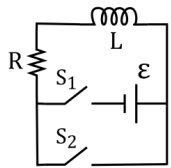- A. 7.635E-01 V
- B. 9.162E-01 V
- C. 1.099E+00 V
- D. 1.319E+00 V**
- E. 1.583E+00 V



18. Suppose switch  $S_1$  is suddenly closed at time  $t=0$  in the figure shown. What is the current at  $t = 6.45$  s if  $\epsilon = 7.01$  V ,  $R = 7.04 \Omega$  , and  $L = 8.75$  H?

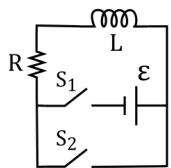
- A. 9.902E-01 V**
- B. 1.188E+00 V
- C. 1.426E+00 V
- D. 1.711E+00 V
- E. 2.053E+00 V



19. Suppose switch  $S_1$  is suddenly closed at time  $t=0$  in the figure shown. What is the current at  $t = 1.55$  s if  $\epsilon = 5.97$  V ,  $R = 7.74 \Omega$  , and  $L = 2.62$  H?


- A. 3.682E-01 V
- B. 4.418E-01 V
- C. 5.301E-01 V
- D. 6.362E-01 V
- E. 7.634E-01 V**

2.5

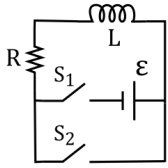


1. Suppose switch  $S_1$  in the figure shown was closed and remained closed long enough to achieve steady state. At  $t=0$   $S_1$  is opened as  $S_2$  is closed. How long will it take for the energy stored in the inductor to be reduced to 1.79

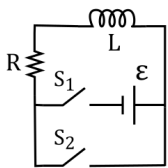- A.  $-1.442\text{E}+00$  s
- B.  $-1.586\text{E}+00$  s
- C.  $-1.744\text{E}+00$  s
- D.  $-1.919\text{E}+00$  s
- E.  $-2.111\text{E}+00$  s




2. Suppose switch  $S_1$  in the figure shown was closed and remained closed long enough to achieve steady state. At  $t=0$   $S_1$  is opened as  $S_2$  is closed. How long will it take for the energy stored in the inductor to be reduced to 1.43

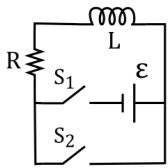- A.  $-4.120\text{E}-01$  s
- B.  $-4.532\text{E}-01$  s
- C.  $-4.985\text{E}-01$  s
- D.  $-5.483\text{E}-01$  s
- E.  $-6.031\text{E}-01$  s



3. Suppose switch  $S_1$  in the figure shown was closed and remained closed long enough to achieve steady state. At  $t=0$   $S_1$  is opened as  $S_2$  is closed. How long will it take for the energy stored in the inductor to be reduced to 1.67

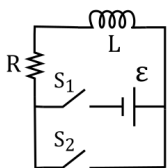- A.  $-1.047\text{E}+00$  s
- B.  $-1.152\text{E}+00$  s**
- C.  $-1.267\text{E}+00$  s
- D.  $-1.393\text{E}+00$  s
- E.  $-1.533\text{E}+00$  s




4. Suppose switch  $S_1$  in the figure shown was closed and remained closed long enough to achieve steady state. At  $t=0$   $S_1$  is opened as  $S_2$  is closed. How long will it take for the energy stored in the inductor to be reduced to 1.44

- A.  $-3.114\text{E}-01$  s
- B.  $-3.425\text{E}-01$  s

C. **-3.767E-01 s**

D. -4.144E-01 s

E. -4.559E-01 s

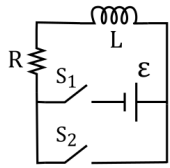

5. Suppose switch  $S_1$  in the figure shown was closed and remained closed long enough to achieve steady state. At  $t=0$   $S_1$  is opened as  $S_2$  is closed. How long will it take for the energy stored in the inductor to be reduced to 2.78


A. -2.296E+00 s

B. **-2.525E+00 s**

C. -2.778E+00 s

D. -3.056E+00 s

E. -3.361E+00 s

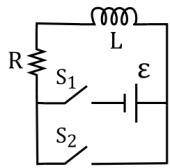

6. Suppose switch  $S_1$  in the figure shown was closed and remained closed long enough to achieve steady state. At  $t=0$   $S_1$  is opened as  $S_2$  is closed. How long will it take for the energy stored in the inductor to be reduced to 2.59


A. **-1.614E+00 s**

B. -1.775E+00 s

C. -1.952E+00 s

D. -2.148E+00 s

E. -2.362E+00 s

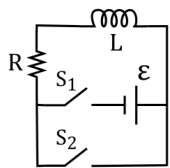

7. Suppose switch  $S_1$  in the figure shown was closed and remained closed long enough to achieve steady state. At  $t=0$   $S_1$  is opened as  $S_2$  is closed. How long will it take for the energy stored in the inductor to be reduced to 2.69


A. -8.773E-01 s

B. -9.651E-01 s

C. -1.062E+00 s


D. **-1.168E+00 s**

E. -1.284E+00 s

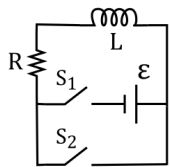


8. Suppose switch  $S_1$  in the figure shown was closed and remained closed long enough to achieve steady state. At  $t=0$   $S_1$  is opened as  $S_2$  is closed. How long will it take for the energy stored in the inductor to be reduced to 2.63

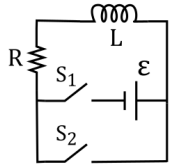- A. **-3.137E-01 s**
- B. -3.451E-01 s
- C. -3.796E-01 s
- D. -4.176E-01 s
- E. -4.593E-01 s




9. Suppose switch  $S_1$  in the figure shown was closed and remained closed long enough to achieve steady state. At  $t=0$   $S_1$  is opened as  $S_2$  is closed. How long will it take for the energy stored in the inductor to be reduced to 1.65

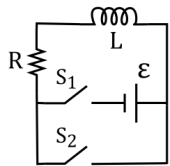- A. -2.476E+00 s
- B. -2.724E+00 s
- C. -2.996E+00 s
- D. -3.296E+00 s
- E. **-3.625E+00 s**




10. Suppose switch  $S_1$  in the figure shown was closed and remained closed long enough to achieve steady state. At  $t=0$   $S_1$  is opened as  $S_2$  is closed. How long will it take for the energy stored in the inductor to be reduced to 2.16

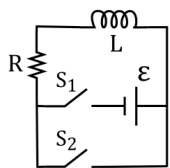- A. -2.110E+00 s
- B. **-2.321E+00 s**
- C. -2.553E+00 s
- D. -2.809E+00 s
- E. -3.090E+00 s




11. Suppose switch  $S_1$  in the figure shown was closed and remained closed long enough to achieve steady state. At  $t=0$   $S_1$  is opened as  $S_2$  is closed. How long will it take for the energy stored in the inductor to be reduced to 1.82

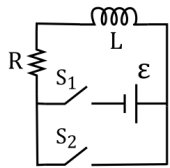- A. -9.593E-01 s
- B. -1.055E+00 s
- C. **-1.161E+00 s**
- D. -1.277E+00 s
- E. -1.405E+00 s




12. Suppose switch  $S_1$  in the figure shown was closed and remained closed long enough to achieve steady state. At  $t=0$   $S_1$  is opened as  $S_2$  is closed. How long will it take for the energy stored in the inductor to be reduced to 1.53

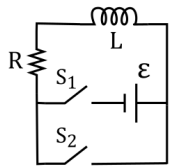- A. **-5.192E+00 s**
- B. -5.711E+00 s
- C. -6.282E+00 s
- D. -6.910E+00 s
- E. -7.601E+00 s




13. Suppose switch  $S_1$  in the figure shown was closed and remained closed long enough to achieve steady state. At  $t=0$   $S_1$  is opened as  $S_2$  is closed. How long will it take for the energy stored in the inductor to be reduced to 2.01

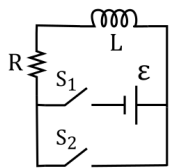- A. -8.659E-01 s
- B. -9.525E-01 s
- C. **-1.048E+00 s**
- D. -1.153E+00 s
- E. -1.268E+00 s



14. Suppose switch  $S_1$  in the figure shown was closed and remained closed long enough to achieve steady state. At  $t=0$   $S_1$  is opened as  $S_2$  is closed. How long will it take for the energy stored in the inductor to be reduced to 2.7

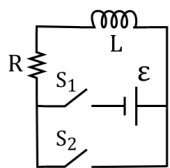
- A. **-5.757E+00 s**
- B. -6.333E+00 s
- C. -6.966E+00 s
- D. -7.663E+00 s
- E. -8.429E+00 s



15. Suppose switch  $S_1$  in the figure shown was closed and remained closed long enough to achieve steady state. At  $t=0$   $S_1$  is opened as  $S_2$  is closed. How long will it take for the energy stored in the inductor to be reduced to 1.56


- A. -4.939E+00 s
- B. -5.433E+00 s
- C. **-5.976E+00 s**

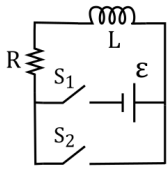- D.  $-6.574\text{E}+00\text{ s}$   
**E.  $-7.231\text{E}+00\text{ s}$**




16. Suppose switch  $S_1$  in the figure shown was closed and remained closed long enough to achieve steady state. At  $t=0$   $S_1$  is opened as  $S_2$  is closed. How long will it take for the energy stored in the inductor to be reduced to 1.96

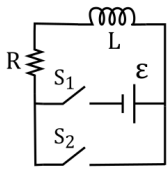- A.  $-1.700\text{E}+00\text{ s}$   
 B.  $-1.870\text{E}+00\text{ s}$   
 C.  $-2.057\text{E}+00\text{ s}$   
**D.  $-2.262\text{E}+00\text{ s}$**   
 E.  $-2.489\text{E}+00\text{ s}$




17. Suppose switch  $S_1$  in the figure shown was closed and remained closed long enough to achieve steady state. At  $t=0$   $S_1$  is opened as  $S_2$  is closed. How long will it take for the energy stored in the inductor to be reduced to 2.28

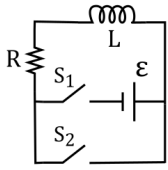- A.  $-6.429\text{E}-01\text{ s}$   
 B.  $-7.072\text{E}-01\text{ s}$   
 C.  $-7.779\text{E}-01\text{ s}$   
 D.  $-8.557\text{E}-01\text{ s}$   
**E.  $-9.412\text{E}-01\text{ s}$**



18. Suppose switch  $S_1$  in the figure shown was closed and remained closed long enough to achieve steady state. At  $t=0$   $S_1$  is opened as  $S_2$  is closed. How long will it take for the energy stored in the inductor to be reduced to 2.54

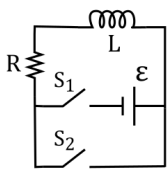- A.  $-2.540\text{E}+00\text{ s}$   
 B.  $-2.794\text{E}+00\text{ s}$   
 C.  $-3.073\text{E}+00\text{ s}$   
 D.  $-3.381\text{E}+00\text{ s}$   
**E.  $-3.719\text{E}+00\text{ s}$**



19. Suppose switch  $S_1$  in the figure shown was closed and remained closed long enough to achieve steady state. At  $t=0$   $S_1$  is opened as  $S_2$  is closed. How long will it take for the energy stored in the inductor to be reduced to 2.23



- A.  $-1.345\text{E}+00$  s
- B.  $-1.480\text{E}+00$  s
- C.  $-1.628\text{E}+00$  s
- D.  $-1.790\text{E}+00$  s**
- E.  $-1.969\text{E}+00$  s

## 2.6

1. In an LC circuit, the self-inductance is  $0.0134$  H and the capacitance is  $3.280\text{E}-06$  F. At  $t=0$  all the energy is stored in the capacitor, which has a charge of  $5.930\text{E}-05$  C. How long does it take for the capacitor to become completely discharged?
  - A.  $2.722\text{E}-04$  s
  - B.  $2.994\text{E}-04$  s
  - C.  $3.293\text{E}-04$  s**
  - D.  $3.622\text{E}-04$  s
  - E.  $3.985\text{E}-04$  s
2. In an LC circuit, the self-inductance is  $0.0424$  H and the capacitance is  $7.790\text{E}-06$  F. At  $t=0$  all the energy is stored in the capacitor, which has a charge of  $6.230\text{E}-05$  C. How long does it take for the capacitor to become completely discharged?
  - A.  $6.166\text{E}-04$  s
  - B.  $6.783\text{E}-04$  s
  - C.  $7.461\text{E}-04$  s
  - D.  $8.207\text{E}-04$  s
  - E.  $9.028\text{E}-04$  s**
3. In an LC circuit, the self-inductance is  $0.0126$  H and the capacitance is  $3.350\text{E}-06$  F. At  $t=0$  all the energy is stored in the capacitor, which has a charge of  $7.420\text{E}-05$  C. How long does it take for the capacitor to become completely discharged?
  - A.  $2.204\text{E}-04$  s
  - B.  $2.425\text{E}-04$  s
  - C.  $2.667\text{E}-04$  s
  - D.  $2.934\text{E}-04$  s
  - E.  $3.227\text{E}-04$  s**
4. In an LC circuit, the self-inductance is  $0.0216$  H and the capacitance is  $6.450\text{E}-06$  F. At  $t=0$  all the energy is stored in the capacitor, which has a charge of  $1.240\text{E}-05$  C. How long does it take for the capacitor to become completely discharged?
  - A.  $4.846\text{E}-04$  s
  - B.  $5.330\text{E}-04$  s
  - C.  $5.863\text{E}-04$  s**
  - D.  $6.449\text{E}-04$  s
  - E.  $7.094\text{E}-04$  s
5. In an LC circuit, the self-inductance is  $0.0735$  H and the capacitance is  $2.300\text{E}-06$  F. At  $t=0$  all the energy is stored in the capacitor, which has a charge of  $3.220\text{E}-05$  C. How long does it take for the capacitor to become completely discharged?

- A. 4.411E-04 s
- B. 4.852E-04 s
- C. 5.338E-04 s
- D. 5.871E-04 s
- E. 6.458E-04 s**

6. In an LC circuit, the self-inductance is 0.025 H and the capacitance is 3.530E-06 F. At  $t=0$  all the energy is stored in the capacitor, which has a charge of 7.770E-05 C. How long does it take for the capacitor to become completely discharged?

- A. 3.856E-04 s
- B. 4.242E-04 s
- C. 4.666E-04 s**
- D. 5.133E-04 s
- E. 5.646E-04 s

7. In an LC circuit, the self-inductance is 0.0689 H and the capacitance is 2.110E-06 F. At  $t=0$  all the energy is stored in the capacitor, which has a charge of 7.220E-05 C. How long does it take for the capacitor to become completely discharged?

- A. 4.950E-04 s
- B. 5.445E-04 s
- C. 5.989E-04 s**
- D. 6.588E-04 s
- E. 7.247E-04 s

8. In an LC circuit, the self-inductance is 0.0464 H and the capacitance is 7.350E-06 F. At  $t=0$  all the energy is stored in the capacitor, which has a charge of 3.280E-05 C. How long does it take for the capacitor to become completely discharged?

- A. 8.339E-04 s
- B. 9.173E-04 s**
- C. 1.009E-03 s
- D. 1.110E-03 s
- E. 1.221E-03 s

9. In an LC circuit, the self-inductance is 0.0237 H and the capacitance is 6.140E-06 F. At  $t=0$  all the energy is stored in the capacitor, which has a charge of 8.260E-05 C. How long does it take for the capacitor to become completely discharged?

- A. 4.093E-04 s
- B. 4.502E-04 s
- C. 4.952E-04 s
- D. 5.447E-04 s
- E. 5.992E-04 s**

10. In an LC circuit, the self-inductance is 0.0815 H and the capacitance is 6.520E-06 F. At  $t=0$  all the energy is stored in the capacitor, which has a charge of 8.410E-05 C. How long does it take for the capacitor to become completely discharged?

- A. 7.821E-04 s

- B. 8.603E-04 s
- C. 9.463E-04 s
- D. 1.041E-03 s
- E. 1.145E-03 s**

11. In an LC circuit, the self-inductance is 0.0795 H and the capacitance is 7.930E-06 F. At  $t=0$  all the energy is stored in the capacitor, which has a charge of 2.420E-05 C. How long does it take for the capacitor to become completely discharged?

- A. 9.370E-04 s
- B. 1.031E-03 s
- C. 1.134E-03 s
- D. 1.247E-03 s**
- E. 1.372E-03 s

12. In an LC circuit, the self-inductance is 0.0116 H and the capacitance is 7.040E-06 F. At  $t=0$  all the energy is stored in the capacitor, which has a charge of 6.140E-05 C. How long does it take for the capacitor to become completely discharged?

- A. 4.489E-04 s**
- B. 4.938E-04 s
- C. 5.432E-04 s
- D. 5.975E-04 s
- E. 6.572E-04 s

13. In an LC circuit, the self-inductance is 0.0307 H and the capacitance is 5.330E-06 F. At  $t=0$  all the energy is stored in the capacitor, which has a charge of 1.840E-05 C. How long does it take for the capacitor to become completely discharged?

- A. 5.251E-04 s
- B. 5.776E-04 s
- C. 6.354E-04 s**
- D. 6.989E-04 s
- E. 7.688E-04 s

14. In an LC circuit, the self-inductance is 0.0273 H and the capacitance is 6.440E-06 F. At  $t=0$  all the energy is stored in the capacitor, which has a charge of 6.620E-05 C. How long does it take for the capacitor to become completely discharged?

- A. 5.443E-04 s
- B. 5.988E-04 s
- C. 6.586E-04 s**
- D. 7.245E-04 s
- E. 7.969E-04 s

15. In an LC circuit, the self-inductance is 0.0156 H and the capacitance is 6.950E-06 F. At  $t=0$  all the energy is stored in the capacitor, which has a charge of 4.830E-05 C. How long does it take for the capacitor to become completely discharged?

- A. 3.886E-04 s
- B. 4.275E-04 s

- C. 4.702E-04 s
- D. 5.172E-04 s**
- E. 5.689E-04 s

16. In an LC circuit, the self-inductance is 0.035 H and the capacitance is 4.620E-06 F. At  $t=0$  all the energy is stored in the capacitor, which has a charge of 8.250E-05 C. How long does it take for the capacitor to become completely discharged?

- A. 6.316E-04 s**
- B. 6.948E-04 s
- C. 7.643E-04 s
- D. 8.407E-04 s
- E. 9.248E-04 s

17. In an LC circuit, the self-inductance is 0.0399 H and the capacitance is 8.450E-06 F. At  $t=0$  all the energy is stored in the capacitor, which has a charge of 6.480E-05 C. How long does it take for the capacitor to become completely discharged?

- A. 6.230E-04 s
- B. 6.853E-04 s
- C. 7.538E-04 s
- D. 8.292E-04 s
- E. 9.121E-04 s**

18. In an LC circuit, the self-inductance is 0.0262 H and the capacitance is 4.540E-06 F. At  $t=0$  all the energy is stored in the capacitor, which has a charge of 4.700E-05 C. How long does it take for the capacitor to become completely discharged?

- A. 4.070E-04 s
- B. 4.477E-04 s
- C. 4.925E-04 s
- D. 5.417E-04 s**
- E. 5.959E-04 s

19. In an LC circuit, the self-inductance is 0.0776 H and the capacitance is 6.940E-06 F. At  $t=0$  all the energy is stored in the capacitor, which has a charge of 3.400E-05 C. How long does it take for the capacitor to become completely discharged?

- A. 1.048E-03 s
- B. 1.153E-03 s**
- C. 1.268E-03 s
- D. 1.395E-03 s
- E. 1.534E-03 s

## 3 Attribution

### Notes

<sup>1</sup>Example 14.1 from OpenStax University Physics 2: [https://cnx.org/contents/eg-XcBxE@9.7:H8S6dNUY@2/141-Mutual-Inductance\\_1](https://cnx.org/contents/eg-XcBxE@9.7:H8S6dNUY@2/141-Mutual-Inductance_1) placed in Public Domain by Guy Vandegrift: <https://en.wikiversity.org/wiki/special:permalink/1892308>

<sup>2</sup>Example 14.2 OpenStax University Physics 2: [https://cnx.org/contents/eg-XcBxE@9.7:9IPDyGBX@2/142-Self-Inductance-and-Induct\\_1](https://cnx.org/contents/eg-XcBxE@9.7:9IPDyGBX@2/142-Self-Inductance-and-Induct_1) placed in Public Domain by Guy Vandegrift: <https://en.wikiversity.org/wiki/special:permalink/1892308>

<sup>3</sup>Example 14.6 from OpenStax University Physics 2: [https://cnx.org/contents/eg-XcBxE@9.7:gPV9xl9u@2/143-Energy-in-a-Magnetic-Field\\_1](https://cnx.org/contents/eg-XcBxE@9.7:gPV9xl9u@2/143-Energy-in-a-Magnetic-Field_1) placed in Public Domain by Guy Vandegrift: <https://en.wikiversity.org/wiki/special:permalink/1892308>

<sup>4</sup>Example 14.4 from OpenStax University Physics 2: [https://cnx.org/contents/eg-XcBxE@9.7:vsb1s41R@3/144-RL-Circuits\\_1](https://cnx.org/contents/eg-XcBxE@9.7:vsb1s41R@3/144-RL-Circuits_1) placed in Public Domain by Guy Vandegrift: <https://en.wikiversity.org/wiki/special:permalink/1892308>

<sup>5</sup>Example 14.6 from OpenStax University Physics 2: [https://cnx.org/contents/eg-XcBxE@9.7:tIIYnK5w@2/145-Oscillations-in-an-LC-Circ\\_1](https://cnx.org/contents/eg-XcBxE@9.7:tIIYnK5w@2/145-Oscillations-in-an-LC-Circ_1) placed in Public Domain by Guy Vandegrift: <https://en.wikiversity.org/wiki/special:permalink/1892308>