

# FSM Example (2A)

---


Copyright (c) 2013 - 2014 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".

Please send corrections (or suggestions) to [youngwlim@hotmail.com](mailto:youngwlim@hotmail.com).

This document was produced by using OpenOffice and Octave.

# FSM Inputs and Outputs

 


Traffic Lights - Outputs

$L_A$   $L_B$

Sensor - Inputs

$T_A$   $T_B$

# States

 

# Moore FSM State Transition Table

$S_1$	$S_0$	$T_A$	$T_B$	$S'_1$	$S'_0$
0	0	0	X	0	1
0	0	1	X	0	0
0	1	X	X	1	0
1	0	X	0	1	1
1	0	X	1	1	0
1	1	X	X	0	0

$S_1$	$S_0$	$T_A$	$T_B$	$S'_1$
0	0	0	X	0
0	0	1	X	0
0	1	X	X	1
1	0	X	0	1
1	0	X	1	1
1	1	X	X	0

$\bar{S}_1 S_0$



0	1	X	X	1
---	---	---	---	---

$S_1 \bar{S}_0 \bar{T}_B$



1	0	X	0	1
---	---	---	---	---


$S_1 \bar{S}_0 T_B$



1	0	X	1	1
---	---	---	---	---

$$S'_1 = \bar{S}_1 S_0 + S_1 \bar{S}_0$$

$$= S_1 \oplus S_0$$

 

$\bar{S}_1 \bar{S}_0 \bar{T}_A$



$S_1$	$S_0$	$T_A$	$T_B$	$S'_0$
0	0	0	X	1
0	0	1	X	0
0	1	X	X	0
1	0	X	0	1
1	0	X	1	0
1	1	X	X	0


$S_1 \bar{S}_0 \bar{T}_B$



$$S'_0 = \bar{S}_1 \bar{S}_0 \bar{T}_A + S_1 \bar{S}_0 \bar{T}_B$$

# States

$S_1$	$S_2$	$L_{A1}$	$L_{A0}$	$L_{B1}$	$L_{B0}$
0	0	0	0	1	0
0	1	0	1	1	0
1	0	1	0	0	0
1	1	1	0	0	1

 

- 00
- 01
- 10

$S_1$	$S_2$	$L_{A1}$
0	0	0
0	1	0
1	0	1
1	1	1

$$L_{A1} = S_1$$

$S_1$	$S_2$	$L_{A0}$
0	0	0
0	1	1
1	0	0
1	1	0

$$L_{A0} = \overline{S_1} S_0$$




$S_1$	$S_2$	$L_{B1}$
0	0	1
0	1	1
1	0	0
1	1	0

$$L_{B1} = \overline{S_1}$$

$S_1$	$S_2$	$L_{B0}$
0	0	0
0	1	0
1	0	0
1	1	1

$$L_{A0} = S_1 S_0$$


# Moore FSM (1)

 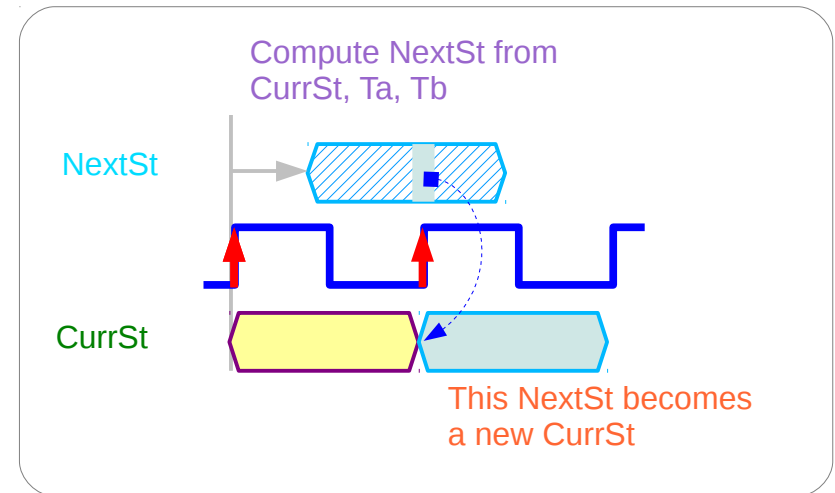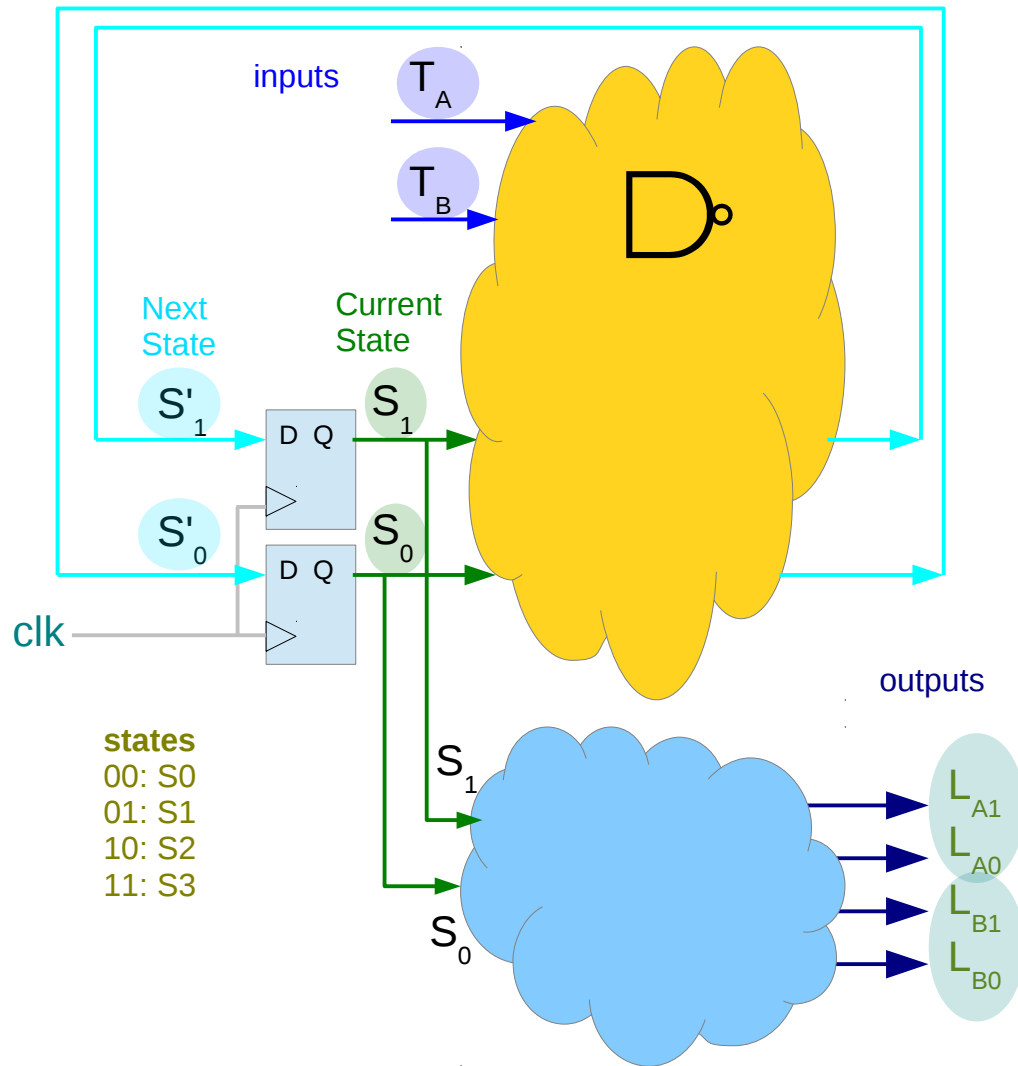

**outputs (LA/LB)**

00: Green  
01: Yellow  
10: Red  
11: X

# Moore FSM

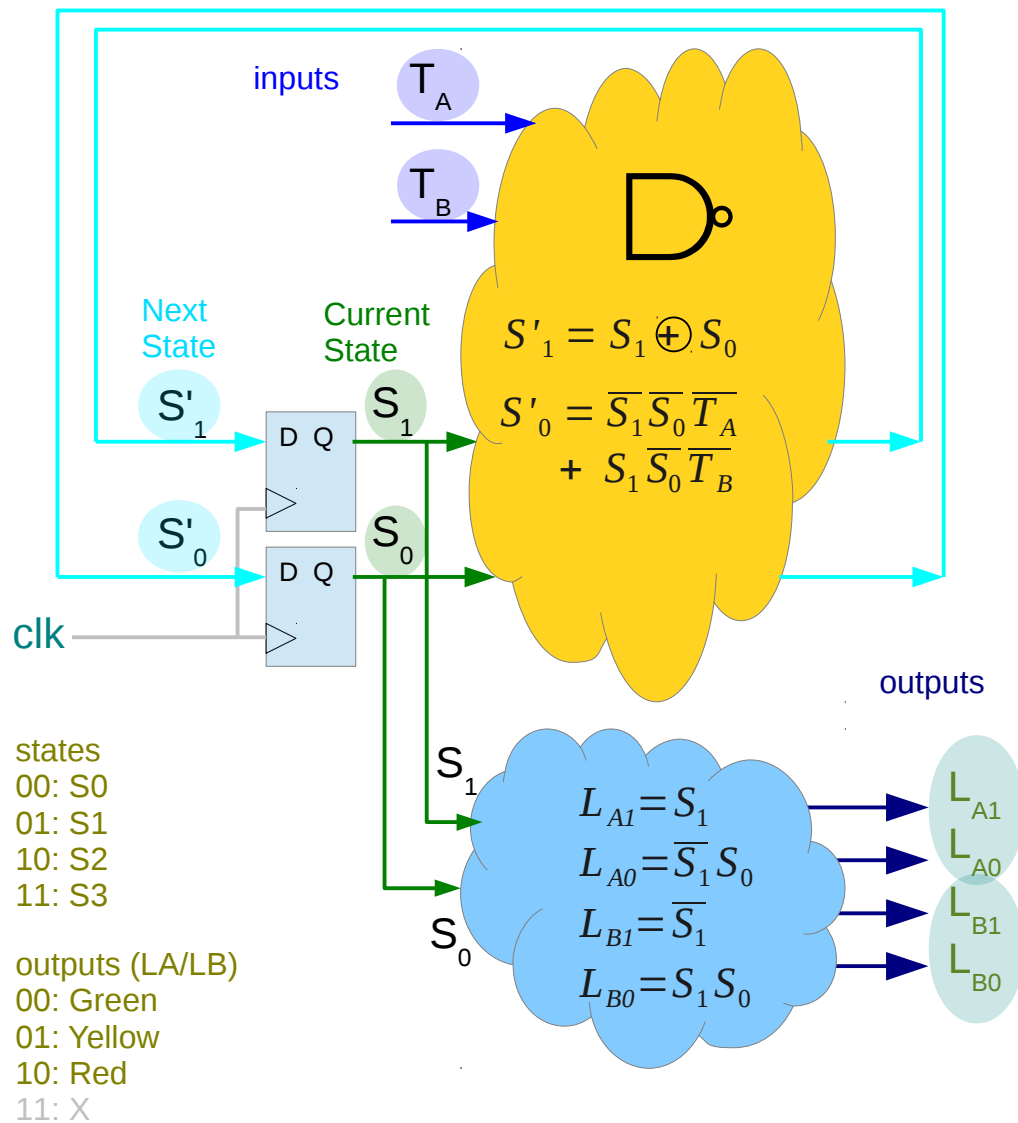

Inputs

$T_A$   $T_B$

Current State

$S_1$   $S_0$

Next States

$$S'_1 = S_1 \oplus S_0$$

$$S'_0 = \overline{S_1} \overline{S_0} T_A + S_1 \overline{S_0} T_B$$

Current State

$S_1$   $S_0$

Outputs

$$L_{A1} = S_1 \quad L_{B1} = \overline{S_1}$$

$$L_{A0} = \overline{S_1} S_0 \quad L_{B0} = S_1 S_0$$



# Verilog Gate Level Design - testbench

```
`timescale 1ns/100ps

module traffic_controller_testbench;

    parameter cycle = 40;

    reg clock;

    always
    begin
        #(cycle/2) clock=~clock;
    end

    traffic_controller DUT (.clock(clock),
                           .reset(reset),
                           .TA(TA),
                           .TB(TB),
                           .LA(LA),
                           .LB(LB) );

    reg    reset;
    reg    TA, TB;
    wire [1:0] LA, LB;

    initial
    begin
        clock = 1;
        reset = 1;
        TA = 1;
        TB = 0;

        #1;
        #(cycle)  reset = 0;
        #(cycle)  TB = 1;
        #(cycle)  TA = 0;
        #(cycle*3) TA = 1;
                 TB = 0;
        #(cycle*3) TA = 0;
    end

    initial
    begin
        $dumpfile("traffic.vcd");
        $dumpvars(0, DUT);
        #(cycle * 10);
        $finish;
    end

endmodule
```

# Verilog Gate Level Design - traffic\_gate.v

```
module traffic_controller(clock, reset, TA, TB, LA, LB);
  input clock, reset;
  input TA, TB;
  output [1:0] LA, LB;

  reg [1:0] S;
  wire [1:0] NextS;

  always @(posedge clock)
  begin: SEQ
    if (reset)
      #8 S = 2'b00;
    else
      #8 S = NextS;
  end


  not #8 (S1b, S[1]);
  not #8 (S0b, S[0]);
  not #8 (TA b, TA);
  not #8 (TB b, TB);

  xor #8 (NextS[1], S[1], S[0]);
  or #8 (NextS[0], NS1, NS2);
  and #8 (NS1, S1b, S0b, TA b);
  and #8 (NS2, S[1], S0b, TB b);


  buf #8 (LA[1], S[1]);
  and #8 (LA[0], S1b, S[0]);
  not #8 (LB[1], S[1]);
  and #8 (LB[0], S[1], S[0]);

endmodule
```


# VCD Output with zero delay

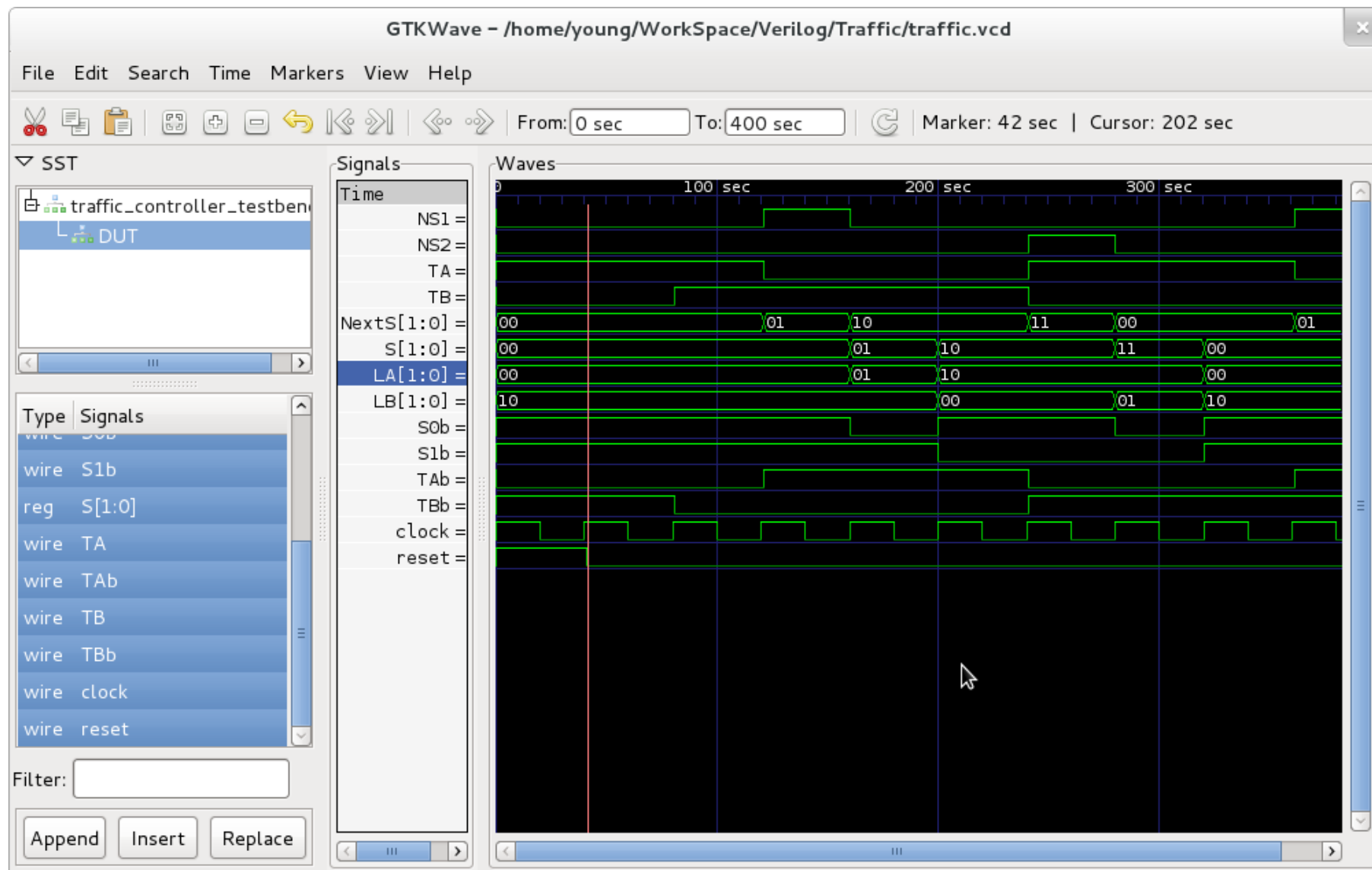


# VCD Output with gate delays

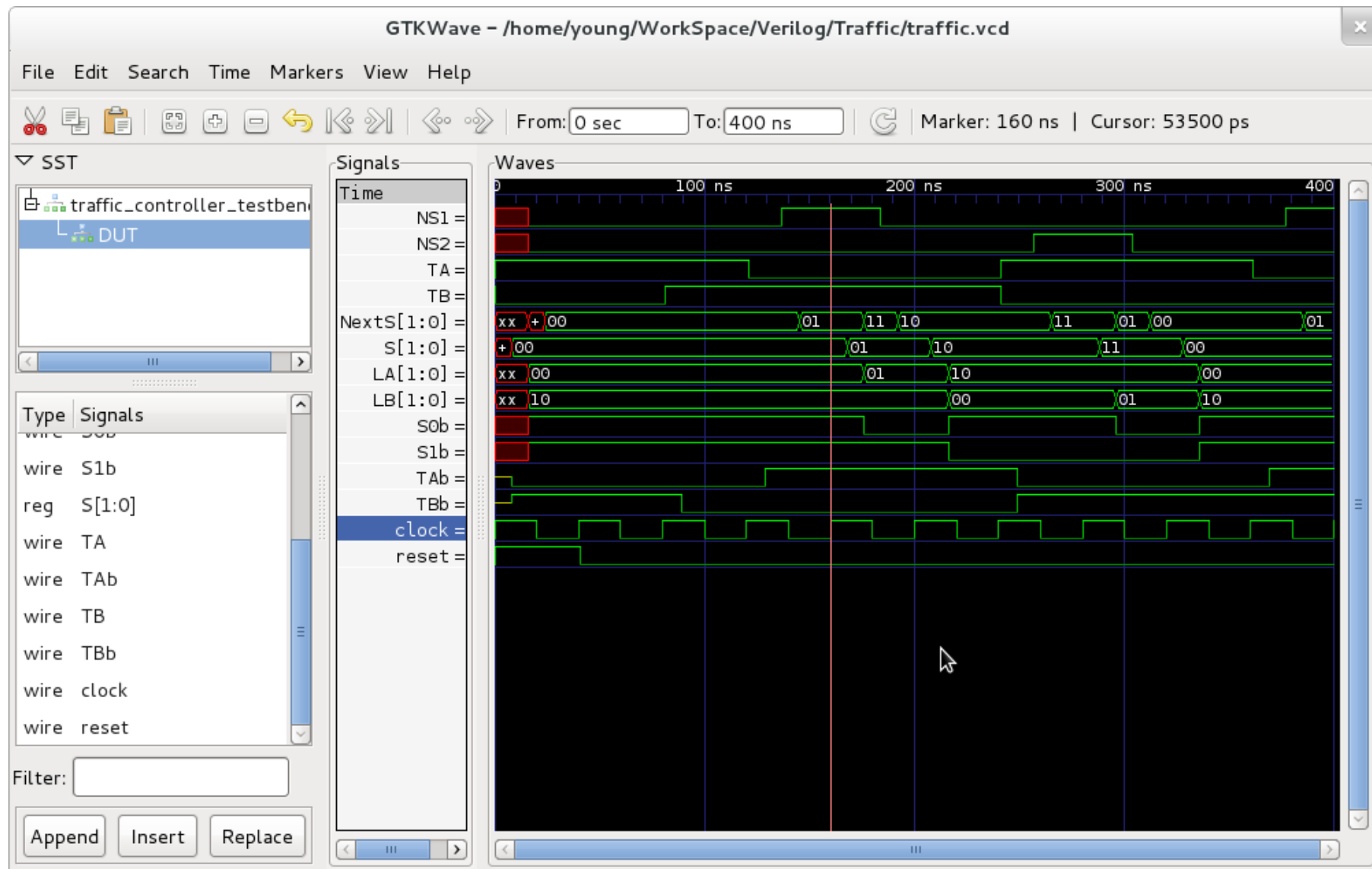


# VCD Output with gate delays

 

## Output Delay

 

# Divide By N Counter FSM

 

Input: none

Output: Y=1 every 3 cycles

State Transition Table

Curr St	Next St
S0	S1
S1	S2
S2	S0

Output Table

Curr St	Output
S0	1
S1	0
S2	0

# Encoding States

State Transition Table

Curr St	Next St
S0	S1
S1	S2
S2	S0

Output Table

Curr St	Output
S0	1
S1	0
S2	0

$S_1$	$S_0$	$S'_1$	$S'_0$
0	0	0	1
0	1	1	0
1	0	0	0

$S_1$	$S_0$	Y
0	0	1
0	1	0
1	0	0

$$S'_1 = \overline{S_1} S_0$$

$$S'_0 = \overline{S_1} \overline{S_0}$$

$$Y = \overline{S_1} \overline{S_0}$$

State Transition Table

Curr St	Next St
S0	S1
S1	S2
S2	S0

Output Table

Curr St	Output
S0	1
S1	0
S2	0

$S_2$	$S_1$	$S_0$	$S'_2$	$S'_1$	$S'_0$
0	0	1	0	1	0
0	1	0	1	0	0
1	0	0	0	0	1

$S_2$	$S_1$	$S_0$	Y
0	0	1	1
0	1	0	0
1	0	0	0

$$S'_2 = \overline{S_2} S_1 \overline{S_0} \Rightarrow S_1$$

$$S'_1 = \overline{S_2} \overline{S_1} S_0 \Rightarrow S_0$$

$$S'_0 = S_2 \overline{S_1} \overline{S_0} \Rightarrow S_2$$

$$Y = \overline{S_2} \overline{S_1} S_0 \Rightarrow S_0$$

## References

- [1] <http://en.wikipedia.org/>
- [2] D.M. Harris, S. L. Harris, "Digital Design and Computer Architecture"