

RLC Transient Response (H.1)

20150612


The necessities in Electric Circuit
wikiversity

Copyright (c) 2015 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".

DC Steady State Solution

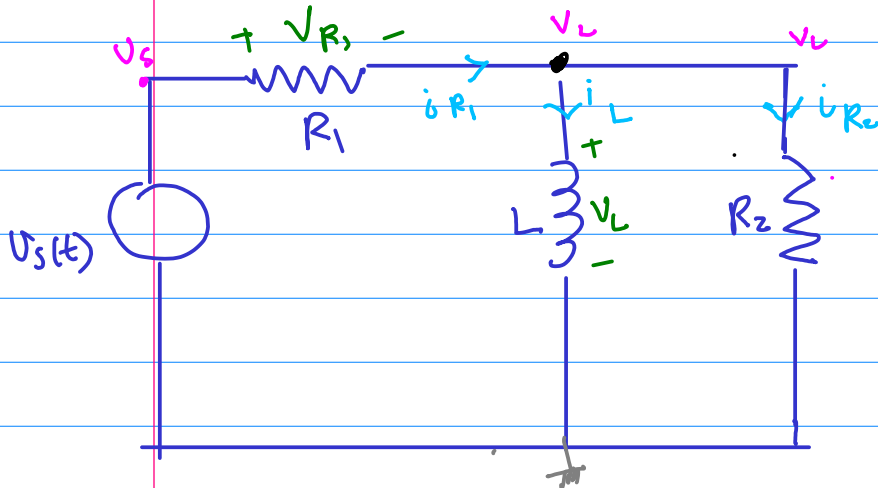변하지 않는 input에 대한 Steady state 출력 값
Constant input



$$v_L = L \frac{di_L}{dt}$$

KCL $i_{R_1} - i_L - i_{R_2} = 0$

$$\frac{v_s - v_L}{R_1} - i_L - \frac{v_L}{R_2} = 0$$

$$\frac{v_s}{R_1} - \frac{L}{R_1} \frac{di_L}{dt} - i_L - \frac{L}{R_2} \frac{di_L}{dt} = 0$$

$$- \left(\frac{L}{R_1} + \frac{L}{R_2} \right) \frac{di_L}{dt} - i_L + \frac{v_s}{R_1} = 0$$

$$\frac{L(R_1 + R_2)}{R_1 R_2} \frac{di_L}{dt} + i_L = \frac{1}{R_1} v_s$$


$$\tau \frac{dx}{dt} + x(t) = K_s F$$

$$\frac{di_L}{dt} + \frac{R_1 R_2}{L(R_1 + R_2)} i_L = \frac{R_2}{L(R_1 + R_2)} v_s$$

$$\frac{L(R_1 + R_2)}{R_1 R_2} \frac{di_L}{dt} + i_L = \frac{1}{R_1} U_S$$

$$\tau \frac{dx}{dt} + |x(t)| = K_S \bar{F}$$

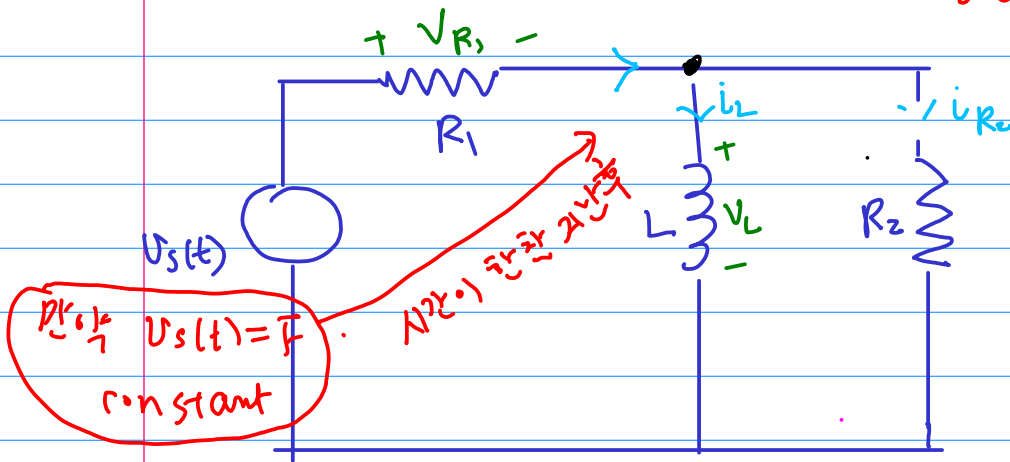흐르는 전류가 일정 (변함 X) $\rightarrow \frac{di_L}{dt} = 0$






$U_S(t) = \bar{F}$
 constant

$$\frac{L(R_1 + R_2)}{R_1 R_2} \frac{di_L(\infty)}{dt} + i_L(\infty) = \frac{1}{R_1} \bar{F}$$


$$\tau \frac{dx(\infty)}{dt} + |x(\infty)| = K_S \bar{F}$$

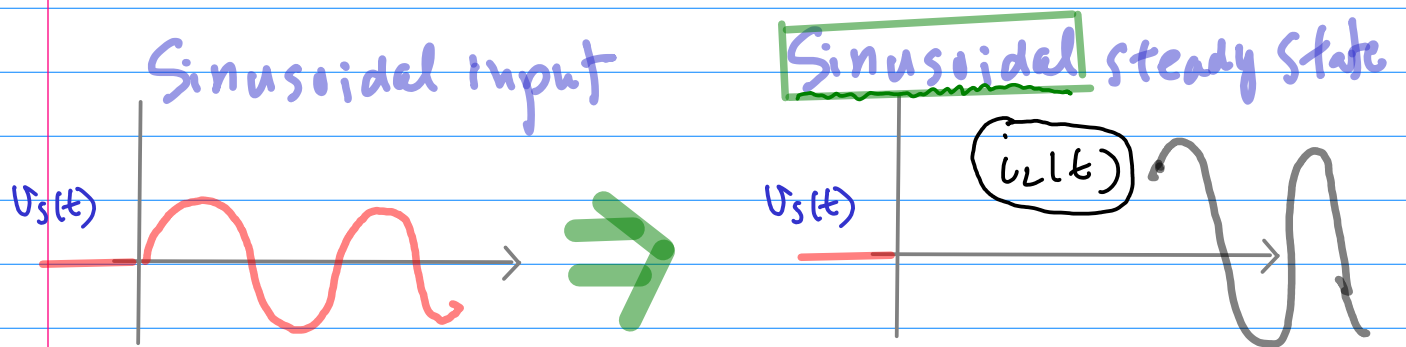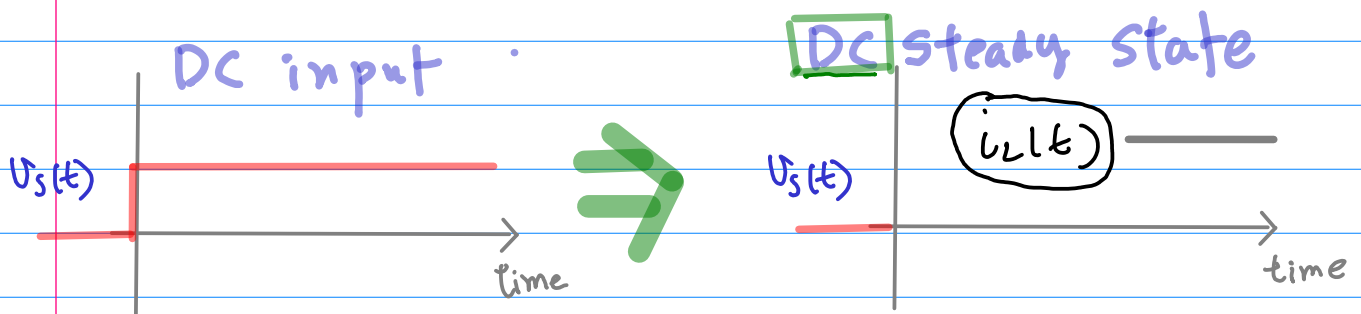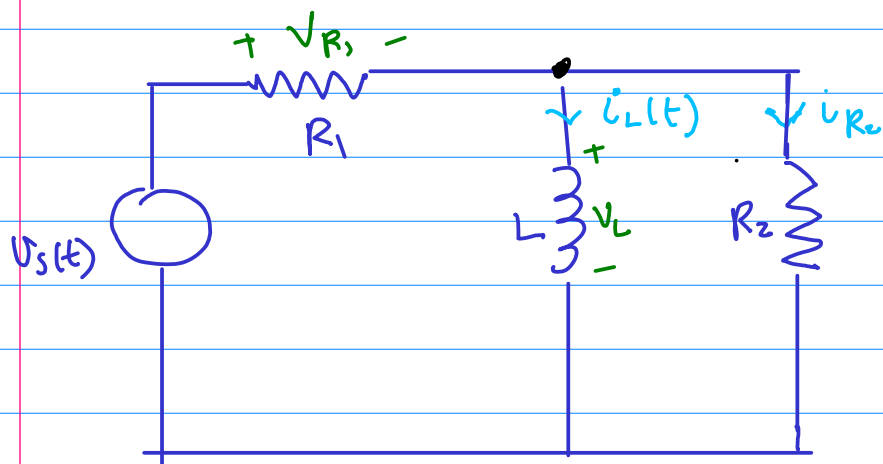$i_L(\infty) = \frac{1}{R_1} \bar{F}$ \boxed{DC} steady state 2V 6A



phasor
+
Impedance

DC Steady state

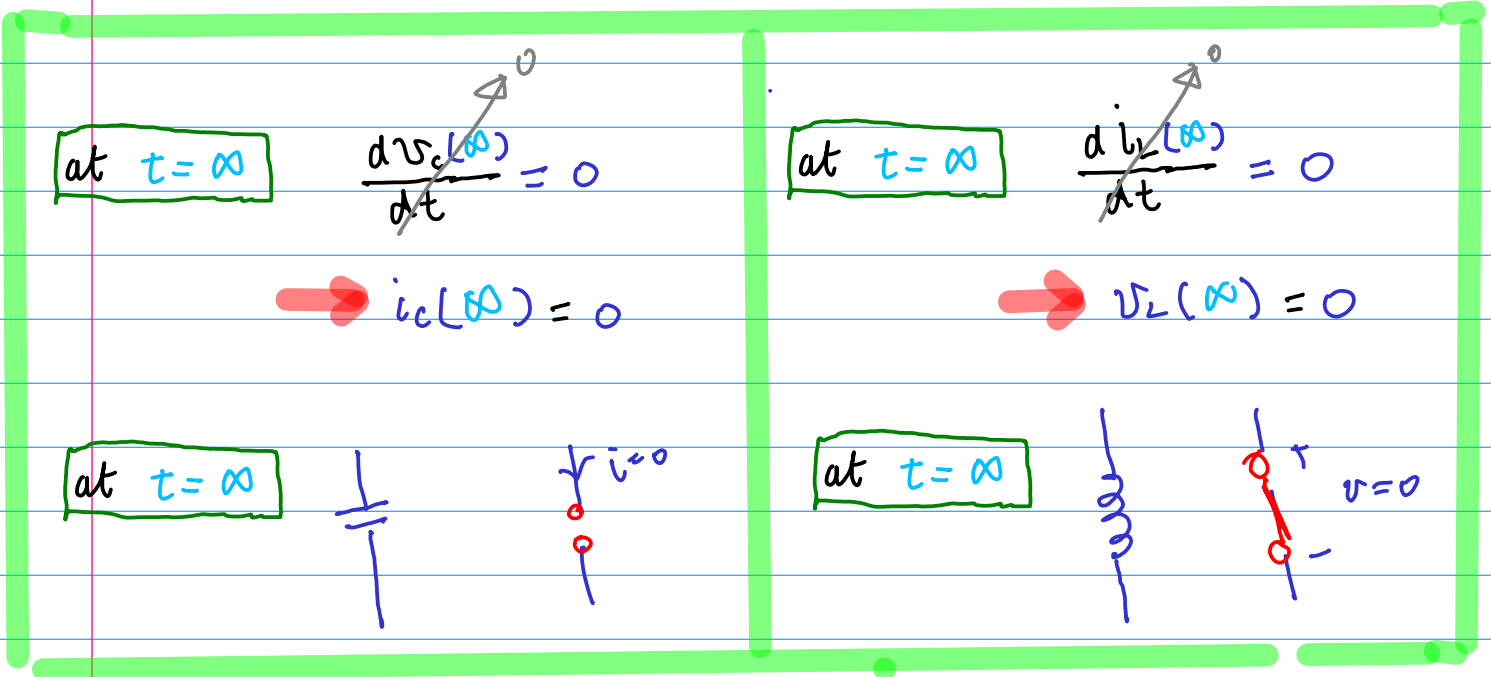

$$\tau \left(\frac{dx}{dt} \right) + 1 x(t) = K_s F \quad x(\infty) = \underline{K_s F}$$

$$\frac{1}{\omega_0^2} \left(\frac{d^2x(t)}{dt^2} \right) + 2 \zeta \frac{1}{\omega_n} \left(\frac{dx(t)}{dt} \right) + 1 x(t) = K f(t)$$

$$\underline{x(\infty) = K f(t)}$$

constant input을 가하는 Steady state onky $x(t)$ 는 $t = \infty$ 에서 $\frac{dx}{dt} = 0$ 이므로

$$\frac{d^2x}{dt^2} = \frac{dx}{dt} = 0$$


Sinusoidal Steady state

at $t = \infty$

$$\frac{d v_c(t)}{dt} = 0$$

→ $i_c(\infty) = 0$

at $t = \infty$

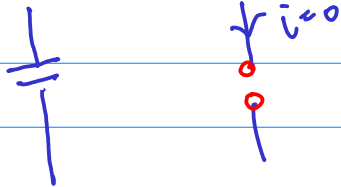


at $t = \infty$


$$\frac{d i_L(t)}{dt} = 0$$

→ $v_L(\infty) = 0$

at $t = \infty$

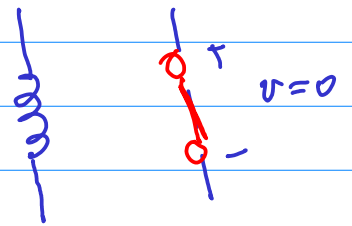

$$v_c(t) = A \cos \omega t$$


$$i_c = C \frac{d v_c}{dt}$$

$$I = \frac{1}{j \omega C} V$$

Transient Response : 1st Order System

$$\tau \frac{dx}{dt} + x(t) = K_s \bar{F}$$

$$x(t) \begin{cases} \rightarrow V_c(t) \\ \rightarrow i_L(t) \end{cases}$$

- ① find $x(0^-)$ & $x(\infty)$ 2 steady state values
- ② find $x(0^+)$ & $\dot{x}(0^+)$ initial conditions
- ③ find 1st order diff Eq

$$\tau \frac{dx}{dt} + x(t) = K_s \bar{F}$$

- ④ find τ


- ⑤ find $x(t) = \underbrace{x_h(t)} + x_p(t)$ $x(\infty)$

- ⑥ find $\alpha = [x(0) - x(\infty)]$

$$\tau \frac{dx}{dt} + x(t) = K_s \bar{F}$$









$$x(t) = [x(0) - x(\infty)] e^{-t/\tau} + x(\infty) \quad t \geq 0$$

DC input

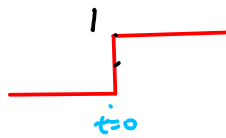


$$u(t) = \begin{cases} 1 & t > 0 \\ 0 & t < 0 \end{cases}$$


step function

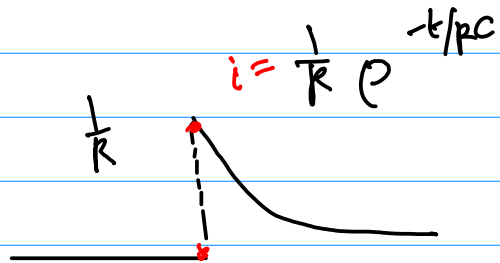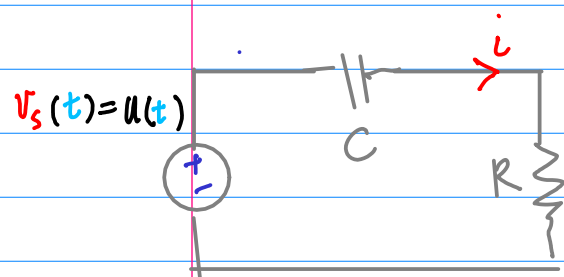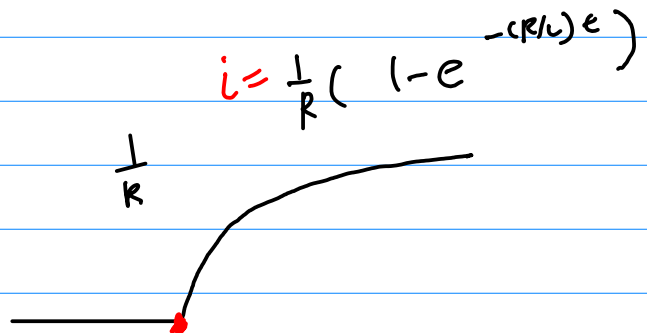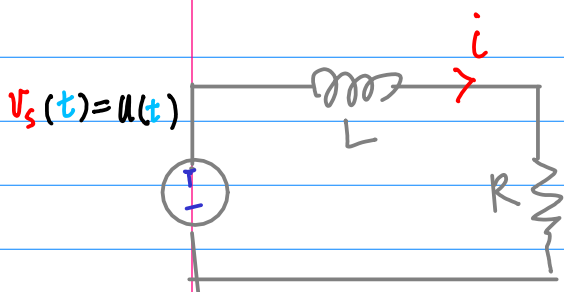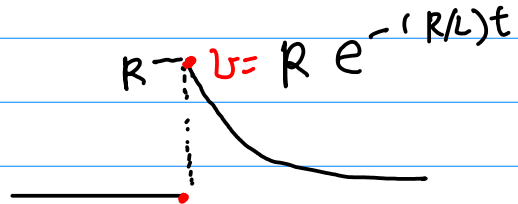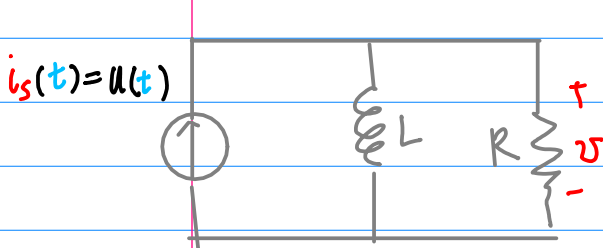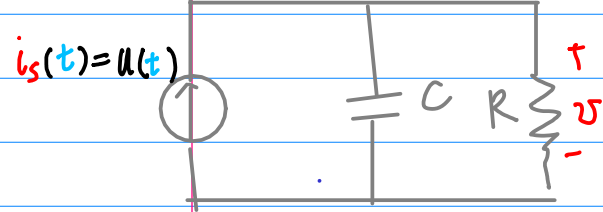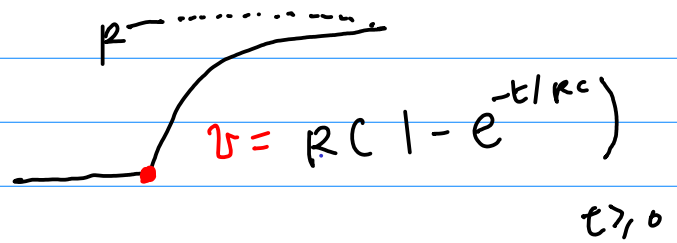


Unit step function

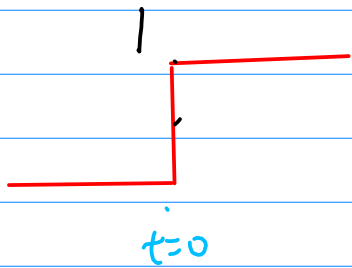
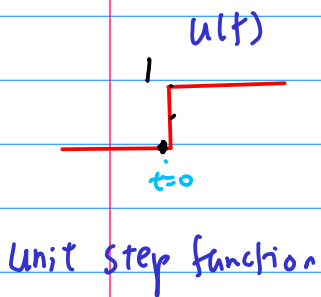
$$u(t) = \begin{cases} 1 & t > 0 \\ 0 & t < 0 \end{cases}$$



Step response

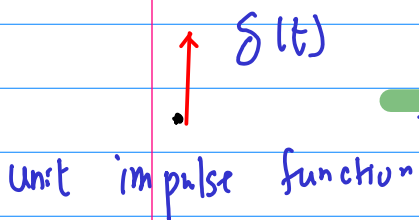


Impulse response $h(t)$

Zero State Response (ZSR)


$t < 0$

input $x(t) = 0$

no initial condition.

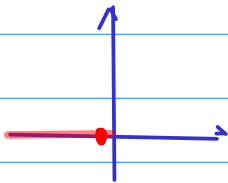

output $y(t) = 0$

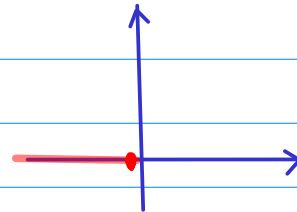

$t > 0$ 일 때

non-zero input $x(t)$ 에 의한
output response

Zero Input Response (ZIR)

$t > 0$









input $x(t) = 0$ no input

non-zero initial condition에 의해









output $t > 0$ 나타남

→ transient response 일 수 있음.


$t=0^+$

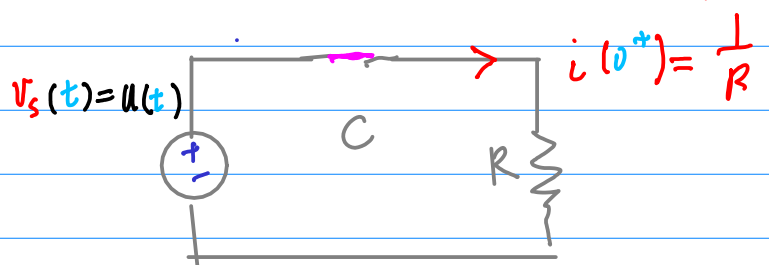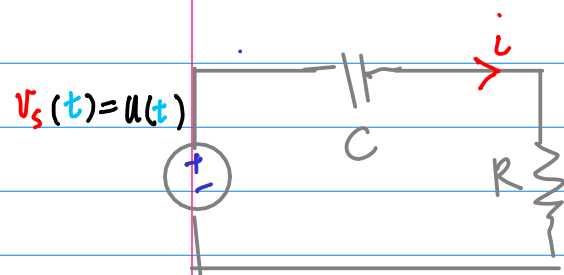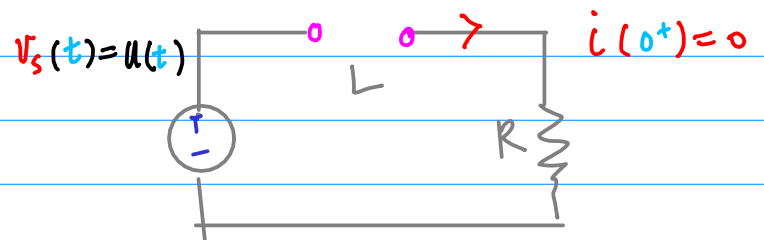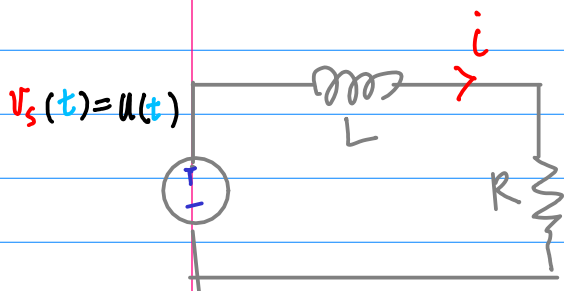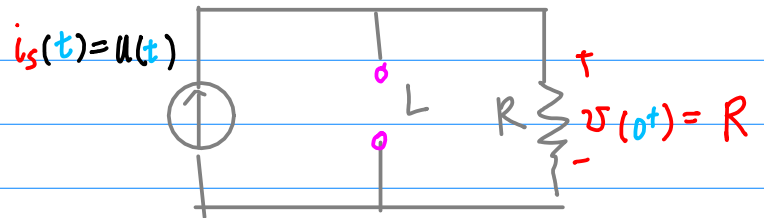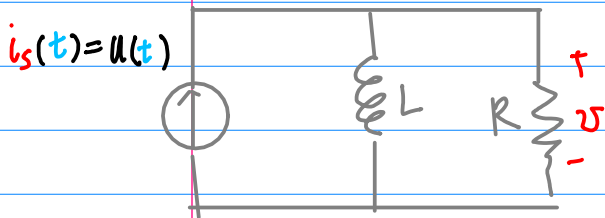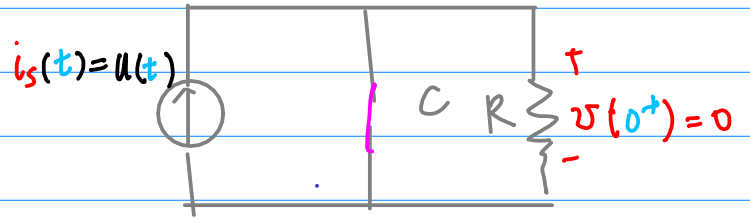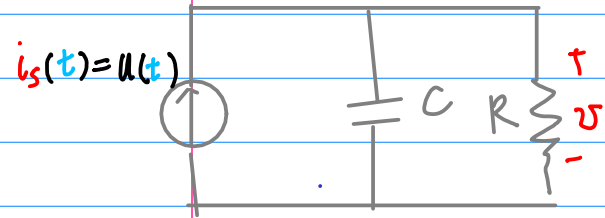


$t = \infty$

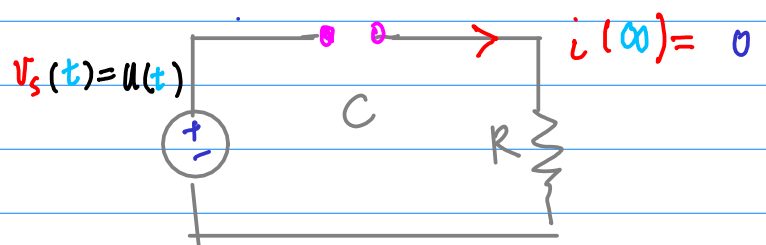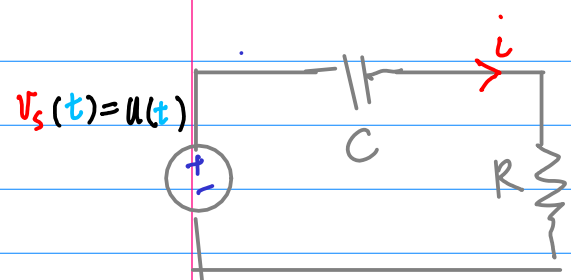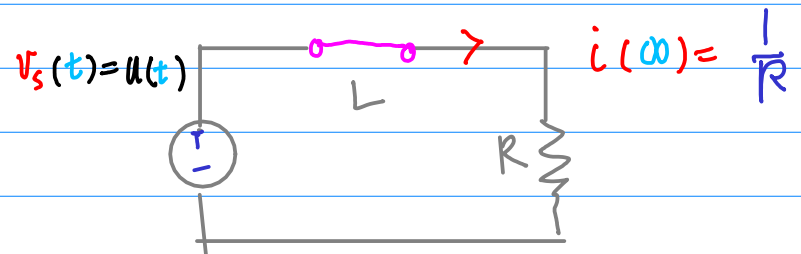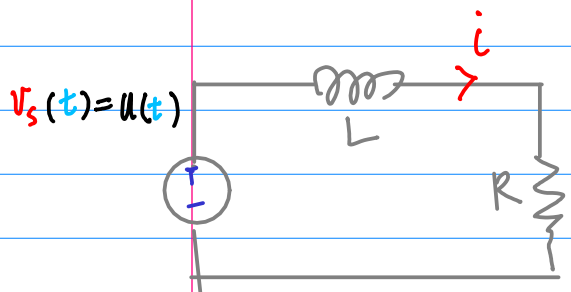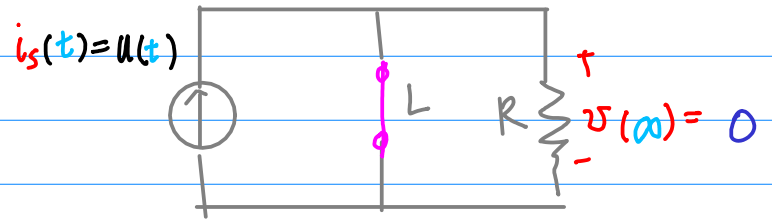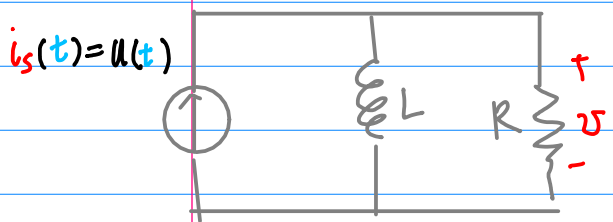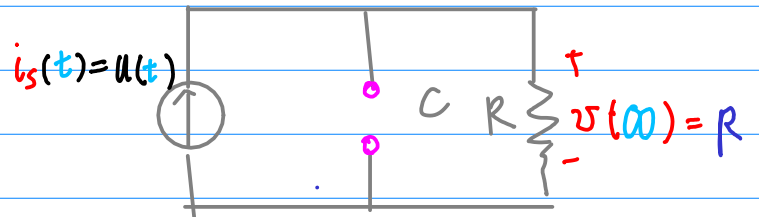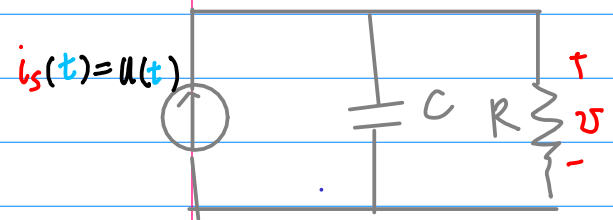


$i_s(t) = u(t)$

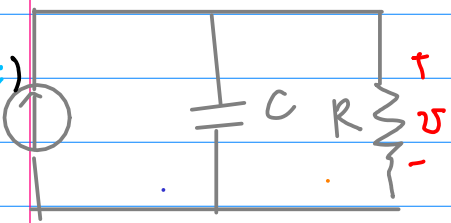

$v(0^+) = 0 \quad v(\infty) = R$

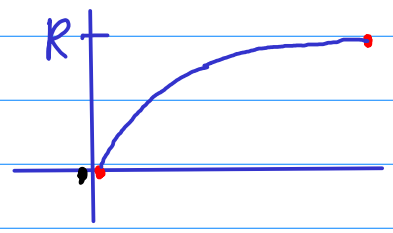


$i_s(t) = u(t)$

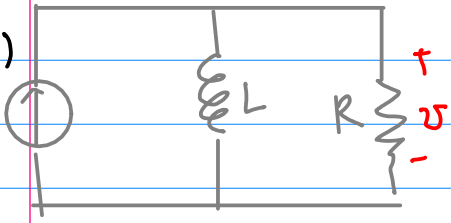


$v(0^+) = R \quad v(\infty) = 0$


discontinuous

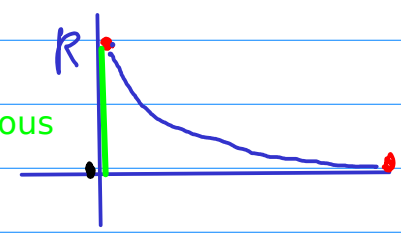


$v_s(t) = u(t)$

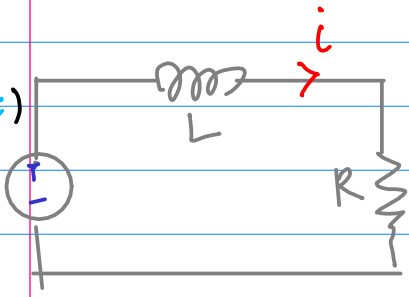

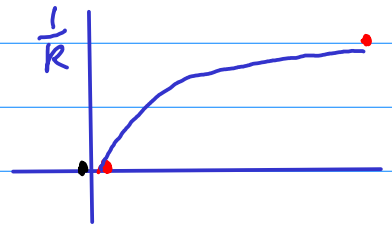$i(0^+) = 0 \quad i(\infty) = \frac{1}{R}$




$v_s(t) = u(t)$

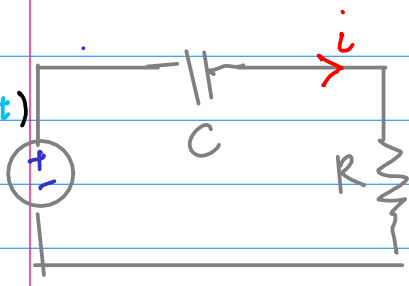

$i(0^+) = \frac{1}{R} \quad i(\infty) = 0$


discontinuous

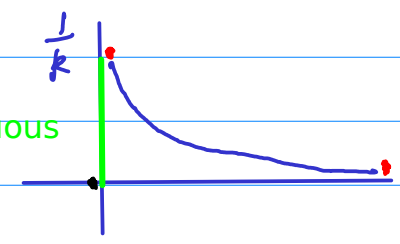

ODE


init cond 0^+

 $t > 0$

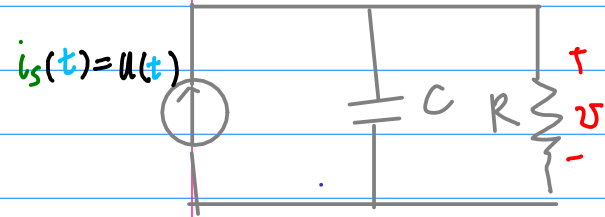

$$C \frac{dv}{dt} + \frac{v}{R} = i_s$$
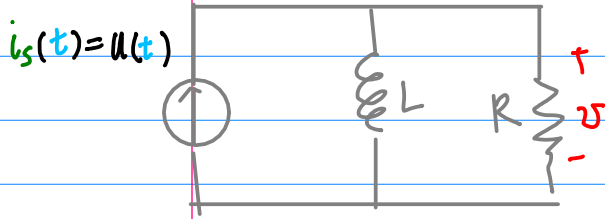
$$\frac{dv}{dt} + \frac{v}{RC} = \frac{1}{C} i_s$$




$$L \frac{di}{dt} = v \quad i_2 = \frac{1}{L} \int v(t) dt$$

$$\frac{1}{L} \int_0^t v dt + \frac{v}{R} = i_s$$


$$\frac{dv}{dt} + \frac{R}{L} v = R \frac{di_s}{dt}$$
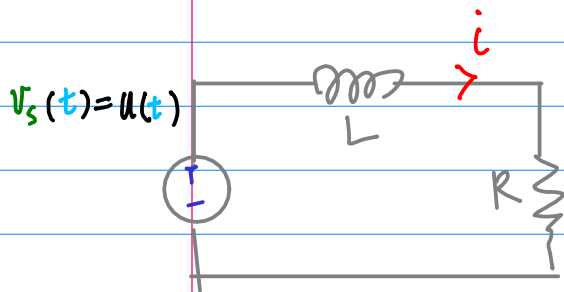
$$\frac{1}{L} v + \frac{1}{R} \frac{dv}{dt} = \frac{di_s}{dt}$$



$$L \frac{di}{dt} + R i = v_s$$
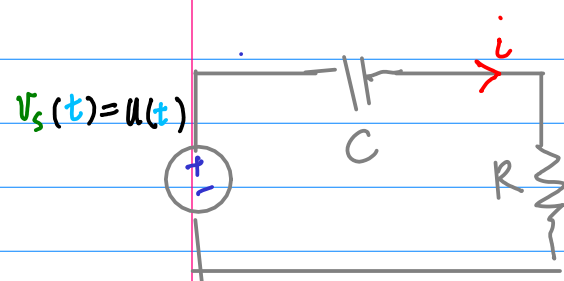
$$\frac{di}{dt} + \frac{R}{L} i = \frac{1}{L} v_s$$




$$C \frac{dv_c}{dt} = i \quad v_c = \frac{1}{C} \int i_c dt$$

$$\frac{1}{C} \int_0^t i dt + R i = v_s$$

$$\frac{di}{dt} + \frac{1}{RC} i = \frac{1}{R} \frac{dv_s}{dt}$$

$$\frac{1}{C} i + R \frac{di}{dt} = \frac{dv_s}{dt}$$

I

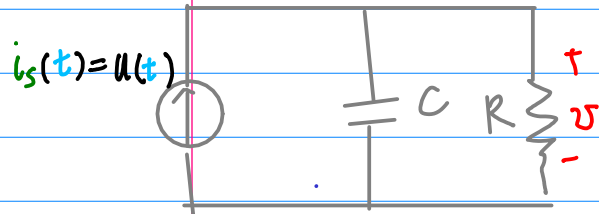

$$C \frac{dv}{dt} + \frac{v}{R} = i_s$$

$$\frac{dv}{dt} + \frac{v}{RC} = \frac{1}{C} i_s$$

$$v_h = C_1 e^{-\frac{t}{RC}}$$

$$v_p = A$$

$$0 + \frac{A}{RC} = \frac{1}{C}$$

$$A = R$$

Initial condition $v(0^+) = 0$

$$v(t) = C_1 e^{-\frac{t}{RC}} + R$$

$$v(0^+) = C_1 e^{-\frac{0^+}{RC}} + R = 0$$

$$C_1 = -R$$

$$v(t) = -R e^{-\frac{t}{RC}} + R = R(1 - e^{-\frac{t}{RC}})$$

$$\frac{dv}{dt} + \frac{v}{RC} = \frac{1}{C} i_s$$

Laplace Transform

$$sV(s) - v(0^-) + \frac{1}{RC} V(s) = \frac{1}{sC}$$

$$(s + \frac{1}{RC}) V(s) = v(0^-) + \frac{1}{sC}$$


$$V(s) = \frac{v(0^-)}{(s + \frac{1}{RC})} + \frac{1/C}{s(s + \frac{1}{RC})}$$

initial condition of response

input $u(t)$ of response

$$V(s) = \frac{1/c}{s(s + \frac{1}{RC})} = \frac{R/c}{R/c} \left(\frac{1}{s} - \frac{1}{s + \frac{1}{RC}} \right)$$
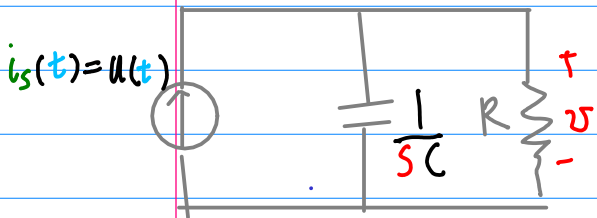
$$v(t) = R \left(1 - e^{-\frac{t}{RC}} \right)$$



$$\frac{1}{sC} \parallel R = \frac{1}{sC + \frac{1}{R}} = \frac{R}{sRC + 1}$$




$I_s(s)$

$$\frac{R}{sRC + 1} = V(s)$$

$$V(s) = \frac{R}{s(sRC + 1)} = \frac{1/c}{s(s + \frac{1}{RC})}$$

(4)

$$v_s(t) = u(t)$$

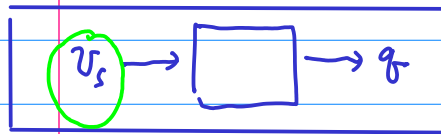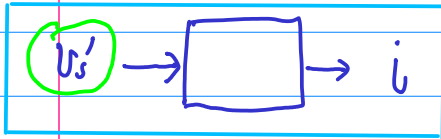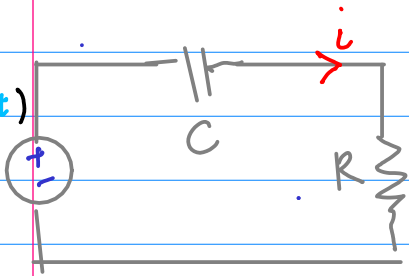

$$C \frac{dv_c}{dt} = i_c \quad v_c = \frac{1}{C} \int i_c dt$$

$$\frac{1}{C} \int_0^t i dt + Ri = v_s$$

$$\frac{1}{C} i + R \frac{di}{dt} = \frac{dv_s}{dt}$$

$$\frac{di}{dt} + \frac{1}{RC} i = \frac{1}{R} \frac{dv_s}{dt}$$

$$\frac{dq}{dt} + \frac{1}{RC} q = \frac{1}{R} v_s$$

$$q_h(t) = c_1 e^{-\frac{t}{RC}}$$

$$q_p(t) = A \quad 0 + \frac{1}{RC} A = \frac{1}{R}$$

$$= C$$


$$q(t) = c_1 e^{-\frac{t}{RC}} + C$$

$$q(0^+) = c_1 e^{-\frac{0^+}{RC}} + C = 0 \quad c_1 = -C$$

$$q(t) = C(1 - e^{-\frac{t}{RC}})$$

$$i(t) = q'(t) = \frac{1}{R} e^{-\frac{t}{RC}}$$

$$V_s(t) = u(t)$$

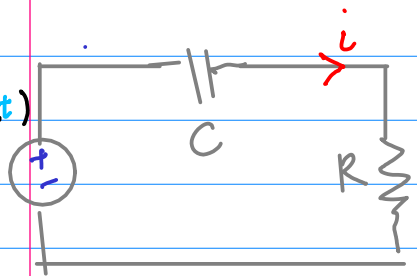

$$C \frac{dv_c}{dt} = i_c \quad v_c = \frac{1}{C} \int i_c dt$$

$$\frac{1}{C} \int_0^t i dt + Ri = v_s$$

$$\frac{1}{C} i + R \frac{di}{dt} = \frac{dv_s}{dt}$$

$$\frac{di}{dt} + \frac{1}{RC} i = \frac{1}{R} \frac{dv_s}{dt}$$


$$s \bar{I}(s) - i(0^-) + \frac{1}{RC} \bar{I}(s) = \frac{1}{R} (s V(s) - v(0^-))$$

$$(s + \frac{1}{RC}) \bar{I}(s) = \frac{1}{R} s \frac{1}{s}$$

$$\bar{I}(s) = \frac{1}{R} \frac{1}{(s + \frac{1}{RC})}$$

$$i(t) = \frac{1}{R} e^{-\frac{t}{RC}}$$

$$\frac{1}{sC} \quad sL$$

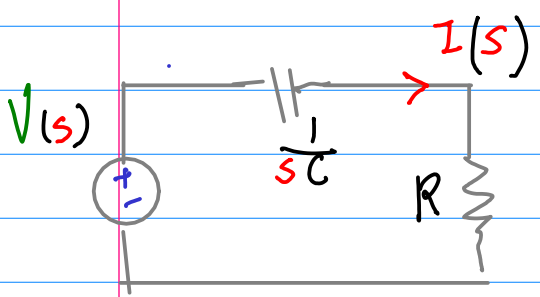


$$I(s) = \frac{V(s)}{(\frac{1}{sC} + R)} = \frac{\frac{1}{s}}{(\frac{1}{sC} + R)}$$

$$\frac{1/R}{\frac{1}{RC} + s}$$


$$\frac{1}{R} e^{-\frac{t}{RC}}$$

$$y^{(N)} + a_1 y^{(N-1)} + \dots + a_{N-1} y^{(1)} + a_N y = x$$

base system

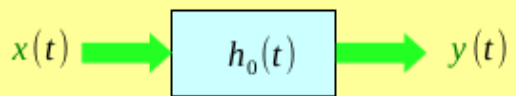

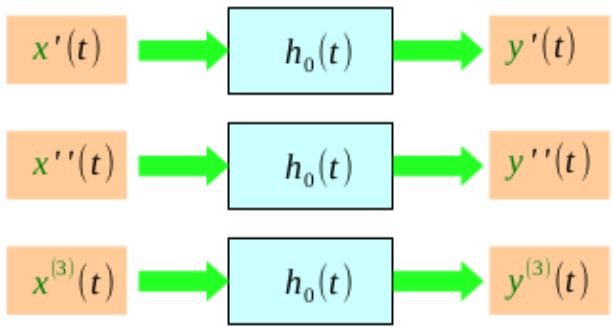notation: $y^{(N)} = \frac{d^N y}{dt^N} = \frac{d^N}{dt^N} y(t)$



$$y'' + a y' + b y(t) = x(t)$$

$$y'' + a y' + b y'(t) = x'(t)$$

$$\frac{d^2}{dt^2} \left(\frac{dy}{dt} \right) + a \frac{d}{dt} \left(\frac{dy}{dt} \right) + b \left(\frac{dy}{dt} \right) = \left(\frac{dx}{dt} \right)$$

$$y'' + a y' + b y(t) = x(t)$$

Transient Response : 2nd Order System

$$\frac{1}{\omega_0^2} \frac{d^2 x(t)}{dt^2} + 2 \frac{\zeta}{\omega_n} \frac{dx(t)}{dt} + 1 x(t) = K f(t)$$

$$x(t) \begin{cases} \rightarrow V_c(t) \\ \rightarrow i_L(t) \end{cases}$$

① find $x(0^-)$ & $x(\infty)$ 2 steady state values

② find $x(0^+)$ & $\dot{x}(0^+)$ initial conditions

③ find 2nd order diff Eq.

$$\frac{1}{\omega_0^2} \frac{d^2 x(t)}{dt^2} + 2 \frac{\zeta}{\omega_n} \frac{dx(t)}{dt} + 1 x(t) = K f(t)$$

④ find ω_n & ζ

⑤ find $x(t) = \underbrace{x_h(t)} + \underbrace{x_p(t)} = x(\infty)$

⑥ find α_1 & α_2

Constant input : DC

$$\frac{1}{\omega_0^2} \frac{d^2 x(t)}{dt^2} + 2 \zeta \frac{dx(t)}{dt} + 1 x(t) = K f(t)$$

(a) $\zeta > 1$	(b) $\zeta = 1$	(c) $\zeta < 1$
$\alpha_1 e^{(-\zeta\omega_n + \sqrt{\zeta^2 - 1}\omega_n)t}$ + $\alpha_2 e^{(-\zeta\omega_n - \sqrt{\zeta^2 - 1}\omega_n)t}$ + $x(\infty)$	$\alpha_1 e^{(-\zeta\omega_n)t}$ + $\alpha_2 t e^{(-\zeta\omega_n)t}$ + $x(\infty)$	$\alpha_1 e^{(-\zeta\omega_n + j\sqrt{1-\zeta^2}\omega_n)t}$ + $\alpha_2 e^{(-\zeta\omega_n - j\sqrt{1-\zeta^2}\omega_n)t}$ + $x(\infty)$

$x(\infty)$... particular for ced

Homogeneous sol \rightarrow natural response $\rightarrow 0$ vanishes

$$\begin{aligned} & \alpha_1 e^{(-\zeta\omega_n + \sqrt{\zeta^2 - 1}\omega_n)t} + \alpha_2 e^{(-\zeta\omega_n - \sqrt{\zeta^2 - 1}\omega_n)t} \\ & \alpha_1 e^{(-\zeta\omega_n)t} + \alpha_2 t e^{(-\zeta\omega_n)t} \\ & \alpha_1 e^{(-\zeta\omega_n + j\sqrt{1-\zeta^2}\omega_n)t} + \alpha_2 e^{(-\zeta\omega_n - j\sqrt{1-\zeta^2}\omega_n)t} \end{aligned}$$

$$e^{-\zeta\omega_n t}$$

$$e^{-\zeta\omega_n t} \rightarrow 0$$

$$\boxed{\zeta > 0}$$

$$\omega_n > 0$$

$$t > 0$$



$$\begin{aligned} & c_1 e^{-\zeta\omega_n t} \cos(\sqrt{1-\zeta^2}\omega_n t) \\ & + c_2 e^{-\zeta\omega_n t} \sin(\sqrt{1-\zeta^2}\omega_n t) \end{aligned}$$

① find $x(0^-)$ & $x(\infty)$



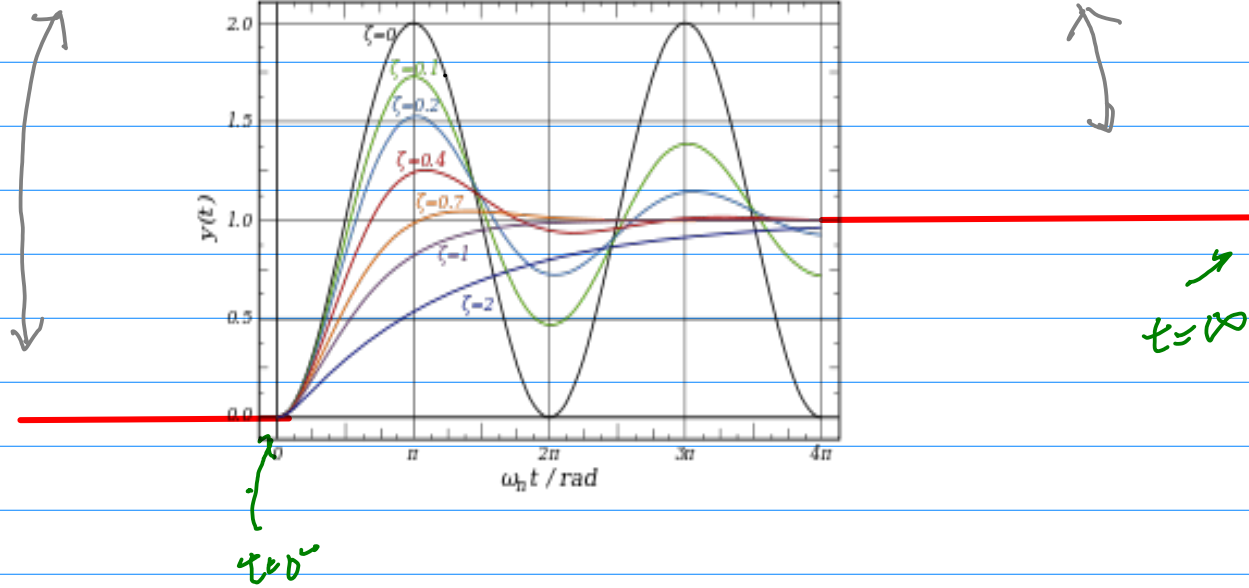
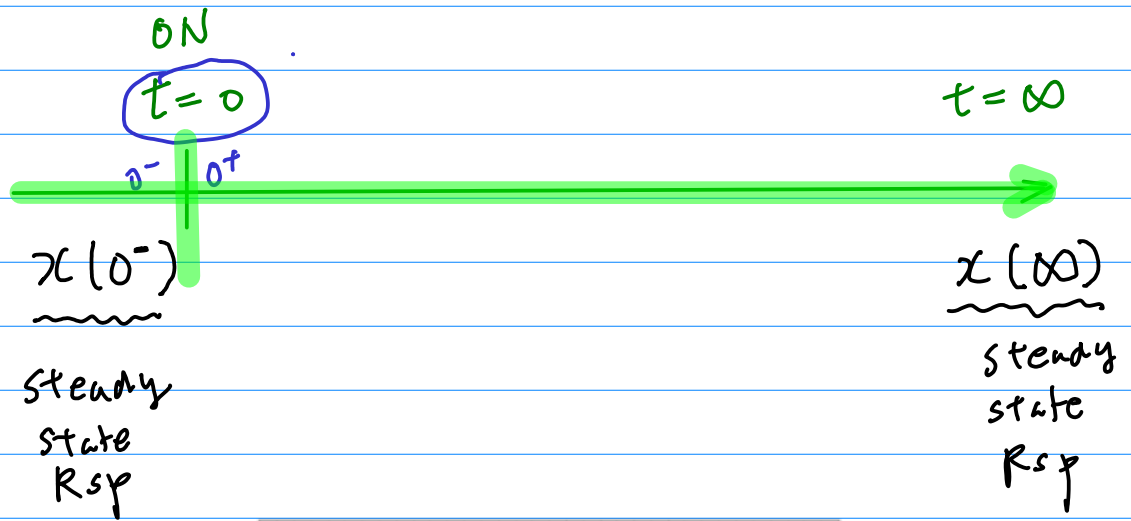


Fig 5.80 $t = 0^-$

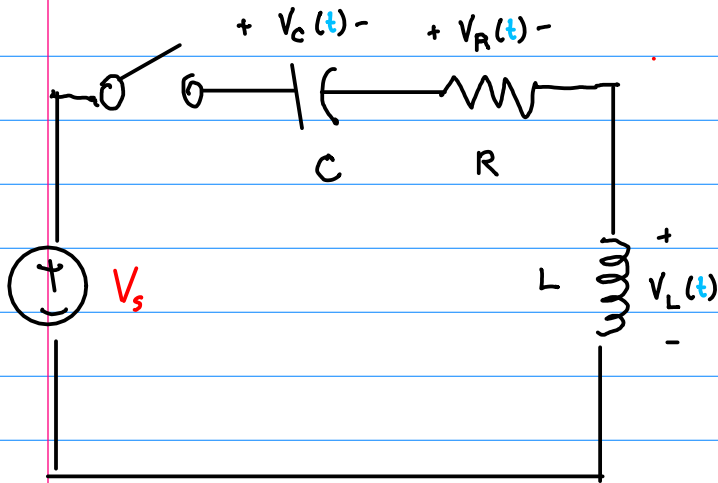


$\frac{d}{dt} \ln(1)$
 \downarrow
 $\begin{cases} V_C(0^-) = 5 \\ i_L(0^-) = 0 \end{cases}$

$t = 0^+$

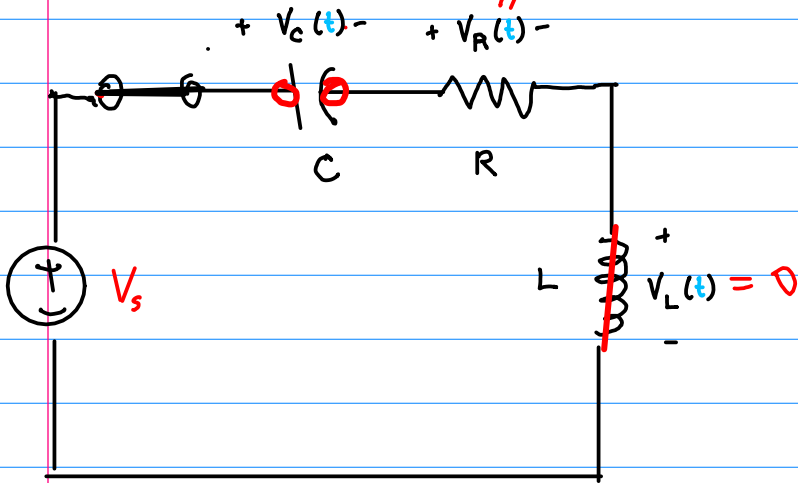


$\begin{cases} V_C(\infty) = 25 \\ i_L(\infty) = 0 \end{cases}$

$t = 0^-$

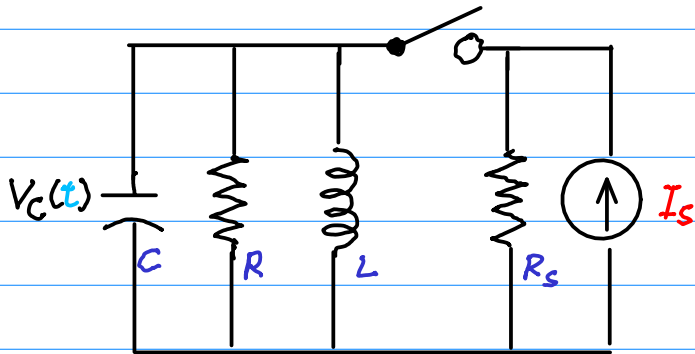

$$i_L(0^-) = 0$$
$$U_C(0^-) = 0$$

$t = \infty$


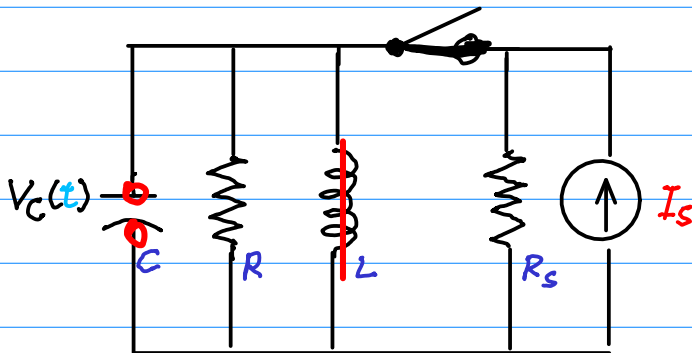


$$i_L(\infty) = I_s$$
$$U_C(\infty) = 0$$

② find $x(0^+)$, $\dot{x}(0^+)$




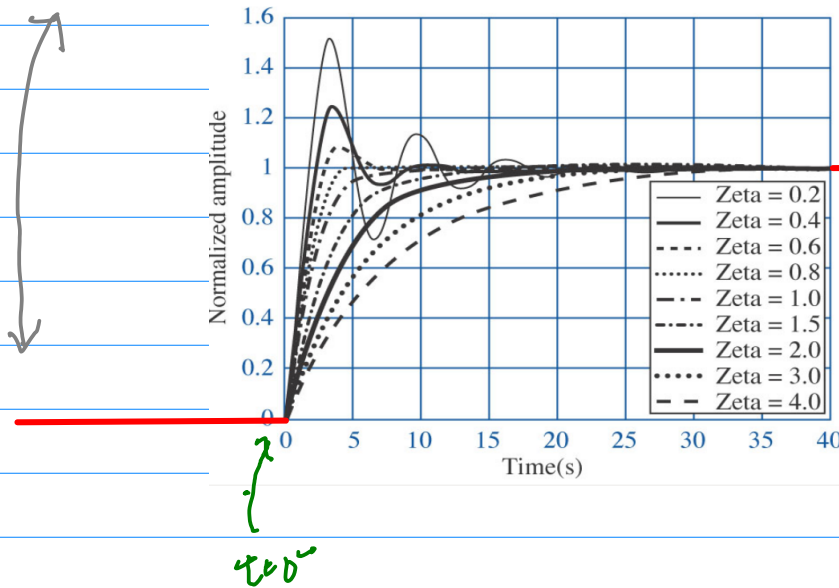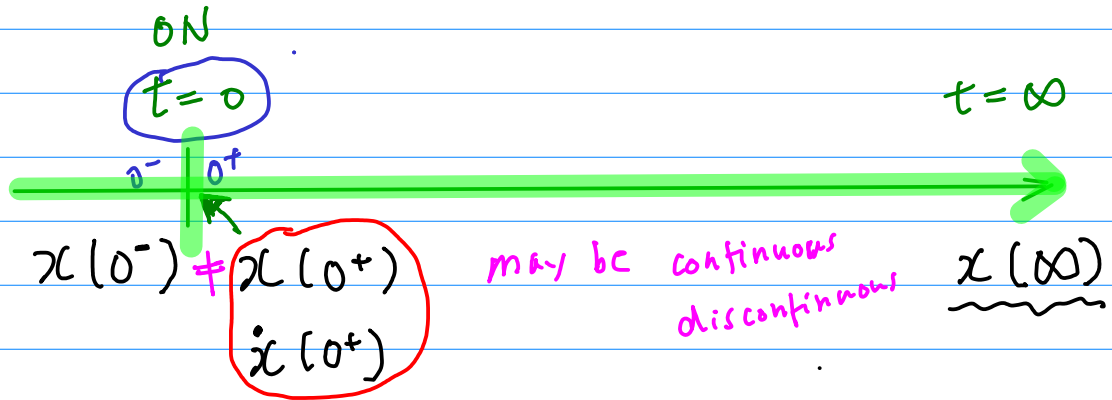continuous v_C : $v_C(0^-) = v_C(0^+)$
 continuous i_L : $i_L(0^-) = i_L(0^+)$



Step 2

$t = 0^+$

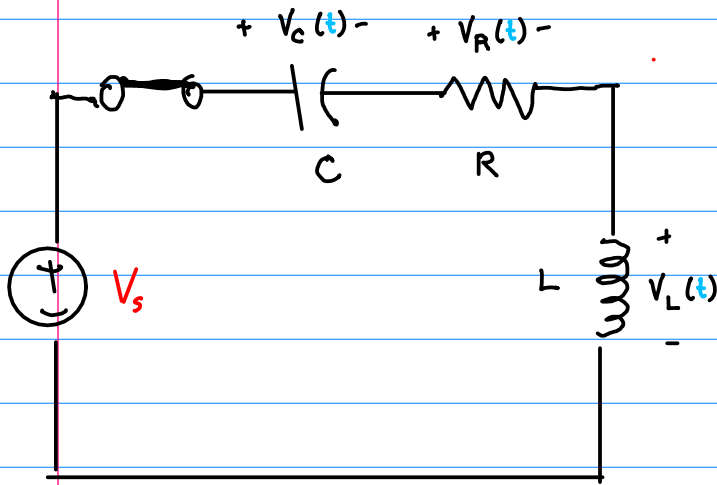

$\frac{2}{21} \text{ mV}$

$$\begin{cases} V_c(0^-) = 5 = V_c(0^+) \\ i_L(0^-) = 0 = i_L(0^+) \end{cases}$$

continue

$$i_L'(0^+) = ?$$

$t = 0^+$ KVL


$$V_s - V_c(0^+) - R i_L(0^+) - V_L(0^+) = 0$$

$$V_s - V_c(0^+) - R i_L(0^+) - L \frac{di_L(0^+)}{dt} = 0$$

$$\frac{di_L(0^+)}{dt} = \frac{1}{L} \left(\underbrace{V_s}_{4V} - \underbrace{V_c(0^+)}_{5} - \underbrace{R i_L(0^+)}_{0} \right)$$

seepz

$t=0^+$

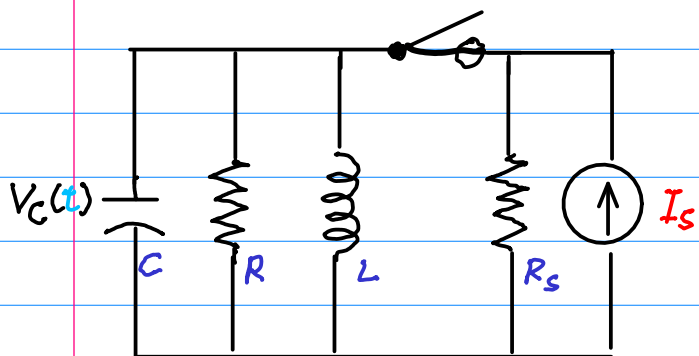

$$i_L(0^-) = 0 = i_L(0^+)$$
$$V_C(0^-) = 0 = V_C(0^+)$$

$$V_C'(0^+) = ?$$

$$I_s - \frac{V_C(t)}{R_s} - i_L(t) - \frac{V_C(t)}{R} - C \frac{dV_C(t)}{dt} = 0$$

$$I_s - \frac{V_C(0^+)}{R_s} - i_L(0^+) - \frac{V_C(0^+)}{R} - C \frac{dV_C(0^+)}{dt} = 0$$

$$\frac{dV_C(0^+)}{dt} = \frac{1}{C} I_s$$

③ find 2nd order diff eq

$$\frac{1}{\omega_0^2} \frac{d^2 x(t)}{dt^2} + 2 \zeta \frac{dx(t)}{dt} + 1 x(t) = K f(t)$$


$t > 0$ \Rightarrow switch "ON"

$$x(t) = \begin{cases} v_c(t) & \leftarrow \text{parallel same volt.} \\ \underline{i_L(t)} & \leftarrow \text{series same current} \end{cases}$$

$$LC \frac{d^2 i_L}{dt^2} + RL \frac{di_L}{dt} + 1 i_L(t) = 0$$

$$LC \frac{d^2 v_c}{dt^2} + L \left(\frac{R_s + R}{R_s R} \right) \frac{dv_c}{dt} + 1 v_c(t) = 0$$

$t > 0$

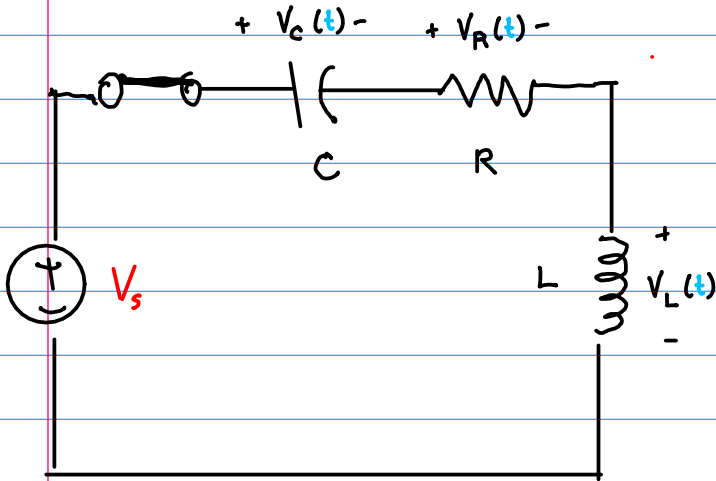

$$V_s - V_C(t) - R \cdot i_L(t) - L \frac{di_L}{dt} = 0$$

$$V_C(t) = \frac{1}{C} \int_{-\infty}^t i_L(t) dt$$

$$\frac{d}{dt} \left\{ V_s - \frac{1}{C} \int_{-\infty}^t i_L(t) dt - R \cdot i_L(t) - L \frac{di_L}{dt} = 0 \right\}$$


↓
KVL

$$-\frac{1}{C} i_L(t) - R \cdot \frac{di_L}{dt} - L \frac{d^2 i_L}{dt^2} = 0$$

$$\dot{I}_L(t) + R L \frac{di_L}{dt} + L C \frac{d^2 i_L}{dt^2} = 0$$

$$L C \frac{d^2 i_L}{dt^2} + R L \frac{di_L}{dt} + 1 \dot{I}_L(t) = 0$$

$t > 0$

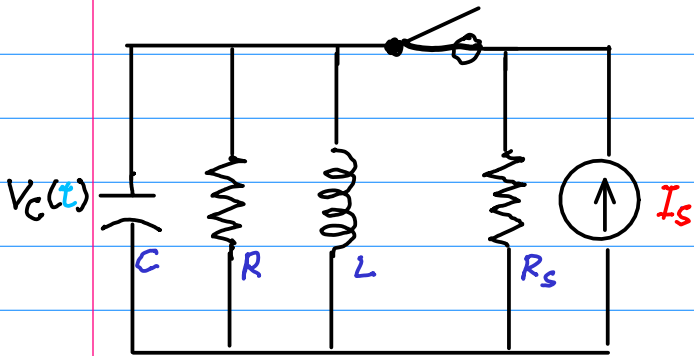

$$L \frac{di_L}{dt} = v_L$$

$$i_L = \frac{1}{L} \int v_L dt$$

KCL

$$I_s - \frac{v_c(t)}{R_s} - i_L(t) - \frac{v_c(t)}{R} - C \frac{dv_c(t)}{dt} = 0$$

$$i_L(t) = \frac{1}{L} \int_{-\infty}^{\infty} v_c(t) dt$$

$$\left\{ \frac{d}{dt} \left[I_s - \frac{v_c(t)}{R_s} - \frac{1}{L} \int_{-\infty}^{\infty} v_c(t) dt - \frac{v_c(t)}{R} - C \frac{dv_c(t)}{dt} \right] = 0 \right\}$$

$$\left(\frac{1}{R_s} + \frac{1}{R} \right) \frac{dv_c}{dt} + \frac{1}{L} v_c(t) + C \frac{d^2 v_c}{dt^2} = 0$$

$$L C \frac{d^2 v_c}{dt^2} + L \left(\frac{R_s + R}{R_s R} \right) \frac{dv_c}{dt} + v_c(t) = 0$$


④

Find

ω_n &

ζ

↑ natural freq ↑ damping ratio

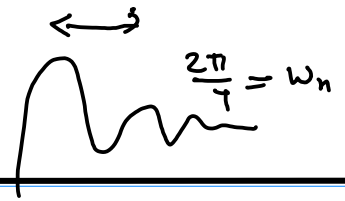

$$\frac{1}{\omega_n^2} \frac{d^2 x(t)}{dt^2} + 2 \frac{\zeta}{\omega_n} \frac{dx(t)}{dt} + 1 x(t) = K f(t)$$

$$LC \frac{d^2 i_L}{dt^2} + RC \frac{di_L}{dt} + 1 i_L(t) = 0$$

$$\omega_n = \sqrt{\frac{1}{LC}} = 1000$$

$$\zeta = RC \frac{\omega_n}{2} = 2.5 \quad \text{overdamping}$$

$$LC \frac{d^2 v_C}{dt^2} + L \left(\frac{R_s + R}{R_s R} \right) \frac{dv_C}{dt} + 1 v_C(t) = 0$$

$$\omega_n = \sqrt{\frac{1}{LC}} = 660$$

$$\zeta = L \left(\right) \frac{\omega_n}{2} = 1 \quad \text{critical damping}$$

5) find $x(t) = \underline{x_h(t)} + x_p(t)$ $x(\infty)$

§ out circuit

5 > 1

$$D > 0$$

2 distinct real roots m_1, m_2

$$x_h(t) \Leftarrow x_h(t) = C_1 e^{m_1 t} + C_2 e^{m_2 t}$$

5 = 1

$$D = 0$$

repeated real root m_1

$$x_h(t) \Leftarrow x_h(t) = C_1 e^{m_1 t} + C_2 t e^{m_1 t}$$

5 < 1

$$D < 0$$

2 complex conjugate root $m_1 = \alpha + j\beta, m_2 = \alpha - j\beta$

$$x_h(t) \Leftarrow x_h(t) = C_1 e^{(\alpha + j\beta)t} + C_2 e^{(\alpha - j\beta)t}$$
$$= e^{\alpha t} (C_3 \cos(\beta t) + C_4 \sin(\beta t))$$

(a) $\zeta > 1$

$$x(t) = x_N(t) + x_F(t)$$

$$\begin{aligned} &= \alpha_1 e^{(-\zeta\omega_n + \sqrt{\zeta^2 - 1}\omega_n)t} \\ &+ \alpha_2 e^{(-\zeta\omega_n - \sqrt{\zeta^2 - 1}\omega_n)t} \\ &+ x(\infty) \end{aligned}$$

$t \geq 0$

(b) $\zeta = 1$


$$x(t) = x_N(t) + x_F(t)$$

$$\begin{aligned} &= \alpha_1 e^{(-\zeta\omega_n)t} \\ &+ \alpha_2 t e^{(-\zeta\omega_n)t} \\ &+ x(\infty) \end{aligned}$$

 (c) $\zeta < 1$

$$x(t) = x_N(t) + x_F(t)$$

$$\begin{aligned} &= \alpha_1 e^{(-\zeta\omega_n + j\sqrt{1-\zeta^2}\omega_n)t} \\ &+ \alpha_2 e^{(-\zeta\omega_n - j\sqrt{1-\zeta^2}\omega_n)t} \\ &+ x(\infty) \end{aligned}$$



① find α_1 & α_2

initial condition

$$\begin{cases} i_L(0^+) \\ \dot{i}_L(0^+) \end{cases}$$

$$\begin{cases} v_C(0^+) \\ \dot{v}_C(0^+) \end{cases}$$

Step 2

② $\zeta > 1$

$$x(t) = \alpha_1 e^{(-\zeta\omega_n + \sqrt{\zeta^2 - 1}\omega_n)t} + \alpha_2 e^{(-\zeta\omega_n - \sqrt{\zeta^2 - 1}\omega_n)t} + x(\infty)$$

$x'(t) \Big|_{t=0^+}$
 $t \geq 0$

③ $\zeta = 1$

$$x(t) = \alpha_1 e^{(-\zeta\omega_n)t} + \alpha_2 t e^{(-\zeta\omega_n)t} + x(\infty)$$

$x'(t) \Big|_{t=0^+}$

④ $\zeta < 1$

$$x(t) = \alpha_1 e^{(-\zeta\omega_n + j\sqrt{1-\zeta^2}\omega_n)t} + \alpha_2 e^{(-\zeta\omega_n - j\sqrt{1-\zeta^2}\omega_n)t} + x(\infty)$$

