

Capacitor in an AC circuit


Copyright (c) 2011 - 2017 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".


Please send corrections (or suggestions) to youngwlim@hotmail.com.

This document was produced by using OpenOffice and Octave.


Everchanging signal pairs

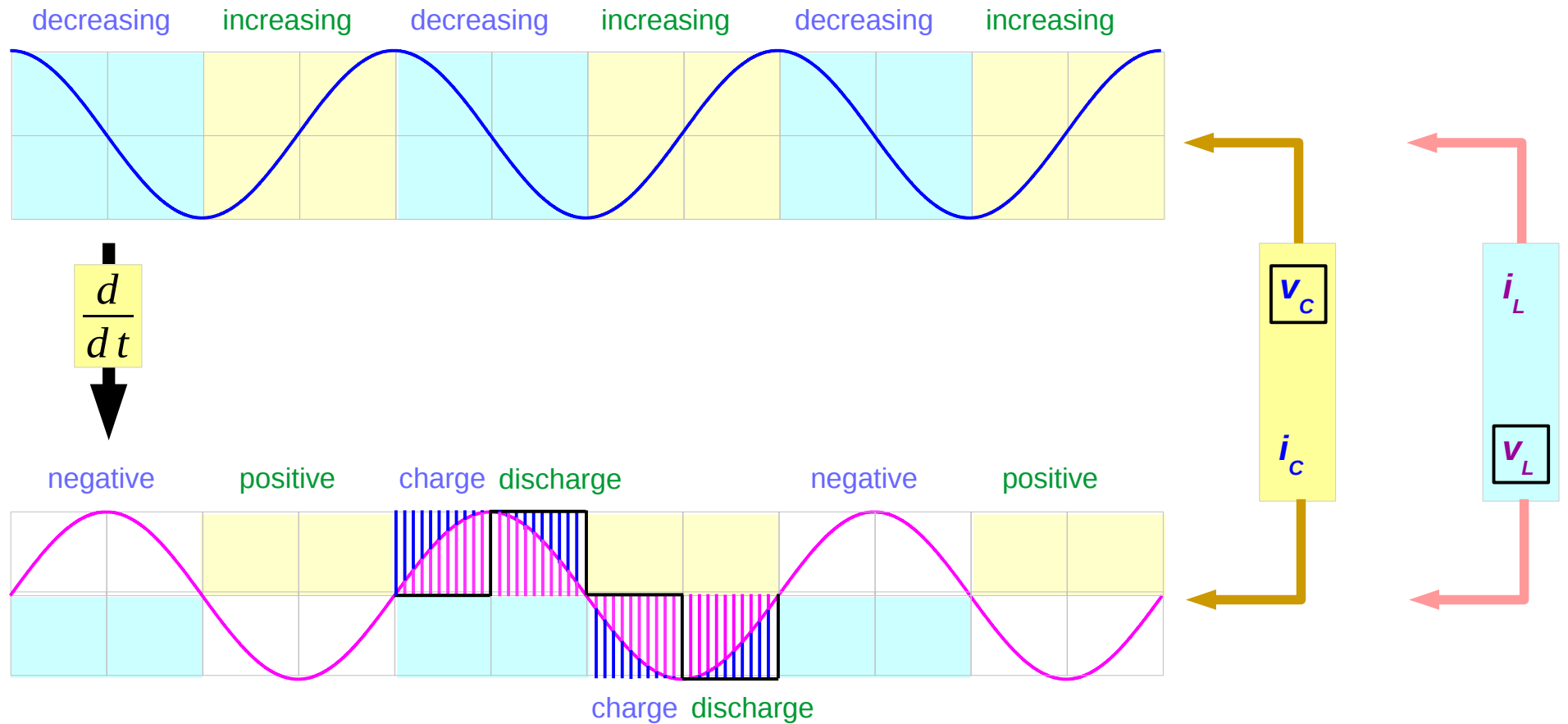


Capacitor Current

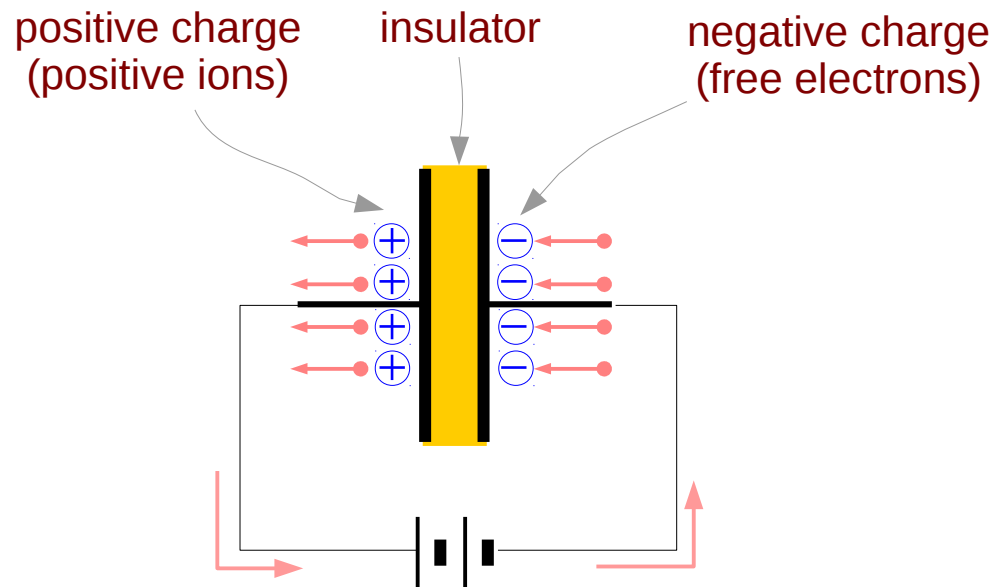

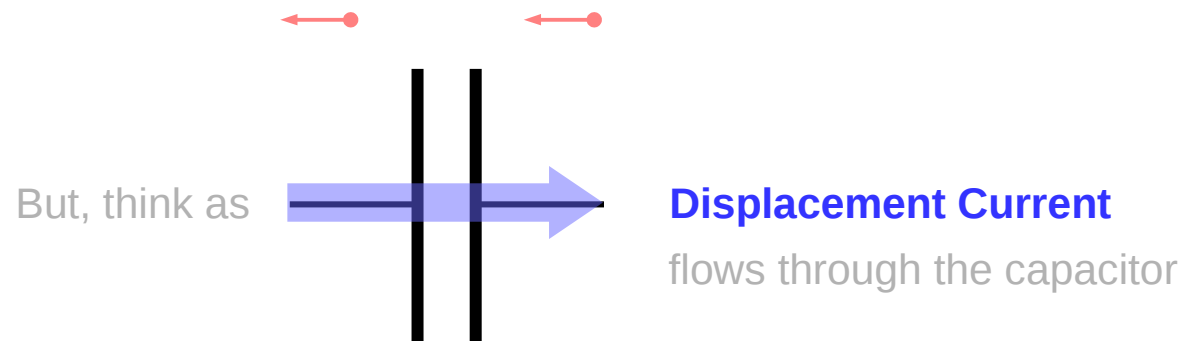No actual electrons movement across insulator materials




Positive ions and free electrons

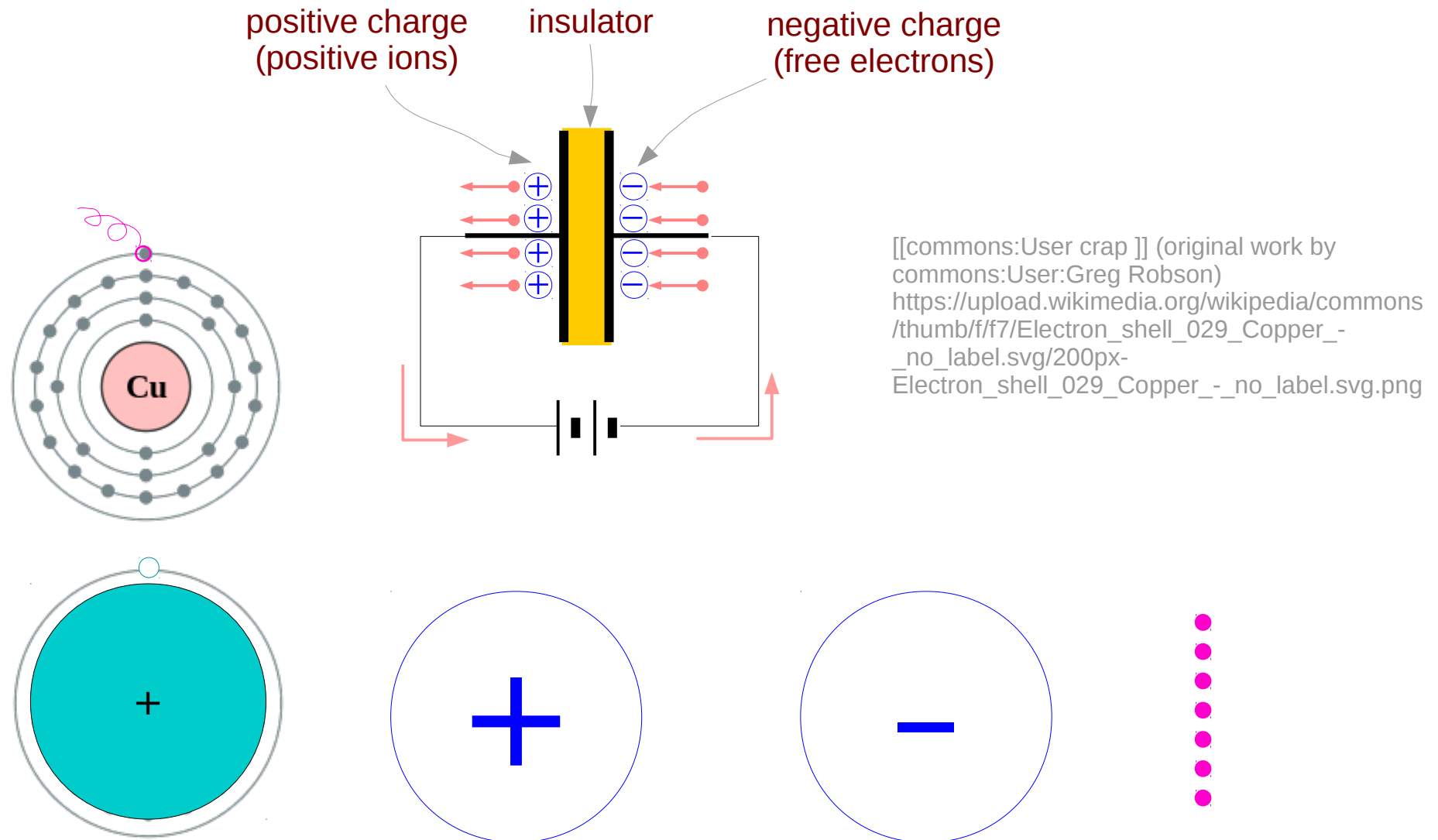

Three States



positive charge
(positive ions)

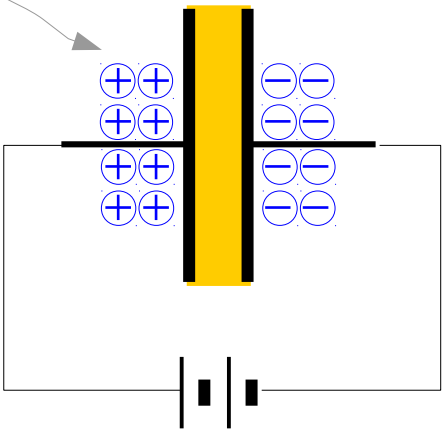Positively Charged State
fully charged → no current




negative charge
(free electrons)

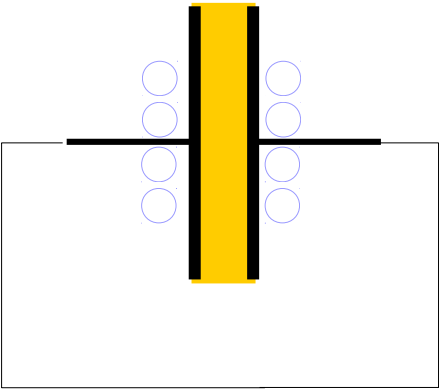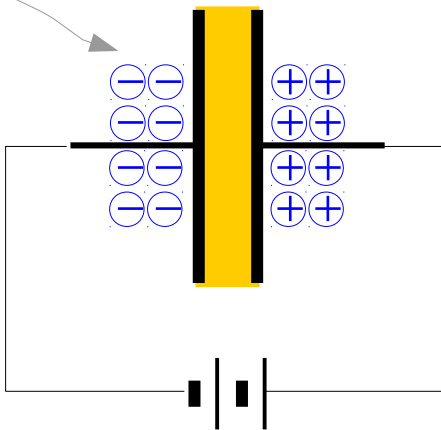Negatively Charged State
fully charged → no current



Fully Discharged State
possible large current


Currents in the Fully Discharged State

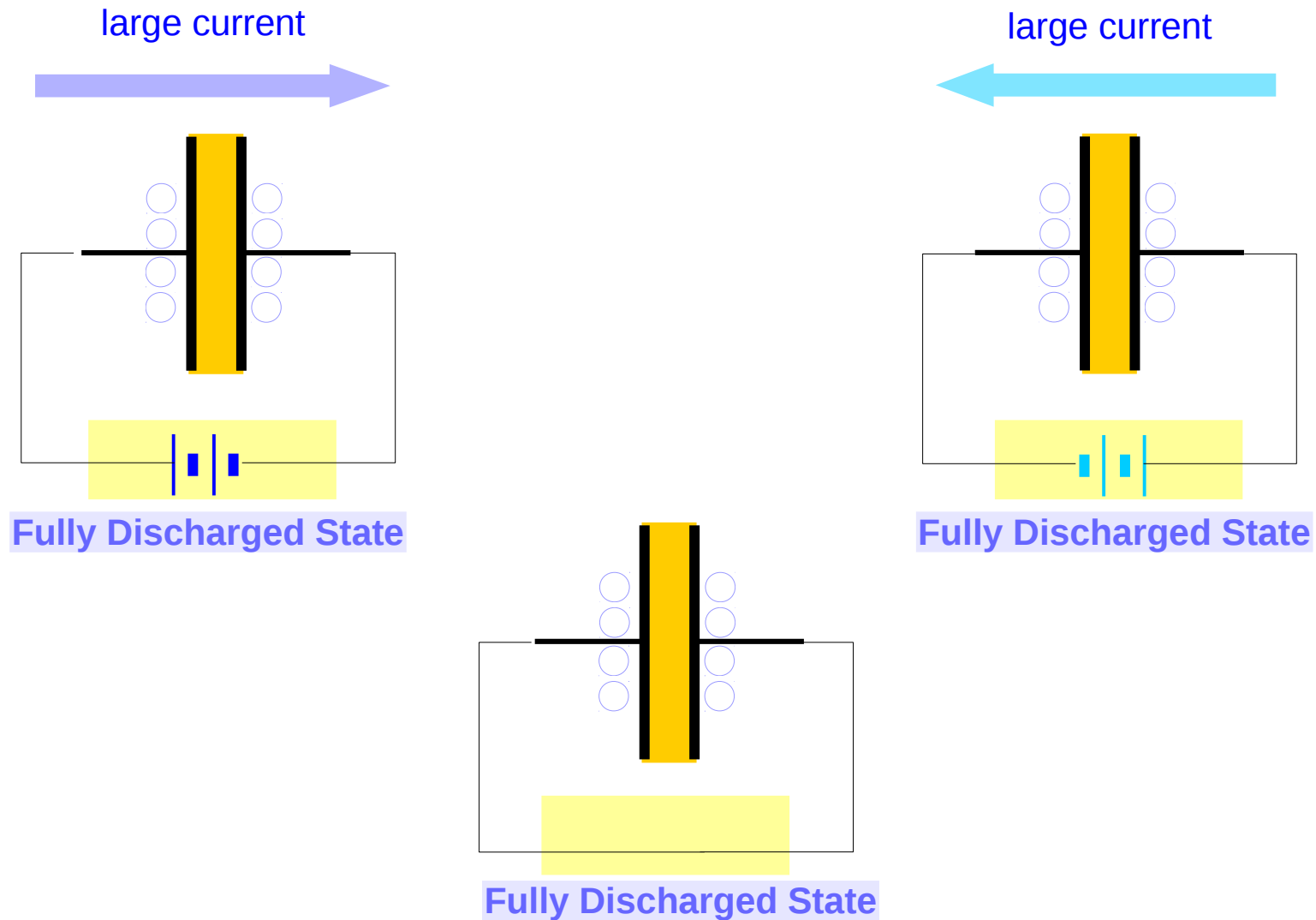

Inter-State Current Flowing

Under Positively Charging



(+) current flow direction

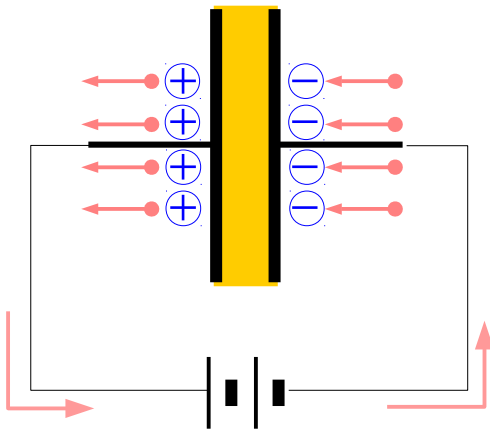

electron flow direction

Under Negatively Charging

(-) current flow direction

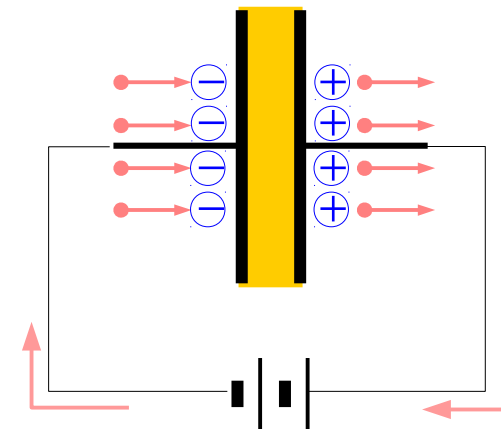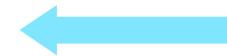


electron flow direction

Inter-State Current Flowing

Fully Discharged State

Initial large current


(+) current flow direction

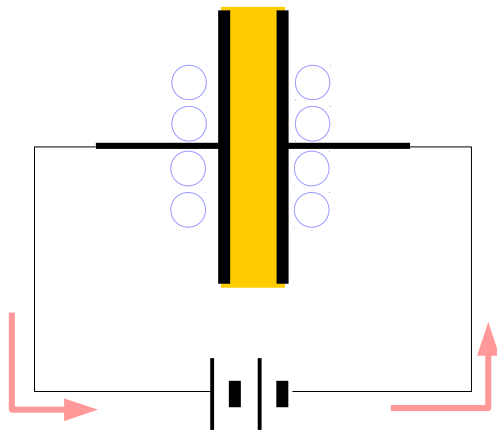

electron flow direction

Under Positively Charging


(+) current flow direction

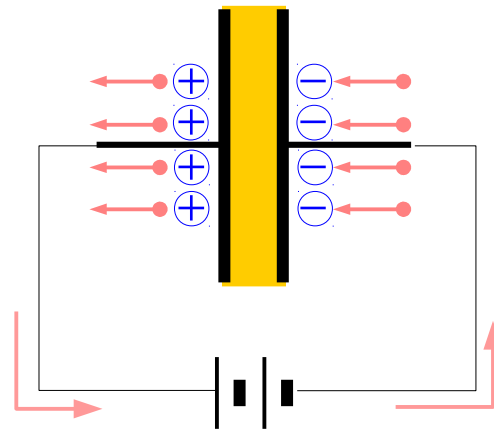

electron flow direction

Positively Charged State

no current

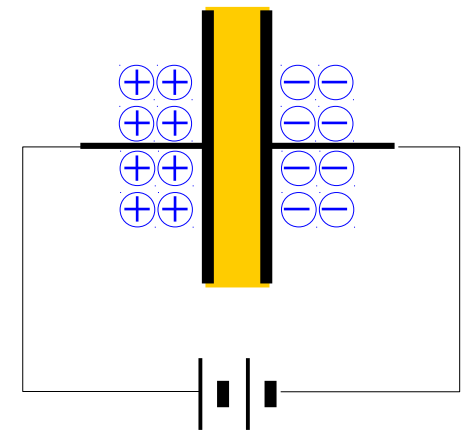


Crowded →
No more space

Inter-State Current Flowing

Fully Discharged State

Initial large current


(-) current flow direction

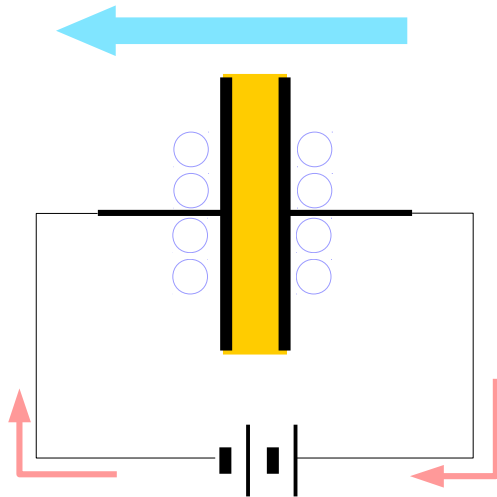

electron flow direction

Under Negatively Charging


(-) current flow direction

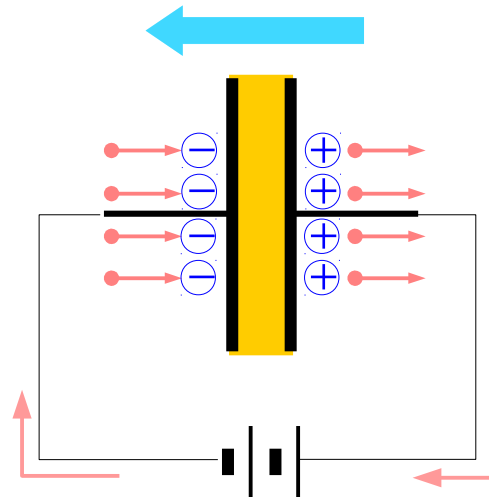

electron flow direction



Negatively Charged State

no current


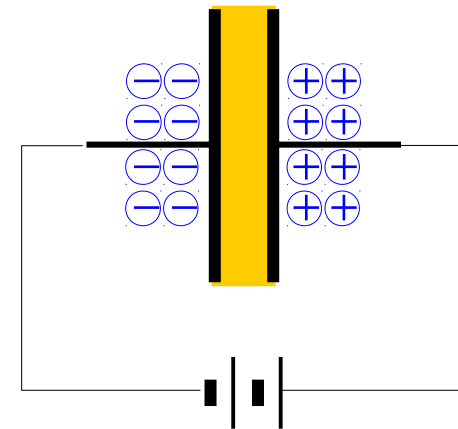


Crowded →
No more space


An AC Voltage Source

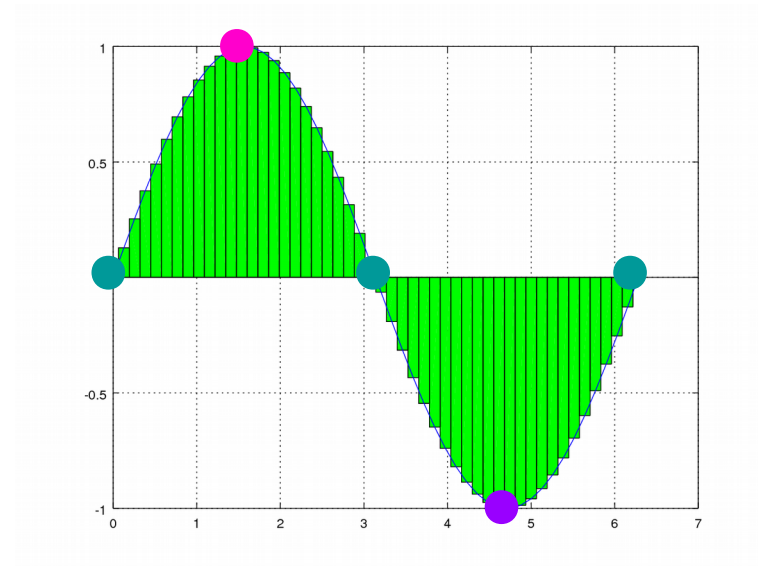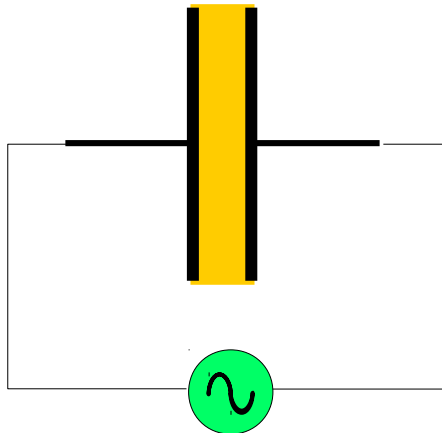

An AC Voltage Source

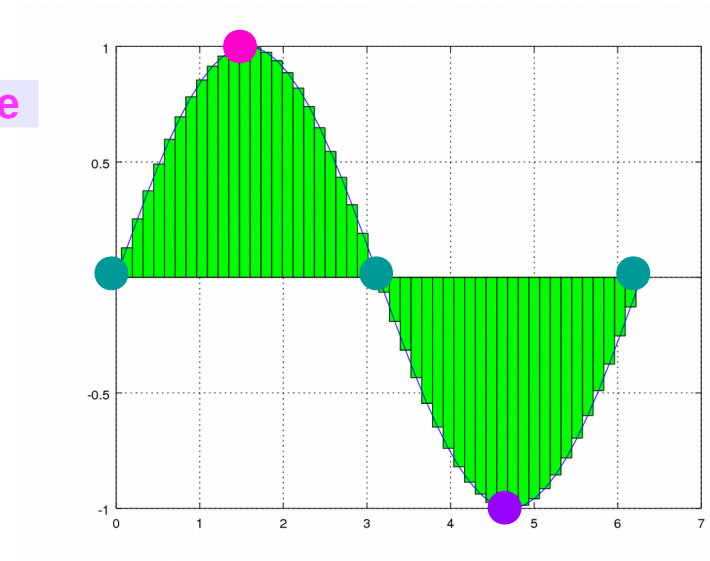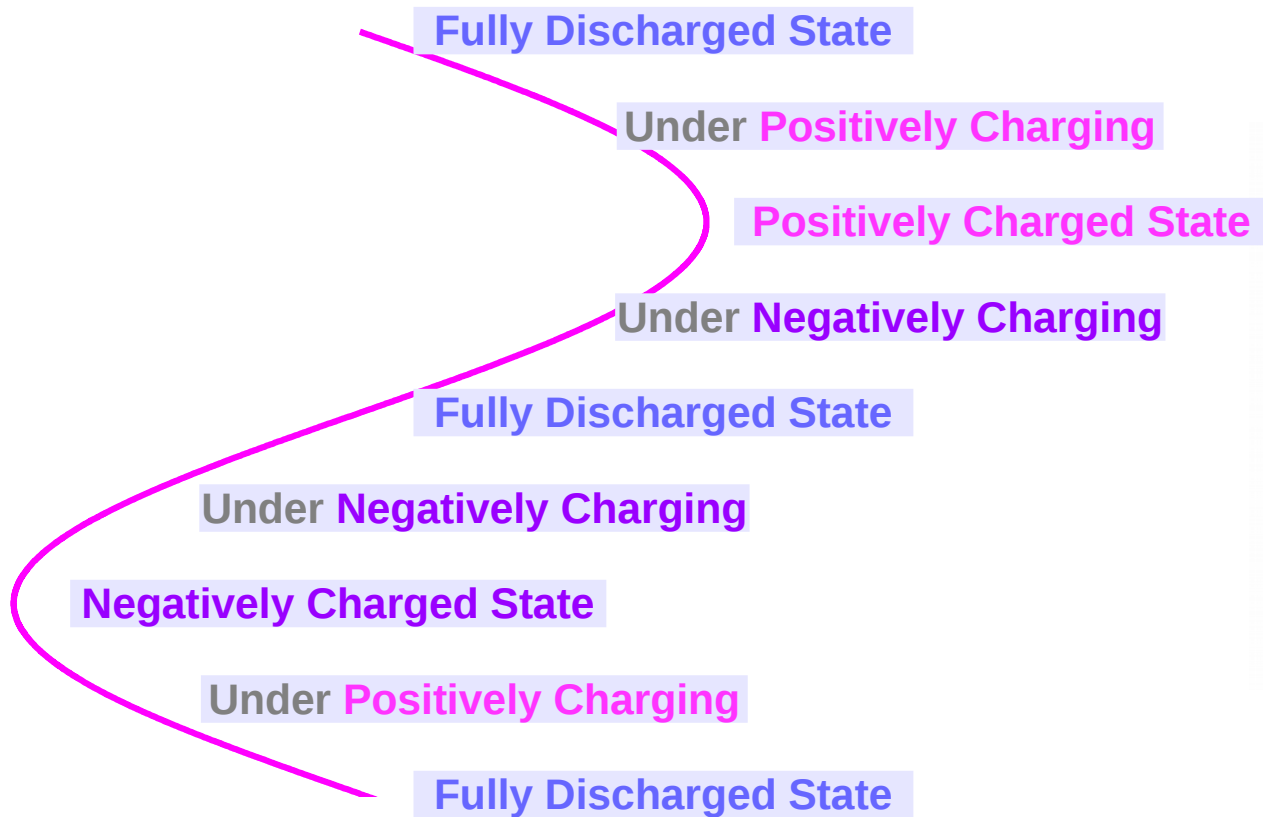


Fully Charged and Fully Discharged


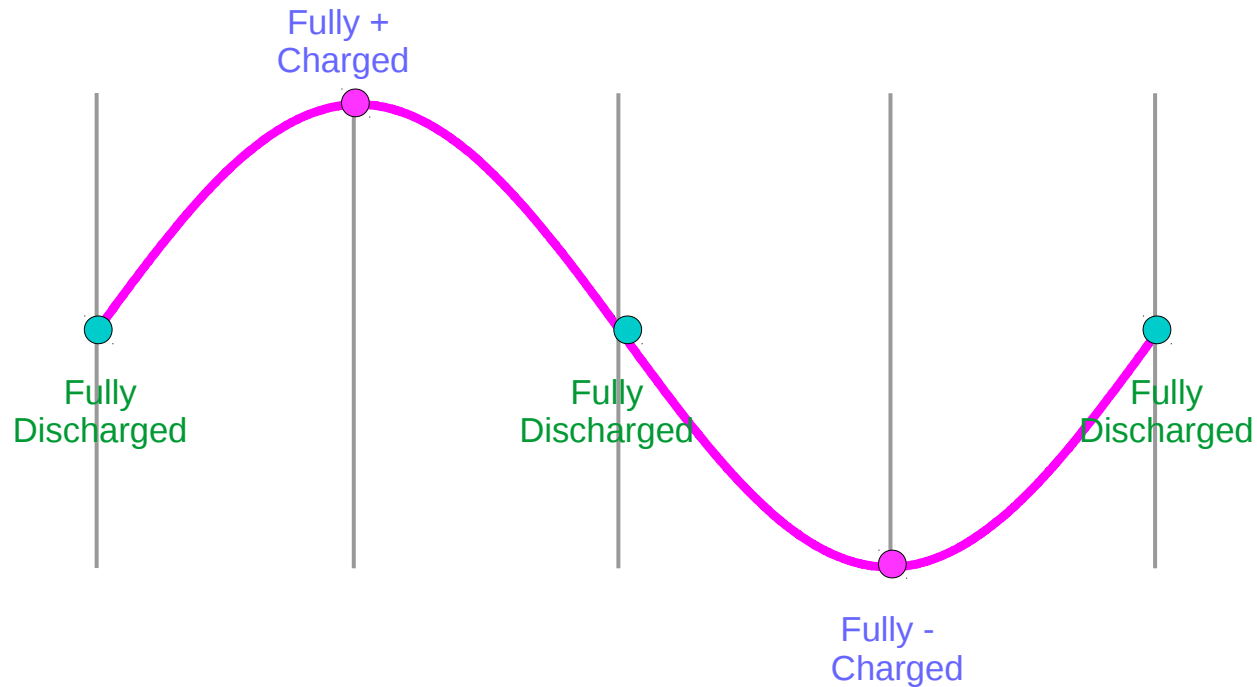


	(+) Charging	(-) Charging	(-) Charging	(+) Charging
(+) current	(+) current	(-) current	(-) current	(+) current
	(+) Charging	(+) Discharging	(-) Charging	(-) Discharging



A Cycle

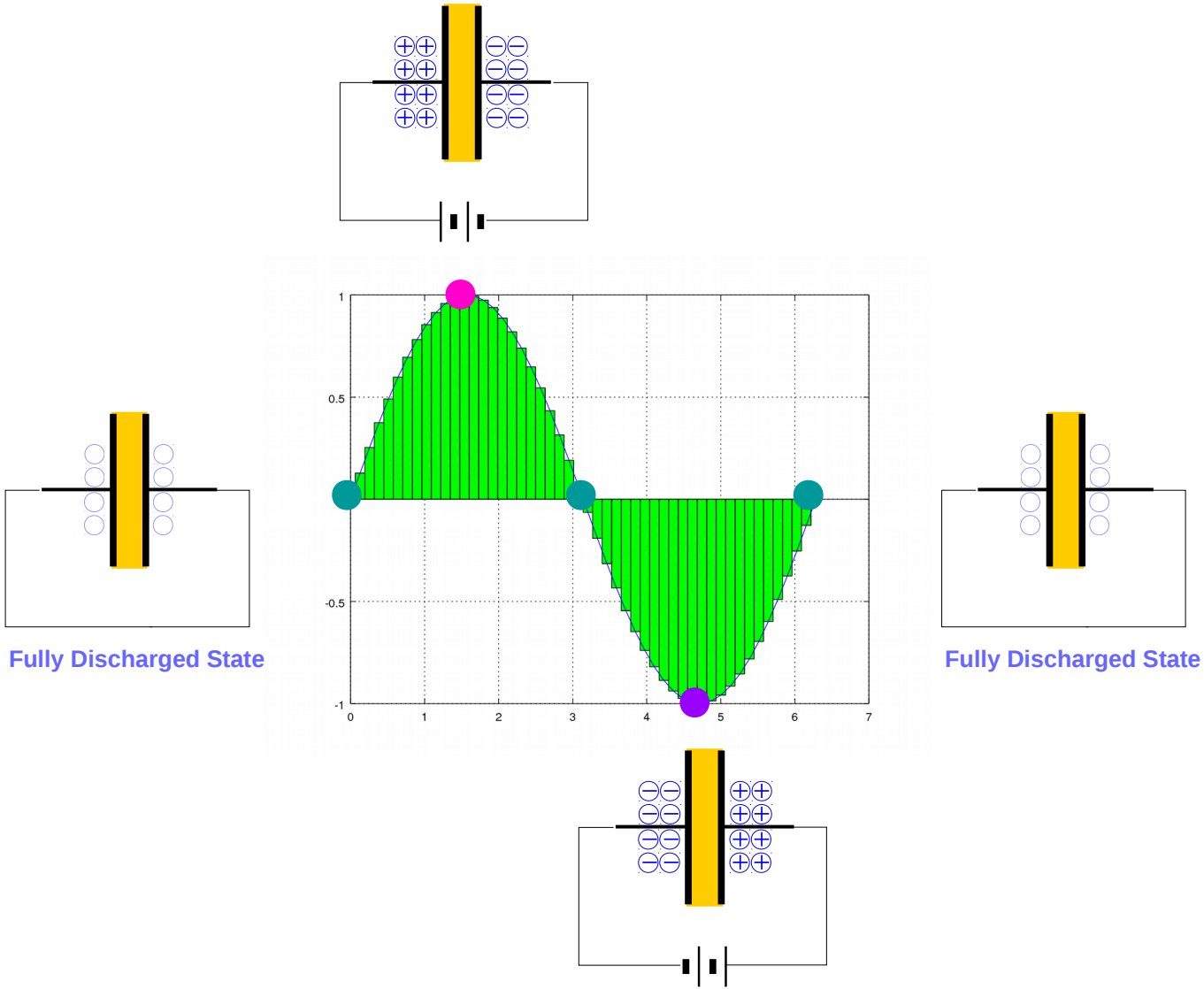


State Transition Diagram

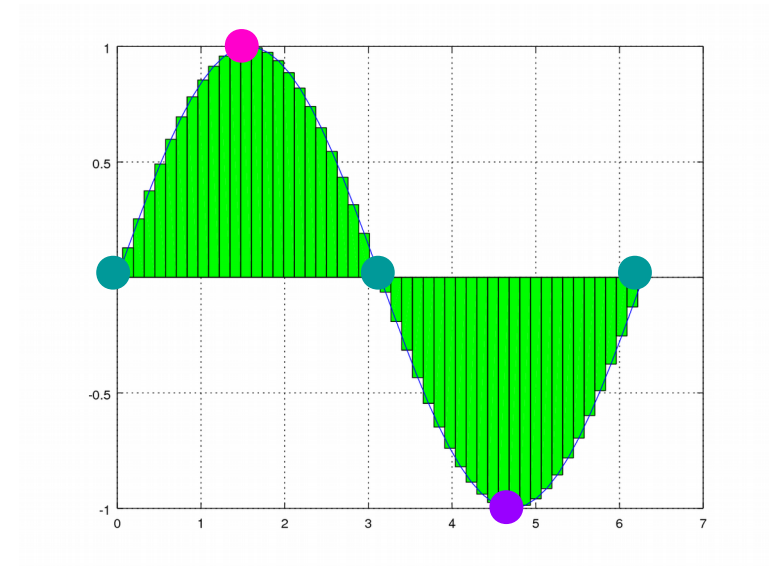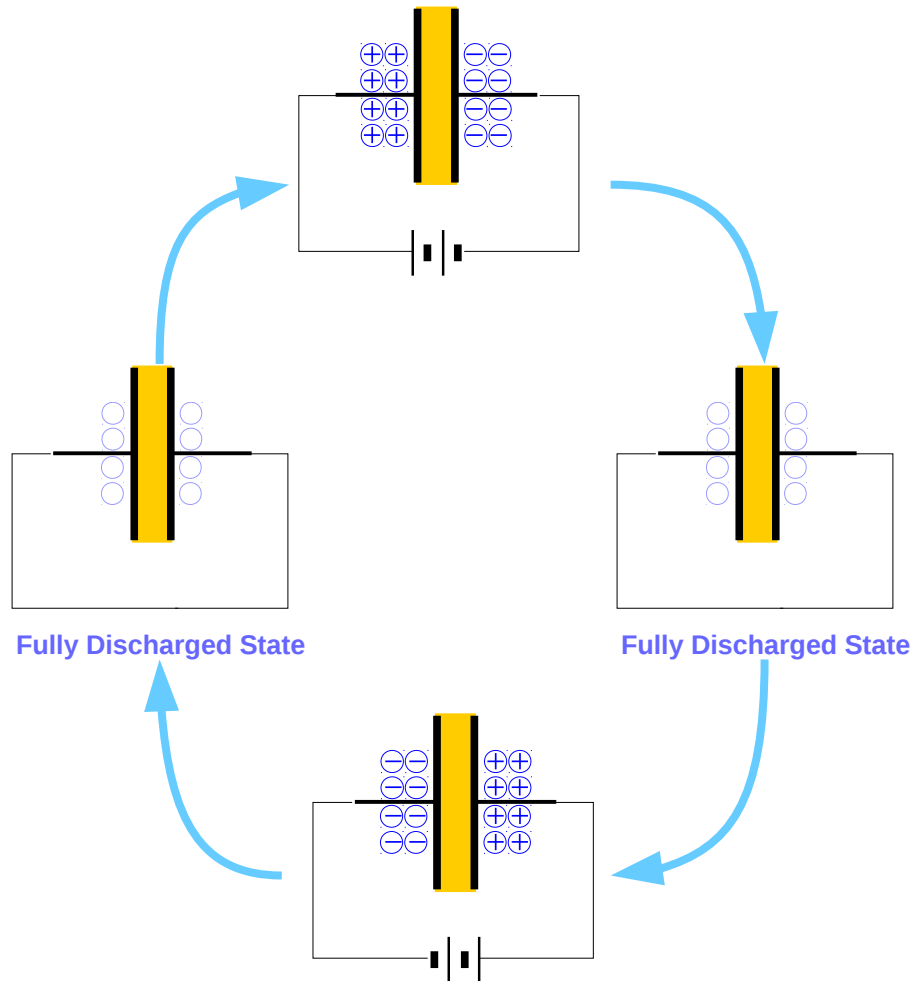

Current Flow

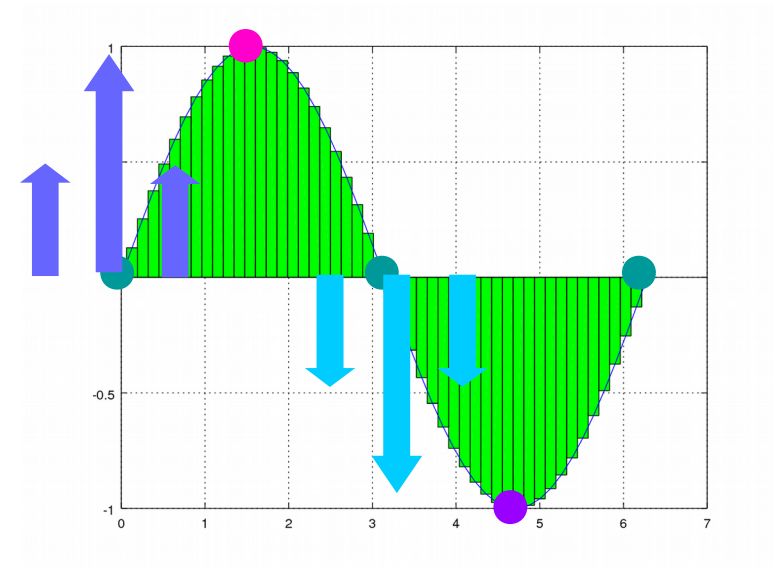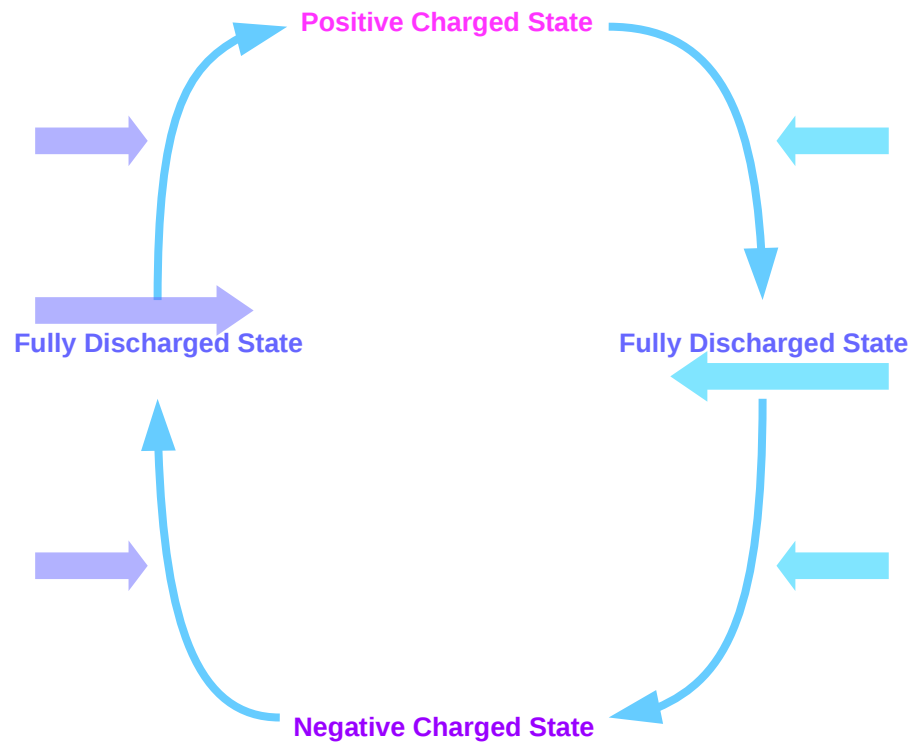

Fully Charged and Fully Discharged

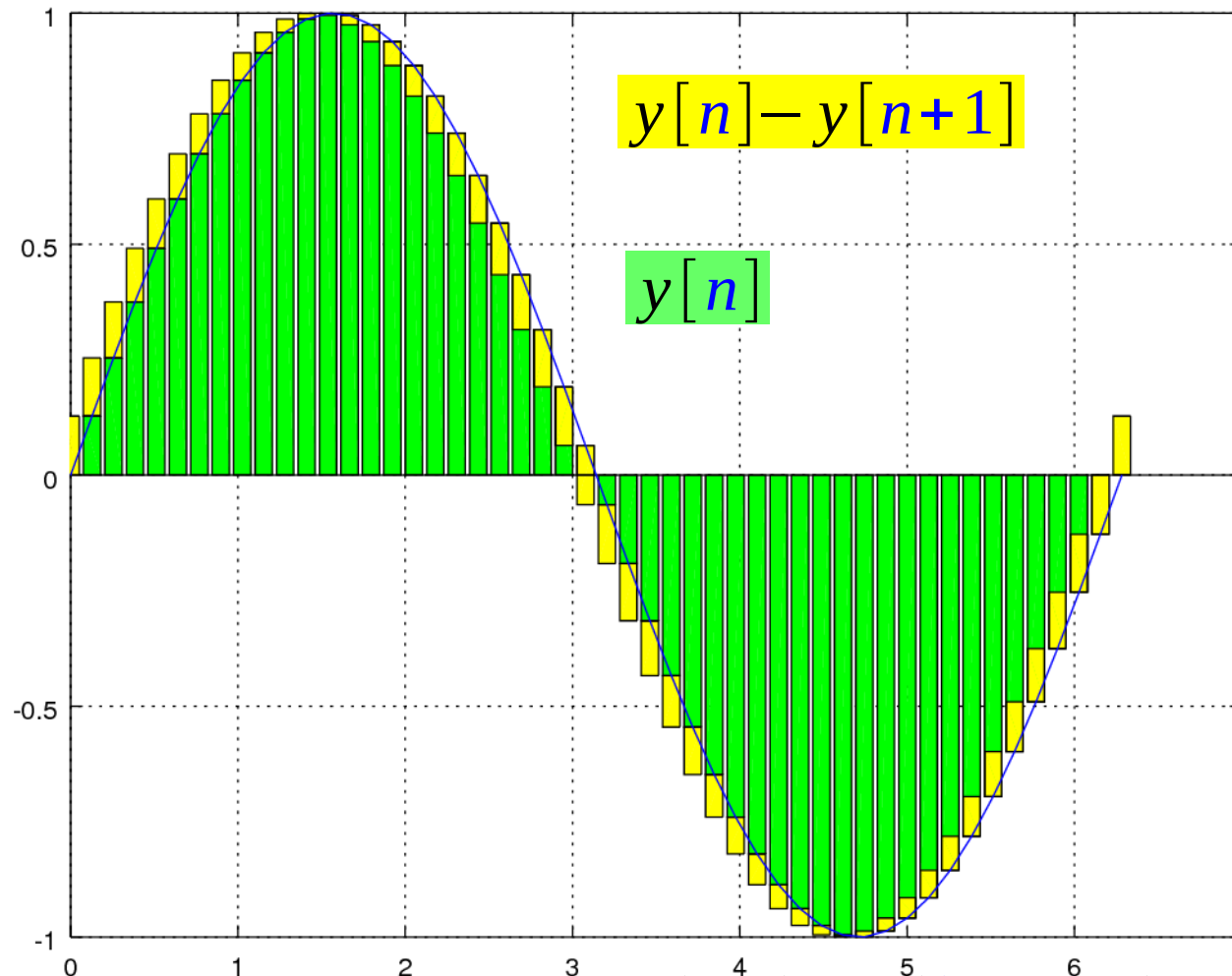


```
h = bar(t1, [y1' y2'],  
"stacked")  
set(h(1), "facecolor", "g");  
set(h(2), "facecolor", "y");  
hold on  
plot(t1, y1)  
axis([0 7 -1 1]);
```

$$y[n] - y[n+1] = y(nT) - y((n+1)T) = \sin(nT) - \sin((n+1)T)$$

Continuous Charging and Discharging Operations


Incremental Voltage Increment \rightarrow + Charging incrementally

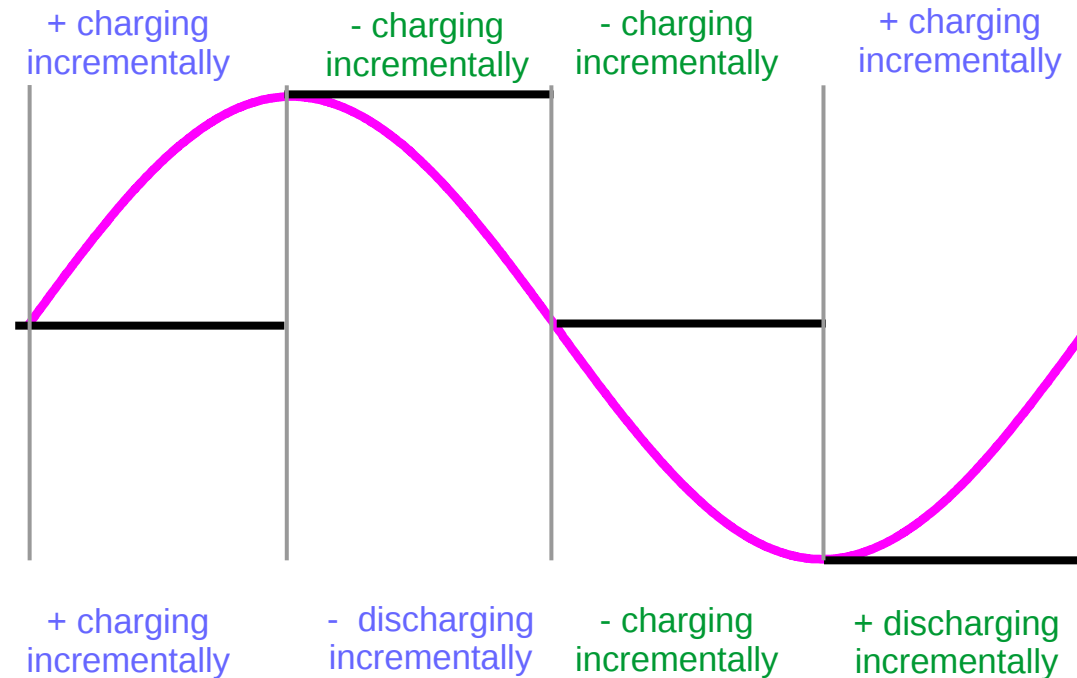Incremental Voltage Decrement \rightarrow - Charging incrementally




Fully Discharged : Large Current

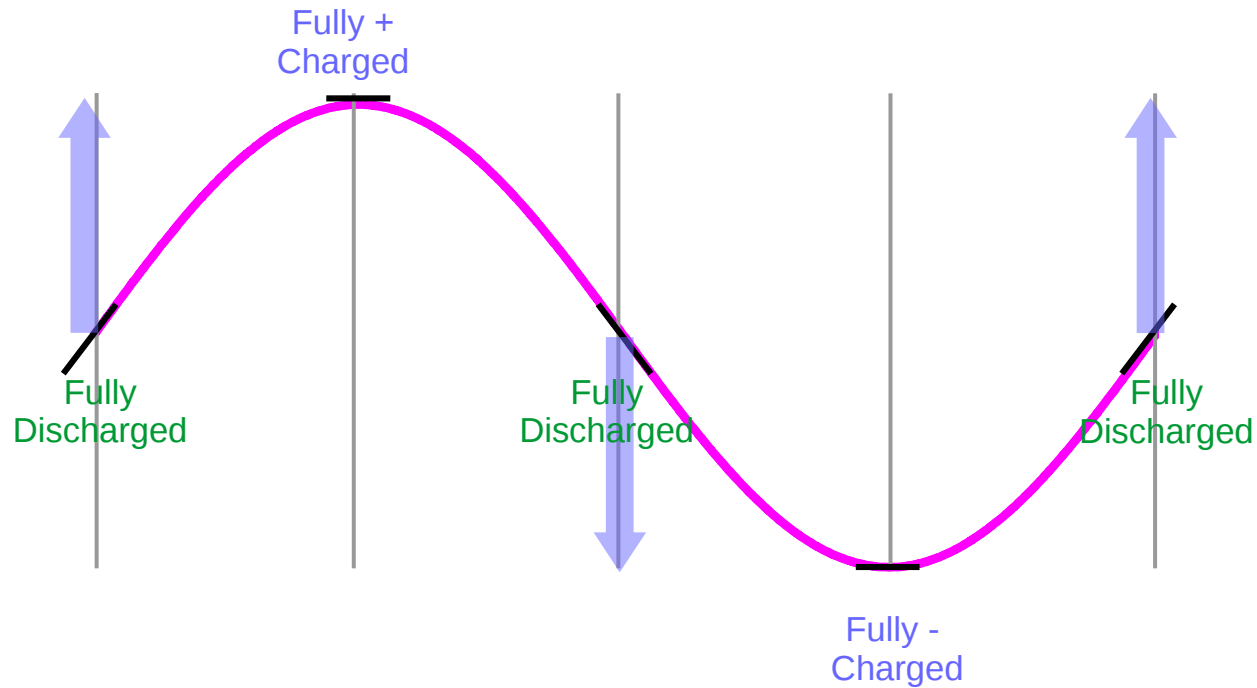Incremental Voltage Increment → Continuous Charging
Incremental Voltage Decrement → Continuous Discharging




$y[n+1] - y[n]$

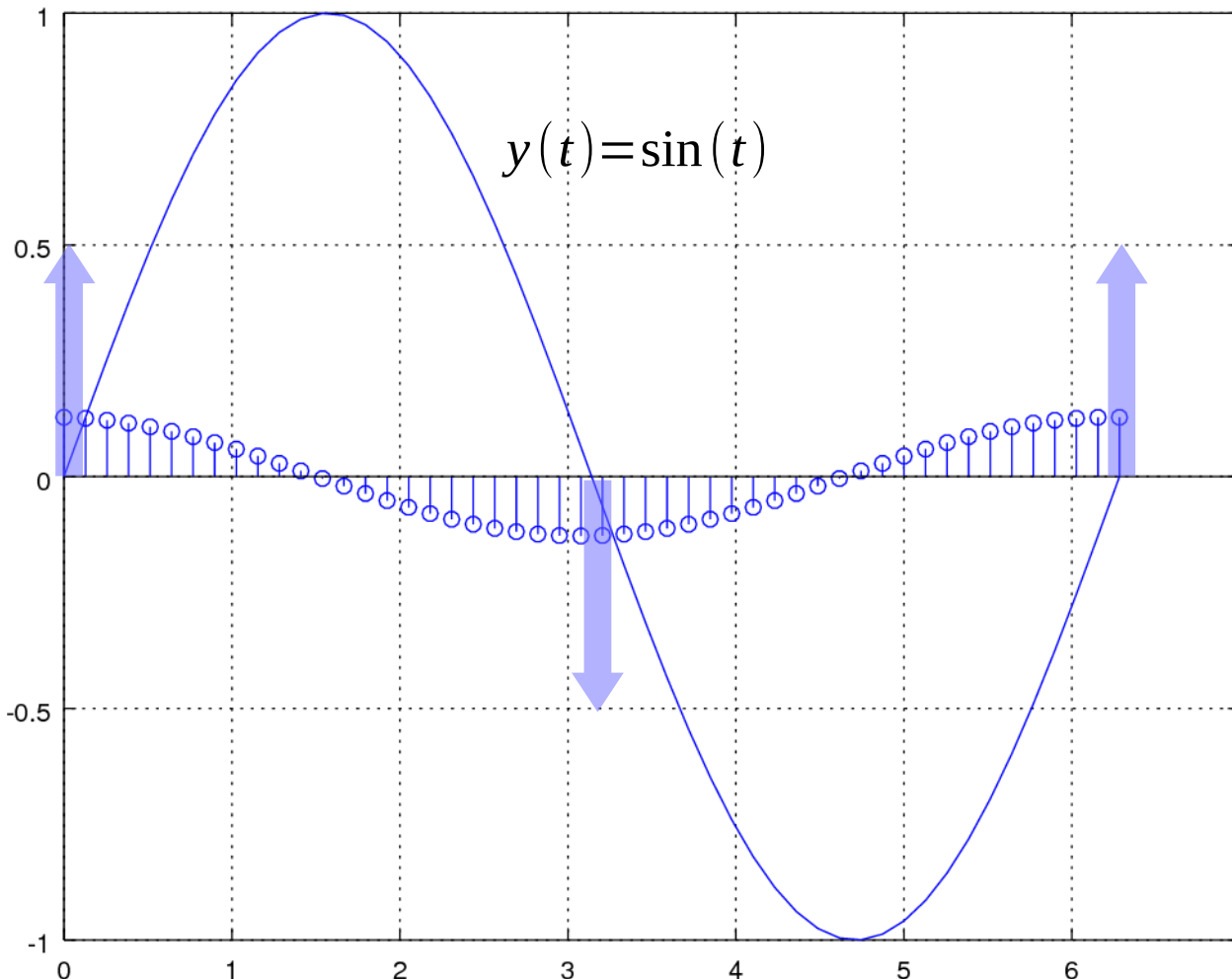

```
t = linspace(0, pi*2, 50);  
t1 = t;  
t2 = t + t(2);  
y1 = sin(t1);  
y2 = sin(t2) - sin(t1);  
stem(t1, y2)  
hold on  
plot(t1, y1)
```

$$y[n] - y[n+1] = y(nT) - y((n+1)T) = \sin(nT) - \sin((n+1)T)$$


Fully Charged and Fully Discharged

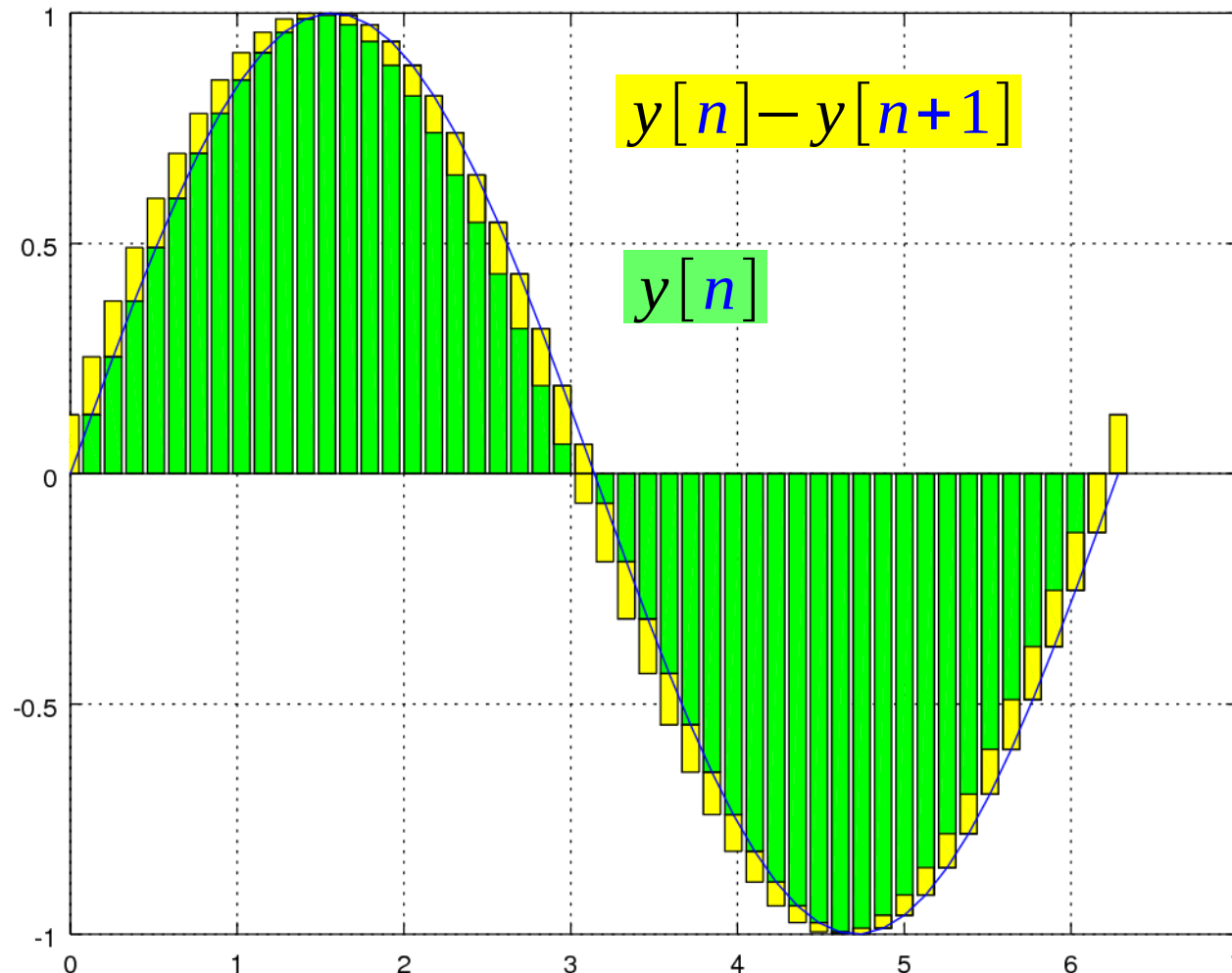

```
h = bar(t1, [y1' y2'],  
"stacked")  
set(h(1), "facecolor", "g");  
set(h(2), "facecolor", "y");  
hold on  
plot(t1, y1)  
axis([0 7 -1 1]);
```

$$y[n] - y[n+1] = y(nT) - y((n+1)T) = \sin(nT) - \sin((n+1)T)$$

Fully Charged and Fully Discharged

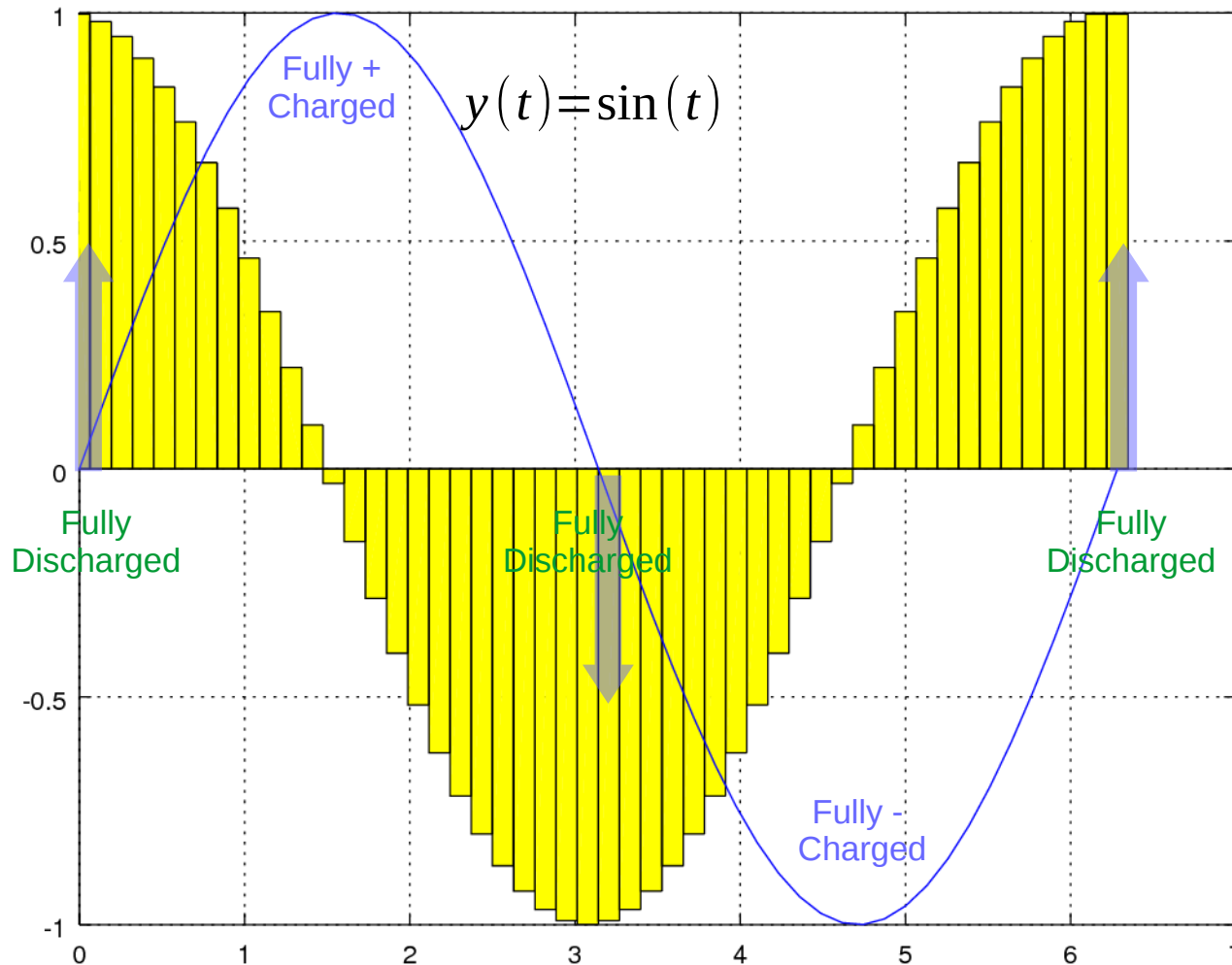


```
h = bar(t1, y2/t(2), "hist")
set(h(1), "facecolor", "y");
hold on
plot(t1, y1)
axis([0 7 -1 1]);
```

$$\frac{y[n] - y[n+1]}{T}$$

$$\propto \frac{dy}{dt}$$

Fully Charged and Fully Discharged

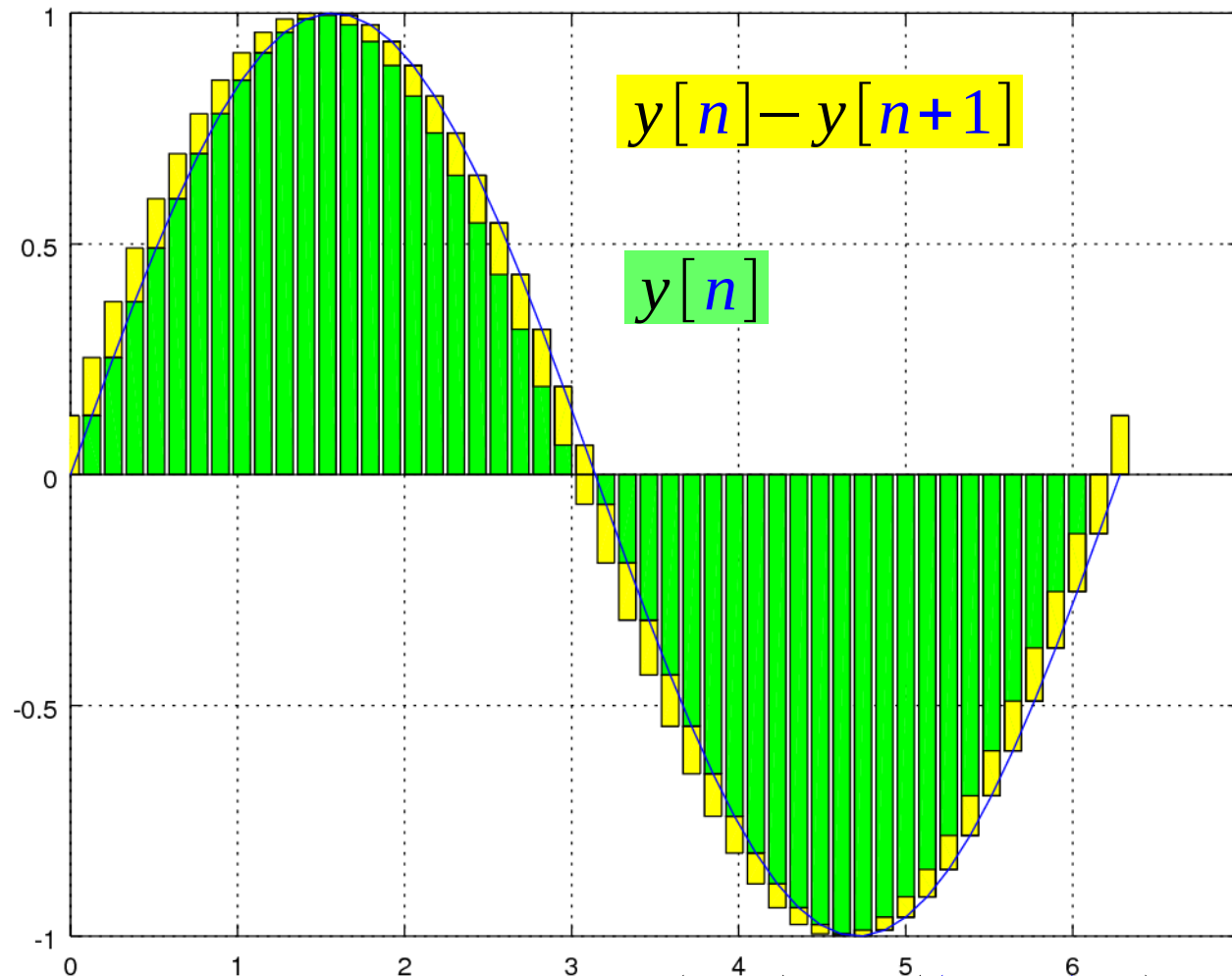


```


h = bar(t1, [y1' y2'],
"stacked")
set(h(1), "facecolor", "g");
set(h(2), "facecolor", "y");
hold on
plot(t1, y1)
axis([0 pi]);
    
```

$$y[n] - y[n+1] = y(nT) - y((n+1)T) = \sin(nT) - \sin((n+1)T)$$

Everchanging signal pairs

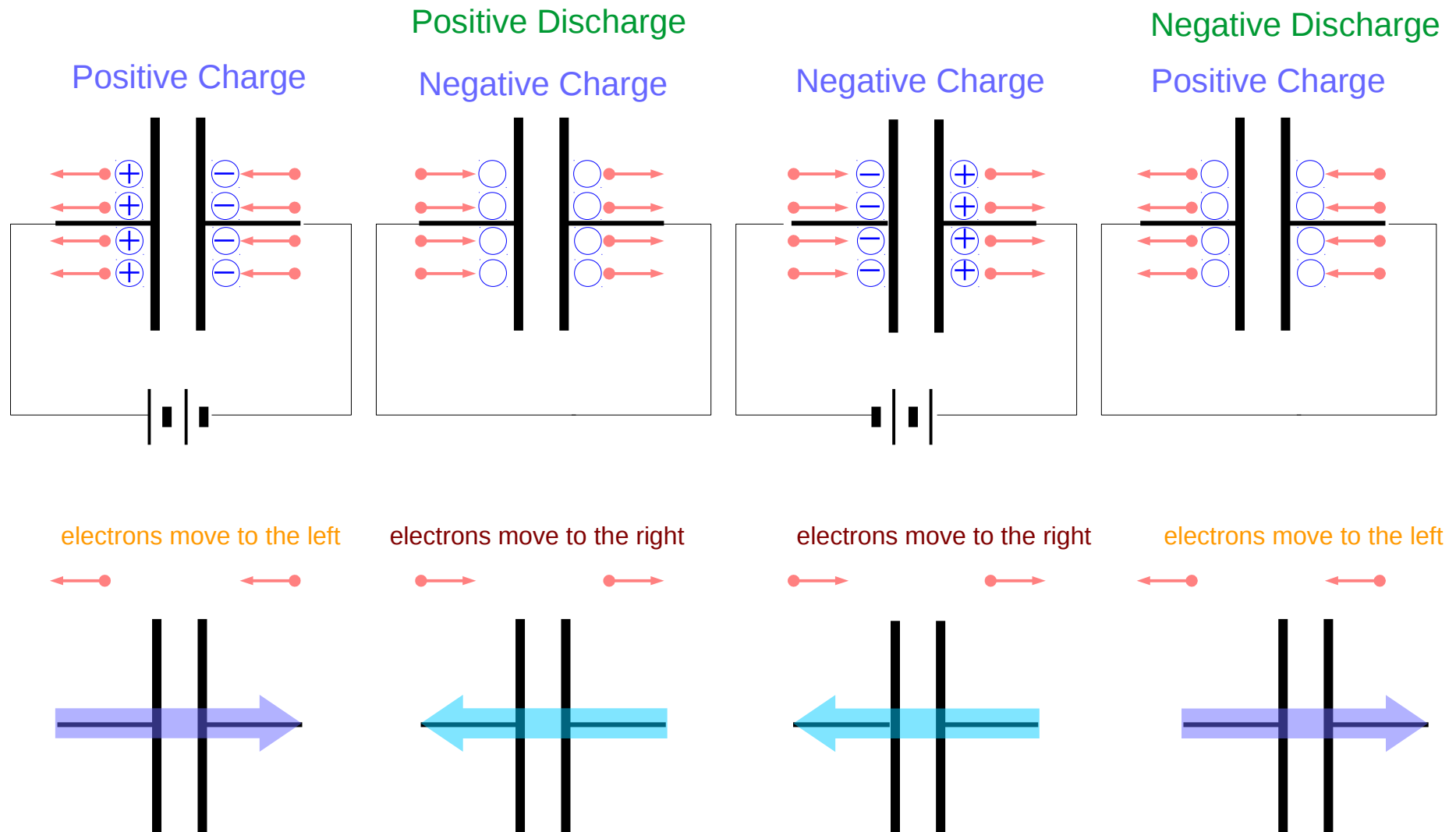


Everchanging signal pairs

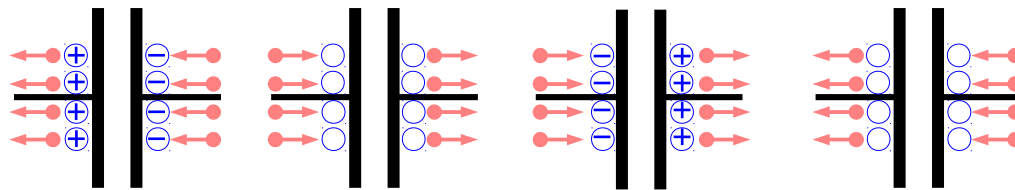


charge

discharge

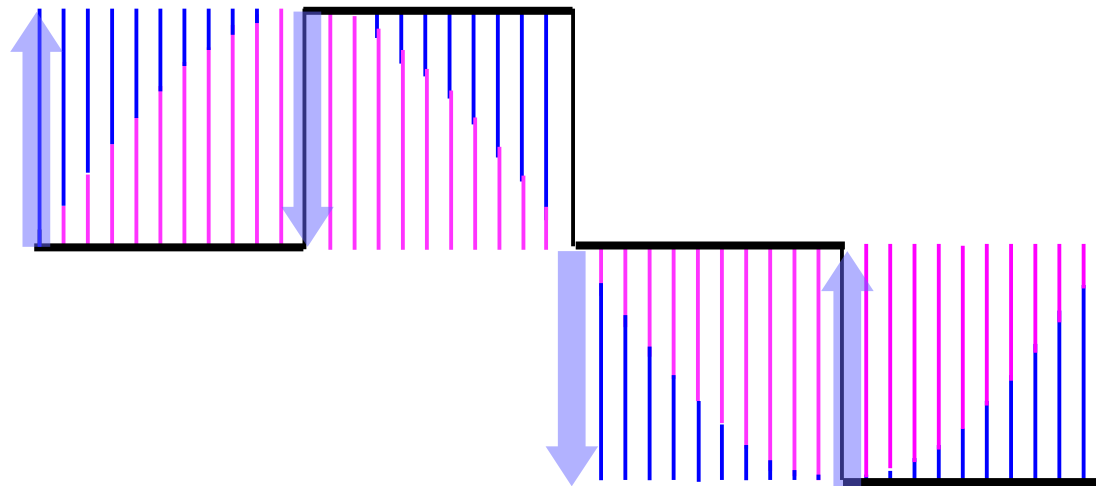


charge

discharge

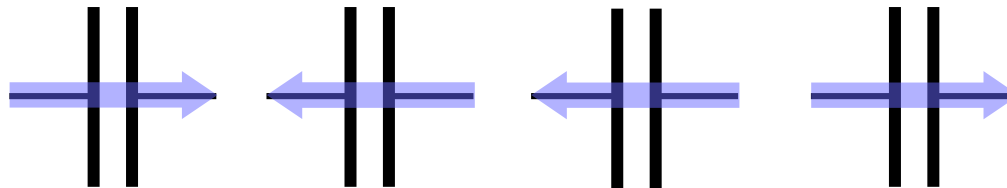


Everchanging signal pairs

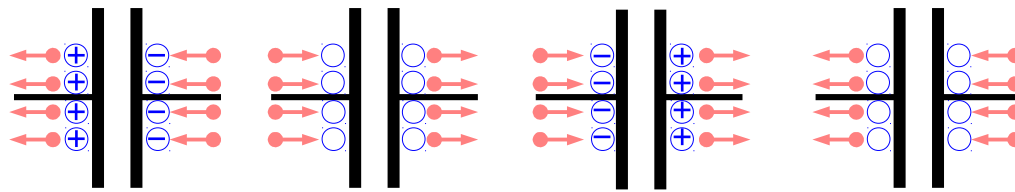


charge

discharge

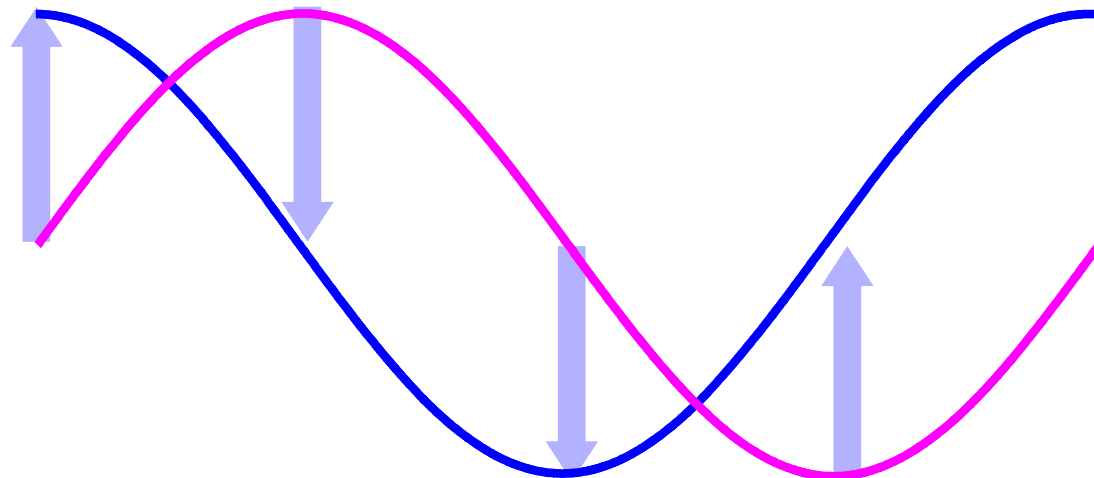


charge


discharge

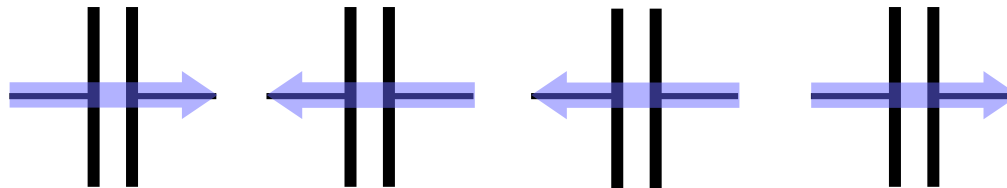

Everchanging signal pairs

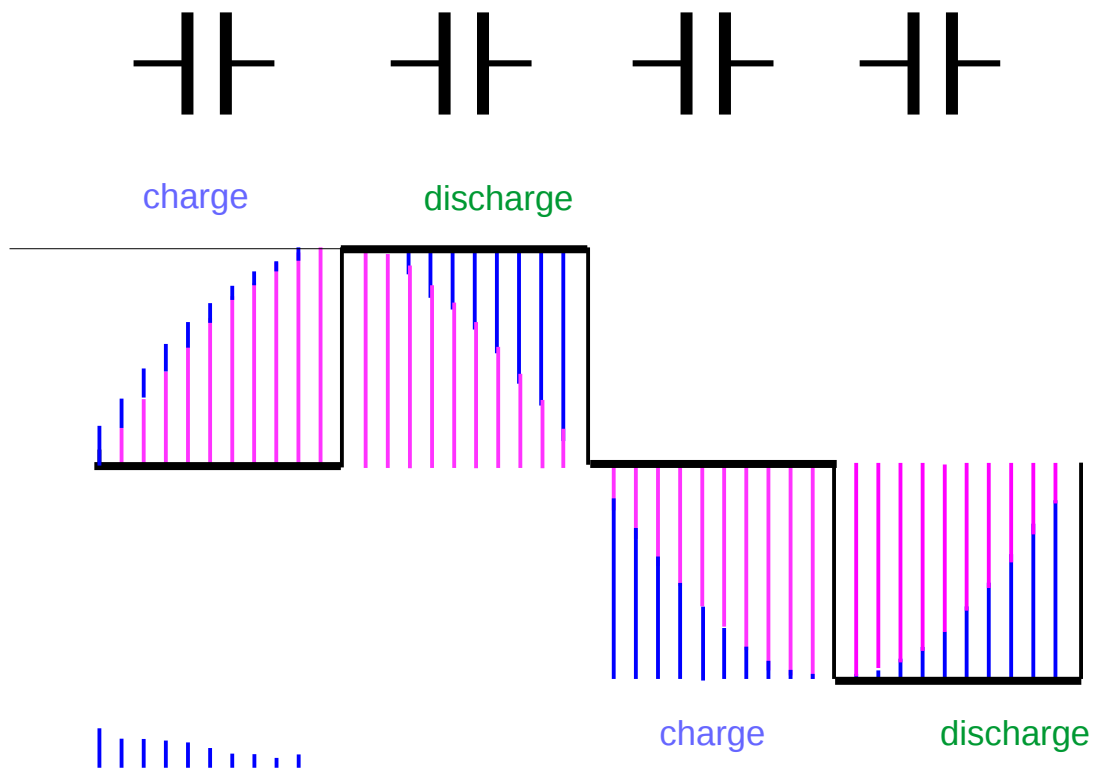


Everchanging signal pairs

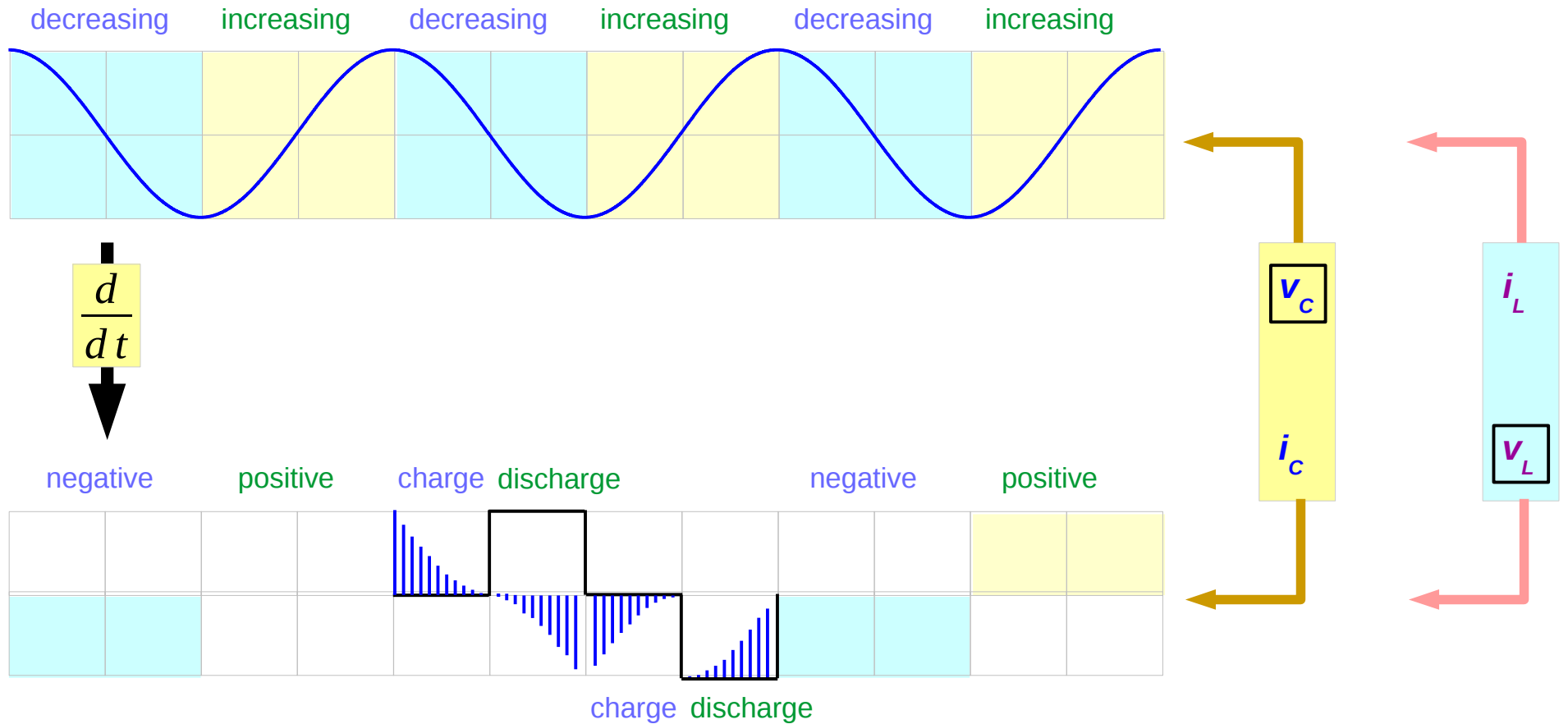

I leads V by 90°

Initial charge

 


SHORT

V = 0

I : peak


Full charge

 

OPEN

I = 0

V : peak

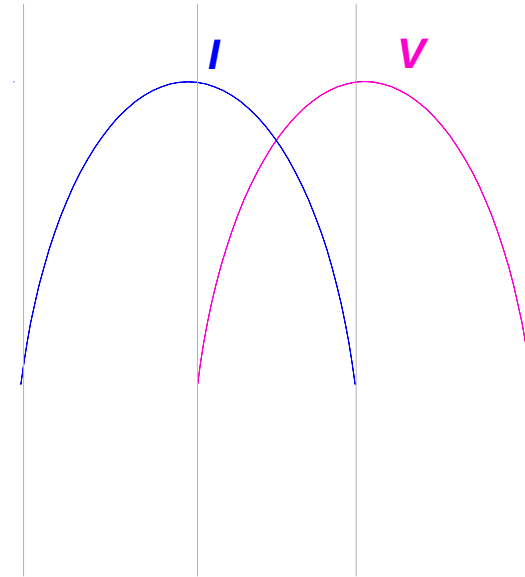

References

[1] <http://en.wikipedia.org/>

[2] J.H. McClellan, et al., Signal Processing First, Pearson Prentice Hall, 2003