

Carry Skip Adder (5A)

-
-

Copyright (c) 2021 – 2013 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".


https://en.wikipedia.org/wiki/AND_gate
https://en.wikipedia.org/wiki/OR_gate
https://en.wikipedia.org/wiki/XOR_gate
https://en.wikipedia.org/wiki/NAND_gate

Please send corrections (or suggestions) to youngwlim@hotmail.com.


This document was produced by using OpenOffice and Octave.

Propagated and Generated Carries


propagated carry

 


propagated carry

 


killed carry

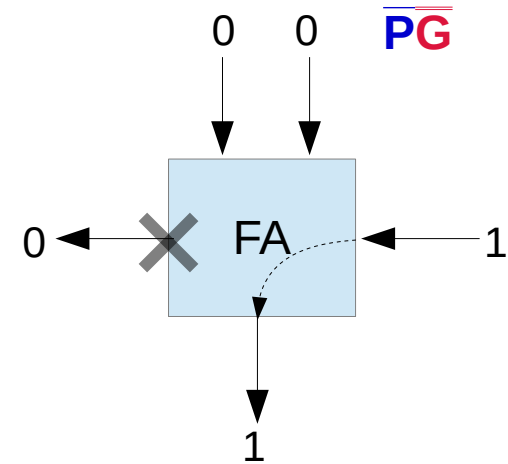


generated carry

 


generated carry

 

killed carry

 


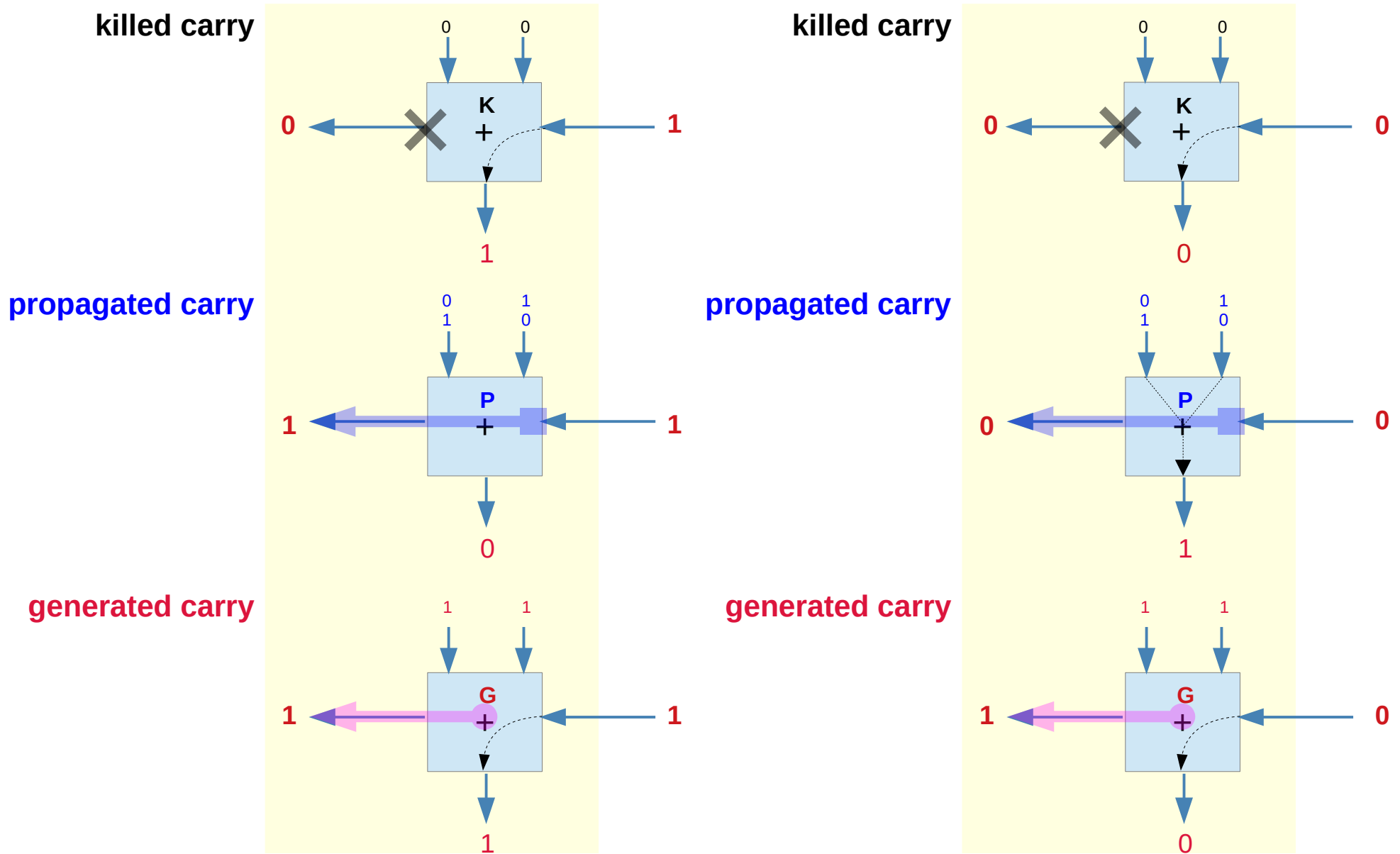Carry Kill, Propagate, Generate conditions (2)



Carry Kill, Propagate, Generate conditions (1)

X	Y		
0	0	K	Kill ($=\bar{P}\bar{G}$)
0	1	P	Propagate
1	0	P	Propagate
1	1	G	Generate

 

Unless the two FA's are in **propagate** mode, the transition of **Cin** does not affect the transition of **Cout**


Critical path – all FA's in **propagate** mode

Broken paths for any FA in other mode
- kill mode, **generate** mode


<https://electronics.stackexchange.com/questions/21251/critical-path-for-carry-skip-adder>

Carry Kill, Propagate, Generate conditions (3)


X	Y		
0	0	K	Kill ($=\bar{P}G$)
0	1	P	Propagate
1	0	P	Propagate
1	1	G	Generate

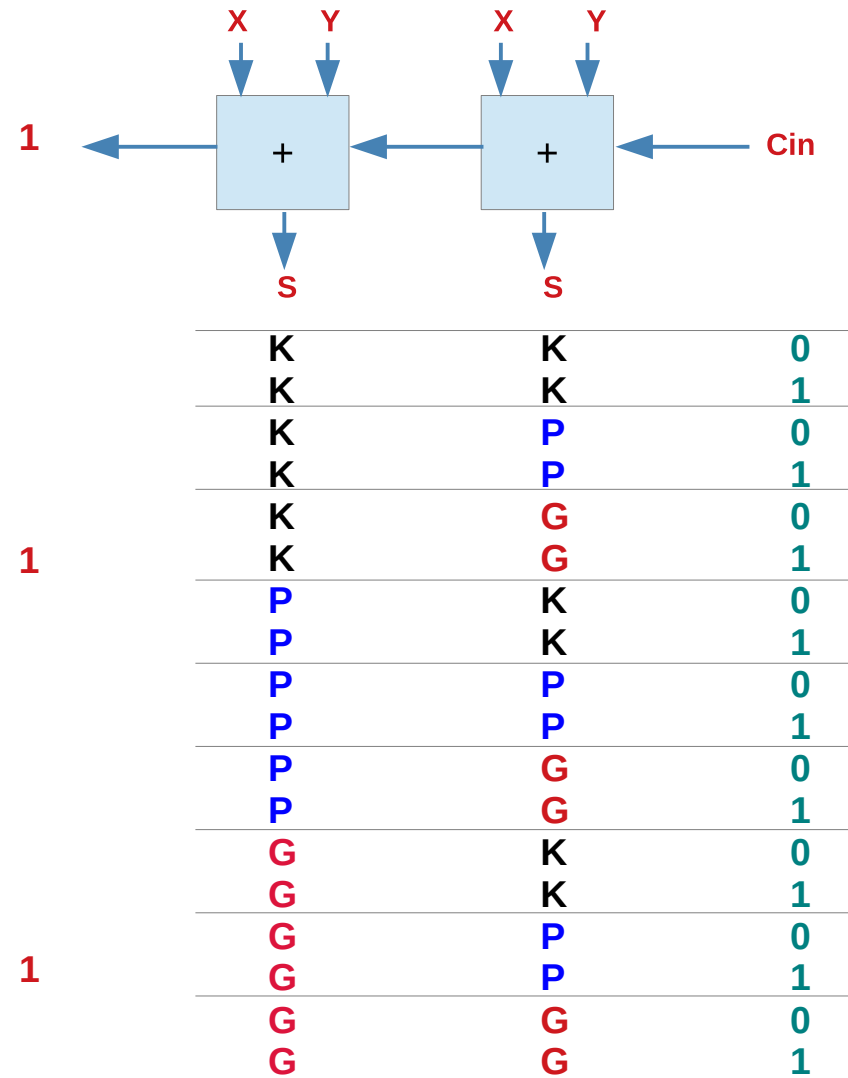

 
Carry Kill, Propagate, Generate conditions (4)



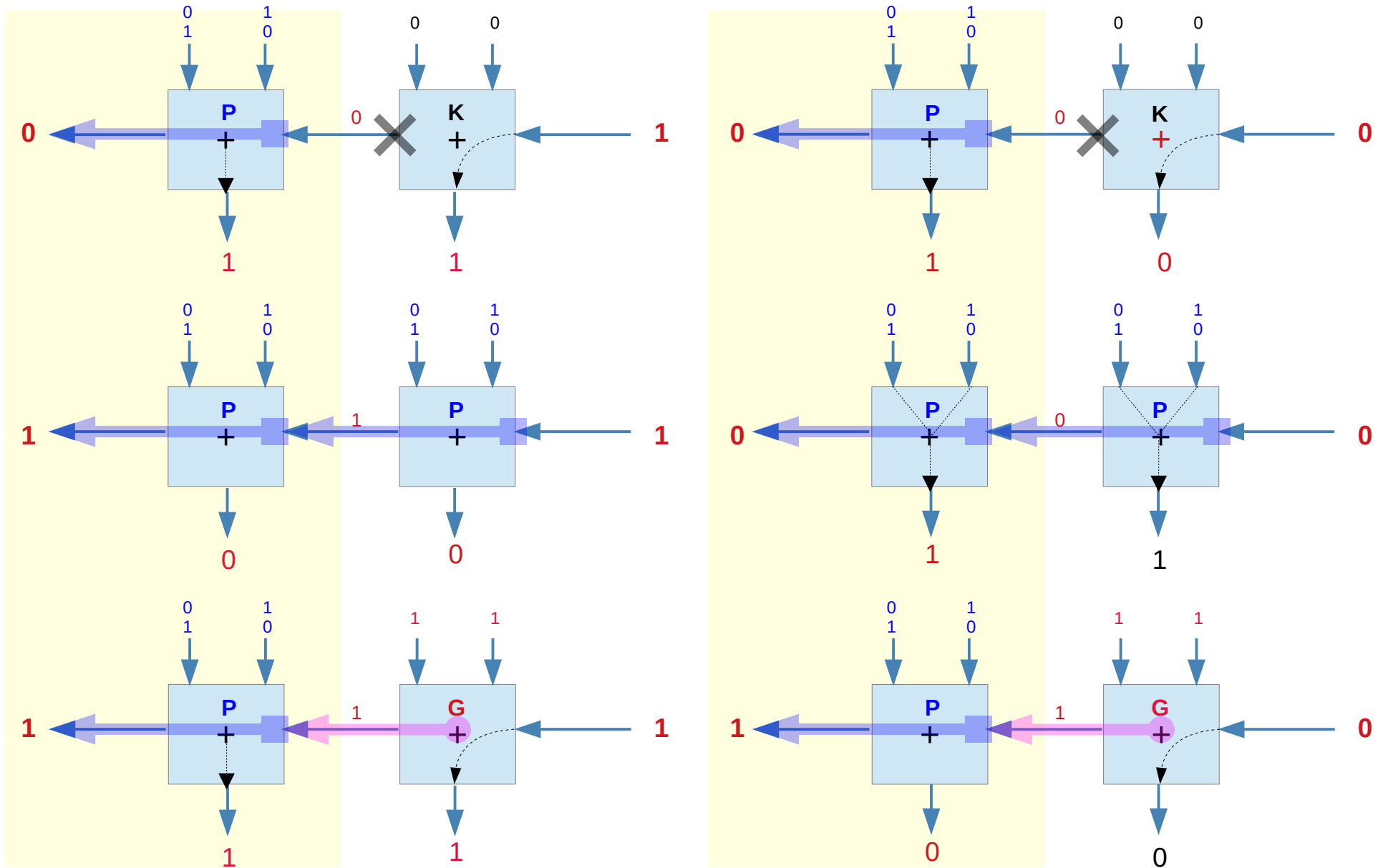
Carry Kill, Propagate, Generate conditions (5)



 Carry Kill, Propagate, Generate conditions (6)




Cases for Cout1 = 1

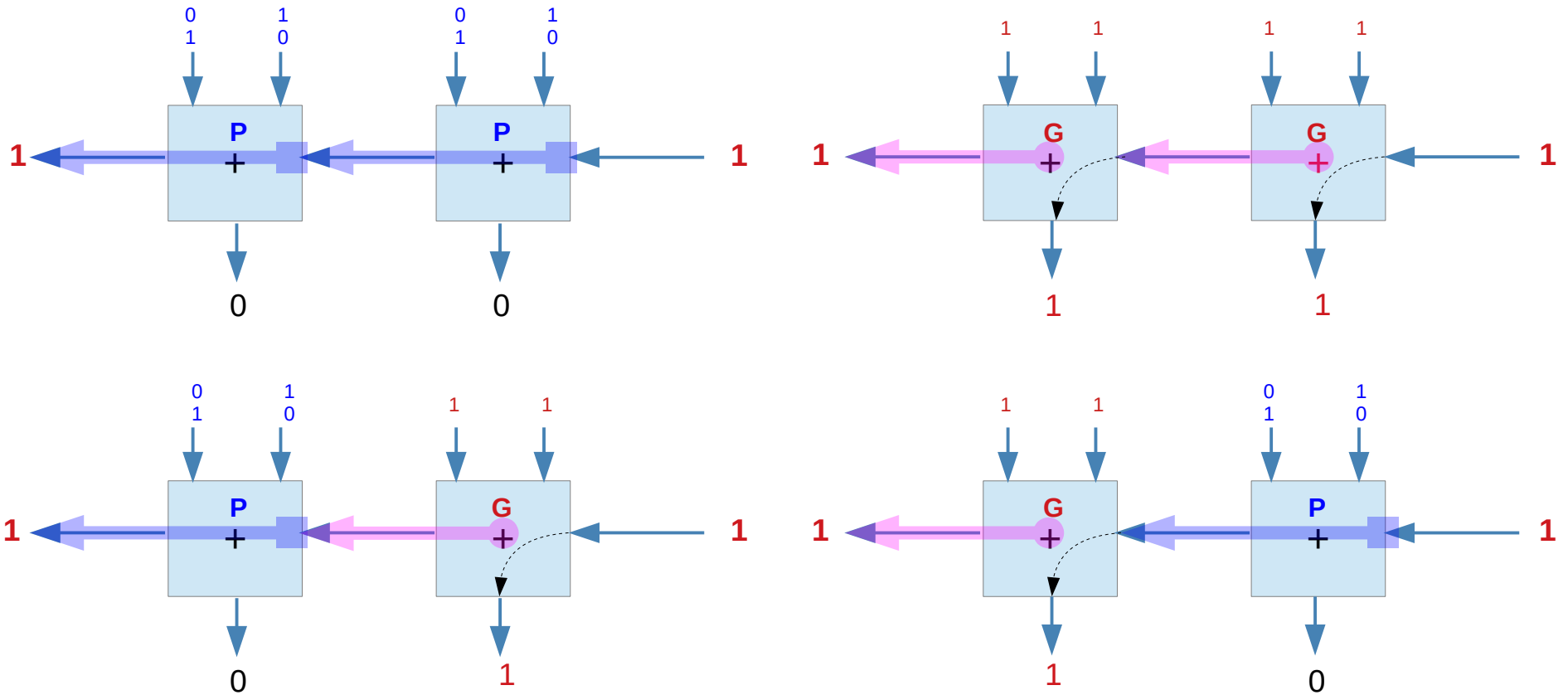

X	Y		
0	0	K	Kill ($=\overline{PG}$)
0	1	P	Propagate
1	0	P	Propagate
1	1	G	Generate

Cases for Cout1 = 0

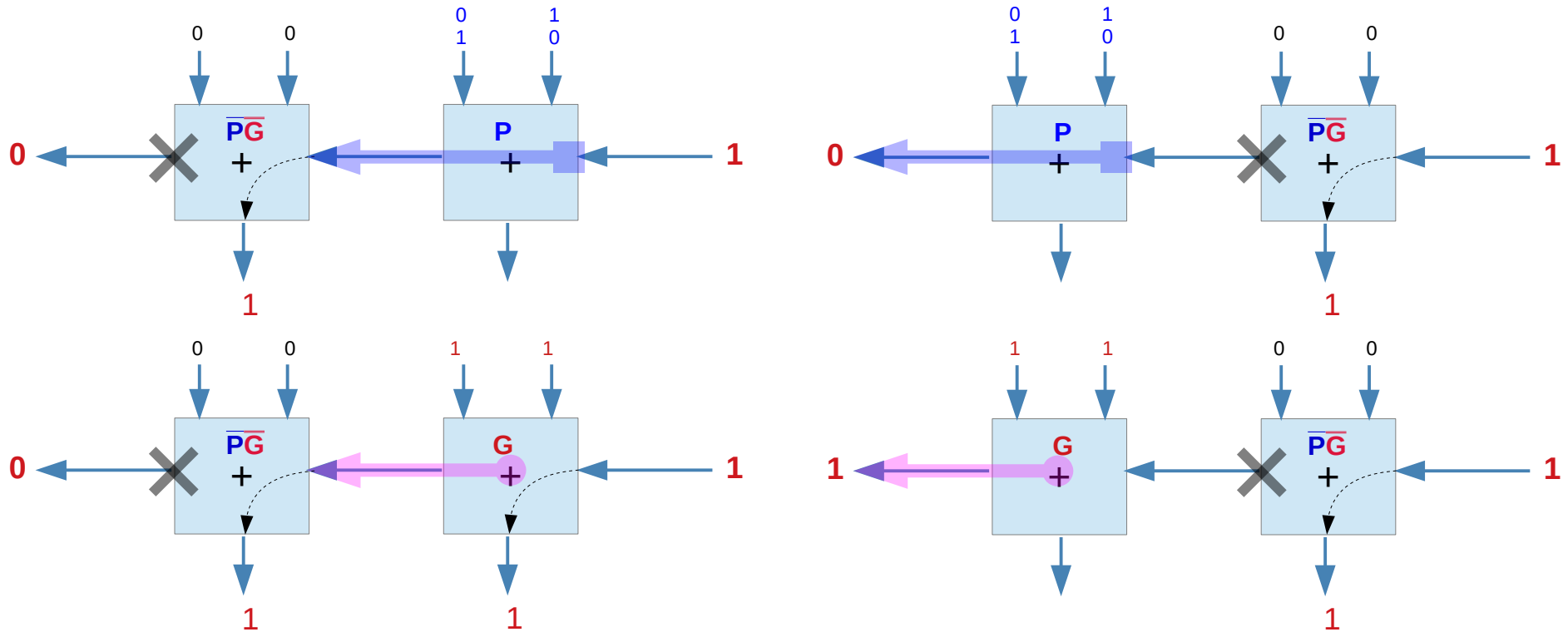

X	Y		
0	0	K	Kill ($=\overline{PG}$)
0	1	P	Propagate
1	0	P	Propagate
1	1	G	Generate

Carry Lookahead Adder

Carry Lookahead Adder

$$p_i = a_i \oplus b_i$$

$$g_i = a_i \wedge b_i$$

$$c_1 = g_0 + p_0 \wedge c_0$$


$$c_2 = g_1 + p_1 \wedge c_1$$

$$c_3 = g_2 + p_2 \wedge c_2$$

$$c_4 = g_3 + p_3 \wedge c_3$$


generated carry

propagated carry

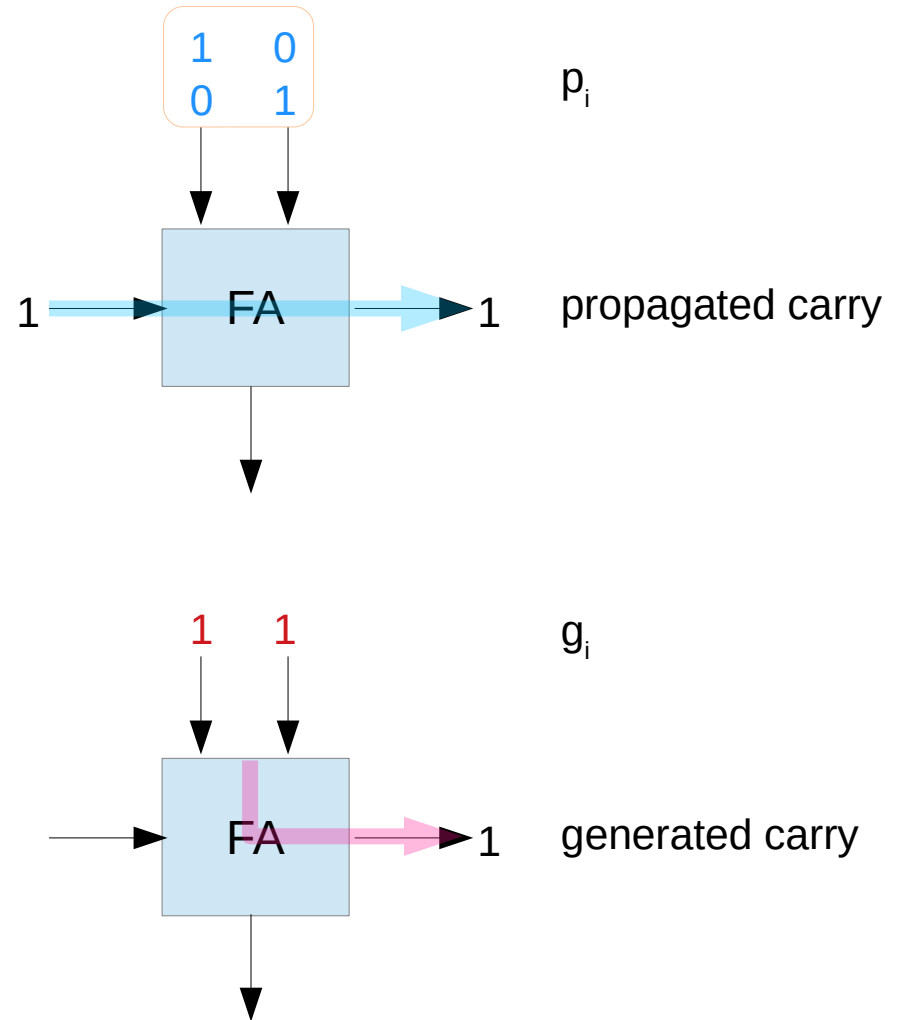

https://en.wikipedia.org/wiki/Carry-skip_adder


FA with P & G

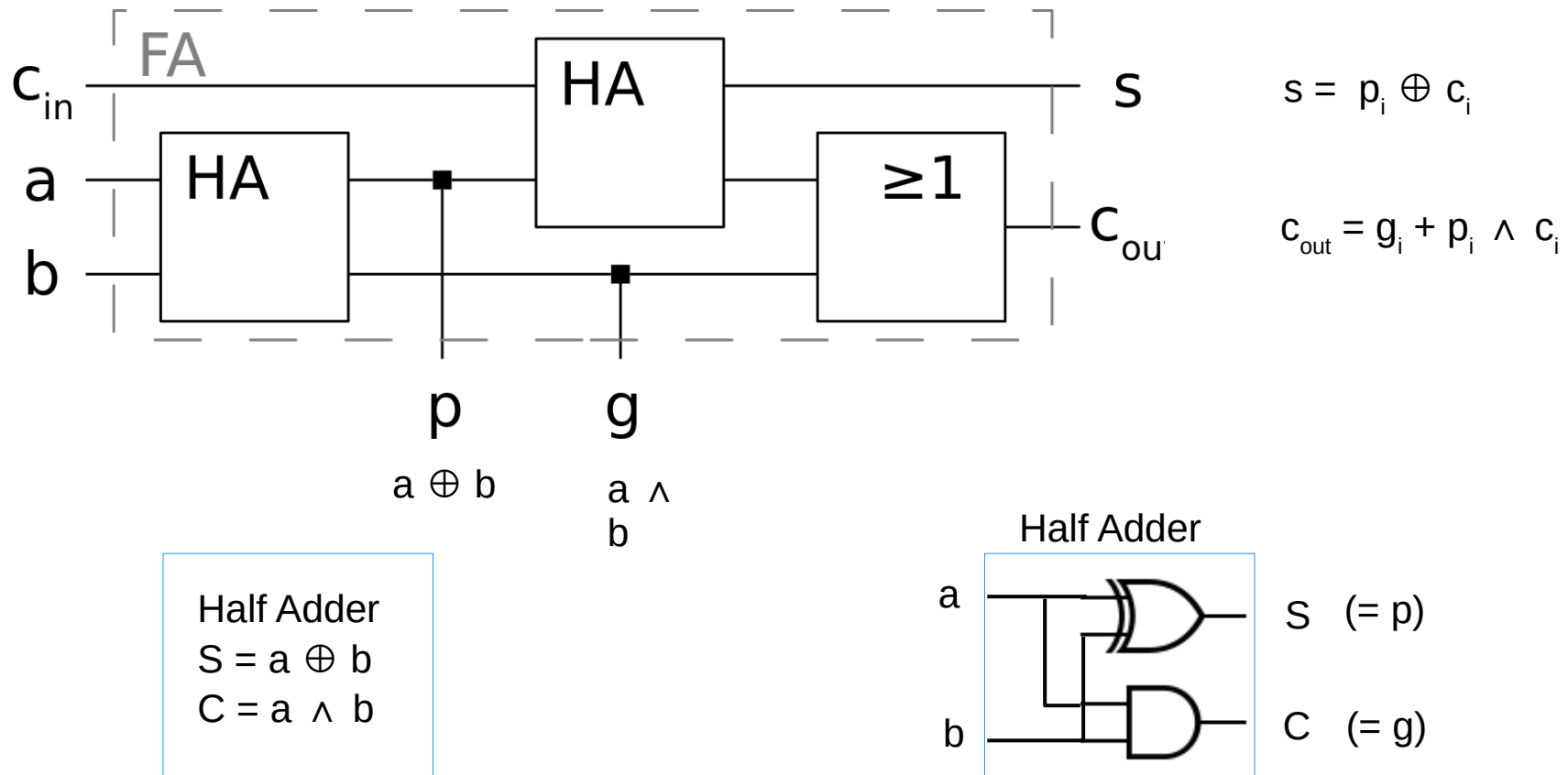

Full adder with additional generate and propagate signals.

https://en.wikipedia.org/wiki/Carry-skip_adder

4-bit Full Adder with P and G

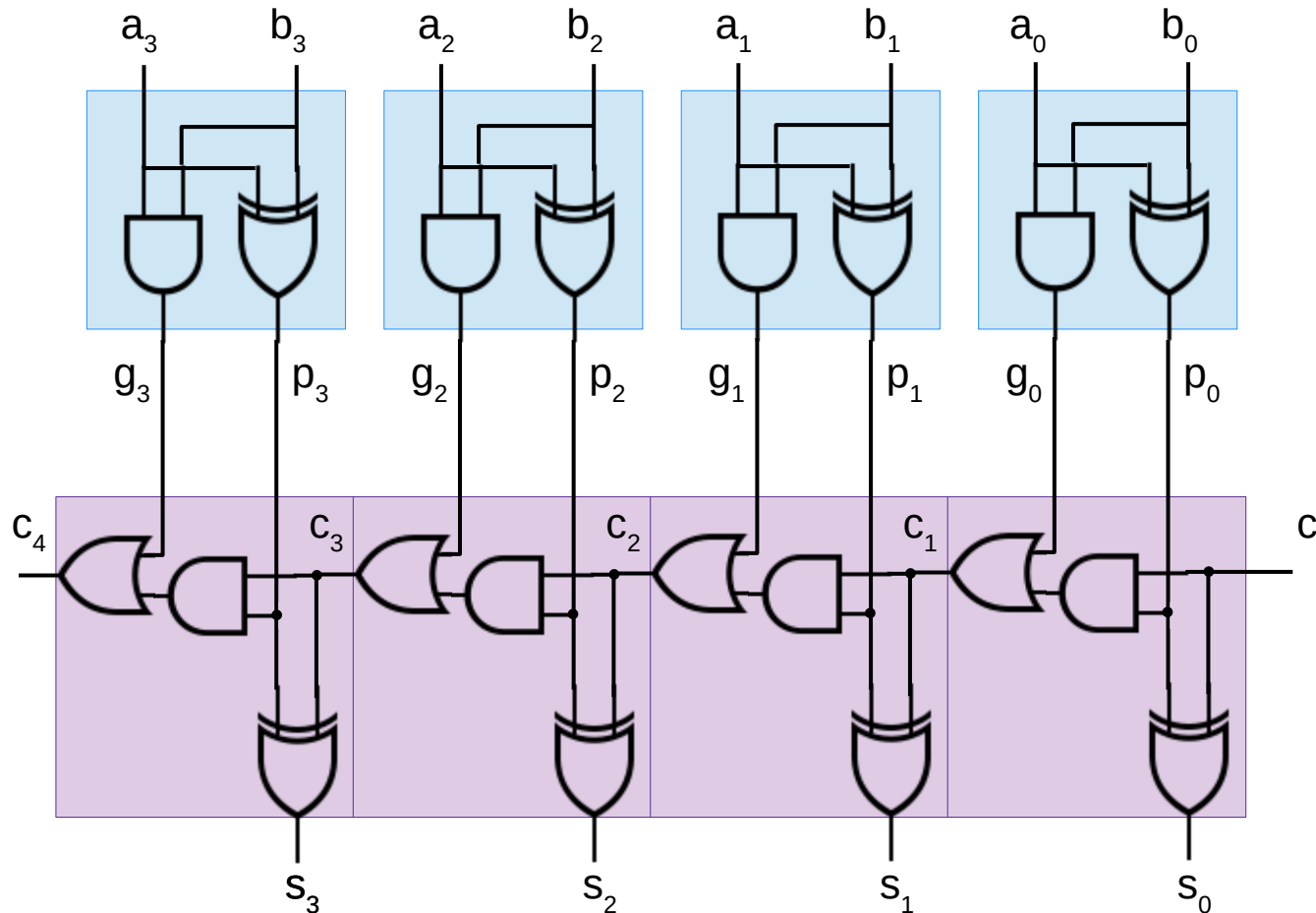

Half Adder

$$p_i = a_i \oplus b_i$$

$$g_i = a_i \wedge b_i$$

$$c_{i+1} = g_i + p_i c_i$$

$$s_i = p_i \oplus c_i$$

<https://upload.wikimedia.org/wikiversity/en/1/18/RCA.Note.H.1.20151215.pdf>

FA with P & G

for each operand input bit pair (a_i , b_i)
the propagate-conditions $p_i = a_i \oplus b_i$
are determined using an XOR-Gate .

when all propagate-conditions are true,


$$\begin{aligned} s &= p_{n-1} \wedge p_{n-2} \wedge \cdots \wedge p_1 \wedge p_0 = p_{[0:n-1]} \\ &= (a_{n-1} \oplus b_{n-1}) \wedge (a_{n-2} \oplus b_{n-2}) \wedge \cdots \wedge (a_1 \oplus b_1) \wedge (a_0 \oplus b_0) \end{aligned}$$

then the carry-in bit c_0 determines the carry-out bit c_n

c_0 can be propagated to c_{out} only when $s = 1$

https://en.wikipedia.org/wiki/Carry-skip_adder

C_0 propagation condition

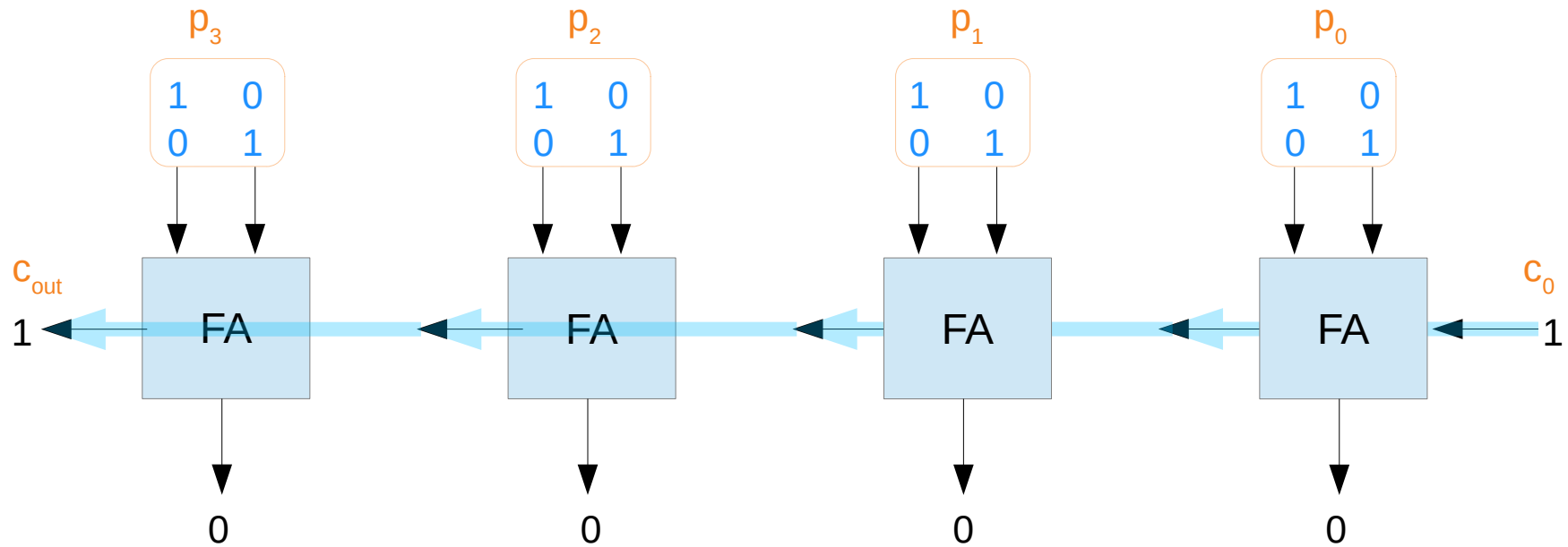

c_0 can be propagated to c_{out} only when $s = 1$

$$s = p_{n-1} \wedge p_{n-2} \wedge \cdots \wedge p_1 \wedge p_0 = p_{[0:n-1]}$$
$$= (a_{n-1} \oplus b_{n-1}) \wedge (a_{n-2} \oplus b_{n-2}) \wedge \cdots \wedge (a_1 \oplus b_1) \wedge (a_0 \oplus b_0)$$

https://en.wikipedia.org/wiki/Carry-skip_adder

FA with P & G

The n-bit **carry skip adder** consists of
a n-bit **carry-ripple-chain**,
a n-input **AND-gate** and
one **multiplexer**.


Each propagate bit p_i that is provided by the carry-ripple-chain
is connected to the n-input AND-gate.

The resulting bit is used as the select bit of a multiplexer
that switches either the last carry-bit c_n or the carry-in c_0
to the carry-out signal c_{out}

$$s = p_{n-1} \wedge p_{n-2} \wedge \cdots \wedge p_1 \wedge p_0 = p_{[0:n-1]}$$

https://en.wikipedia.org/wiki/Carry-skip_adder

4-bit Carry Skip Adder

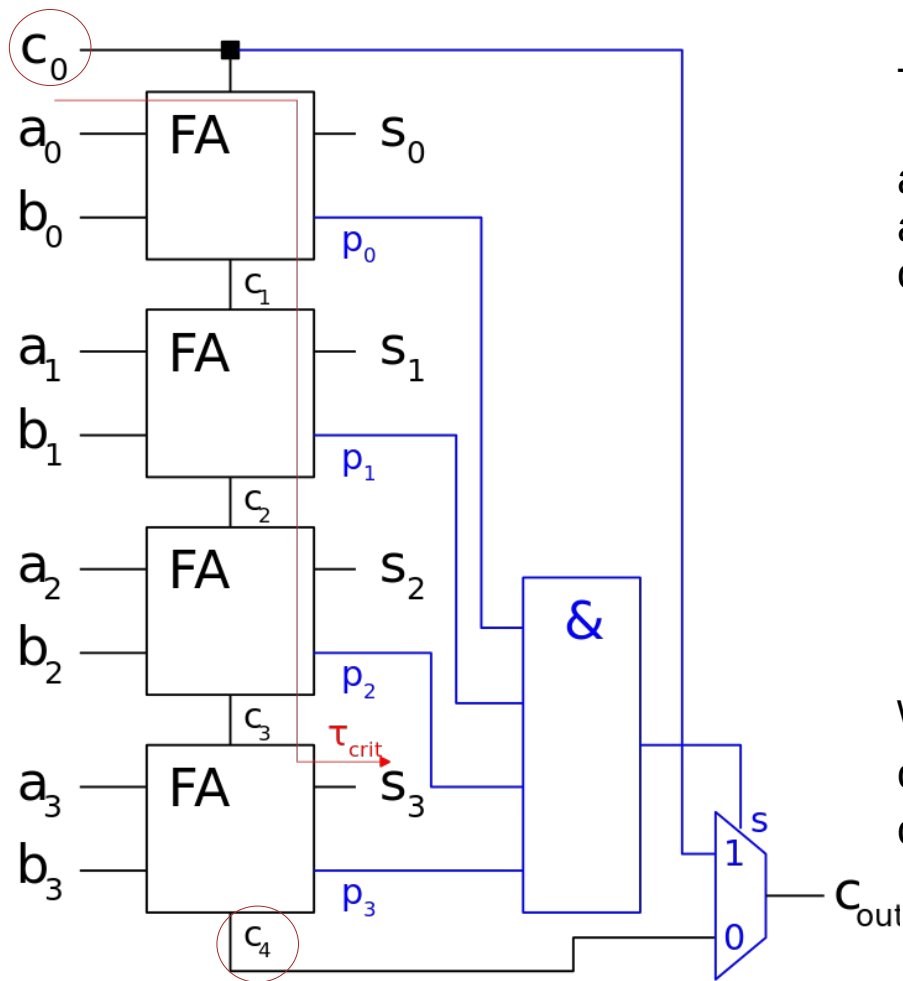

The n-bit-carry-skip adder consists of

a n-bit **carry-ripple-chain**,
a n-input **AND-gate** and
one **multiplexer**.

a multiplexer switches
either the last carry-bit c_n or the carry-in c_0
to the carry-out signal c_{out}



$$s = p_{n-1} \wedge p_{n-2} \wedge \dots \wedge p_1 \wedge p_0 = p_{[0:n-1]}$$

when $s = 1$, $c_{out} \leftarrow c_0$


otherwise, internally generated carries
can be propagated to c_{out}

https://en.wikipedia.org/wiki/Carry-skip_adder

Carry Skip Adder

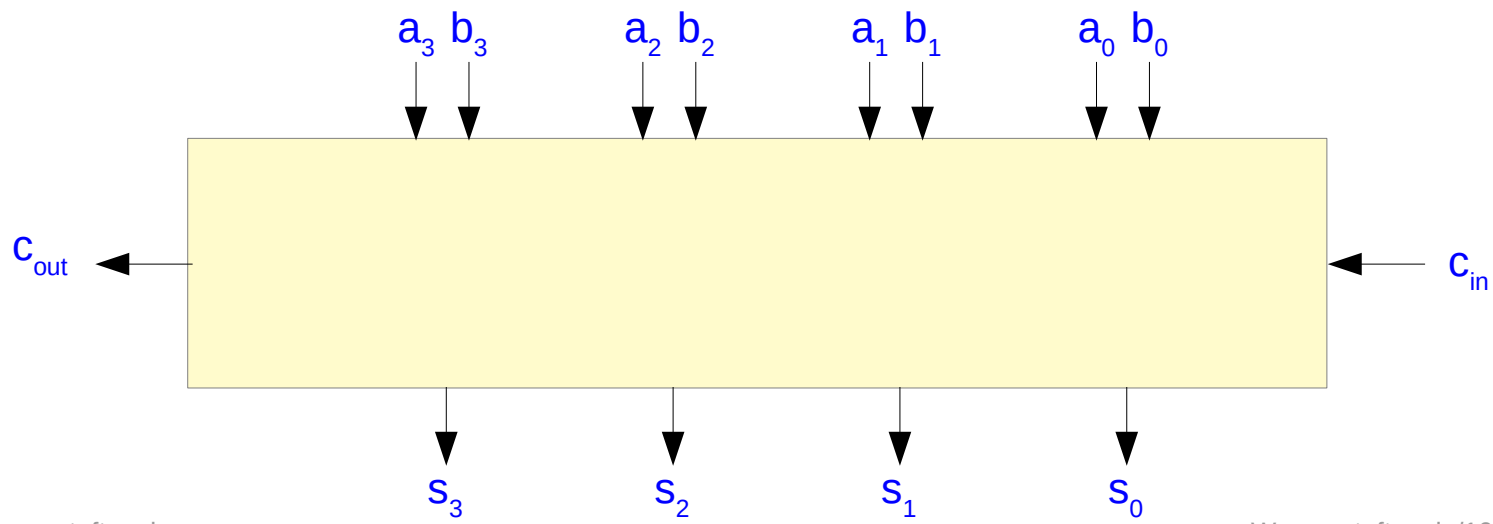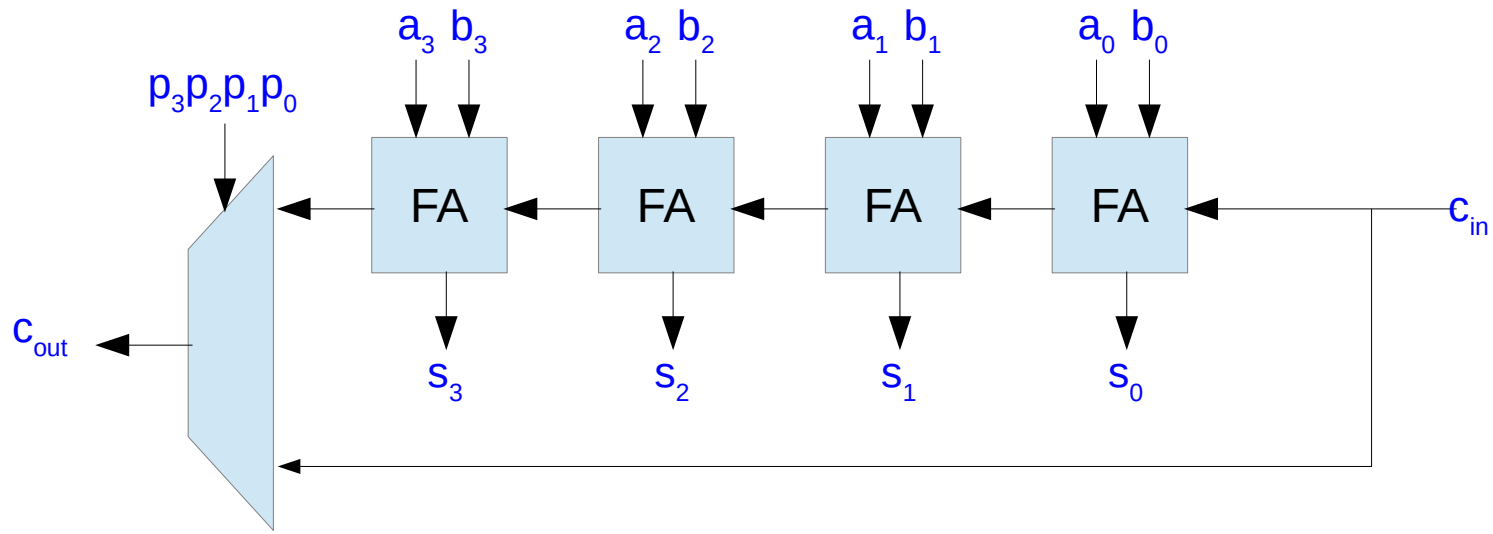

Carry Skip Adder

 

Block Carry Skip Adder


Block-carry-skip adders are composed of a number of carry-skip adders. There are two types of block-carry-skip adders. The two operands

$A = (a_{n-1}, a_{n-2}, \dots, a_1, a_0)$ and $B = (b_{n-1}, b_{n-2}, \dots, b_1, b_0)$ are split in k blocks of $(m_k, m_{k-1}, \dots, m_2, m_1)$ bits.

- Why are block-carry-skip-adders used?
- Should the block-size be constant or variable?
- Fixed block width vs. variable block width

https://en.wikipedia.org/wiki/Carry-skip_adder

Block Carry Skip Adder

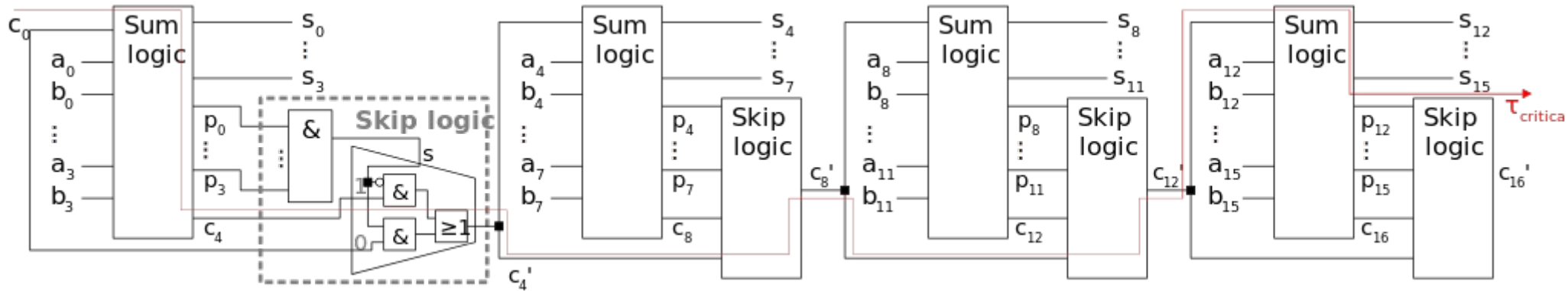

https://en.wikipedia.org/wiki/Carry-skip_adder

Carry Skip Adder

Since the **Cin-to-Cout** represents the longest path in the ripple-carry-adder, an obvious attempt is to accelerate carry propagation through the adder.



This is accomplished by using **Carry-Propagate** p_i signals within a group of bits.

If all the p_i signals within the group are $p_i = 1$, the condition exist for the carry to bypass the entire group:

$$P = p_i \cdot p_{i+1} \cdot p_{i+2} \cdot \dots \cdot p_{i+k-1}$$

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

Carry Skip Adder

  

Carry Skip Adder

The **Carry Skip Adder** (CSKA) divides the words to be added into groups of equal size of **k-bits**.

The basic structure of an **N-bit Carry Skip Adder**

Within the group, carry propagates in a ripple-carry fashion.

In addition, an AND gate is used to form the **group propagate** signal **P**.


$$P = p_i \cdot p_{i+1} \cdot p_{i+2} \cdot \dots \cdot p_{i+k-1}$$

If $P = 1$ the condition exists for carry to bypass (skip) over the group


Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

Carry Skip Adder

$$N = R \cdot k$$

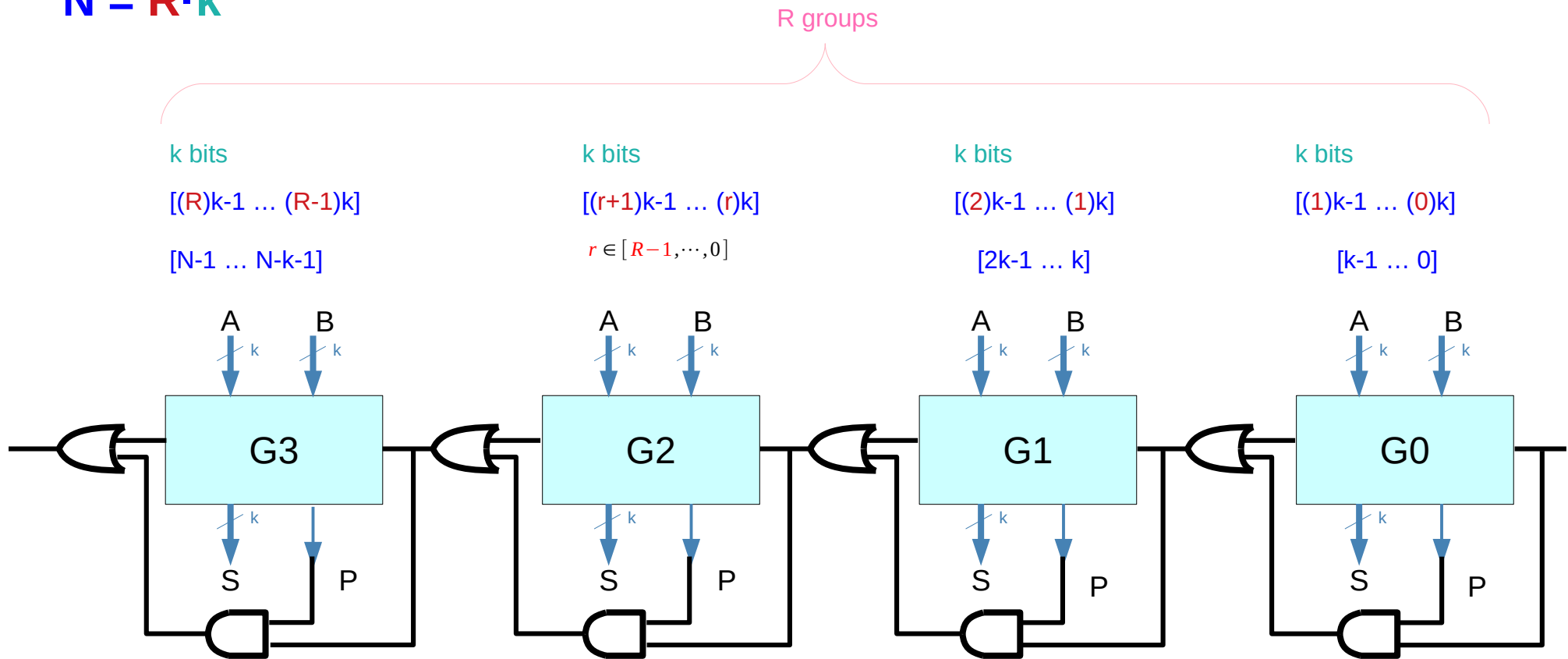

Carry Skip Adder

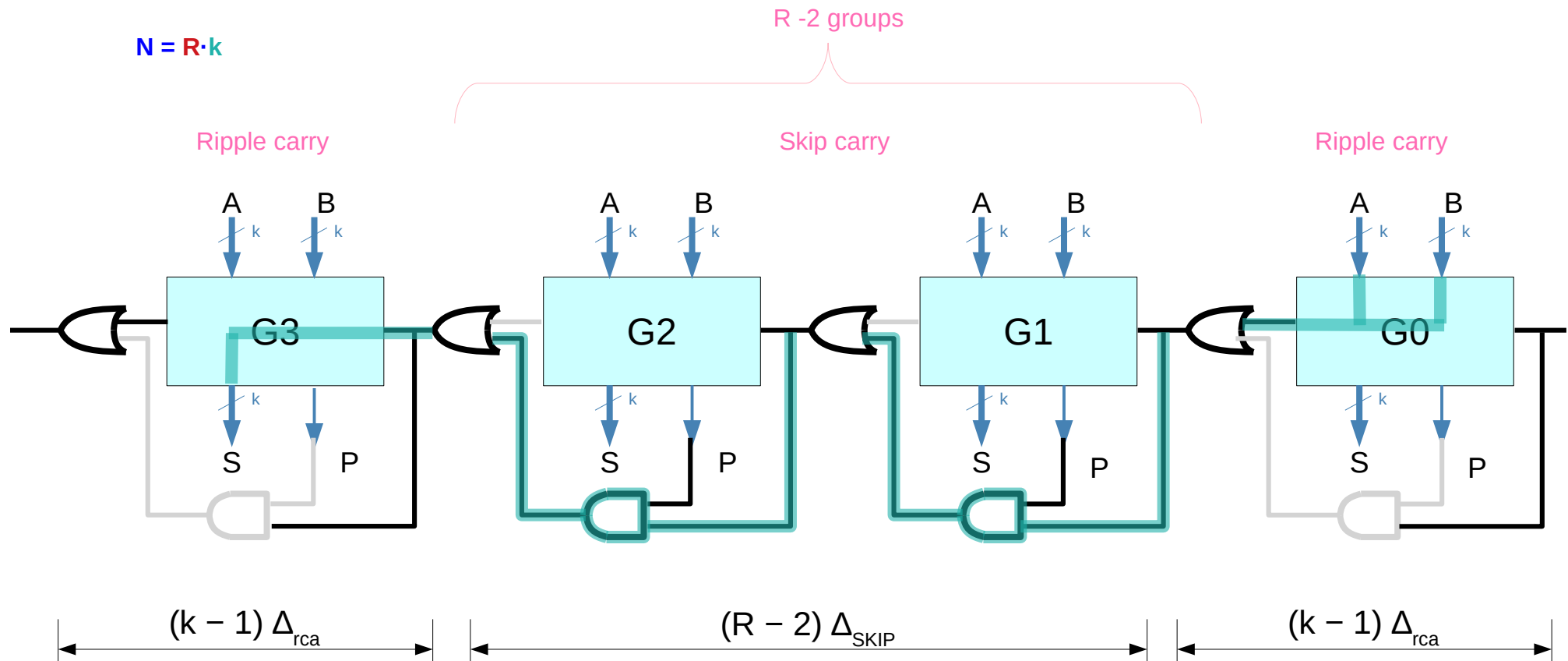



Any kill or generate condition results in divided (broken) critical paths

All FA's in R-2 groups must have the propagate condition

Carry Skip Adder


Ripple through $k-1$ bits

$$(k-1) \Delta_{rca}$$

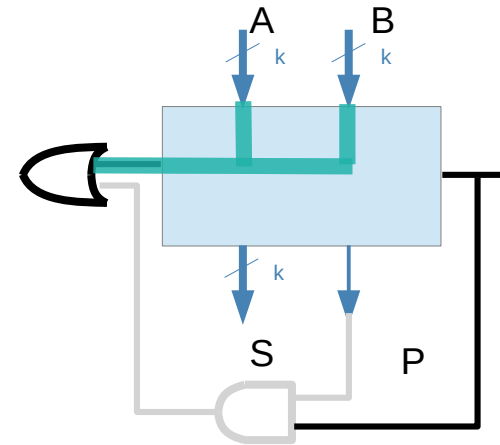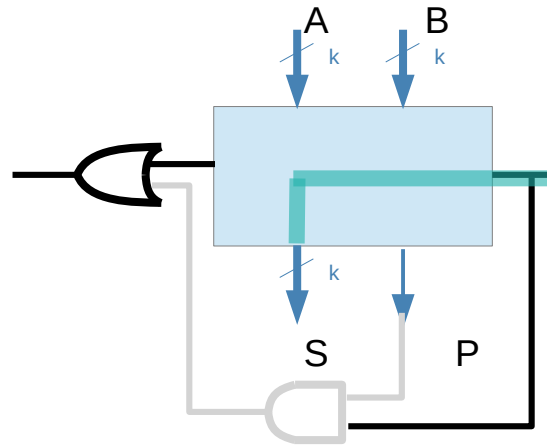

Skip carry

$$\Delta_{\text{SKIP}}$$

 

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

Carry Skip Adder

The maximal delay Δ of a Carry Skip Adder is encountered when **carry** is generated in the **least-significant bit** position,

- rippling through $k-1$ bit positions,
- skipping over $R-2 = N/k-2$ groups in the middle,
- rippling to the $k-1$ bits of most significant group and
- being assimilated in the N -th bit position to produce the sum S_N :

$$\begin{aligned}\Delta_{\text{CSA}} &= (k - 1) \Delta_{\text{rca}} + (R - 2) \Delta_{\text{SKIP}} + (k - 1) \Delta_{\text{rca}} \\ &= 2 (k - 1) \Delta_{\text{rca}} + (R - 2) \Delta_{\text{SKIP}} \\ &= 2 (k - 1) \Delta_{\text{rca}} + (N/k - 2) \Delta_{\text{SKIP}}\end{aligned}$$

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers


Carry Skip Adder

$$\begin{aligned}\Delta_{\text{CSA}} &= (k - 1) \Delta_{\text{rca}} + (R - 2) \Delta_{\text{SKIP}} + (k - 1) \Delta_{\text{rca}} \\ &= 2(k - 1) \Delta_{\text{rca}} + (R - 2) \Delta_{\text{SKIP}} \\ &= 2(k - 1) \Delta_{\text{rca}} + (N/k - 2) \Delta_{\text{SKIP}}\end{aligned}$$

Carry Skip Adder is faster than RCA at the expense of a few relatively simple modifications.



The delay is still linearly dependent on the size of the adder N , however this linear dependence is reduced by a factor of $1/k$

$$N = R \cdot k$$

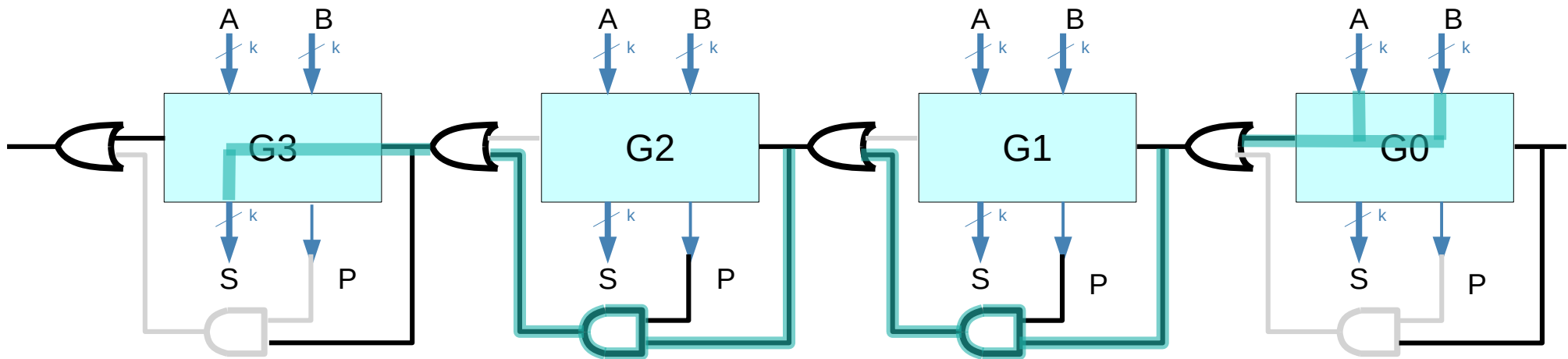

Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

Design C (9) – When Cout1 = 1

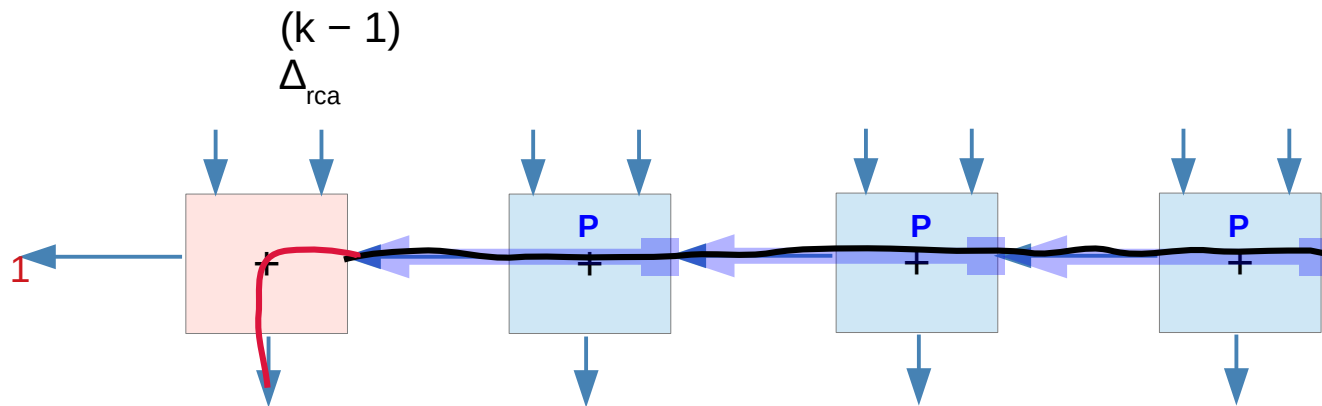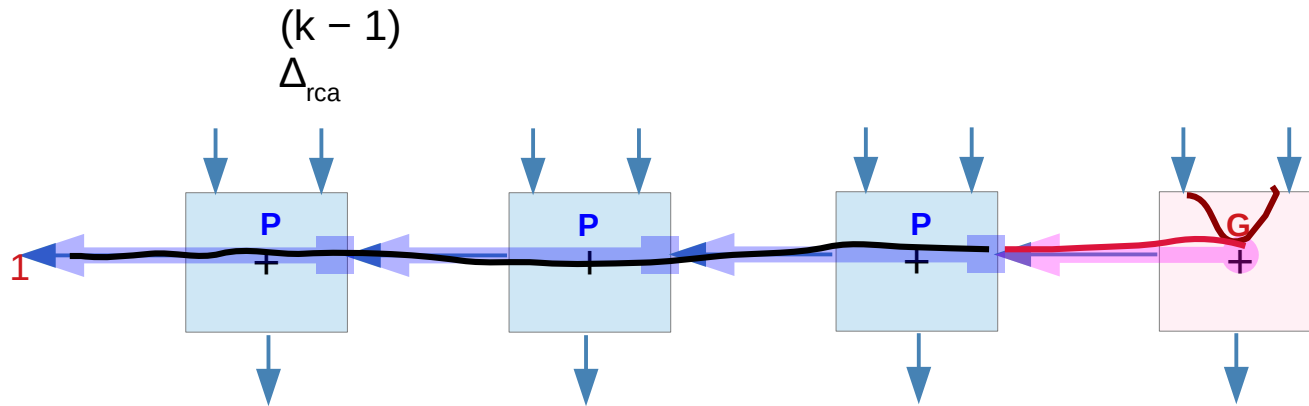

High Performance Carry Chains for FPGAs, S. Hauck, M. M. Hosler, T. W. Fry

Carry Skip Adder

If an arbitrary block generated a carry by itself,
The carry will always propagate to the next block
However, if the second block generates a carry itself,
Or kill the carry, then that is the end of the critical path

If the second block propagates the carry, then we see
The advantage of the CSA architecture

<https://electronics.stackexchange.com/questions/21251/critical-path-for-carry-skip-adder>

<https://electronics.stackexchange.com/questions/21251/critical-path-for-carry-skip-adder>

References

- [1] en.wikipedia.org
- [2] Parhami, “Computer Arithmetic Algorithms and Hardware Designs”