

Combinational Gates (3A)

Transistor Level Design



Copyright (c) 2011-2016 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".

Please send corrections (or suggestions) to youngwlim@hotmail.com.

This document was produced by using OpenOffice and Octave.


nMOS : series and parallel connections

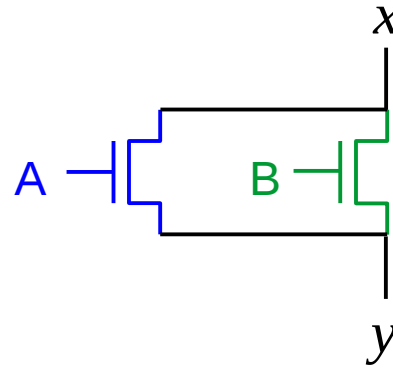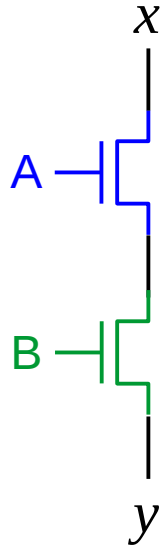


$$x = y \text{ if } A \cdot B$$

$$x = y \text{ if } A + B$$

pMOS : series and parallel connections


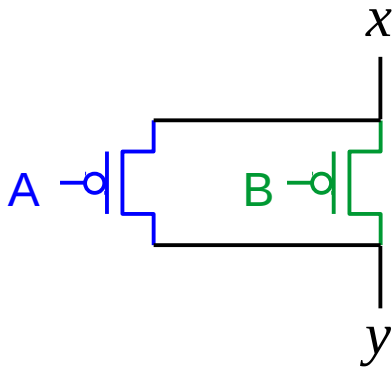

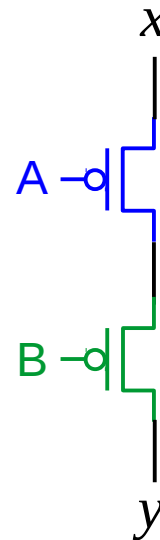
$$x = y \text{ if } \frac{\bar{A} + \bar{B}}{A \cdot B}$$




$$x = y \text{ if } \frac{\bar{A} \cdot \bar{B}}{A + B}$$



NAND Gate

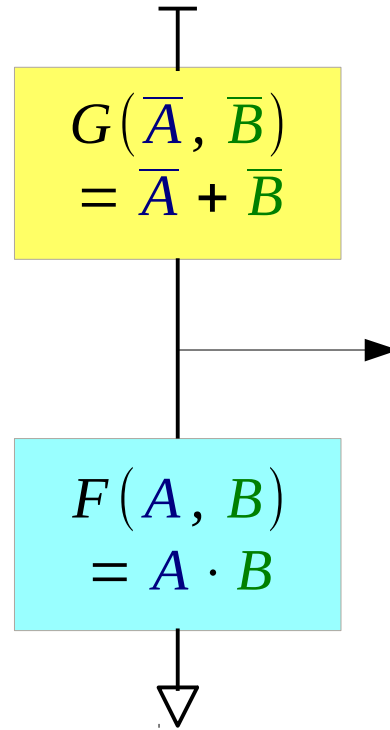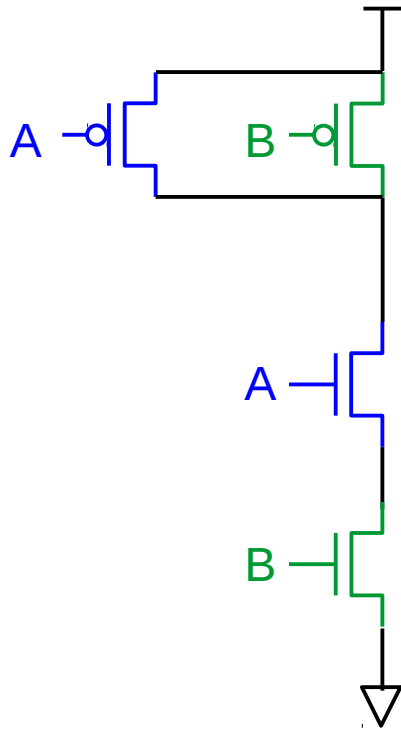

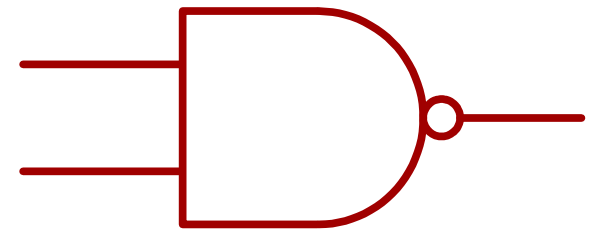
$$\overline{F(A, B)} = G(\overline{A}, \overline{B})$$
$$\overline{A \cdot B} = \overline{A} + \overline{B}$$







NOR Gate

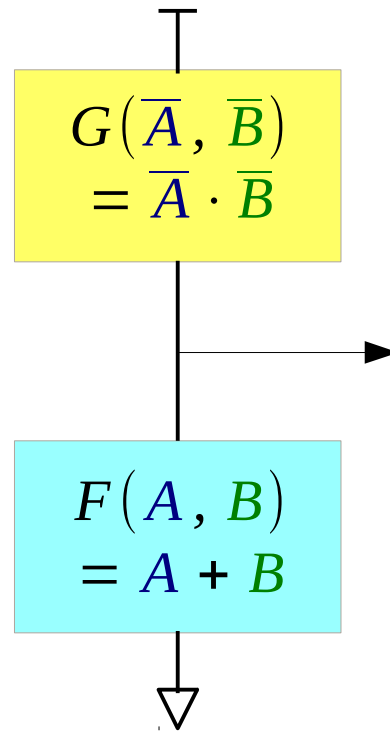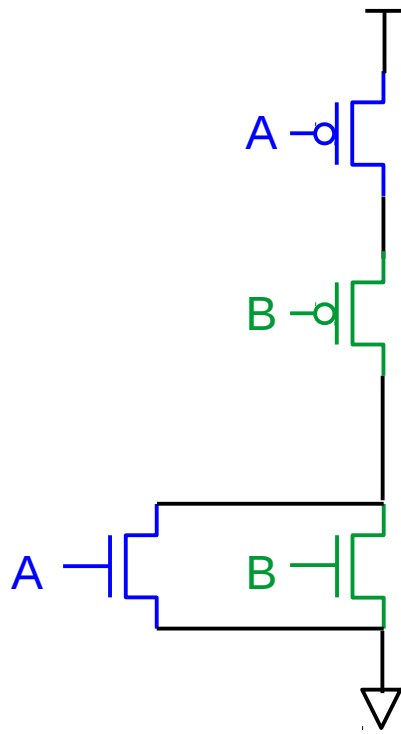

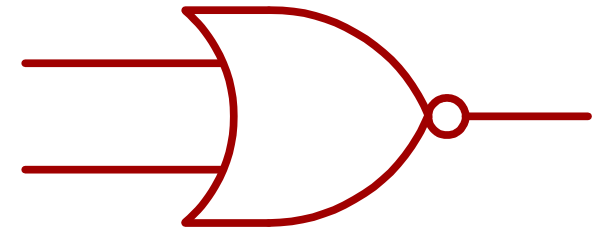
$$\overline{F(A, B)} = G(\bar{A}, \bar{B})$$
$$\overline{A + B} = \bar{A} \cdot \bar{B}$$




Circuit Families

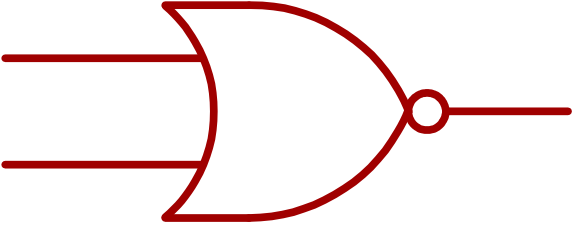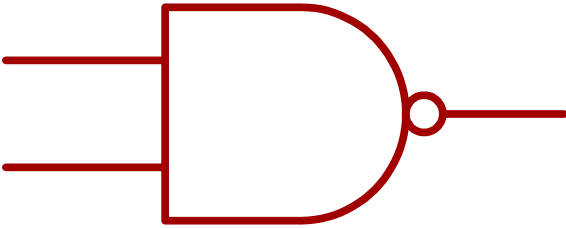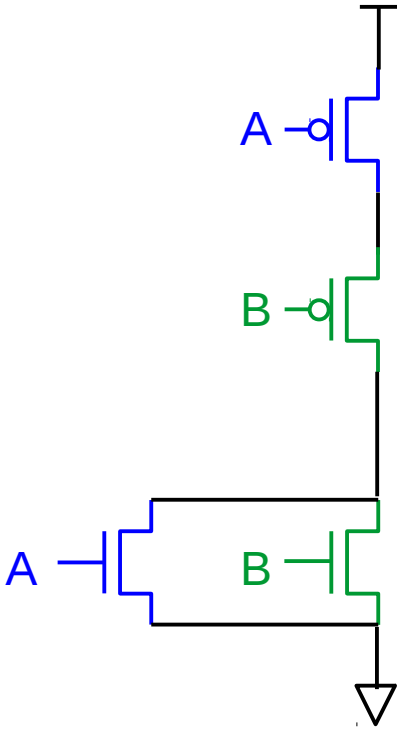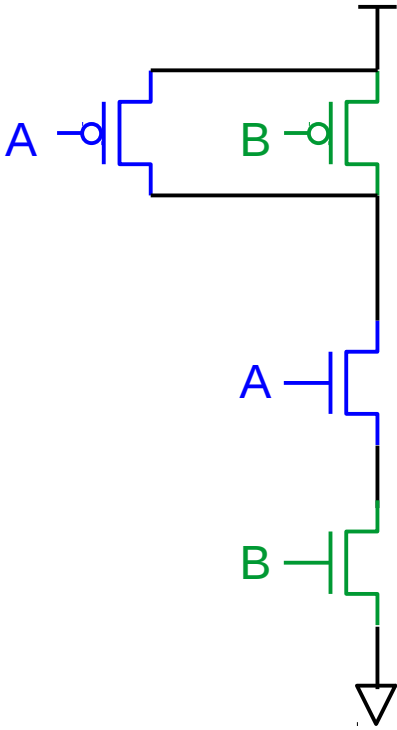

Circuit Families

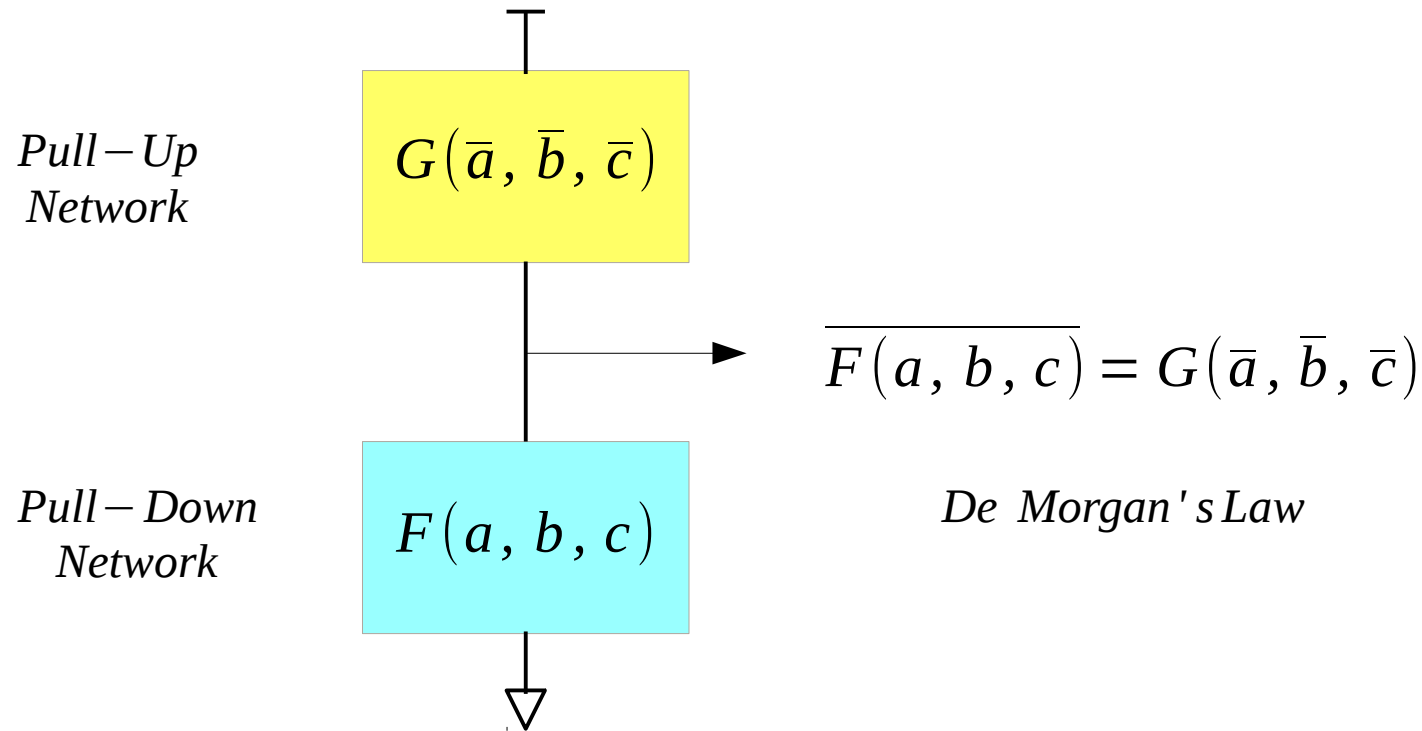

nMOS Operating Modes

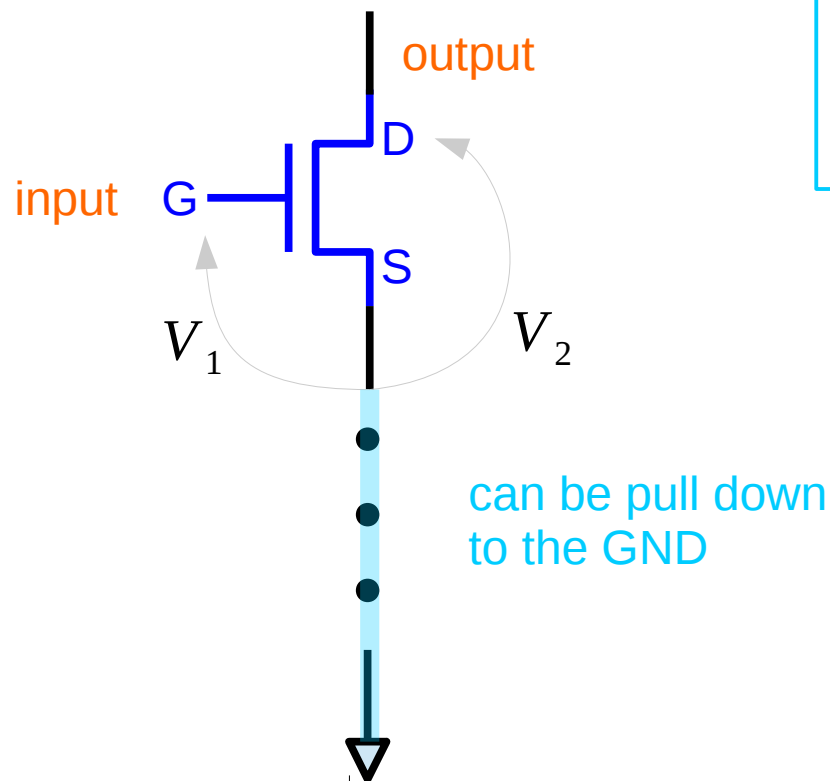

$$V_1 < V_{th}$$

OFF

$$V_1 - V_{th} > 0$$

$$V_1 - V_{th} > V_2$$

LIN

$$I_{DS} \propto v_{GS}$$



$$V_1 - V_{th} > 0$$

$$V_1 - V_{th} < V_2$$


SAT

$$I_{DS} = I_{SAT}$$


Pass Transistor

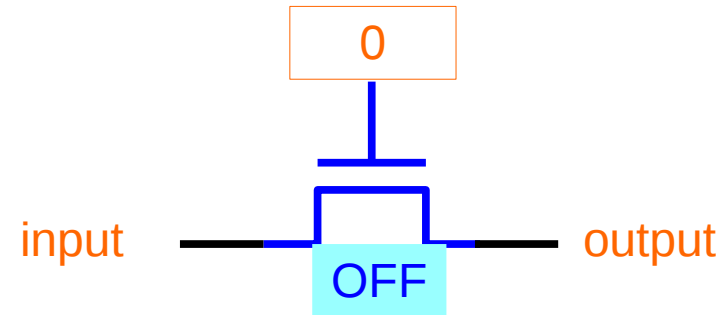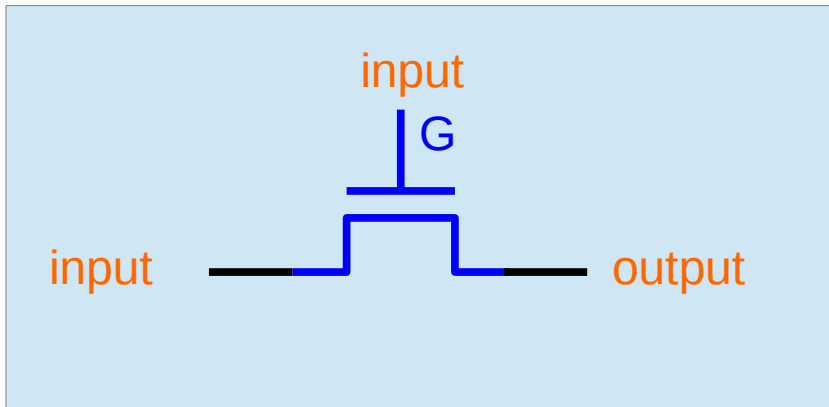


Threshold drop

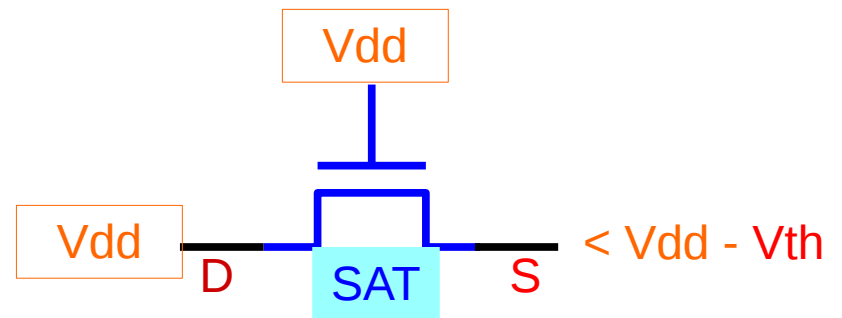






can be pull down to the GND

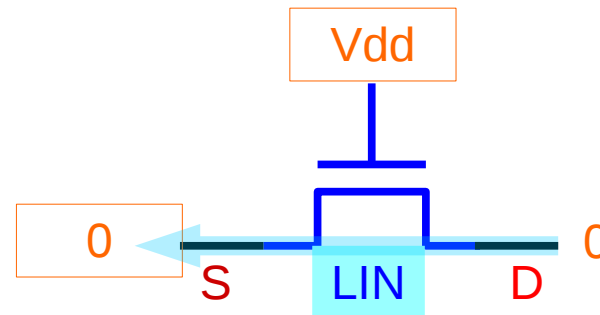

Strong 0 and Weak 1

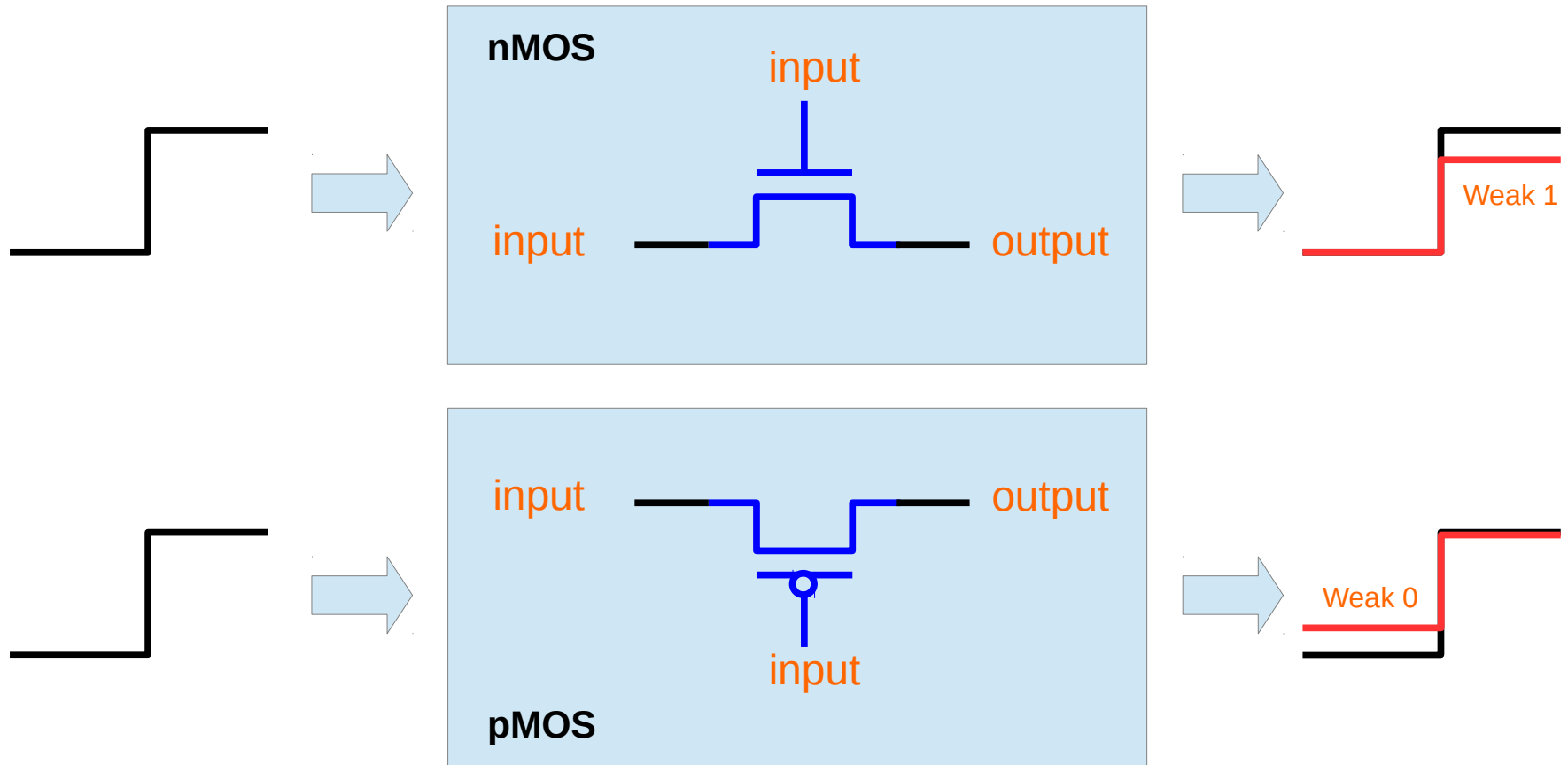


Pass Transistor

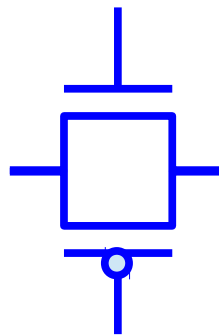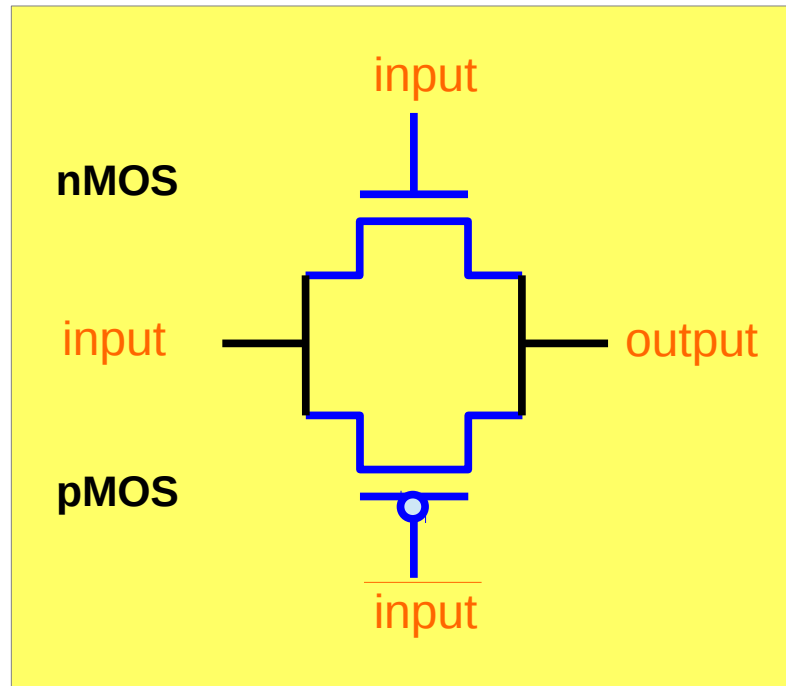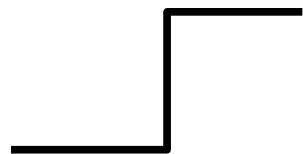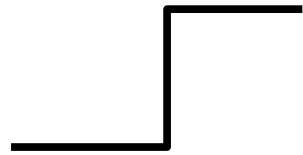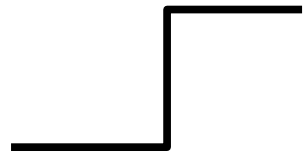


+



=

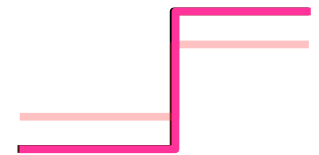

Pass Transistor

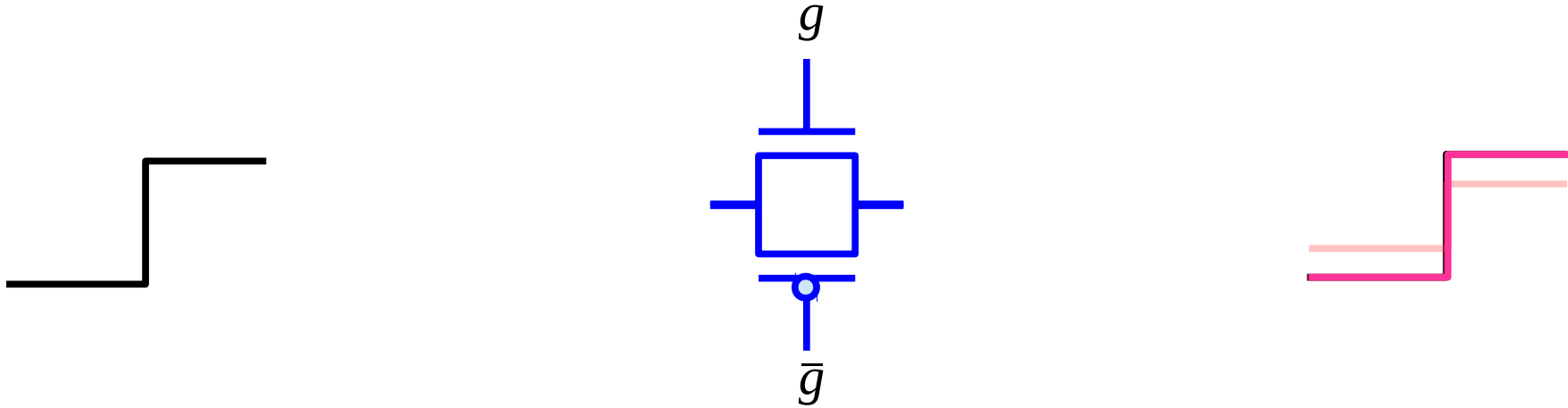

Pass strong 1 and strong 0

When $g = V_{dd}$ that is
 $\bar{g} = 0$

Circuit Families

Circuit Families

- Static CMOS
- Ratioed Circuits
- Cascade Voltage Switch Logic
- Dynamic Circuits
- Pass Transistor Circuits

References

- [1] <http://en.wikipedia.org/>
- [2] <http://www.allaboutcircuits.com/>
- [3] W. Wolf, "Modern VLSI Design : Systems on Silicon"
- [4] N. Weste, D. Harris, "CMOS VLSI Design: A Circuits and Systems Perspective"
- [5] J. P. Uyemura, "Introduction to VLSI Circuits and Systems"
- [6] https://en.wikiversity.org/wiki/The_necessities_in_SOC_Design
- [7] https://en.wikiversity.org/wiki/The_necessities_in_Digital_Design
- [8] https://en.wikiversity.org/wiki/The_necessities_in_Computer_Design
- [9] https://en.wikiversity.org/wiki/The_necessities_in_Computer_Architecture
- [10] https://en.wikiversity.org/wiki/The_necessities_in_Computer_Organization