

VHDL Carry Chain Adder (6C)

-
-

Copyright (c) 2021 -- 2010 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".

Please send corrections (or suggestions) to youngwlim@hotmail.com.

This document was produced by using OpenOffice and Octave.


GP Cell

$x(i), y(i) : (\log_2 B)$ -bit number

Generate	$G_i = a_i \cdot b_i$
Propagate	$P_i = a_i \oplus b_i$

Generate	$g(i) = 1$	If $x(i) + y(i) > (B - 1)$
	0	otherwise

Propagate	$p(i) = 1$	If $x(i) + y(i) = (B - 1)$
	0	otherwise

 


Synthesis of Arithmetic Circuits: FPGA, ASIC and Ebedded Systems, J-P Deschamps et al

Carry Chain Cell (1)

$q(i+1), q(i)$: 1-bit number

$$c_{out} = G_i + P_i c_i$$


$q(i+1) = q(i)$	when $p(i) = 1$	Propagate
$= g(i)$	otherwise	Generate

 

Synthesis of Arithmetic Circuits: FPGA, ASIC and Embedded Systems, J-P Deschamps et al

Carry Chain Cell (2)

$q(i+1)$	= $q(i)$	when $p(i) = 1$	Propagate
	= $g(i)$	otherwise	Generate

 


Synthesis of Arithmetic Circuits: FPGA, ASIC and Embedded Systems, J-P Deschamps et al

$$c_{out} = G_i + P_i c_i$$

Mod B Sum Cell

$$z(i) = (x(i) + y(i) + q(i)) \bmod B$$

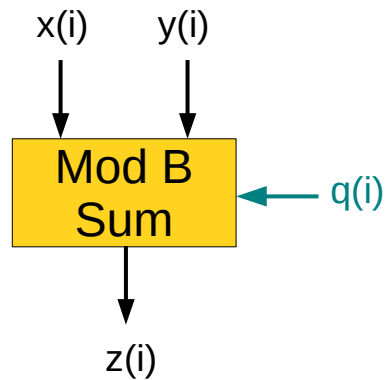

Synthesis of Arithmetic Circuits: FPGA, ASIC and Embedded Systems, J-P Deschamps et al

4-ary Carry Chain Addition Example

Generate $g(i) = 1$ If $x(i) + y(i) > 3$
 0 otherwise

Propagate $p(i) = 1$ If $x(i) + y(i) = 3$
 0 otherwise

$q(i+1)$ = $q(i)$ when $p(i) = 1$ Propagate
 = $g(i)$ otherwise Generate


$$z(i) = (x(i) + y(i) + q(i)) \bmod 4$$

	0	1	2	3
0	0	1	2	3
1	1	2	3	4
2	2	3	4	5
3	3	4	5	6

$p(i)$	0	1	2	3
0	0	0	0	1
1	0	0	1	0
2	0	1	0	0
3	1	0	0	0

$g(i)$	0	1	2	3
0	0	0	0	0
1	0	0	0	1
2	0	0	1	1
3	0	1	1	1

Carry Chain Adder

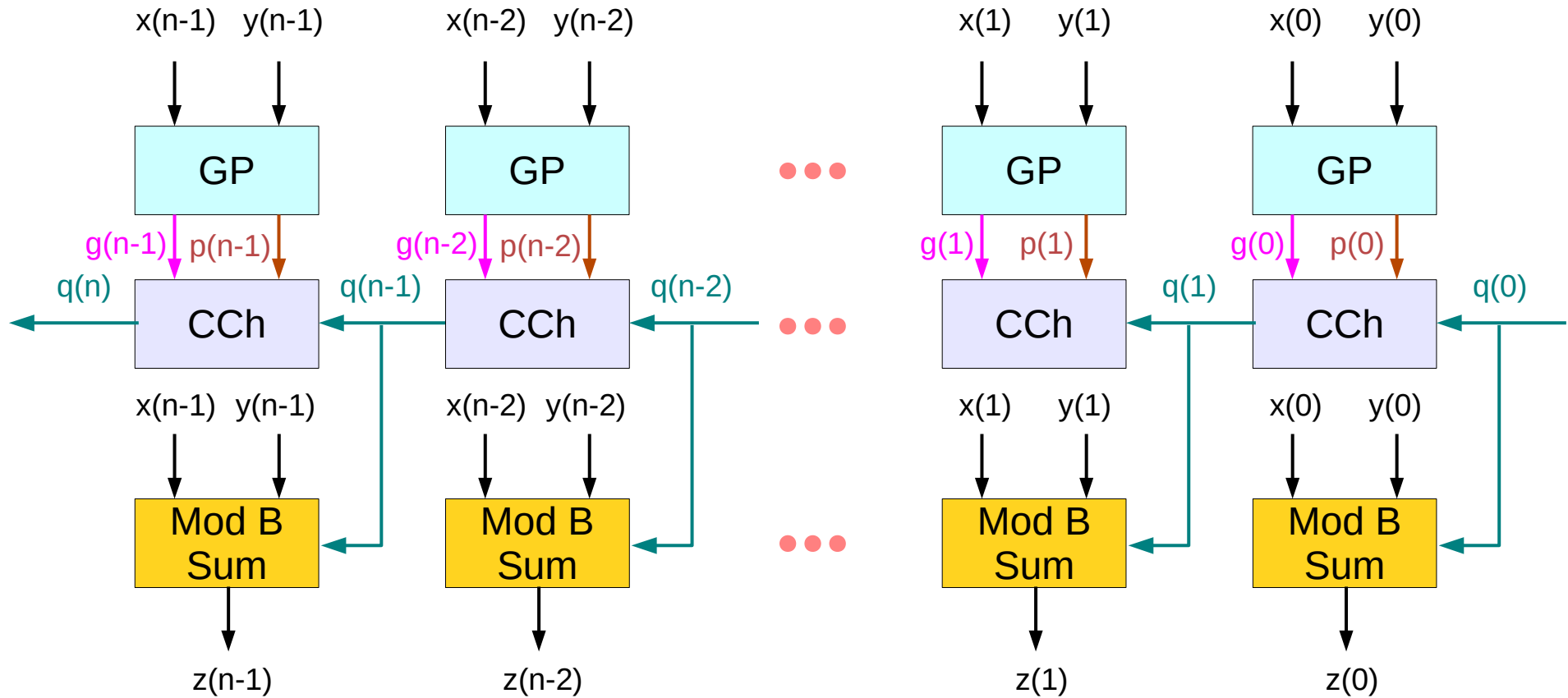

Synthesis of Arithmetic Circuits: FPGA, ASIC and Embedded Systems, J-P Deschamps et al

Carry Chain Addition

```
-- computation of the generation and propagation conditions
for i in 0..n-1 loop
    g(i) := g(x(i), y(i));
    p(i) := p(x(i), y(i));
end loop

-- carry computation
q(0) := c_in;
for i in 0..n-1 loop
    if p(i)=1 then q(i+1):=q(i); else q(i+1):=g(i); end if;
end loop

-- sum computation
for i in 0..n-1 loop
    z(i) := (x(i)+y(i)+q(i)) mod B
end loop;
z(n) := q(n);
```

Synthesis of Arithmetic Circuits: FPGA, ASIC and Embedded Systems, J-P Deschamps et al

Computation Decomposition

the first iteraton includes **2.n B-ary** operations

computation of $g(i)$ and $p(i)$ that could be executed in parallel

```
g(i) := g(x(i), y(i));
```

```
p(i) := p(x(i), y(i));
```

The second iteration is made up of **n** iteration steps

that must be used executed sequentially

as $q(i+1)$ is a function of $q(i)$

consists of **binary** operation only

```
if p(i)=1 then q(i+1):=q(i); else q(i+1):=g(i); end if;
```

the last iteration includes **n B-ary** operations


computation of $z(i)$ that could be executed in parallel

```
z(i) := (x(i)+y(i)+q(i)) mod B
```

Synthesis of Arithmetic Circuits: FPGA, ASIC and Ebedded Systems, J-P Deschamps et al

Sequential and concurrent computations

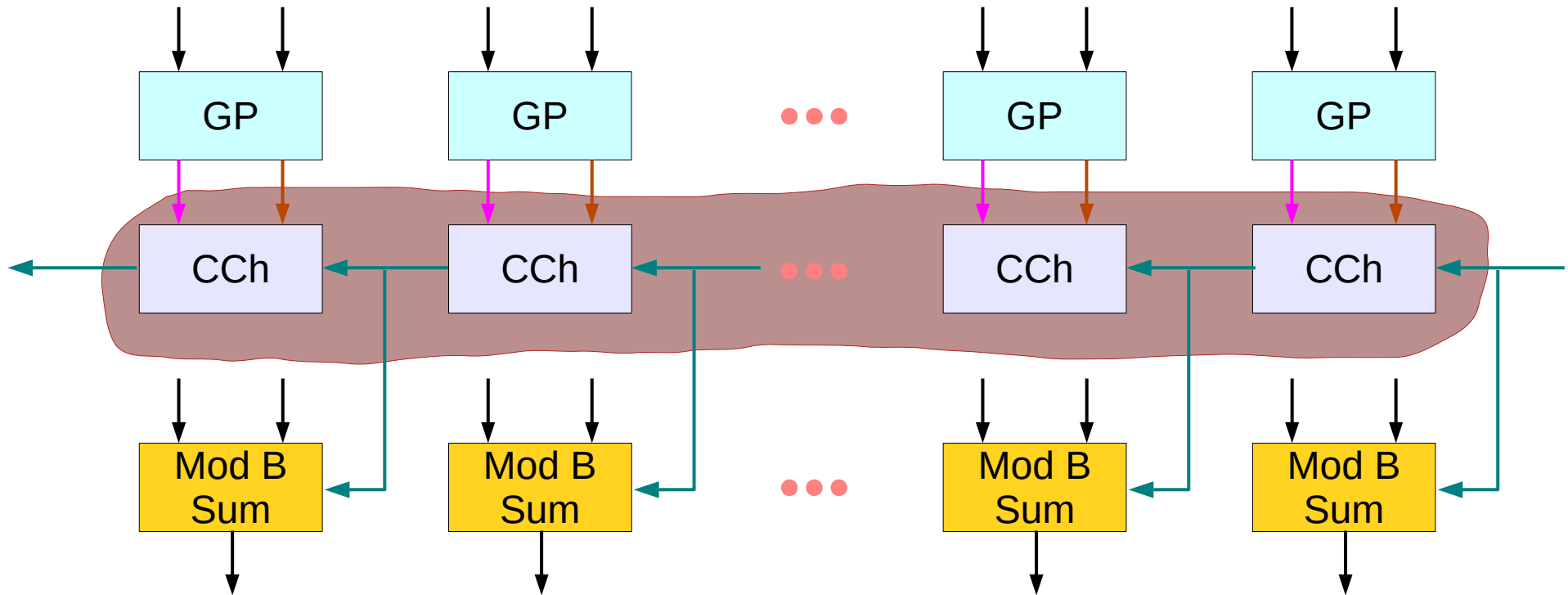Splits the operations into **concurrent B-ary** ones (1st and 3rd iterations)
And **sequential binary** ones (2nd iterations)



Synthesis of Arithmetic Circuits: FPGA, ASIC and Embedded Systems, J-P Deschamps et al

B-ary n-digit Carry Chain Adder VHDL Code

```
q(0) <= c_in;

iterative_step for i in 0 to n-1 generate
    p(i) <= '1' when x(i)+y(i) = B-1 else '0';
    g(i) <= '1' when x(i)+y(i) > B-1 else '0';
    with p(i) select q(i+1) <= q(i) when '1', g(i) when others;
    z(i) <= (x(i)+y(i)+ conv_integer(q(i))) mod B;
end generate;

c_out <= q(n);
```


Computation Substitution

The **sequential binary** operations are the same whatever base **B** is

However, the expected computation time can be reduced
by the substitution of the relatively complex instruction

```
if  $x(i)+y(i)+q(i)>B-1$  then  $q(i+1):=1$  else  $q(i+1):=0$  end if;
```
 
```
if  $p(i)=1$  then  $q(i+1):=q(i)$  else  $q(i+1):=g(i)$ ; end if;
```



Synthesis of Arithmetic Circuits: FPGA, ASIC and Embedded Systems, J-P Deschamps et al

Relaxing $g(i)$

```
if  $p(i)=1$  then  $q(i+1) := q(i)$  else  $q(i+1) := g(i)$ ; end if;
```

the corresponding Boolean equation

$$q(i+1) = p(i).q(i) \vee \text{not}(p(i)).g(i)$$

the generate function $g(a,b)$ can be relaxed as follows

$g(a,b) = 1$	if $a + b > B-1$ when $p(i) = 0$ $\text{not}(p(i))=1$
$g(a,b) = 0$	if $a + b < B-1$ when $p(i) = 0$ $\text{not}(p(i))=1$
$g(a,b) = 1/0$ dont care	if $a + b = B-1$ when $p(i) = 1$ $\text{not}(p(i))=0$

the original generate and propagate function

$g(a,b) = 1$	if $a + b > B-1$,
$g(a,b) = 0$	otherwise

$p(a,b) = 1$	if $a + b = B-1$,
$p(a,b) = 0$	otherwise

Synthesis of Arithmetic Circuits: FPGA, ASIC and Embedded Systems, J-P Deschamps et al

Relaxed $g(i)$ Examples

	0	1	2	3
0	0	1	2	3
1	1	2	3	4
2	2	3	4	5
3	3	4	5	6

$p(i)$	0	1	2	3
0	0	0	0	1
1	0	0	1	0
2	0	1	0	0
3	1	0	0	0

$g(i)$	0	1	2	3
0	0	0	0	0
1	0	0	0	1
2	0	0	1	1
3	0	1	1	1

Original $g(i)$: 4-ary

	0	1	2	3
0	0	1	2	3
1	1	2	3	4
2	2	3	4	5
3	3	4	5	6

$p(i)$	0	1	2	3
0	0	0	0	1
1	0	0	1	0
2	0	1	0	0
3	1	0	0	0

$g(i)$	0	1	2	3
0	0	0	0	X
1	0	0	X	1
2	0	X	1	1
3	X	1	1	1

Relaxed $g(i)$: 4-ary

	0	1
0	0	1
1	1	2

$p(i)$	0	1
0	0	1
1	1	0


$g(i)$	0	1
0	0	X
1	X	1

Relaxed $g(i)$: binary

Multiplexer Carry Chain

if $p(i)=1$ then $q(i+1):= q(i)$ else $q(i+1):=g(i)$; end if;
 
$$q(i+1) = p(i).q(i) \vee \text{not}(p(i)).g(i)$$



	0	1
0	0	1
1	1	2

$p(i)$	0	1
0	0	1
1	1	0

$g(i)$	0	1
0	0	X
1	X	1

References

[1] <http://en.wikipedia.org/>

[2] J-P Deschamps, et. al., “Sunthesis of Arithmetic Circuits”, 2006