

Combinational Circuit Background

Copyright (c) 2011 - 2015 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".

Please send corrections (or suggestions) to youngwlim@hotmail.com.


This document was produced by using OpenOffice and Octave.

Decoder

Decoder Truth Table


x	y	z	D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

inputs output

 


Truth Table and minterms


x	y	z	D_0
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

 


x	y	z	D_1
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

 


x	y	z	D_2
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

 

x	y	z	D_3
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

 

x	y	z	D_4
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

 


x	y	z	D_5
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0



x	y	z	D_6
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0



x	y	z	D_7
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

 

$$\bar{x}\bar{y}\bar{z} = D_0$$

$$\bar{x}\bar{y}z = D_1$$

$$\bar{x}y\bar{z} = D_2$$

$$\bar{x}yz = D_3$$

$$x\bar{y}\bar{z} = D_4$$

$$x\bar{y}z = D_5$$

$$xy\bar{z} = D_6$$

$$xyz = D_7$$

decoder.v

```
`timescale 1ns/100ps

module decoder();
  wire D0, D1, D2, D3, D4, D5, D6, D7;
  reg x, y, z;

  not (xb, x);
  not (yb, y);
  not (zb, z);

  and (D0, xb, yb, zb); // D0 = minterm m0
  and (D1, xb, yb, z ); // D1 = minterm m1
  and (D2, xb, y , zb); // D2 = minterm m2
  and (D3, xb, y , z ); // D3 = minterm m3
  and (D4, x , yb, zb); // D4 = minterm m4
  and (D5, x , yb, z ); // D5 = minterm m5
  and (D6, x , y , zb); // D6 = minterm m6
  and (D7, x , y , z ); // D7 = minterm m7

  // Testbench Code goes here
  initial begin
    $dumpfile("decoder.vcd");
    $dumpvars(0, decoder);

    $monitor ("[x y z] = %b%b%b [D0, D1, D2, D3]
              = %b%b%b%b%b%b%b%b%b",
              x, y, z, D0, D1, D2, D3, D4, D5, D6, D7);


    x = 0;
    y = 0;
    z = 0;

    #8 $finish;
  end

  always #4 x = ~x;
  always #2 y = ~y;
  always #1 z = ~z;

endmodule
```

decoder.v simulation

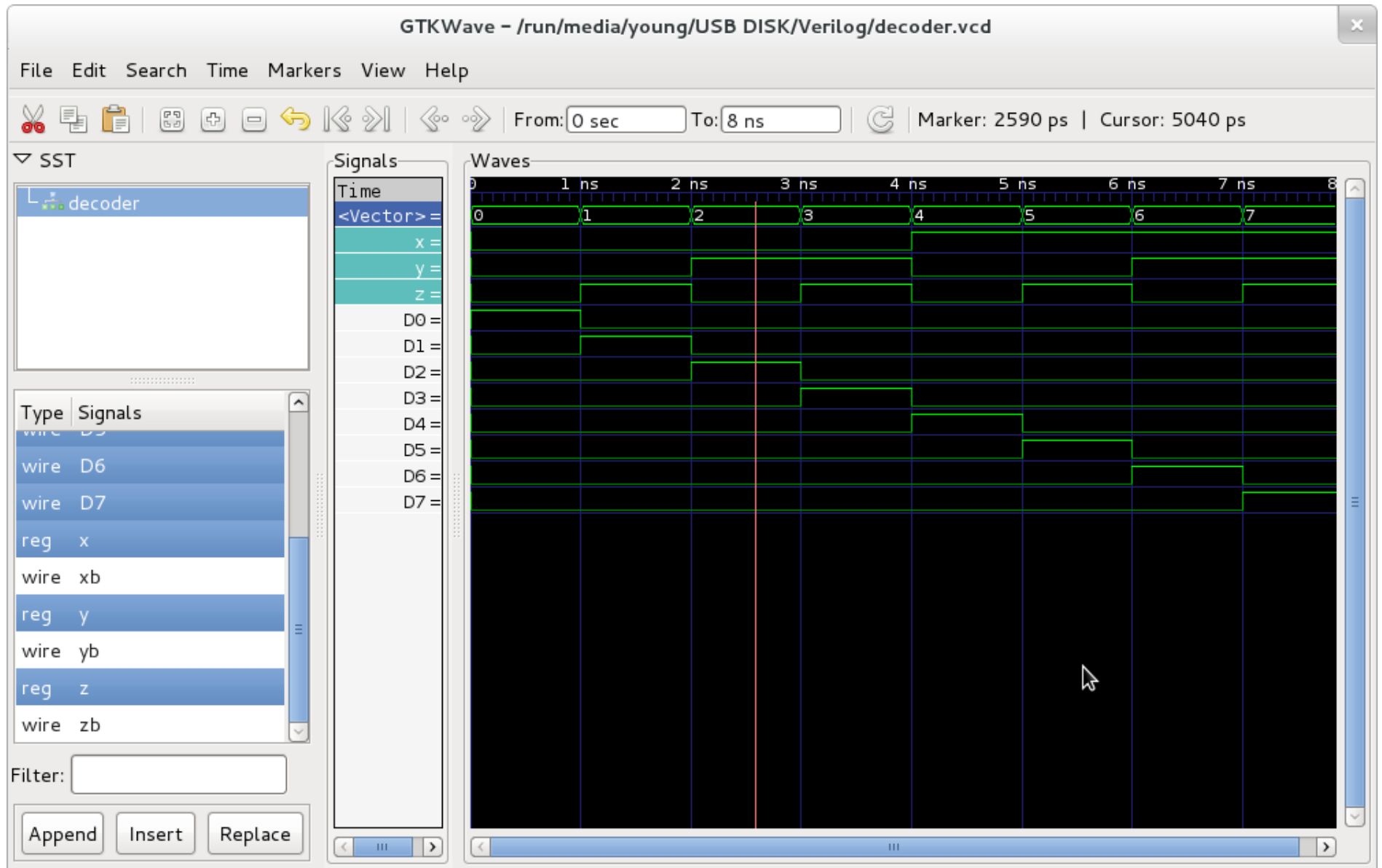

Behavioral Decoder


```
`timescale 1ns/100ps

module decoder(A, D);
  input [2:0] A;
  output [7:0] D;
  reg [7:0] D;


  always @(A)
  begin
    case (A)
      0: D = 8'b00000001;
      1: D = 8'b00000010;
      2: D = 8'b00000100;
      3: D = 8'b00001000;
      4: D = 8'b00010000;
      5: D = 8'b00100000;
      6: D = 8'b01000000;
      7: D = 8'b10000000;
      default: D = 8b'X;
    endcase
  end

endmodule
```


Decoder Schematic

 


Decoder Wavefpr,

 

	z.X	y.X	x.X	D0.X	D1.X	D2.X	D3.X	D4.X	D5.X	D6.X	D7.X
0000	0	0	0	1	0	0	0	0	0	0	0
0001	0	0	1	0	1	0	0	0	0	0	0
0010	0	1	0	0	0	1	0	0	0	0	0
0011	0	1	1	0	0	0	1	0	0	0	0
0100	1	0	0	0	0	0	0	1	0	0	0
0101	1	0	1	0	0	0	0	0	1	0	0
0110	1	1	0	0	0	0	0	0	0	1	0
0111	1	1	1	0	0	0	0	0	0	0	1
1000	0	0	0	1	0	0	0	0	0	0	0

Encoder



Truth Table

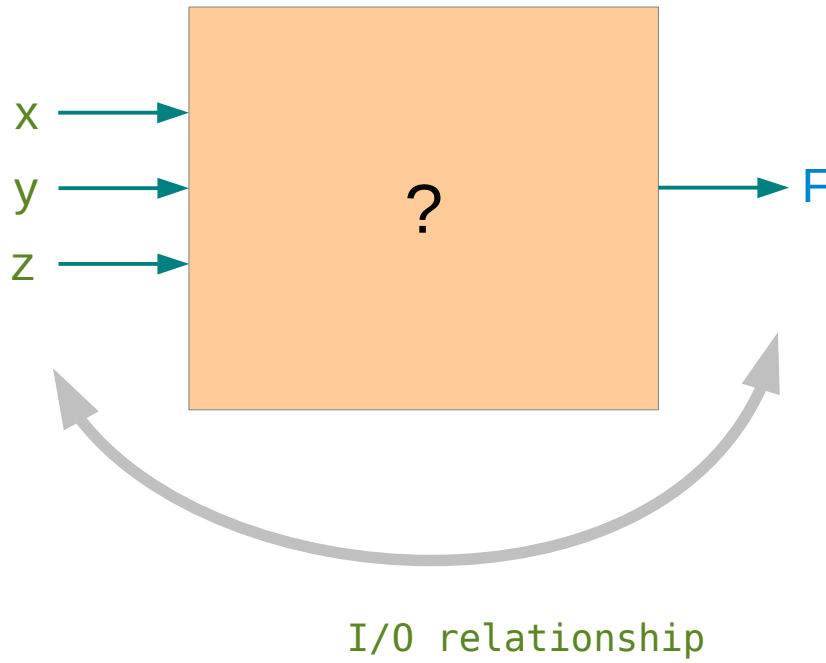

x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

inputs output


SOP and POS

  




Truth Table

D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7	x	y	z
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

inputs output

 

Truth Table and minterms

 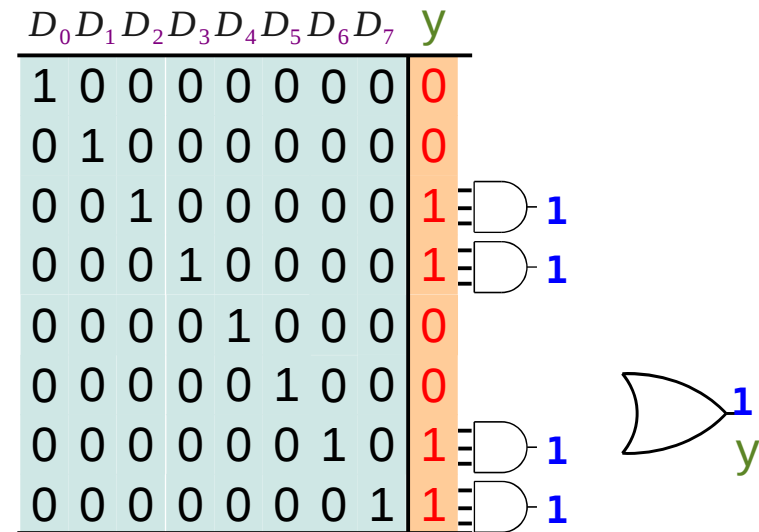 

Functions x, y, z




D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7	x	y	z
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

$$\bar{D}_0 \bar{D}_1 \bar{D}_2 \bar{D}_3 D_4 \bar{D}_5 \bar{D}_6 \bar{D}_7 + \bar{D}_0 \bar{D}_1 \bar{D}_2 \bar{D}_3 \bar{D}_4 D_5 \bar{D}_6 \bar{D}_7 + \bar{D}_0 \bar{D}_1 \bar{D}_2 \bar{D}_3 \bar{D}_4 \bar{D}_5 D_6 \bar{D}_7 + \bar{D}_0 \bar{D}_1 \bar{D}_2 \bar{D}_3 \bar{D}_4 \bar{D}_5 \bar{D}_6 D_7 = x$$

$$\bar{D}_0 \bar{D}_1 D_2 \bar{D}_3 \bar{D}_4 \bar{D}_5 \bar{D}_6 \bar{D}_7 + \bar{D}_0 \bar{D}_1 \bar{D}_2 D_3 \bar{D}_4 \bar{D}_5 \bar{D}_6 \bar{D}_7 + \bar{D}_0 \bar{D}_1 \bar{D}_2 \bar{D}_3 \bar{D}_4 \bar{D}_5 D_6 \bar{D}_7 + \bar{D}_0 \bar{D}_1 \bar{D}_2 \bar{D}_3 \bar{D}_4 \bar{D}_5 \bar{D}_6 D_7 = y$$

$$\bar{D}_0 D_1 \bar{D}_2 \bar{D}_3 \bar{D}_4 \bar{D}_5 \bar{D}_6 \bar{D}_7 + \bar{D}_0 \bar{D}_1 \bar{D}_2 D_3 \bar{D}_4 \bar{D}_5 \bar{D}_6 \bar{D}_7 + \bar{D}_0 \bar{D}_1 \bar{D}_2 \bar{D}_3 \bar{D}_4 D_5 \bar{D}_6 \bar{D}_7 + \bar{D}_0 \bar{D}_1 \bar{D}_2 \bar{D}_3 \bar{D}_4 \bar{D}_5 \bar{D}_6 D_7 = z$$

Another Functions x, y, z

 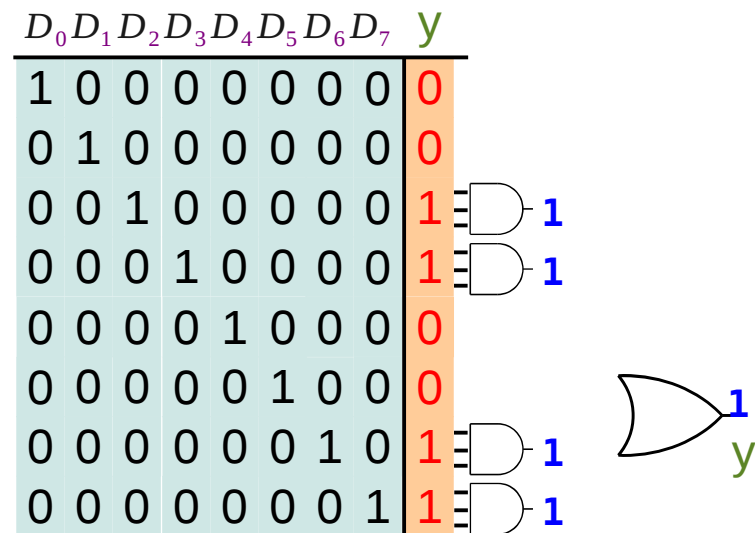 

$$D_4 + D_5 + D_6 + D_7 = x$$

$$D_2 + D_3 + D_6 + D_7 = y$$


$$D_1 + D_3 + D_5 + D_7 = z$$

Problems

D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7	x	y	z
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

inputs

output

 

Priority Encoder: Truth Table

D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7	x	y	z	v
1	0	0	0	0	0	0	0	0	0	0	1
X	1	0	0	0	0	0	0	0	0	1	1
X	X	1	0	0	0	0	0	0	1	0	1
X	X	X	1	0	0	0	0	0	1	1	1
X	X	X	X	1	0	0	0	1	0	0	1
X	X	X	X	X	1	0	0	1	0	1	1
X	X	X	X	X	X	1	0	1	1	0	1
X	X	X	X	X	X	X	1	1	1	1	1
0	0	0	0	0	0	0	0	X	X	X	0

inputs output

Priority Encoder: Truth Table

D_0	D_1	D_2	D_3	x	y	v
1	0	0	0	0	0	1
X	1	0	0	0	1	1
X	X	1	0	1	0	1
X	X	X	1	1	1	1
0	0	0	0	X	X	0

```

if (d3) xy=11
else if (d2) xy = 10;
else if (d1) xy = 01;
else if (d0) xy = 00;
    
```

D_0	D_1	D_2	D_3	x	y	v
1	0	0	0	0	0	1
0	1	0	0	0	1	1
1	1	0	0	0	1	1
0	0	1	0	1	0	1
0	1	1	0	1	0	1
1	0	1	0	1	0	1
1	1	1	0	1	0	1
0	0	0	1	1	1	1
0	0	1	1	1	1	1
0	1	0	1	1	1	1
0	1	1	1	1	1	1
1	0	0	1	1	1	1
1	0	1	1	1	1	1
1	1	0	1	1	1	1
1	1	1	1	1	1	1
0	0	0	0	X	X	0

D_0	D_1	D_2	D_3	x	y	v
0	0	0	0	X	X	0
0	0	0	1	1	1	1
0	0	1	0	1	0	1
0	0	1	1	1	1	1
0	1	0	0	0	1	1
0	1	0	1	1	1	1
0	1	1	0	1	0	1
0	1	1	1	1	1	1
1	0	0	0	0	0	1
1	0	0	1	1	1	1
1	0	1	0	1	0	1
1	0	1	1	1	1	1
1	1	0	0	0	1	1
1	1	0	1	1	1	1
1	1	1	0	1	0	1
1	1	1	1	1	1	1

Priority Encoder: Truth Table

X	1	1	1
0	1	1	1
0	1	1	1
0	1	1	1

$$x = D_2 + D_3$$

X	1	1	0
1	1	1	0
1	1	1	0
0	1	1	0

$$y = D_3 + D_1 \bar{D}_2$$

0	1	1	1
1	1	1	1
1	1	1	1
1	1	1	1

$$v = D_0 + D_1 + D_2 + D_3$$

D_0	D_1	D_2	D_3	x	y	v
0	0	0	0	X	X	0
0	0	0	1	1	1	1
0	0	1	0	1	0	1
0	0	1	1	1	1	1
0	1	0	0	0	1	1
0	1	0	1	1	1	1
0	1	1	0	1	0	1
0	1	1	1	1	1	1
1	0	0	0	0	0	1
1	0	0	1	1	1	1
1	0	1	0	1	0	1
1	0	1	1	1	1	1
1	1	0	0	0	1	1
1	1	0	1	1	1	1
1	1	1	0	1	0	1
1	1	1	1	1	1	1

pencoder.v

```
`timescale 1ns/100ps

// Testbench Code goes here
initial begin
    $dumpfile("pencoder.vcd");
    $dumpvars(0, pencoder);

    $monitor ("[D0, D1, D2, D3] = %b %b %b %b [x y] = %b %b v = %b",
        D0, D1, D2, D3, x, y, v);

    D0 = 0;
    D1 = 0;
    D2 = 0;
    D3 = 0;

    #16 $finish;
end

always #8 D0 = ~D0;
always #4 D1 = ~D1;
always #2 D2 = ~D2;
always #1 D3 = ~D3;

module pencoder();
    reg D0, D1, D2, D3;
    wire P;

    //Invert the sel signals
    not (D2b, D2);

    // 3-input AND gate
    and (P, D1, D2b);

    or (x, D2, D3);
    or (y, D3, P);
    or (v, D0, D1, D2, D3);

endmodule
```

pencoder.v

```
`timescale 1ns/100ps

module pencoder();
  reg D0, D1, D2, D3;
  wire P;


  //Invert the sel signals
  not (D2b, D2);

  // 3-input AND gate
  and (P, D1, D2b);

  or (x, D2, D3);
  or (y, D3, P);
  or (v, D0, D1, D2, D3);
endmodule

/*
#1 {D0,D1,D2,D3} = 4'b0000; // 0
#1 {D0,D1,D2,D3} = 4'b0001; // 1
#1 {D0,D1,D2,D3} = 4'b0010; // 2
#1 {D0,D1,D2,D3} = 4'b0011; // 3
#1 {D0,D1,D2,D3} = 4'b0100; // 4
#1 {D0,D1,D2,D3} = 4'b0101; // 5
#1 {D0,D1,D2,D3} = 4'b0110; // 6
#1 {D0,D1,D2,D3} = 4'b0111; // 7
#1 {D0,D1,D2,D3} = 4'b1000; // 8
#1 {D0,D1,D2,D3} = 4'b1001; // 9
#1 {D0,D1,D2,D3} = 4'b1010; // 10
#1 {D0,D1,D2,D3} = 4'b1011; // 11
#1 {D0,D1,D2,D3} = 4'b1100; // 12
#1 {D0,D1,D2,D3} = 4'b1101; // 13
#1 {D0,D1,D2,D3} = 4'b1110; // 14
#1 {D0,D1,D2,D3} = 4'b1111; // 15
*/
```

Priority Encoder: Truth Table

 

binary encoder

```
module encoder(D, E);  
  
input [7:0] D;  
output [2:0] E;  
reg [2:0] E;  
  
always @(D)  
begin  
    if (D == 8'b00000001) E = 0;  
    else if (D == 8'b00000010) E = 1;  
    else if (D == 8'b00000100) E = 2;  
    else if (D == 8'b00001000) E = 3;  
    else if (D == 8'b00010000) E = 4;  
    else if (D == 8'b00100000) E = 5;  
    else if (D == 8'b01000000) E = 6;  
    else if (D == 8'b10000000) E = 7;  
    else E = 3'bX;  
end  
  
endmodule
```

priority encoder

```
module pencoder(D, E);
```

```
input [7:0] D;
```

```
output [2:0] E;
```

```
reg [2:0] E;
```

```
always @(D)
```

```
begin
```

```
    if (D[0]) E = 0;
```

```
    else if (D[1]) E = 1;
```

```
    else if (D[2]) E = 2;
```

```
    else if (D[3]) E = 3;
```

```
    else if (D[4]) E = 4;
```

```
    else if (D[5]) E = 5;
```

```
    else if (D[6]) E = 6;
```

```
    else if (D[7]) E = 7;
```

```
    else E = 3'bX;
```

```
end
```

```
endmodule
```


Multiplexer

Simple Gates

```
module gates();  
    wire out0;  
    wire out1;  
    wire out2;  
  
    reg in1, in2, in3, in4;  
  
    not U1 (out0, in1);  
    and U2 (out1, in1, in2, in3, in4);  
    xor U3 (out2, in1, in2, in3);  
  
    initial begin  
        $dumpfile("gates.vcd");  
        $dumpvars(0, gates);  
  
        $monitor(  
            "in1=%b in2=%b in3=%b in4=%b out0=%b out1=%b out2=%b",  
            in1,in2,in3,in4, out0,out1,out2);  
  
        in1 = 0;  
        in2 = 0;  
        in3 = 0;  
        in4 = 0;  
  
        #1 in1 = 1;  
        #1 in2 = 1;  
        #1 in3 = 1;  
        #1 in4 = 1;  
        #1  
  
        $finish;  
    end  
  
endmodule
```

from www.asic-world.com

Simple Gates

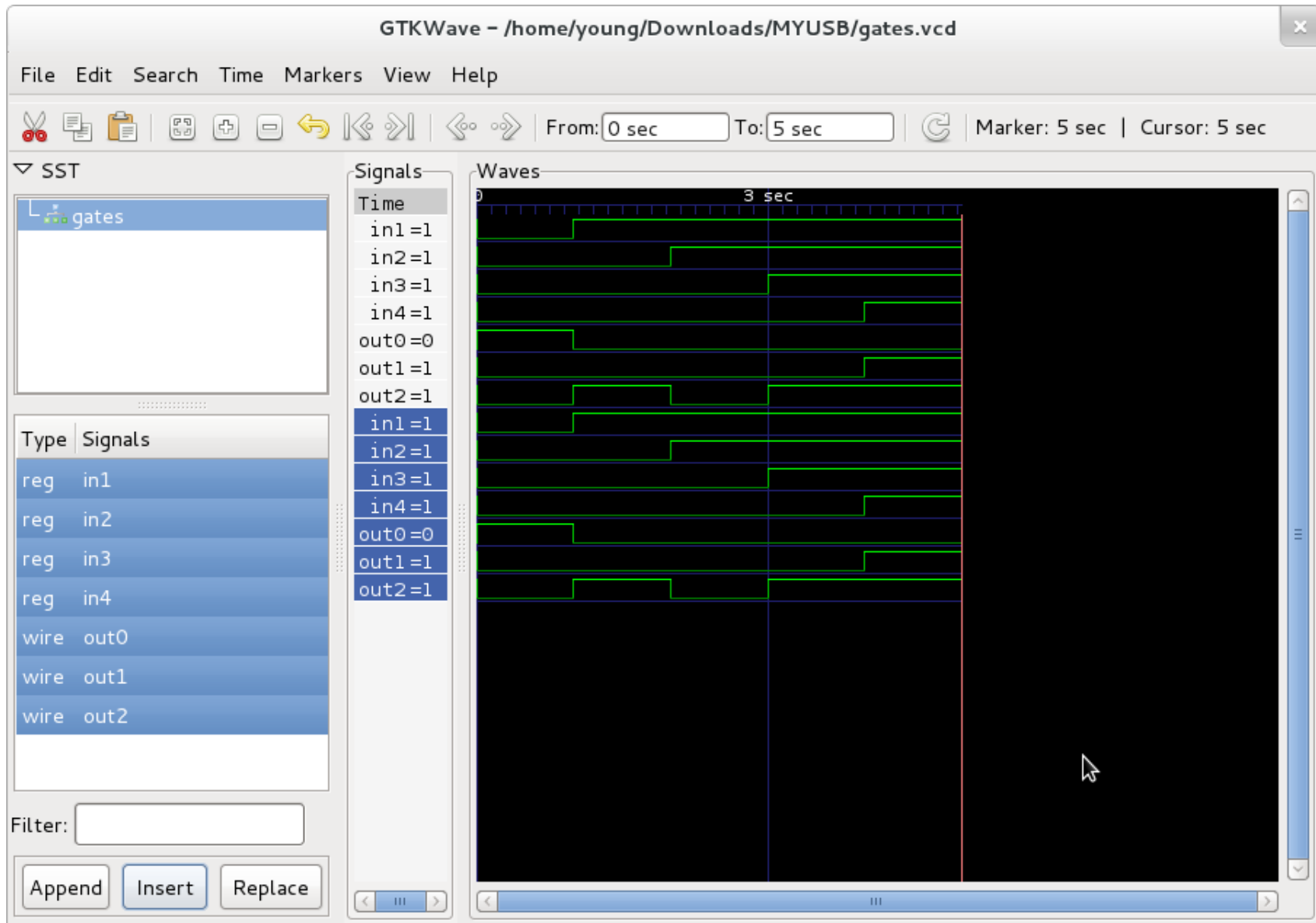

Multiplexer

```
module mux_from_gates ();
  reg c0,c1,c2,c3, A,B;
  wire Y;

  //Invert the sel signals
  not (a_inv, A);
  not (b_inv, B);

  // 3-input AND gate
  and (y0, c0, a_inv, b_inv); // 00
  and (y1, c1, a_inv, B);    // 01
  and (y2, c2, A,    b_inv); // 10
  and (y3, c3, A,    B);     // 11

  // 4-input OR gate
  or (Y, y0, y1, y2, y3);

  initial begin
    $dumpfile("mux.vcd");
    $dumpvars(0,mux_from_gates);

    $monitor (
      "c0 = %b c1 = %b c2 = %b c3 = %b A = %b B = %b Y = %b",
      c0, c1, c2, c3, A, B, Y);


    c0 = 0;
    c1 = 0;
    c2 = 0;
    c3 = 0;
    A = 0;
    B = 0;

    #1 A = 1;
    #2 B = 1;
    #4 A = 0;
    #8 $finish;
  end

  always #1 c0 = ~c0;
  always #2 c1 = ~c1;
  always #3 c2 = ~c2;
  always #4 c3 = ~c3;
endmodule
```

from www.asic-world.com

Multiplexer

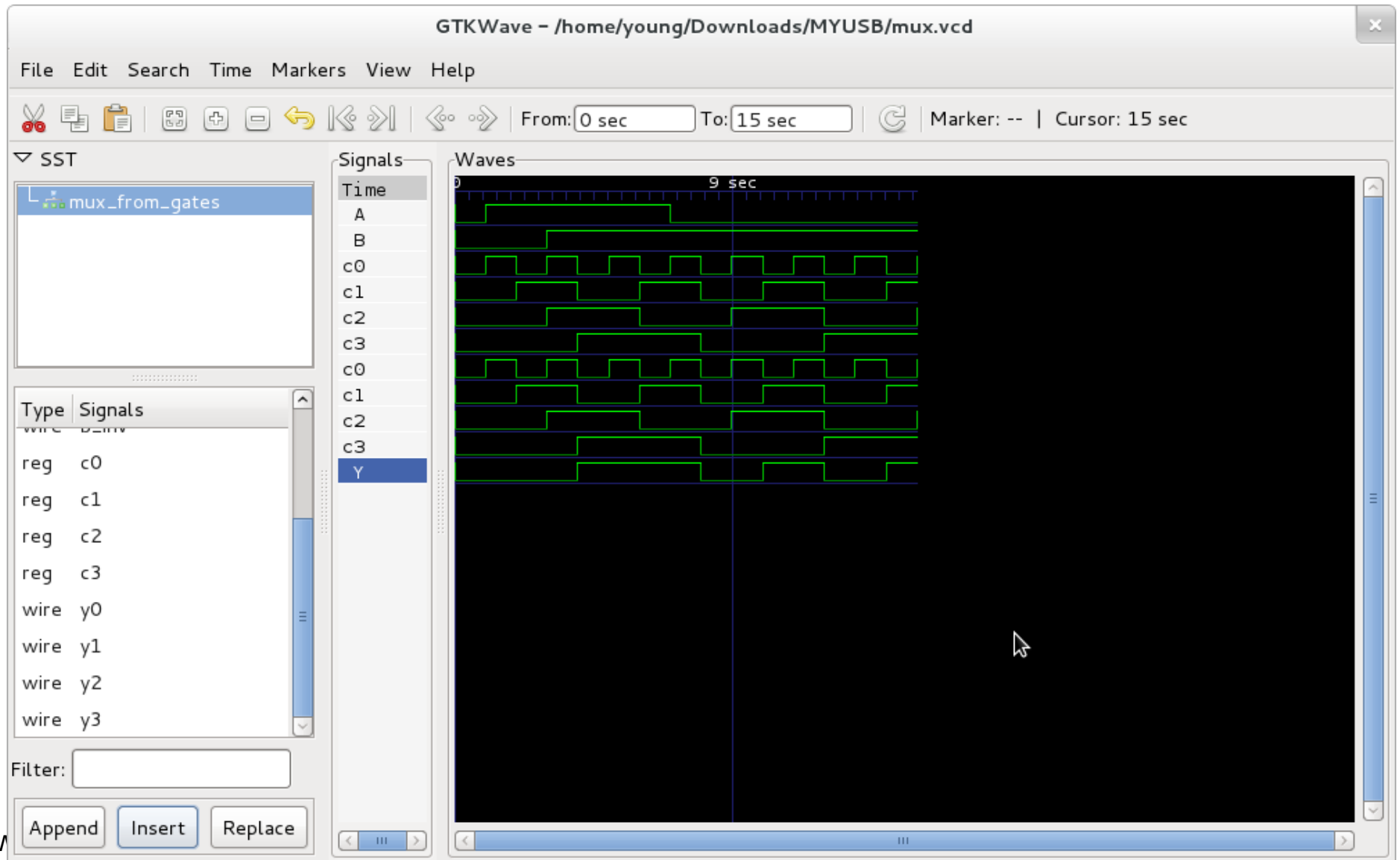

from v

Multiplexer


```
module mux(sel, D0, D1, D2, D3, Y)
  input [1:0] sel;
  input D0, D1, D2, D3;
  output Y;
  reg Y;

  always @(sel or D0 or D1 or D2 or D3)
    case (sel)
      2'b00 : Y = D0;
      2'b01 : Y = D1;
      2'b10 : Y = D2;
      2'b11 : Y = D3;
      default: Y = D0;
    endcase

endmodule
```

from www.asic-world.com

Multiplexer Schematic

 


Adder (RCA)


Truth Table

x	y	C_i	C_o	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


inputs output

 

SOP



 

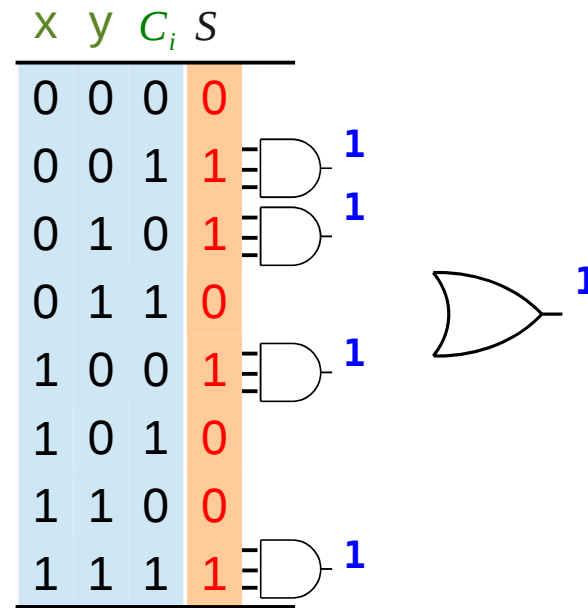
$$C_o = \bar{x}yC_i + x\bar{y}C_i + xy\bar{C}_i + xyC_i$$




$$S = \bar{x}\bar{y}C_i + \bar{x}y\bar{C}_i + x\bar{y}\bar{C}_i + xyC_i$$

K-Map

  
 


$$C_o = yC_i + xC_i + xy$$

 

$$S = \bar{x}\bar{y}C_i + \bar{x}y\bar{C}_i + x\bar{y}\bar{C}_i + xyC_i$$

Boolean Algebra

  


$$C_o = yC_i + xC_i + xy$$

$$S = \bar{x}\bar{y}C_i + \bar{x}y\bar{C}_i + x\bar{y}\bar{C}_i + xyC_i$$

$$\begin{aligned} C_o &= (x + y)C_i + xy \\ &= (\bar{x}y + x\bar{y} + xy)C_i + xy \\ &= (\bar{x}y + x\bar{y})C_i + xy(C_i + 1) \\ &= (x \oplus y)C_i + xy \end{aligned}$$


$$\begin{aligned} S &= (\bar{x}\bar{y} + xy)C_i + (\bar{x}y + x\bar{y})\bar{C}_i \\ &= \overline{(x \oplus y)}C_i + (x \oplus y)\bar{C}_i \\ &= (x \oplus y) \oplus C_i \end{aligned}$$

Boolean Algebra

 


$$C_o = yC_i + xC_i + xy$$
 
$$\begin{aligned} C_o &= (x + y)C_i + xy \\ &= (\bar{x}y + x\bar{y} + xy)C_i + xy \\ &= (\bar{x}y + x\bar{y})C_i + xy(C_i + 1) \\ &= (x \oplus y)C_i + xy \end{aligned}$$




$$S = \bar{x}\bar{y}C_i + \bar{x}y\bar{C}_i + x\bar{y}\bar{C}_i + xyC_i$$

 
$$\begin{aligned} S &= (\bar{x}\bar{y} + xy)C_i + (\bar{x}y + x\bar{y})\bar{C}_i \\ &= \overline{(x \oplus y)}C_i + (x \oplus y)\bar{C}_i \\ &= (x \oplus y) \oplus C_i \end{aligned}$$



Full Adder in Qucs

 

4-Bit Adder in Qucs

 

adder_tb.v

```
`timescale 1ns/100ps

module adder_tb;

reg signed [3:0] i, j, k, flag;

wire signed [3:0] S;

adder4 A4 (i, j, 1'b0, Co, S);

initial
begin
    $dumpfile("test.vcd");
    $dumpvars(0, adder_tb);
end

initial
begin
    i = -4'd8;
    j = -4'd8;

    repeat (16)
    begin
        repeat (16)
        begin
            k = i + j;

            flag = {i[3], j[3], k[3]};
            #1

            if ((flag == 3'b110) || (flag == 3'b001))
                $display("i=%d j=%d k=%d S=%d OV", i , j, k, S);
            else
                $display("i=%d j=%d k=%d S=%d", i , j, k, S);

            j = j + 4'b1;
        end
        i = i + 4'b1;
    end
end // initial begin

endmodule
```

adder4.v, fa_gate.v fa_flow.v

adder4.v

```
module adder4(A, B, Ci, Co, S);
  input [3:0] A, B;
  input Ci;

  output Co;
  output [3:0] S;

  wire[3:1] C;

  fa fa0 (A[0], B[0], Ci, C[1], S[0]);
  fa fa1 (A[1], B[1], C[1], C[2], S[1]);
  fa fa2 (A[2], B[2], C[2], C[3], S[2]);
  fa fa3 (A[3], B[3], C[3], Co, S[3]);

endmodule
```

```
iverilog adder_tb.v adder4.v fa_gate.v
vvp a.out
```

```
iverilog adder_tb.v adder4.v fa_flow.v
vvp a.out
```

fa_gate.v

```
module fa(a, b, c, Co, S);
  input a, b, c;
  output Co, S;

  wire P, S, G, PC;

  xor #0.1 U1 (P, a, b);
  xor #0.1 U2 (S, P, c);
  and #0.1 U3 (G, a, b);
  and #0.1 U4 (PC, P, c);
  or #0.1 U5 (Co, G, PC);
endmodule
```

fa_flow.v

```
module fa(a, b, c, Co, S);
  input a, b, c;
  output Co, S;

  wire P, S, G, PC;

  assign #0.1 P = a ^ b;
  assign #0.1 S = P ^ c;
  assign #0.1 G = a & b;
  assign #0.1 PC = P & c;
  assign #0.1 Co = G | PC;
endmodule
```

adder4.v, fa_behav.v, fa_arith.v

adder4.v

```
module adder4(A, B, Ci, Co, S);  
  input [3:0] A, B;  
  input Ci;
```

```
  output Co;  
  output [3:0] S;
```

```
  wire[3:1] C;
```

```
  fa fa0 (A[0], B[0], Ci, C[1], S[0]);  
  fa fa1 (A[1], B[1], C[1], C[2], S[1]);  
  fa fa2 (A[2], B[2], C[2], C[3], S[2]);  
  fa fa3 (A[3], B[3], C[3], Co, S[3]);
```

```
endmodule
```

```
iverilog adder_tb.v adder4.v fa_behav.v  
vvp a.out
```

```
iverilog adder_tb.v adder4.v fa_arith.v  
vvp a.out
```

fa_behav.v

```
module fa(a, b, c, Co, S);  
  input a, b, c;  
  output Co, S;
```

```
  reg P, S, G, PC, Co;
```

```
  always @(a or b)  
    #0.1 P = a ^ b;
```

```
  always @(P or c)  
    #0.1 S = P ^ c;
```

```
  always @(a or b)  
    #0.1 G = a & b;
```

```
  always @(P or c)  
    #0.1 PC = P & c;
```

```
  always @(G or PC)  
    #0.1 Co = G | PC;
```

```
endmodule
```

fa_arith.v

```
module fa(a, b, c, Co, S);  
  input a, b, c;  
  output Co, S;
```

```
  reg S, Co;
```

```
  always @(a or b or c)  
    #0.1 {Co, S} = a + b + c;
```

```
endmodule
```

Output

```
[young@ubook Workspace]$ iverilog adder_tb.v adder4.v fa_gate.v
```


```
[young@ubook Workspace]$ vvp a.out
```

```
VCD info: dumpfile test.vcd opened for output.
```


```
i=-8 j=-8 k= 0 S= 0 OV  
i=-8 j=-7 k= 1 S= 1 OV  
i=-8 j=-6 k= 2 S= 2 OV  
i=-8 j=-5 k= 3 S= 3 OV  
i=-8 j=-4 k= 4 S= 4 OV  
i=-8 j=-3 k= 5 S= 5 OV  
i=-8 j=-2 k= 6 S= 6 OV  
i=-8 j=-1 k= 7 S= 7 OV  
i=-8 j= 0 k=-8 S=-8  
i=-8 j= 1 k=-7 S=-7  
i=-8 j= 2 k=-6 S=-6  
i=-8 j= 3 k=-5 S=-5  
i=-8 j= 4 k=-4 S=-4  
i=-8 j= 5 k=-3 S=-3  
i=-8 j= 6 k=-2 S=-2  
i=-8 j= 7 k=-1 S=-1  
i=-7 j=-8 k= 1 S= 1 OV  
i=-7 j=-7 k= 2 S= 2 OV  
i=-7 j=-6 k= 3 S= 3 OV  
i=-7 j=-5 k= 4 S= 4 OV  
i=-7 j=-4 k= 5 S= 5 OV  
i=-7 j=-3 k= 6 S= 6 OV  
i=-7 j=-2 k= 7 S= 7 OV
```

```
i=-7 j=-1 k=-8 S=-8  
i=-7 j= 0 k=-7 S=-7  
i=-7 j= 1 k=-6 S=-6  
i=-7 j= 2 k=-5 S=-5  
i=-7 j= 3 k=-4 S=-4  
i=-7 j= 4 k=-3 S=-3  
i=-7 j= 5 k=-2 S=-2  
i=-7 j= 6 k=-1 S=-1  
i=-7 j= 7 k= 0 S= 0  
i=-6 j=-8 k= 2 S= 2 OV  
i=-6 j=-7 k= 3 S= 3 OV  
i=-6 j=-6 k= 4 S= 4 OV  
i=-6 j=-5 k= 5 S= 5 OV  
i=-6 j=-4 k= 6 S= 6 OV  
i=-6 j=-3 k= 7 S= 7 OV  
i=-6 j=-2 k=-8 S=-8  
i=-6 j=-1 k=-7 S=-7  
i=-6 j= 0 k=-6 S=-6  
i=-6 j= 1 k=-5 S=-5  
i=-6 j= 2 k=-4 S=-4  
i=-6 j= 3 k=-3 S=-3  
i=-6 j= 4 k=-2 S=-2
```

Waveform (1)

 

Waveform (2)

 

\$dumpvars()

`$dumpfile("filename.vcd")`

`$dumpvar` dumps all variables in the design.

`$dumpvar(1, top)` dumps all the variables in module top, but not modules instantiated in top.

`$dumpvar(2, top)` dumps all the variables in module top and 1 level below.

`$dumpvar(n, top)` dumps all the variables in module top and n-1 levels below.

`$dumpvar(0, top)` dumps all the variables in module top and all level below.

`$dumpon` initiates the dump.

`$dumpoff` stop dumping.

NAME

vvp - Icarus Verilog vvp runtime engine

SYNOPSIS

```
vvp [-sv] [-Mpath] [-mmodule] [-llogfile] inputfile [extended-args...]
```

DESCRIPTION

vvp is the run time engine that executes the default compiled form generated by Icarus Verilog. The output from the iverilog command is not by itself executable on any platform. Instead, the vvp program is invoked to execute the generated output file.

References

- [1] <http://en.wikipedia.org/>
- [2] M. M. Mano, C. R. Kime, “Logic and Computer Design Fundamentals”, 4th ed.
- [3] J. Stephenson, Understanding Metastability in FPGAs. Altera Corporation white paper. July 2009.