

BJT Topologies - Basic Bias


Copyright (c) 2012 - 2017 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".


Please send corrections (or suggestions) to youngwlim@hotmail.com.

This document was produced by using OpenOffice and Octave.


BJT Amplifier Topologies

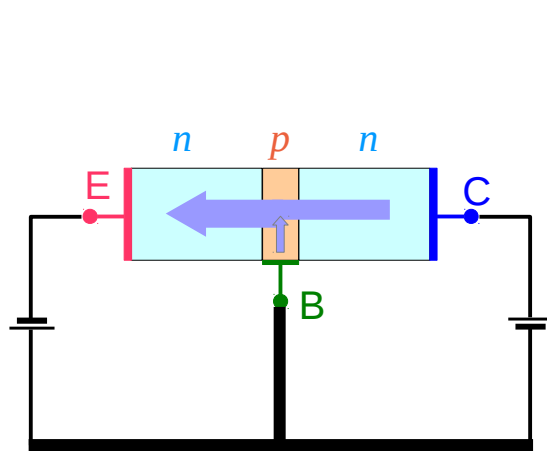


Common Base

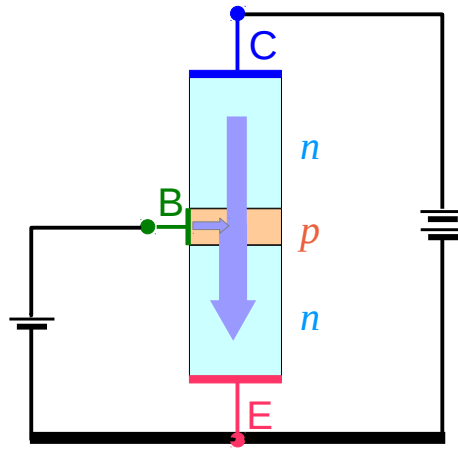


Common Emitter

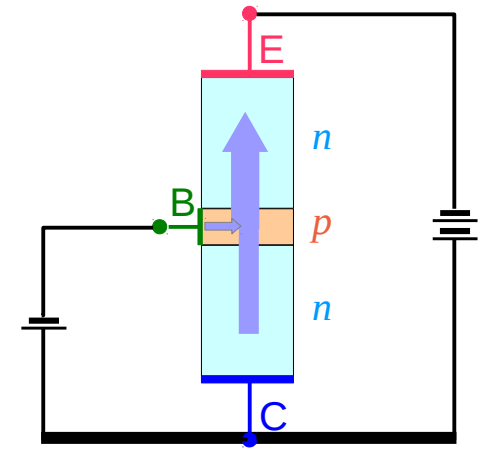


Common Collector

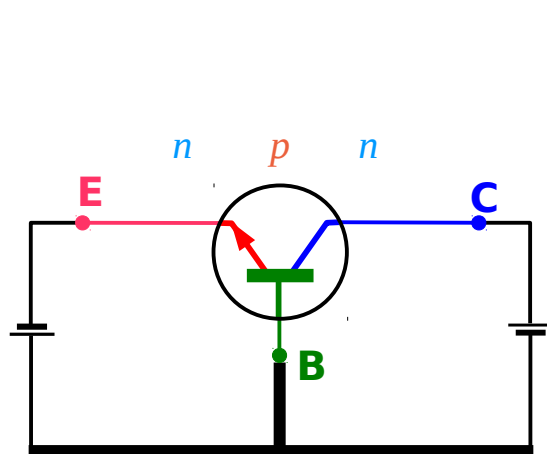

Common Base

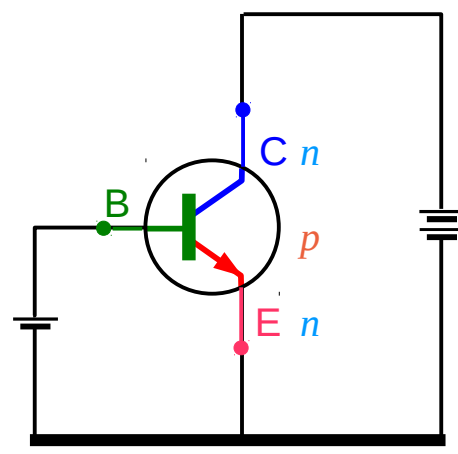


Common Emitter

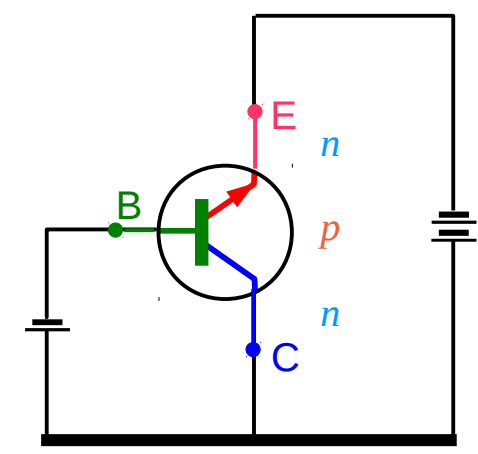


Common Collector

Common Base Topology

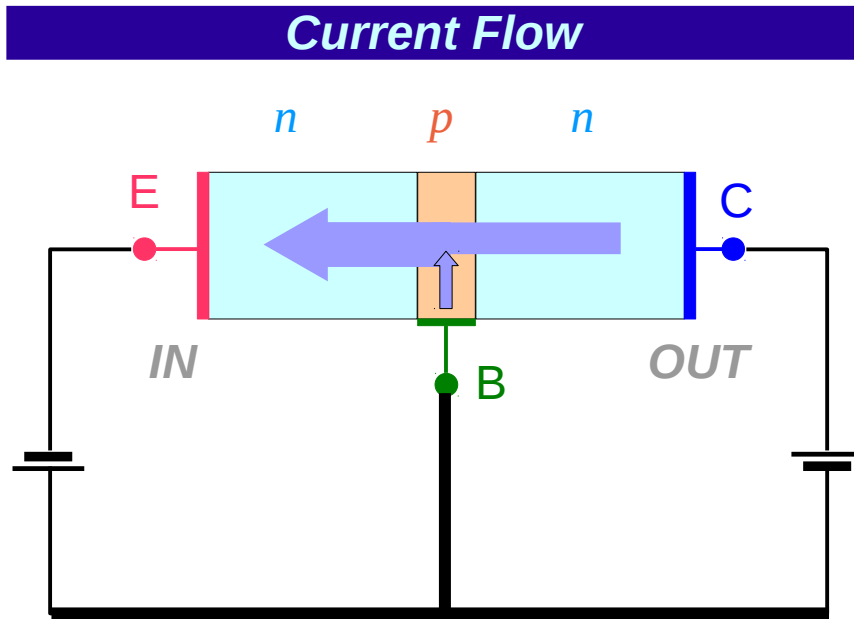


Common Base

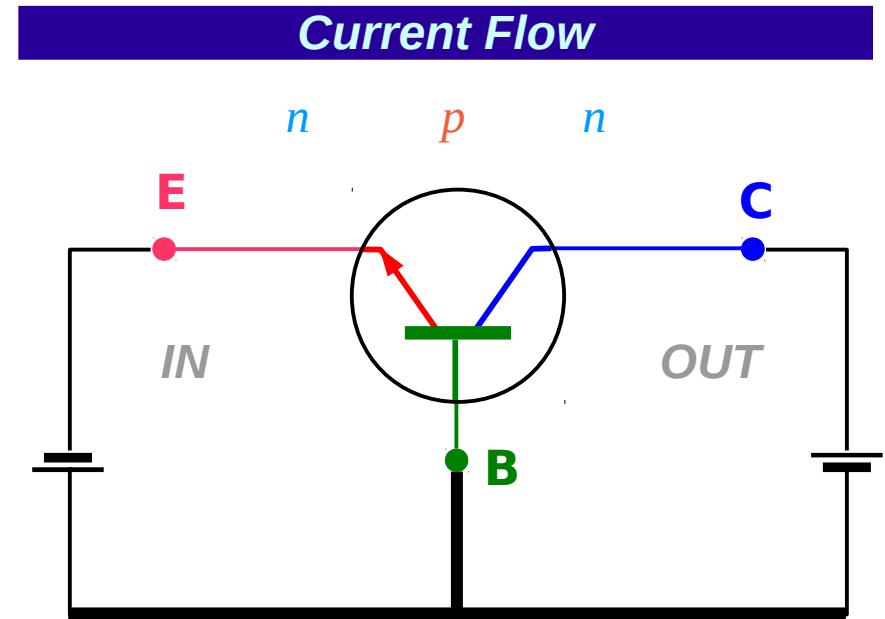

Common Base


Common Emitter Topology

Current Flow

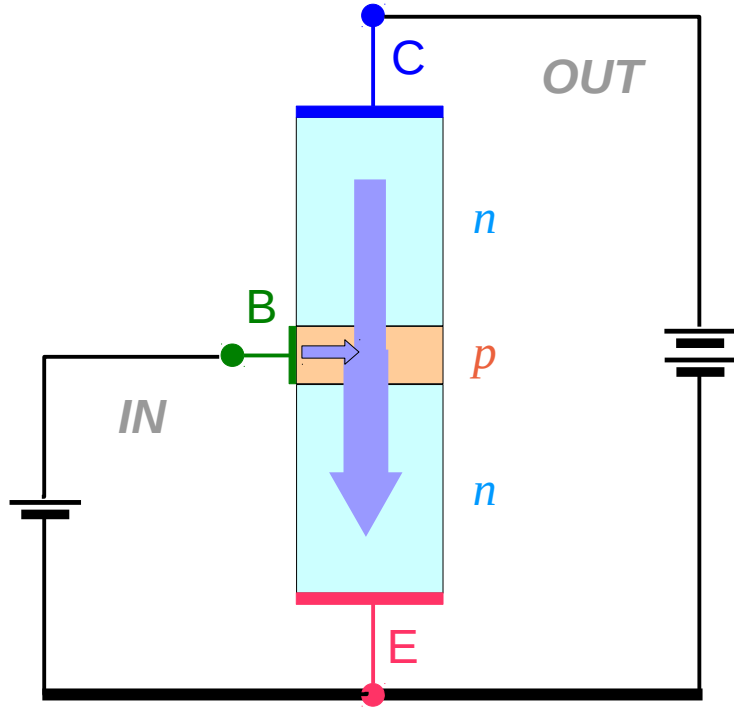

Common Emitter


Current Flow

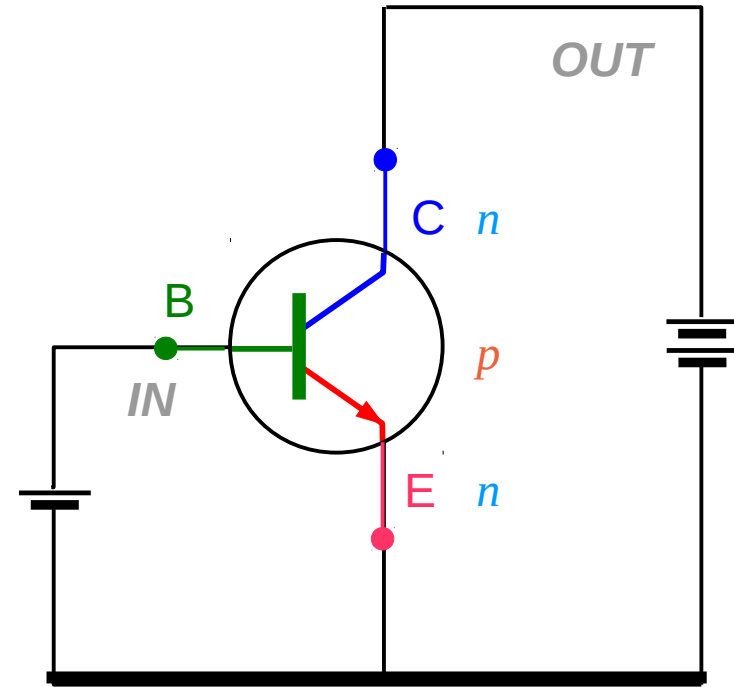

Common Emitter


Common Collector Topology

Current Flow

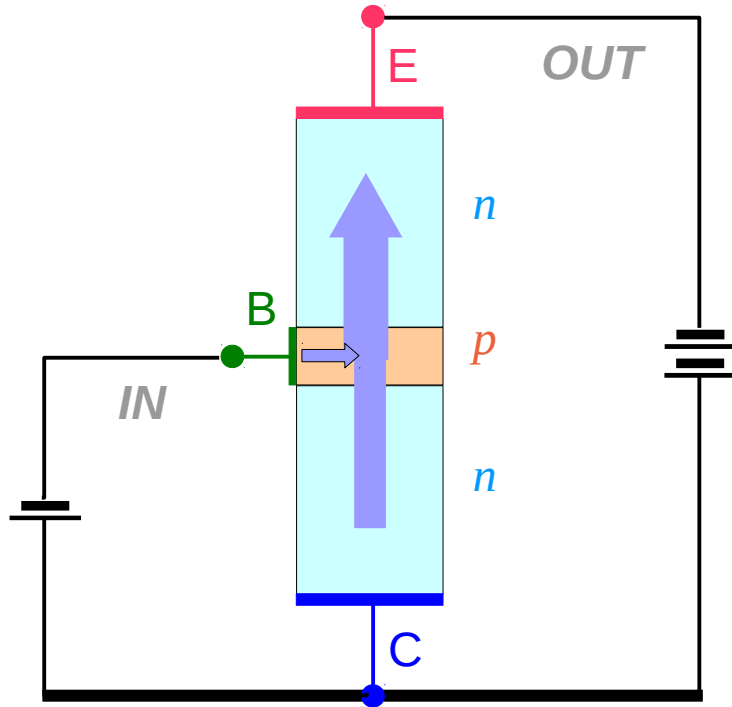

Common Collector


Current Flow

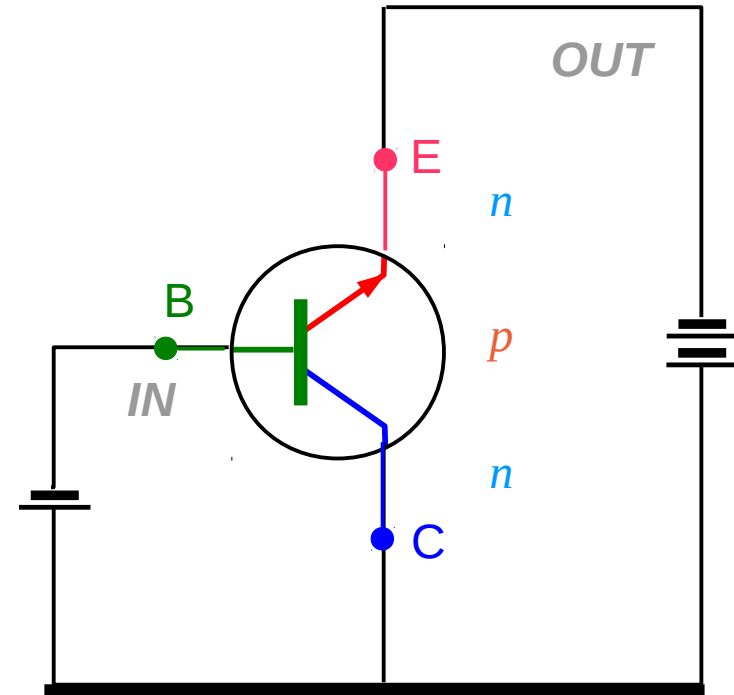


Common Collector

Forward bias (BE) & Reverse bias (CB)





Common Base

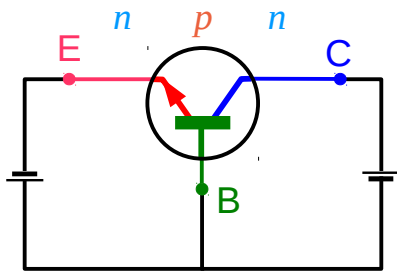

Common Emitter

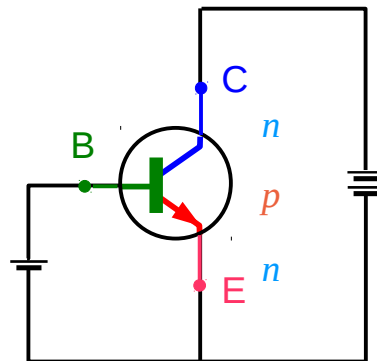

Common Collector

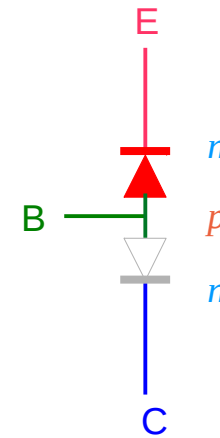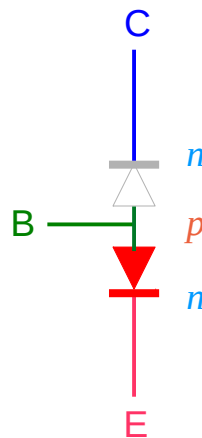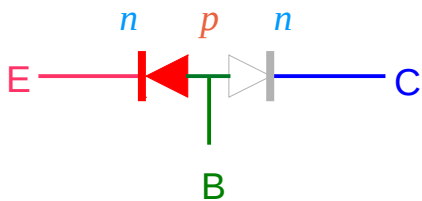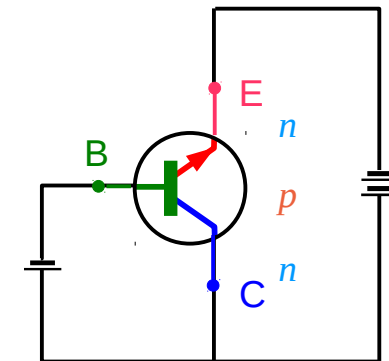

V_{BE} forward bias
 V_{CB} reverse bias


==

V_{BE} forward bias
 V_{CB} reverse bias


==

V_{BE} forward bias
 V_{CB} reverse bias


Bias for Active Region

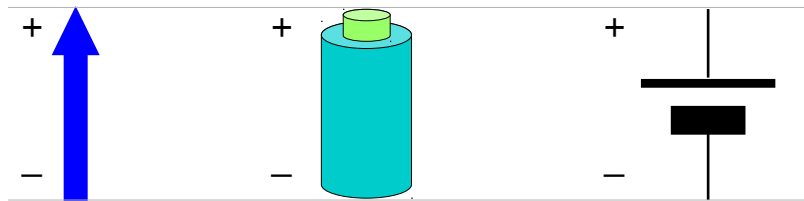


Common Base

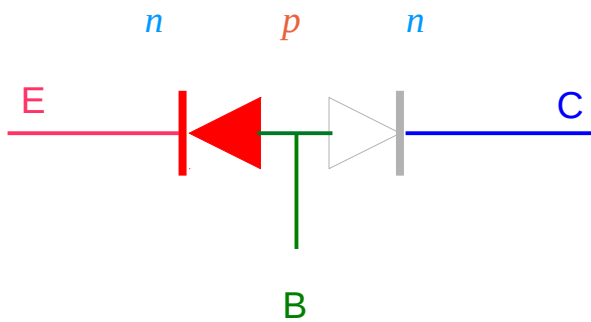

Common Emitter

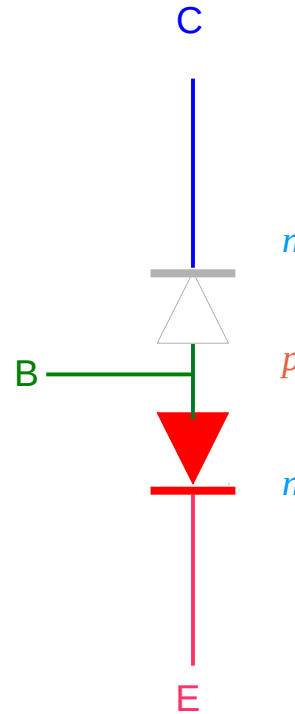

Common Collector

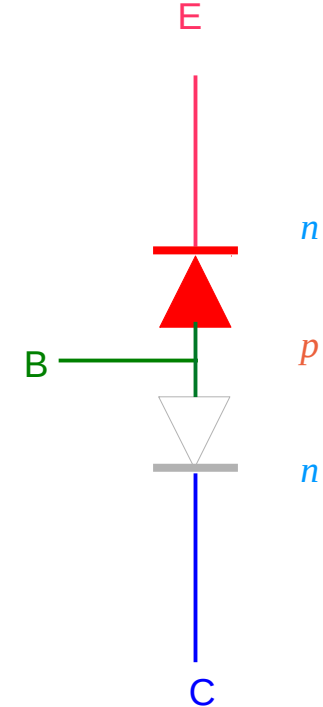

V_{BE} forward bias
 V_{CB} reverse bias

Active region

==

V_{BE} forward bias
 V_{CB} reverse bias


Active region

==

V_{BE} forward bias
 V_{CB} reverse bias

Active region


Common Base

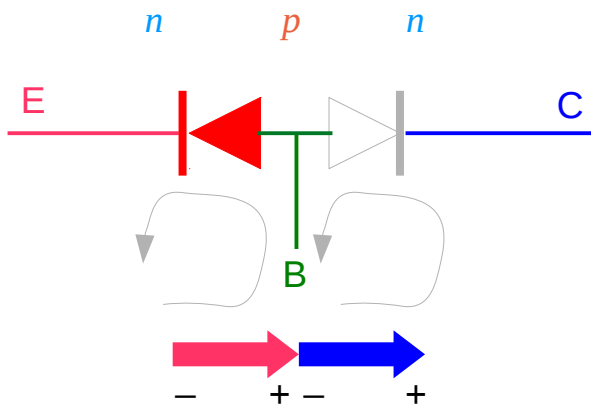

V_{BE} forward bias
 V_{CB} reverse bias

Active region


Common Emitter

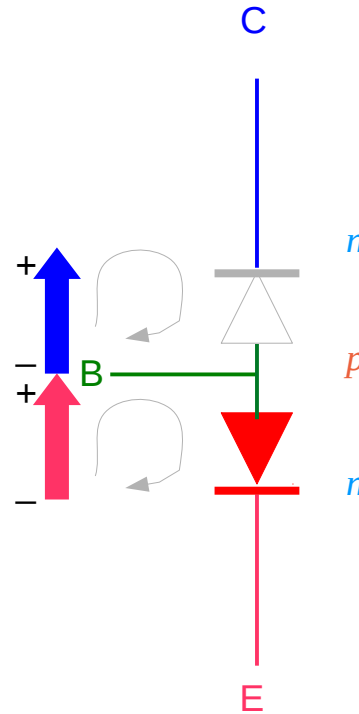

V_{BE} forward bias
 V_{CB} reverse bias

Active region

Common Collector

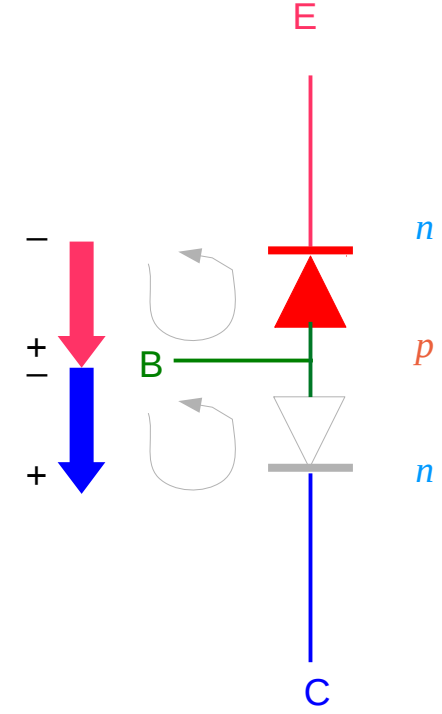



V_{BE} forward bias
 V_{CB} reverse bias

Active region

Polarities of Two voltage supplies

Active Region



Common Base

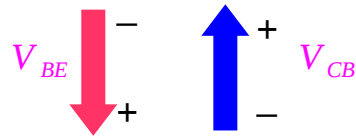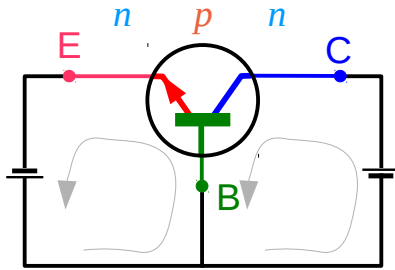

V_{BE} forward bias
 V_{CB} reverse bias

Active region



Common Emitter

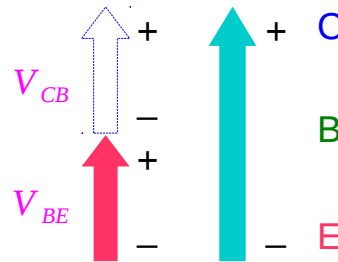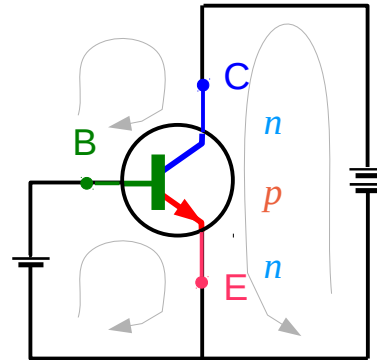

V_{BE} forward bias
 V_{CB} reverse bias

Active region

Common Collector

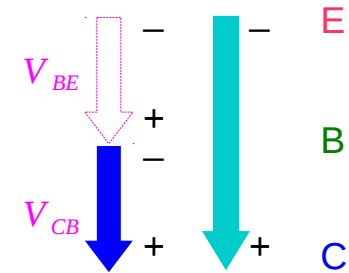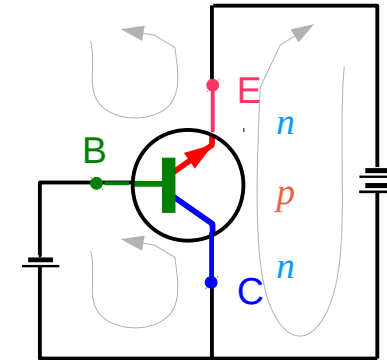


V_{BE} forward bias
 V_{CB} reverse bias

Active region


Two voltage supplies Bias

Active Region



Common Base

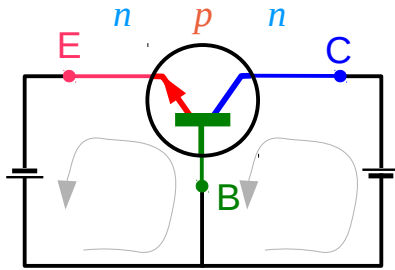

Common Emitter

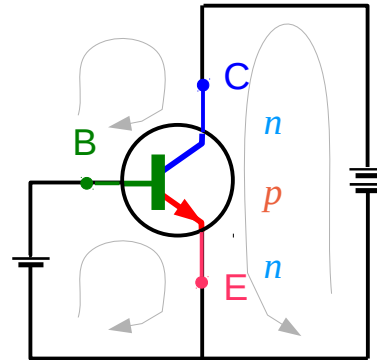


Common Collector

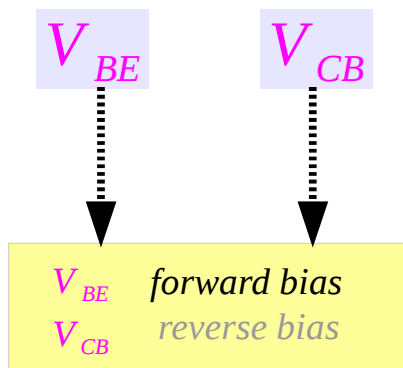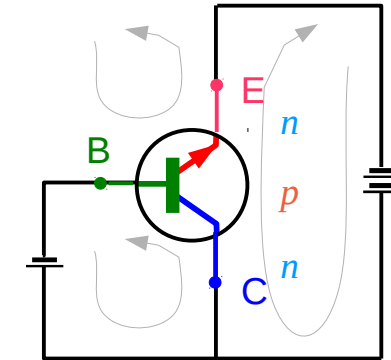


Active region

=

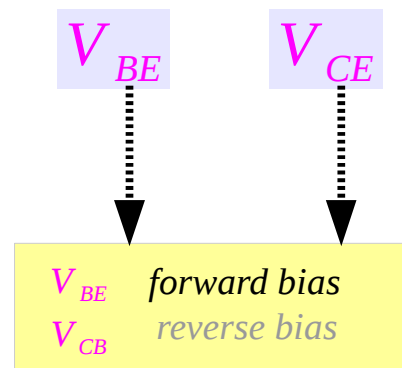


Active region

=

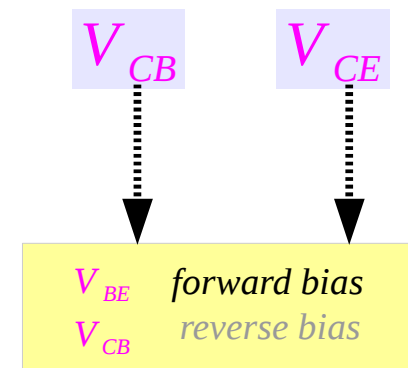


Active region


Common Base

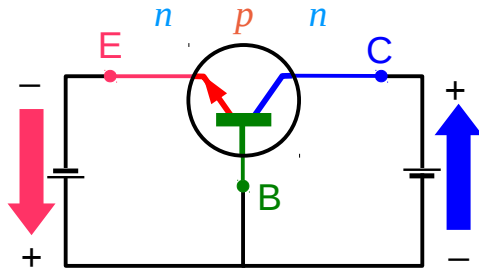


Direct Control

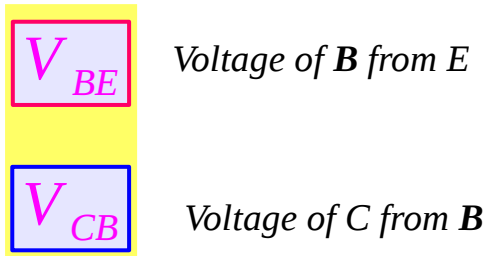


Common Emitter

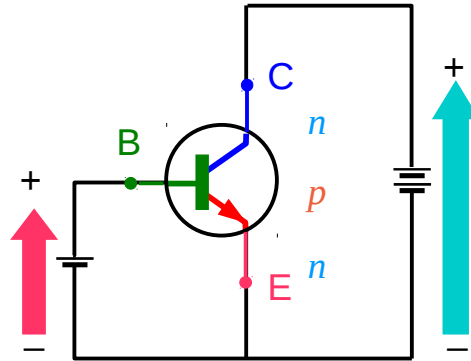


Indirect Control

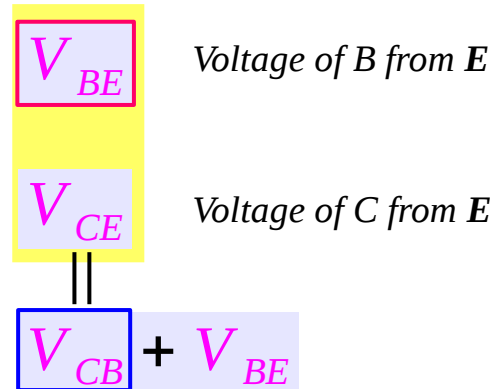



Common Collector

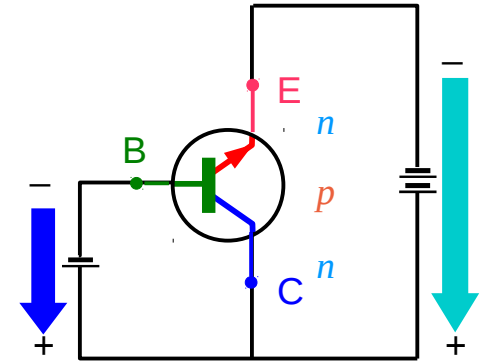


Indirect Control

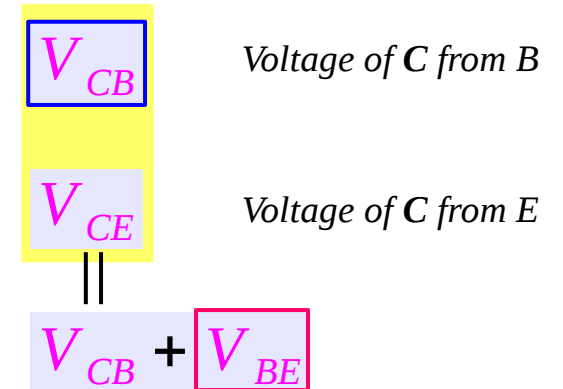

Input Characteristics

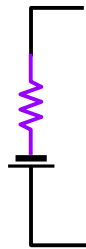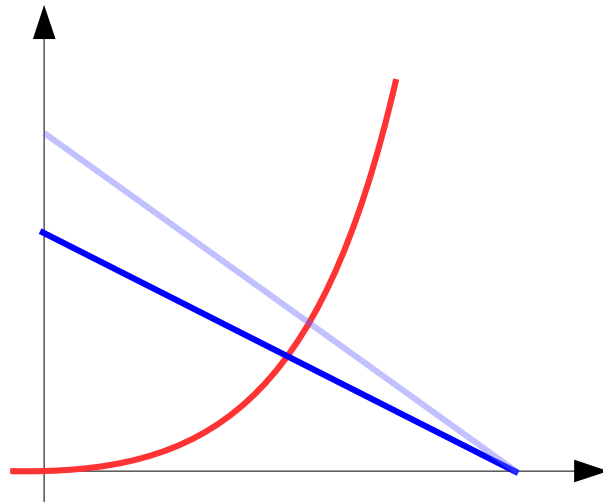


Output Characteristics

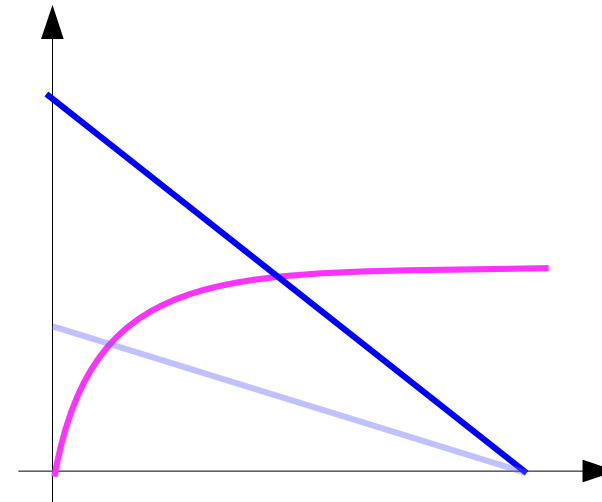


Two Voltage Sources

Active Region



Common Base

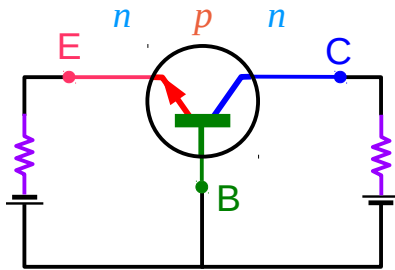


Common Emitter

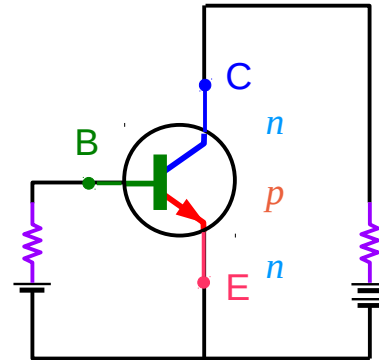


Common Collector

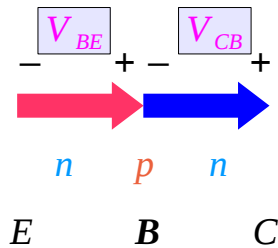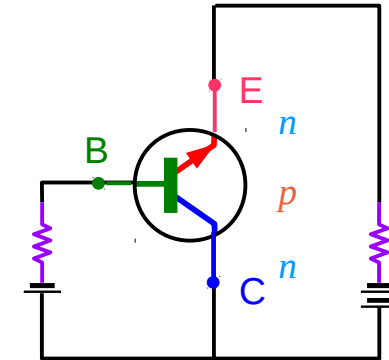

Active region


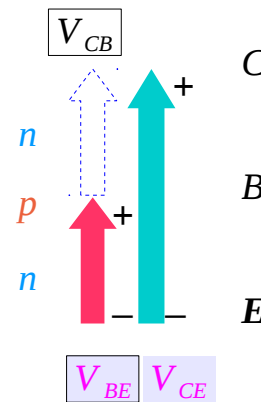


Active region

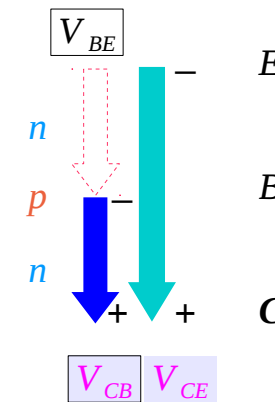



Active region

Common Emitter

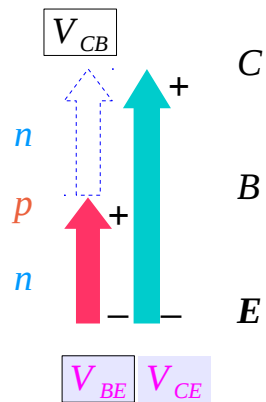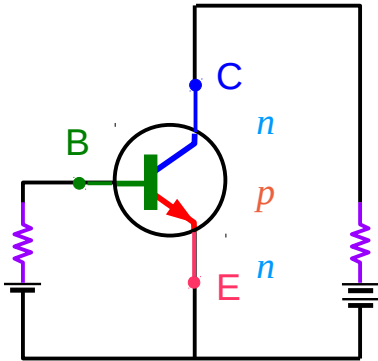



Active region

Common Collector 2

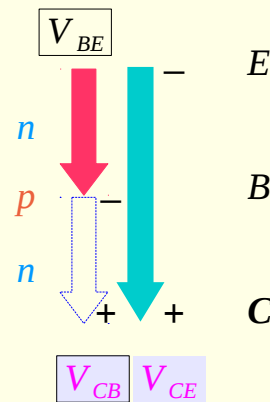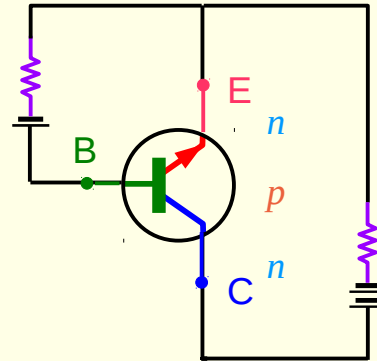


Active region

Common Collector

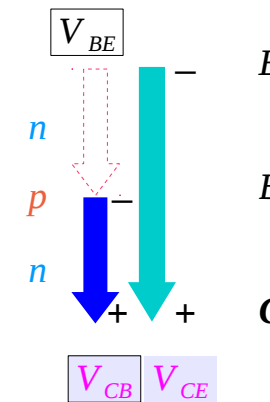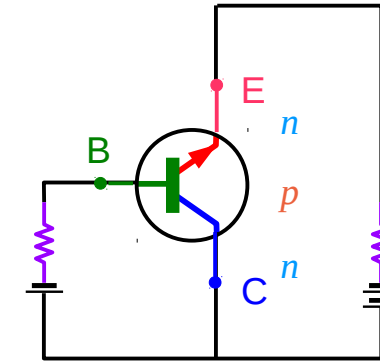

Active region

Bias for Saturation Region



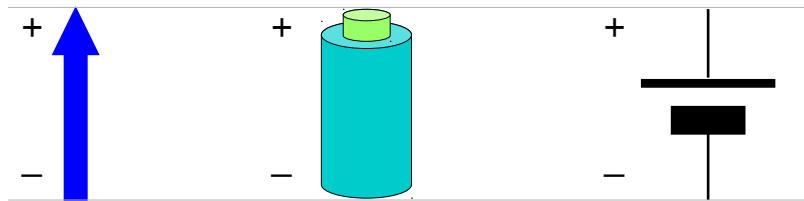


Biassing Back-to-back Diodes - Saturation Region

Common Base

Common Emitter

Common Collector

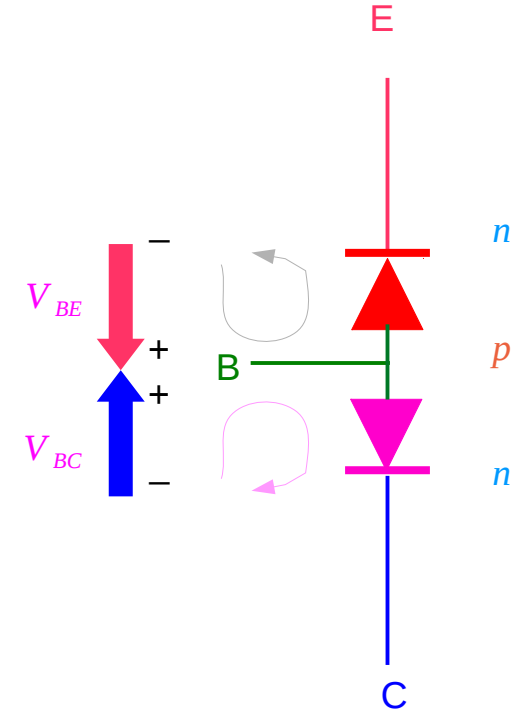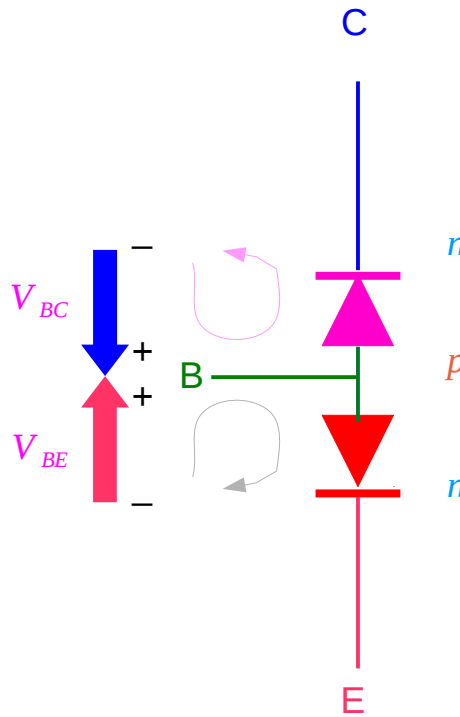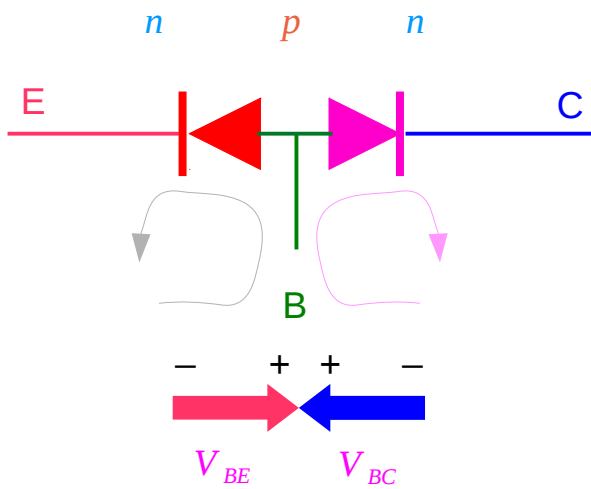

V_{BE} forward bias
 V_{BC} forward bias

==

V_{BE} forward bias
 V_{BC} forward bias

==

V_{BE} forward bias
 V_{BC} forward bias


saturation

saturation

saturation

Two voltage supplies - Saturation Region

Common Base


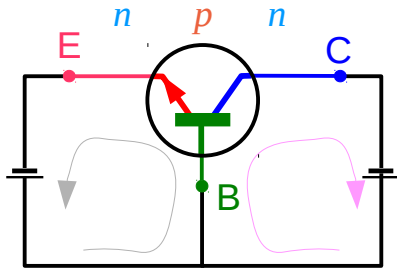


V_{BE} V_{BC}

V_{BE} forward bias
 V_{BC} forward bias

saturation

Common Emitter

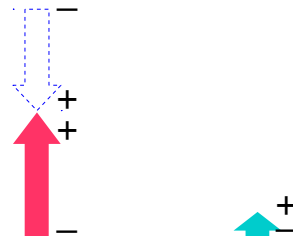
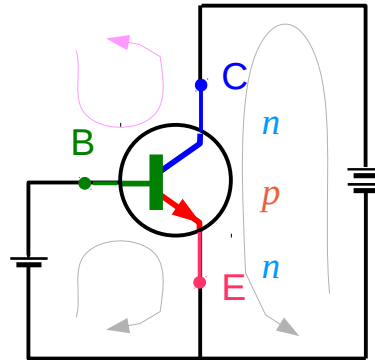


V_{BE} V_{CE}

V_{BE} forward bias
 V_{BC} forward bias

saturation

Common Collector

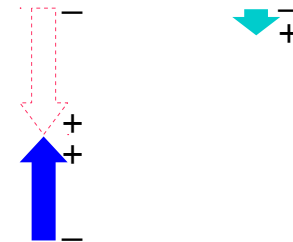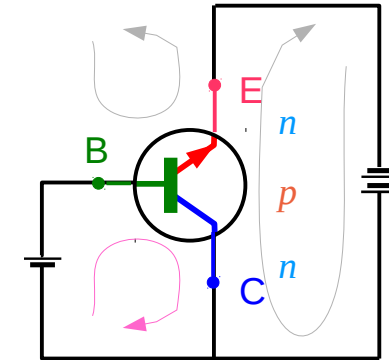


V_{BC} V_{EC}

V_{BE} forward bias
 V_{BC} forward bias


saturation

Two voltage supplies with resistors - Sat Region



Common Base

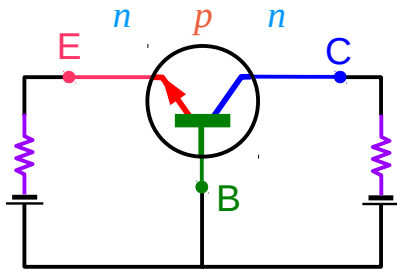


Common Emitter

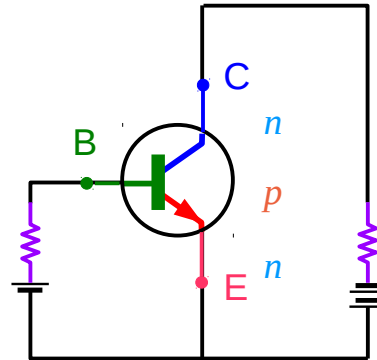


Common Collector

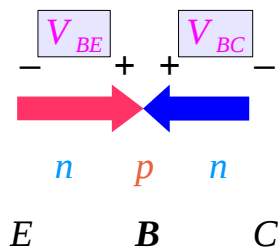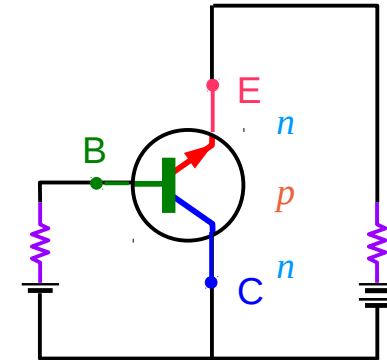

saturation

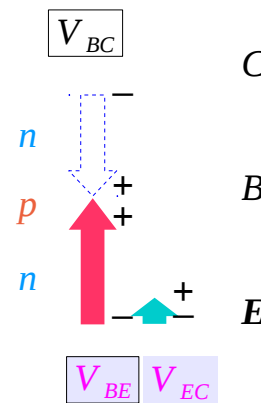



saturation

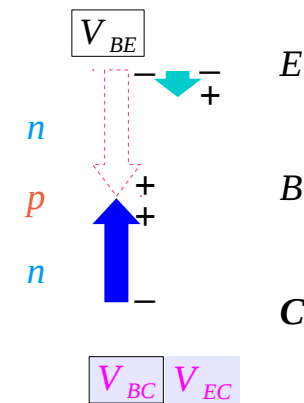

saturation



CE & CC Comparison - Saturation Region

Common Emitter

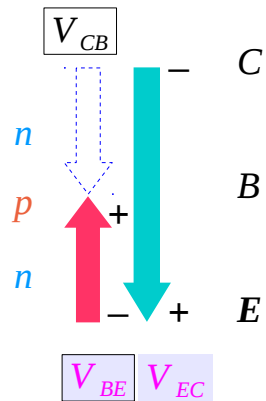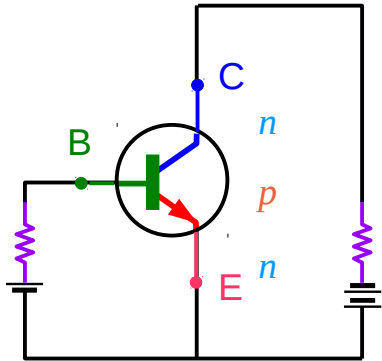



saturation

Common Collector 2

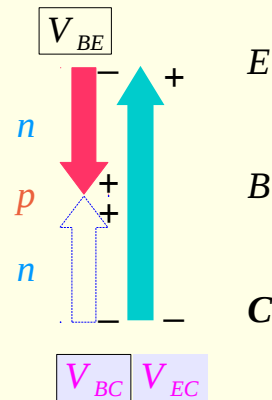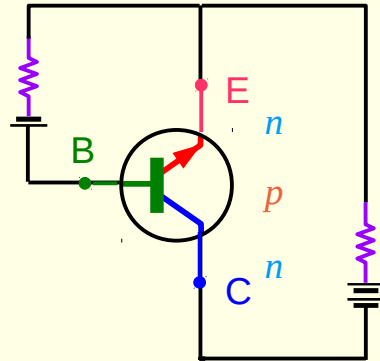

saturation


Common Collector

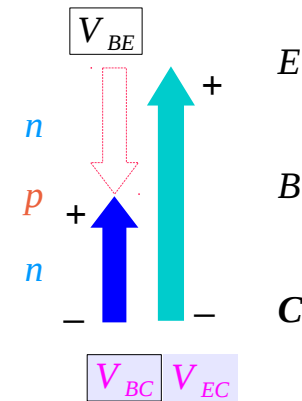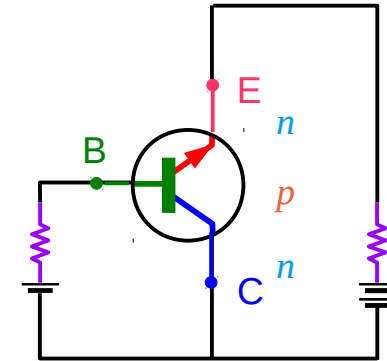


saturation

Active and Saturation Regions (1)

Common Base

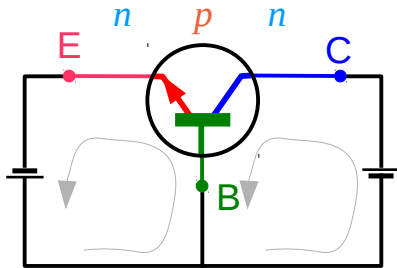


active

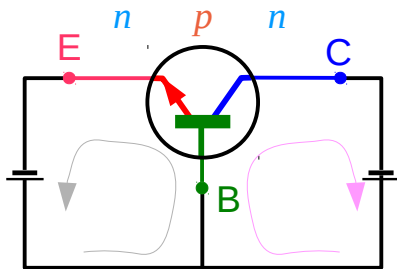


saturation

Common Emitter

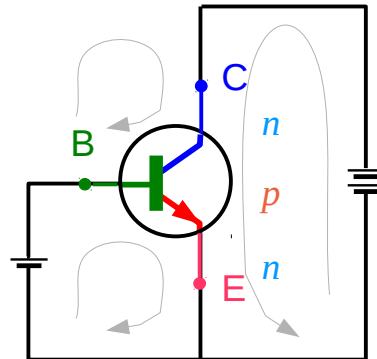


active

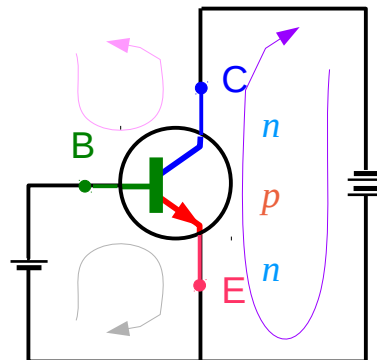


saturation

Common Collector

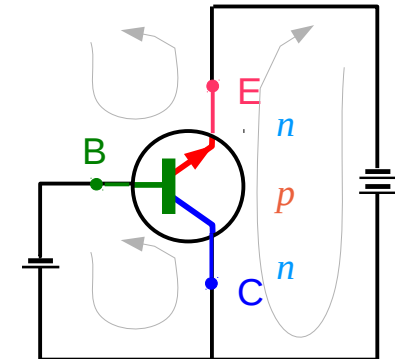


active

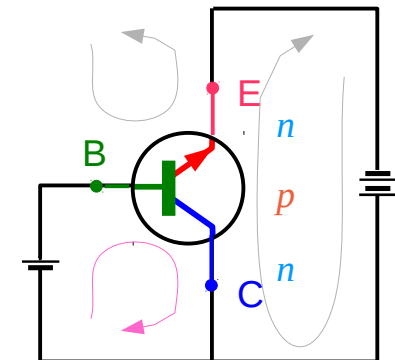


saturation

Active and Saturation Regions (2)

Common Base

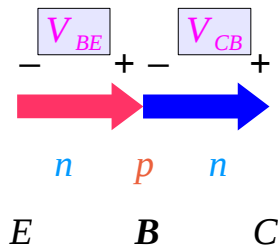


active

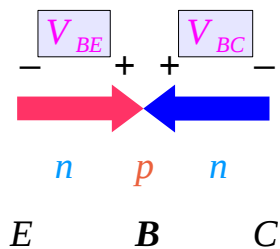


saturation

Common Emitter

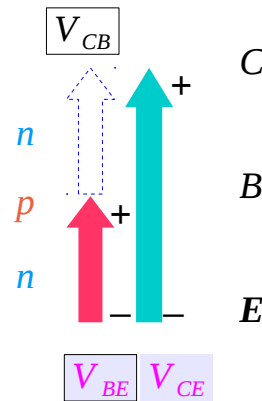


active

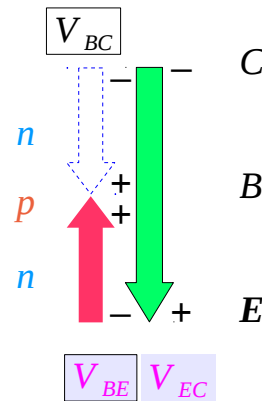


saturation

Common Collector

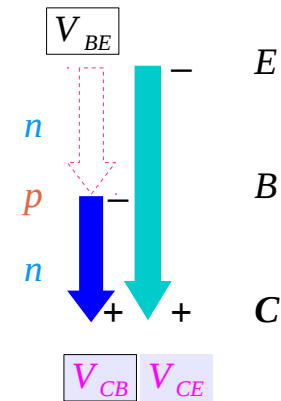


active

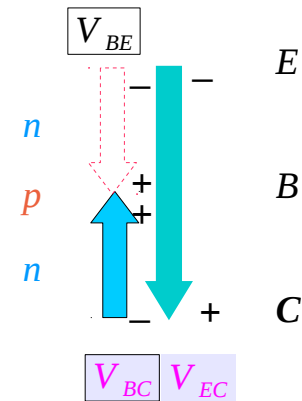


saturation

Active and Saturation Regions (3)

Common Emitter


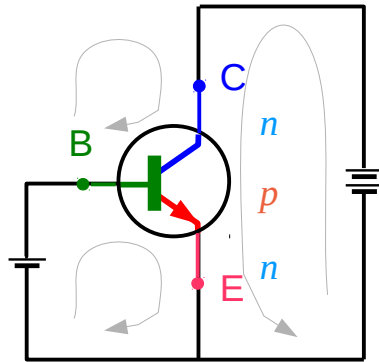


active

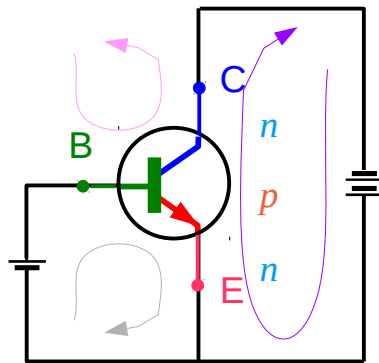


saturation

Common Collector 2

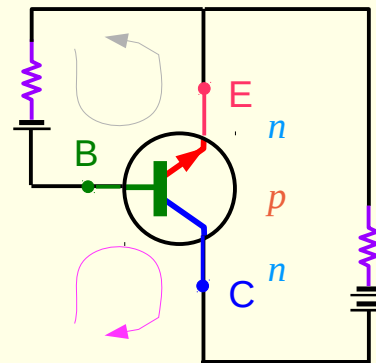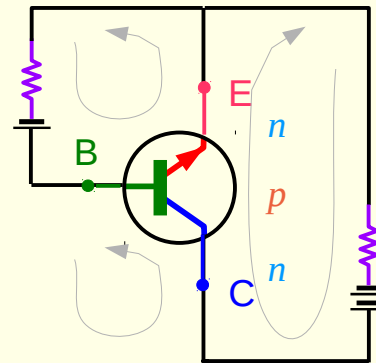


saturation

Common Collector

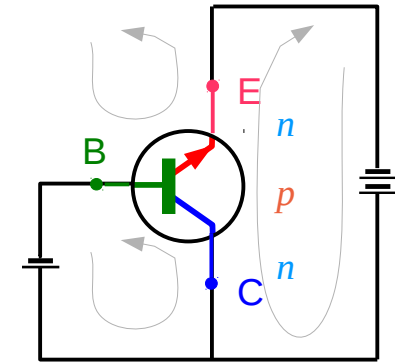


active

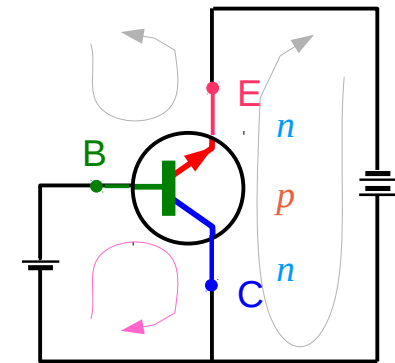


saturation

Active and Saturation Regions (4)

Common Emitter

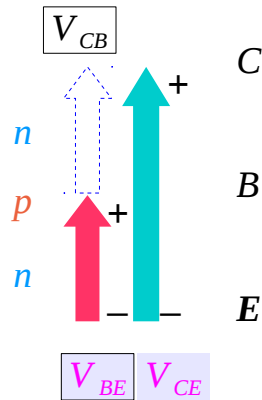


active

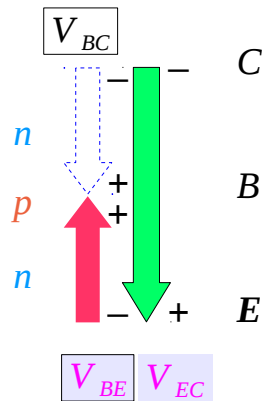


saturation

Common Collector 2

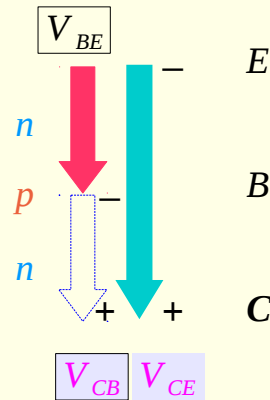


active

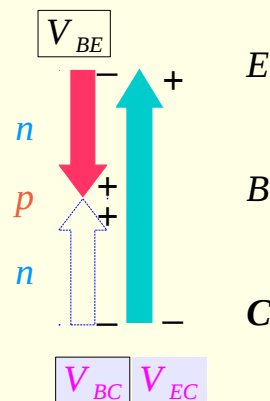


saturation

Common Collector

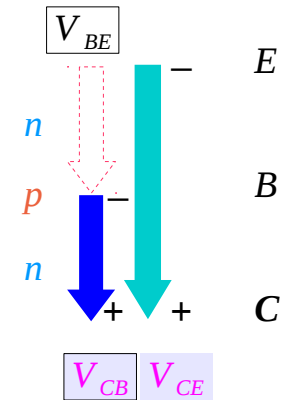


active

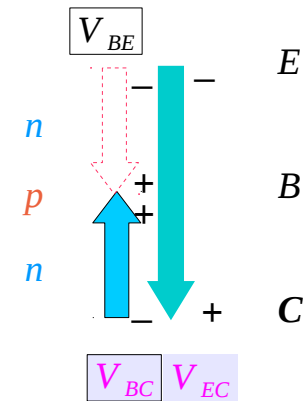

saturation


Active and Saturation Regions (2)

Common Base

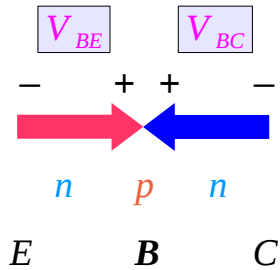


saturation

Common Emitter

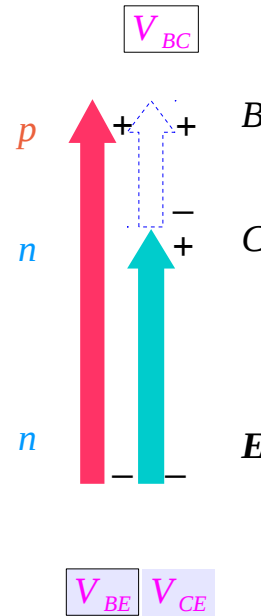

saturation


Common Collector

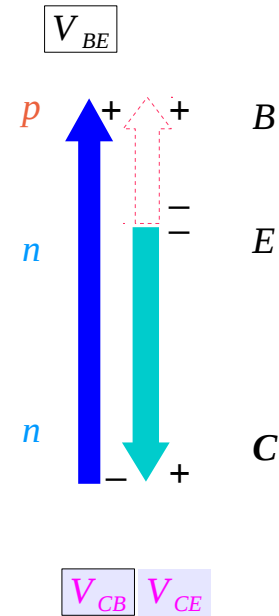

saturation


Active and Saturation Regions (2)

Common Base

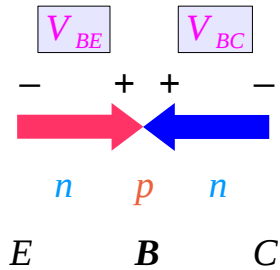


saturation

Common Emitter

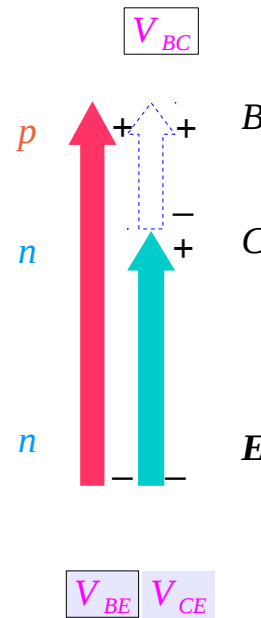


saturation

Common Collector

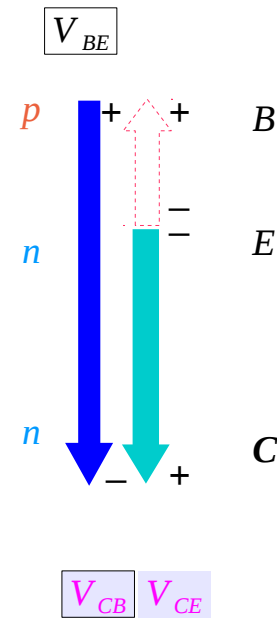


saturation

Common Base (1)

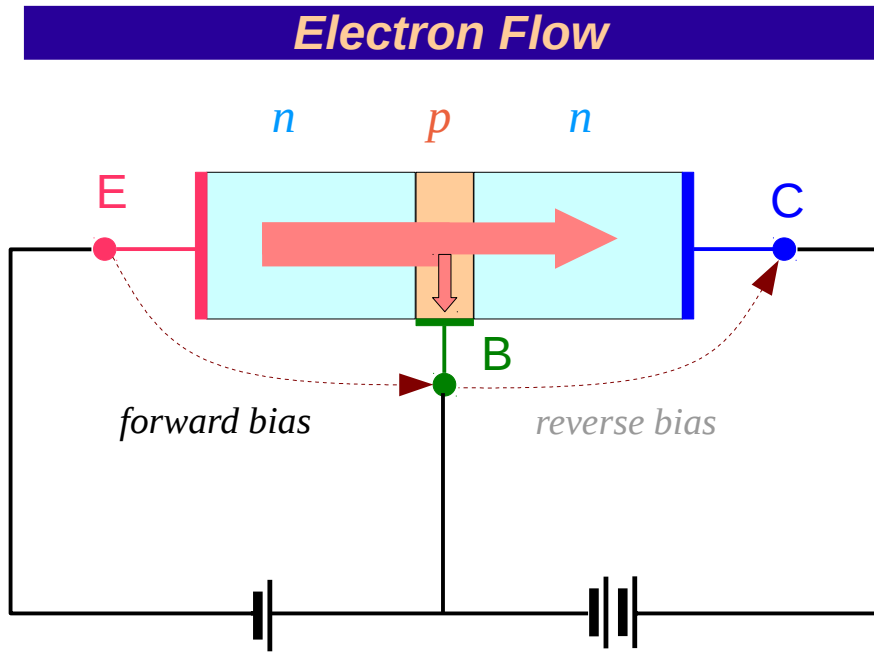


Common Base

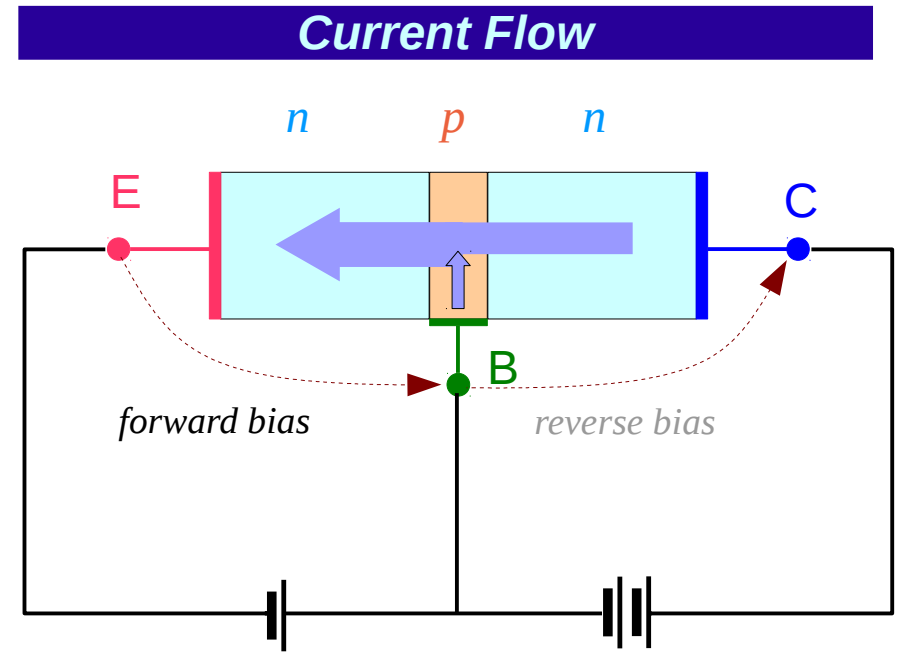

Common Base


Common Base (2)

Electron Flow


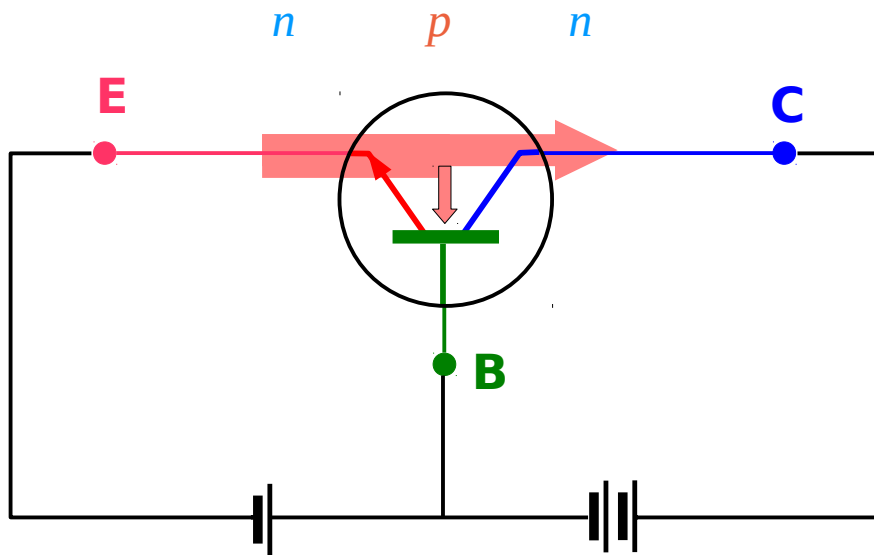


Common Base

Current Flow

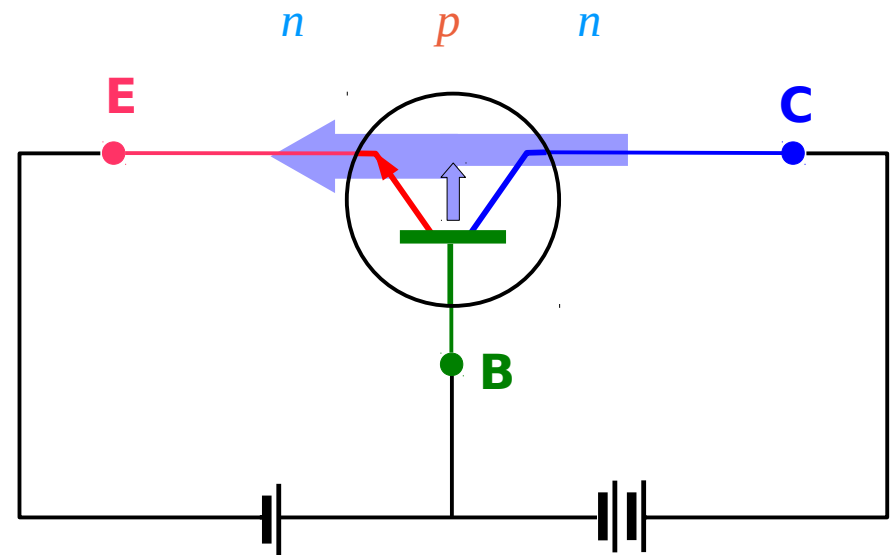


Common Base

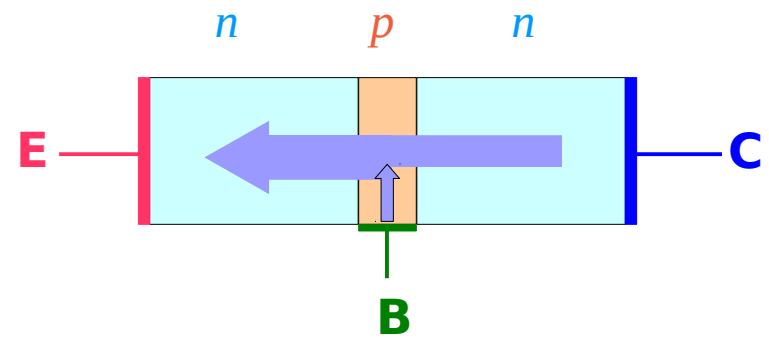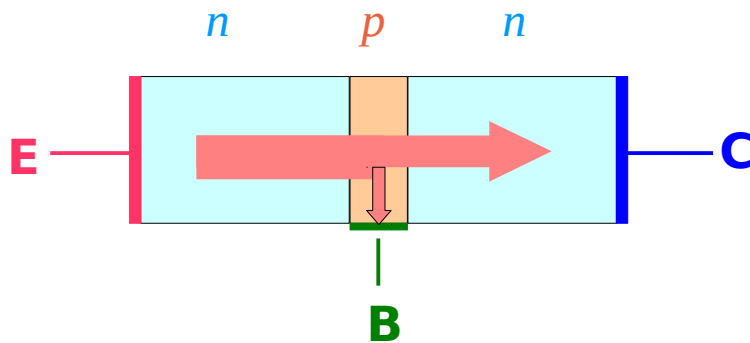


Common Emitter (1)

Electron Flow

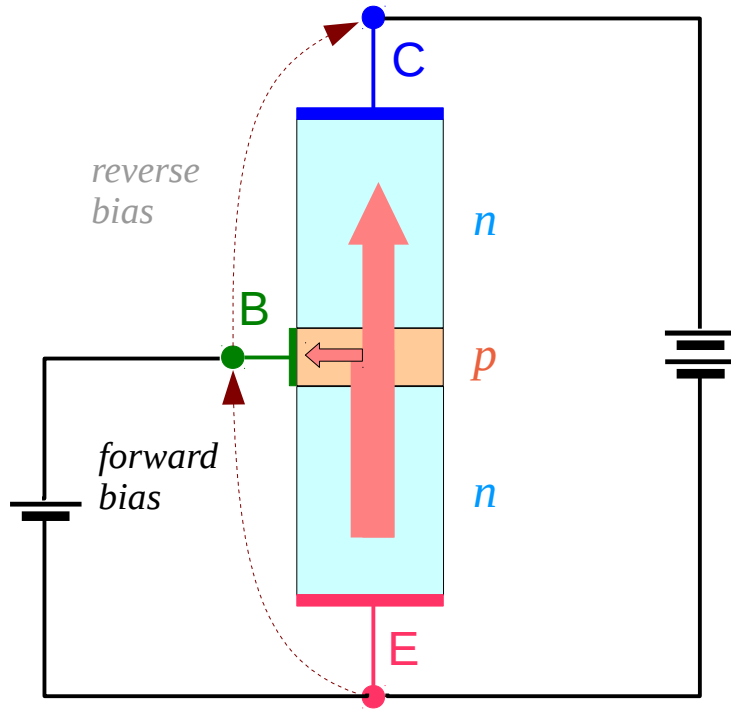

Common Emitter


Current Flow

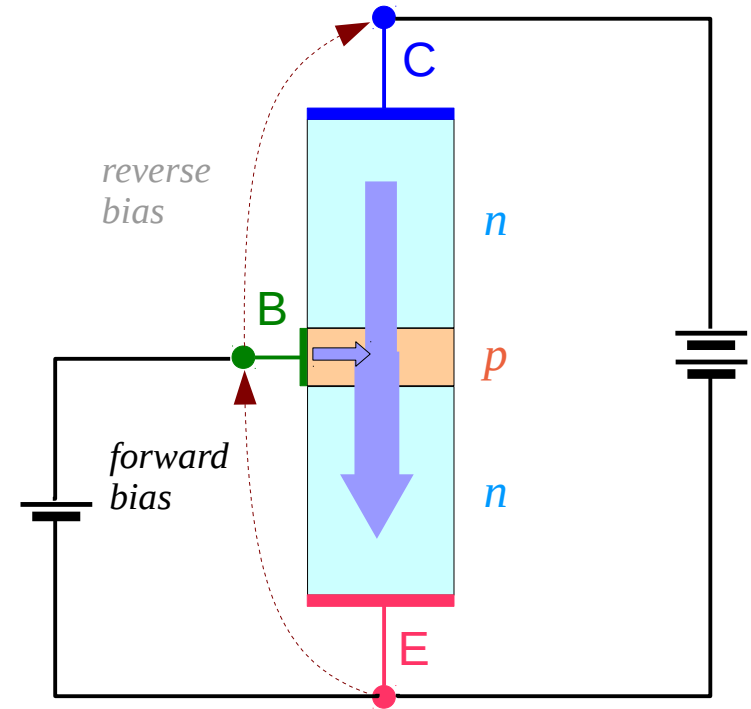


Common Emitter

Common Emitter (2)


Electron Flow

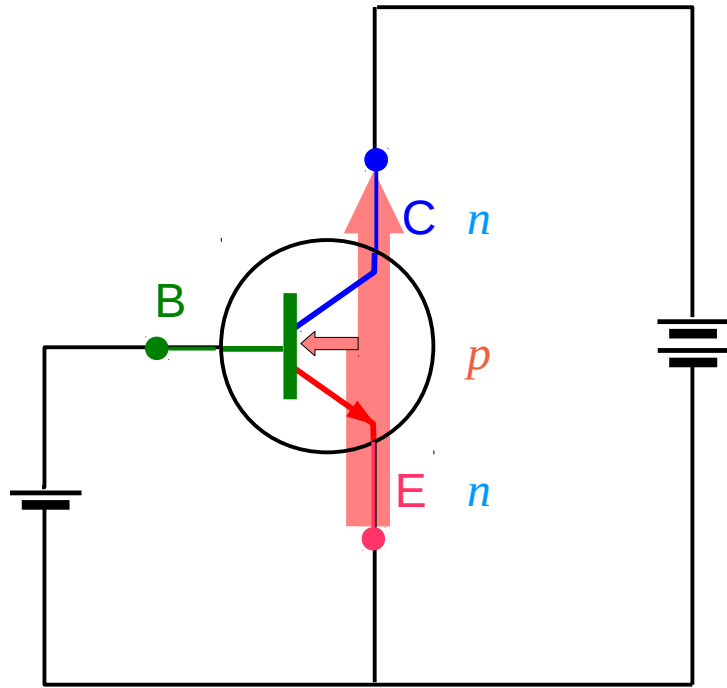


Common Emitter

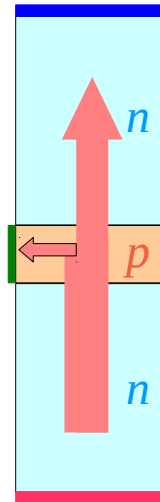

Current Flow

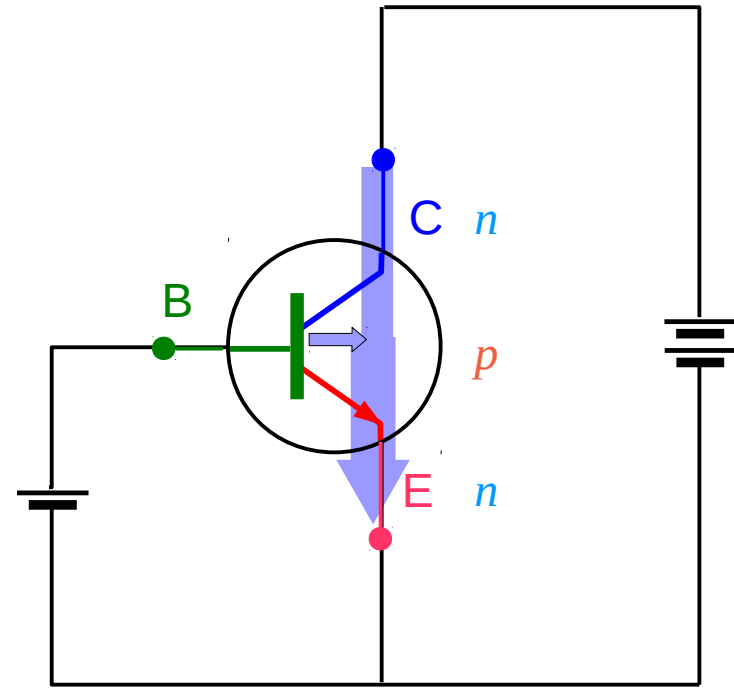


Common Emitter

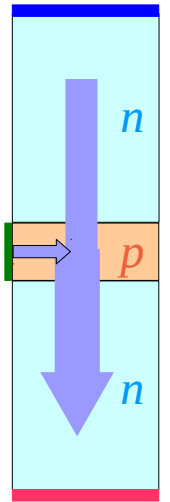


Common Collector (1)

Electron Flow

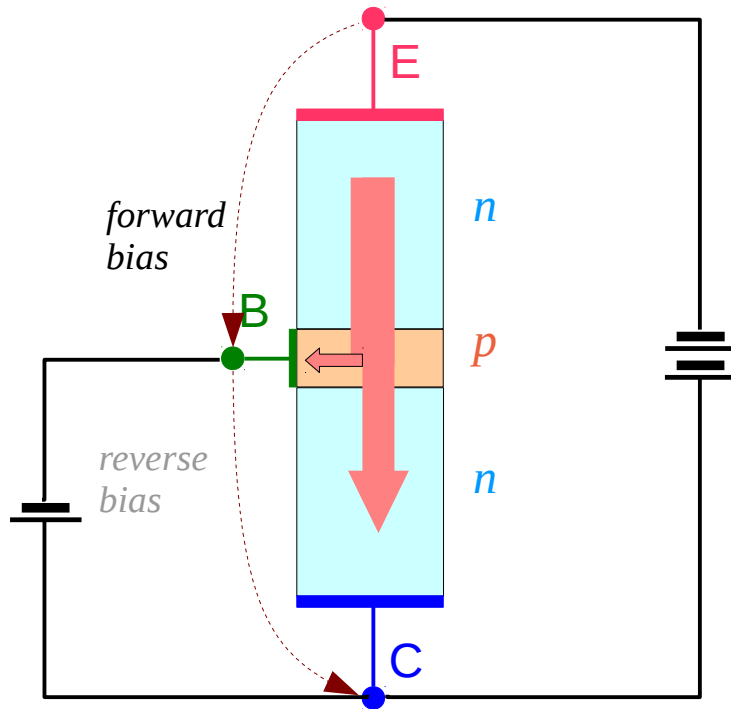

Common Collector


Current Flow

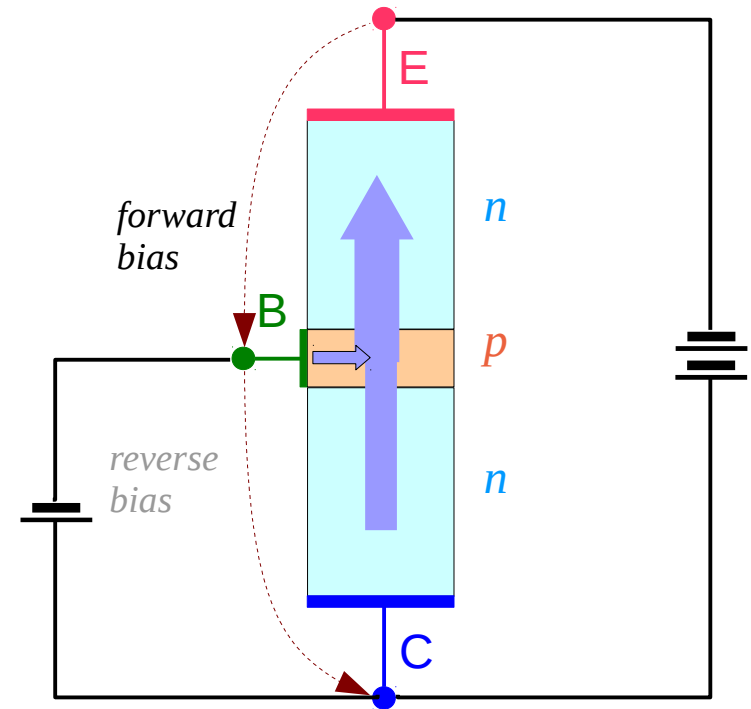


Common Collector

Common Collector (2)


Electron Flow

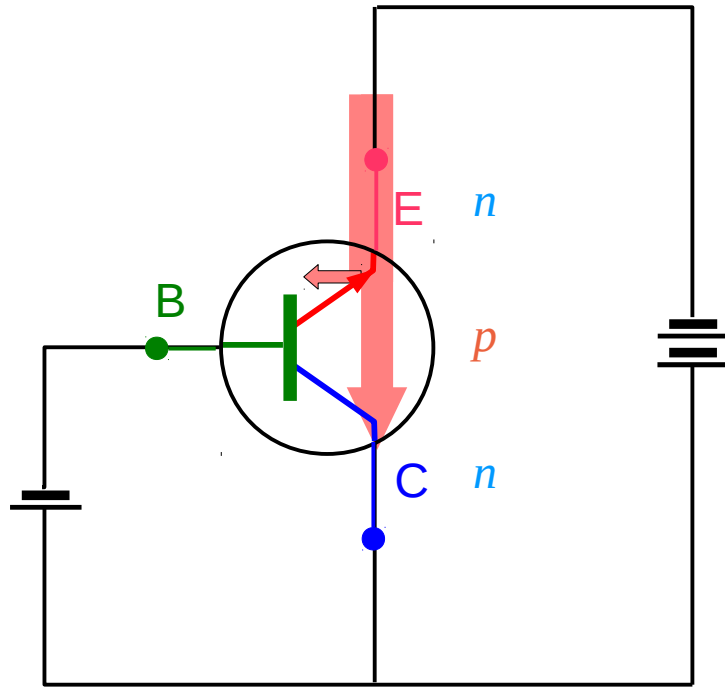


Common Collector

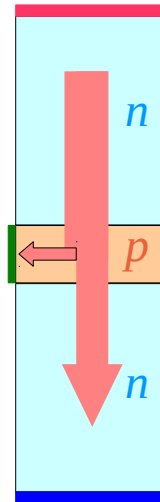


Current Flow

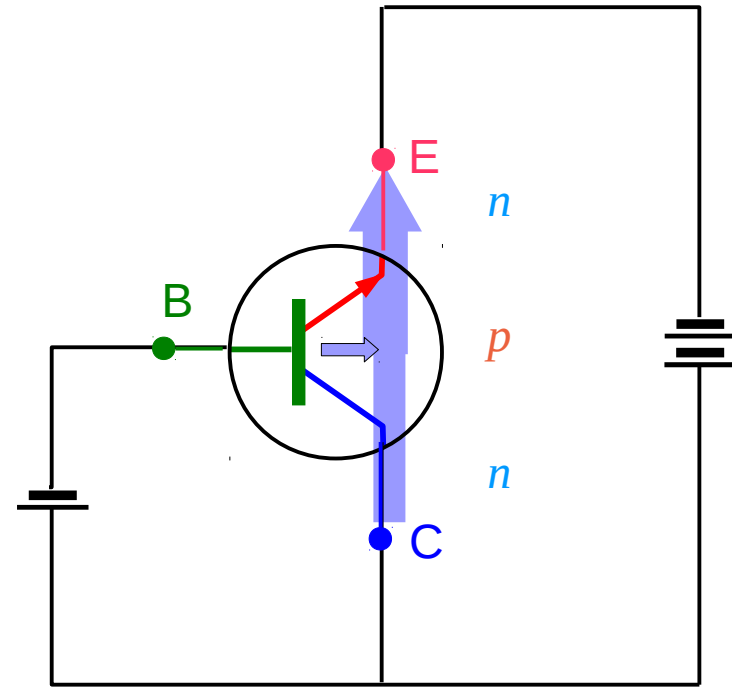


Common Collector

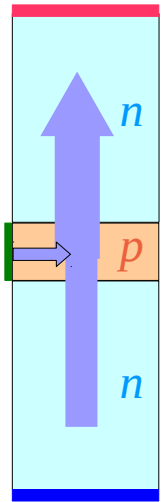


BJT Bias

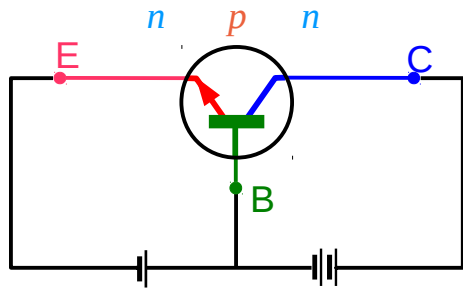




Common Base

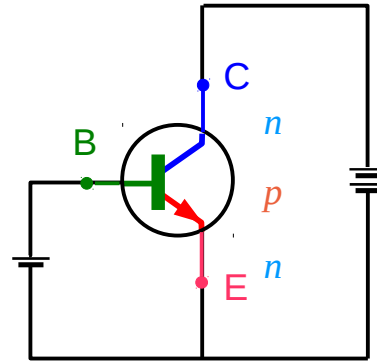


Common Emitter

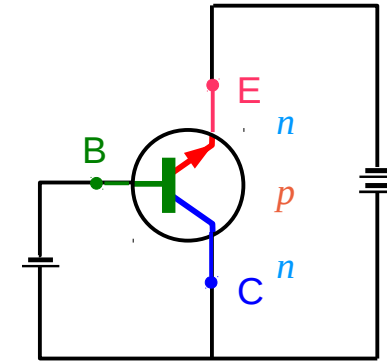


Common Collector

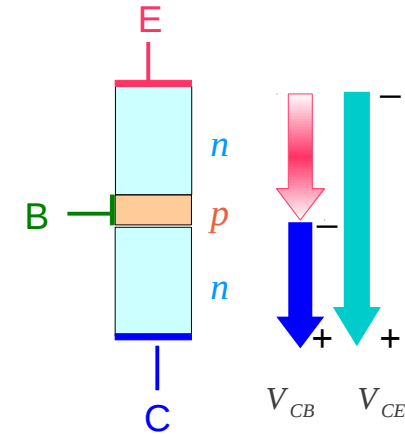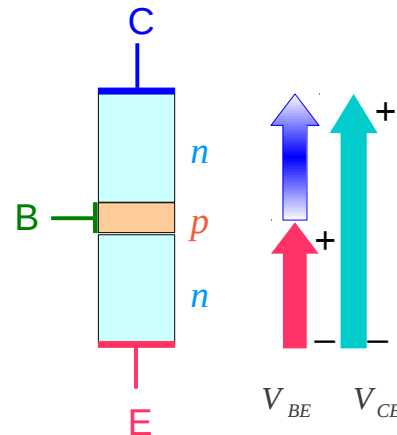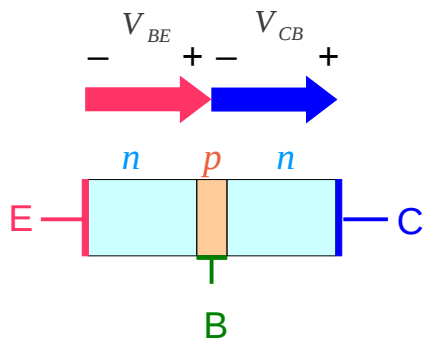


Common Emitter (2)

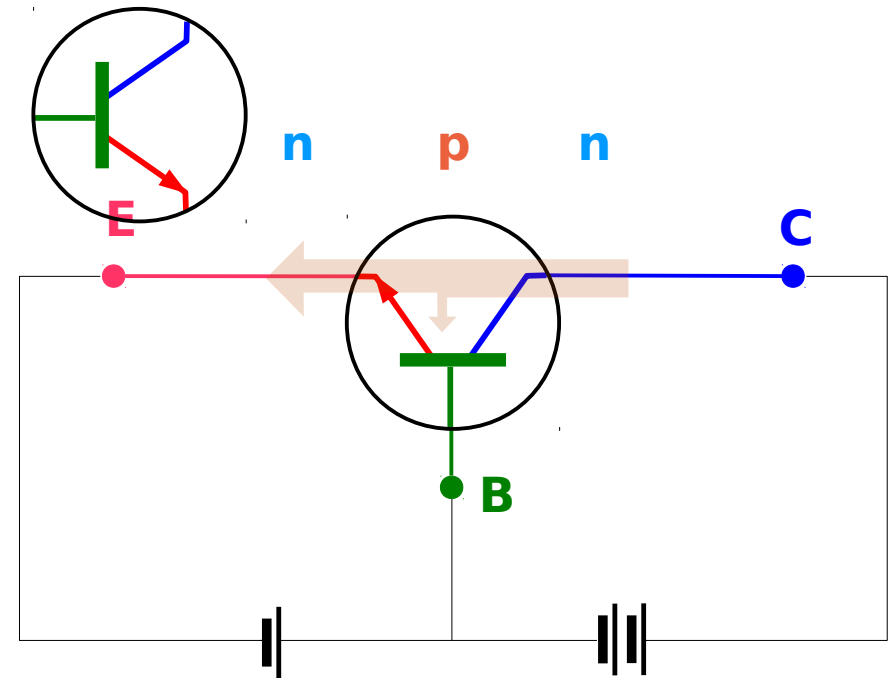

Electron Flow

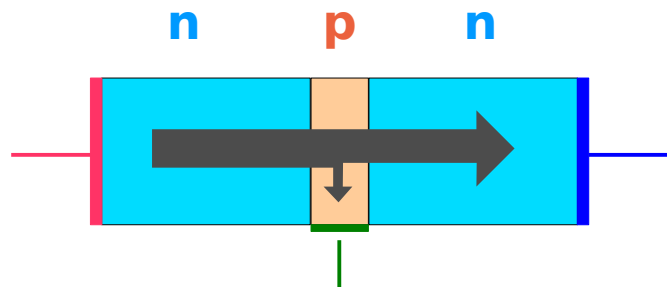

Current Flow

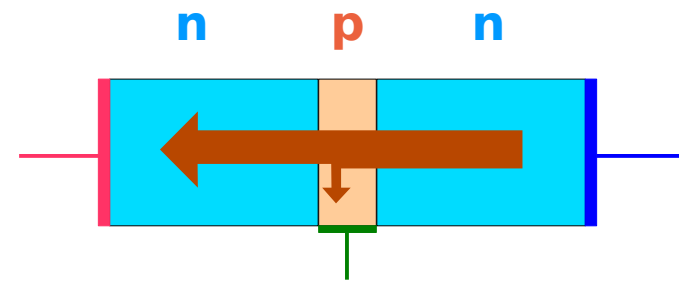

References

[1] <http://en.wikipedia.org/>

[2] J.H. McClellan, et al., *Signal Processing First*, Pearson Prentice Hall, 2003