# Variable Block Adder (1C)

•

•


Copyright (c) 2024 - 2010 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".

Please send corrections (or suggestions) to youngwlim@hotmail.com.

This document was produced by using OpenOffice and Octave.

## Carry Skip Adder

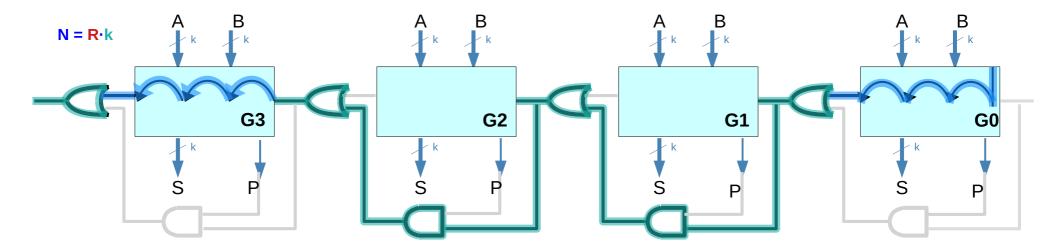

Fixed block size = k bits

$$| \leftarrow (k-1) \Delta_{rca}$$

$$(k-1) \Delta_{rca}$$

$$(k-1) \Delta_{rca}$$

$$(k-1) \Delta_{rca}$$

$$(k-1) \Delta_{rca}$$

$$(k-1) \Delta_{rca}$$

Variable block size =  $x_i$  bits for the i-th group


$$(x_i - 1) t$$

$$(m-2)T$$

$$(x_j - 1) t$$

t denote the time required for a carry signal to ripple across a bit T denote the time required for the signal to skip over a group of bits m denotes the optimal number of groups for an n-bit carry chain


### Carry Skip Adder – fixed block size

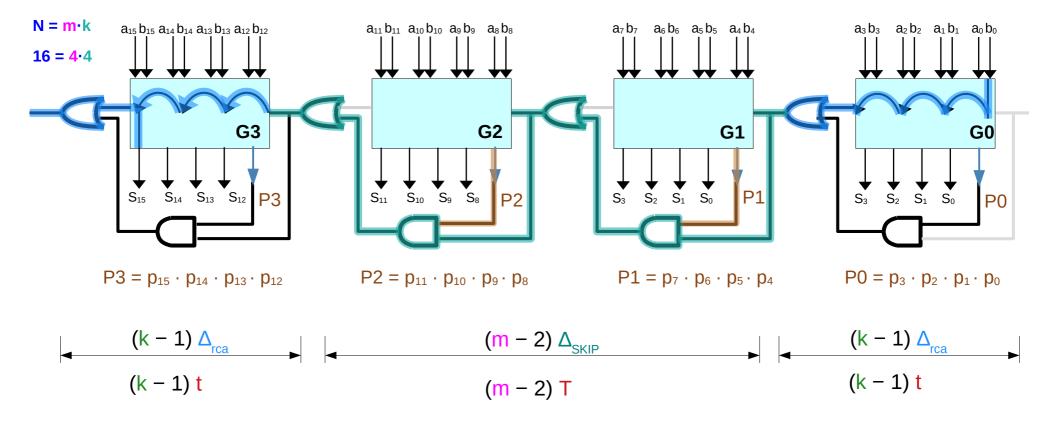


t denote the time required for a carry signal to ripple across a bit
 T denote the time required for the signal to skip over a group of bits
 m denotes the optimal number of groups for an n-bit carry chain

Fixed Block Size  $\Rightarrow$  delay(P3) = delay(P2) = delay(P1) = delay(P0) = Fixed Delay

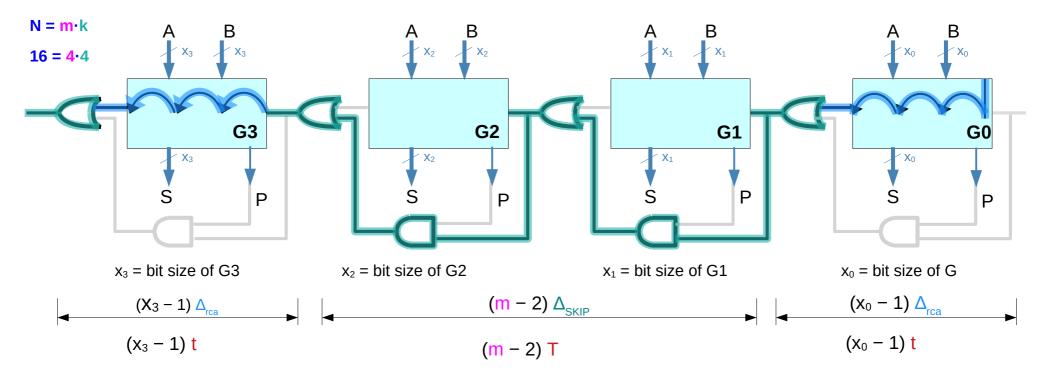
## Carry Skip Adder – maximum carry delay (3)



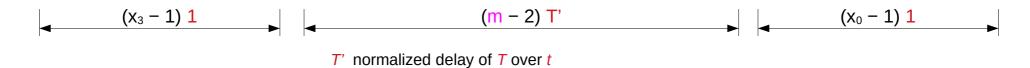*t* denote the time required for a carry signal to ripple across a bit *T* denote the time required for the signal to skip over a group of bits *m* denotes the optimal number of groups for an n-bit carry chain



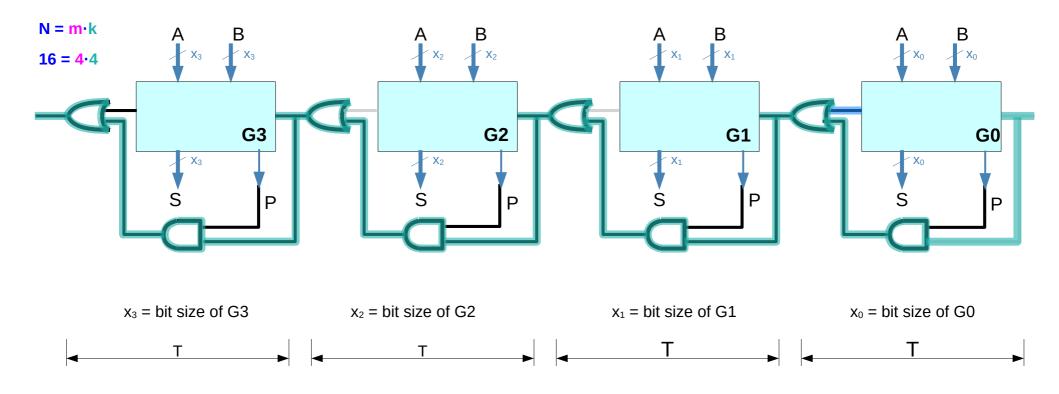
## Carry Skip Adder – maximum carry delay (3)




**Carry Skip Delays** 
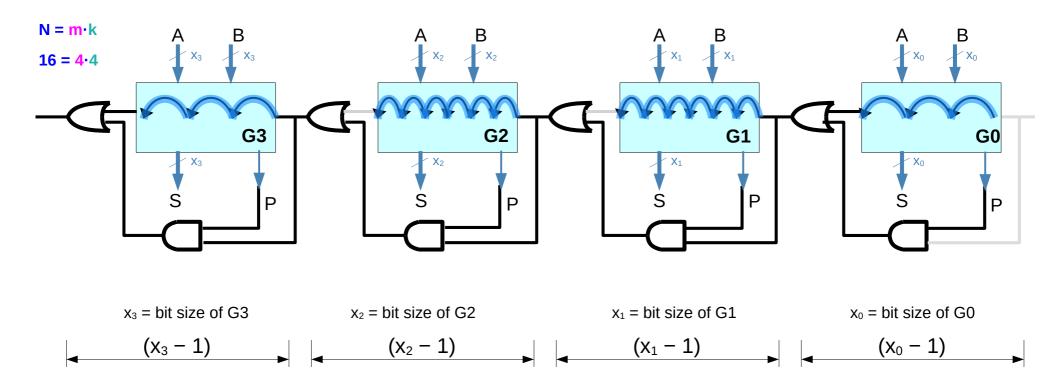
## Carry Skip Adder – maximum carry delay (3)



**Carry Ripple delays** 

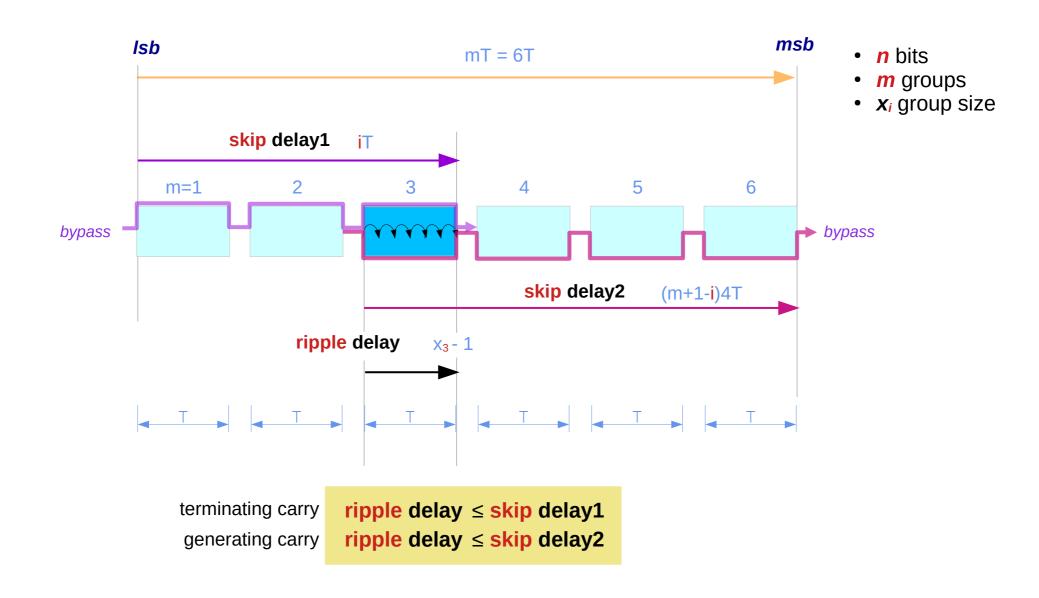
## Minimum skip path delay $y_i$ of the $i^{th}$ group




**Variable Block Adder** 

(1C)

### Parallel Delay Paths

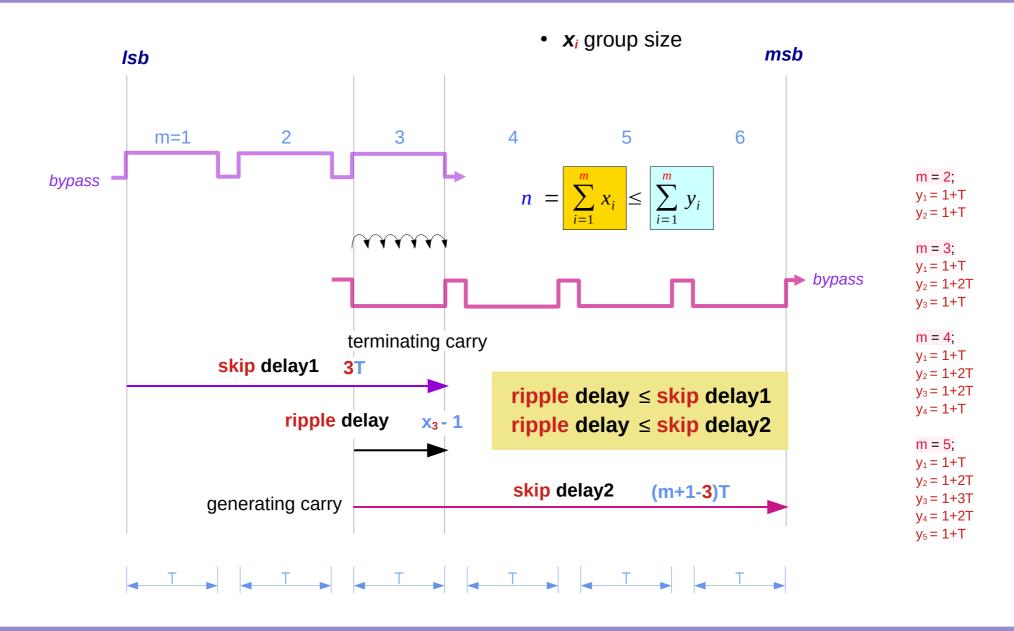

## Minimum skip path delay $y_i$ of the $i^{th}$ group

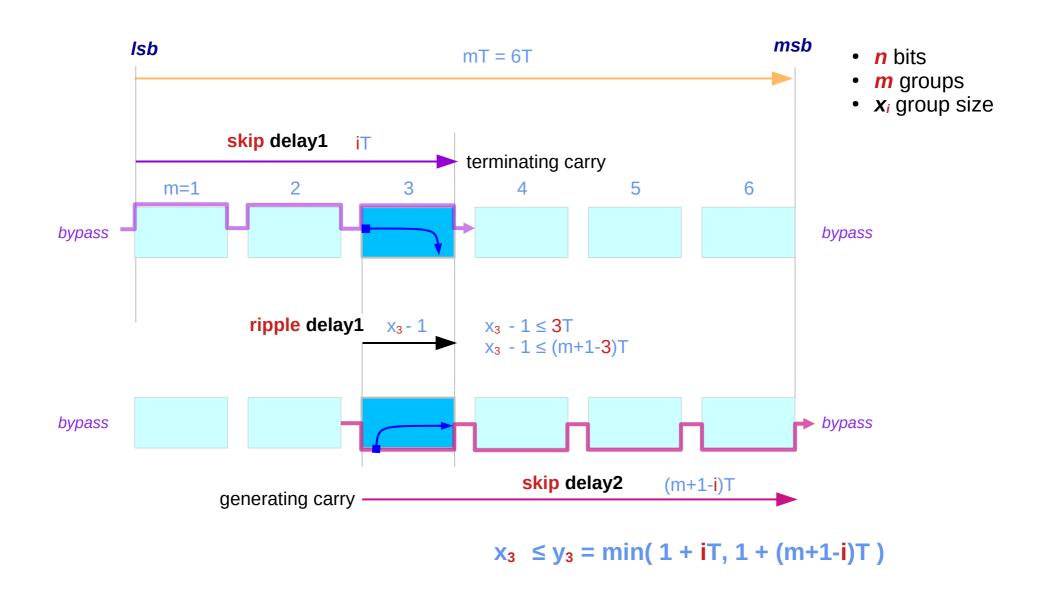


**Method 1** – using a histogram

Let  $\frac{m}{m}$  be the <u>smallest</u> positive integer such that

$$n \leq \sum_{i=1}^{m} y_i$$

$$m = 2$$
;  
while  $(y_1+\dots+y_m < n)$   $m = m+1$ ;

$$y_i = min\{1+iT, 1+(m+1-i)T\}, i = 1,...,m$$

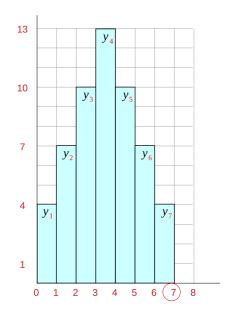

Method 2 – using a closed formula

Let m be the <u>smallest</u> positive integer such that

$$n \le m + \frac{1}{2}mT + \frac{1}{4}m^2T + (1 - (-1)^m)\frac{1}{8}T$$



Oklobdzija: High-Speed VLSI arithmetic units : adders and multipliers

 $0 \leq x_i \leq y_i, i = 1, \dots, m$ 


#### **Method 1** – using a histogram

Let *m* be the <u>smallest</u> positive integer such that

$$n \leq \sum_{i=1}^{m} y_i$$

$$m = 2$$
;  
while  $(y_1+\dots+y_m < n)$   $m = m+1$ ;

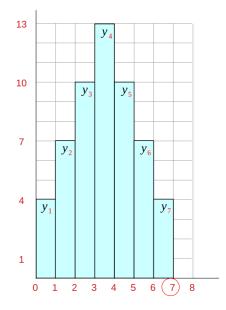
$$y_i = min\{1+iT, 1+(m+1-i)T\}, i = 1,...,m$$





```
\begin{split} &m=2; \ T=3 \\ &y_1=\min \left\{1+T,\, 1+2T\right\}=1+T \\ &y_2=\min \left\{1+2T,\, 1+T\right\}=1+T \\ &=4 \\ \\ &m=3; \ T=3 \\ &y_1=\min \left\{1+T,\, 1+3T\right\}=1+T \\ &=4 \\ \\ &y_2=\min \left\{1+2T,\, 1+2T\right\}=1+2T \\ &=7 \\ &y_3=\min \left\{1+3T,\, 1+T\right\}=1+T \\ &=4 \\ \\ &m=4; \ T=3 \\ &y_1=\min \left\{1+T,\, 1+4T\right\}=1+T \\ &=4 \\ &y_2=\min \left\{1+2T,\, 1+3T\right\}=1+2T \\ &=7 \\ &y_3=\min \left\{1+3T,\, 1+2T\right\}=1+2T \\ &=7 \\ &y_4=\min \left\{1+4T,\, 1+T\right\}=1+T \\ &=4 \\ \end{split}
```

```
\begin{array}{lll} m=5; & T=3 \\ y_1=min \left\{1+T,\, 1+5T\right\} & = 1+T & = 4 \\ y_2=min \left\{1+2T,\, 1+4T\right\} & = 1+2T & = 7 \\ y_3=min \left\{1+3T,\, 1+3T\right\} & = 1+3T & = 10 \\ y_4=min \left\{1+4T,\, 1+2T\right\} & = 1+2T & = 7 \\ y_5=min \left\{1+5T,\, 1+T\right\} & = 1+T & = 4 \\ \end{array}
\begin{array}{lll} m=6; & T=3 \\ y_1=min \left\{1+T,\, 1+6T\right\} & = 1+T & = 4 \\ y_2=min \left\{1+2T,\, 1+5T\right\} & = 1+2T & = 7 \\ y_3=min \left\{1+3T,\, 1+4T\right\} & = 1+3T & = 10 \\ y_4=min \left\{1+4T,\, 1+3T\right\} & = 1+3T & = 10 \\ y_5=min \left\{1+5T,\, 1+2T\right\} & = 1+2T & = 7 \\ y_6=min \left\{1+6T,\, 1+T\right\} & = 1+T & = 4 \end{array}
```

```
\begin{array}{lll} m=7; & \textbf{T=3} \\ y_1=\min \left\{1+T, \ 1+7T\right\} & = 1+T=4 \\ y_2=\min \left\{1+2T, \ 1+6T\right\} & = 1+2T=7 \\ y_3=\min \left\{1+3T, \ 1+5T\right\} & = 1+3T=10 \\ y_4=\min \left\{1+4T, \ 1+4T\right\} & = 1+4T=13 \\ y_5=\min \left\{1+5T, \ 1+3T\right\} & = 1+3T=10 \\ y_6=\min \left\{1+6T, \ 1+2T\right\} & = 1+2T=7 \\ y_7=\min \left\{1+7T, \ 1+1T\right\} & = 1+T=4 \end{array}
```

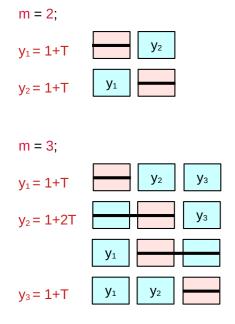


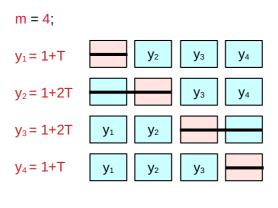

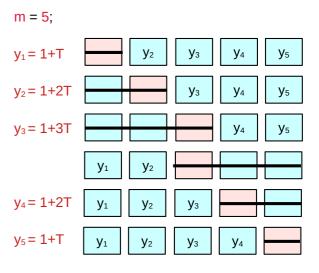


```
m = 2;
x_1 \le 1 + T
x_2 \le 1 + T
```

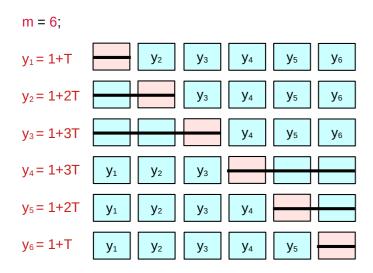m = 4;  $x_1 \le 1+T$   $x_2 \le 1+2T$   $x_3 \le 1+2T$  $x_4 \le 1+T$  m = 5;  $X_1 \le 1+T$   $X_2 \le 1+2T$   $X_3 \le 2+3T$   $X_4 \le 1+2T$  $X_5 \le 1+T$ 



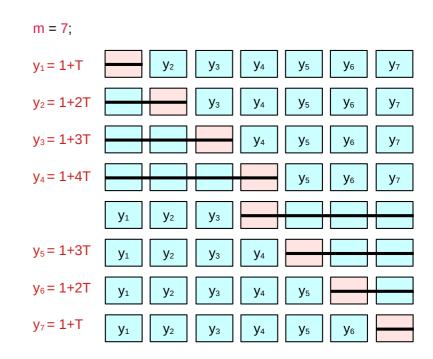m = 6;  $x_1 \le 1+T$   $x_2 \le 1+2T$   $x_3 \le 1+3T$   $x_4 \le 1+3T$   $x_5 \le 1+2T$  $x_6 \le 1+T$ 



m = 7;  $x_1 \le 1+T$   $x_2 \le 1+2T$   $x_3 \le 1+3T$   $x_4 \le 1+4T$   $x_5 \le 1+3T$   $x_6 \le 1+2T$   $x_7 \le 1+T$ 


#### **Method 1** – using a histogram


Let *m* be the <u>smallest</u> positive integer such that

$$n \leq \sum_{i=1}^{m} y_i$$

$$m = 2;$$
  
while  $(y_1 + \dots + y_m < n)$   $m = m+1;$ 
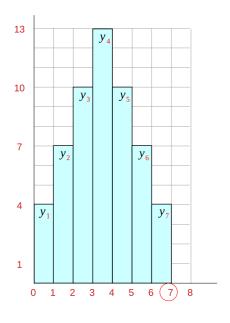
$$y_i = min\{1+iT,1+(m+1-i)T\}, i = 1,...,m$$



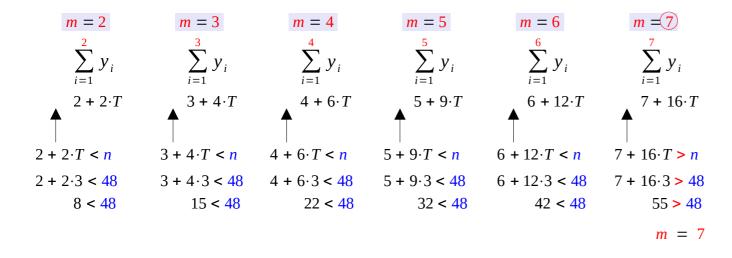

$$\begin{array}{c}
n = 48 \\
T = 3
\end{array}$$

$$m = 7$$

## Determining x<sub>i</sub>

construct a histogram whose i-th column has height  $y_i$ 

so these  $y_i$ 's are <u>at least n unit squares</u> in the histogram, starting with the first row, shade in n of the squares, <u>row by row</u>

let  $x_i$  denote the number of shaded squares in column i of the histogram,


$$i = 1, ..., m$$


$$0 \leq x_i \leq y_i, \quad i=1,...,m$$

$$n = \sum_{i=1}^{m} x_i \leq \sum_{i=1}^{m} y_i$$

$$n = \sum_{i=1}^{7} x_i$$

 $n = 4+7+8+9+9+7+4=48 < 7+16\cdot 3=55$ 

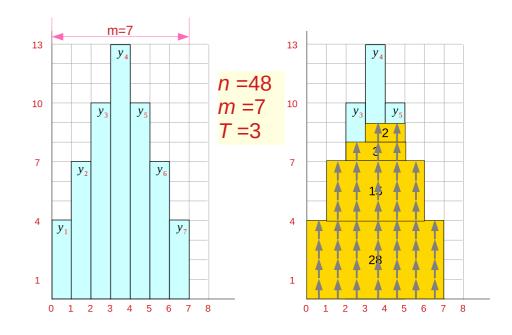

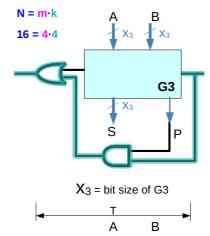

	T = 3
$\leq$	$y_1 = 4$
$\leq$	$y_2 = 7$
<	$y_3 = 10$
<	$y_4 = 13$
<	$y_5 = 10$
≤	$y_6 = 7$
≤	$y_7 = 4$
	< </td

### Procedure

(I) Let m be the smallest positive integer such that

$$n \le m + \frac{1}{2}mT + \frac{1}{4}m^2T + (1 - (-1)^m)\frac{1}{8}T = \sum_{i=1}^m y_i$$
•  $m = 7$  groups
•  $i$ -th group has  $x_i$  bits (size)
• constant skip delay  $T = T(x)$ 

- total n = 48 bits
- m = 7 groups
- constant skip delay  $T = T(x_i) = 3$

(II) Let

$$y_i = min\{1+iT, 1+(m+1-i)T\}, i = 1,...,m$$

and construct a histogram whose *i-th* column has height *y*, for example, for T=3, and n=48, we have m=7

(III) It is easily verified that the area of the histogram in (II) is

$$\sum_{i=1}^{m} y_{i} = \left[ m + \frac{1}{2} m T + \frac{1}{4} m^{2} T + (1 - (-1)^{m}) \frac{1}{8} T \right] \ge n$$

so these are at least *n* unit squares in the histogram starting with the first row, shade in *n* of the squares, row by row Let  $x_i$  denote the number of shaded squares in column i of the histogram,

$$y_i = \sum_{i=1}^m x_i \le \sum_{i=1}^m y_i$$

i = 1, ..., m

$$y_i = min\{1+iT, 1+(m+1-i)T\}, i = 1,...,m$$

$$y_1 = min\{1+1\cdot T, 1+(m+1-1)T\} = 1+T$$
  
 $y_m = min\{1+m\cdot T, 1+(m+1-m)T\} = 1+T$ 

$$y_2 = min\{1+2\cdot T, 1+(m+1-2)T\} = 1+2T$$
  
 $y_{m-1} = min\{1+(m-1)\cdot T, 1+(m+1-(m-1))T\} = 1+2T$ 


$$y_3 = min\{1+3\cdot T, 1+(m+1-3)T\} = 1+3T$$
  
 $y_{m-2} = min\{1+(m-2)\cdot T, 1+(m+1-(m-2))T\} = 1+3T$ 

the scheme (i), (ii), (iii) gives the max prop time *mT* 

$$x_1 \le y_1 = 1 + T$$
$$x_m \le y_m = 1 + T$$

$$x_2 \le y_2 = 1+2T$$
 $x_{m-1} \le y_{m-1} = 1+2T$ 
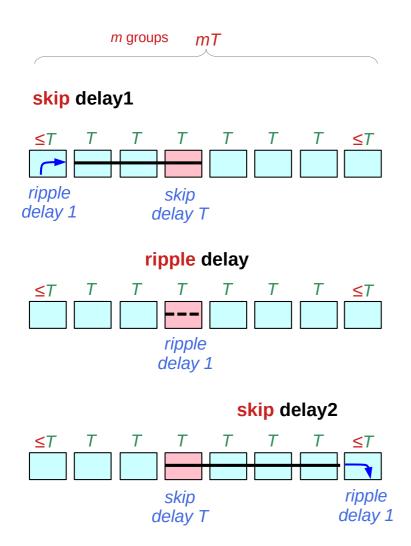
$$x_3 \le y_3 = 1+3T$$
  
 $x_{m-2} \le y_{m-2} = 1+3T$ 



```
the scheme (i), (ii), (iii)
gives the max prop time mT
skip delay1
                                generating carry
                 iΤ
ripple delay
                 x_i - 1
                                terminating carry
skip delay2
                 (m+1-i)T
x_i - 1 \leq iT
x_{i} - 1 \le (m+1-i)T
x_i \leq 1 + iT
x_i \le 1 + (m+1-i)T
x_i \le \min \{1 + iT, 1 + (m+1-i)T\}
X_i \leq y_i
y_i = \min \{1 + iT, 1 + (m+1-i)T\}
```

$$y_i = min\{1+iT, 1+(m+1-i)T\}, i = 1,...,m$$

the scheme (i), (ii), (iii) gives the max prop time *mT* 

$$y_1 = min\{1+1\cdot T, 1+(m+1-1)T\} = 1+T$$
  
 $y_m = min\{1+m\cdot T, 1+(m+1-m)T\} = 1+T$ 


$$x_1 \le y_1 = 1 + T$$

$$x_{m} \leq y_{m} = 1 + T$$

$$\begin{array}{lll} x_1 \ -1 \le 1T & & x_1 \ -1 \le T \\ x_1 \ -1 \le (m+1-1)T & & x_1 \ -1 \le mT \end{array}$$

$$\begin{array}{lll} x_m - 1 \leq mT & & x_m - 1 \leq mT \\ x_m - 1 \leq (m+1-m)T & & x_m - 1 \leq T \end{array}$$

#### maximum propagation time

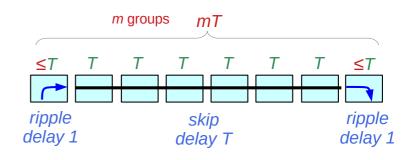

$$P_{max} = P_{1,m} \le mT$$

$$P = P_{i,j} \leq mT$$

**Lemma 1** When the bits of a carry skip adder are grouped according to the scheme (i)-(iii), the maximum propagation time of a carry signal is *mT* 


the scheme (i), (ii), (iii) gives the max prop time *mT* 

The carry generated at the  $2^{nd}$  bit position and terminating at the  $(n-1)^{th}$  bit position clearly has propagation time mT.

We must show that *any other* carry signal has propagation time  $\underline{smaller}$  than or equal to  $\underline{mT}$ 

propagation time of a carry signal  $\leq mT$ the maximum propagation time = mT

#### maximum propagation time

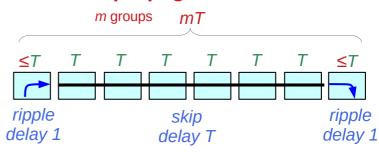

$$P_{max} = P_{1,m} \leq mT$$

### Procedure

(I) Let m be the smallest positive integer

$$n \leq \sum_{i=1}^{m} y_i \qquad i = 1, ..., m$$

$$i = 1, ..., m$$

(II) Let

$$y_i = min\{1+iT,1+(m+1-i)T\}$$

(III) Let  $x_i$ , i = 1, ..., m

starting with the first row, row by row

$$n = \sum_{i=1}^{m} x_i \le \sum_{i=1}^{m} y_i$$

Variable block size =  $x_i$  bits for the i-th group

the scheme (i), (ii), (iii) gives the max propagation time mT

Oklobdzija: High-Speed VLSI arithmetic units: adders and multipliers

#### find the smallest m

$$n \leq \sum_{i=1}^{m} y_i = \sum_{i=1}^{m} \min\{1+iT, 1+(m+1-i)T\}$$

$$m = 2;$$
  
while  $(y_1 + \dots + y_m < n)$   $m = m+1;$ 

### **Propagation Time P**

#### find the <u>smallest</u> *m*


$$n \leq \sum_{i=1}^{m} y_i = \sum_{i=1}^{m} \min\{1+iT, 1+(m+1-i)T\}$$

$$m = 2;$$
  
while  $(y_1 + \dots + y_m < n)$   $m = m+1;$ 


the scheme (i), (ii), (iii) gives the max propagation time mT

propagation time of a carry signal  $\leq mT$ the maximum propagation time = mT

#### propagation time

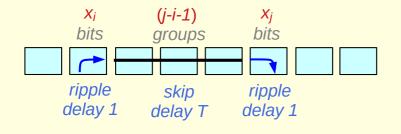
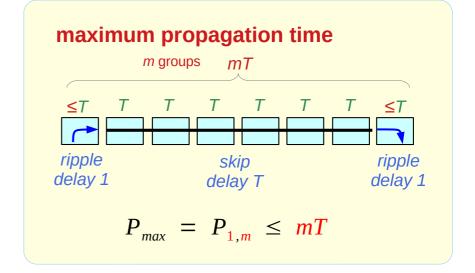
$$P = P_{i,j} \qquad \forall i, \forall j \quad 1 \leq i, j \leq m$$



### Maximum delay and optimal group size

the maximum propagation time  $\infty$  the number of groups

 $D \propto m$ 

- <u>not</u> an optimal optimal division
  - larger number of groups →
  - larger delays →

- when group size m is not optimal
   then there is an optimal group size = r
  - the maximum delay with the group size m  $D_m = mT$
  - the maximum delay with the group size r  $D_r = rT$
  - r must be smaller than m  $r \le m$

$$D_r < D_m$$

$$\rightarrow rT < mT$$

$$\rightarrow r < m$$

## Maximum delay of a carry signal

**Lemma 2** Let *D* denote the maximum delay of a carry signal in a *n* bit carry skip adder with group sizes chosen optimally. Then


• r groups

$$(m-1)T \leq D \leq mT$$

Since we have exhibited a <u>division</u> of the carry chain into groups In such a way that the <u>maximum delay</u> of a carry signal is mT We clearly have  $D \leq mT$ 

the maximum delay = D the optimal group size = m

$$(m-1)T \leq D \leq mT$$

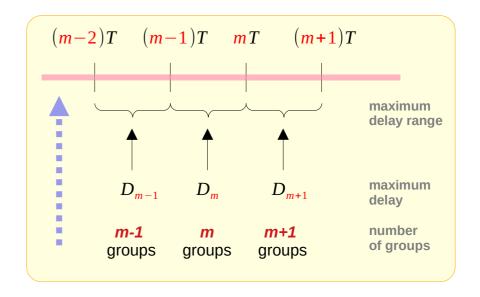


## Maximum delay of a carry signal

$$(m-1)T \leq D \leq mT$$

Assume there are **r** groups the propagation delay of P: any carry signal path  $\leq mT$ then 2 cases: even r, odd r upper bound for each of these 2 cases the max of P D: prove mT - D < T + 1 $\longrightarrow$   $mT-D \leq T$  $diff(mT, D) \leq T$  $(m-1)T \leq D$ diff  $(mT, max P) \leq T$ lower bound  $(m-1)T \leq D$ 
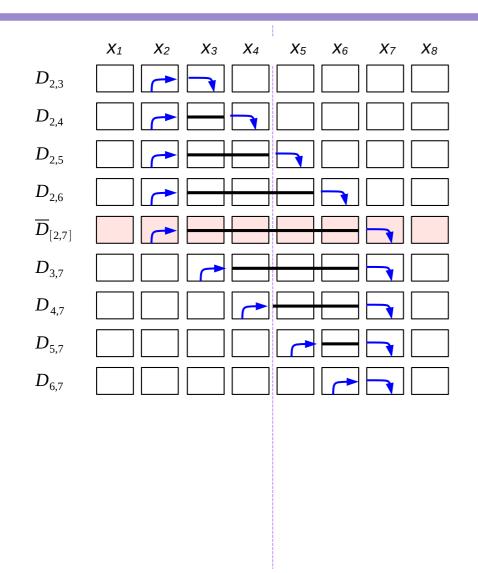
## Maximum delays of carry signals (r = 2k)




 $\overline{D}_{[2,7]}$  = the maximum delay of carry signals  $\leq D$  generated in the i-th group and terminated in the j-th group such that  $2 \leq i, j \leq 7$ 

$$\overline{D}_{[2,7]} = \max \left\{ \begin{bmatrix} D_{2,3}, & D_{2,4}, & D_{2,5}, & D_{2,6}, \\ & D_{2,7}, & \\ D_{3,7}, & D_{4,7}, & D_{5,7}, & D_{6,7} \end{bmatrix} \right\}$$

$$\overline{D}_{[2,7]} = \overline{D}_{[2,8-2+1]} = \overline{D}_{[s,8-s+1]}, s = 2$$

 $\overline{D}_{[s,r-s+1]}$  = the maximum delay of carry signals generated in the i-th group and terminated in the j-th group such that  $s \le i, j \le r-s+1$ 
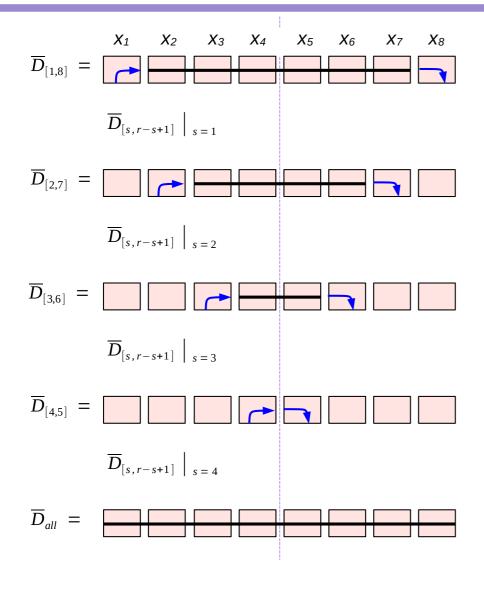
## Maximum delays of carry signals (r = 2k)



Oklobdzija: High-Speed VLSI arithmetic units: adders and multipliers

$$\overline{D}_{[1,8]} =$$
 The maximum delay of carry signals  $\leq D$  generated in the i-th group or terminated in the j-th group such that  $1 \leq i, j \leq 8$ 

$$\overline{D}_{[2,7]} =$$
The maximum delay of carry signals  $\leq D$  generated in the i-th group or terminated in the j-th group such that  $2 \leq i$ ,  $j \leq 7$ 

$$\overline{D}_{[3,6]} =$$
 The maximum delay of carry signals  $\leq D$  generated in the i-th group or terminated in the j-th group such that  $3 \leq i, j \leq 6$ 


$$\overline{D}_{[4,5]} =$$
 The maximum delay of carry signals  $\leq D$  generated in the i-th group or terminated in the j-th group such that  $4 \leq i, j \leq 5$ 

$$\overline{D}_{all} = All \, skip \, delay$$

$$_{D}=\max\{\overline{D}_{[1,8]},\ \overline{D}_{[2,7]},\ \overline{D}_{[3,6]},\ \overline{D}_{[4,5]}\}$$
 Max delay of all carry signals

 $\leq D$ 
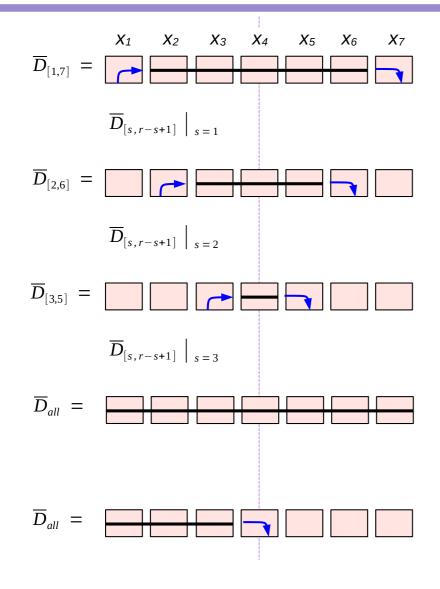
## Maximum delays of carry signals (r = 2k+1)



Oklobdzija: High-Speed VLSI arithmetic units: adders and multipliers

$$\overline{D}_{[1,7]} =$$
 The maximum delay of carry signals  $\leq D$  generated in the i-th group or terminated in the j-th group such that  $1 \leq i, j \leq 8$ 

$$\overline{D}_{[2,6]} =$$
The maximum delay of carry signals  $\leq D$  generated in the i-th group or terminated in the j-th group such that  $2 \leq i, j \leq 7$ 

$$\overline{D}_{[3,65]} =$$
 The maximum delay of carry signals  $\leq D$  generated in the i-th group or terminated in the j-th group such that  $3 \leq i$ ,  $j \leq 6$ 

$$\overline{D}_{all} = All \, \text{skip delay}$$

$$\widetilde{D}_{all}$$
 = Comparable to all skip delay

$$D = max\{\overline{D}_{[1,8]}, \overline{D}_{[2,7]}, \overline{D}_{[3,6]}, \overline{D}_{[4,5]}\}$$

Max delay of all carry signals

 $\leq D$ 

## Maximum delays of carry signals (r = 2k)


$$\begin{array}{rcl}
D &=& \underset{s=1}{max} & \overline{D}_{[s,r-s+1]} \\
&=& \underset{s=1}{\overset{k}{max}} & \overline{D}_{[s,2k+1-s]} \\
&=& \underset{s=1}{\overset{4}{max}} & \overline{D}_{[s,9-s]}
\end{array}$$

Max delay of all carry signals

s=1

 $|\overline{D}_{[2,r-1]}| = D$   $|\overline{D}_{[k,k+1]}| \leq D$   $|\overline{D}_{all}| \leq D$   $(m-1)T \leq D$ Lower bound of D

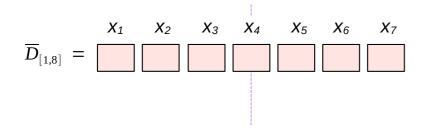
## Maximum delays of carry signals (r = 2k+1)



$$D = \max_{s=1}^{floor(r/2)} \overline{D}_{[s,r-s+1]}$$
$$= \max_{s=1}^{k} \overline{D}_{[s,2k+2-s]}$$


$$= \max_{s=1}^{3} \overline{D}_{[s,8-s]}$$

Max delay of all carry signals

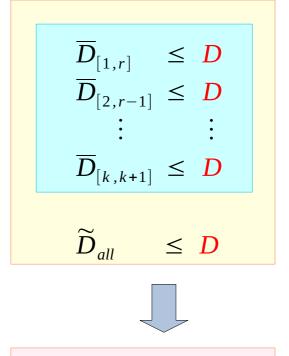


$$(m-1)T \leq D$$
Lower bound of D
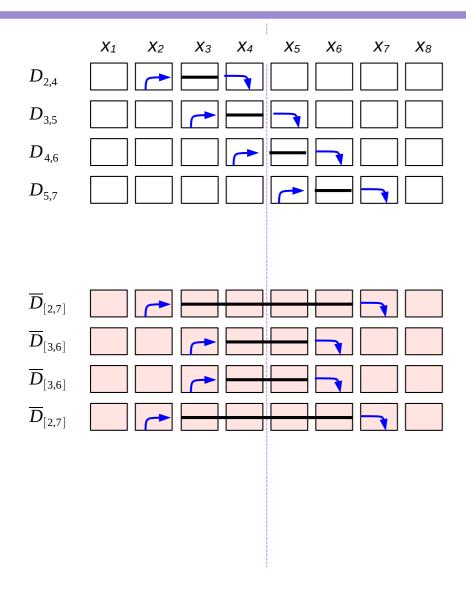
## Example delays of carry signals (r = 2k) (1)


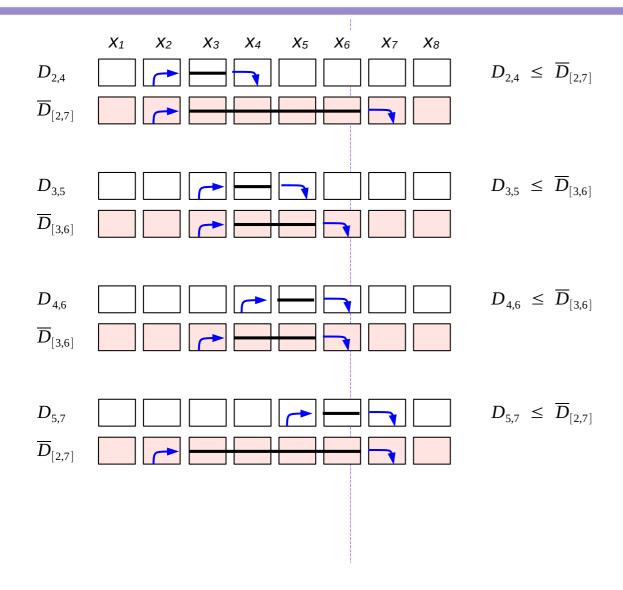
## Example delays of carry signals (r = 2k) (2)



## Optimal division into groups (1-1)

#### **Theorem 1**

The scheme 2(i) - 2(iii) given above for dividing the bits of a carry skip adder into groups is optimal for  $2 \le T \le 7$ 

dividing the bits into groups by the scheme 2(i) - 2(iii) gives m groups

propagation time of a carry signal  $\leq mT$  the maximum propagation time = mT

the maximum delay = Dthe optimal group size = m

$$(m-1)T \leq D \leq mT$$

Oklobdzija: High-Speed VLSI arithmetic units: adders and multipliers

(I) Let m be the smallest positive integer such that

$$n \le m + \frac{1}{2}mT + \frac{1}{4}m^2T + (1 - (-1)^m)\frac{1}{8}T$$

(II) Let 
$$y_i = min\{1+iT, 1+(m+1-i)T\},\ i = 1,...,m$$

and construct a histogram whose *i-th* column has height *y*,

(III) the area of the histogram in (II) is

$$m + \frac{1}{2}mT + \frac{1}{4}m^2T + (1-(-1)^m)\frac{1}{8}T \ge n$$

so these are <u>at least n unit squares</u> in the histogram starting with the first row, shade in n of the squares, <u>row by row</u>
Let  $x_i$  denote the number of shaded squares in column i of the histogram,

$$i = 1, ..., m$$

## Optimal division into groups (1-2)

#### **Assume**

- the scheme by 2(i) 2(iii) (m groups) is not optimal
- let D be the maximum delay corresponding to an optimal division of the bits into groups
- there are *r* groups in the optimal division.

Since a carry in signal to the least significant bit group can skip over each group

we have  $rT \le D \le mT$  so  $r \le m$ 

if m is <u>not</u> optimal, <u>but</u> r is then  $mT \ge rT$  (smaller delay rT) thus  $m \ge r$  (smaller r exists)

Oklobdzija: High-Speed VLSI arithmetic units: adders and multipliers

#### **m** groups

- <u>not</u> optimal division
- -D = maximum delay
- -mT skip delay

#### r groups

- optimal division
- *rT* skip delay

skip delay  $rT \le D \le mT$ 

 $r \leq m$ 

D = max delay is assumedTo be greater than all skipdelay rT of the optimal division

# Optimal division into groups (1-2)

If the optimal division gives *m* groups

$$m$$
 groups  $mT$  (m-1) groups  $mT$ 

Normally, by 2(i) - 2(iii) (m groups) is optimal and its maximum delay D is less than all skip delay mT

$$D \leq mT$$

To prove this, first, negate that

- m is not by the optimal division, but r is
- D is greater than all skip delay of the optimal division

$$D \leq mT$$

$$(m-1)T \leq D$$

- when optimal group size = m the maximum delay  $D_m \le mT$
- when optimal group size = (m-1)the maximum delay  $D_{m-1} \le (m-1)T$

D = maximum delay

$$rT \le D \le mT$$

$$r \le m$$
  $\longrightarrow$   $r < (m-1)$ 

```
rT \le D \le mT so r \le m
```

Optimal division : r groups  $D' \leq all \ skip \ delay \ rT \ (r \ groups)$ 

Non-optimal division : m groups  $D \le all \ skip \ delay \ mT \ (m \ groups)$ too many partitions  $m \ r \le m$ 

Assume max delay D is greater than all skip delay rT of the optimal division

if m is <u>not</u> optimal, <u>but</u> r is then  $mT \ge rT$  (smaller delay rT) thus  $m \ge r$  (smaller r exists)

D is max delay for m groups D' is max delay for r groups then  $D' \le rT \le D \le mT$ 

Oklobdzija: High-Speed VLSI arithmetic units: adders and multipliers

D = maximum delay $rT \le D \le mT$ 

 $r \le m$   $\longrightarrow$  r < (m-1)

we have  $rT \le D \le mT$  so  $r \le m$ 

If 
$$r = m$$
  
then  $D = mT$   $\longrightarrow$   $D = rT$   $rT = D$   
If  $r = m-1$ ,  $(r < m)$   
 $D \ge (m-1)T$   $\longrightarrow$   $D \ge (m-1)T = rT$   $rT \le D$   
if  $r < m-1$ ,  $(r < m)$   
 $D \ge (m-1)T$   $\longrightarrow$   $D \ge (m-1)T > rT$   $rT < D$ 

we have  $rT \le D \le mT$  so  $r \le m$ 

If r = m then D = mT and the **theorem** holds by **lemma** 1

When the bits of a carry skip adder are grouped according to the scheme (i)-(iii), the maximum propagation time of a carry signal is mT

 $(m-1)T \le D \le mT$ 

Oklobdzija: High-Speed VLSI arithmetic units: adders and multipliers

**Lemma 1** When the bits of a carry skip adder are grouped according to the scheme (i)-(iii), the maximum propagation time of a carry signal is mT

**Theorem 1** The scheme 2(i) - 2(iii) given above for dividing the bits of a carry skip adder into groups is optimal for  $2 \le T \le 7$ 

(5) 
$$r=2k$$
  $X = 4-T^2$ 

$$mT-D \le T + \frac{-8(T/n)+4}{\sqrt{4(T/n)+8(T/n^2)} + \sqrt{4(T/n)+4/n^2}}$$

$$r=2k+1 \qquad X = 4$$

$$mT-D \le T + \frac{(T-2)^2/n}{\sqrt{4(T/n)+4(T/n^2)} + \sqrt{4(T/n)+(T/n)^2+4/n^2}}$$

*m* groups – not optimal division *r* groups – optimal division

D = maximum delay

 $rT \le D \le mT$ 

 $r \leq m$ 

```
If r = m-1, (r < m)

m and r have different parities and

it follows from (5)

that mT - D \le T for 2 \le T \le 7
```

so that  $D \ge (m-1)T$ since r = m-1,  $D \ge (m-1)T = rT$   $rT \le D$ 

This means that a signal which skips over each of the r groups (rT) has delay less than the maximum D.

 $rT \le D \le mT$ 

*m* is <u>not</u> optimal division *r* is optimal division

Oklobdzija: High-Speed VLSI arithmetic units: adders and multipliers

**Lemma 1** When the bits of a carry skip adder are grouped according to the scheme (i)-(iii), the maximum propagation time of a carry signal is mT

**Theorem 1** The scheme 2(i) - 2(iii) given above for dividing the bits of a carry skip adder into groups is optimal for  $2 \le T \le 7$ 

$$(5) \quad r=2k \qquad \qquad X = 4 - T^2$$

$$mT-D \le T + \frac{-8(T/n)+4}{\sqrt{4(T/n)+8(T/n^2)} + \sqrt{4(T/n)+4/n^2}}$$

$$r=2k+1 \qquad X=4$$

$$mT-D \le T + \frac{(T-2)^2/n}{\sqrt{4(T/n)+4(T/n^2)} + \sqrt{4(T/n)+(T/n)^2+4/n^2}}$$

*m* groups – not optimal division *r* groups – optimal division

D = maximum delay

 $rT \le D \le mT$ 

 $r \leq m$ 

```
Similarly,
if r < m-1, (r < m)
(m-1)T \le D
since r < m-1,
rT < (m-1)T \le D
```

so that a signal which skips over each group has delay rT < D.

```
rT < D \le mT
```


*m* is <u>not</u> optimal division *r* is optimal division

*m* groups – not optimal division *r* groups – optimal division

*D* = maximum delay

 $rT \le D \le mT$ 

 $r \leq m$ 

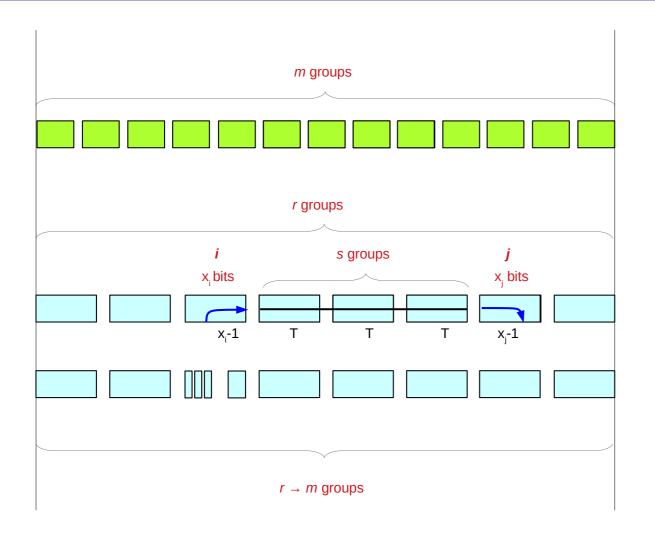

*m* groups – not optimal division *r* groups – optimal division

*D* = maximum delay

 $rT \le D \le mT$ 

 $r \leq m$ 

if **m** is <u>not</u> optimal, <u>but</u> **r** is


$$(((r +1) +1) +1) \dots \longrightarrow m$$
 contradiction!  $r$  must be  $m$ 

It follows that a signal with delay D

must <u>start</u> in a group *i*, <u>ripple</u> to the <u>end</u> of group *i*,

then skip over s < r groups and

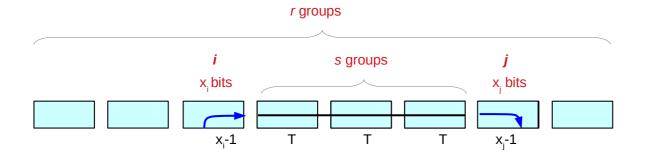either <u>terminate</u>, or <u>ripple</u> through the first few bits of a group j > i.



D = maximum delay

*r* groups – optimal division


*m* groups – not optimal division

 $rT \le D \le mT$ 


 $r \leq m$ 

Let  $x_i$  and  $x_j$  denote the lengths of the *i-th* and *j-th* groups respectively.

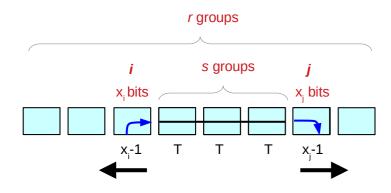Assume that i is chosen as <u>small</u> as possible and j as <u>large</u> as possible. (longer path)



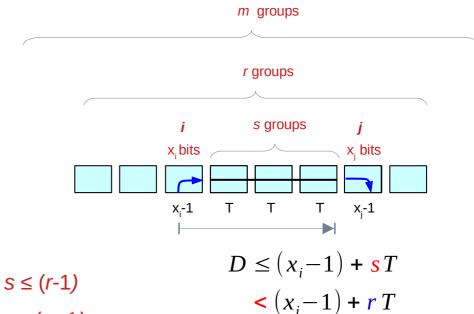A signal <u>originating</u> in group i, <u>rippling</u> to the end of this group i and then skipping over the next s group has delay  $(x_i - 1) + sT$ 



$$D \leq (x_i - 1) + sT$$

$$\leq (x_i - 1) + (r - 1)T$$

$$\leq (x_i - 1) + (m - 2)T.$$

$$s < r \text{ groups} \implies s \leq (r - 1)$$

$$r < m \text{ groups} \implies r \leq (m - 1)$$

$$s < r < m$$
  
 $s \le (r-1) < (m-1)$   
 $s \le (r-1) \le (m-2)$ 

Oklobdzija: High-Speed VLSI arithmetic units: adders and multipliers

if **m** is <u>not</u> optimal, <u>but</u> **r** is

 $<(x_i-1)+mT$ .

$$D \le (x_i - 1) + sT$$

$$\le (x_i - 1) + (r - 1)T$$

$$\le (x_i - 1) + (m - 2)T$$

$$(m-1)T \le D$$
  
 $D \le (x_i-1) + (m-2)T$ 

$$(m-1)T \le D \le (x_i-1) + (m-2)T$$

$$(m-1)T \le (x_i-1) + (m-2)T$$

$$T \le (x_i - 1)$$

$$T + 1 \le x_i$$


Since  $D \ge (m-1)T$ this implies that  $x_i \ge T+1$ 

Divide group *i* into two groups such that the group containing the msb has size T.

Since the *i*-th group is the first group in which a signal having maximum delay can originate,

this subdivision does not increase the delay of any carry signal of maximum delay

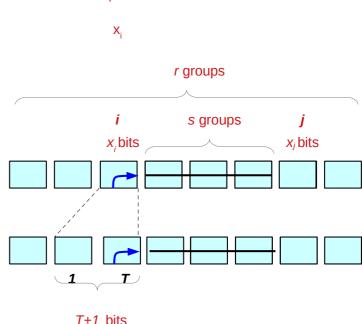However, it increases the number of groups by 1



 $x_i \ge T+1$  bits size

$$\begin{split} D &\leq (x_i - 1) + sT & (m - 1)T < D \\ &\leq (x_i - 1) + (r - 1)T & D < (x_i - 1) + (m - 2)T \\ &\leq (x_i - 1) + (m - 2)T. & x_i \geq (T + 1) \end{split}$$


Suppose now that a carry signal <u>originates</u> in a group i, <u>ripples</u> to its end, <u>skips</u> over  $s \le r-2$  groups and <u>finally ripples</u> through the first few bits of a group j and terminates.

### We then have

$$D \le (x_i - 1) + sT + (x_j - 1)$$
  
 
$$\le x_i + x_j - 2 + (m - 3)T$$

So that either  $x_i \ge T+1$  or  $x_i \ge T+1$ 
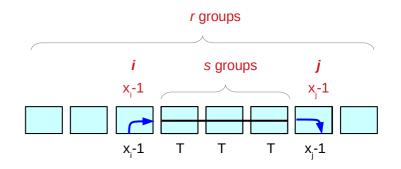
$$s < r$$
 groups  $s < r$  groups  $s \le (r-1)$  groups  $s \le (r-2)$  groups  $r < m$  groups  $r \le (m-1)$  groups  $r \le (m-2)$  groups




$$s < r < m$$

$$s \le (r-1) < (m-1)$$

$$s \le (r-1) \le (m-2)$$

$$s \le (r-2) \le (m-3)$$

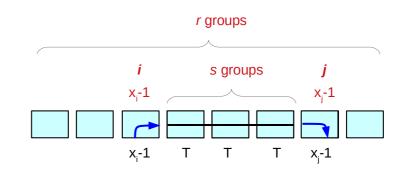

$$D \leq (x_{i}-1) + sT + (x_{j}-1)$$

$$\leq x_{i} + x_{j} - 2 + (r-2)T$$

$$\leq x_{i} + x_{j} - 2 + (m-3)T$$

$$(m-1)T < D$$

$$D < (x_i-1) + (m-2)T \qquad \Longrightarrow x_i \ge (T+1)$$

$$D < (x_i-1) + (m-2)T \qquad \Longrightarrow x_i \ge (T+1)$$

 $s \leq (r-2)$ 


So that either  $x_i \ge T+1$  or  $x_i \ge T+1$ 

So that either  $x_i \ge T+1$  or  $x_j \ge T+1$ 

This means that we can subdivide one of the groups *i*, *j* without increasing *D* not both of them

Continuing in this way, we can always increase the number r of group in an optimal division of a carry chain by 1 without increasing D if r < m

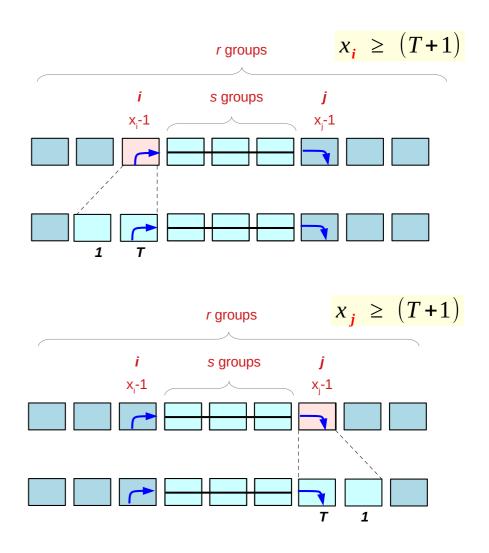
This means that we can arrive at an optimal division of the carry chain into m groups.



$$x_i \geq (T+1) > (T+2) \cdots$$

$$x_i \geq (T+1)$$

$$x_i \geq (T+2)$$

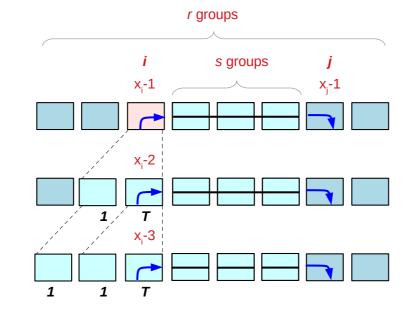

$$D \le (x_i - 1) + sT$$
  

$$\le (x_i - 1) + (r - 1)T$$
  


$$\le (x_i - 1) + (m - 2)T$$

$$(m-1)T \le D \le (x_i-1) + (m-2)T$$

if m is <u>not</u> optimal, <u>but</u> r is

$$(((r +1) +1) +1) \dots \longrightarrow m$$

contradiction! m must be r

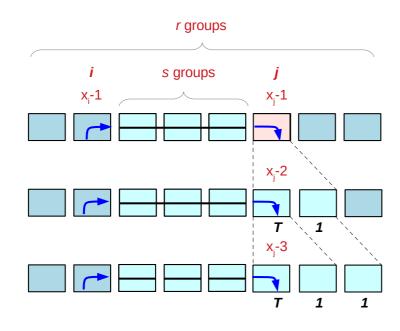

if m is <u>not</u> optimal, <u>but</u> r is

$$(((r +1) +1) +1) \dots \longrightarrow m$$
contradiction!  $m$  must be  $r$ 

$$x_i \geq (T+1) > (T+2) \cdots$$

$$x_i \geq (T+1)$$


$$x_i \geq (T+2)$$


$$D \le (x_i - 1) + sT$$

$$\le (x_i - 1) + (r - 1)T$$

$$\le (x_i - 1) + (m - 2)T$$


$$(m-1)T \le D \le (x_i-1) + (m-2)T$$

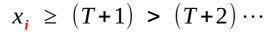

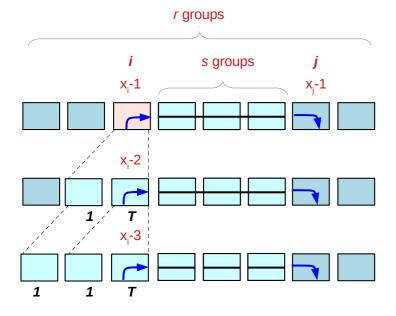

if m is <u>not</u> optimal, <u>but</u> r is  $(((r +1) +1) +1) \dots \longrightarrow m$ contradiction! m must be r

$$x_j \geq (T+1) > (T+2) \cdots$$

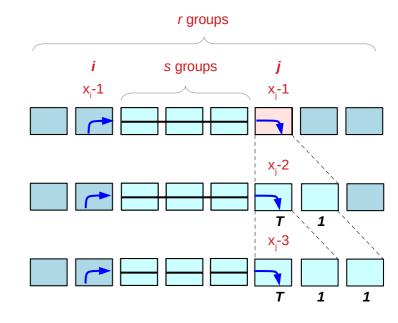

if 
$$m$$
 is not optimal, but  $r$  is
$$(((r +1) +1) +1) ... \longrightarrow m$$
contradiction!  $m$  must be  $r$ 

Normally, by 2(i) - 2(iii) (m groups) is optimal and its maximum delay D is less than all skip delay mT

 $D \leq mT$ 

To prove this, first, negate that

- m is <u>not</u> by the optimal division, but r is
- D is greater than all skip delay of the optimal division

### **Assume**

- the scheme by 2(i) 2(iii)
   (*m* groups) is not optimal
- let D be the maximum delay corresponding to an optimal division
- there are **r** groups in the optimal division.

$$(...(((r+1)+1)+1) ... +1) \rightarrow m : optimal$$

if **m** is <u>not</u> optimal, <u>but</u> **r** is

$$(((r +1) +1) +1) \dots \longrightarrow m$$

contradiction! m must be r

We must then have  $D \ge mT$  which, together with **Lemma 2**, Implies D = mT

This completes the proof of the theorem

*m* groups – not optimal division *r* groups – optimal division

D = maximum delay

 $rT \le D \le mT$ 

 $r \leq m$ 

Oklobdzija: High-Speed VLSI arithmetic units: adders and multipliers

### Lemma 2

Let *D* denote the maximum delay of a carry signal in a *n* bit carry skip adder with group sizes chosen optimally.

$$(m-1)T \leq D \leq mT$$

#### Theorem 1

The scheme 2(i) - 2(iii) given above for dividing the bits of a carry skip adder into groups is optimal for  $2 \le T \le 7$