

Tiny CPU - ISA (2A)


Copyright (c) 2014 - 2016 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".

Please send corrections (or suggestions) to youngwlim@hotmail.com.



This document was produced by using LibreOffice and Octave.

CPU and MEM

 



Based on <http://www.ele.uri.edu/Courses/ele306/f01/Tinydoc.pdf>

Memory Data Register

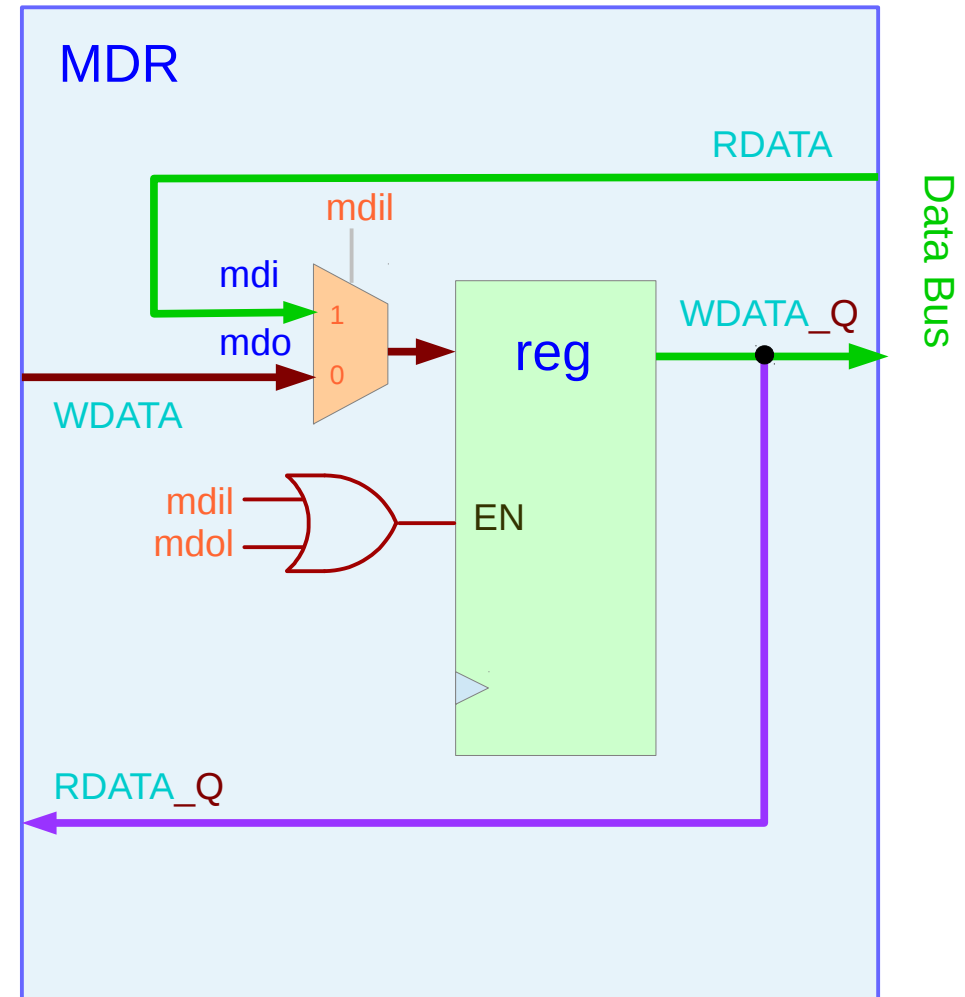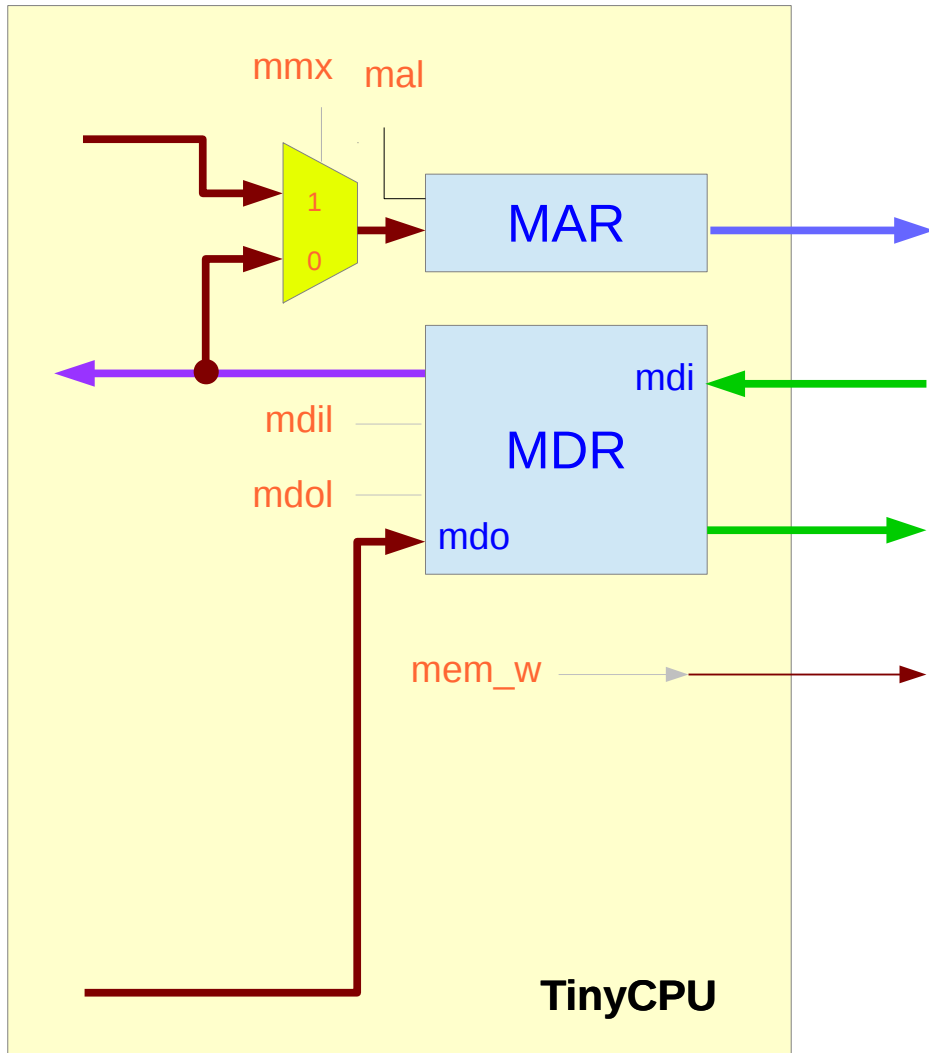


Based on <http://www.ele.uri.edu/Courses/ele306/f01/Tinydoc.pdf>


Memory Access Operations

  





Memory Interface

 




Memory Map

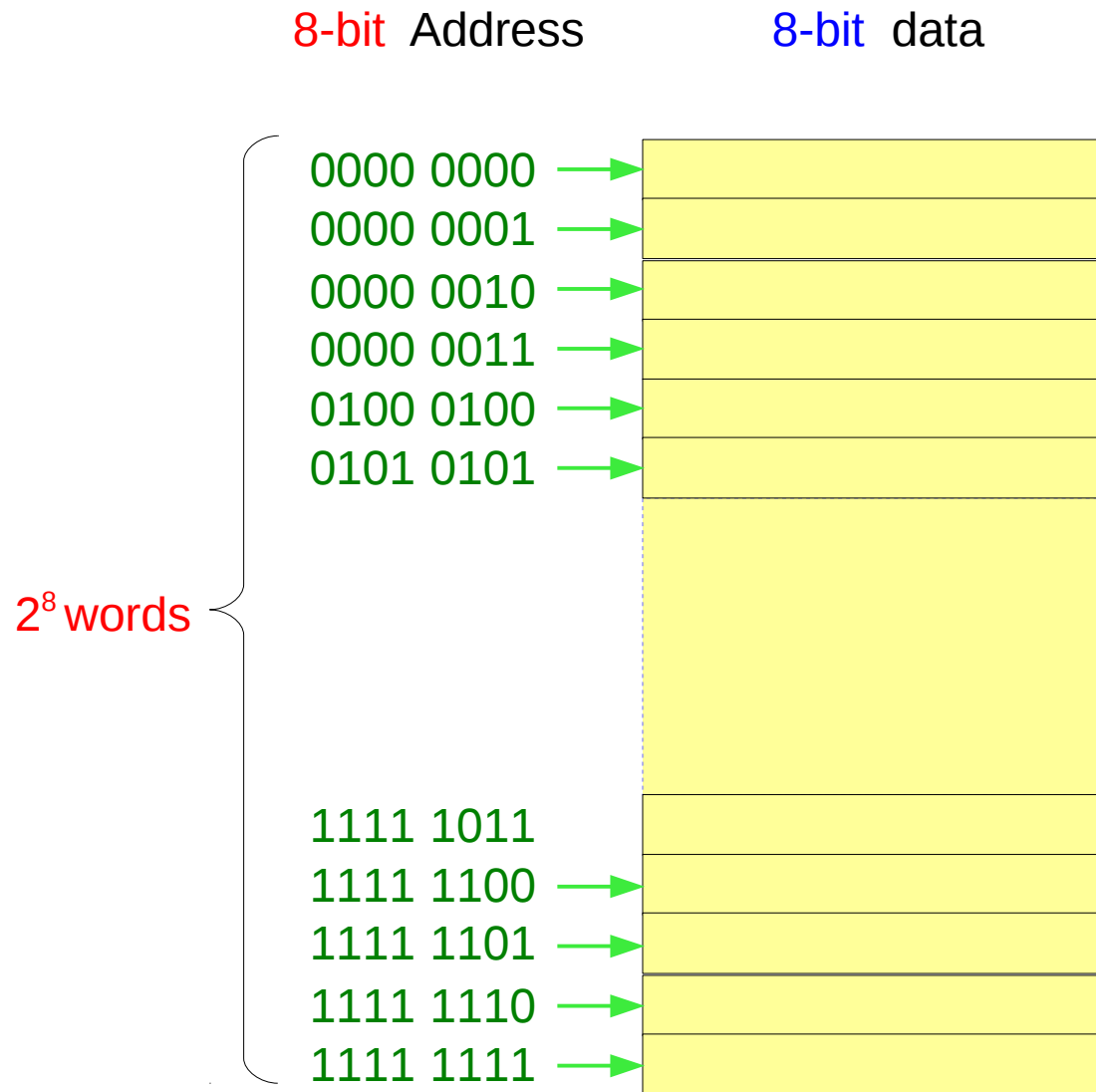




Memory Write Cycle

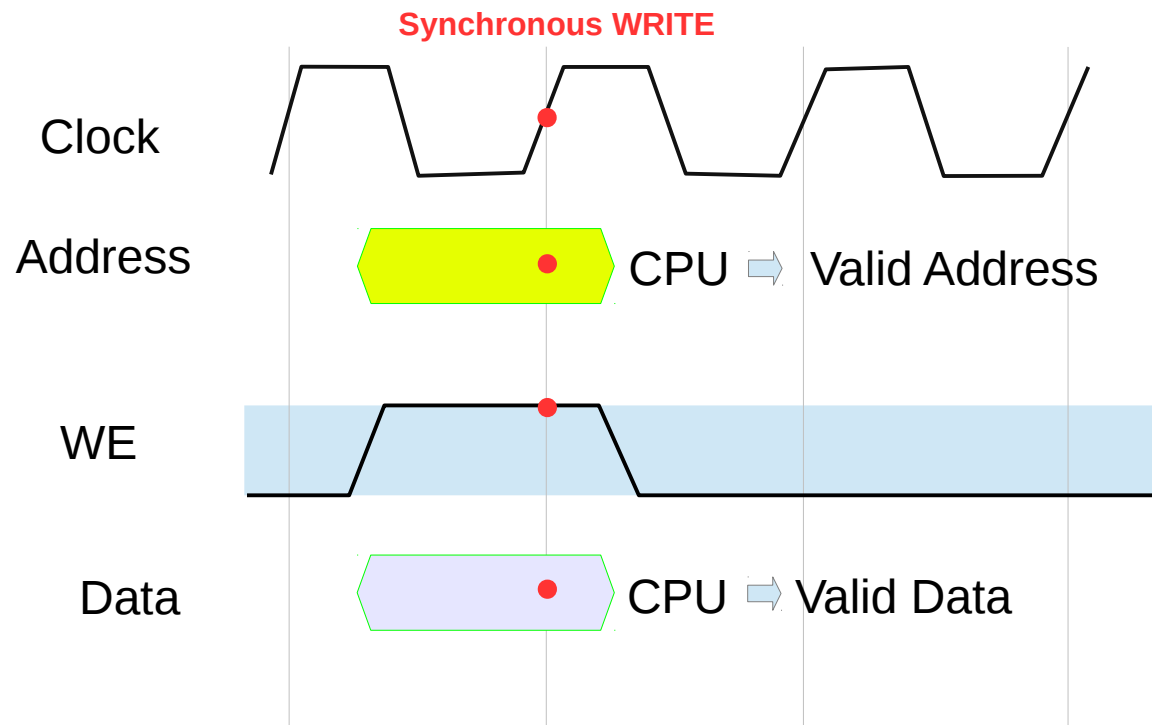   





Memory Read Cycle - Synchronous

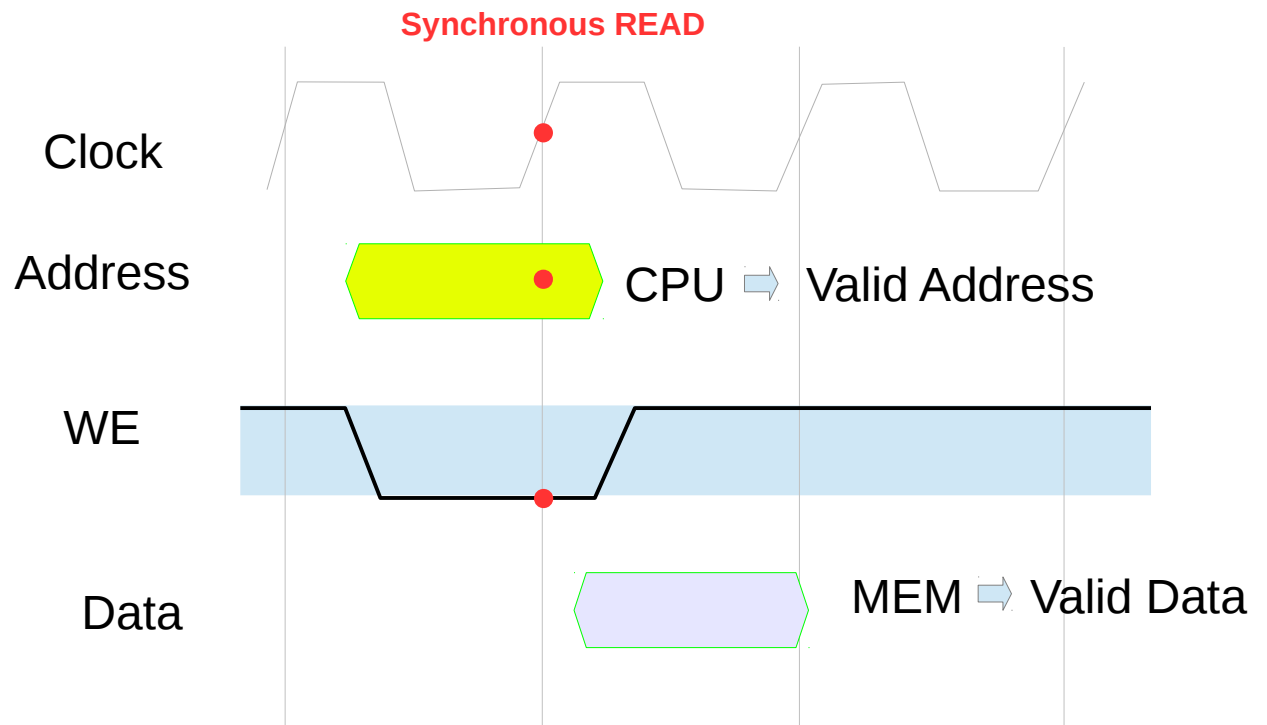  

Memory Read Cycle - Asynchronous

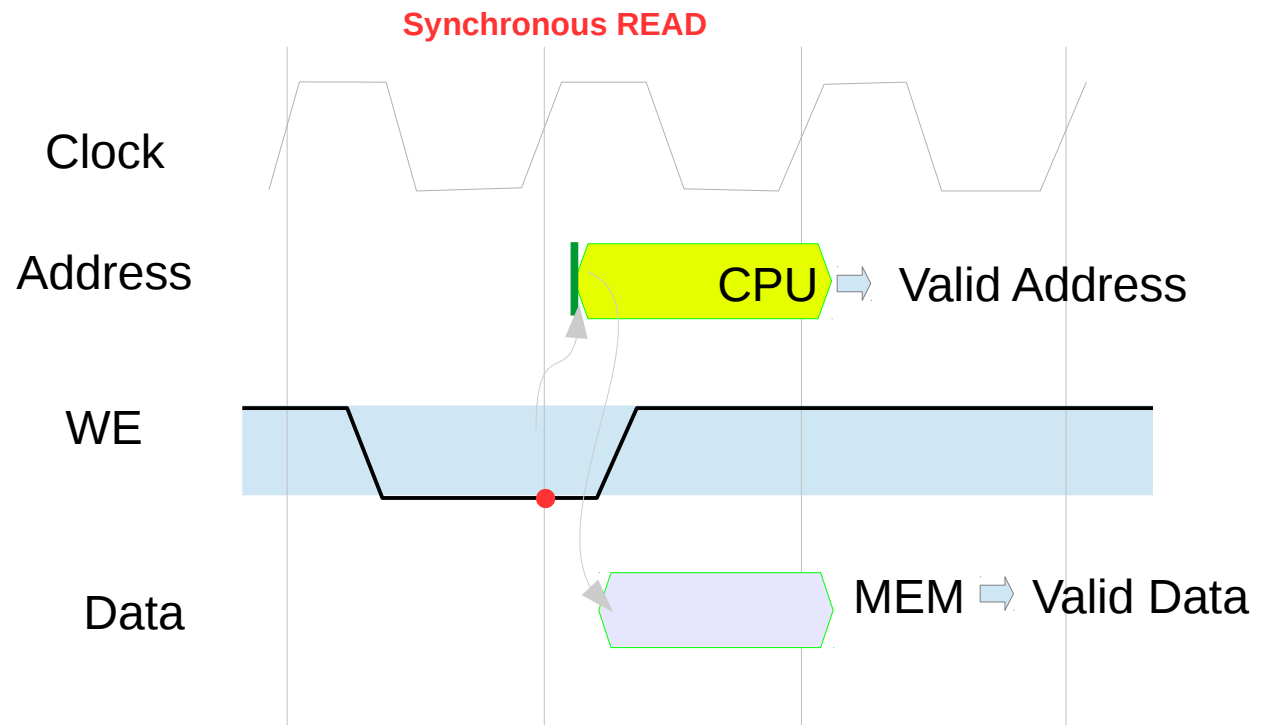 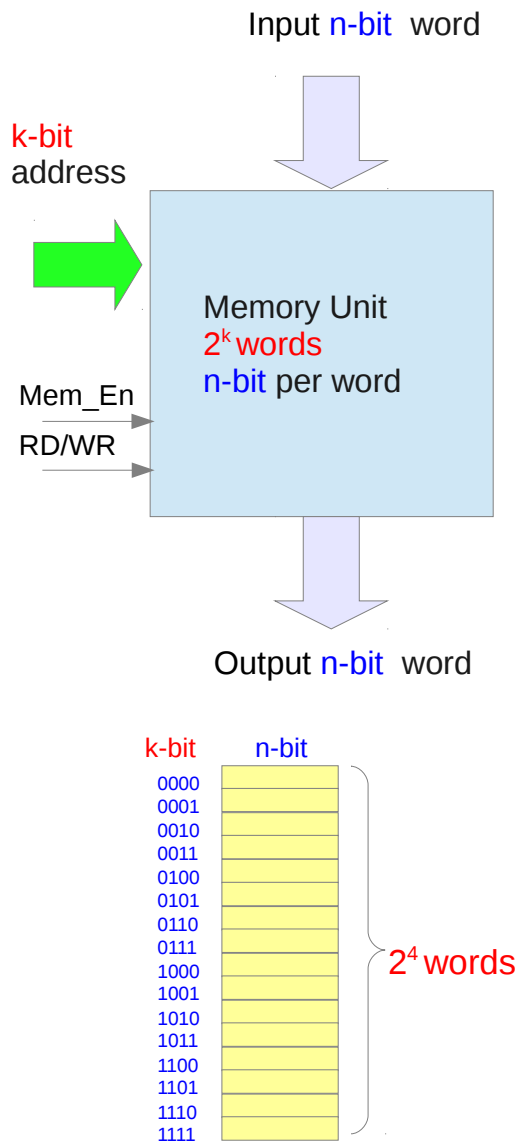

Async & Sync Read Cycle

    

Virtex LUT RAM

```
module ram16x1(q, a, d, we, clk);  
output    q;  
input     d;  
input [3:0] a;  
input     clk, we;
```

```
reg       mem [15:0];
```

```
always @(posedge clk) begin  
    if(we)  
        mem[a] <= d;  
end
```

```
assign q = mem[a];
```


```
endmodule
```

Synchronous
Write

Asynchronous
Read

<http://www-inst.eecs.berkeley.edu/~cs150>

LUT RAM Timing

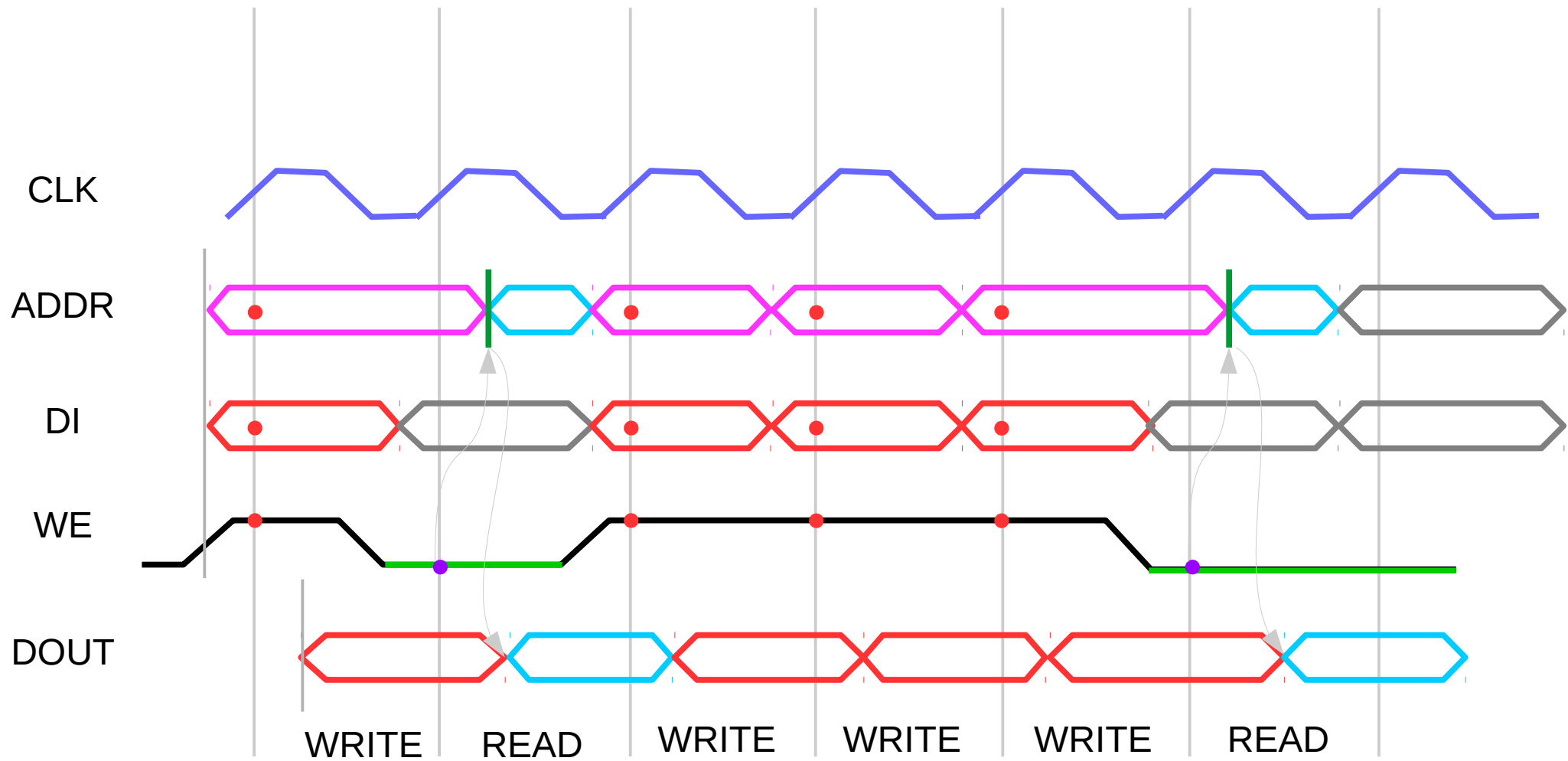


Xilinx Document

Virtex Block RAM




Every block SelectRAM

 - synchronous write
- synchronous read
- dual-ported
- independent control signals
- independent data widths
- independent CLKA & CLKB
- 4096-bit RAM






<http://www-inst.eecs.berkeley.edu/~cs150>




Sync **RD** Cycle - worst & best case

  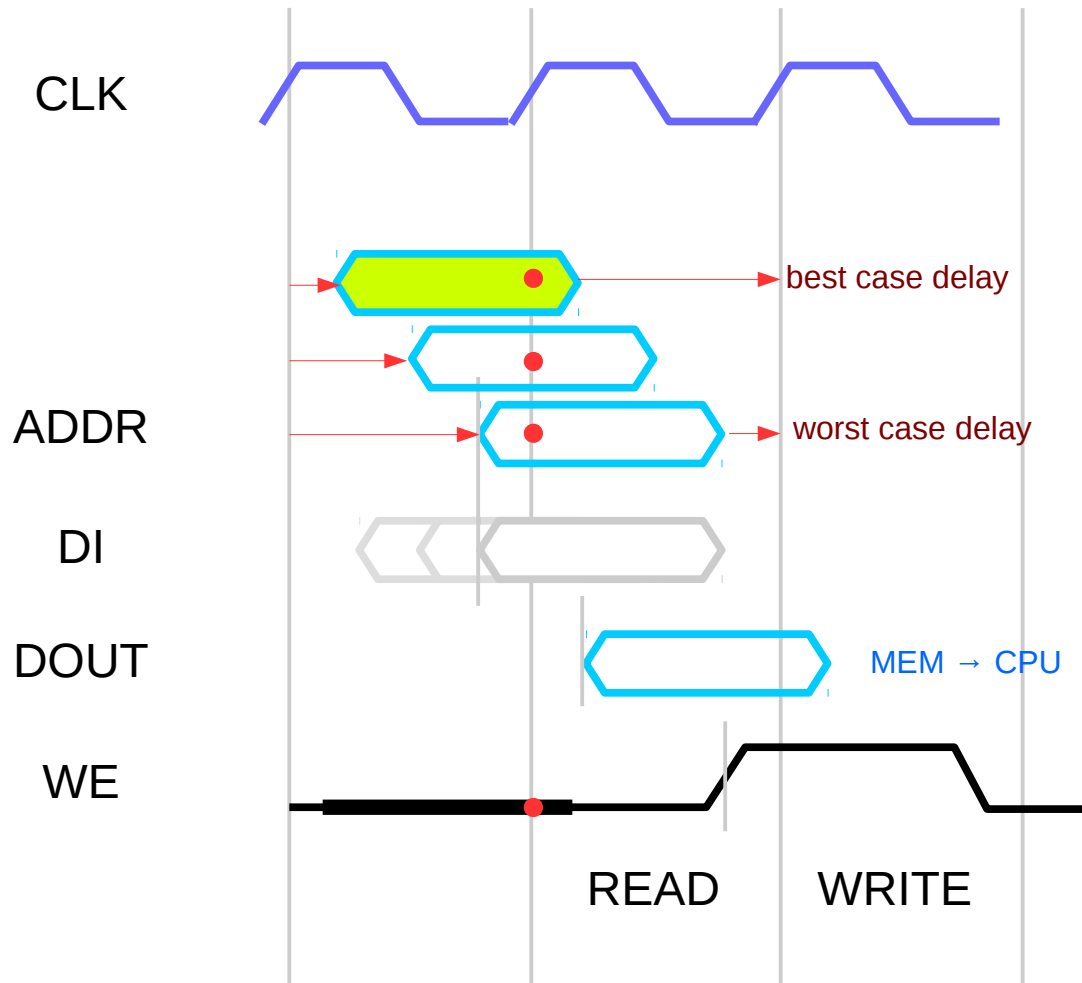

Async **RD** Cycle - worst & best case

  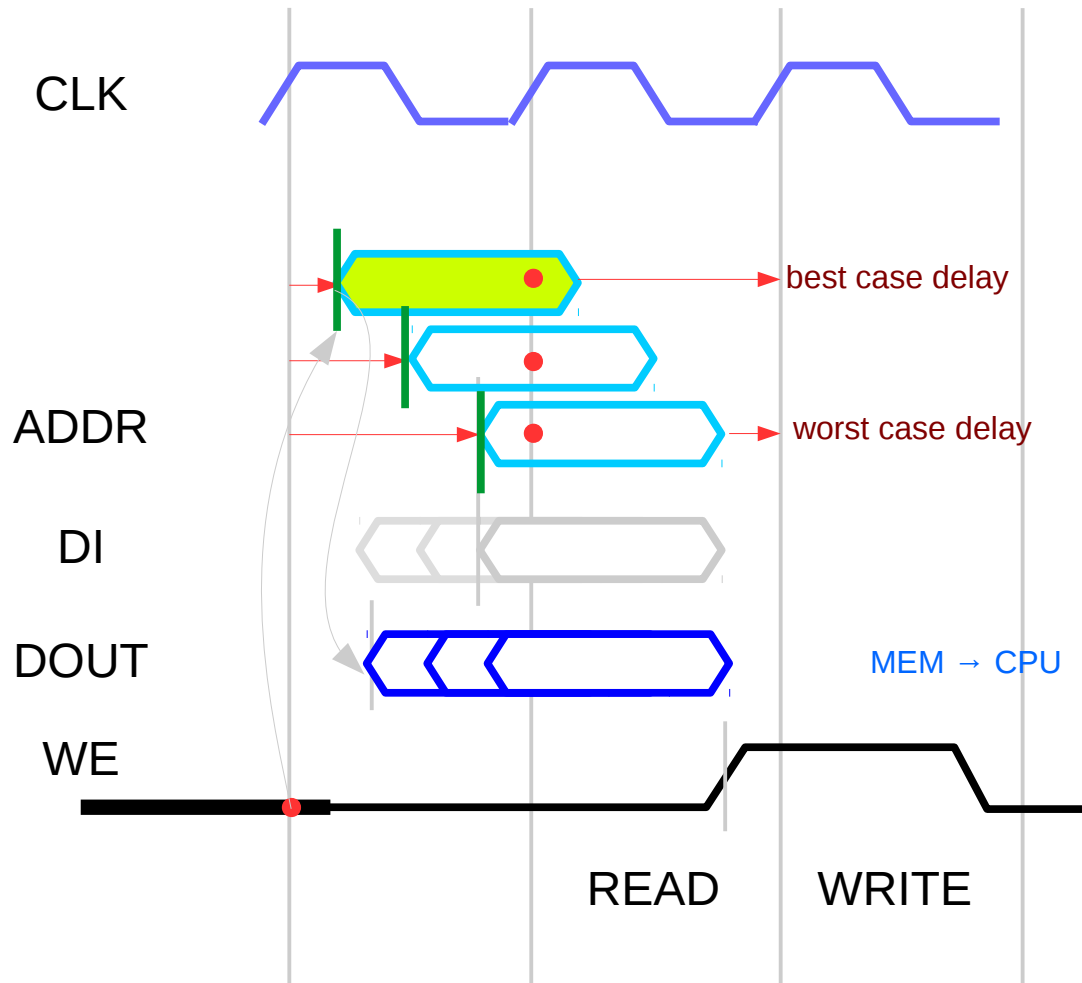

WR Cycle - worst & best case

  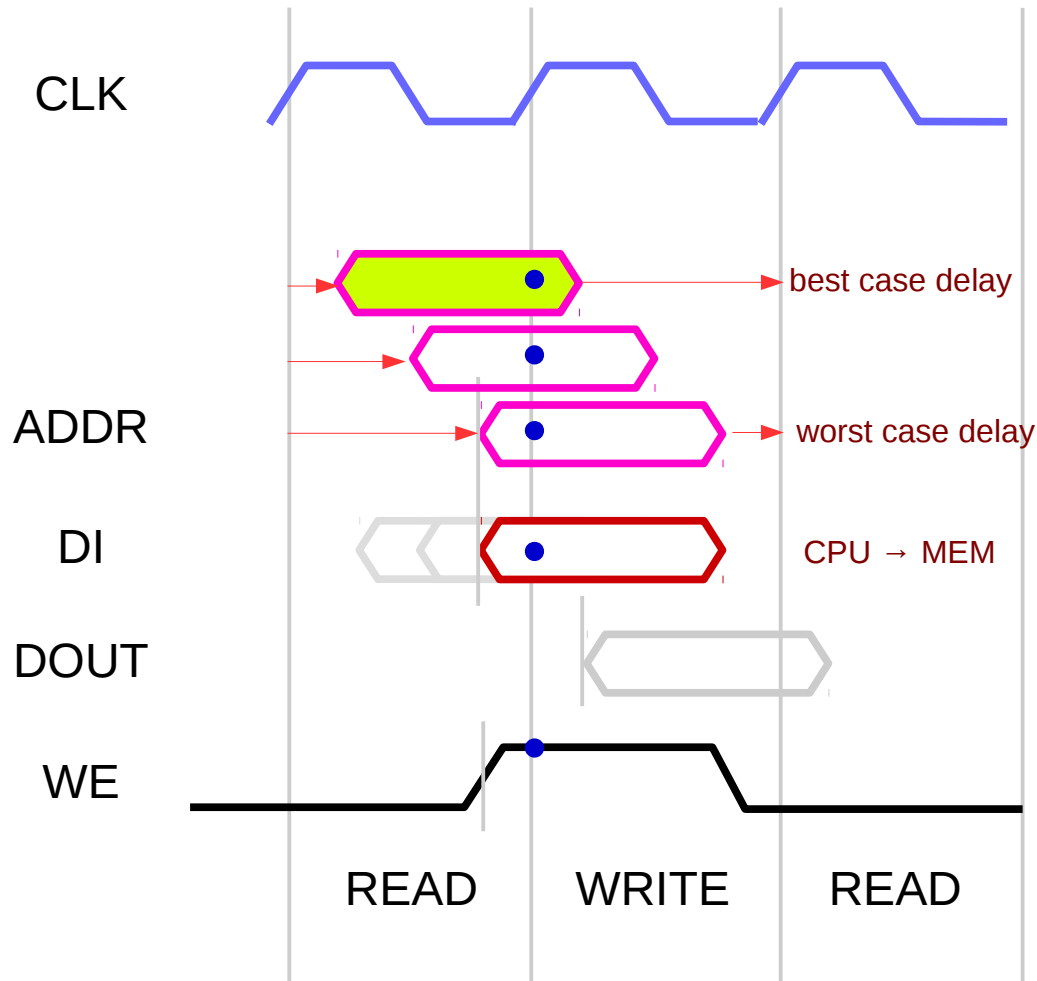

Waveform Viewer Timing (1)

* timing figures without delay (Ideal case)


RTL functional simulation

* timing figures with delay


Gate level simulation
with SDF annotation

Waveform Viewer Timing (2)

Sync WRITE

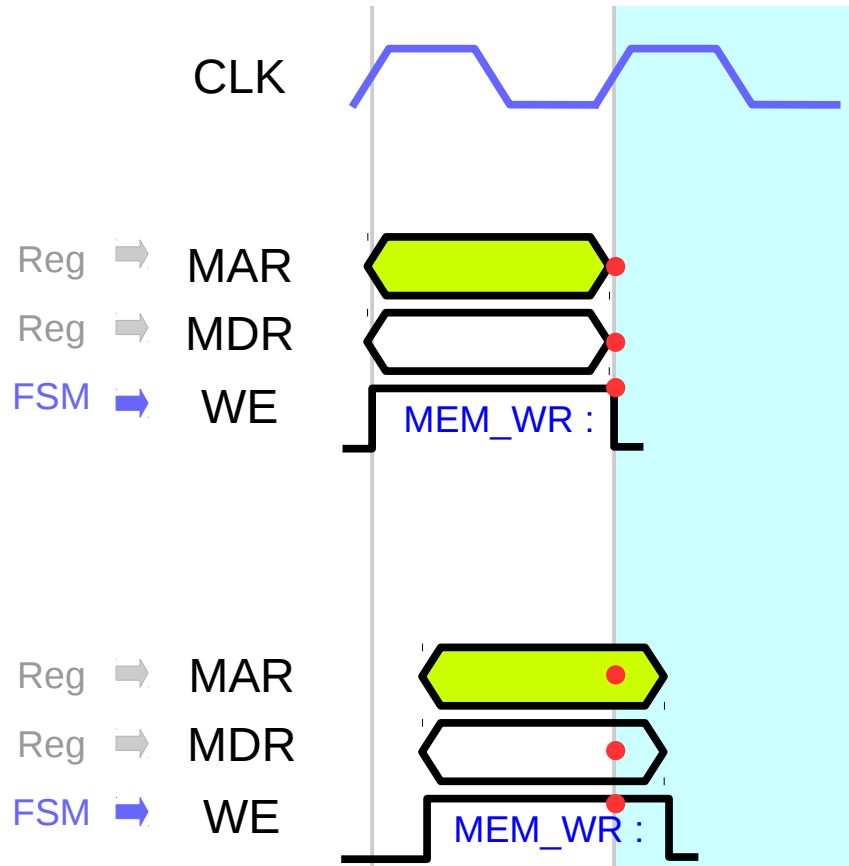

Sync READ

 

timing figures without delay (Ideal case)

timing figures with delay


unintended write cycle!

MEM_RD: One cycle ahead

Waveform Viewer Timing (3)

Sync READ



Async READ

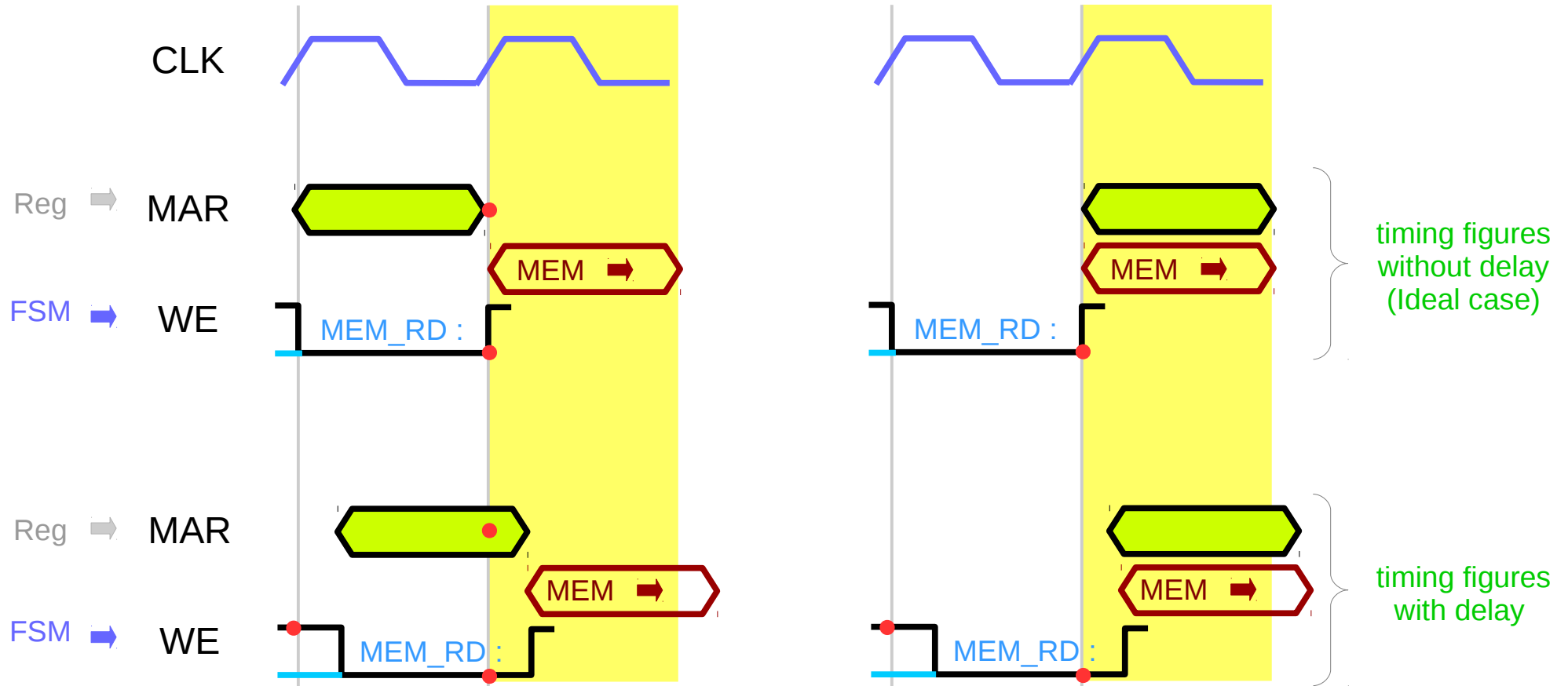

unintended write cycle!


MEM_RD :
One cycle ahead

LUT as a combination logic block

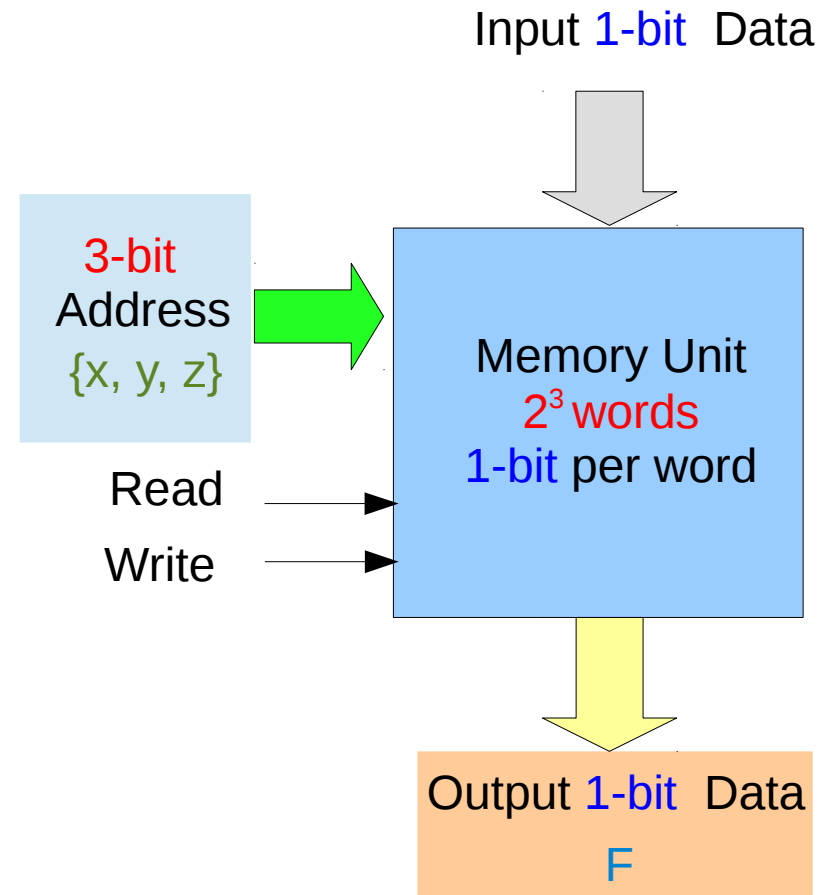 

LUT : Async Read


Async READ

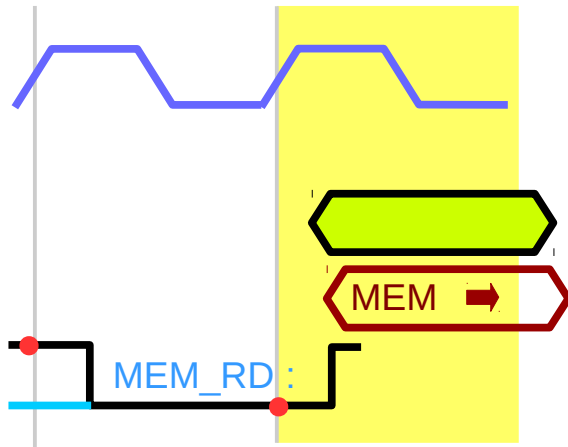


Address : Inputs
Data : Outputs

The outputs available in the same cycle where the inputs are applied

 
Combinational Logic Block :
A set of Boolean Functions



LUT Data Write

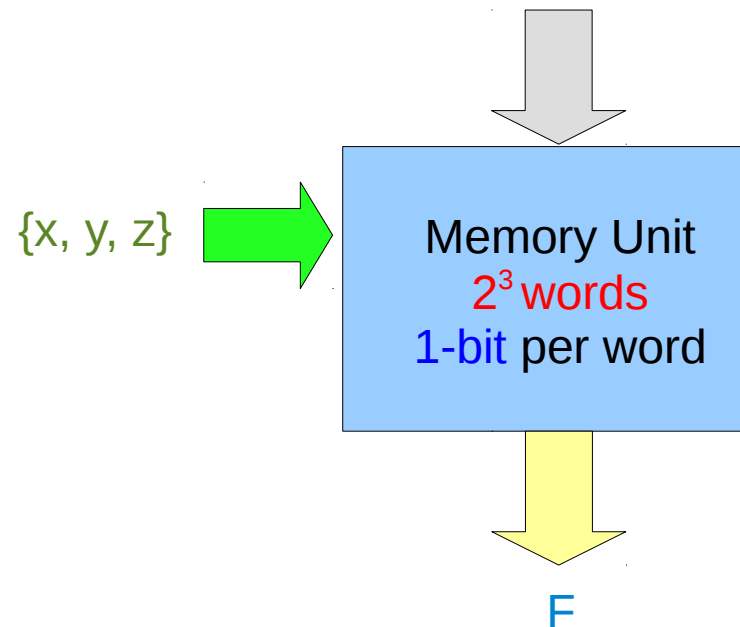


Instruction Set Architecture

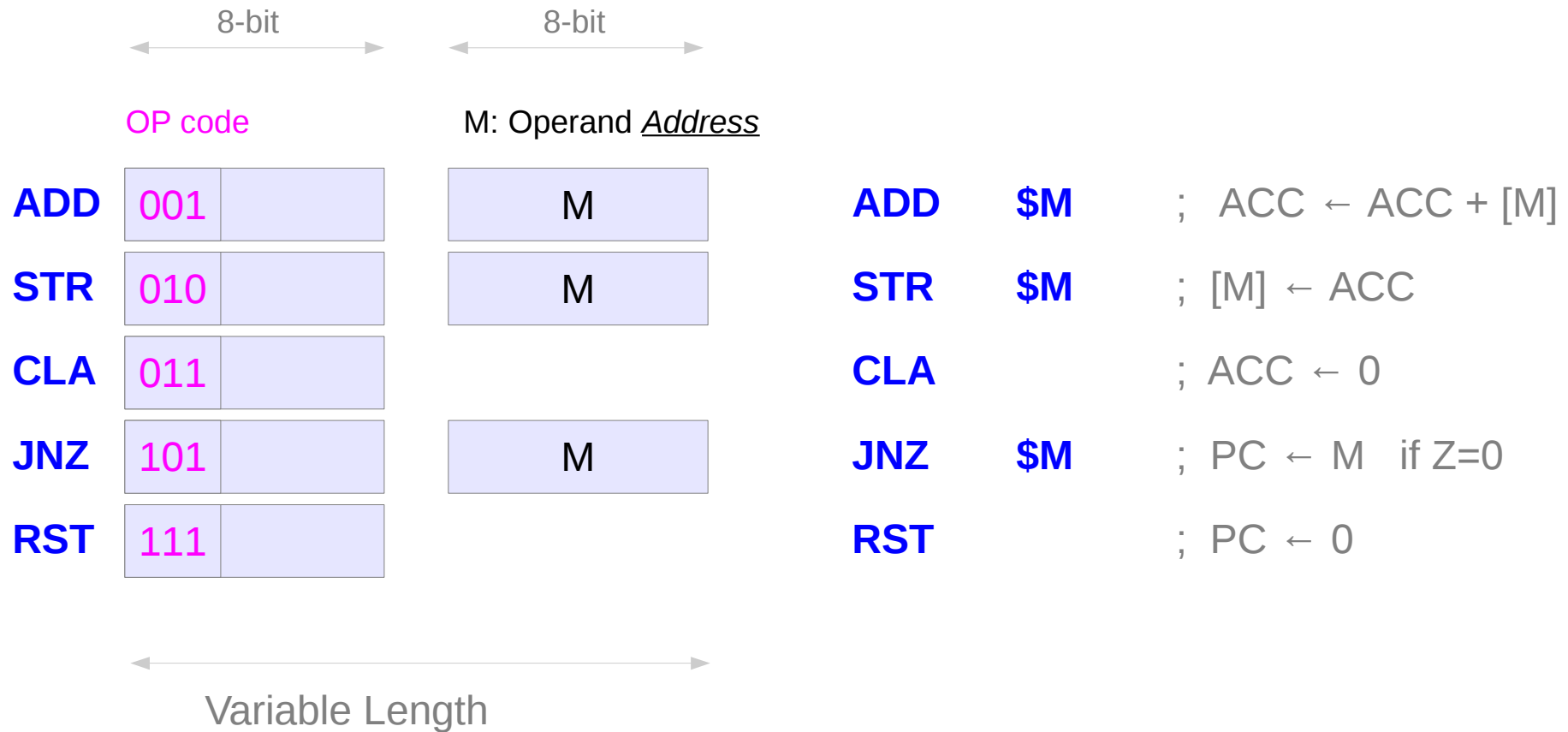

Based on <http://www.ele.uri.edu/Courses/ele306/f01/Tinydoc.pdf>

ADD Operation


ADD \$M ; ACC ← ACC + [M]

 

Based on <http://www.ele.uri.edu/Courses/ele306/f01/Tinydoc.pdf>

STR Operation



STR **\$M** ; [M] ← ACC

 

Based on <http://www.ele.uri.edu/Courses/ele306/f01/Tinydoc.pdf>

CLA Operation


```
CLA ; ACC ← 0
```

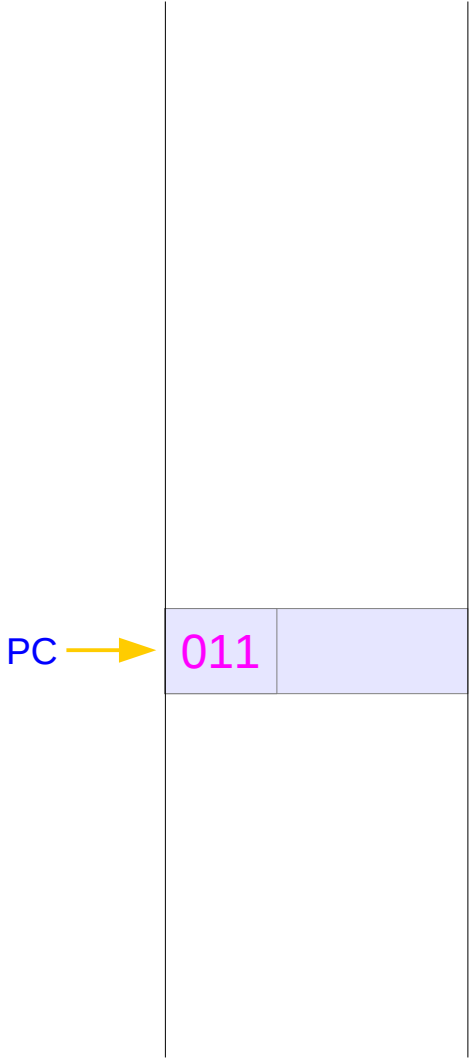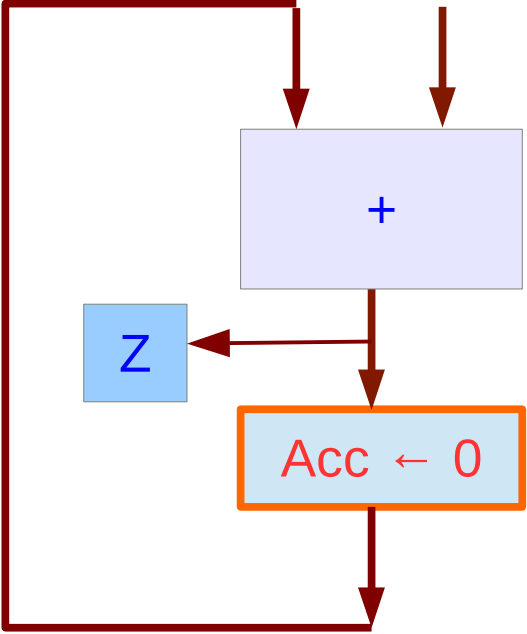

Based on <http://www.ele.uri.edu/Courses/ele306/f01/Tinydoc.pdf>

JNZ Operation

JNZ \$M ; PC ← M if Z=0

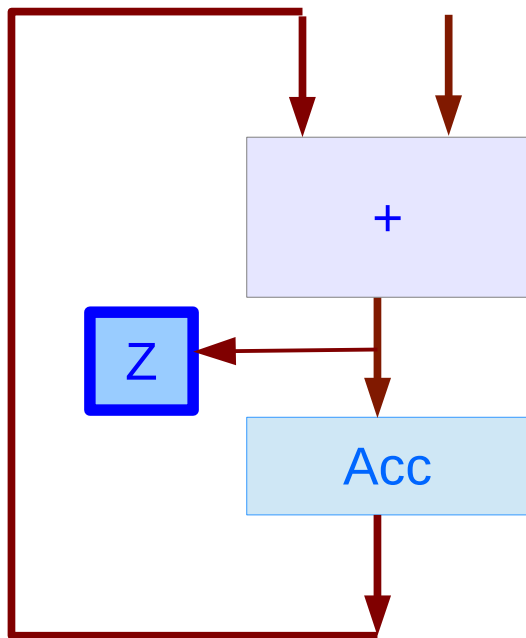


If ACC is **not** zero
flag Z=0

If ACC is **zero**
flag Z=1

New PC → M


PC → 101

New PC → inst

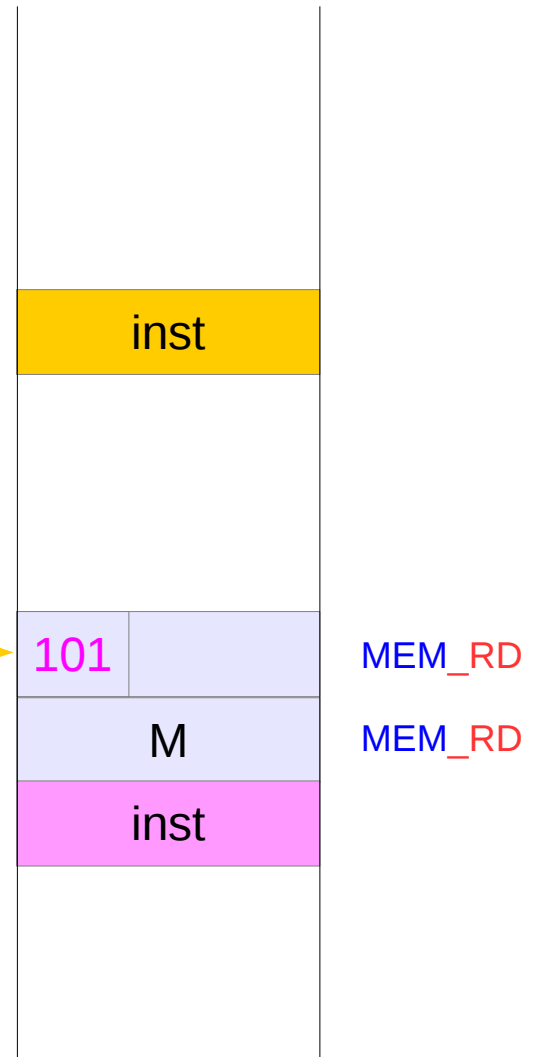

Based on <http://www.ele.uri.edu/Courses/ele306/f01/Tinydoc.pdf>

RST Operation

 


Based on <http://www.ele.uri.edu/Courses/ele306/f01/Tinydoc.pdf>

MEM Access in ADD Instruction

2 RD – Instruction

1 RD – Operand

 

```
ADD $M ; ACC ← ACC + [M]
```

	MAR	MDR
MEM_RD	PC	OPCode001 →
MEM_RD	PC' = PC+1	M →
MEM_RD	M	[M] →


Based on <http://www.ele.uri.edu/Courses/ele306/f01/Tinydoc.pdf>

MEM Access STR Instruction

2 RD – Instruction

1 WR – Operand


STR \$M ; [M] ← ACC

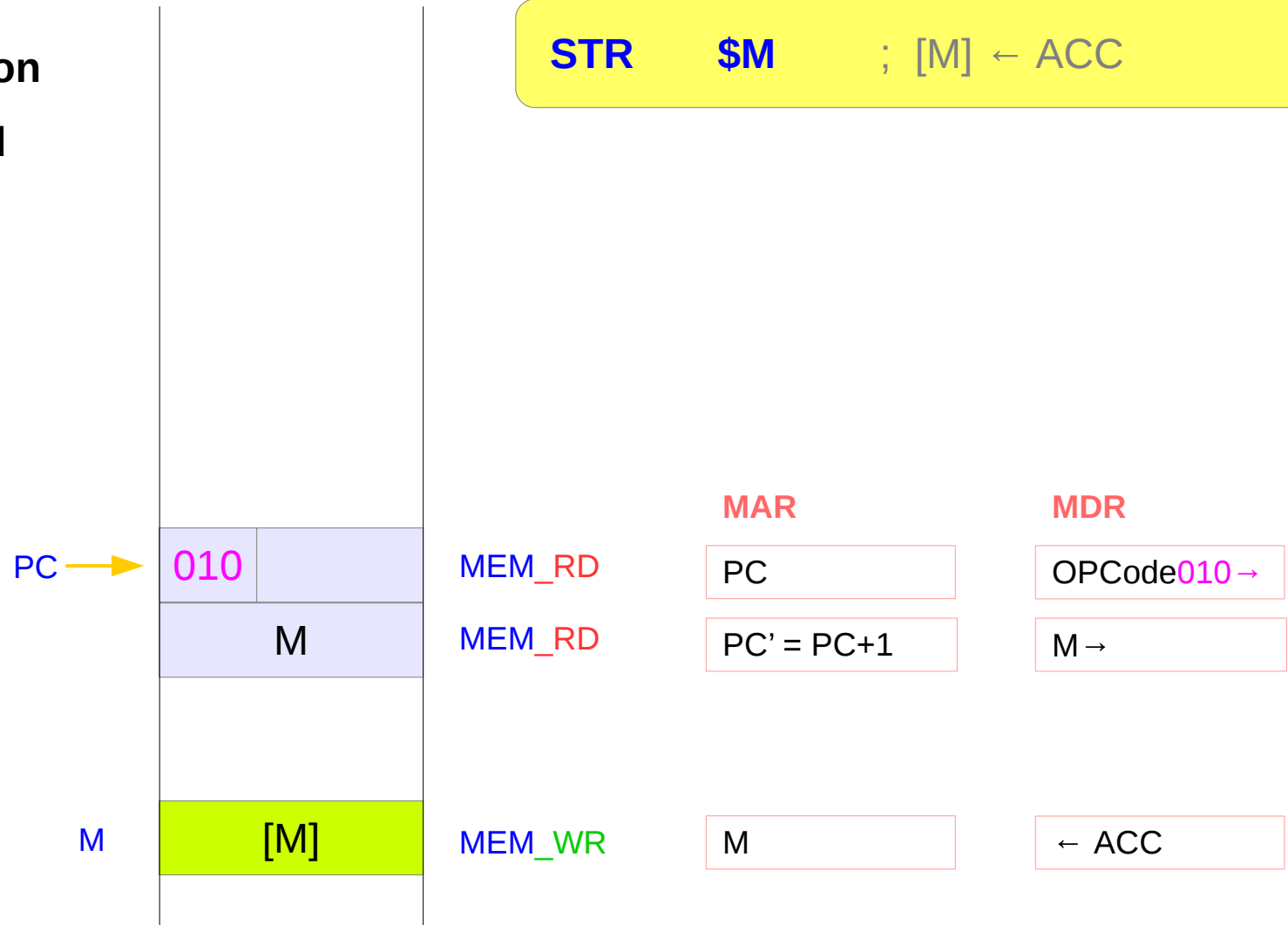

Based on <http://www.ele.uri.edu/Courses/ele306/f01/Tinydoc.pdf>

MEM Access CLA Instruction


1 RD – Instruction

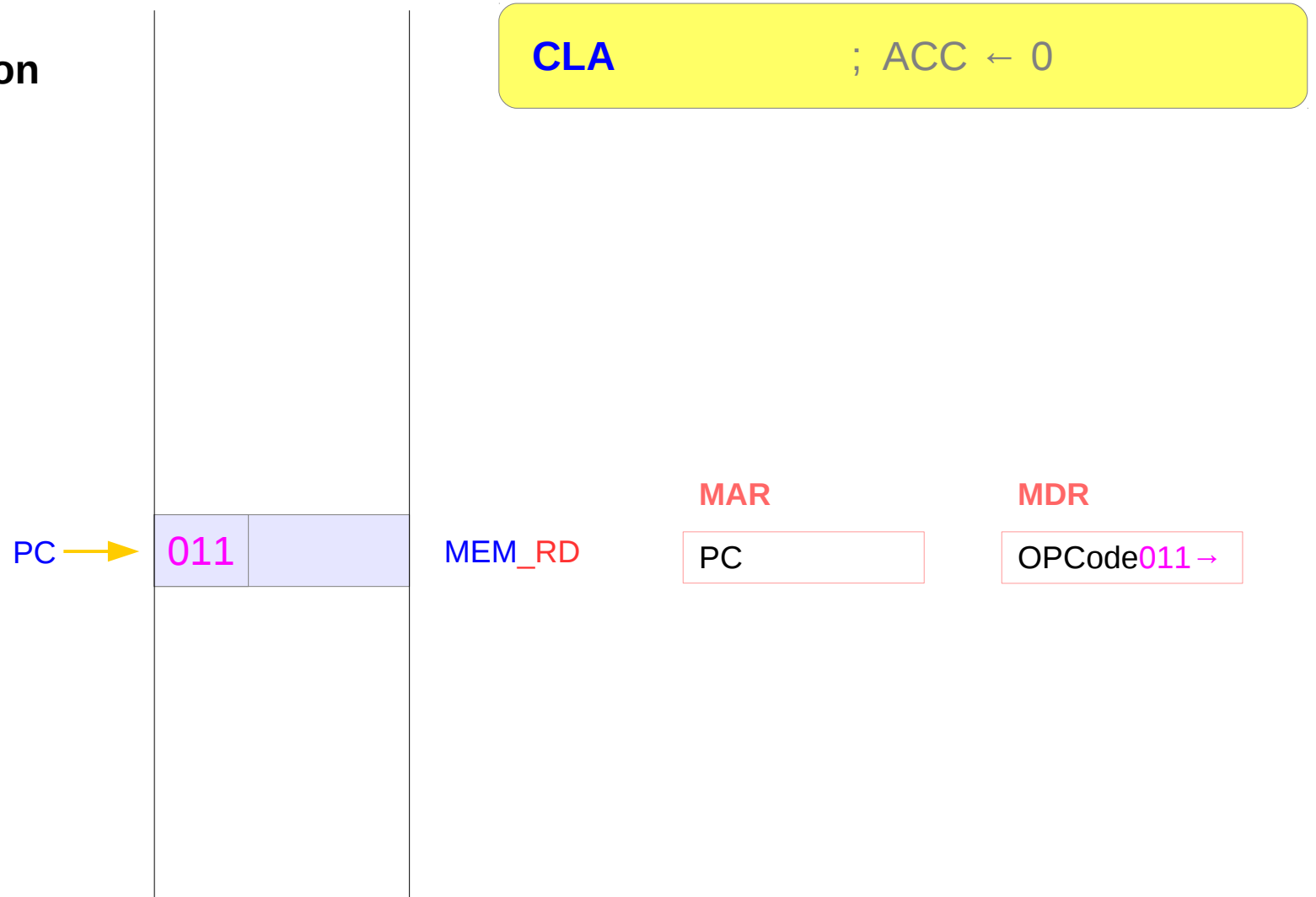


Based on <http://www.ele.uri.edu/Courses/ele306/f01/Tinydoc.pdf>

MEM Access JNZ Instruction

2 RD – Instruction

 


```
JNZ $M ; PC ← M if Z=0
```

 

Based on <http://www.ele.uri.edu/Courses/ele306/f01/Tinydoc.pdf>

MEM Access RST Instruction

1 RD – Instruction

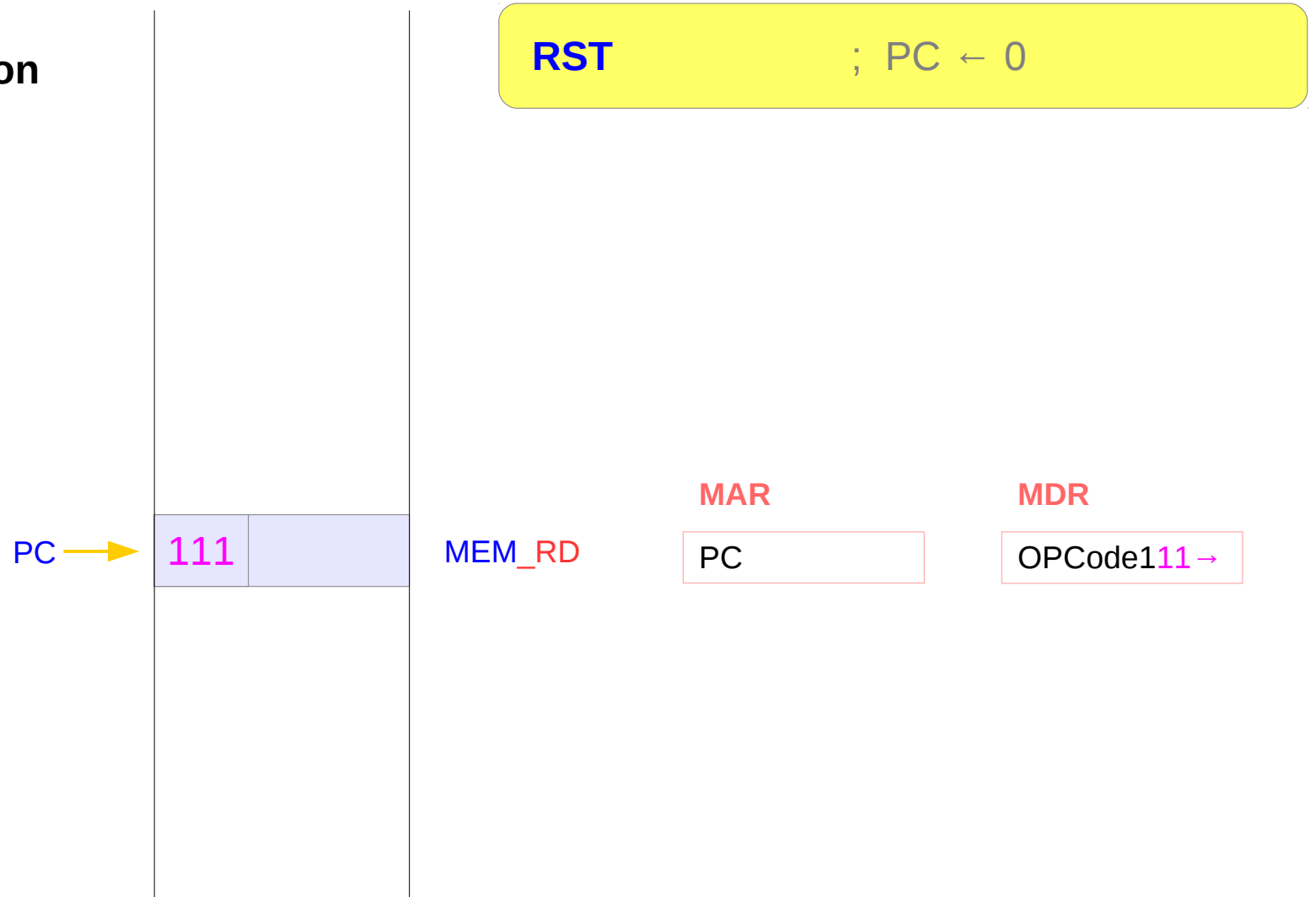

Based on <http://www.ele.uri.edu/Courses/ele306/f01/Tinydoc.pdf>

Addr. Machine Codes

00	60		CLA		;Clear Acc and then adding the operand is
01	20 78		ADD \$ONE		;equivalent to move the operand to Acc
03	40 FF		STR \$FF		
05	A0 01		JNZ \$01		
07	E0		RST		
78	01	ONE:	DAT	0000 0001	;Constant 1

00 → 01 → ... → FE → FF → 00

00	60
01	20
02	78
03	40
04	FF
05	A0
06	01
07	E0
78	01

FF	
----	--

References

- [1] <http://en.wikipedia.org/>
- [2] https://en.wikiversity.org/wiki/The_necessities_in_SOC_Design
- [3] https://en.wikiversity.org/wiki/The_necessities_in_Digital_Design
- [4] https://en.wikiversity.org/wiki/The_necessities_in_Computer_Design
- [5] https://en.wikiversity.org/wiki/The_necessities_in_Computer_Architecture
- [6] https://en.wikiversity.org/wiki/The_necessities_in_Computer_Organization
- [7] https://en.wikiversity.org/wiki/Understanding_Embedded_Software
- [8] Digital Systems, Hill, Peterson, 1987
- [9] <http://en.wikipedia.org/>
- [10] <http://www.ele.uri.edu/Courses/ele306/f01/Tinydoc.pdf>