
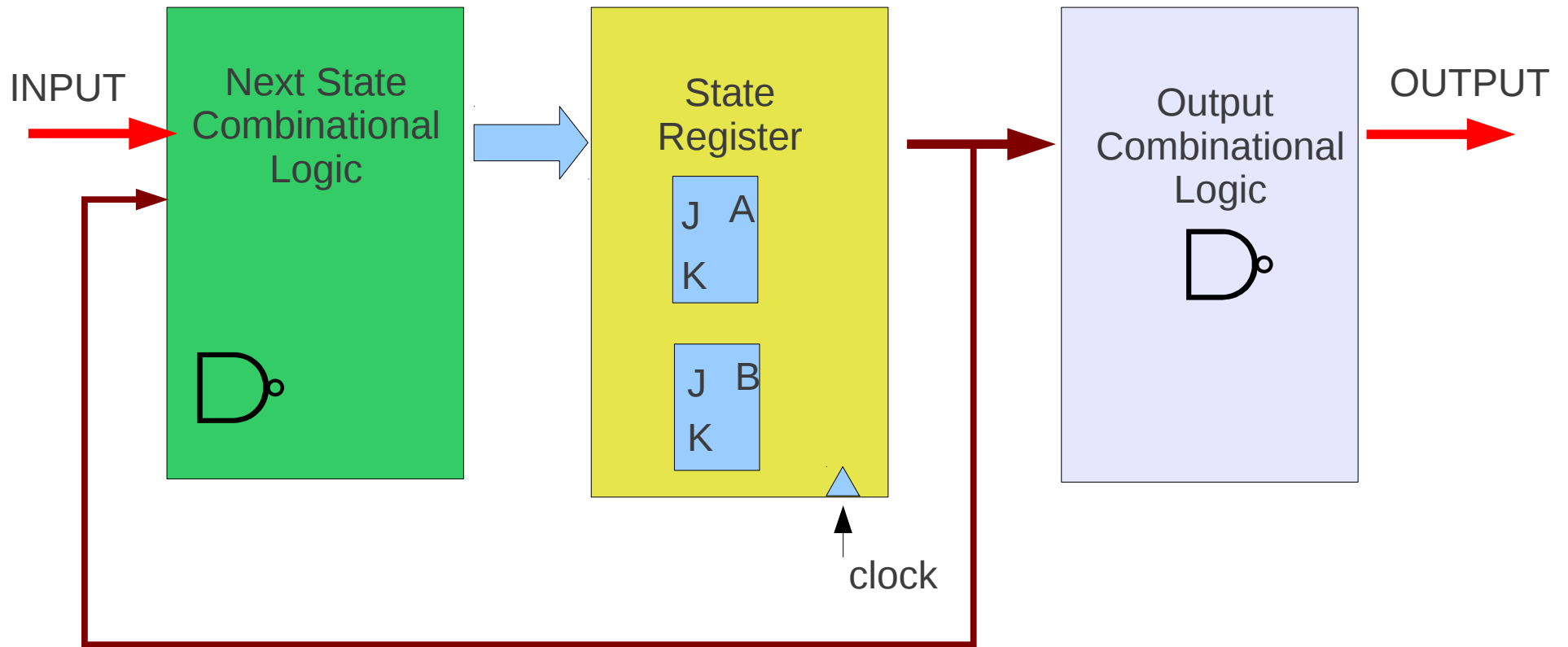



# Moore Machine

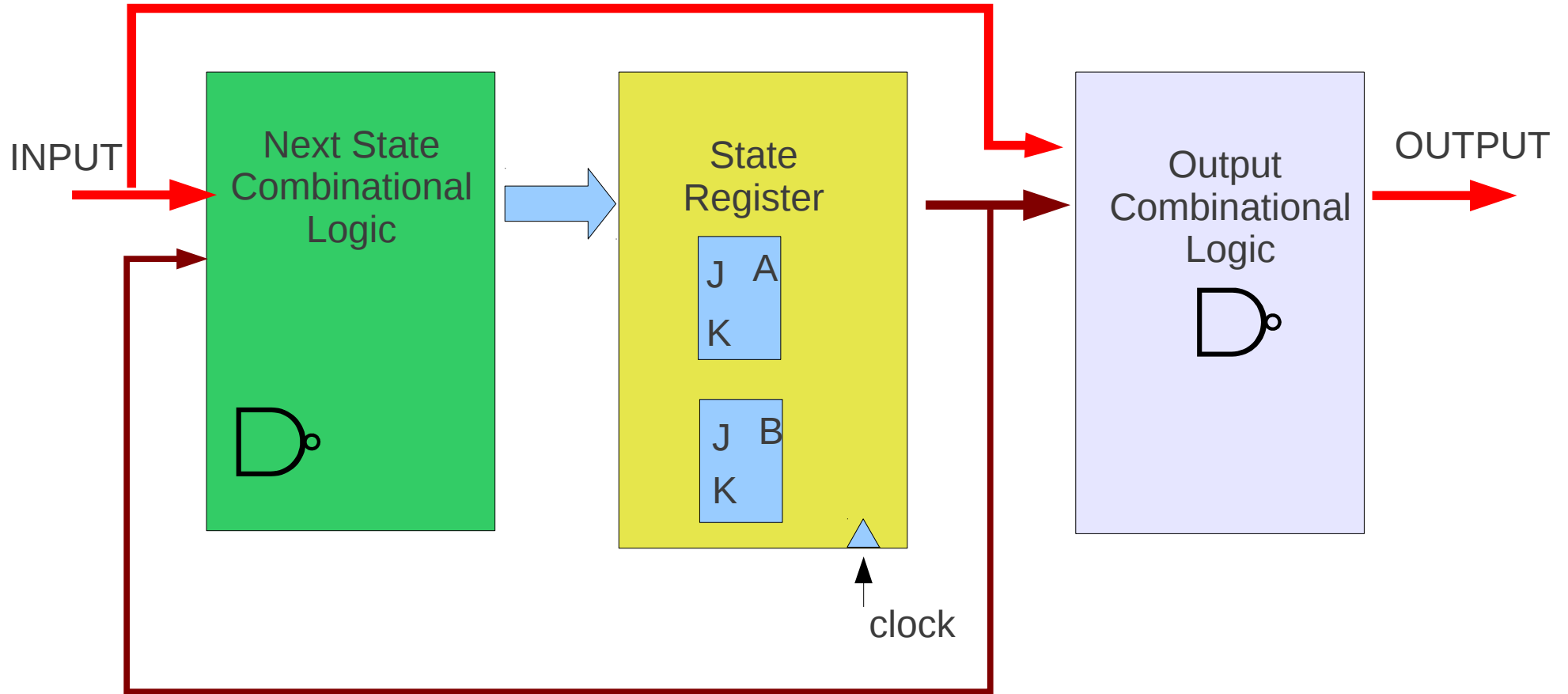

# Mealy Machine




# State Diagram

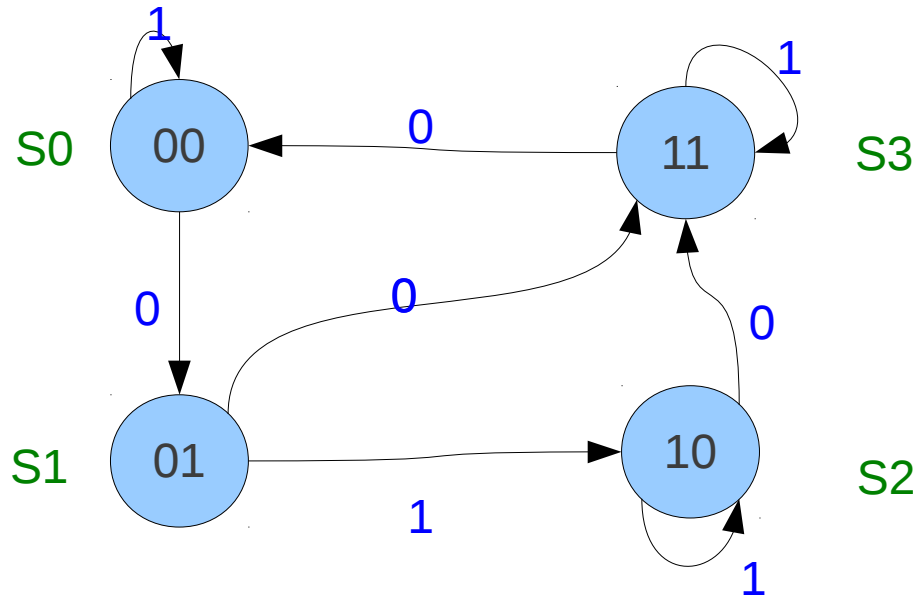

**State Table 5.4**

present State		input x	next State		FF Inputs			
A	B		A	B	JA	KA	JB	KB
0	0	0	0	1	0	0	1	0
0	0	1	0	0	0	0	0	1
0	1	0	1	1	1	1	1	0
0	1	1	1	0	1	0	0	1
1	0	0	1	1	0	0	1	1
1	0	1	1	0	0	0	0	0
1	1	0	0	0	1	1	1	1
1	1	1	1	1	1	0	0	0


# State Diagram

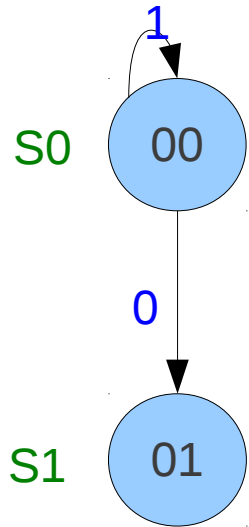

# State Table

present State		input x	next State		FF Inputs			
A	B		A	B	JA	KA	JB	KB
0	0	0	0	1	0	0	1	0
0	0	1	0	0	0	0	0	1
0	1	0	1	1	1	1	1	0
0	1	1	1	0	1	0	0	1
1	0	0	1	1	0	0	1	1
1	0	1	1	0	0	0	0	0
1	1	0	0	0	1	1	1	1
1	1	1	1	1	1	0	0	0


# State Diagram

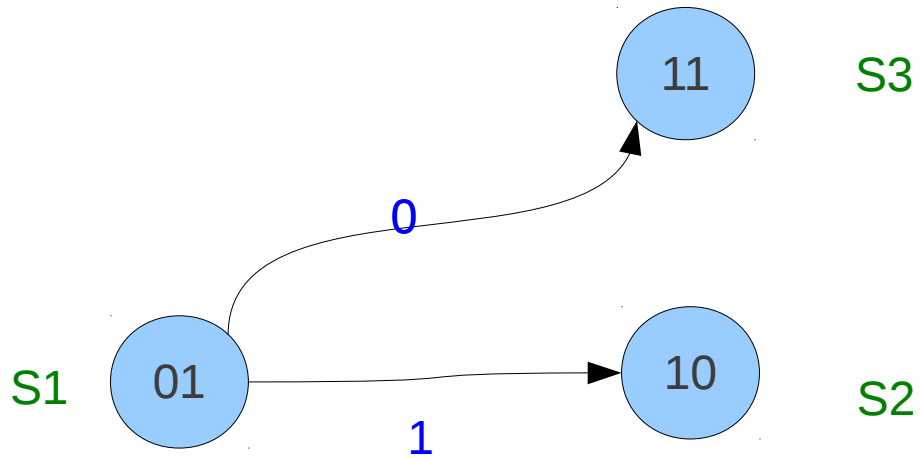

## State Table

present State		input x	next State		FF Inputs			
A	B		A	B	JA	KA	JB	KB
0	0	0	0	1	0	0	1	0
0	0	1	0	0	0	0	0	1
0	1	0	1	1	1	1	1	0
0	1	1	1	0	1	0	0	1
1	0	0	1	1	0	0	1	1
1	0	1	1	0	0	0	0	0
1	1	0	0	0	1	1	1	1
1	1	1	1	1	1	0	0	0

# State Diagram

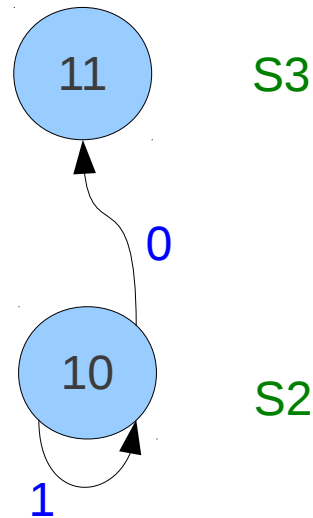


## State Table

present State		input x	next State		FF Inputs			
A	B		A	B	JA	KA	JB	KB
0	0	0	0	1	0	0	1	0
0	0	1	0	0	0	0	0	1
0	1	0	1	1	1	1	1	0
0	1	1	1	0	1	0	0	1
1	0	0	1	1	0	0	1	1
1	0	1	1	0	0	0	0	0
1	1	0	0	0	1	1	1	1
1	1	1	1	1	1	0	0	0




# State Diagram

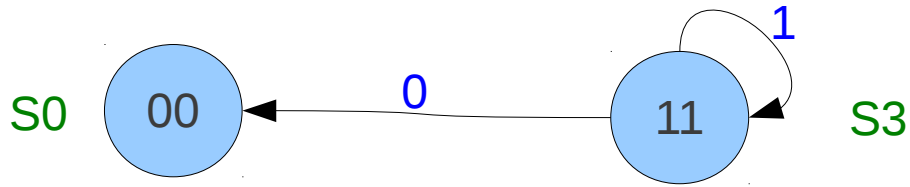

## State Table 5.4

present State		input x	next State		FF Inputs			
A	B		A	B	JA	KA	JB	KB
0	0	0	0	1	0	0	1	0
0	0	1	0	0	0	0	0	1
0	1	0	1	1	1	1	1	0
0	1	1	1	0	1	0	0	1
1	0	0	1	1	0	0	1	1
1	0	1	1	0	0	0	0	0
1	1	0	0	0	1	1	1	1
1	1	1	1	1	1	0	0	0

# Moore Machine

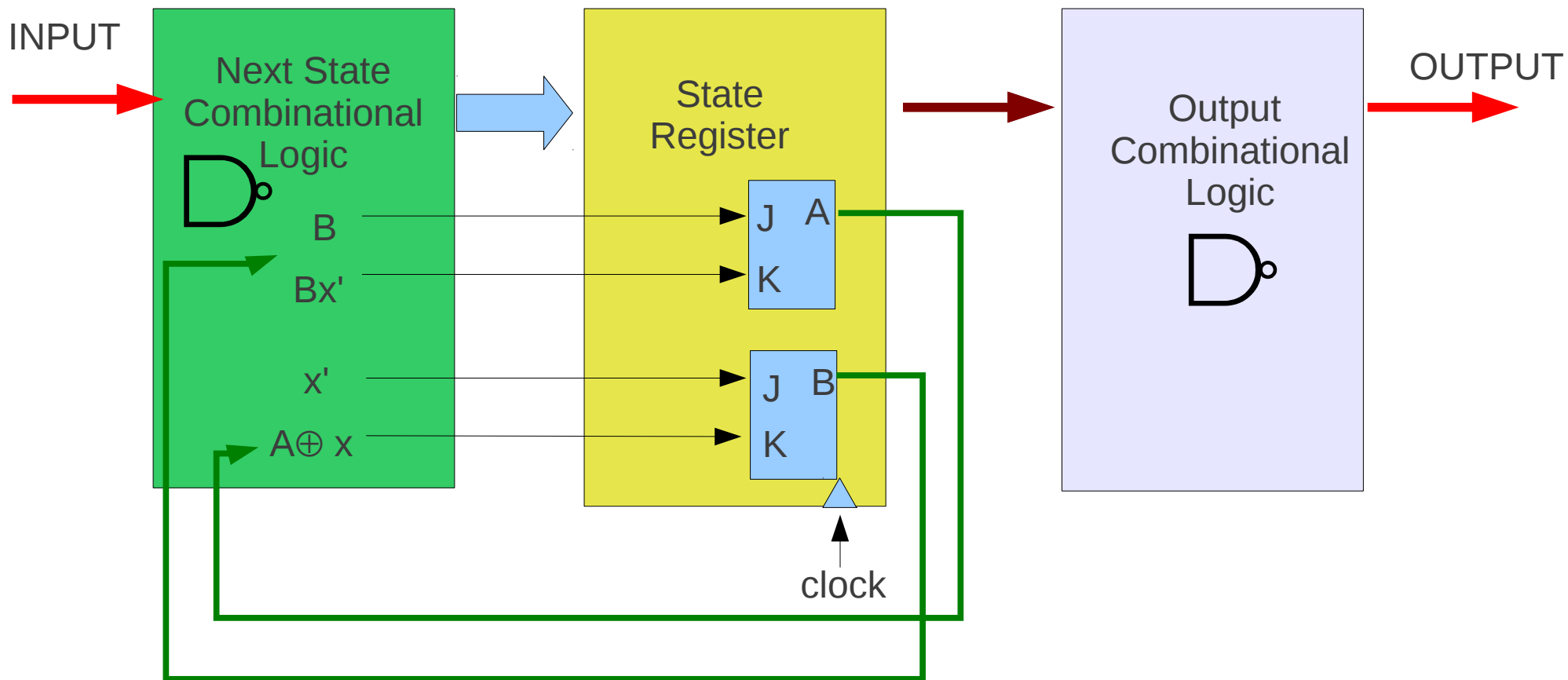



# Characteristic Equations

$$Q(t+1) = D$$

**D** FlipFlop


$$Q(t+1) = JQ' + K'Q$$

**JK** FlipFlop

$$Q(t+1) = T Q = TQ' + T'Q$$


**T** FlipFlop

## State Diagram in Fig 5.27

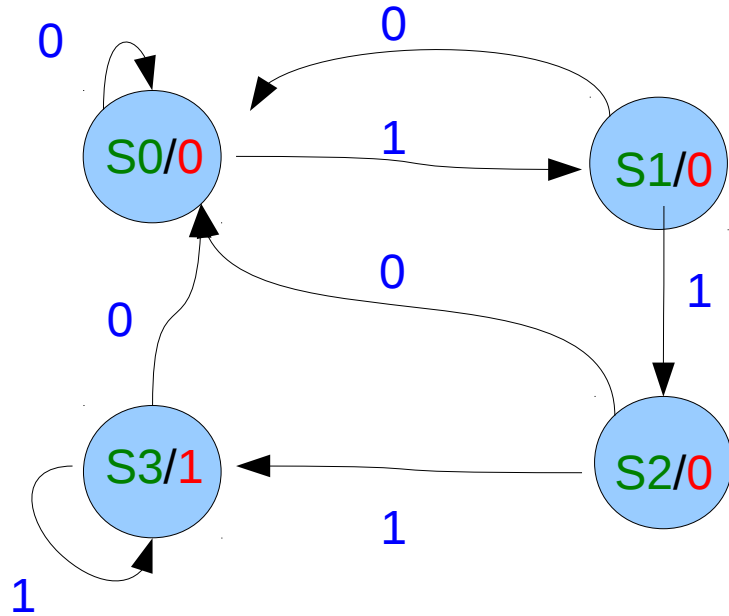

## State Table 5.11


present State		input	next State		FF Inputs				Output
A	B		A	B	JA	KA	JB	KB	
0	0	0	0	0					0
0	0	1	0	1					0
0	1	0	0	0					0
0	1	1	1	0					0
1	0	0	0	0					0
1	0	1	1	1					0
1	1	0	0	0					1
1	1	1	1	1					1

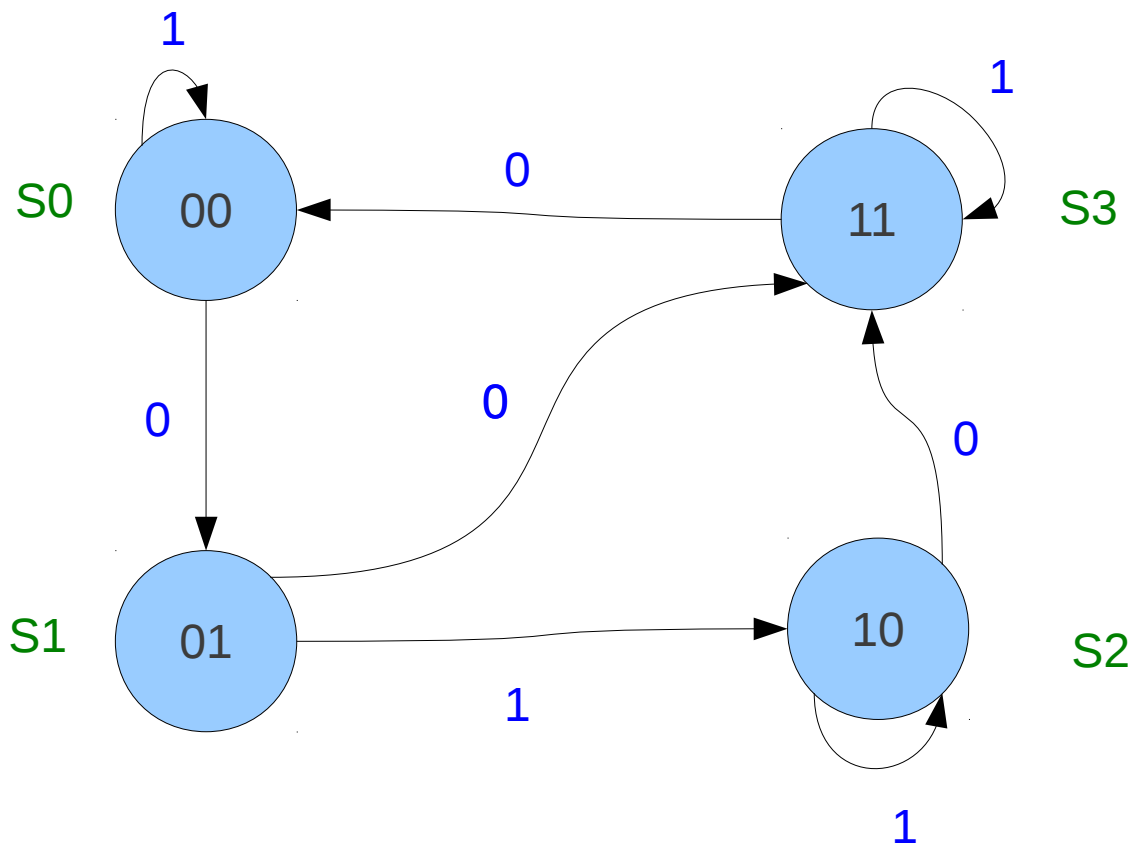

J	A
K	

J	B
K	

# State Diagram in Fig 5.20

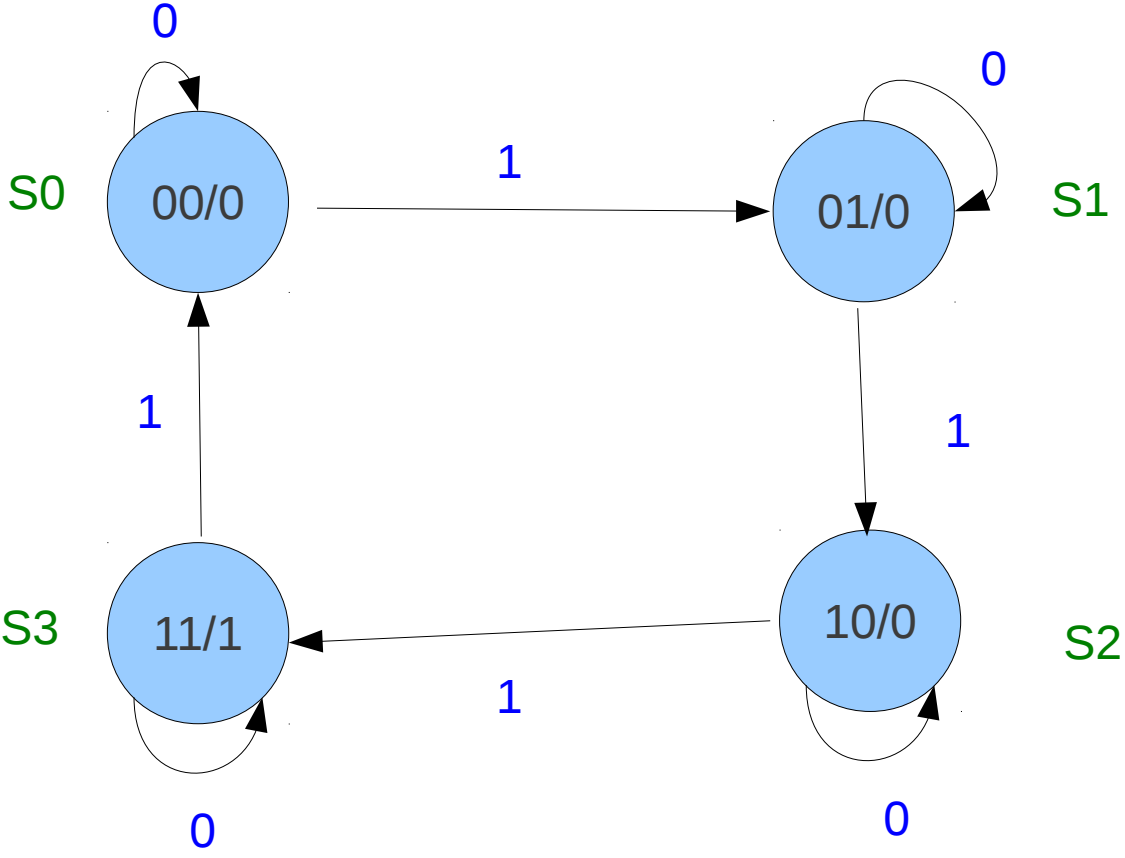

J	A
K	

J	B
K	

## State Diagram from Table 5.13

