

# BJT Overview Amplifiers (H.2)

20170114

Copyright (c) 2016 - 2017 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".


# References

Based

[1] Floyd, Electronic Devices 7th ed

[2] Cook,

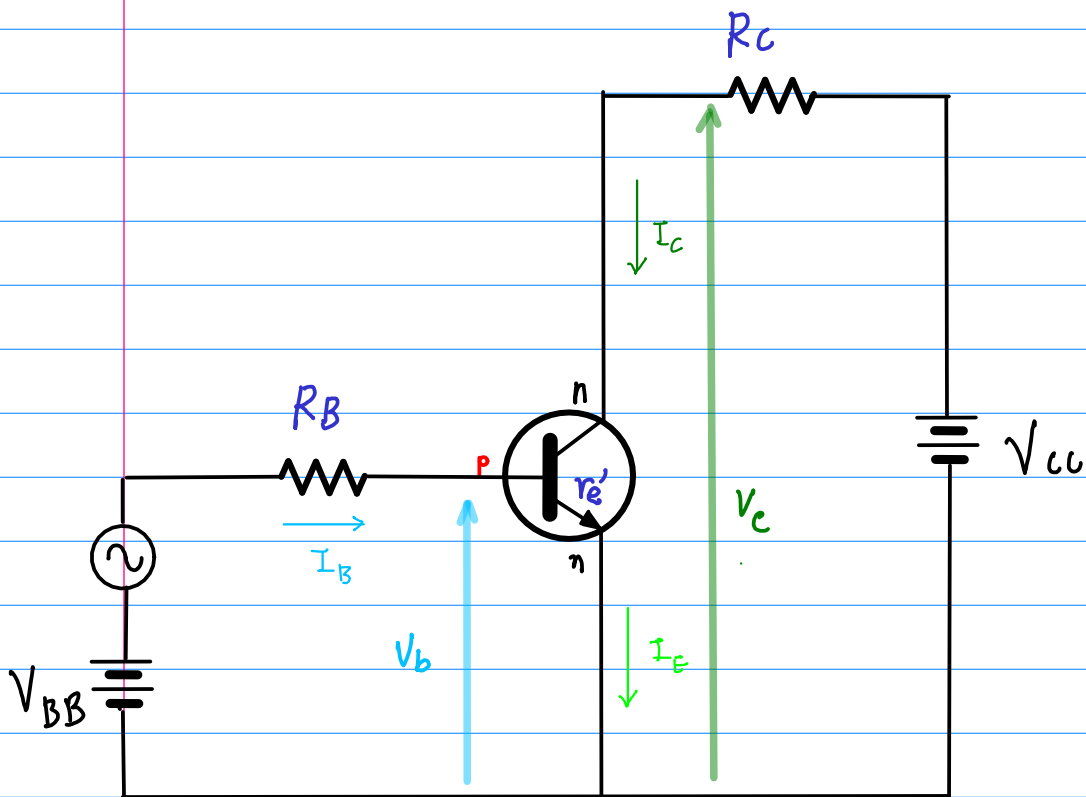[2] [en.wikipedia.org](http://en.wikipedia.org)



$$I_e \approx I_c = \frac{V_b}{r_e'}$$

$$V_c = I_c R_C \approx V_e$$

$$V_b = V_{in} - I_b R_B$$

$$A_v = \frac{V_c}{V_b} \approx \frac{I_e R_C}{I_e r_e'} = \frac{R_C}{r_e'}$$