

Carry Chain Adder (6A)

-
-

Copyright (c) 2021 -- 2010 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".

Please send corrections (or suggestions) to youngwlim@hotmail.com.

This document was produced by using OpenOffice and Octave.

Manchester Carry Chain


the output node $\overline{q(i+1)}$ is precharged,
when the synchronization signal is equal to 0 ($ck=0$),

$p(i)$	0	1
0	0	1
1	1	0

$g(i)$	0	1
0	0	0
1	0	1

when $ck=1$, the output node is discharged
if either $p(i)=1$ and the preceding node $\overline{q(i)}$
has been discharged, or
if $g(i)=1$.

 
In order that it works properly
 $g(i)$ and $p(i)$ should not be equal to 1 simultaneously
so that the definition of $g(i)$ cannot be relaxed
as in the preceding case



Manchester Carry Chain

Synthesis of Arithmetic Circuits: FPGA, ASIC and Ebedded Systems, J-P Deschamps et al


Carry section of FA

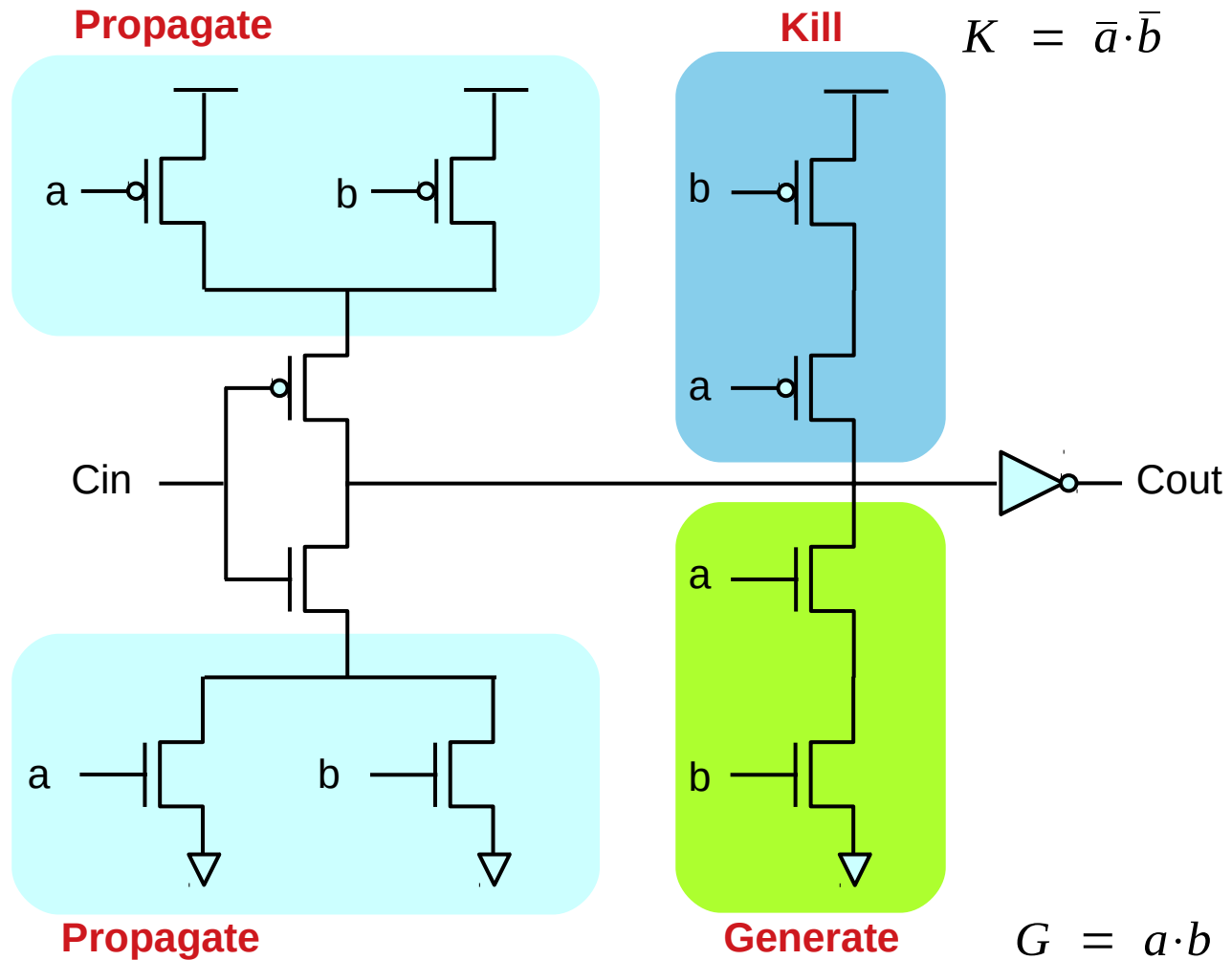

Digital Electronics and Design with VHDL, V, A < Pedroni


Static Carry Circuit
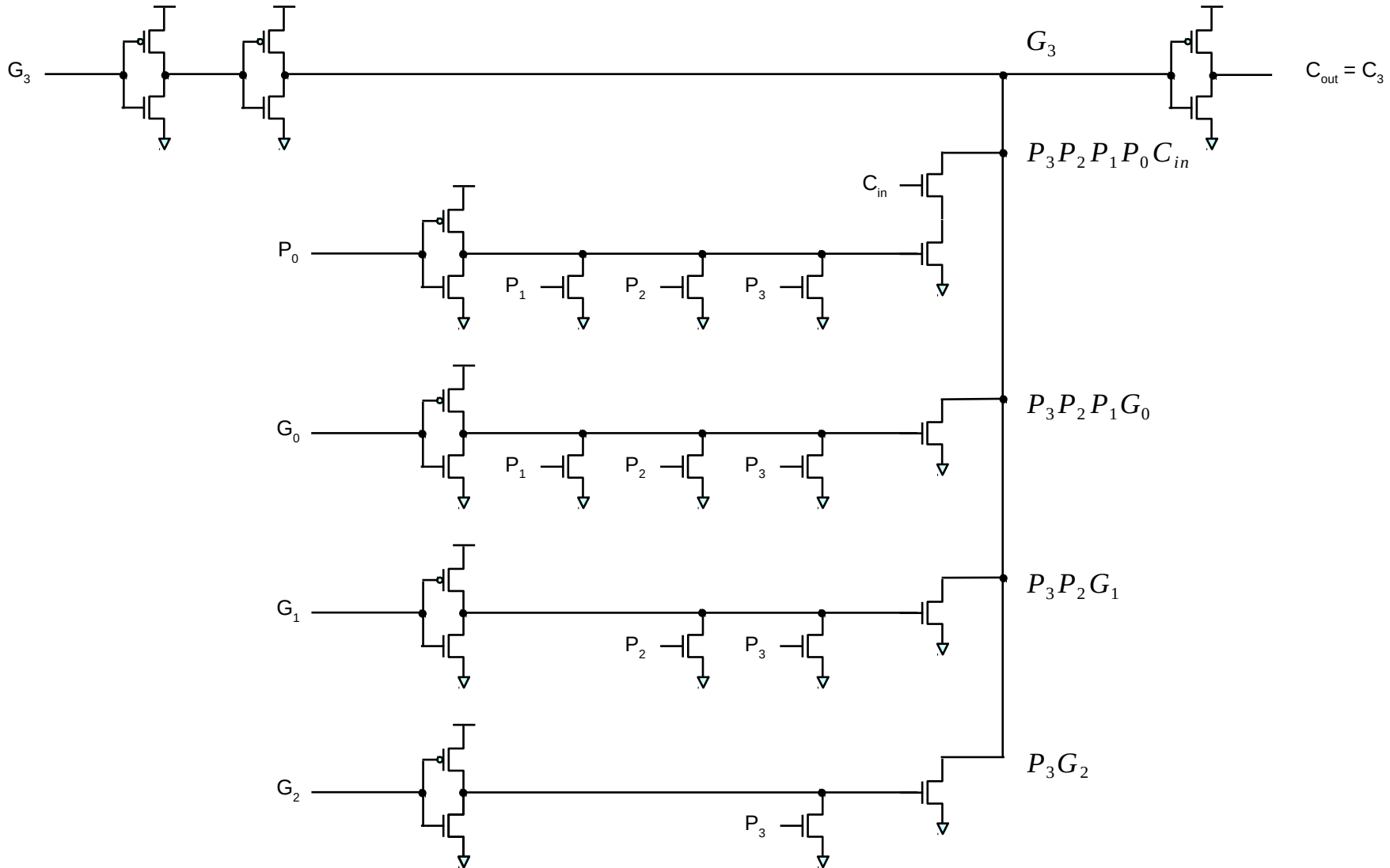
$$G_3 + P_3G_2 + P_3P_2G_1 + P_3P_2P_1G_0 + P_3P_2P_1P_0c_{in} = c_3$$



Principles of CMOS VLSI design – A Systems Perspective, N Weste, K Eshraghian

Static Carry Circuit - using G, P

 



P cannot be relaxed

$$P = a \oplus b$$

$$G = a \cdot b$$


~~$$P = a + b$$~~

Static Carry Circuit - using G, P

  


$$P = a \oplus b$$

$$G = a \cdot b$$

 

Digital Electronics and Design with VHDL, V, A < Pedroni

Static Carry Circuit - using G, P, K

 


$$P = a \oplus b$$


$$G = a \cdot b$$

$$K = \bar{a} \cdot \bar{b}$$


Static Carry Circuit - using G, P, K

 

$$P = a \oplus b$$


 


$$G = a \cdot b$$

 





$$K = \bar{a} \cdot \bar{b}$$

Static Carry Circuit - using Multiplexer

  



Digital Electronics and Design with VHDL, V, A < Pedroni

Static Carry Circuit - using Multiplexer

    



Digital Electronics and Design with VHDL, V, A < Pedroni

  Static Carry Circuit - using multiplexers



Digital Electronics and Design with VHDL, V, A < Pedroni

  Static Carry Circuit - using multiplexers




Principles of CMOS VLSI design – A Systems Perspective, N Weste, K Eshraghian

Static Carry Circuit – using multiplexers

A multiplexer-based 4-bit adder

cascading four such stages
supplying P_i, G_i

 This is commonly called
a **Manchester carry adder**




not Manchester carry chain adder

There is some similarity with the domino carry circuit (nMos)
Manchester carry chain adder

However, the intermediate carry gates are no longer needed, (G_i, P_i)
Because the carry values are available in a distributed fashion

Principles of CMOS VLSI design – A Systems Perspective, N Weste, K Eshraghian

Static Carry Circuit - using multiplexers

 

The 4-bit adder is chosen to reduce the number of series-propagate transistors Which improves the speed

Note that if all propagate signals are true, and CI is high , six series n-transistors Pull the output node lo in the case of the dynamic gate While five transistors re in series in the static gate

Principles of CMOS VLSI design – A Systems Perspective, N Weste, K Eshraghian

Manchester Carry Chain – Dynamic Logic

However, not all logic families have these **internal nodes**, CMOS being a major example.


Dynamic logic can support shared logic,
as can transmission gate logic.

One of the major downsides of the Manchester carry chain is that the **capacitive load** of all of these outputs, together with the resistance of the transistors causes the **propagation delay** to increase much *more quickly* than a regular carry lookahead.

A Manchester-carry-chain section generally doesn't exceed 4 bits.

https://en.wikipedia.org/wiki/Carry-lookahead_adder


Dynamic Carry Circuit – using G, P

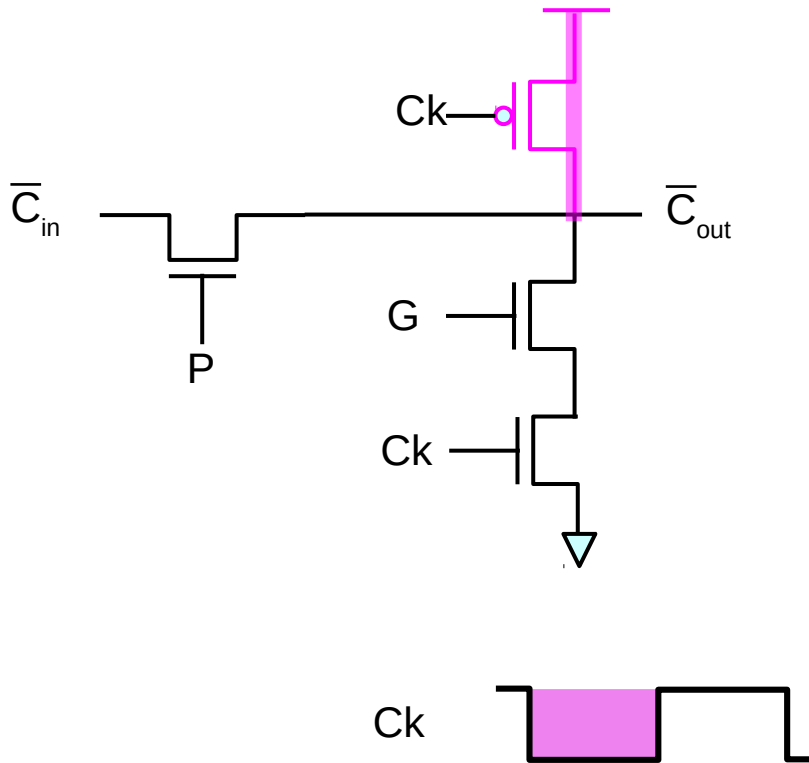

When **CLK** is **low**, the output node is precharged by the **pull-up** transistor

Principles of CMOS VLSI design – A Systems Perspective, N Weste, K Eshraghian

Dynamic Carry Circuit – using G, P

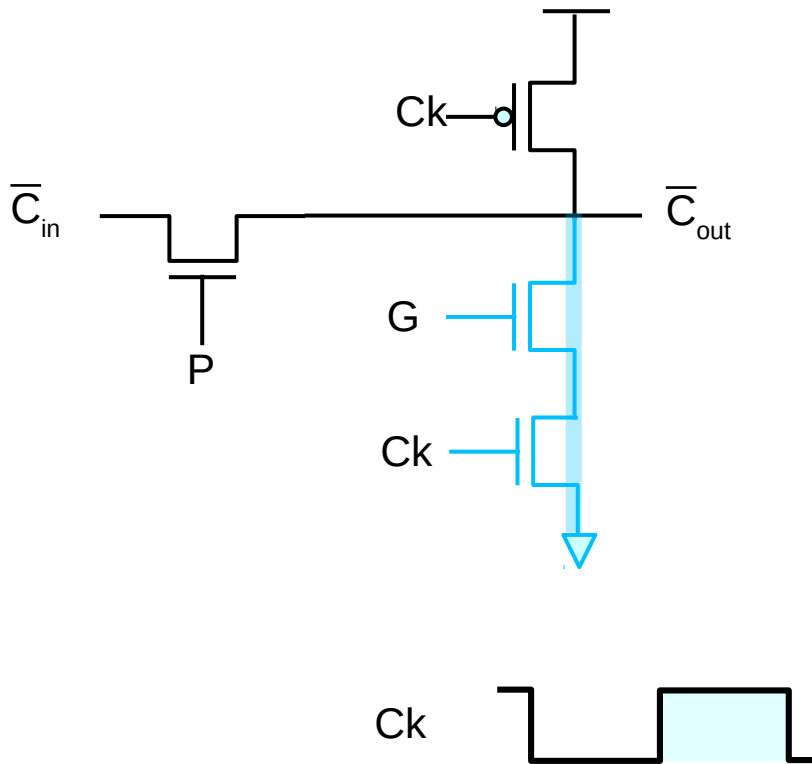


When **CLK** goes **high**,
the n **pull-down** transistor turns on
If carry generate **G=AB** is **true**,
then the output node **discharge**

$$c_i = G_i + P_i c_{i-1}$$

Principles of CMOS VLSI design – A Systems Perspective, N Weste, K Eshraghian

Dynamic Carry Circuit – using G, P

 

When **CLK** goes **high**,
the n **pull-down** transistor turns on
If carry propagate **P=A+B** is **true**,
then a **previous carry** may be coupled
to the output node,
conditionally discharging it


Note that in this circuit CARRY is actually propagated




$$c_i = G_i + P_i c_{i-1}$$

Dynamic Carry Circuit – using G, P

$$c_i = G_i + P_i c_{i-1}$$

 

$$c_i = G_i + P_i c_{i-1}$$

 


This requires P must not be relaxed

$$P = a \oplus b$$


$p(i)$	0	1
0	0	1
1	1	0

$g(i)$	0	1
0	0	0
1	0	1

Dynamic Manchester Carry-Chain Adder

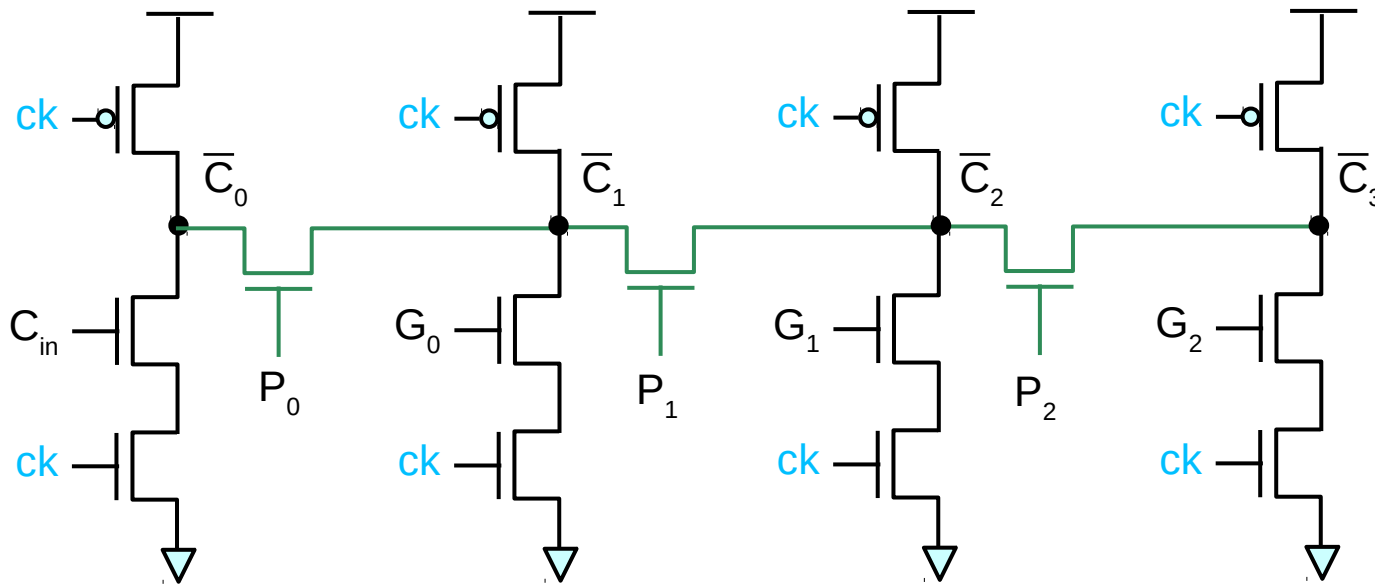


Other representation I

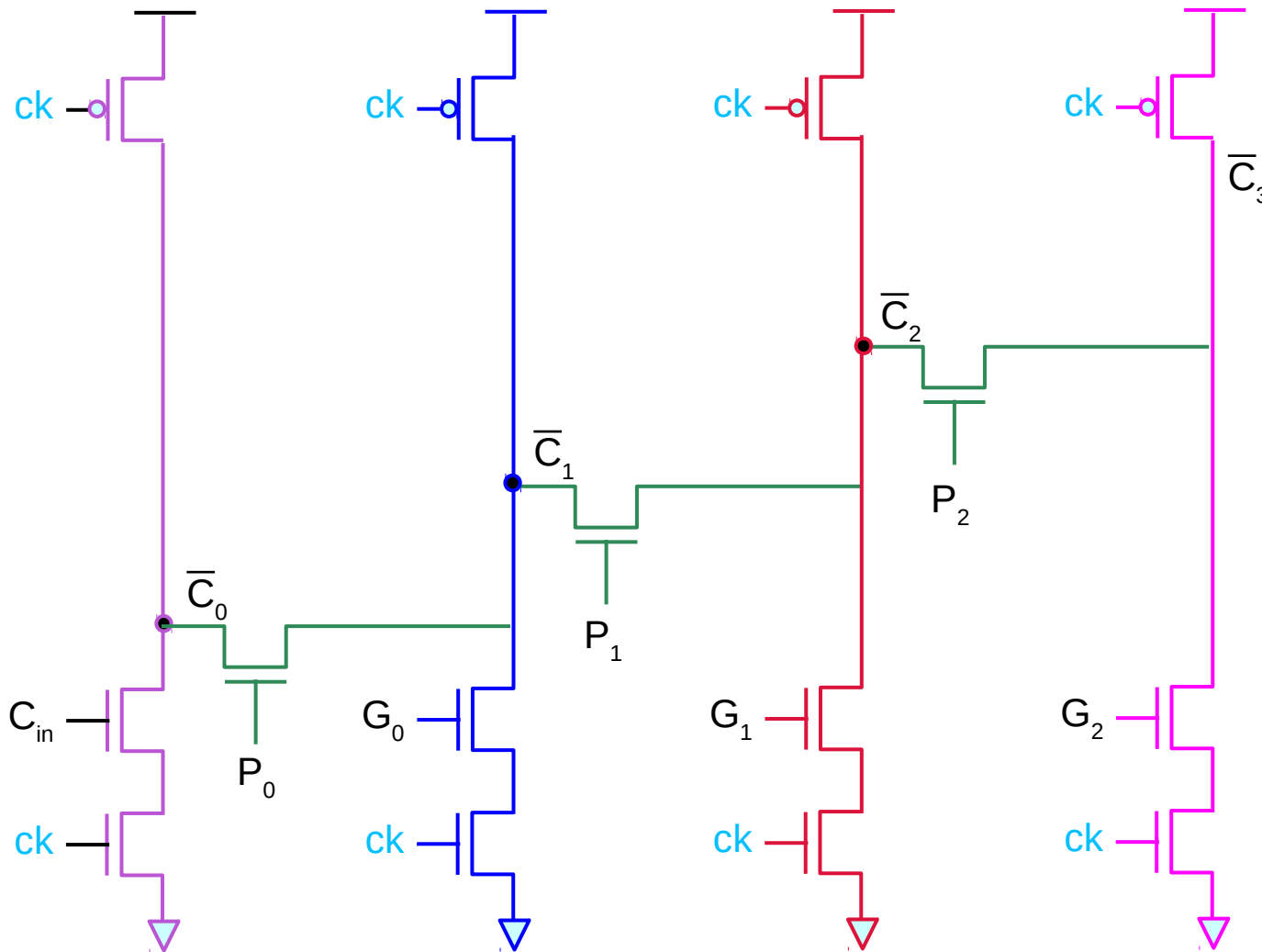


Digital Electronics and Design with VHDL, V, A < Pedroni

Other representation II

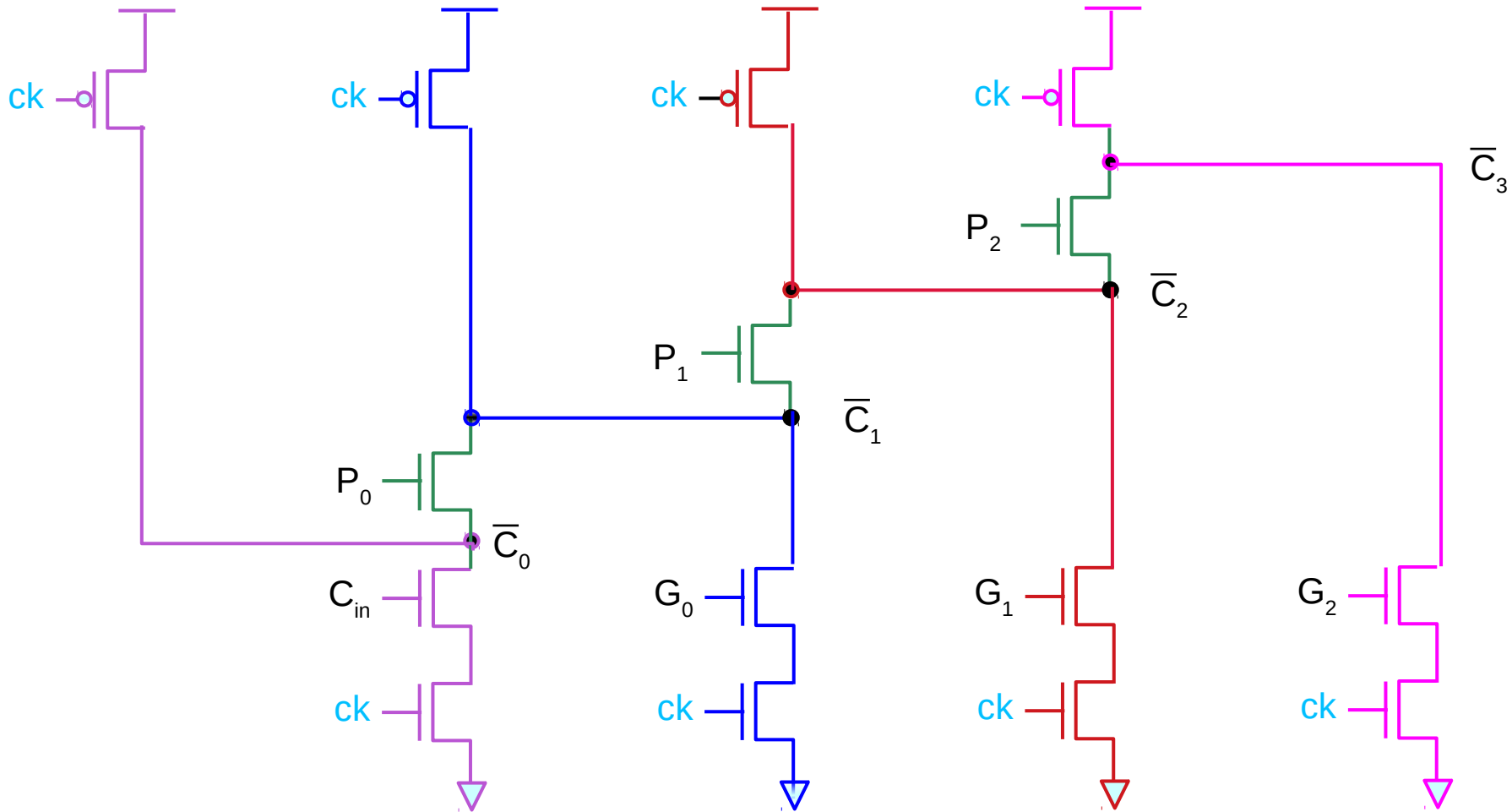

Digital Electronics and Design with VHDL, V. A. Pedroni


Dynamic Carry Circuit - C_0

 

$$c_0 = G_0 + P_0 c_{in}$$


$$c_{out} = P c_i + G$$

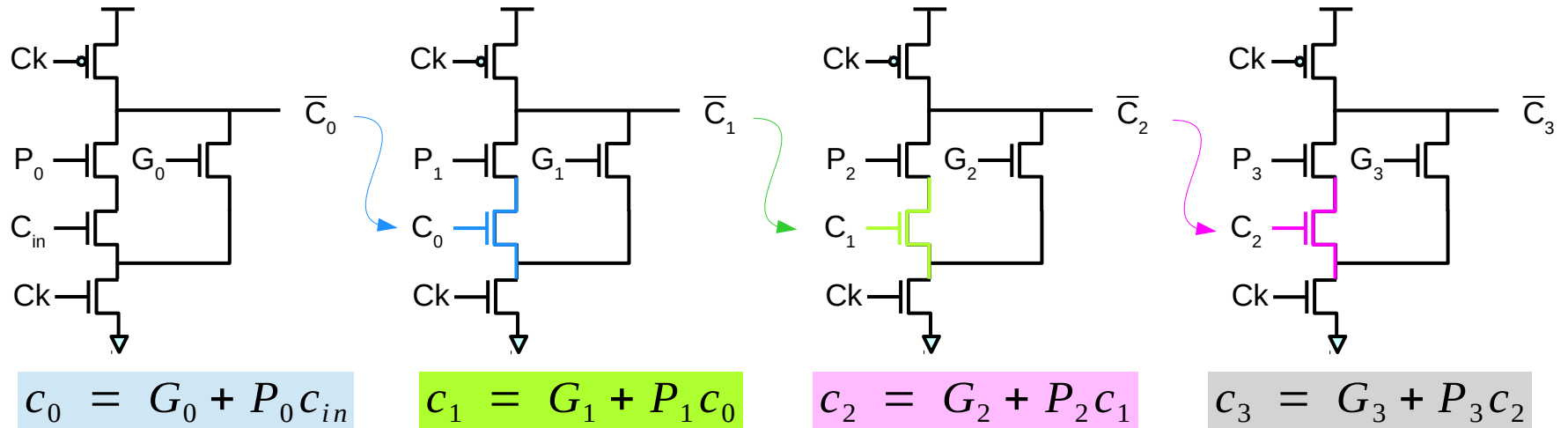Dynamic Carry Circuit - C_0, C_1, C_2, C_3




Principles of CMOS VLSI design – A Systems Perspective, N Weste, K Eshraghian

Dynamic Carry Circuit - C_1

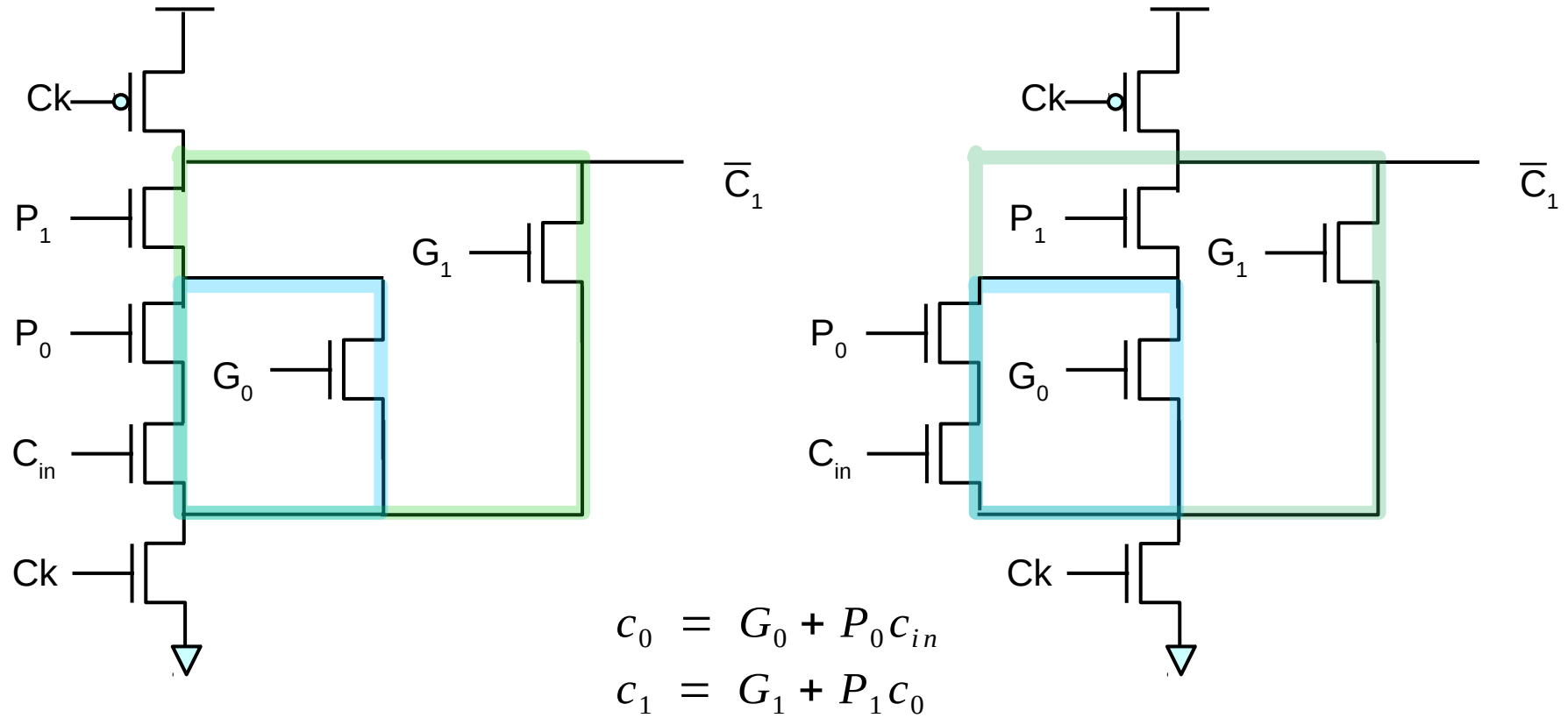

Principles of CMOS VLSI design – A Systems Perspective, N Weste, K Eshraghian

Dynamic Carry Circuit - C₂ (1)

 


$$c_0 = G_0 + P_0 c_{in}$$

$$c_1 = G_1 + P_1 c_0$$

$$c_2 = G_2 + P_2 c_1$$

Principles of CMOS VLSI design – A Systems Perspective, N Weste, K Eshraghian

Dynamic Carry Circuit - C₂ (2)

 


$$c_0 = G_0 + P_0 c_{in}$$

$$c_1 = G_1 + P_1 c_0$$

$$c_2 = G_2 + P_2 c_1$$

Principles of CMOS VLSI design – A Systems Perspective, N Weste, K Eshraghian

Dynamic Carry Circuit - C_3 (1)

 

$$c_0 = G_0 + P_0 c_{in}$$


$$c_1 = G_1 + P_1 c_0$$

$$c_2 = G_2 + P_2 c_1$$

$$c_3 = G_3 + P_3 c_2$$

Principles of CMOS VLSI design – A Systems Perspective, N Weste, K Eshraghian

Dynamic Carry Circuit - C_3 (2)

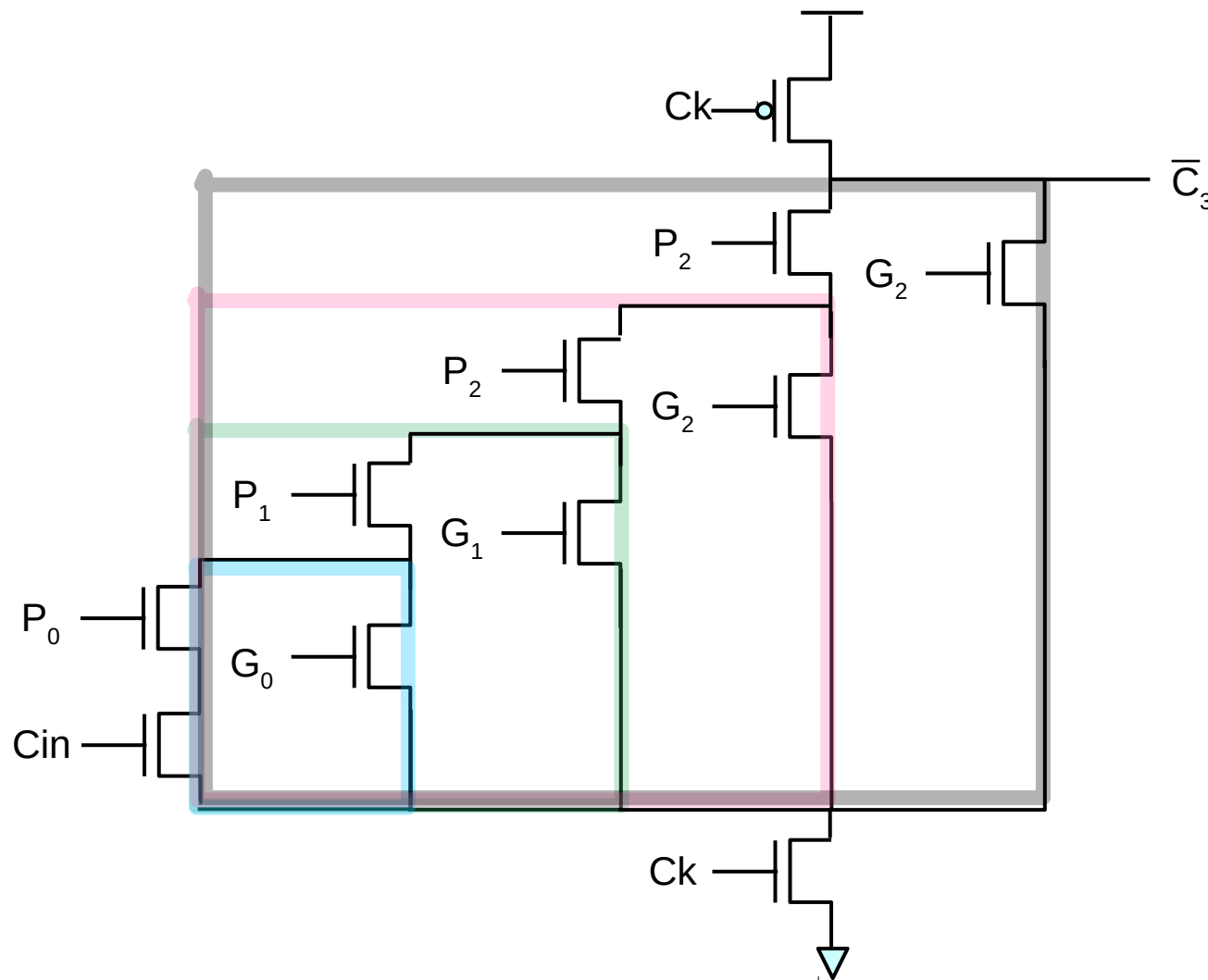

$$c_0 = G_0 + P_0 c_{in}$$


$$c_1 = G_1 + P_1 c_0$$

$$c_2 = G_2 + P_2 c_1$$


$$c_3 = G_3 + P_3 c_2$$

Principles of CMOS VLSI design – A Systems Perspective, N Weste, K Eshraghian


Dynamic Carry Circuit - C_3 (3)

 


$$c_0 = G_0 + P_0 c_{in}$$

 


$$c_1 = G_1 + P_1 c_0$$

 

$$c_2 = G_2 + P_2 c_1$$

 

$$c_3 = G_3 + P_3 c_2$$

 

Principles of CMOS VLSI design – A Systems Perspective, N Weste, K Eshraghian

References

[1] <http://en.wikipedia.org/>

[2] J-P Deschamps, et. al., “Sunthesis of Arithmetic Circuits”, 2006